
 


# NAND & NOR Implementation (Two-Level Implementation)




(a) AND-Invert

 

(b) Invert-OR



Eg 1  $F = AB + CD$

   

Eg 2 Implement the following Boolean function with NAND gates.

$$F(x, y, z) = (1, 2, 3, 4, 5, 7)$$



\* Use K-map and simplify the function into Sum-of-Product form.

		yz			
		00	01	11	10
x	0		1	1	1
	1	1	1	1	

Annotations:   
 - A group of three 1s in the top row (x=0) is labeled  $\overline{x}y$ .   
 - A group of three 1s in the bottom row (x=1) is labeled  $x\overline{y}$ .   
 - A group of two 1s in the middle column (y=1) is labeled  $z$ .

$$F = \overline{x}y + x\overline{y} + z$$

$$F = x\bar{y} + \bar{x}y + z$$

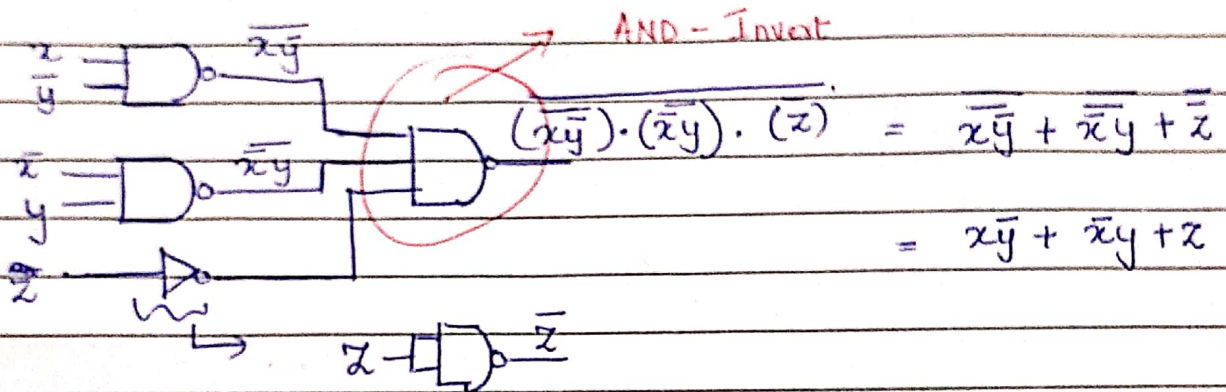 


Eg 3 : Implement the function  $F = \bar{w}\bar{x} + \bar{x}\bar{z}$  using only NAND gates.

$$F = \bar{w}\bar{x} + \bar{x}\bar{z}$$

Taking double complement on both sides.
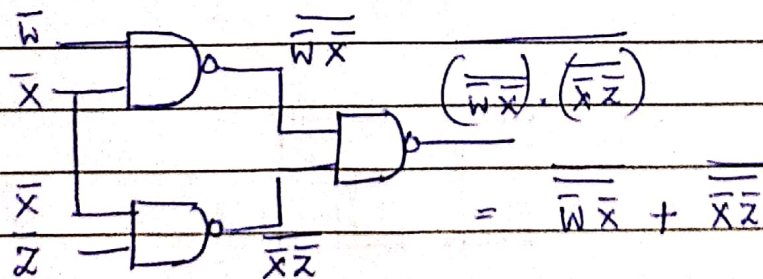
$$\begin{aligned} \overline{\overline{F}} &= \overline{\overline{\bar{w}\bar{x} + \bar{x}\bar{z}}} \\ &= (\overline{\bar{w}\bar{x}}) \cdot (\overline{\bar{x}\bar{z}}) \end{aligned}$$



$$F = \bar{w}\bar{x} + \bar{x}\bar{z}$$




DATE

## Multi level NAND Circuits


Eg: 1  $F = A(CD + B) + B\bar{C}$

{ AND - OR Implementation

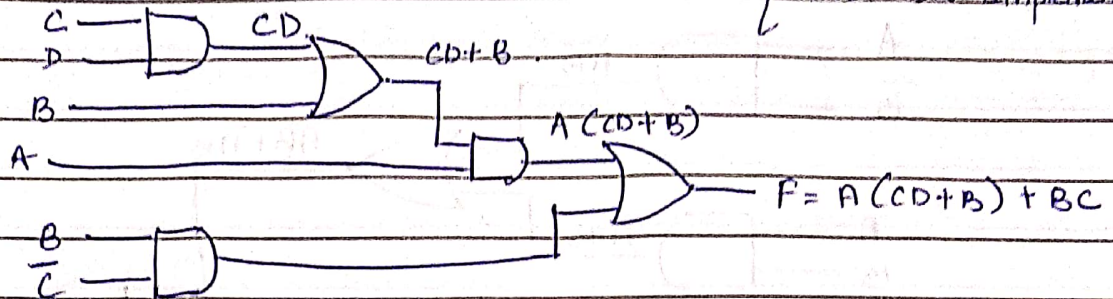

\* Procedure to convert AND-OR diagram into an NAND diagram is as follows-

 1. Convert all AND gates to NAND gates with AND-invert graphic symbols.
2. Convert all OR gates to NAND gates with invert-OR graphic symbols.
3. Check all the bubbles in the diagram. For every bubble that is not compensated by another small circle along the same line, insert an inverter.






DATE


(4)

Eq 2  $F = (AB + \bar{A}\bar{B})(C + \bar{D})$

AND - OR gates

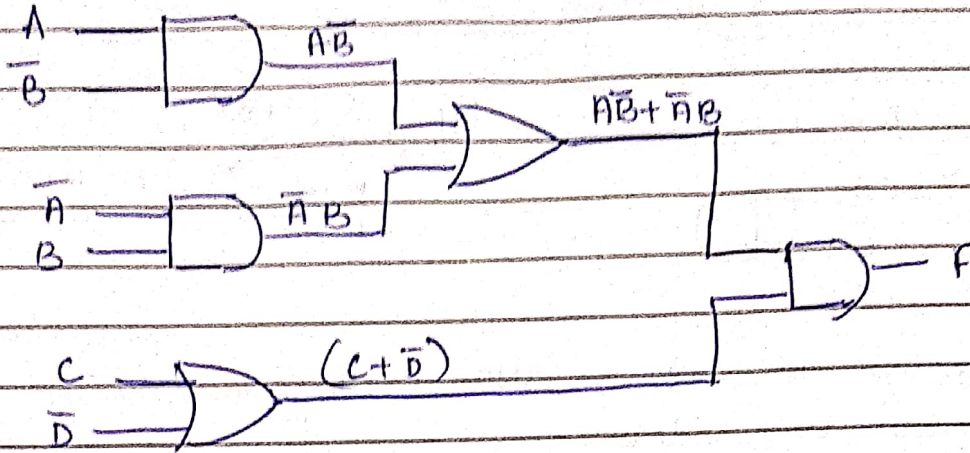



NAND gates

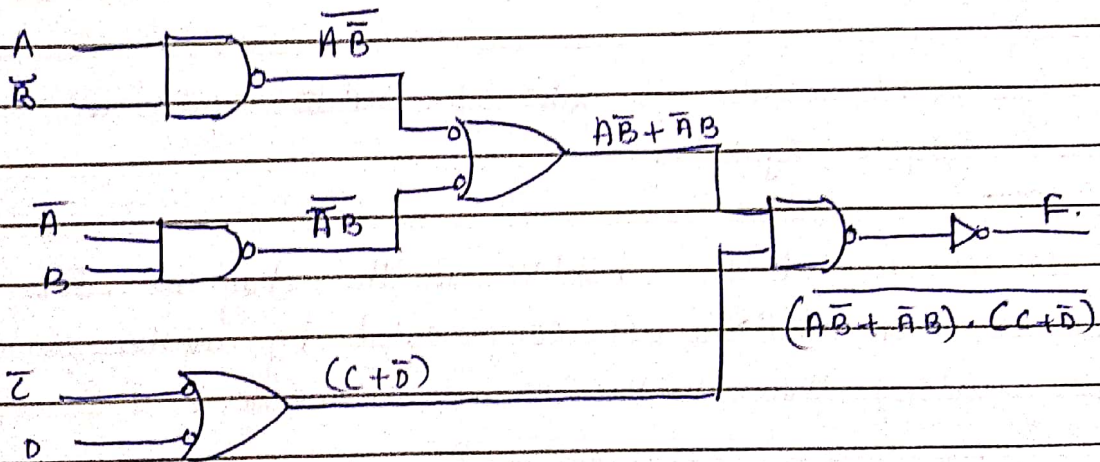


## NOR Implementation.

(a) OR - Invert

(b) Invert - AND

  

Ex  $F = (A+B)(C+D)E$

 

## OTHER TWO LEVEL IMPLEMENTATION

Some NAND or NOR gates allow the possibility of a wire connection between the outputs of two logic functions. This type of logic is called wired Logic.


Example:

(1) TTL NAND gates when tied together performs a wired-AND logic.


(2) The NOR outputs of ECL gates can be tied together to perform a wired-OR logic.



(a) A wired TTL NAND gate

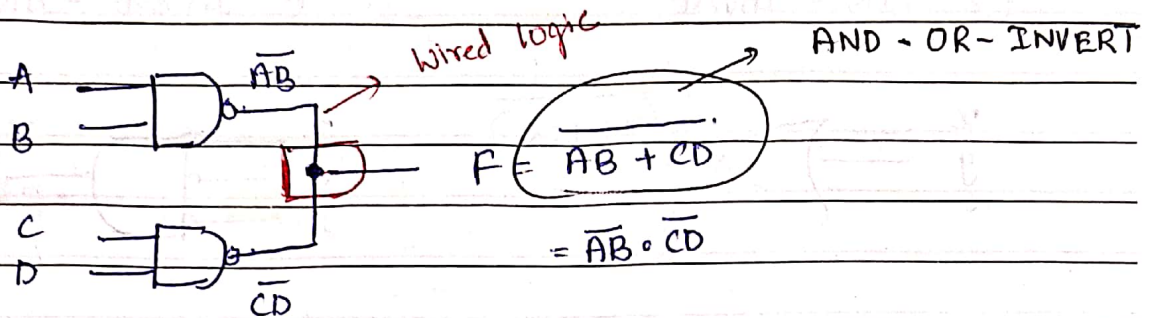

(b) Wired-OR in ECL logic

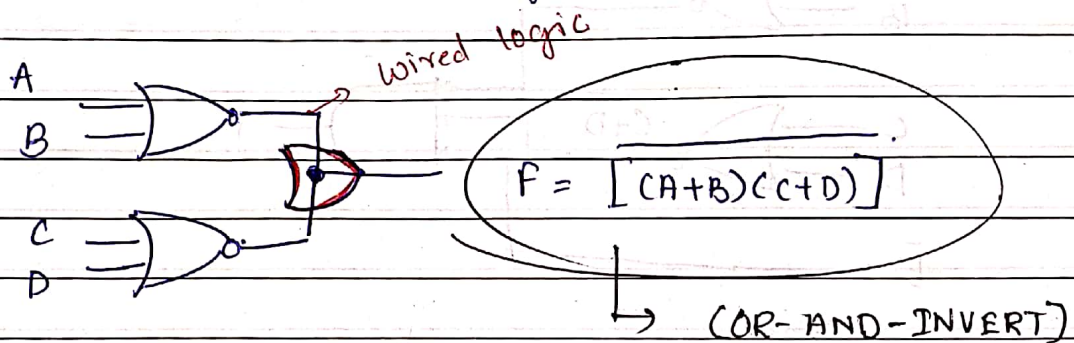

TTL  $\rightarrow$  Transistor Transistor Logic }  $\rightarrow$  Transistor logic families.  
 ECL  $\rightarrow$  Emitter Coupled Logic

Note:

A wired-Logic does not produce a physical Second-level gate, since it is just a wire connection.

## Nondegenerate Forms.

When we talk about the two-level combinations. We consider four types of gates

1. AND
2. OR
3. NAND
4. NOR.

Total no of combinations we get for a two level combination are 16, since we have four gates.

$$2^4 = 16$$

no of gates

no of level [we consider two level combination]

For combinations such as ~~NAND - AND~~, ~~OR - OR~~, ~~AND - OR~~, ~~OR - AND~~, ~~NAND - NAND~~, ~~NOR - NOR~~, ~~OR - NAND~~, ~~NAND - NOR~~. It degenerates into single operation.

\* Hence 8 combinations become degenerate forms

\* While the rest 8 combinations fall under non-degenerate forms.

The eight nondegenerate forms are

AND - OR	OR - AND
NAND - NAND	AND - NAND
NOR - OR	OR - NOR
OR - NAND	NAND -

AND - OR	OR - AND
NAND - NAND	NOR - NOR
NOR - OR	NAND - AND
OR - NAND	AND - NOR



16 combinations

⑧

AND - AND

AND - OR ✓

AND - NAND

AND - NOR ✓

OR - AND ✓

OR - OR

OR - NAND ✓

OR - NOR

NAND - AND ✓

NAND - OR

NAND - NAND ✓

NAND - NOR

NOR - AND

NOR - OR ✓


NOR - NAND

NOR - NOR ✓

Degenerate forms


↳

 Because they degenerate into a single operation.



↳ Gets degenerated into single operation

OR - AND

 


↳ It will not get degenerated into single operation (Non-degenerate form).




# AND-OR-INVERT Implementation.

$$F = (AB + CD + E)$$

(a) AND-NOR.

 


(b) AND-NOR.

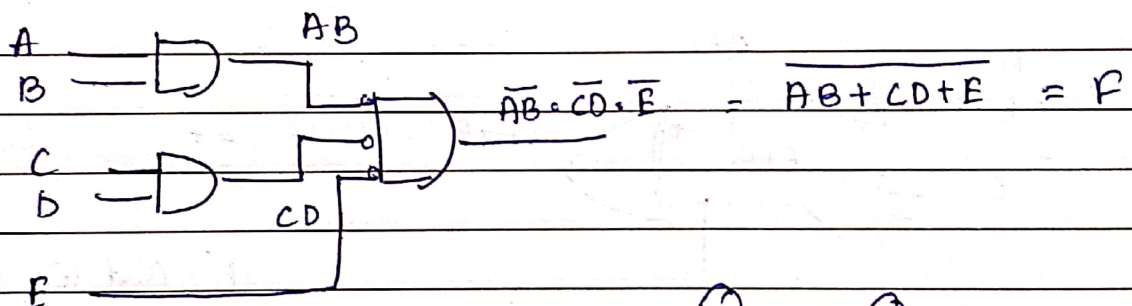

(b) and (c) are equivalent Nondegenerate forms.


(c) NAND-AND

 


OR-AND-INVERT

$$F = [(A+B)(C+D)E]$$

## (a) OR-NAND

 

## (b) OR-NAND

 

(b) and (c) are equivalent non degenerate forms

## (c) NOR-OR

