

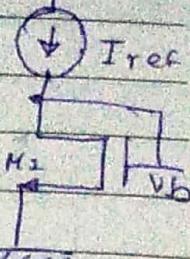


I_{SS} → how do we generate V_{GS}

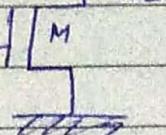

↓ done ↑ the potential each node act as cofactor

BASIC CURRENT MIRROR CIRCUIT

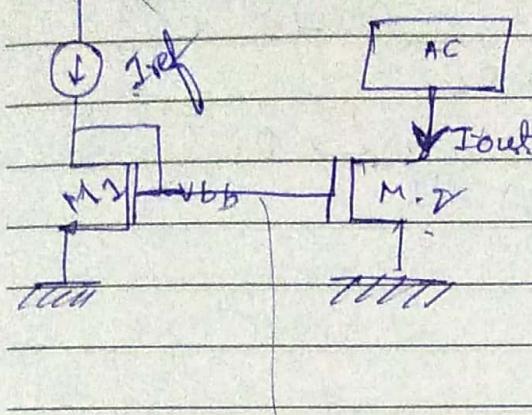

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{\omega}{L} \right)_1 (V_{GS1} - V_{TH1})^2$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left(\frac{\omega}{L} \right)_2 (V_{GS2} - V_{TH2})^2$$

$$\frac{I_{out}}{I_{ref}} = \frac{(w/L)_2}{(\omega/L)_1}$$

* Advantage: We can bias on number of rbs by using only one reference (Band gap ref)


$$I_{out} = \frac{(\omega/L)_2}{(\omega/L)_1} \cdot I_{ref}$$

* All done, assuming there is no channel length modulation

16th Oct' 19

Q: For following Ckt calculate Output Current on

(ω/L_4) / (ω/L_3) / (ω/L_2)

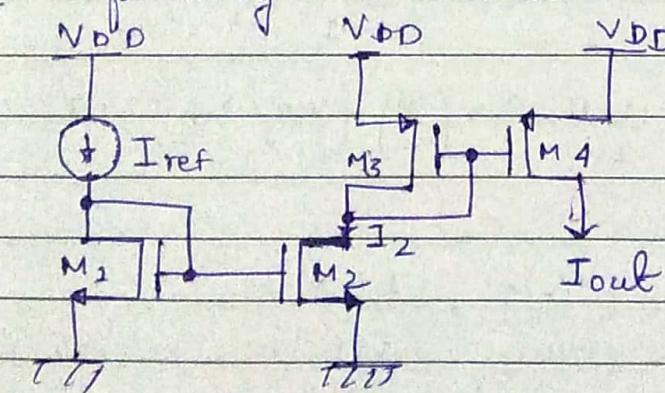

$$I_2 = \frac{(w/L)_2}{(w/L)_1} \times I_{ref}$$


CURRENT STEERING CKT

$$I_{out} = \frac{(\omega/L)_4}{(\omega/L)_3} \times I_2 = \frac{(\omega/L)_4}{(\omega/L)_3} \times \frac{(w/L)_2}{(w/L)_1} \times I_{ref}$$

→ here we steer current from one branch to another branch

DATE

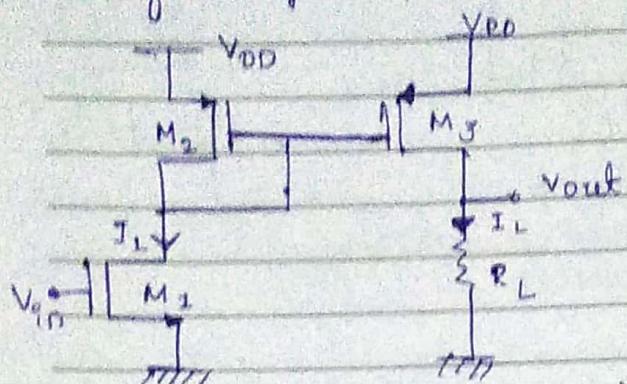Q:2. For the following circuit, find small signal voltage gain
 Find current flowing through
 $v_{out} = R_c$



Coz it's a small signal
 $I_1 = \frac{g_m}{2} v_{in}$


$$I_{out} = \frac{(w/L)_3}{(w/L)_2} \cdot \frac{g_m}{2} v_{in}$$

$$V_o = I_{out} \times R_L$$

$$= \frac{(w/L)_3}{(w/L)_2} \cdot \frac{g_m}{2} v_{in} \times R_L$$

$$A_v = \frac{V_o}{v_{in}} = \frac{(w/L)_3}{(w/L)_2} \cdot \frac{g_m}{2} R_L$$

INCLUDING CHANNEL LENGTH MODULATION:

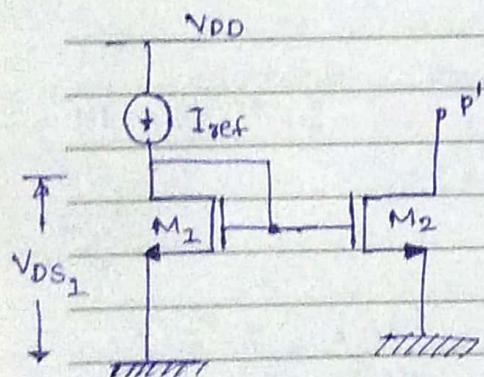

$$V_{DS1} = V_{GS1} - V_{DS2}$$

coz it depends on another variable will come on top


$$I_{ref} = \frac{1}{2} \mu n C_{ox} \left(\frac{w}{L}\right)_1 (V_{GS1} - V_{th1})^2 (1 + \alpha V_{DS1})$$

$$I_{out} = \frac{1}{2} \mu n C_{ox} \left(\frac{w}{L}\right)_2 (V_{GS2} - V_{th2})^2 (1 + \alpha V_{DS2})$$

$$\frac{I_{out}}{I_{ref}} = \frac{(w/L)_2}{(w/L)_1} \cdot \frac{(1 + \alpha V_{DS2})}{(1 + \alpha V_{DS1})}$$


How can we match the potentials of both the transistors?
 Cascade stage used to ↑ the output impedance,
 place one more common gate on the common source

CASCODE CURRENT MIRROR CKT

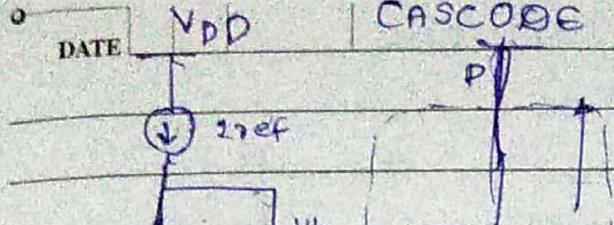

$$v_b = v_{gs} g + v_{zc}$$

Shielding property

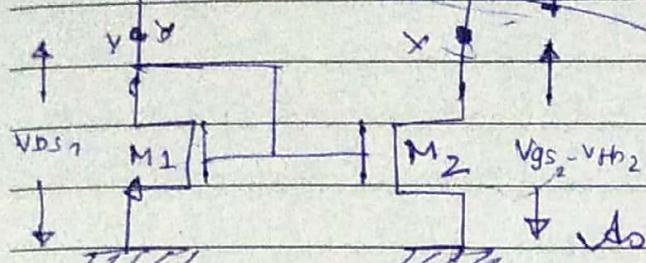

only if $V_{GS4} = V_{GS3}$; $V_{GS2} = V_{GS1}$

$$\left(\frac{\omega}{\zeta}\right)_4 = \left(\frac{\omega}{\zeta}\right)_3$$

$$\underline{V_{GS2} = V_{GS1}}$$

 As we ↑ the P, it will not affect the bottom transistor is protected

1st Oct '19

To make $V_x = V_y$

$$V_b = V_{gS_3} + V_x$$

To generate V_b , we connected 1 more diode load.

We need to make $V_N = V_{GS_3} + V_x$

$$v_N = v_{9S4} + v_{2}$$

If we make that condition satisfied any $v_N = v_b$

* Imp. trade off $\rightarrow v_{GS1} = v_{GS2}$ is the assumed condition

If we maintain them in saturation region my $V_{GS2} \neq V_{GS1}$
 coz one more Nth factor become extra there.

We can't get $I_{\text{out}} \neq I_{\text{ref}}$

To overcome this ^{out + ref} need to add one more V_{th} at M_2
 but our V_p will \uparrow by V_{th} its a large amount

APPLICATIONS (Current Mirror)


2) Fair housing

DATE



ACTIVE CURRENT MIRROR

Basic current mirror \rightarrow var like active load.

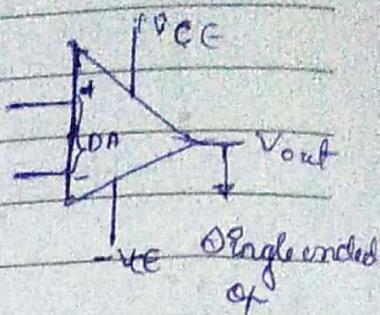- * Input of an op-amp is Differential amplifier
- * Op-amp can (741) give only one output, var double ended output.



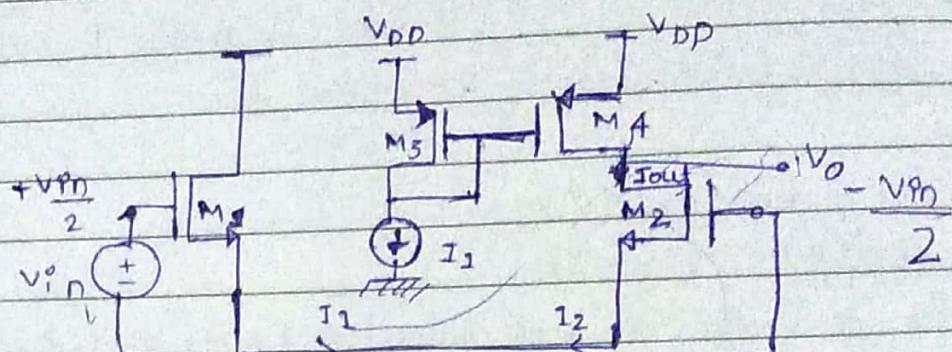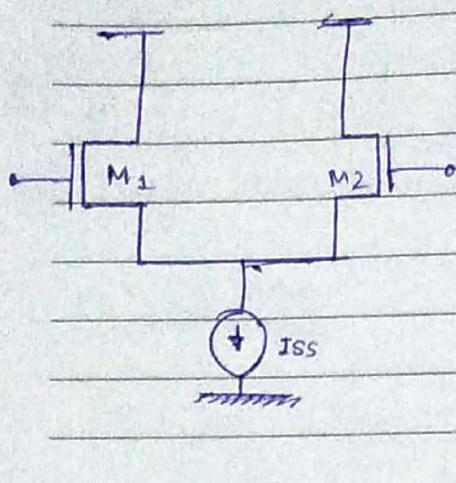Taking output at one end. More active load, we can also do that with p-mos



Unbalanced differential amplifier, op taken from single end

Q: Why do we need to replace active resistive with only active basic current mirror act as active load

Q: How do we find the gain of this ckt?



$$I_1 + I_2 = I_{SS}$$

Wkly $A_v = G_m R_{out} \rightarrow \text{①}$
 $\hookrightarrow (\text{of wkt})$

$$G_m = \frac{I_{out}}{V_{in}}$$

$$I_1 = g_{m1} \cdot \frac{V_{in}}{2}$$


$$I_{out} = I_1 \quad [\text{If we match } (\omega_1/\omega)_1 = (\omega_1/\omega)_3]$$

$$G_m = \frac{I_1}{V_{pp}} = \frac{g_{m1} V_{in}}{2 V_{pp}} = \frac{g_{m1}}{2}$$

DATE


To find Root

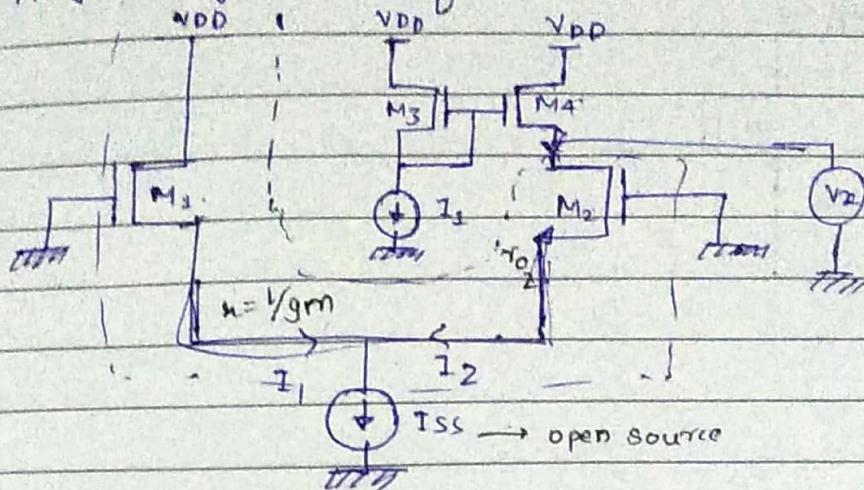- 1) Short the input
 - 2) apply voltage source, findout I_x



resistance offered by the below part

H_2O_2 is denoted with $\frac{1}{6}$ m

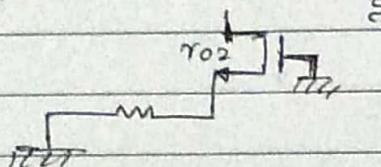

→ Common Source Degeneration

$$R_{out} = \left[1 + (\frac{g_m}{g_{mb}} + r_o) R_S + r_o \right]$$

$$= \left(1 + \frac{g_m \tau_{02}}{g_m} \right) \frac{1}{\tau_{02}} + \tau_{02} \quad (\text{if } g_m \text{ is very small})$$

(Same $\omega_L = \text{Same } \xi_n$)

$$\approx -270_2$$

$$\text{Total res} = 2\tau_{02} || \tau_{04}$$



$$A_{10} = \frac{g m_1}{2} (2 r_{02} / r_{04})$$

* Convex mirror used to amplify the signal & to leave the vct.

DATE

SMALL & SIGNAL EQUIVALENT OF ACTIVE CURRENT MIRROR


Make all the dc sources to zero

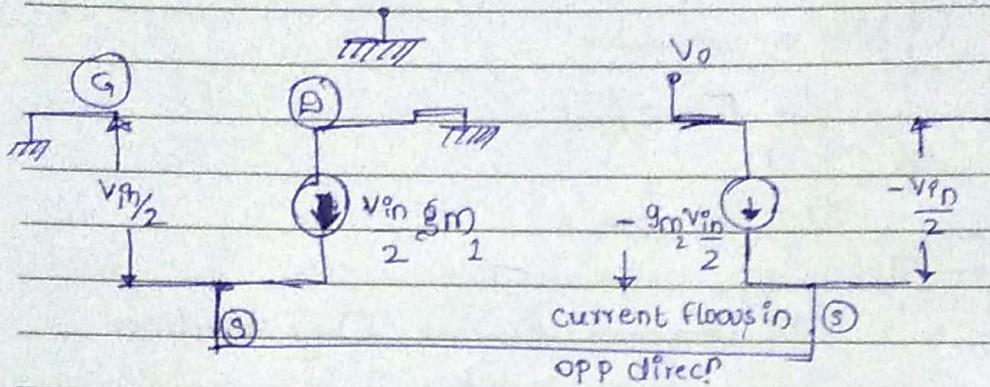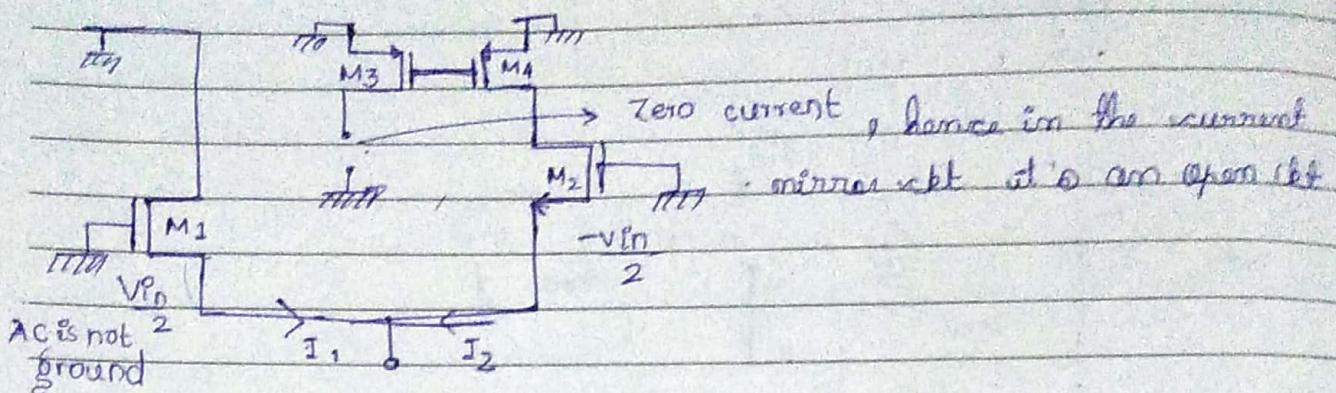


$$I_{out} = +\text{gm}_1 \frac{V_{in}}{2}$$

connected

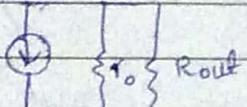* M_3 , gate & drain are grounded, common node = $\frac{1}{2\text{gm}_1}$



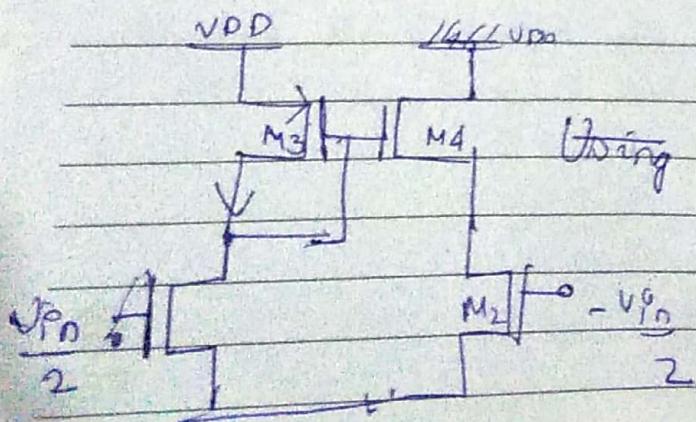- * Is it is final circuit proper or some issues are there?
- Drawback: Gain is half.



abi

Using current M_1 towe can bias node M_2 * Observed that output \propto current of M_2 by $\propto M_1$



Small signal analysis

$$A_{v0} = G_m R_{out}$$

$$G_m = \frac{I_{out}}{V_{in}}$$

diode connected

$$R_3 = ?$$

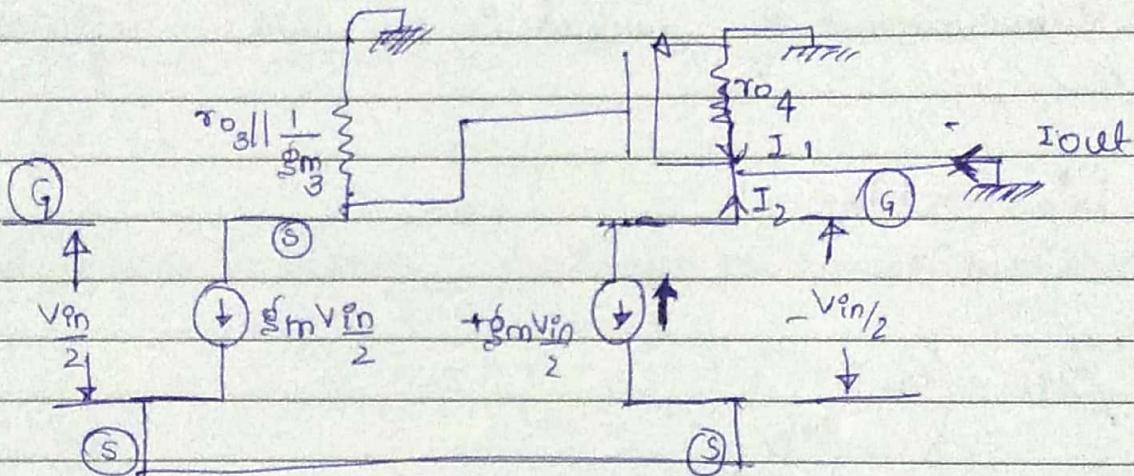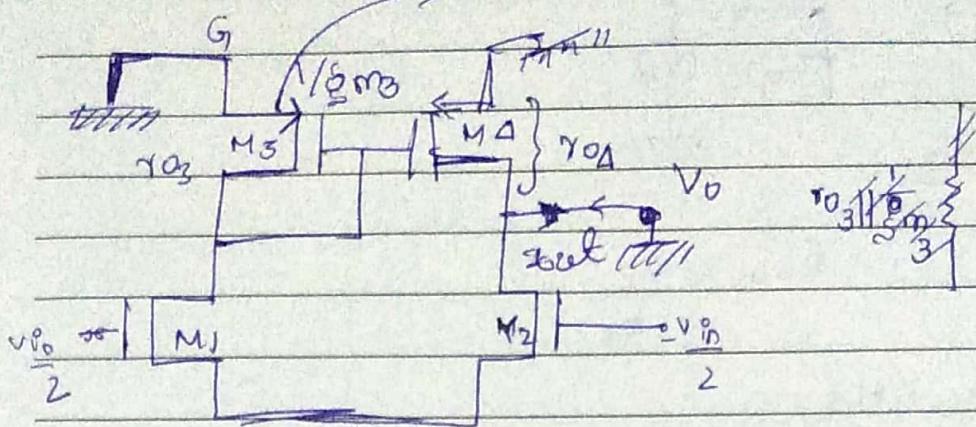

$$I_{out} = I_1 + I_2 = 0$$

$$I_{out} = - (I_1 + I_2)$$

$$= - \left(\frac{\partial m \frac{V_{in}}{2}}{\partial v} + \frac{\partial m V_{in}}{2} \right)$$

$$I_{out} = - \frac{\partial m}{\partial v} V_{in}$$


$$\frac{I_{out}}{V_{in}} = \frac{-\frac{\partial m}{\partial v}}{2} = \frac{g_m}{2}$$

R_{out} is

$$- \frac{\partial m}{\partial v} = \frac{I_{out}}{V_{in}} \quad [\text{current is flowing in opp direction}]$$

$$G_m = - \frac{\partial m}{\partial v}$$

DATE

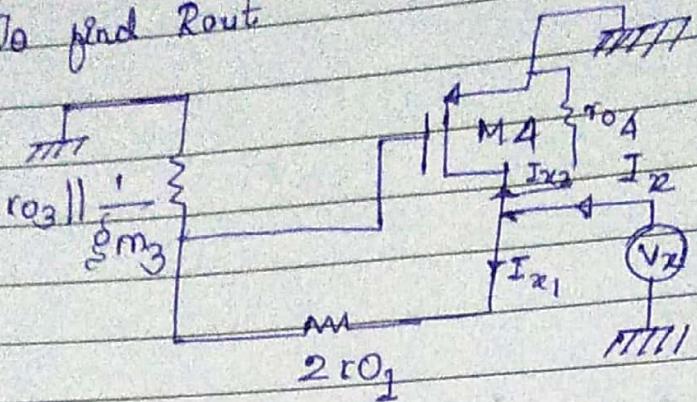To find R_{out} 

$$I_x = I_{x_1} + I_{x_2}$$

$$R_{out} = \frac{V_x}{I_x}$$

through

$I_{x_2} \rightarrow$ flows M_1, M_2 & M_3

** We should take account of current in M_1 which is reflected at the M_4 .

$$I_x = I_{x_1} + I_{x_2} + I_{x_1}$$

$$= 2 I_{x_1} + I_{x_2}$$

$$I_{x_1} = \frac{V_x}{2r_{o_1} + \left(r_{o_3} \parallel \frac{1}{gm_3} \right)}$$

very very small compared to $2r_{o_1}$

$$I_{x_2} = \frac{V_x - 0}{r_{o_4}}$$

$$I_x = 2 \left[\frac{V_x}{2r_{o_1} + r_{o_3}} + \frac{V_x}{\frac{gm_3 (r_{o_3} + \frac{1}{gm_3})}{r_{o_4}}} \right] + \frac{V_x}{r_{o_4}}$$

$$= \frac{V_x}{r_{o_1}} + \frac{V_x}{r_{o_4}}$$

$$= V_x \left[\frac{1}{r_{o_1}} + \frac{1}{r_{o_4}} \right]$$

$$I_x = V_x \left[r_{o_1} \parallel r_{o_4} \right]$$


$$R_{out} = \frac{V_x}{I_x} = r_{o_1} \parallel r_{o_4} = r_{o_2} \parallel r_{o_4}$$

DATE

$$A_{vz} = G_m R_{out} = -\frac{g_m}{2} (r_{o2} \parallel r_{o4})$$

A COMMON MODE RESPONSE OF ACTIVE CURRENT MIRROR COA

[NOT HERE 4]
SYLLABUS

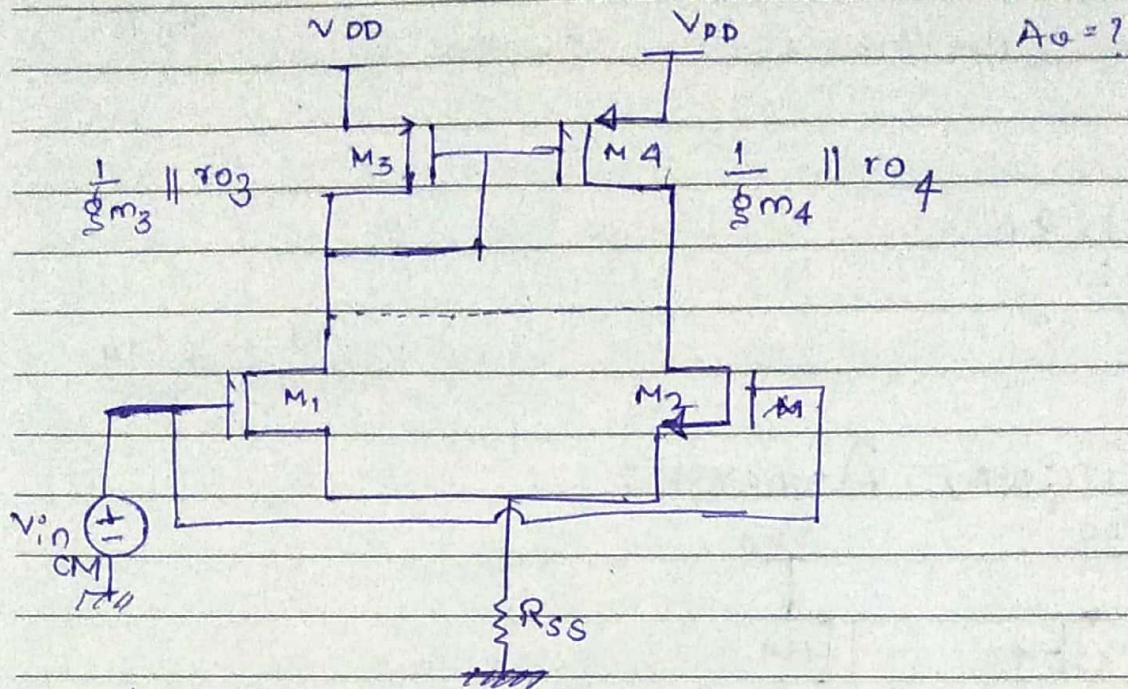

Gate, source is common, drain also common as well shorted

$$\begin{aligned}
 & \frac{1}{2g_m \cdot A} \left\{ \left(\frac{1}{g_m} \parallel r_o \right) \parallel \left(\frac{1}{g_m} \parallel r_o \right) \right\} \xrightarrow{\text{approx}} \frac{1}{g_m} \\
 & \xrightarrow{\text{approx}} \frac{1}{g_m} \xrightarrow{\text{parallel of both}} \frac{1}{2g_m} \\
 & V_{in(CM)} \xrightarrow{\text{M}_1 + M_2} \\
 & \xrightarrow{\text{RSS}} \frac{1}{2g_m} + RSS \\
 & A_v = \frac{\text{Resistance at load}}{\text{Resistance at source}} \\
 & = \frac{-1/2g_m \cdot A}{\frac{1}{2g_m} + RSS} = \frac{-7g_m \cdot A}{(1 + 2g_m \cdot A) RSS} \\
 & = \frac{-\frac{1}{2g_m} \cdot A}{(1 + 2g_m \cdot A) RSS g_m} = \frac{-\partial V_{out}}{\partial V_{in(CM)}}
 \end{aligned}$$

DATE

$$\text{Common Mode Rejection Ratio} = \frac{A(\text{different mode})}{A(\text{common mode})}$$

$$= \frac{\frac{g_m}{2} (r_o 2 || r_o 4)}{g_m r_o}$$

$$1 + 2 g_m r_o R_{SS}, g_m r_o$$


$$= \underbrace{(1 + 2 g_m r_o R_{SS})}_{g_m R_{SS}} \underbrace{g_m r_o \times (r_o 2 || r_o)}_{g_m r_o}$$

$$= (\frac{g_m r_o}{2})(\frac{g_m r_o}{2})$$

$$= (\frac{g_m r_o}{2})^2$$

23rd Oct '19

LARGE SIGNAL ANALYSIS:

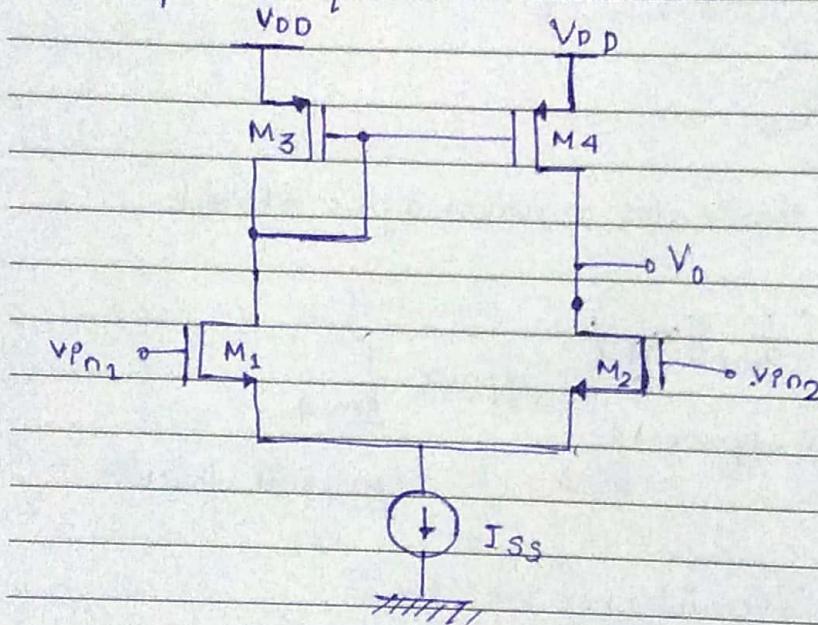

Case 1: When $V_{pn_1} = +ve$ & $V_{pn_2} = 0$

$M_1 = ON$

$M_3 = ON$

$M_4 = ON$

$M_2 = OFF$

$$V_0 = V_{pn_1} - V_{pn_2}$$

* If all transistors on, the current is not flowing in M_2 act as open circuit, the current flowing through M_1 is stored in capacitor such & every node act as a capacitor

DATE

hence $V_o = V_{DD}$


Case 2: When $V_{in_2} = +ve \& V_{in_1} = 0$

$M_4 = M_1 = off = M_3 = V_{DD}$ gate & source at same source potential $V_{GS} = 0$
 $M_2 = ON$

* The charge stored in capacitor will completely discharged = 0


Case 3: If we kept $V_{in_1} = +ve$ & slightly increasing the value of V_{in_2} , so it will start more towards Zero.

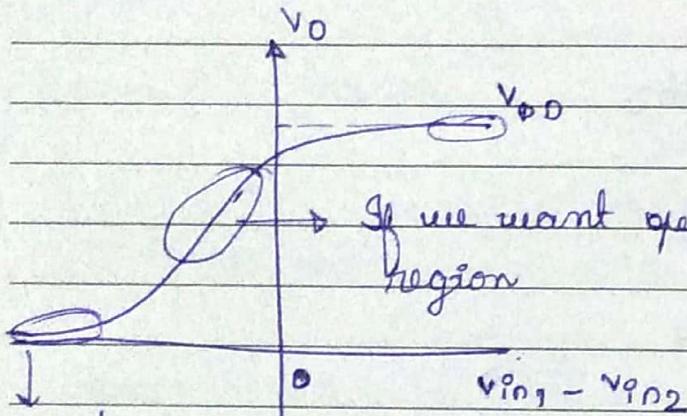* As we applied larger differential input gain / slope will be zero



gain / slope = zero

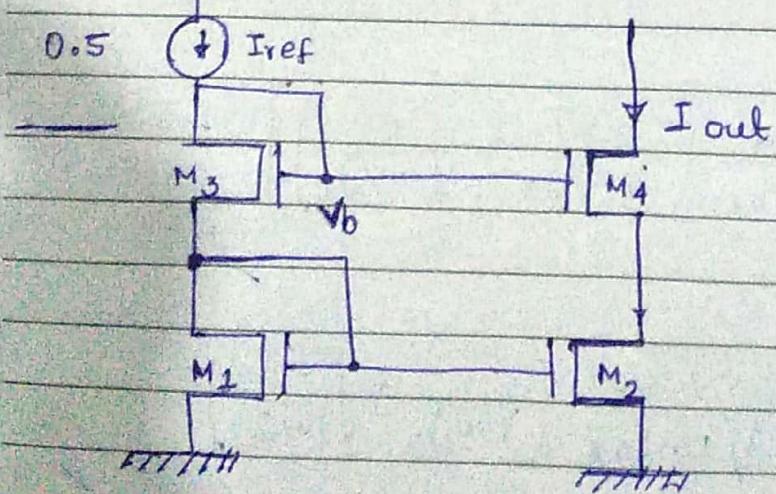Q.1 For following vcbt find max value of I_{ref} \rightarrow the current source (I_{ref}) should sustain a voltage drop of 0.5 V across it



$$I_{ref} = \left(\frac{w/L_3}{w/L_1} \right) \times I_{out}$$

$$I_{out} = \left(\frac{w/L_2}{w/L_1} \right) \times$$

DATE

$$V_b = V_{GS3} + V_{GS1}$$

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_3 \left(V_{GS3} - V_{th3}\right)^2$$

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_1 \left(V_{GS1} - V_{th1}\right)^2$$

$$2 I_{ref} = \mu_n C_{ox} \left(\frac{w}{L}\right)_3 \left(V_{GS3} - V_{th3}\right)^2$$

$$\left(\frac{L}{w}\right)_3 \frac{2 I_{ref}}{\mu_n C_{ox}} = \left(V_{GS3} - V_{th3}\right)^2$$

$$= \sqrt{\frac{2 I_{ref} L_3}{\mu_n C_{ox} w_3}} = V_{GS3} - V_{th3}$$

$$V_{GS3} = V_{th3} + \sqrt{\frac{2 I_{ref} L_3}{\mu_n C_{ox} w_3}}$$

$$V_{GS1} = V_{th1} + \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_1}}$$

$$V_b = V_{th3} + V_{th1} + \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_3}} + \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_1}}$$

$$V_{DD} = V_b = 0.5$$

$$V_{DD} = \left[V_{th3} + V_{th1} + \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox}} \left(\sqrt{\frac{1}{(w/L)_3}} + \sqrt{\frac{1}{(w/L)_1}} \right)} \right] = 0.5$$

$$0.5 - V_{DD} + V_{th3}$$

$$V_{DD} - 0.5 - V_{th3} - V_{th1} = \sqrt{\frac{2 I_{ref}}{\mu_n C_{ox}} \left(\sqrt{\frac{1}{(w/L)_3}} + \sqrt{\frac{1}{(w/L)_1}} \right)}$$

DATE

$$(V_{DD} - 0.5 - V_{TH3} - V_{TH1})^2 = \frac{2 I_{ref}}{\mu_n C_{ox}} \left(\frac{1}{\sqrt{\omega_3}} + \frac{1}{\sqrt{\omega_1}} \right)^2$$

$$I_{ref} = \frac{(V_{DD} - 0.5 - V_{TH3} - V_{TH1})^2 \mu_n C_{ox}}{2 \left[\sqrt{\left(\frac{L}{w}\right)_3} + \sqrt{\left(\frac{L}{w}\right)_1} \right]^2}$$

Q: 2 Design differential amplifier circuit with resistive load for the following specifications, calculate the gain for the designed ckt

$$\text{Power} = 1 \text{ mW}$$

$$V_{TH} = 0.4$$

$$V_{inCM} = 1 \text{ V}$$

$$V_{GS} = V_{TH} = 100 \text{ mV}$$

(Quencher)

$$\mu_n C_{ox} = 100 \text{ nA}^2/\text{V}^2$$

$$V_{DD} = 1.8$$

$$I_D = 5.5 \text{ mA}$$

SS

$$G_m = \frac{2 I_D}{V_{GS} - V_{TH}} = 5.5 \text{ mS}$$

$$G_m = \sqrt{2 I_D \mu_n C_{ox} \left(\frac{w}{L} \right)}$$

$$5.5 \times 10^{-3} = \sqrt{2 \times 0.277 \times 100 \times 10^{-6} \times \left(\frac{w}{L} \right)}$$

$$= 3.025 \times 10^{-5} = 5.54 \times 10^{-3} \left(\frac{w}{L} \right) \Rightarrow \left(\frac{w}{L} \right) = 546$$

$$x = V_{DD} - R_D I_{SS}$$

2

$$V_{GS} - V_{TH} = 1.8 - R_D \left(\frac{0.555}{2} \right)$$

$$A_V = -\frac{g_m}{2} R_D$$


$$100 \times 10^{-3} = 1.8 - 0.2775 R_D$$

$$= 0.03 \quad 33.693 //$$

$$1.7 = 0.2775 R_D$$

$$R_D = 6.126 \text{ k}\Omega$$

X

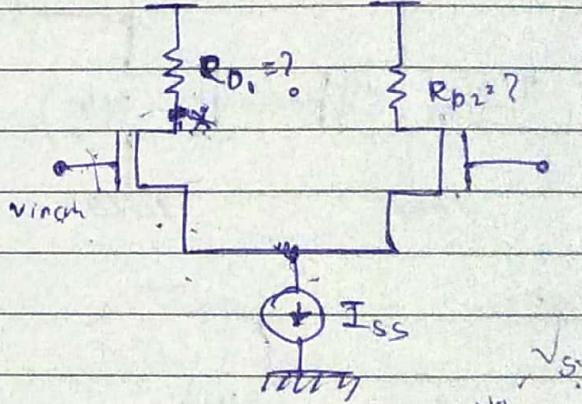

DATE


$$V_{DD} - R_D I_{SS} = V_{inCM} - V_{th}$$

$$1.8 - R_D \left(\frac{0.55}{2} \right)^3 = 0.6$$

$$\Rightarrow R_D = 4.36 \text{ k}\Omega$$

$$A_v = -\frac{g_m}{R_D}$$

$$= -23.98$$

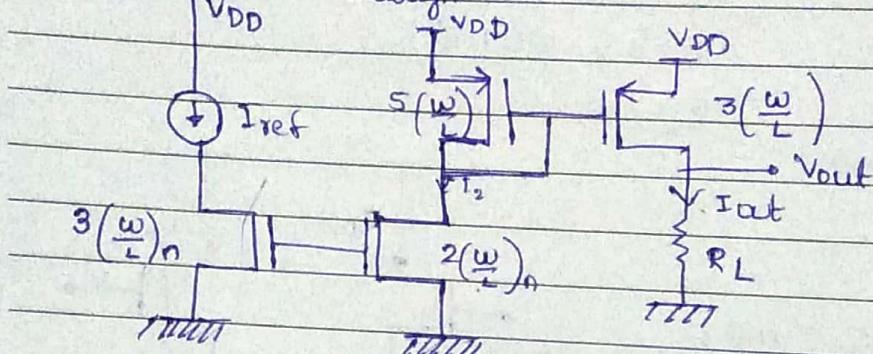24th Oct' 19Q: 2) Find I_{out} through R_L ?

Soln:

$$I_2 = \frac{2\left(\frac{w}{L}\right)}{3\left(\frac{w}{L}\right)} \times I_{ref}$$


$$I_{out} = \frac{3\left(\frac{w}{L}\right)}{5\left(\frac{w}{L}\right)} \times I_2 = \frac{3\left(\frac{w}{L}\right)}{5\left(\frac{w}{L}\right)} \times \frac{2\left(\frac{w}{L}\right)}{3\left(\frac{w}{L}\right)} \times I_{ref}$$

$$\approx \frac{2}{5} I_{ref}$$

Design

Q: 3) For following cbt shown below for the max power of 3mW?

DATE

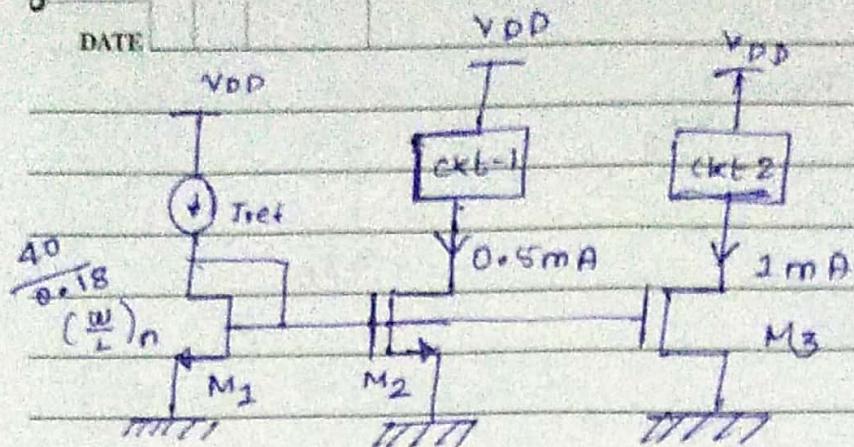

$$V_{DD} = 1.8\text{V}$$

$$P = 3 \times 10^{-3}$$

$$P = V \cdot I$$

$$I = 1.66 \text{ mA} //$$

$$1.667 = 1 + 0.5 + T_{ref}$$

$$E_{\text{ref}} = 0.1 \text{ eV}$$

$$0.5 \times 10^{-6} = \frac{\left(\frac{w}{L}\right)_2}{\left(\frac{w}{L}\right)_1} \times 1.65 \times 10^{-6}$$

$$\left(\frac{\omega}{L}\right)_2 = \frac{0.5}{0.47} \quad \left(\frac{\omega}{L}\right)_0$$


$$= 2 \cdot 94 \left(\frac{w}{L} \right)_0$$

= 653.59

$$1 \times 10^{-3} = \frac{(w/l)_3}{653.59} \times 0.5 \times 10^{-5}$$

$$-\frac{1}{0.5} \times 658.59 = 1307.1$$

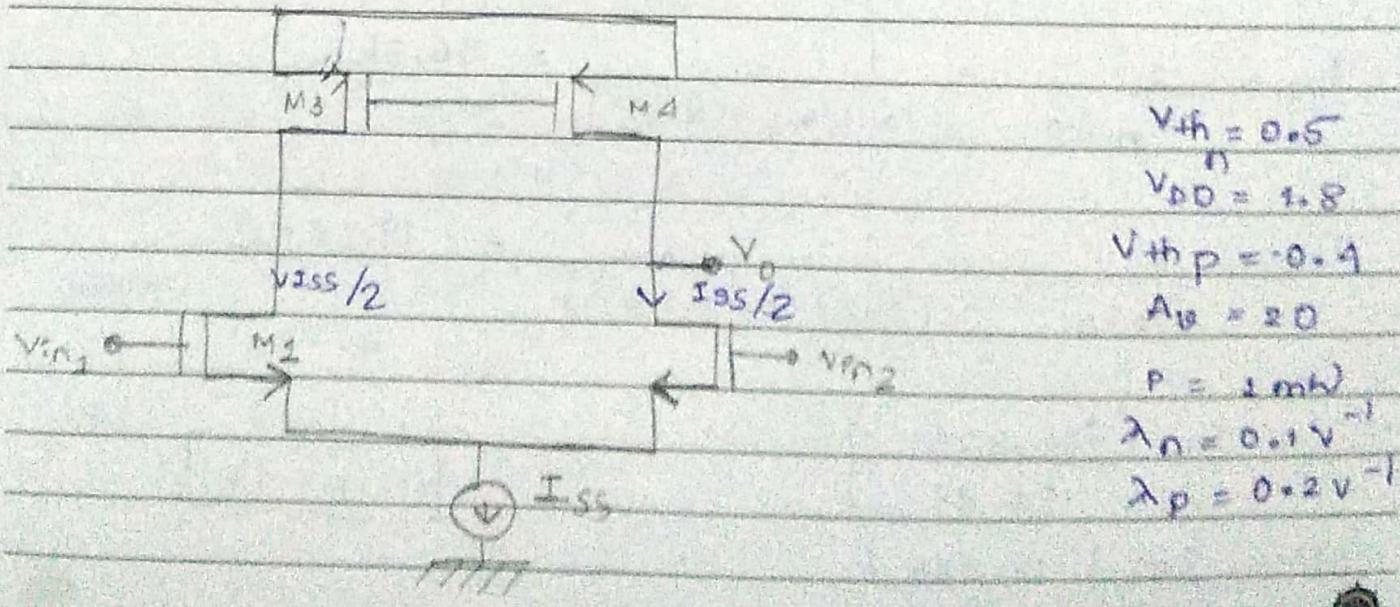Q: Design for the following clk for following specifications,



$$\frac{I}{35} = 0.55 \text{ mA}$$

DATE

$$A_V = 20$$

$$R_D = \frac{1}{\lambda I_D}$$

$$\delta m = \sqrt{2 U_n G_{ox} (\frac{W}{L}) I_D}$$

$$r = \frac{1}{\lambda I_{D_1}}$$

$$A_V = \delta m [\tau_{o1}/(\tau_{o2})]$$

$$= \delta m \left[\frac{\tau_1 \cdot \tau_2}{\tau_1 + \tau_2} \right]$$

$$= \delta m \left[\frac{\frac{1}{\lambda I_{D_1}} \cdot \frac{1}{\lambda I_{D_2}}}{\frac{1}{\lambda I_{D_1}} + \frac{1}{\lambda I_{D_2}}} \right] = A_V = \delta m \left[\frac{1}{\lambda_1 I_D + \lambda_2 I_D} \right]$$

$$20 = \frac{\delta m}{I_D} \left[\frac{1}{0.3} \right]$$

$$A_V = \frac{2 I_D}{I_D (V_{GS} - V_{TH}) (0.3)} = \frac{2}{(V_{GS} - 0.5)(0.3)}$$

$$20 = \frac{2}{V_{GS}(0.3) - 0.15}$$

$$= 20 V_{GS}(0.3) - 20(0.15) = 2 \Rightarrow 6 V_{GS} - 3 = 2$$

$$6 V_{GS} = 2 + 3 = 5$$

$$I_1 = I_2 = 0.25 \text{ mA}$$

$$V_{GS} = 0.833$$

$$\tau_{o2} = \frac{1}{\lambda n I_D} = \frac{1}{(0.1)(0.275 \times 10^{-3})} = 36.3 \text{ k}\Omega$$

$$\tau_{o4} = \frac{1}{\lambda p I_D} = \frac{1}{(0.2)(0.275 \times 10^{-3})} = 18.18 \text{ k}\Omega$$

$$A_V = \delta m \left[\frac{656.304}{54.48} \right]$$

$$20 = \delta m (12.046)$$

$$V_{PDCM} = 1V$$

$$\delta m = 1.66$$

DATE

$$\frac{I_m}{2} = \frac{2 I_D}{V_{GS} - V_{TH}} = 1.66 = \frac{2(0.275 \times 10^{-3})}{V_{GS} - V_{TH}}$$

$$= V_{GS} - V_{TH} = 0.33V$$

$$V_{GS} = 0.83V$$

$$U_{nCOX} = 100 \mu A / \sqrt{2}$$

$$I_D = \frac{1}{2} U_{nCOX} \left(\frac{\omega}{L}\right) (V_{GS} - V_{TH})$$

$$\frac{0.55 \times 10^{-3}}{100 \times 10^{-6} (0.33)^2} = \frac{\omega}{L}$$

$$\left(\frac{\omega}{L}\right)_{1,2} = 50.5$$

$$U_P = 200 \mu A / \sqrt{2}$$

~~$$V_{DS,X} = V_{DS,CM} - V_{TH} = 1 - 0.5 = 0.5$$~~

$$V_{G_3} = V_R = 0.5$$

$$|-V_{BD} + V_{G_3}| = V_{GS}$$

$$V_{GS} = 1.3$$

$$|V_{GS}| - |V_{TH,P}| = 1.3 - 0.4 = 0.9$$

$$I_D \left(\frac{\omega}{L}\right)_{3,4} = \frac{0.555 \times 10^{-3}}{200 \times 10^{-6} \times (0.9)^2} = @ 3.43 //$$

~~Ans~~


A_B = same, ϕ = same

change basic current mirror by resistive load.

DATE

DATE _____

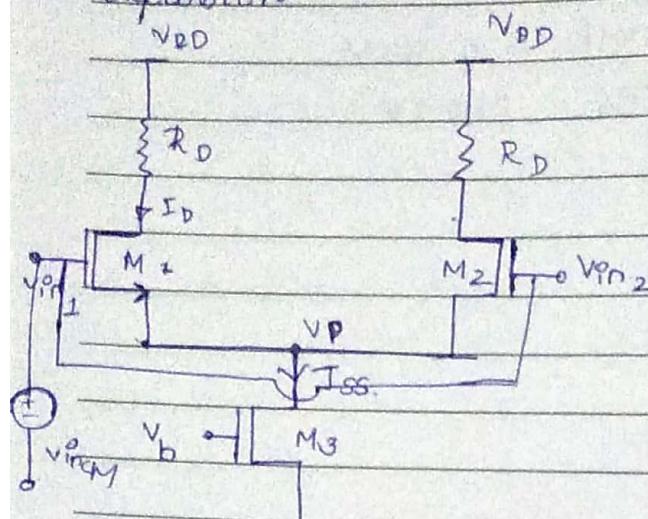② For following ckt, calculate the common mode gain assuming channel length modulation for $M_1 = M_2 = 0$ & for $M_3^{(1)} \neq 0$. Compute gain expression.



$$\lambda_{M_1} = 0 \quad \lambda_{M_3} \neq 0$$

* take r_3 into account, r_1, r_2 can be neglected


* Overdrive voltage is of MgN_2

$$A_{CM} = \frac{-R_D I_{SS}}{(V_{GS} - V_{TH}) + \frac{Z}{\lambda}}$$

$$I_D = \frac{I_{ss}}{2}$$

$$V_{in/1} = - \frac{g_m R_D}{1} (V_{in/M} - V_p),$$
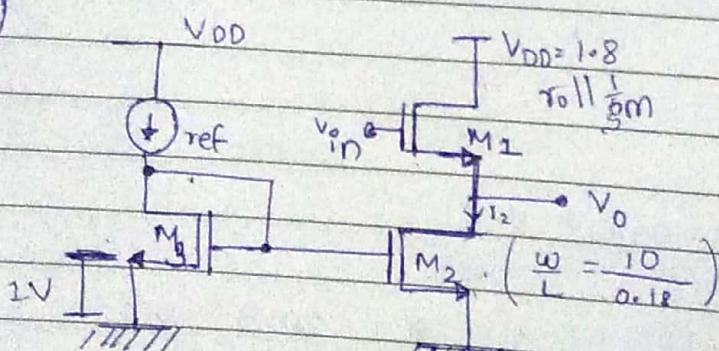
$$V_{n_2} = - \frac{g_m R D}{2} (V_{in CM} - V_p)$$



$$\lambda = 0.1 \text{ v}^{-1}$$

$$v + h = 0.5v$$

$$\Delta b = 0.95 \pm$$

$$UnCo_2 = 100 \mu A^2/V^2$$


$$V_{GS3} = 1V$$

$$I_2 = \frac{\left(\frac{\omega}{L_2}\right)}{\left(\frac{\omega'}{L}\right)_2} \times I_{ref} = \frac{10}{0.18} \times I_{ref} = 55.5 \times I_{ref}$$

Common drain amplifier \rightarrow source follower
 R_s is replaced by Current mirror

DATE

Q01 P 8.1

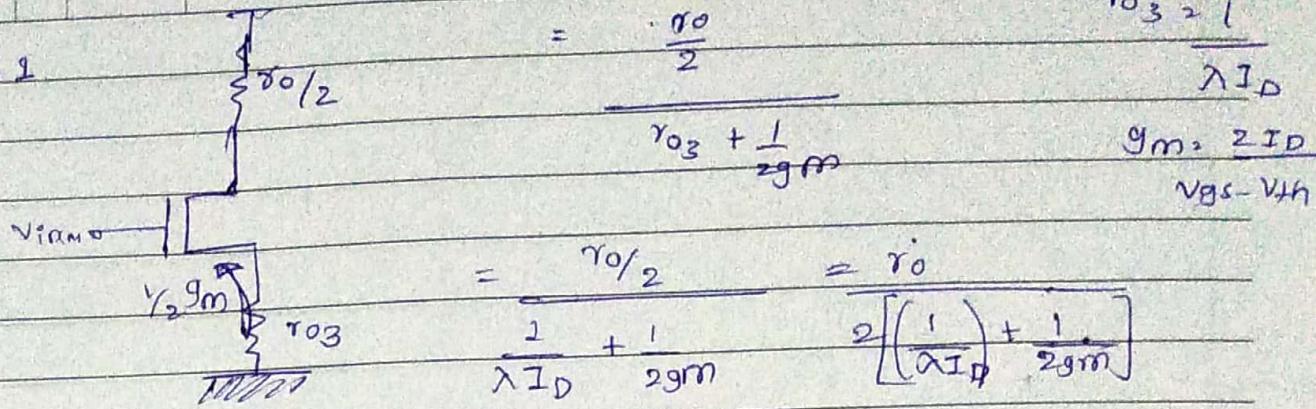

$$= \frac{r_0}{2} \times \frac{2g_m \lambda I_D}{2g_m + \lambda I_D} = \frac{r_0}{2} \left[\left(\frac{1}{\lambda I_D} \right) + \frac{1}{2g_m} \right]$$

Q01 P 8.2

$$I_D = \frac{1}{2} \mu n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{10}{0.18} \right) \left(1 - 0.5 \right)^2$$


$$\approx 0.694 \text{ mA.}$$

$$0.694 \times 10^{-3} = \frac{55.5}{(\omega L)^3} \times 1 \text{ nF.}$$

~~$$r_{o2} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 0.694 \times 10^{-3}} = 14.4 \text{ k}\Omega.$$~~


~~$$g_{m2} = \frac{1}{2}$$~~

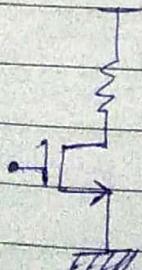For finding max input swing of any vkt theoretically



Absolute potential of gate $V_g = V_{GS} + V_m$.


METHOD TO FIND MAX INPUT SWING LIMITS

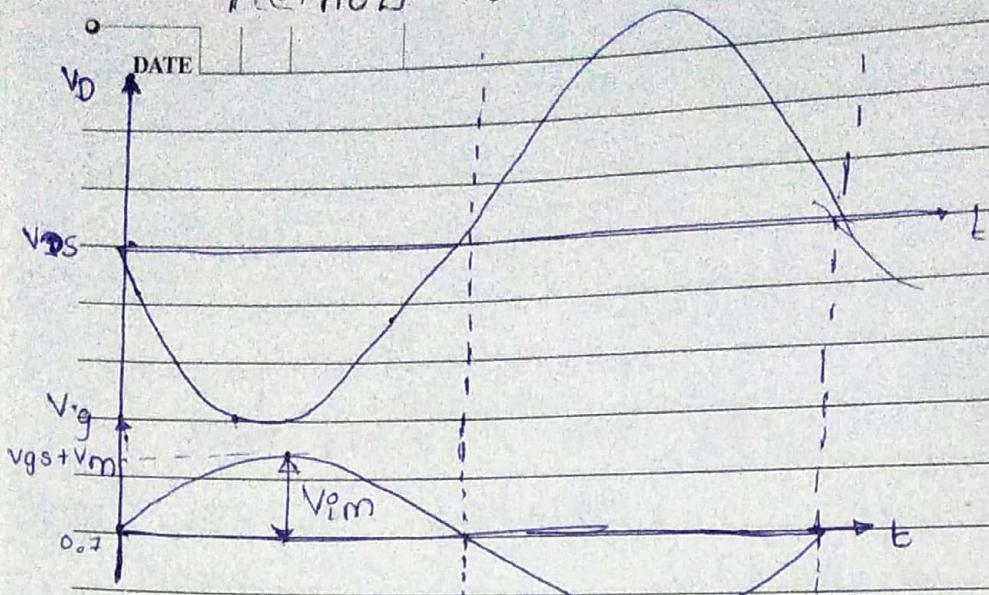

$$V_o = V_{DS} - g_m I_D V_{GS}$$

$$V_o = V_{DS} - g_m I_D V_{IM}$$

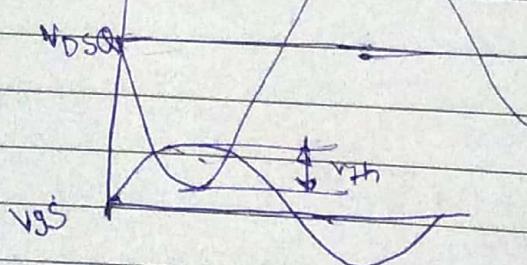To keep in saturation why V_{GS} can go one V_{th} below the gate




$$V_{DS} - g_m R_D V_{GS} = (V_{GS} + V_{th}) - V_{th}$$

$$V_{DS} = g_m R_D V_{IM} + V_{th} = V_{GS} + V_{th}$$



$$V_M = \frac{V_{DS} - V_{GS} + V_{th}}{1 + g_m R_D}$$

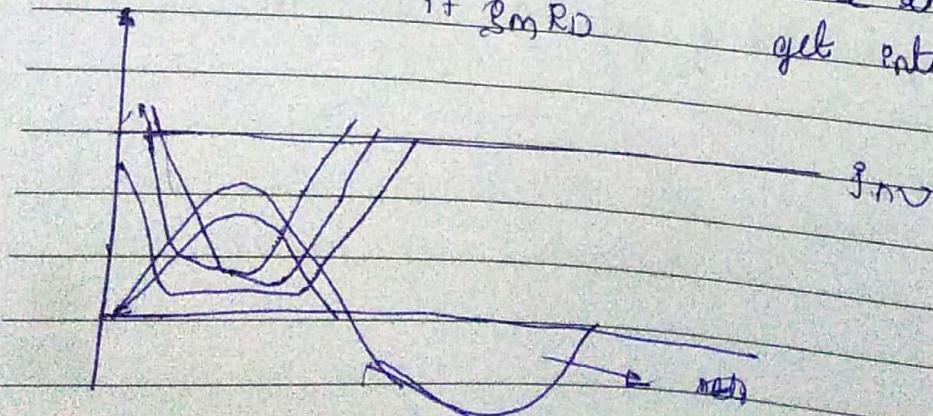More than this, it will get into triode not sat.



DATE

plot velocity current drain?

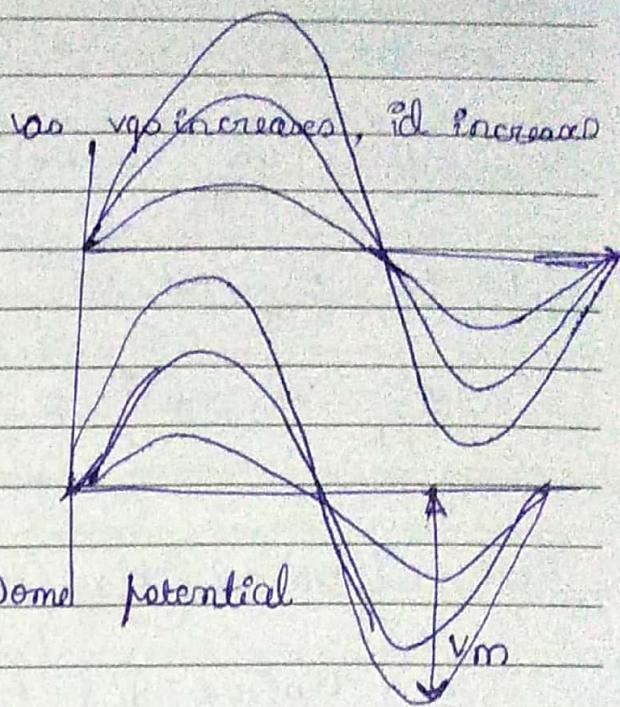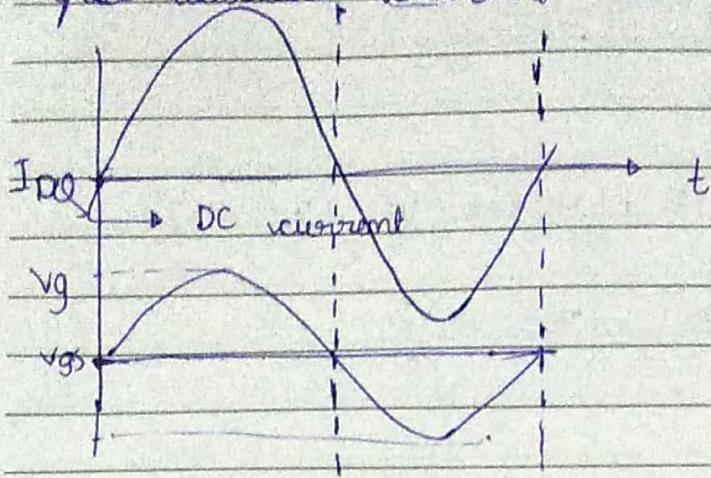

In negative cycle the current at some potential at become zero, $V_{GS} < V_{th}$.

* Now vit will enter into cut off.


$$V_{GS} - g_m V_{DS} = I_D \quad V_M = \frac{I_D}{g_m}$$

$$V_{in} = V_M(\max) = \frac{V_{DS} - V_{GS} + V_{th}}{1 + g_m R_D}$$

$$V_M(\max) = \frac{I_D}{g_m}$$

$$V_{in} = V_M(\max)_1 + V_M(\max)_2 \times 2.$$

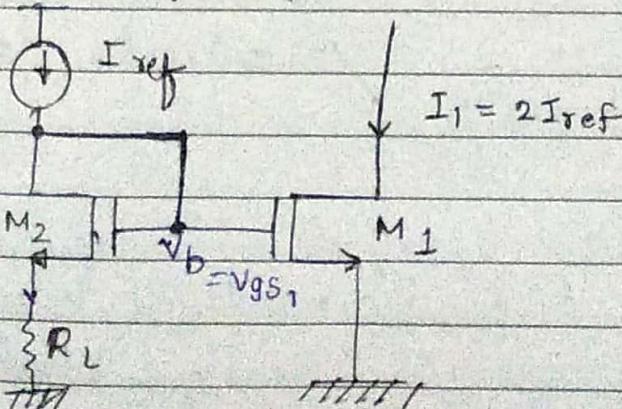Q. For the following circuit, determine $R_L \rightarrow$ current $I_1 = 2 I_{ref}$



$$I_1 = \frac{(\omega/L)_1}{(\omega/L)_2} \times I_{ref}$$

$$2 I_{ref} = \frac{(\omega/L)_1}{(\omega/L)_2} \times I_{ref}$$

$$(\omega/L)_1 = 2 (\omega/L)_2$$

$$\frac{I_{ref}}{I_{ref}} = 2$$

DATE

$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_1 (V_{GS} - V_{th})_1^2$$

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_2 (V_{GS} - V_{th})_2^2$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_1 (V_{GS} - V_{th})_1^2 = 2 \cdot \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_2 (V_{GS} - V_{th})_2^2$$

$$\left(\frac{w}{L}\right)_1 (V_{GS} - V_{th})_1^2 = 2 \left(\frac{w}{L}\right)_2 (V_{GS} - V_{th})_2^2$$

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_2 (V_{GS}_2 - V_{th}_2)^2$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_2 \left(V_{GS}_1 - I_{ref} R_L - V_{th}_2 \right)^2 \rightarrow ①$$

$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_1 (V_{GS}_1 - V_{th}_1)^2 \rightarrow ②$$

$$V_{GS_1} = \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{w}{L}\right)_1}} + V_{th}$$

$$= 2 \sqrt{\frac{I_{ref}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_1}} + V_{th} \rightarrow ③$$

Substitute ③ in ①

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_2 \left[2 \sqrt{\frac{I_{ref}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_1}} + V_{th_1} - I_{ref} R_L - V_{th_2} \right]^2$$

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_2 \left[\frac{4 I_{ref}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_1} + \frac{I_{ref}^2 R_L^2}{4 I_{ref} R_L} - \frac{4 I_{ref} R_L}{\sqrt{\mu_n C_{ox} \left(\frac{w}{L}\right)_1}} \right]$$

DATE _____


$$\frac{\sqrt{2}I_{ref}}{U_n \text{Cox}(\frac{w}{L})_2} = \left(2 \sqrt{\frac{I_{ref}}{U_n \text{Cox}(\frac{w}{L})_1}} - I_{ref} R_L \right)^2$$

Taking square root both sides.

$$\sqrt{\frac{\sqrt{2}I_{ref}}{U_n \text{Cox}(\frac{w}{L})_2}} = 2 \sqrt{\frac{I_{ref}}{U_n \text{Cox}(\frac{w}{L})}} - I_{ref} R_L$$

$$I_{ref} R_L = 2 \sqrt{\frac{I_{ref}}{U_n \text{Cox}(\frac{w}{L})}} - \sqrt{\frac{\sqrt{2}I_{ref}}{U_n \text{Cox}(\frac{w}{L})}}$$
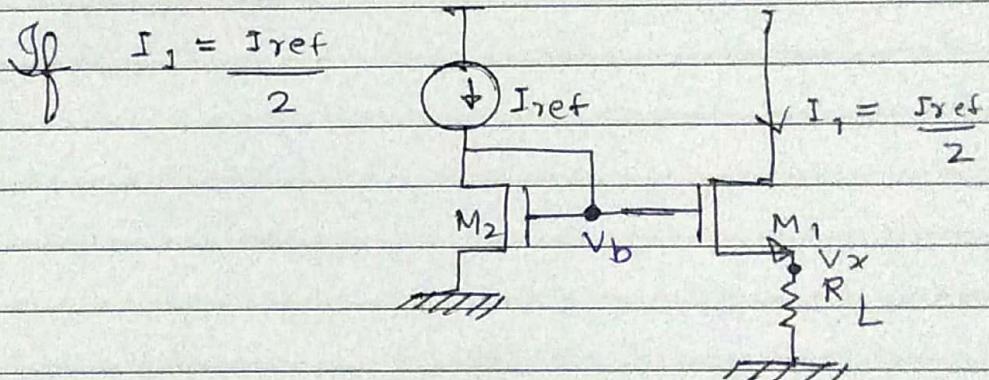
$$R_L = \frac{2 - \sqrt{2}}{\sqrt{I_{ref} U_n \text{Cox}(\frac{w}{L})}}$$



$$V_b = V_{GS2}$$

$$V_x = I_1 R_L$$

$$= \frac{I_{ref} R_L}{2}$$

$$I_1 = \frac{1}{2} U_n \text{Cox} \left(\frac{w}{L} \right)_1 \left(V_{GS1} - V_{TH} \right)^2$$

$$I_{ref} = \frac{1}{2} U_n \text{Cox} \left(\frac{w}{L} \right)_2 \left(V_{GS2} - V_{TH} \right)^2$$

$$V_{GS1} = V_b - V_x = V_{GS2} - \frac{I_{ref} R_L}{2}$$

$$V_{GS2} = \sqrt{\frac{2 I_{ref}}{U_n \text{Cox} \left(\frac{w}{L} \right)_2}} + V_{TH}$$

DATE

$$V_{GS1} = \sqrt{\frac{2I_{ref}}{\mu_n C_{ox} \left(\frac{w}{L}\right)_2}} + V_{th} - \frac{I_{ref} R_L}{2}$$

$$I_{ref} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_2$$

$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_1$$