

Network Analysis & Systems

Koshy George



Dept. of Elect. & Comm. Engineering,
PES University;
PES Centre for Intelligent Systems

UE18EC201: Network Analysis & Systems



Disclaimer (1)

- **Errors and Omissions:** The author assumes no responsibility or liability for any errors or omissions in the contents of this file. The information is provided on an “as is” basis with no guarantees of completeness, accuracy, usefulness or timeliness and without any warranties of any kind whatsoever, express or implied.
- **Breach of Confidentiality:** The information in this file are confidential and intended solely for the non-commercial use of the individual or entity to whom this file has been given, who accepts full responsibility for its use. You are not permitted to disseminate, distribute, or copy this file. If you are not the intended recipient you are notified that disclosing, copying, distributing or taking any action in reliance on the contents of this information is strictly prohibited.



Disclaimer (2)

- **Fair Use:** This file contains copyrighted material the use of which has not always been specifically authorised by the copyright owner.
- **Copyright:** No part of this file may be reproduced, stored in a retrieval system or transmitted in any form or by any means, mechanical, electronic, photocopying, recording or otherwise without the written permission of the author. Copyright ©2019 K. George. All rights reserved.




Network Analysis and Synthesis

Unit III: Network Theorems



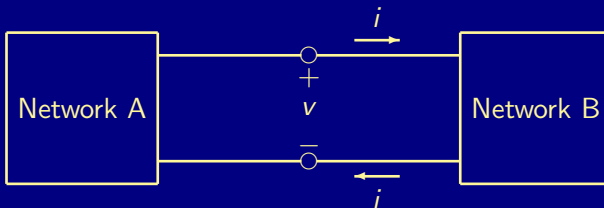Network Theorems — Thévenin and Norton (1)




- Network B is the focus of interest.
- Network A to be replaced by an equivalent network s.t. the current i and the voltage v remain invariant.



Network Theorems — Thévenin and Norton (2)

Assumptions on Network A:

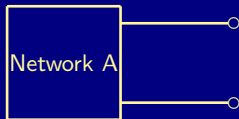

- Linear elements.
- Independent or dependent sources.
- Initial conditions on passive elements.
- No magnetic or controlled-source coupling to Network B.



Network Theorems — Thévenin and Norton (3)

Assumptions on Network B:




- Linear, nonlinear, or time-varying elements.
- Independent or dependent sources.
- Initial conditions on passive elements.
- No magnetic or controlled-source coupling to Network A.



Network Theorems — Thévenin and Norton (4)

Step A: Derive Network C from Network A

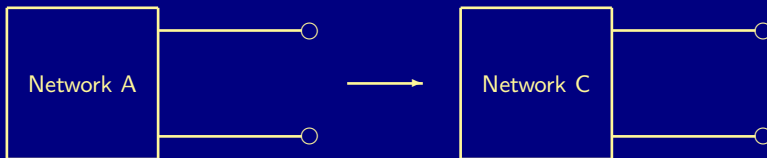


- Set all initial conditions to zero: $v_C = 0$ and $i_L = 0$.
- Turn off all independent sources: $v = 0$ (i.e., s.c.) for voltage sources and $i = 0$ (i.e., o.c.) for current sources.
- Controlled sources continue to operate.
- Determine the driving-point impedance or admittance.



Network Theorems — Thévenin and Norton (5)

Thévenin Equivalent Network:

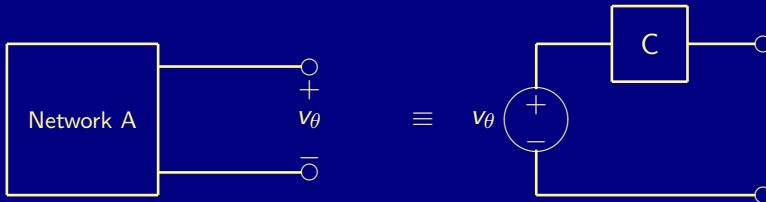


- v_θ is the voltage at the open terminals of network A with network B removed.
- v_θ is connected in series with network C.



Network Theorems — Thévenin and Norton (6)


Norton Equivalent Network:

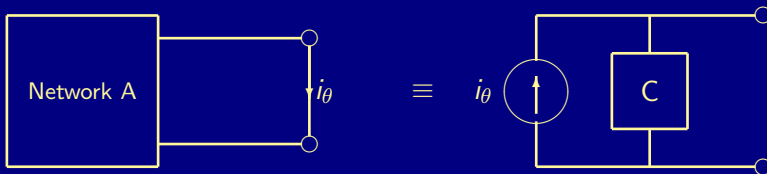

- i_θ is the current in the shorted terminals of network A with network B removed.
- i_θ is connected in parallel with network C.



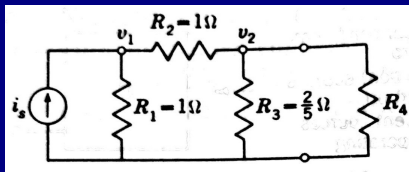
Network Theorems — Thévenin and Norton (7)



Source: Van Valkenburg, 1975.



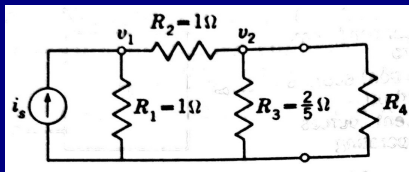Network Theorems — Thévenin and Norton (7)




Source: Van Valkenburg, 1975.

- Find $v_\theta = v_2$: Apply nodal analysis to obtain



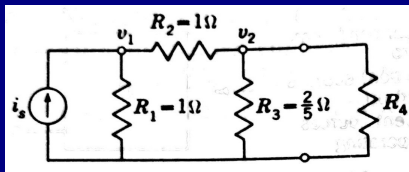Network Theorems — Thévenin and Norton (7)




Source: Van Valkenburg, 1975.

- Find $v_\theta = v_2$: Apply nodal analysis to obtain $v_2 = i_s/6$.
- Find R_θ after open circuiting the current source:



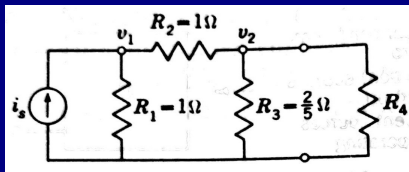Network Theorems — Thévenin and Norton (7)




Source: Van Valkenburg, 1975.

- Find $v_\theta = v_2$: Apply nodal analysis to obtain $v_2 = i_s/6$.
- Find R_θ after open circuiting the current source: $R_\theta = 1/3$.



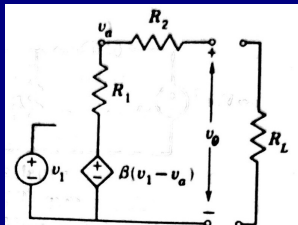Network Theorems — Thévenin and Norton (8)




■ Find v_θ :

Source: Van Valkenburg, 1975.



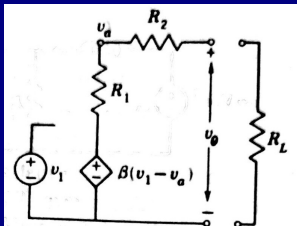Network Theorems — Thévenin and Norton (8)




- Find v_θ : Clearly, $v_\theta = v_a = \beta(v_1 - v_a)$. Therefore,

Source: Van Valkenburg, 1975.



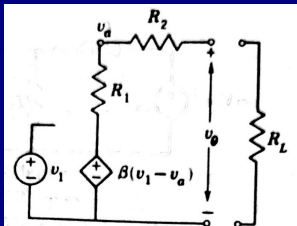Network Theorems — Thévenin and Norton (8)




- Find v_θ : Clearly, $v_\theta = v_a = \beta(v_1 - v_a)$.
Therefore, $v_\theta = \frac{\beta}{1+\beta} v_1$.
- Find R_θ :

Source: Van Valkenburg, 1975.




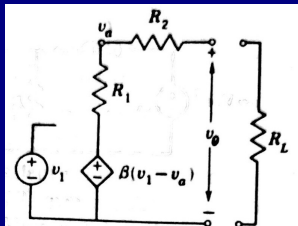Network Theorems — Thévenin and Norton (8)



- Find v_θ : Clearly, $v_\theta = v_a = \beta(v_1 - v_a)$.
Therefore, $v_\theta = \frac{\beta}{1+\beta} v_1$.
- Find R_θ : Set $v_1 = 0$ and connect a voltage source v to the output terminals.


Source: Van Valkenburg, 1975.

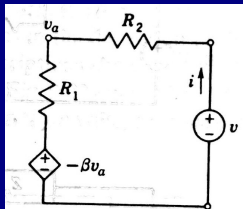

- For the loop,




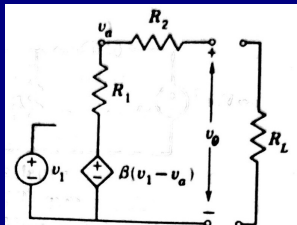Network Theorems — Thévenin and Norton (8)



- Find v_θ : Clearly, $v_\theta = v_a = \beta(v_1 - v_a)$. Therefore, $v_\theta = \frac{\beta}{1+\beta} v_1$.
- Find R_θ : Set $v_1 = 0$ and connect a voltage source v to the output terminals.

Source: Van Valkenburg, 1975.

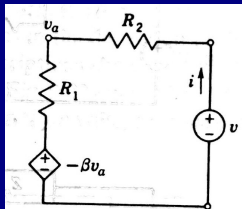


- For the loop,
 $v = iR_2 + v_a = iR_2 + iR_1 - \beta v_a$.
- Therefore,

$$v = i \left(R_2 + R_1 \left(1 - \frac{\beta}{1+\beta} \right) \right)$$



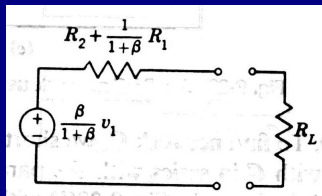Network Theorems — Thévenin and Norton (9)



Thus,


$$v_\theta = \frac{\beta}{1+\beta} v_1$$

and

$$R_\theta = R_2 + R_1 \left(1 - \frac{\beta}{1+\beta} \right) = R_2 + R_1 \frac{1}{1+\beta}$$



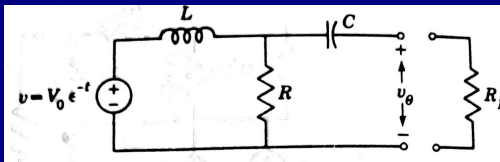Network Theorems — Thévenin and Norton (10)




Source: Van Valkenburg, 1975.

■ Find $V_\theta(s)$:



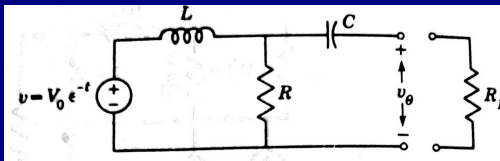Network Theorems — Thévenin and Norton (10)



Source: Van Valkenburg, 1975.


- Find $V_{\theta}(s)$: Clearly,

$$V_{\theta}(s) = \frac{R}{Ls + R} V(s) = \frac{V_0 R}{(Ls + R)(s + 1)}$$

- Find Z_{θ} :



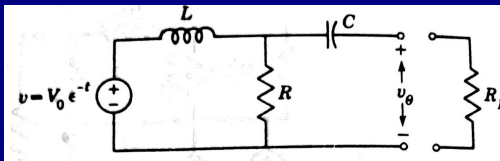Network Theorems — Thévenin and Norton (10)



Source: Van Valkenburg, 1975.

- Find $V_\theta(s)$: Clearly,


$$V_\theta(s) = \frac{R}{Ls + R} V(s) = \frac{V_0 R}{(Ls + R)(s + 1)}$$

- Find Z_θ :

$$Z_\theta(s) = \frac{1}{Cs} + \frac{1}{\frac{1}{R} + \frac{1}{Ls}} = \frac{R(s^2 + (1/RC)s + (1/LC))}{s(s + (R/L))}$$



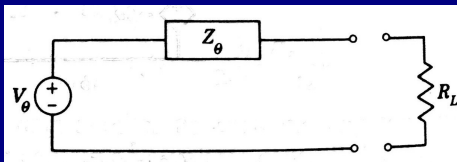Network Theorems — Thévenin and Norton (11)




$$V_{\theta}(s) = \frac{V_0 R}{(Ls + R)(s + 1)}$$

$$Z_{\theta}(s) = \frac{R(s^2 + (1/RC)s + (1/LC))}{s(s + (R/L))}$$



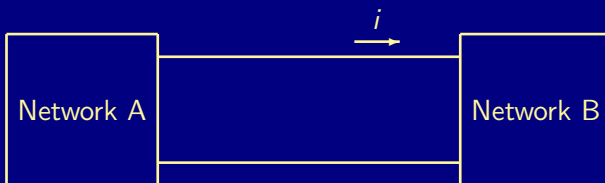
Network Theorems — Thévenin and Norton (12)



- The current $i(t)$ (or, $I(s)$) flows into Network B.



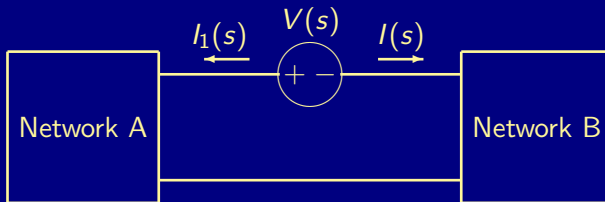
Network Theorems — Thévenin and Norton (13)



- Include a voltage source $V(s)$ so that the resulting current $I_1(s)$ is such that $I_1(s) = -I(s)$.
- Therefore, the net current flowing into network B is zero.



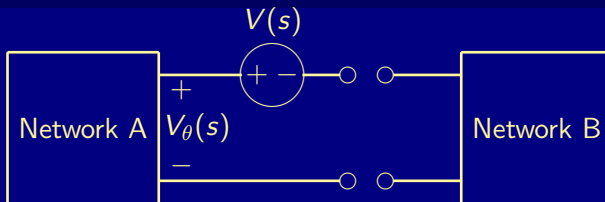
Network Theorems — Thévenin and Norton (13)



- Since the net current flowing into network B is zero, the two networks can be broken without affecting the conditions in network A.
- The voltage at the broken terminals is clearly zero.
- Also, the network B can be shorted.
- By KVL, $V_{\theta}(s) = V(s)$.
- That is, the open circuit voltage at the terminals is $V(s)$.



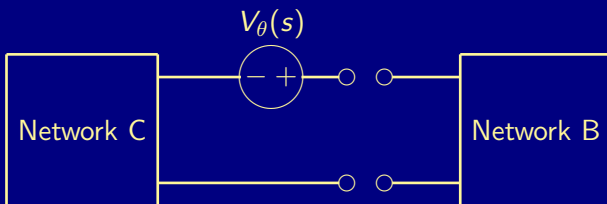
Network Theorems — Thévenin and Norton (14)



- All independent sources are reduced to zero.
- Dependent sources are not changed.
- Thus network A is transformed into network C.
- The polarity of the source $V_{\theta}(s)$ is reversed so that when connected, the current $I(s)$ will flow into network B.



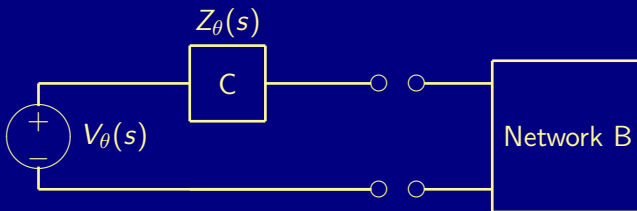Network Theorems — Thévenin and Norton (15)




- Impedance of C is $Z_{\theta}(s)$; the voltage source is $V_{\theta}(s)$.
- If A has only independent sources, then $Z_{\theta}(s)$ is the impedance of the passive network; otherwise, $Z_{\theta}(s)$ must be determined for the active network.
- This is the Thévenin equivalent network.
- If $Z_B(s)$ is the impedance of B, then the current is

$$I(s) = \frac{V_{\theta}(s)}{Z_{\theta}(s) + Z_B(s)}$$



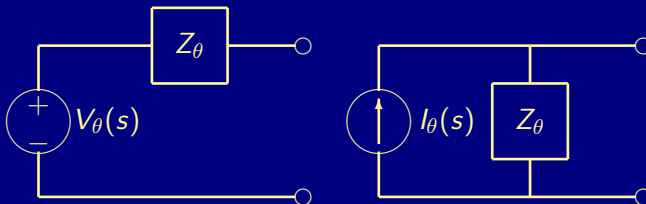Network Theorems — Thévenin and Norton (16)



- Perform source transformation to obtain the current source

$$I_{\theta}(s) = \frac{V_{\theta}(s)}{Z_{\theta}(s)}$$


- This is the Norton equivalent network.
- The voltage of network B is

$$V_B(s) = \frac{I_{\theta}(s)}{Y_{\theta}(s) + Y_B(s)}$$





Examples (1)

Example 6, Van Valkenburg, pp. 267–268:

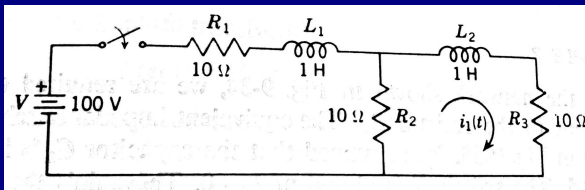


Examples (1)

Example 6, Van Valkenburg, pp. 267–268:

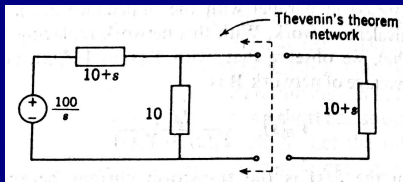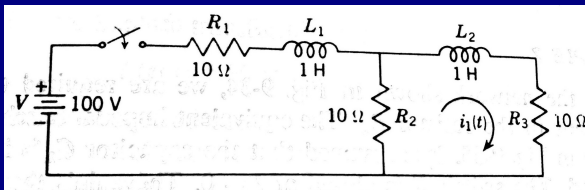


Examples (2)

Example 7, Van Valkenburg, pp. 268–269:

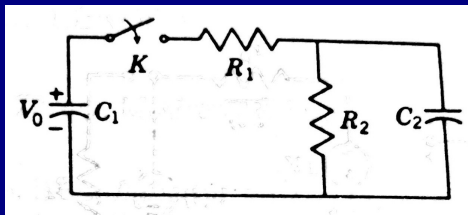

Examples (2)

Example 7, Van Valkenburg, pp. 268–269:

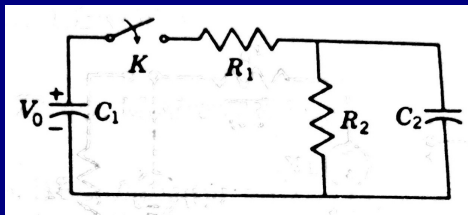

Examples (3)

Example 8, Van Valkenburg, p. 270:

