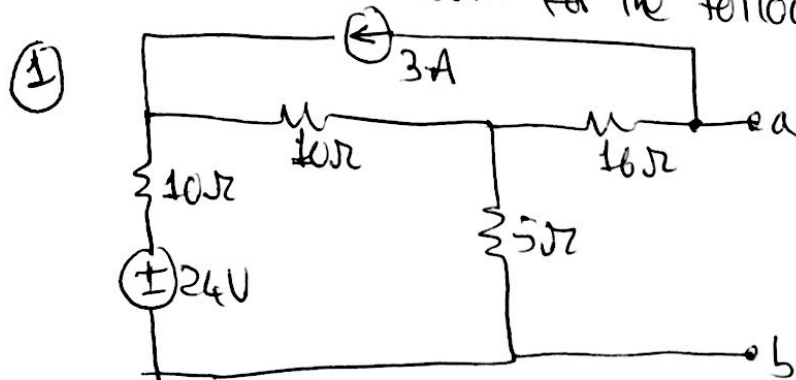


NAS(UE18EC201)  
3rd SEM - Practice Problems  
for MODULE 3 - NETWORK THEOREMS


NAME:- PRAHLAD.D.  
(Faculty)

Date:- 28-10-2019


① Obtain Thevenin's and Norton's equivalent circuits at terminals a-b of the circuit shown. For the following circuits:-



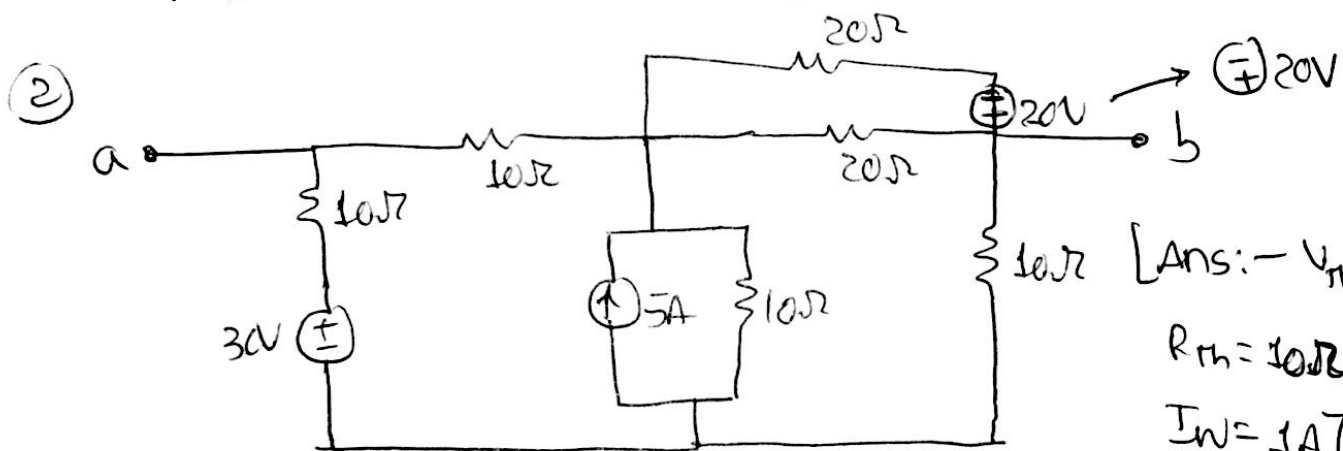
[Ans:-  $V_{th} = -49.2V$   
 $R_{th} = 20\Omega$   
 $I_N = -2.46A$ ]



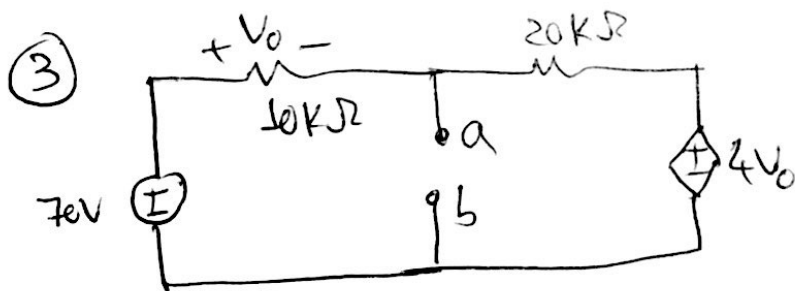
[Ans:-  $V_{th} = 1eV$   
 $R_{th} = 10\Omega$   
 $I_N = 1A$ ]



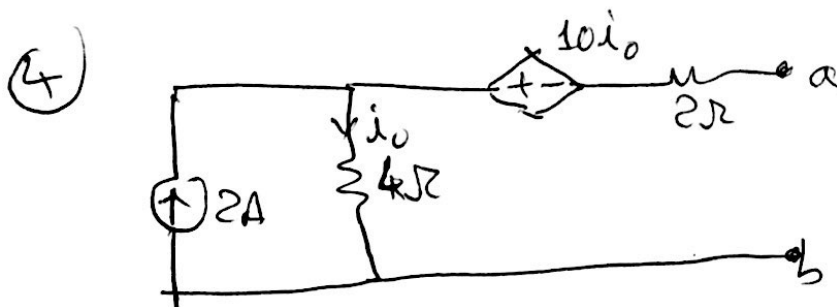[Ans:-  $R_{th} = 2.857k\Omega$   
 $V_{th} = 60V$   $I_N = 21mA$ ]




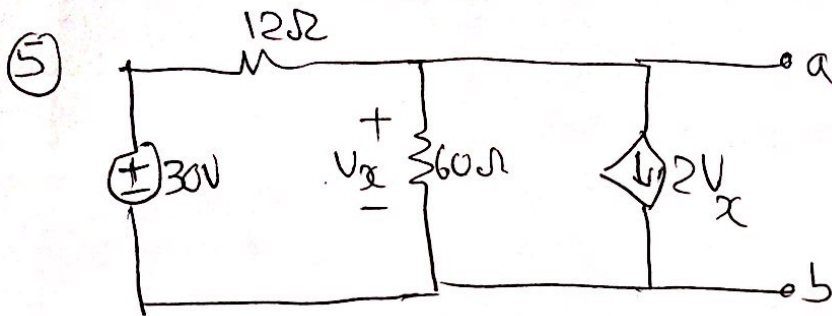[Ans:-  $R_{th} = -4\Omega$   
 $V_{th} = -12V$   
 $I_N = 3A$ ]




[Ans: -  $V_{th} = 1.19V$   
 $R_{th} = R_N = 0.476\Omega$   
 $I_N = 2.5A$ ]

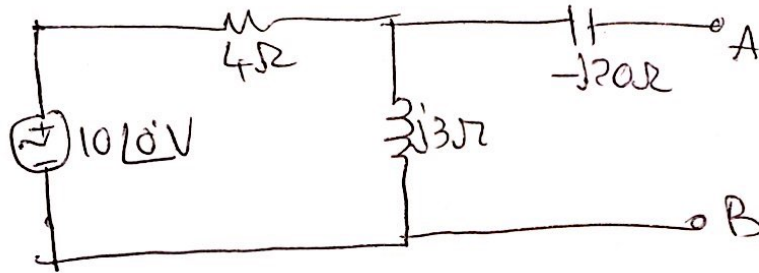⑥ Calculate the current through a load of  $(6+j3)\Omega$  connected b/w A and B, after finding Thevenin's and Norton's eq. ckt.



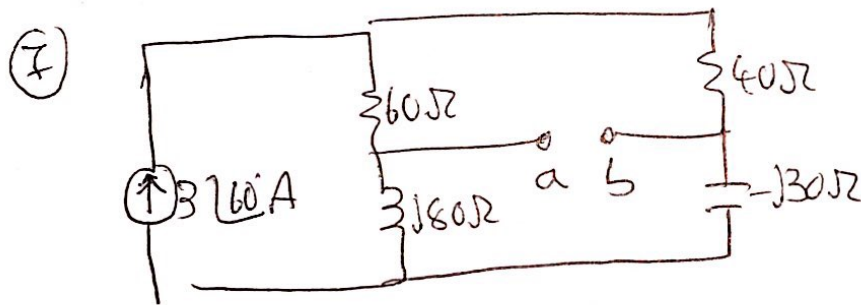
[Ans: -  $Z_{th} = (1.44 - j18.1)\Omega$   
 $V_{th} = (3.6 + j4.8)V$ ]



[Ans: -  $Z_{th} = (20 + j4)\Omega$   
 $I_N = 3\angle60^\circ A$ ]

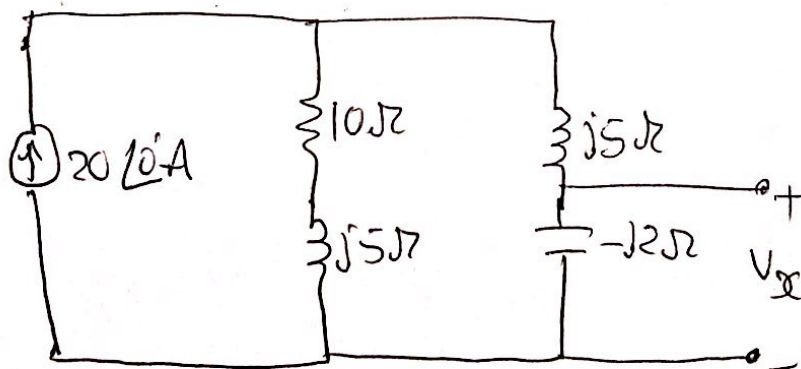
## II Reciprocity and Tellegen's Theorems: and Millman's Theorem

① Verify Reciprocity Theorem for the following circuit.




[Ans: -  
 $V_x = 34.92 \angle -12.09^\circ$ ]

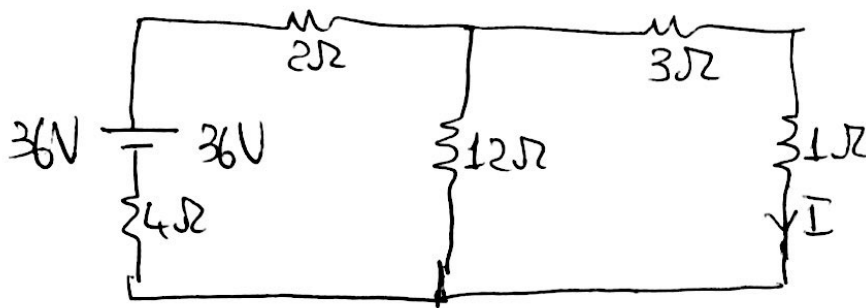② Verify Reciprocity Theorem for the circuit shown.



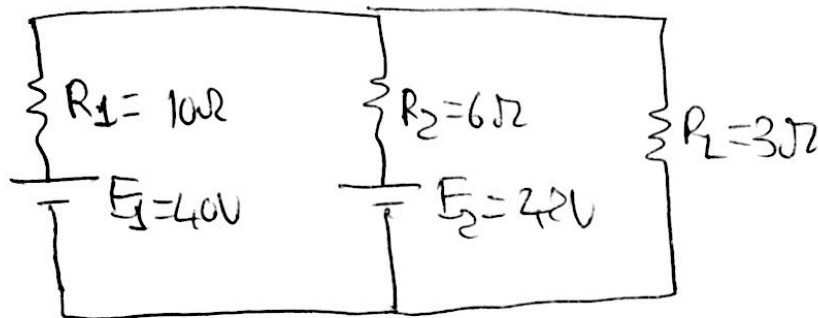③ Using Millman's theorem find the current and voltage across  $R_L$ .




[Ans: -

$$I_L = 6.111 \text{ A}$$


$$V_L = 18.33 \text{ V}]$$

④

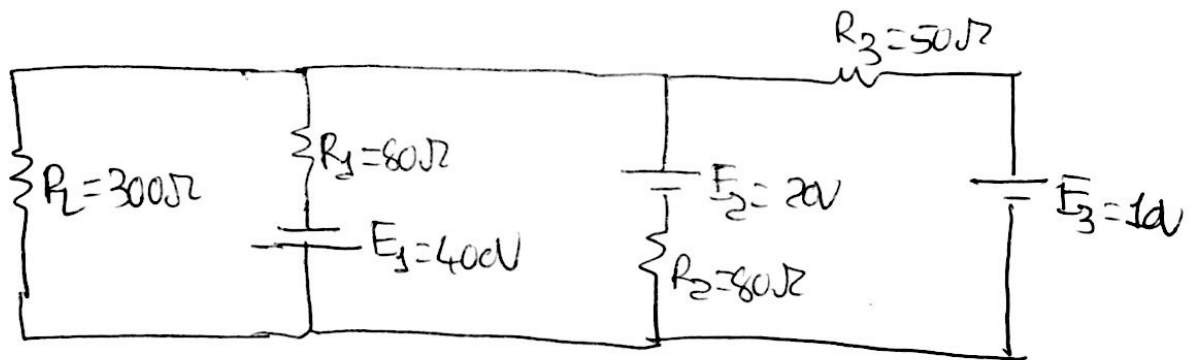

[Ans: -  $I_L = -0.3137 \text{ A}$   
 $V_L = -94.1368 \text{ V}$ ]

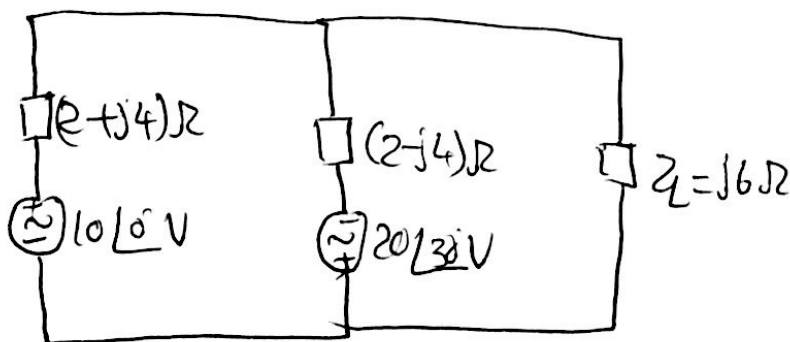⑤ Using Millman's theorem calculate the voltage (V) across a load of  $Z_L = j6\Omega$ , and current through it.




[Ans: -

$$V_L = 3.35 \angle 177^\circ \text{ V}$$

$$I_L = 0.56 \angle 87^\circ \text{ A}]$$


③

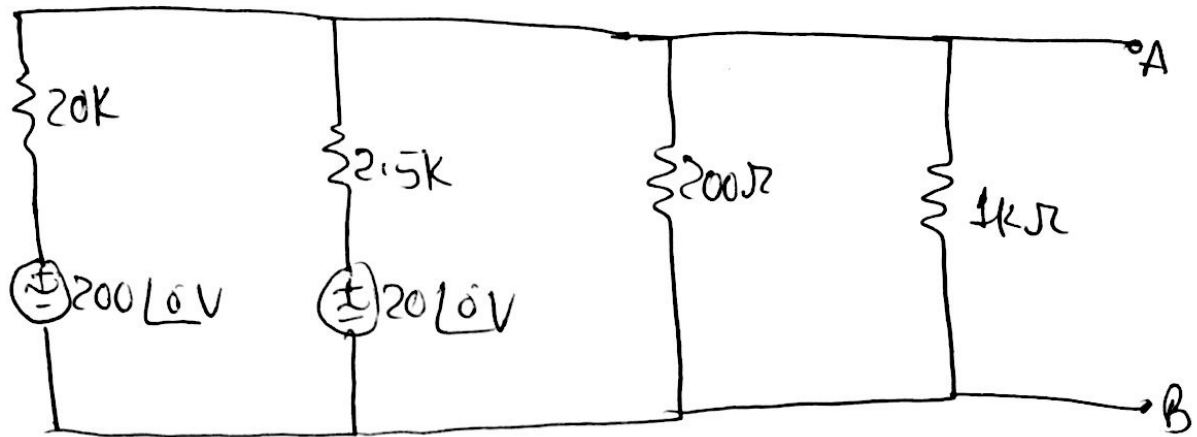3] Using Millman's theorem find the voltage across  $1k\Omega$  resistor




[Ans: -2.79V]

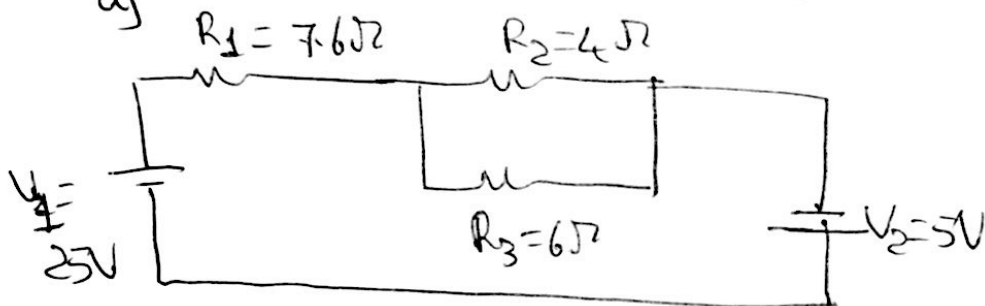4] a) Verify Tellegen's theorem for the circuit shown.




b) Verify Tellegen's theorem for n/w

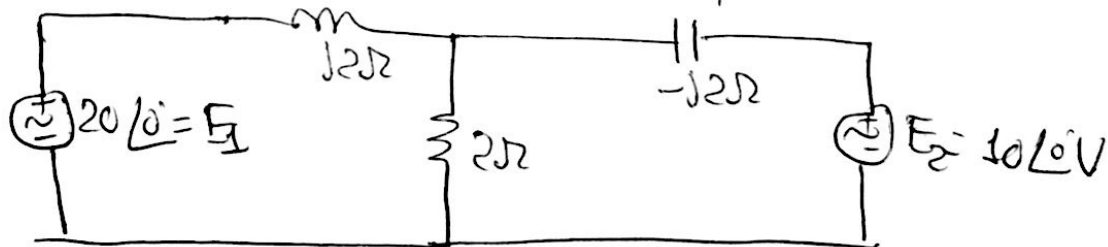


5] Find the average power delivered to  $Z_L = (8 - j11)\Omega$  by a current  $I = 5\angle 20^\circ$  A. [Ans: - $P_{av} = 100$ W]

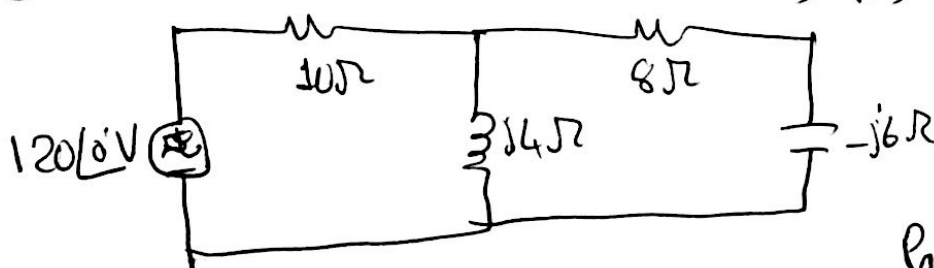6] For the circuit shown find  $Z$ , PF,  $I_{rms}$ , and  $P_{av}$ .




[Ans: -  $Z = 12.7\angle 20.61^\circ \Omega$   
 $I_{rms} = 9.448\angle -20.61^\circ$  A  
 $P_{av} = 1.06129$  kW]

⑦ verify Tellegen's theorem for the ckt.

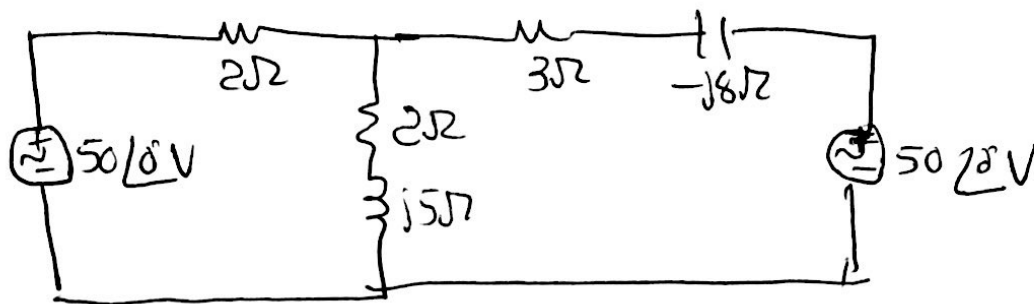
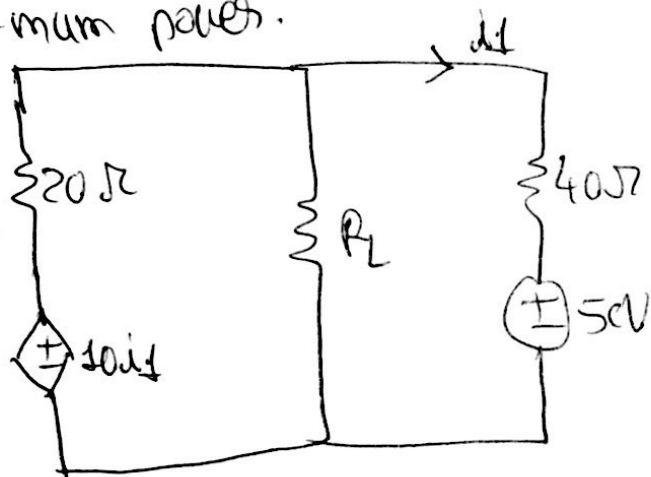
## Superposition Theorem and Maximum Power Transfer Theorem


① Determine  $R_L$  for maximum power transfer, and find max. -mum power.



[Ans: -  $R_L = 16\Omega$

$P_{Lmax} = 1.5625W$

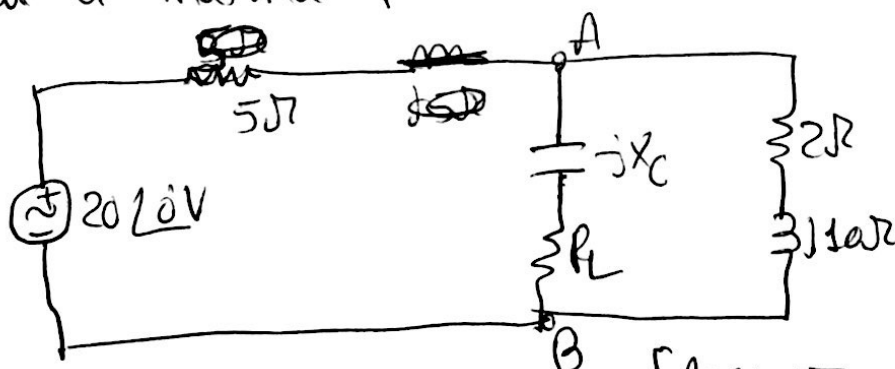② For the circuit shown find the value of  $R_L$  and capacitive reactance  $X_C$  that would result in maximum power transfer. Find the value of maximum power.



[Ans: -  $Z_{th} = (3.7 + j1.6)\Omega$

$V_{th} = 41.8 \angle 68.7^\circ V$

$Z_L = (3.7 - j1.6)\Omega$   $X_C = 1.6\Omega$


⑤

③ Find  $R_L$  for max. power transfer, and find  $P_{max}$




[Ans:-  $R_L = 11.39\Omega$   
 $P_{Lmax} = 0.712W$ ]

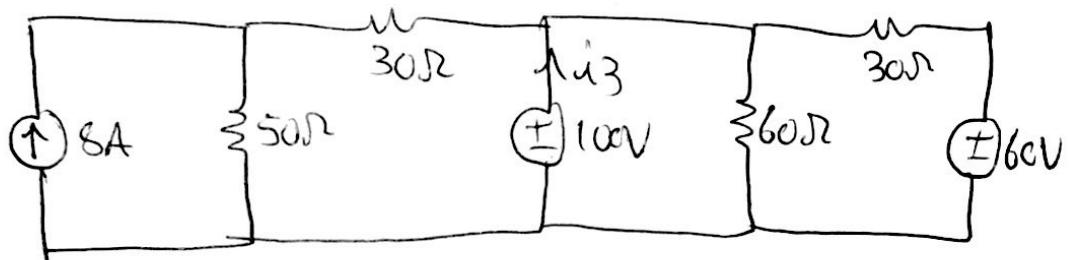④ For circuit shown find the current  $i_3$  using superposition theorem.



[Ans:-  $i_{31}(8A) = -5A$ ,  $i_{32}(100V) = 6.25A$   
 $i_{33}(60V) = -2A$ ;  $i_3(\text{total}) = -0.75A$ ]

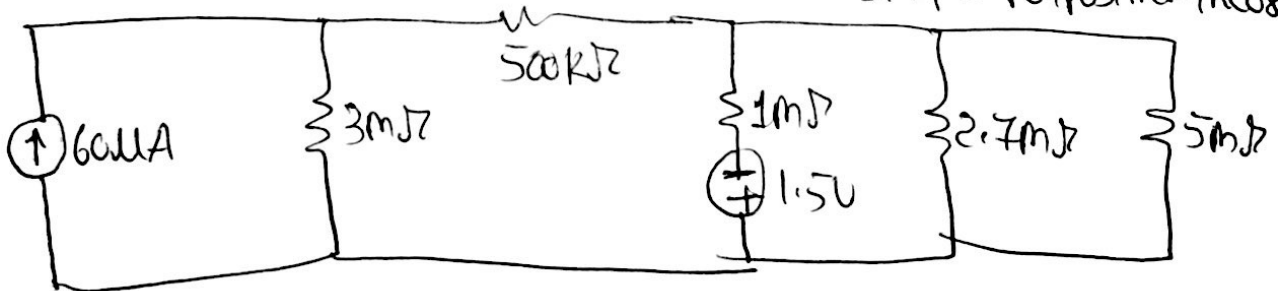⑤ Find power dissipated by  $500k\Omega$  resis. using superposition theorem.




[Ans:-  $I_1(60\mu A) = 43.51\mu A$ ;  $I_2(1.5V) = 0.2308\mu A$   
 $P_{500k} = 956.6\mu W$ ]



⑥ Find  $V_x$  using superposition, if  $V_s = 50 \sin 2t$  and
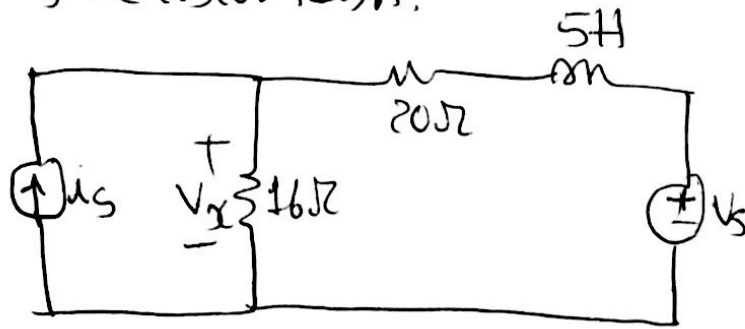
$$i_s = 12 \cos(6t + 10^\circ) \text{ A}$$



[Ans:— Find the ~~impedance~~ <sup>impedance</sup> value of  $L$  corresponding to  $\omega = 2$  for  $V_s$ .


$$\therefore V_x(V_s) = 21.41$$

$$\sin(2t - 15.52^\circ) \text{ V}$$

next Find impedance value of  $L$  corresponding to  $\omega = 6$  for  $i_s$   
 $V_x(i_s) [V_x \text{ due to } i_s] = 147.7 \cos(6t + 26.5^\circ) \text{ V}$

$$\therefore V_x = V_x(\text{due to } i_s) + V_x(\text{due to } V_s)$$

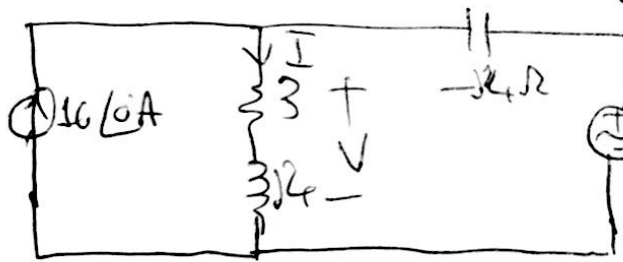
⑦ For the circuit shown find  $V$  using superposition theorem.



[Ans:—  
 $V'(\text{due to } 10/0^\circ \text{ A})$   
 $= (53.3 - j40) \text{ V}$

$$V''(50/90^\circ \text{ V}) = (-66.7 + j50) \text{ V} \quad V = V' + V''$$

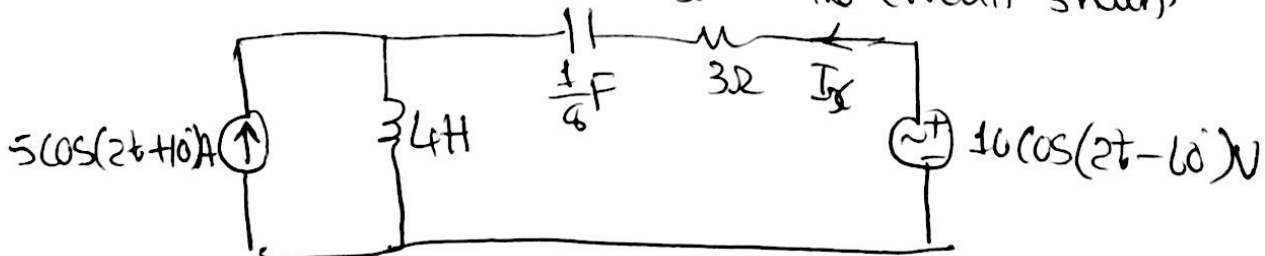⑧ Using superposition find  $I_x$  in the circuit shown.



$$[Ans:— I_x(\text{due to } 10/-60^\circ \text{ V}) = \frac{10 \angle -60^\circ}{3 + j4}$$

$$I_x(\text{due to } 5 \angle 10^\circ \text{ A}) = \frac{-j40 \angle 10^\circ}{3 + j4} \quad \text{total } I_x = 9.902 \angle -129.17^\circ$$

$$I_x = 9.902 \cos(2t - 129.17^\circ) \text{ A} \quad (7)$$