
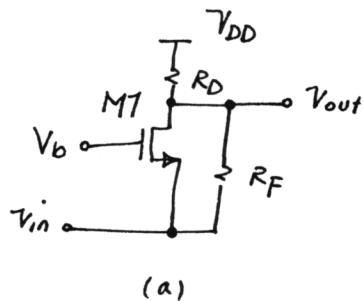
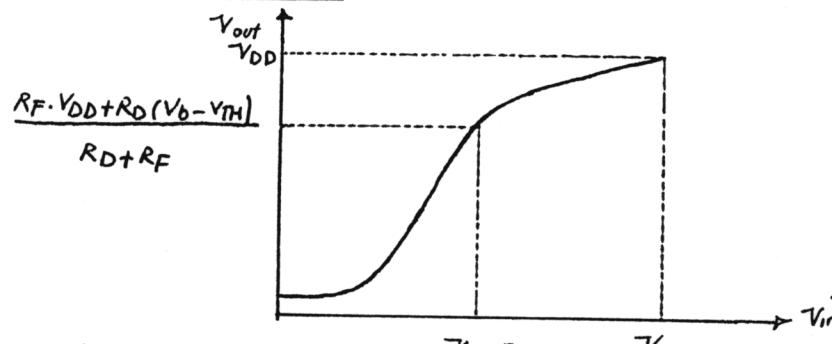
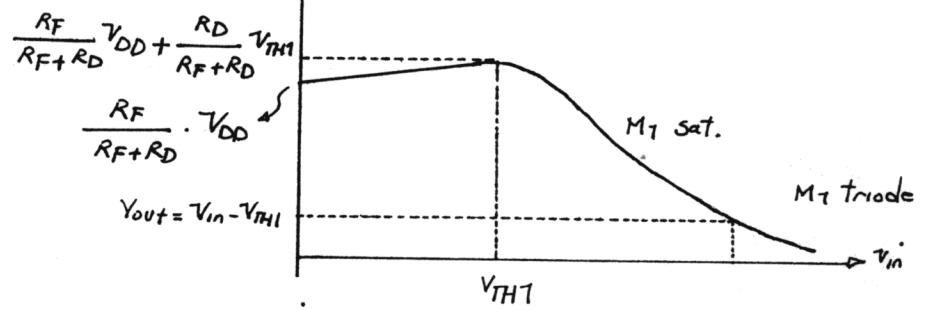





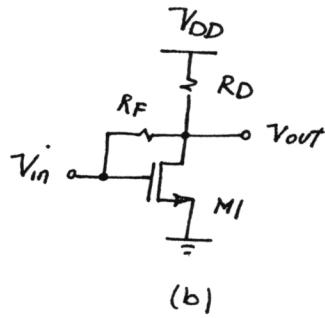
3.1.

Chapter 3



We assume that  $M_1$  is saturated when  $V_{in} = 0$


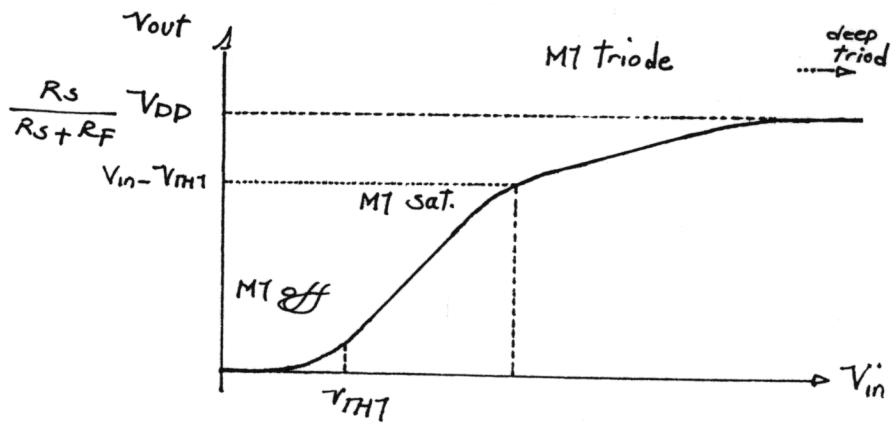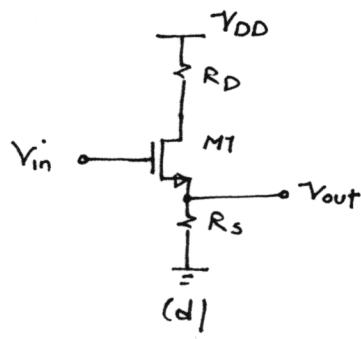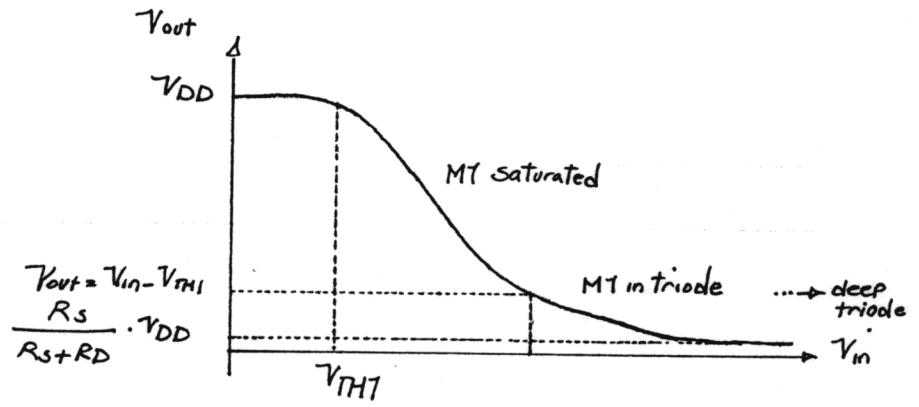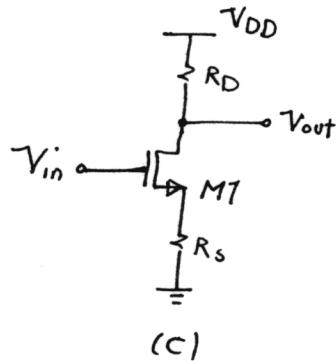
$$\text{if } V_{in} < V_{TH} \rightarrow V_{out} = \frac{R_F}{R_F + R_D} V_{DD} + \frac{R_D}{R_F + R_D} V_{in}$$







3.2



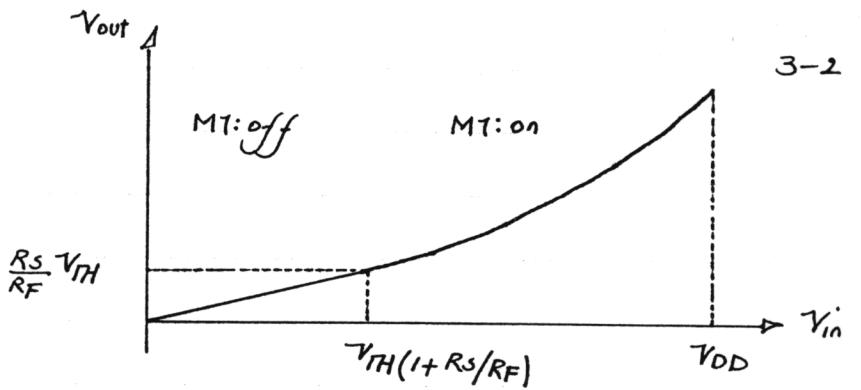
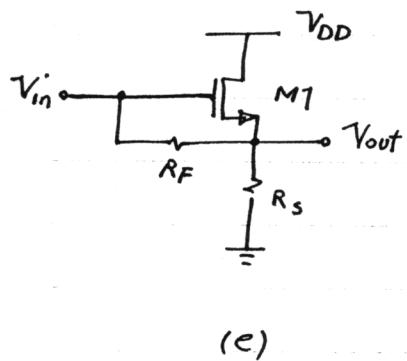


$$\text{if } V_{in} < (1 + R_S / R_F) V_H \rightarrow V_o = \frac{R_S}{R_S + R_F} V_{in}$$



3.2.

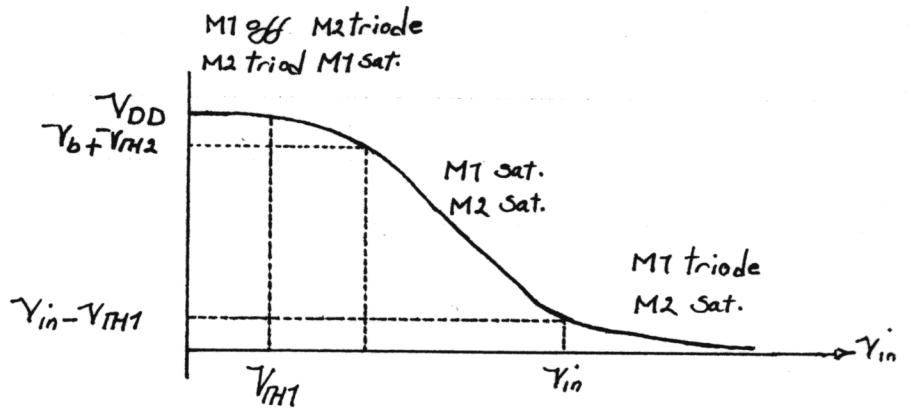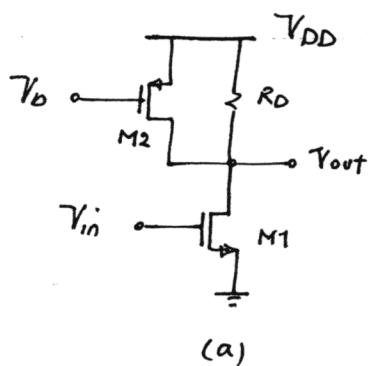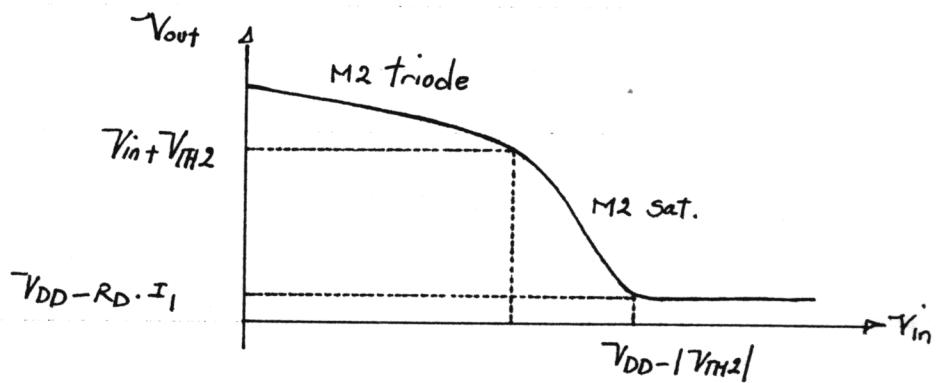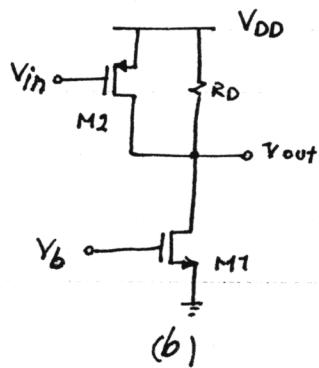


3-3

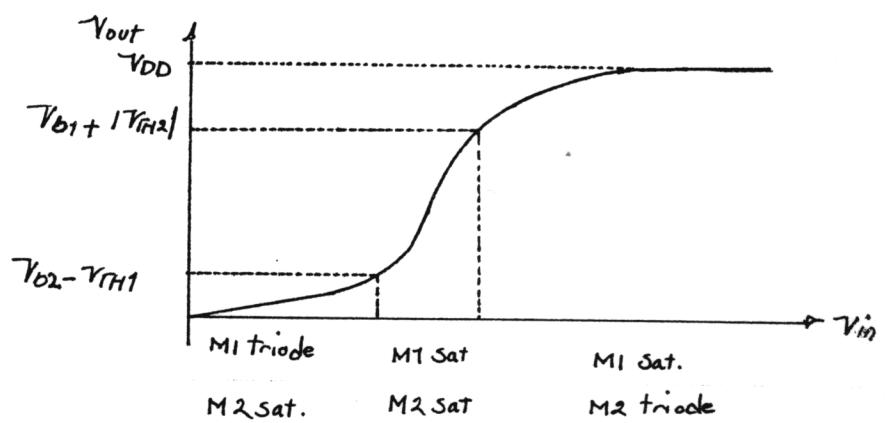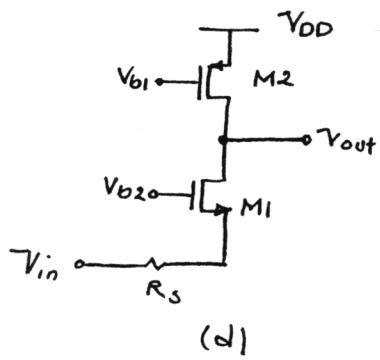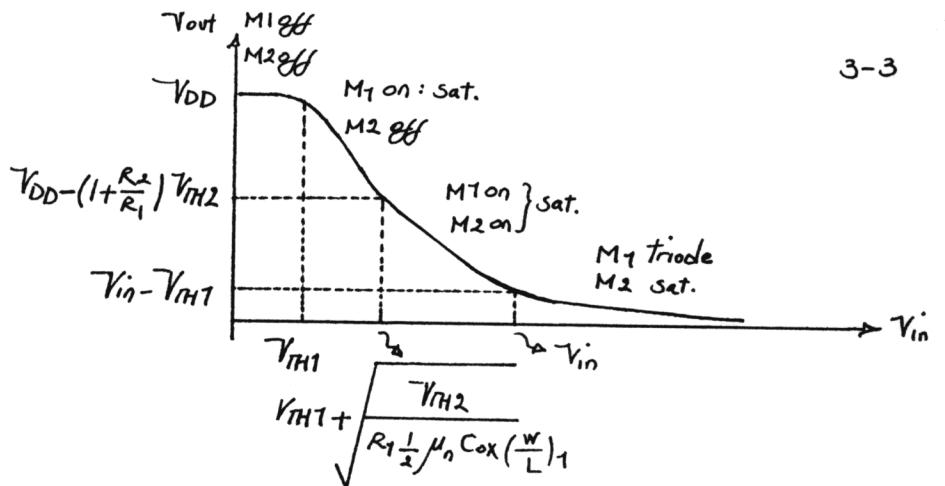
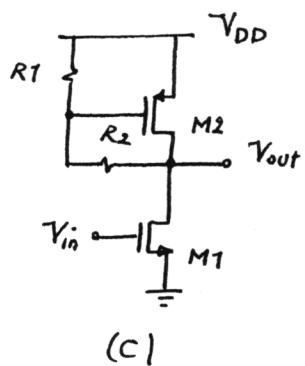


3.2.

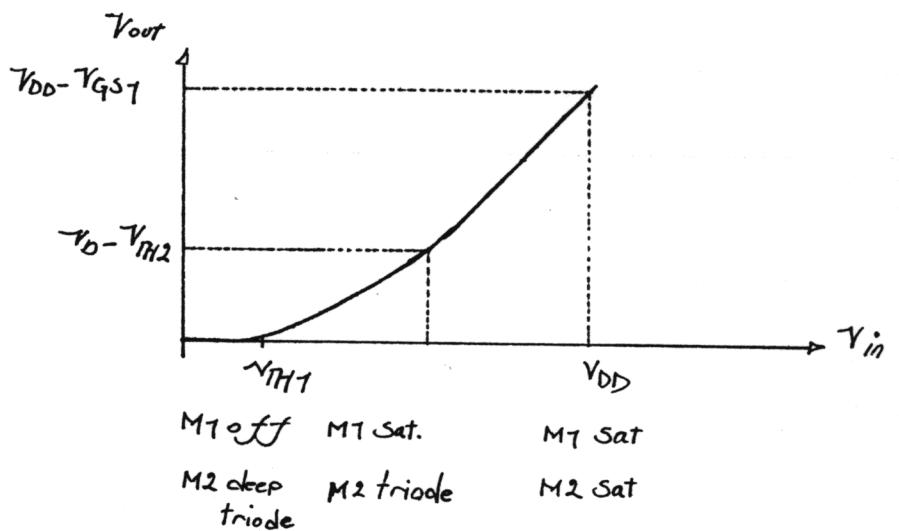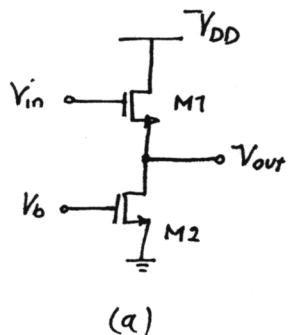


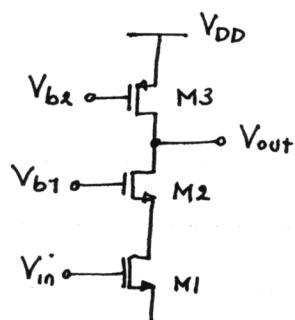


(b)

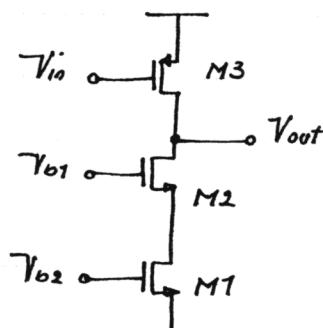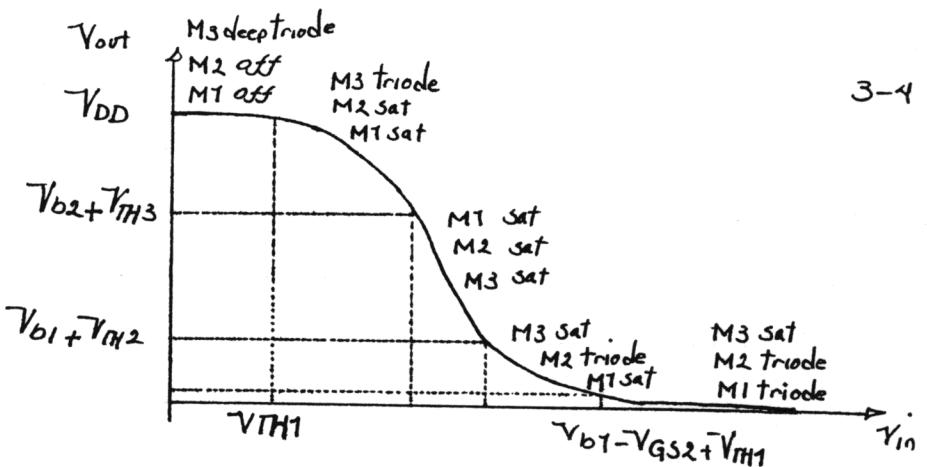


(c)

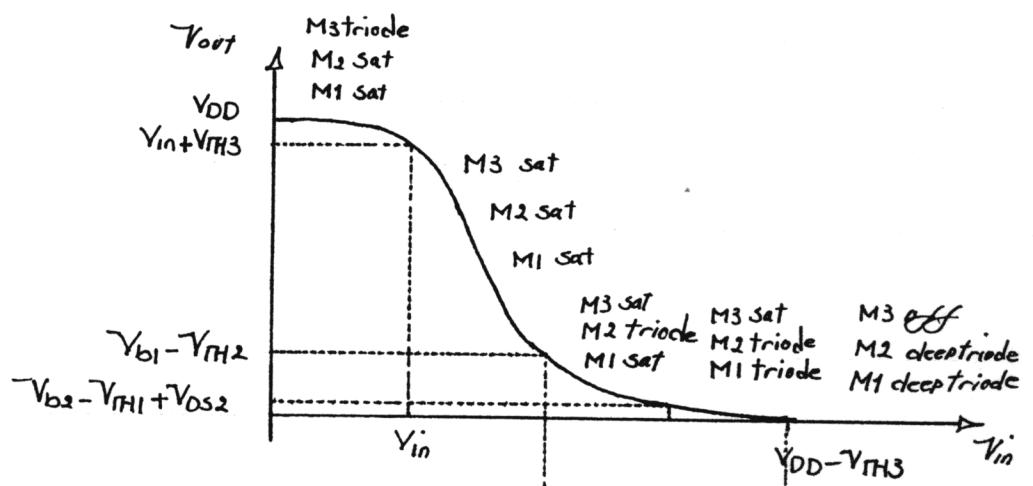

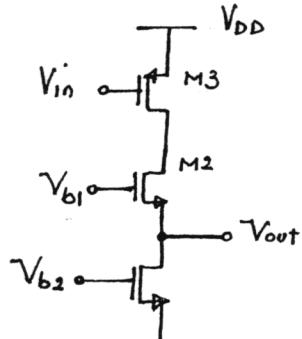
$$V_{DS2} \text{ is obtained from } \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b2} - V_{TH1})^2 = \mu_n C_{ox} \left( \frac{W}{L} \right)_2 \left[ (V_{b1} - V_{b2} + V_{TH1} - V_{TH2}) V_{DS2} - \frac{V_{DS2}}{2} \right]$$



(d)



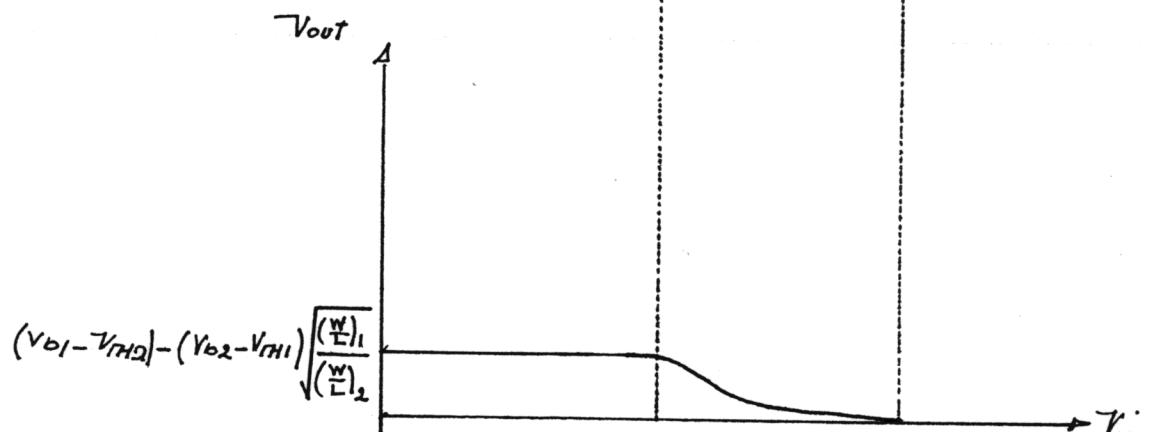


3.3.

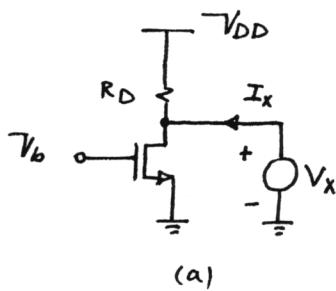

$$V_x^* = V_{DD} - R_D \left( \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_b - V_{TH1})^2 \right)$$

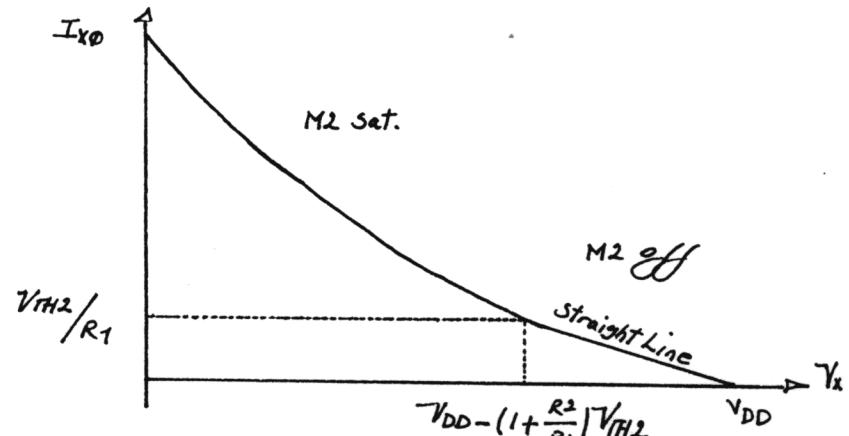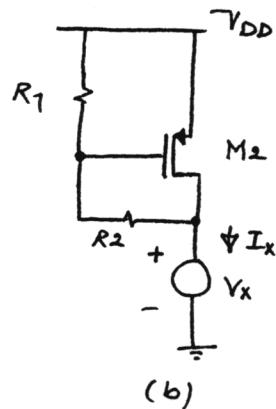
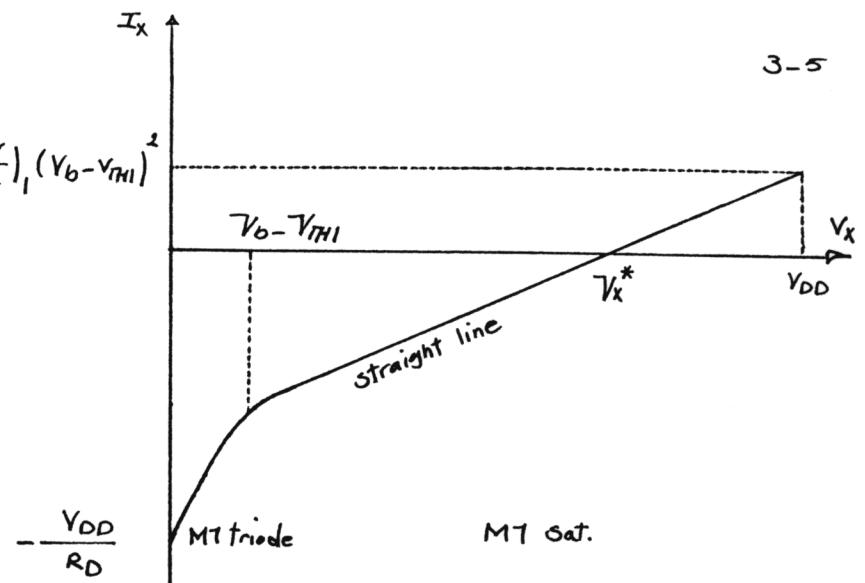
$$\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_b - V_{TH1})^2$$



$\mathcal{F} \quad V_x < V_{DD} - (1 + \frac{R_2}{R_1})V_{TH2}$

$$I_x = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 \left( \frac{(V_{DD} - V_x)}{R_1 + R_2} \cdot R_1 - V_{TH2} \right)^2 + \frac{V_{DD} - V_x}{R_1 + R_2}$$

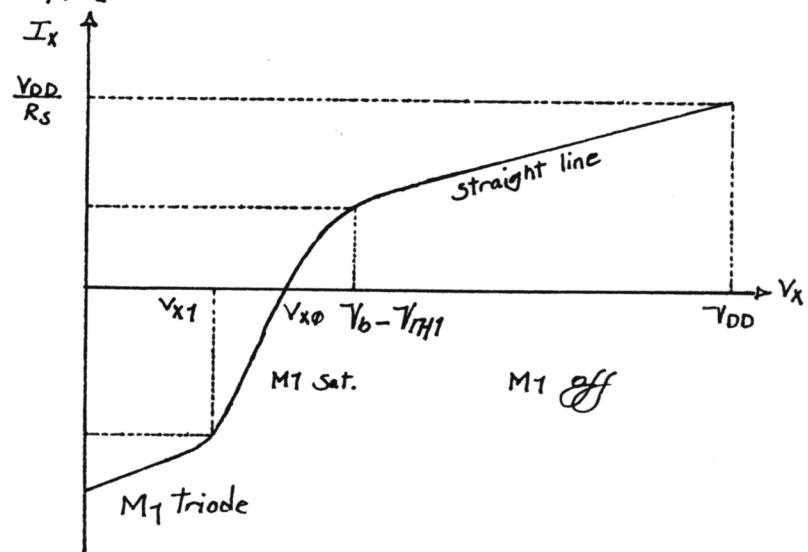
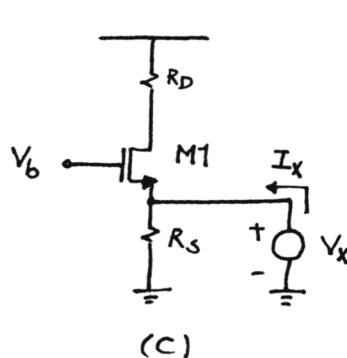
$\mathcal{F} \quad V_x > V_{DD} - (1 + \frac{R_2}{R_1})V_{TH2}$





$$V_{X0} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_b - V_{TH1})^2 \cdot R_D$$

$$-V_{XT} = V_b - V_{TH1} - \left( \frac{2(V_{DD} - V_b + V_{TH1})}{\mu_n C_{ox} \left( \frac{W}{L} \right)_1 \cdot R_D} \right)^{1/2}$$


3.4.

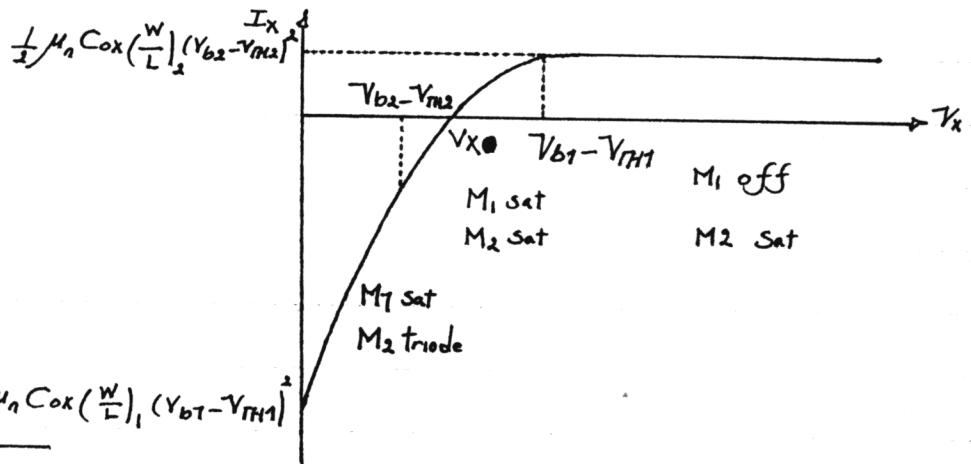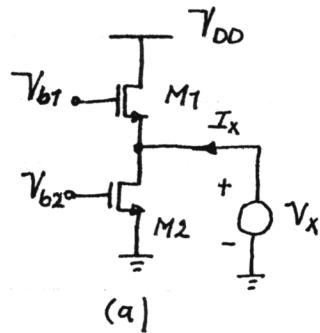

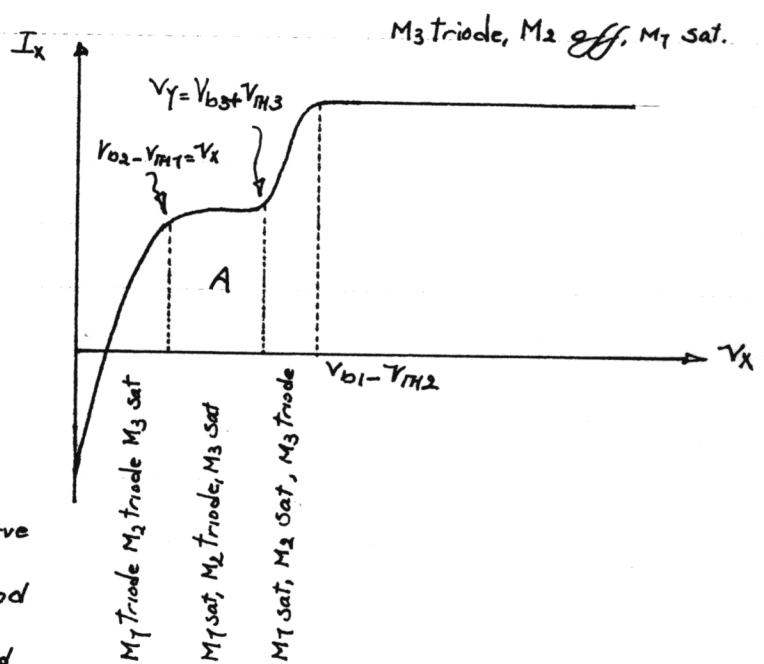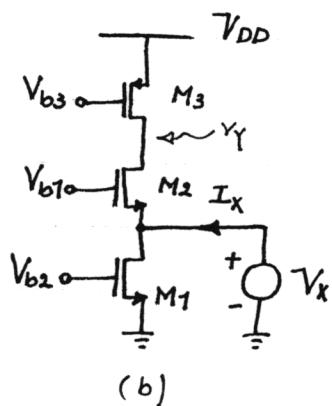
$$V_{X0} = V_{b1} - V_{TH1} - \sqrt{\frac{\left( \frac{W}{L} \right)_2}{\left( \frac{W}{L} \right)_1} (V_{b2} - V_{TH2})}$$



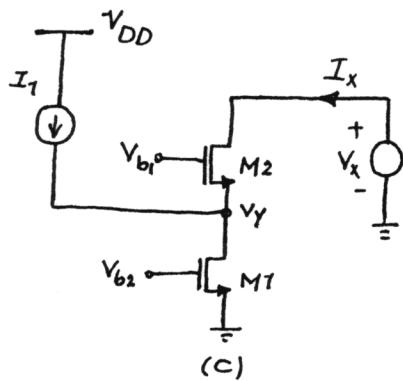
It's worth mentioning that the  $I_x/V_x$  Curve varies with the value of bias voltages and aspect ratios, therefore, some region(s), based on the aforementioned parameters, gets wider or narrower, especially the region called "A" in the above figure.





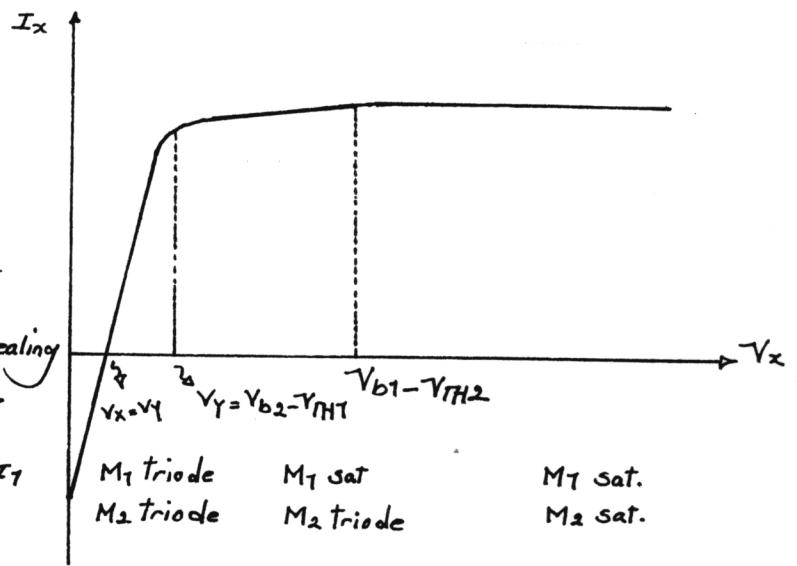
we assume  $V_{b1} > V_{be}$  and both  $M_1$  and  $M_2$  operate in saturation  
region if  $V_x = V_{DD}$





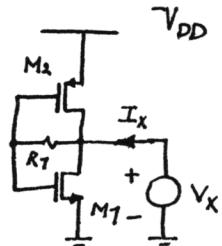Below  $V_x$ , for which  $V_x = V_Y$ , drain current of  $M_2$  flows in opposite direction, revealing the fact the drain and source terminals of  $M_2$  are reversed. As expected, most of  $I_1$  flow through  $M_2$  when  $V_x = 0$ , because we assume that  $V_{b1} > V_{b2}$ .




(d)

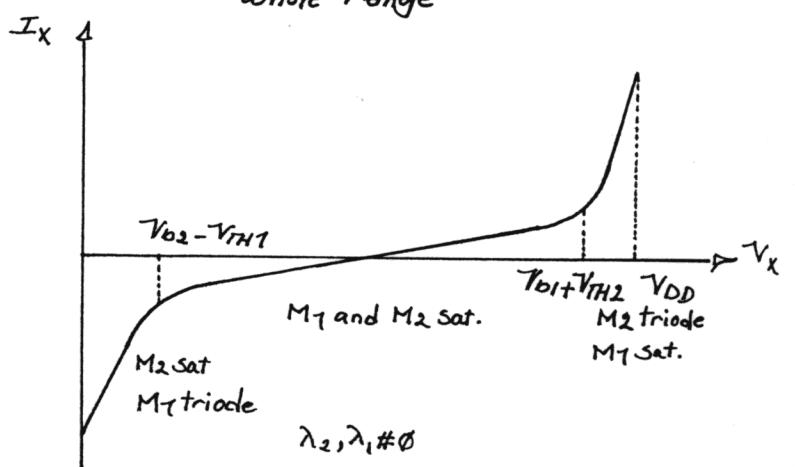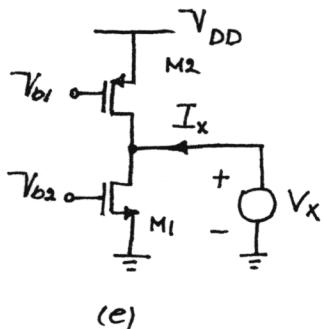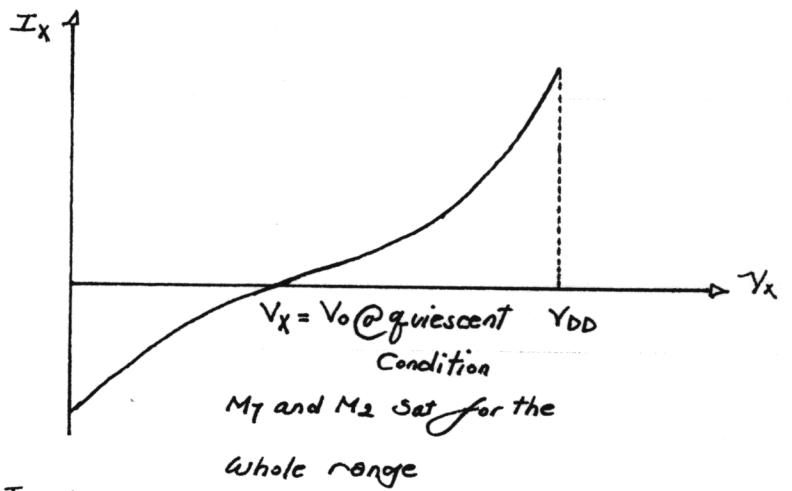

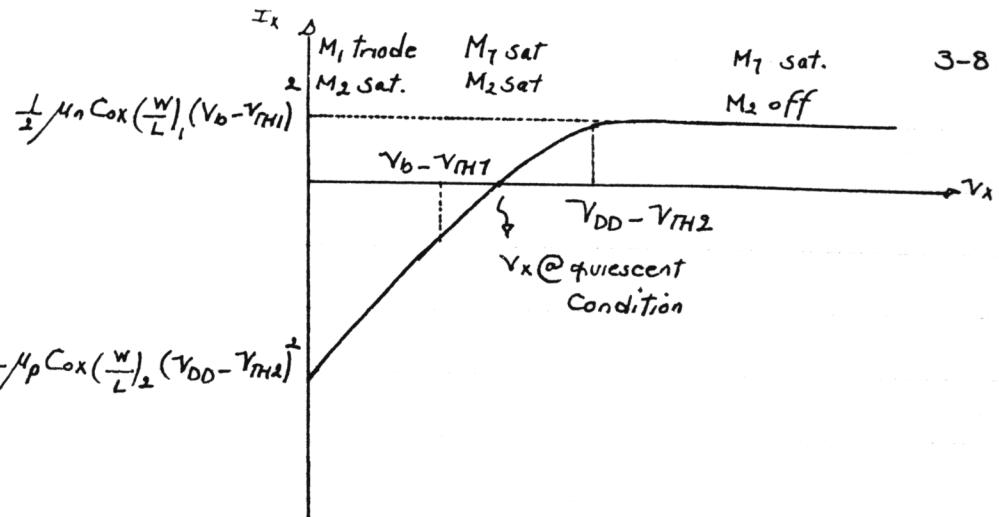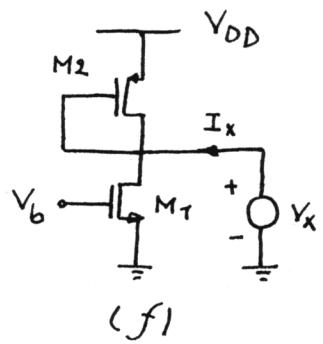


3.5.

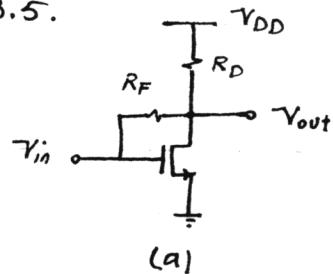


$$\frac{V_o - V_{in}}{R_F} + g_{m1} V_{in} + \frac{V_o}{r_{o1}} + \frac{V_o}{R_D} = 0$$
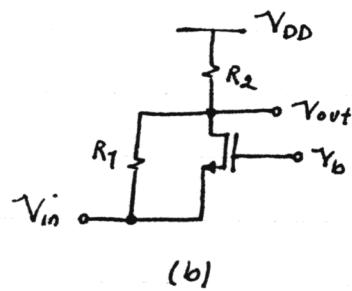
$$A_V = \frac{V_o}{V_{in}} = - \frac{g_{m1} - 1/R_F}{\frac{1}{R_F} + \frac{1}{r_{o1}} + \frac{1}{R_D}}$$




$$\frac{V_o}{R_2} + (V_o - V_{in}) \left( \frac{1}{R_1} + \frac{1}{r_{o1}} \right) - g_{m1} V_{in} = 0$$
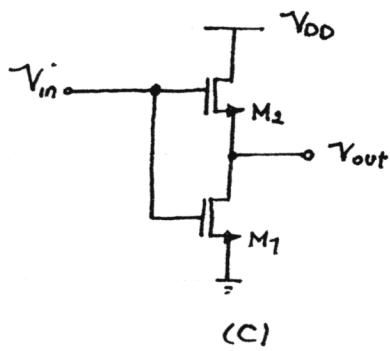
$$\frac{V_o}{V_{in}} = \frac{g_{m1} + \frac{1}{R_1} + \frac{1}{r_{o1}}}{\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{r_{o1}}}$$



$$g_{m2} (V_{in} - V_{out}) + \frac{-V_{out}}{r_{o2}} = g_{m1} V_{in} + \frac{V_{out}}{r_{o1}}$$
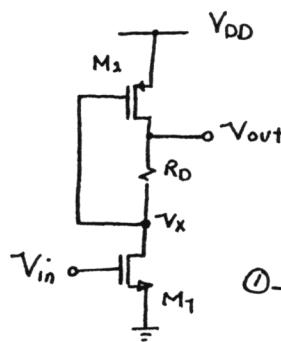
$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1} - g_{m2}}{g_{m2} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}}}$$



$$\textcircled{1} \left( g_{m1} V_{in} + \frac{V_x}{r_{o1}} \right) R_D + V_x = V_{out}, \quad \textcircled{2} \left( g_{m2} V_x + \frac{V_{out}}{r_{o2}} \right) = g_{m1} V_{in} + \frac{V_x}{r_{o1}},$$

$$\textcircled{2} \rightarrow V_x \left( -g_{m2} - \frac{1}{r_{o1}} \right) = g_{m1} V_{in} + \frac{V_{out}}{r_{o2}} \quad \textcircled{2} \rightarrow V_x = - \frac{g_{m1} V_{in} + V_{out}/r_{o2}}{g_{m2} + \frac{1}{r_{o1}}} \quad \textcircled{3}$$


$$\textcircled{1} \rightarrow g_{m1} R_D V_{in} + \left( 1 + \frac{R_D}{r_{o1}} \right) V_x = V_o \quad \textcircled{4}$$

$$(d) \quad \textcircled{3}, \textcircled{4} \rightarrow g_{m1} R_D V_{in} - \frac{\left( 1 + \frac{R_D}{r_{o1}} \right) \left( g_{m1} V_{in} + \frac{V_{out}}{r_{o2}} \right)}{g_{m2} + \frac{1}{r_{o1}}} = V_{out}$$

$$\left[ g_{m1} R_D - \frac{g_{m1} \left( 1 + R_D/r_{o1} \right)}{g_{m2} + \frac{1}{r_{o1}}} \right] V_{in} = \left[ 1 + \frac{\frac{1}{r_{o2}} \left( 1 + R_D/r_{o1} \right)}{g_{m2} + \frac{1}{r_{o1}}} \right] V_{out}$$

$$\left[ g_{m1} R_D \left( g_{m2} + \frac{1}{r_{o1}} \right) - g_{m1} \left( 1 + \frac{R_D}{r_{o1}} \right) \right] V_{in} = \left[ g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \left( 1 + \frac{R_D}{r_{o1}} \right) \right] V_{out}$$
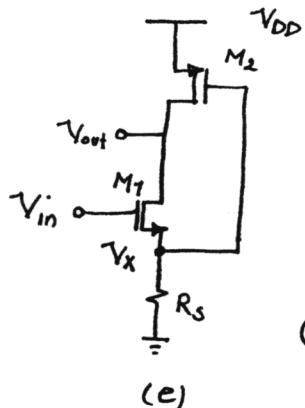
$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (g_{m2} R_D - 1)}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \left( 1 + \frac{R_D}{r_{o1}} \right)}$$



$$-\left( \frac{V_{out}}{r_{o2}} + g_{m2} V_x \right) = \frac{V_{out} - V_x}{r_{o1}} + g_{m1} (V_{in} - V_x) = \frac{V_x}{R_s} \quad \textcircled{1}, \textcircled{2}, \textcircled{3}$$


$$\textcircled{1}, \textcircled{3} \rightarrow V_x = - \frac{V_{out}}{r_{o2} (g_{m2} + \frac{1}{R_s})}$$

$$\textcircled{2}, \textcircled{3} \quad \frac{V_{out}}{r_{o1}} + g_{m1} V_{in} = - \frac{V_{out}}{r_{o2} (g_{m2} + \frac{1}{R_s})} \left( \frac{1}{R_s} + g_{m1} + \frac{1}{r_{o1}} \right)$$

$$\frac{V_{out}}{r_{o1}} \cdot r_{o2} \left( g_{m2} + \frac{1}{R_s} \right) + g_{m1} \cdot V_{in} \cdot r_{o2} \left( g_{m2} + \frac{1}{R_s} \right) = -V_{out} \left( \frac{1}{R_s} + g_{m1} + \frac{1}{r_{o1}} \right)$$


$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1} (g_{m2} + 1/R_s) r_{o2}}{g_{m1} + \frac{1}{R_s} + \frac{1}{r_{o1}} \left[ 1 + r_{o2} (g_{m2} + \frac{1}{R_s}) \right]}$$

3.6.

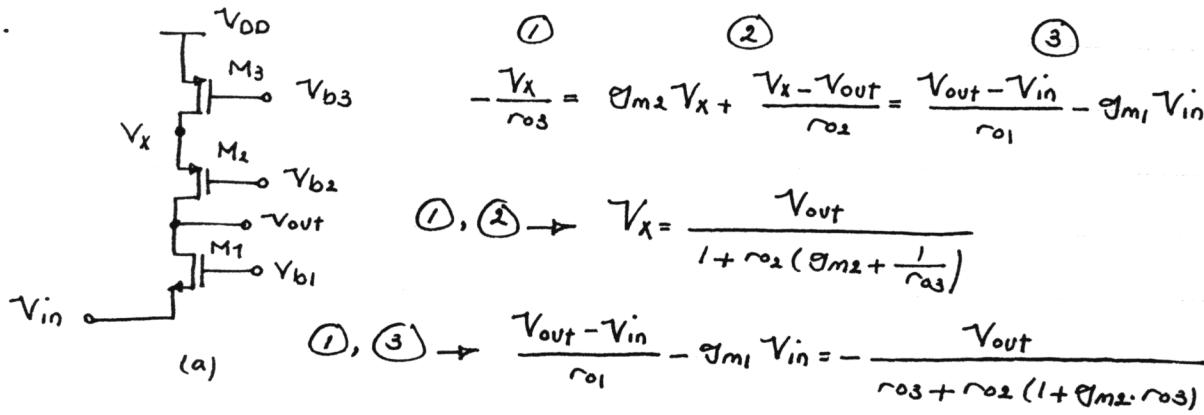



$$V_{out} \left( \frac{1}{r_{o1}} + \frac{1}{r_{o3} + r_{o2}(1 + g_{m2} \cdot r_{o3})} \right) = (g_{m1} + \frac{1}{r_{o1}}) V_{in}$$
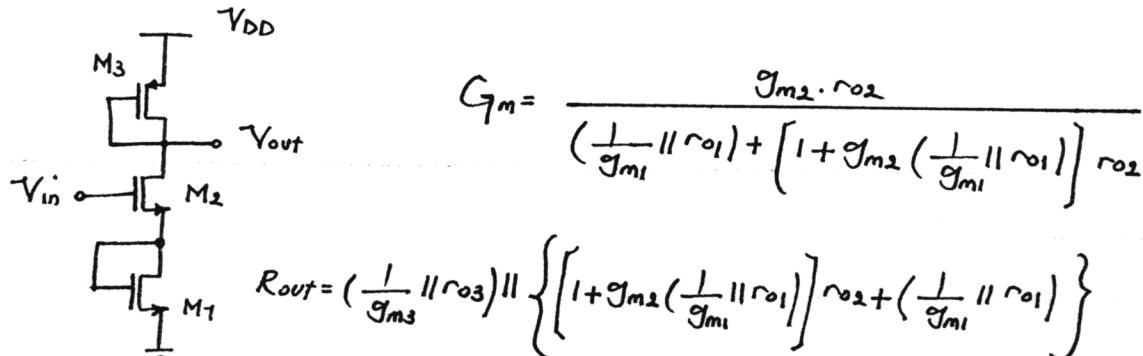
$$\frac{V_{out}}{V_{in}} = \frac{(1 + g_{m1} \cdot r_{o1})(r_{o3} + r_{o2}(1 + g_{m2} \cdot r_{o3}))}{r_{o1} + r_{o3} + r_{o2}(1 + g_{m2} \cdot r_{o3})}$$


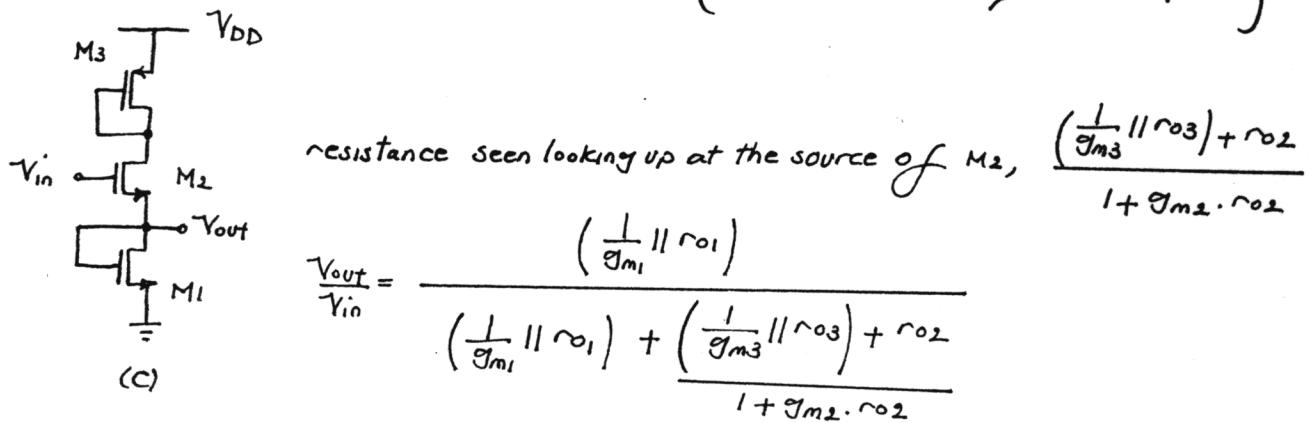
$$(b) A_V = -G_m \cdot R_{out} = -\frac{g_{m2} r_{o2} \left( \frac{1}{g_{m3}} \parallel r_{o3} \right)}{\left( \frac{1}{g_{m3}} \parallel r_{o3} \right) + \left\{ \left[ 1 + g_{m2} \left( \frac{1}{g_{m1}} \parallel r_{o1} \right) \right] r_{o2} + \left( \frac{1}{g_{m1}} \parallel r_{o1} \right) \right\}}$$




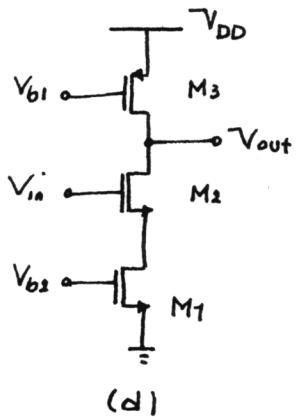

$$G_m = \frac{g_{m_2} \cdot r_{o_2}}{r_{o_1} + [1 + g_{m_2} \cdot r_{o_1}] r_{o_2}}$$

$$R_{out} = r_{o_3} \parallel \left[ (1 + g_{m_2} \cdot r_{o_1}) r_{o_2} + r_{o_1} \right]$$

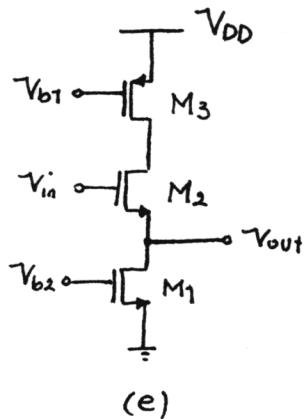
$$\frac{V_{out}}{V_{in}} = -\frac{g_{m_2} \cdot r_{o_2} \cdot r_{o_3}}{r_{o_3} + (1 + g_{m_2} \cdot r_{o_1}) r_{o_2} + r_{o_1}}$$



resistance seen looking up at the source of M<sub>2</sub>

$$R_{in} = \frac{r_{o_3} + r_{o_2}}{1 + g_{m_2} \cdot r_{o_2}}$$
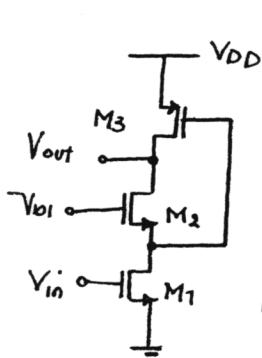
$$\frac{V_{out}}{V_{in}} = \frac{r_{o_1}}{r_{o_1} + \frac{r_{o_3} + r_{o_2}}{1 + g_{m_2} \cdot r_{o_2}}} = \frac{r_{o_1} (1 + g_{m_2} \cdot r_{o_2})}{r_{o_1} (1 + g_{m_2} \cdot r_{o_2}) + r_{o_2} + r_{o_3}}$$



$$\textcircled{1} \quad -\left( \frac{V_{out}}{r_{o_3}} + g_{m_3} V_x \right) = \left( \frac{V_{out} - V_x}{r_{o_2}} - g_{m_2} V_x \right) = \frac{V_x}{r_{o_1}} + g_{m_1} V_{in}$$

$$\textcircled{1}, \textcircled{2} \rightarrow \frac{V_x}{r_{o_2}} + g_{m_2} V_x - g_{m_3} V_x = \frac{V_{out}}{r_{o_2}} + \frac{V_{out}}{r_{o_3}} \rightarrow V_x = \frac{\frac{1}{r_{o_2}} + \frac{1}{r_{o_3}}}{\frac{1}{r_{o_2}} + g_{m_2} - g_{m_3}} V_{out}$$


$$\textcircled{1}, \textcircled{3} \quad -\frac{V_{out}}{r_{o_3}} - g_{m_3} V_x = \frac{V_x}{r_{o_1}} + g_{m_1} V_{in}$$

$$-\frac{V_{out}}{r_{o_3}} - \left( g_{m_3} + \frac{1}{r_{o_1}} \right) \frac{\frac{1}{r_{o_2}} + \frac{1}{r_{o_3}}}{\frac{1}{r_{o_2}} + g_{m_2} - g_{m_3}} V_{out} = g_{m_1} V_{in}$$

$$-V_{out} \left[ \frac{1}{r_{o_3}} + \frac{\left( g_{m_3} + \frac{1}{r_{o_1}} \right) \left( \frac{1}{r_{o_2}} + \frac{1}{r_{o_3}} \right)}{\frac{1}{r_{o_2}} + g_{m_2} - g_{m_3}} \right] = g_{m_1} V_{in}$$

$$-\frac{V_{out}}{V_{in}} \left[ \frac{1}{r_{o3}} + \frac{(1+g_{m3}r_{o1})(r_{o3}+r_{o2})}{r_{o1}r_{o3}[1+(g_{m2}-g_{m3})r_{o2}]} \right] = g_{m1} \cdot V_{in}$$
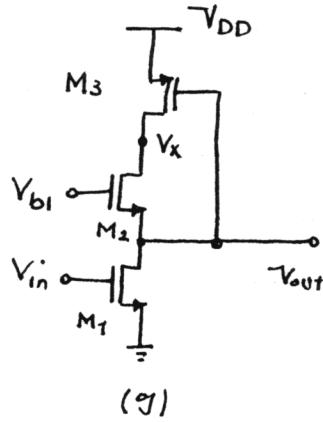
$$\frac{V_{out}}{V_{in}} = -\frac{g_{m1}r_{o1}r_{o3}[1+(g_{m2}-g_{m3})r_{o2}]}{r_{o1}[1+(g_{m2}-g_{m3})r_{o2}] + (1+g_{m3}r_{o1})(r_{o3}+r_{o2})}$$




$$V_x = \frac{\frac{1}{r_{o2}} + g_{m2} - g_{m3}}{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}} \cdot V_{out}$$

$$-\frac{V_x}{r_{o3}} - g_{m3} V_{out} = \frac{V_{out}}{r_{o1}} + g_{m1} \cdot V_{in}$$

$$-\frac{\frac{1}{r_{o2}} + g_{m2} - g_{m3}}{\frac{r_{o3}}{r_{o2}} + 1} V_{out} - g_{m3} V_{out} = \frac{V_{out}}{r_{o1}} + g_{m1} \cdot V_{in}$$

$$-\frac{V_{out}}{V_{in}} \left[ \frac{1+(g_{m2}-g_{m3})r_{o2}}{r_{o3}+r_{o2}} + g_{m3} + \frac{1}{r_{o1}} \right] = g_{m1} \cdot V_{in}$$
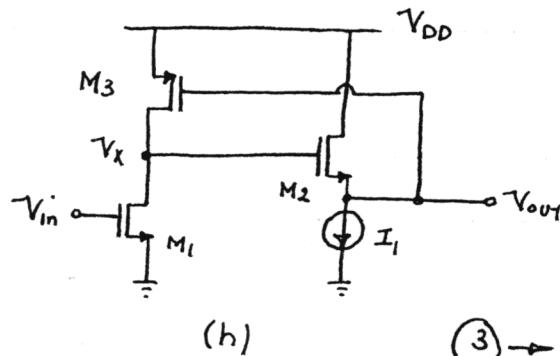
$$\frac{V_{out}}{V_{in}} = -\frac{g_{m1}r_{o1}(r_{o2}+r_{o3})}{r_{o1}[1+(g_{m2}-g_{m3})r_{o2}] + (r_{o2}+r_{o3})(1+g_{m3}r_{o1})}$$



$$-\left( \frac{V_x}{r_{o3}} + g_{m3} V_{out} \right) = g_{m1} V_{in} + \frac{V_x}{r_{o1}} \quad (1)$$


$$-\frac{V_{out}}{r_{o2}} + g_{m2} (V_x - V_{out}) = 0 \quad @ \text{output node} \quad (2)$$

$$(3) \rightarrow V_x = \frac{\frac{1}{r_{o2}} + g_{m2}}{g_{m2}} \cdot V_{out} = \frac{1+g_{m2}r_{o2}}{g_{m2}r_{o2}} V_{out}$$

$$(1), (2) \rightarrow - \left[ \left( \frac{1}{r_{o3}} + \frac{1}{r_{o1}} \right) \frac{1+g_{m2}r_{o2}}{g_{m2}r_{o2}} + g_{m3} \right] V_{out} = g_{m1} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = -\frac{g_{m1} \cdot g_{m2} r_{o1} r_{o2} r_{o3}}{(r_{o1}+r_{o3})(1+g_{m2}r_{o2}) + g_{m2} g_{m3} r_{o1} r_{o2} r_{o3}}$$

3.7.

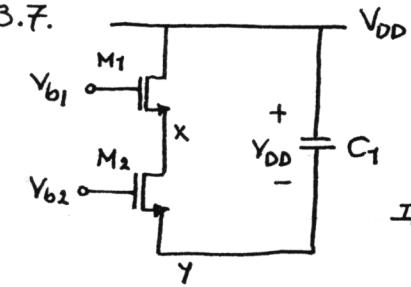

$$V_Y(t=0) = -V_{C_1} + V_{DD} = -V_{DD} + V_{DD} = 0$$

$$I_{D1} = I_{D2} \rightarrow \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 \left[ V_{b1} - V_X(t=0) - V_{TH1} \right]^2 = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 \left( V_{b2} - V_{TH2} \right)^2$$

(9)

$$V_X(t=0) = V_{b1} - V_{TH1} - \sqrt{\frac{\left( \frac{W}{L} \right)_2}{\left( \frac{W}{L} \right)_1} (V_{b2} - V_{TH2})}$$



We assume that  $V_X(t=0) > V_{b2} - V_{TH2}$ , therefore, M<sub>2</sub> is always saturated.


$$\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{b1} - V_X - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{b2} - V_Y - V_{TH2})^2 = C_1 \frac{dV_Y}{dt} \quad (1) \quad (2) \quad (3)$$

$$(2), (3) \rightarrow \frac{dV_Y}{(V_{b2} - V_Y - V_{TH2})^2} = \frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left( \frac{W}{L} \right)_2 dt$$

$$\frac{1}{V_{b2} - V_Y - V_{TH2}} = \frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left( \frac{W}{L} \right)_2 t + K, K = \frac{1}{V_{b2} - V_{TH2}} \text{ because } V_Y(t=0) = 0$$
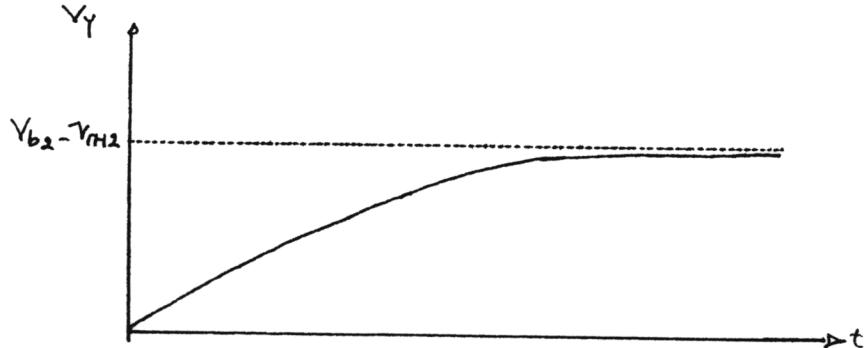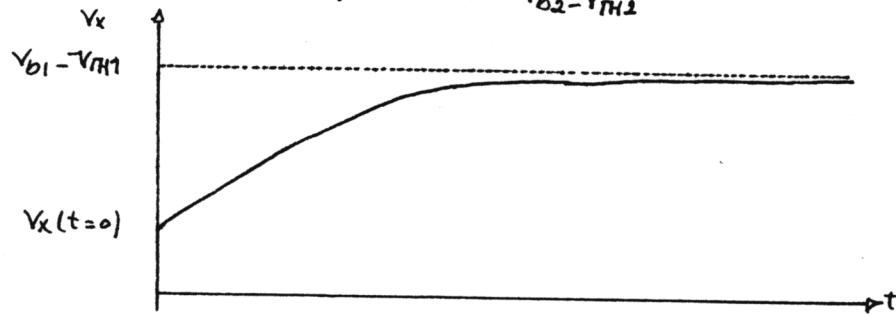
$$V_Y = V_{b2} - V_{TH2} - \frac{1}{\frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left( \frac{W}{L} \right)_2 t + \frac{1}{V_{b2} - V_{TH2}}} , V_X = V_{b1} - V_{TH1} - (V_{b2} - V_Y - V_{TH2}) \sqrt{\frac{\left( \frac{W}{L} \right)_2}{\left( \frac{W}{L} \right)_1}} \leftarrow (2), (1)$$



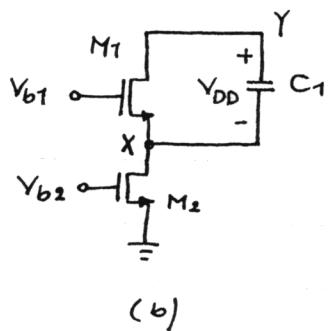

The drain current of  $M_2$  is zero, therefore,  $M_2$  operates in deep triode region, pulling down  $V_x$  to zero potential.  
 $V_x = 0 \text{ for } 0 < t < \infty$   
 $V_Y(t=0) = V_{DD} \rightarrow M_1 \text{ starts in saturation.}$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_1 (V_{b1} - V_{TH1})^2 = -C_1 \frac{dV_{C1}}{dt} = -C_1 \frac{dV_Y}{dt}$$


$$\textcircled{1} \quad V_Y = V_{C1} = V_{DD} - \frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left(\frac{w}{L}\right)_1 (V_{b1} - V_{TH1})^2 t$$


When  $V_Y = V_{b1} - V_{TH1}$ ,  $\textcircled{2}$   $M_1$  enters triode region.

Substituting  $\textcircled{2}$  in  $\textcircled{1}$ , we calculate the time when  $M_1$  is at the edge of triode region.

$$t_1 = \frac{V_{DD} - V_{b1} + V_{TH1}}{\frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left(\frac{w}{L}\right)_1 (V_{b1} - V_{TH1})^2}$$
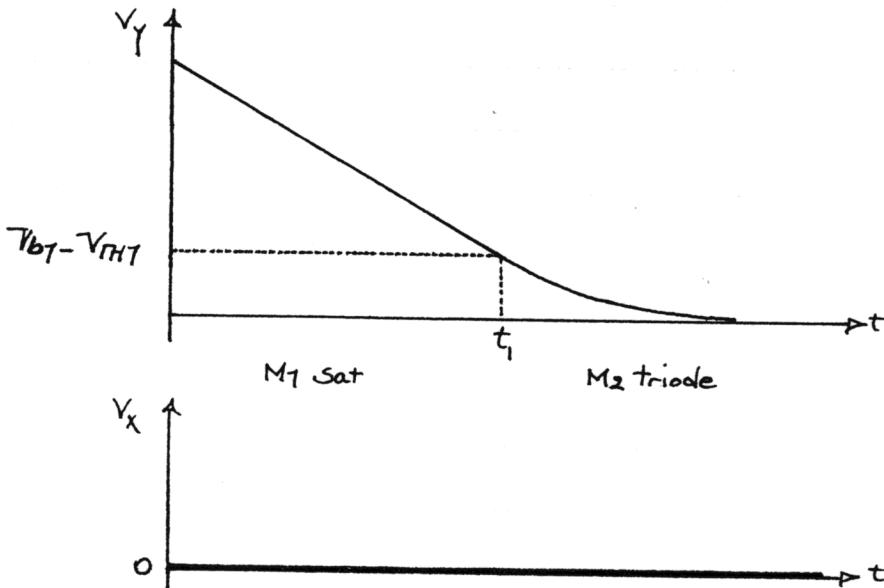
$$\text{For } t > t_1 : \mu_n C_{ox} \left(\frac{w}{L}\right)_1 \left[ (V_{b1} - V_{TH1}) V_Y - \frac{V_Y^2}{2} \right] = -C_1 \frac{dV_Y}{dt} \rightarrow V_Y = \dots$$



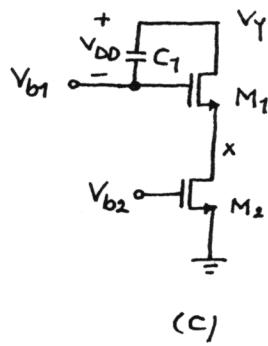

$$V_Y(t=0) = V_{DD} + V_{b1}, \text{ both transistors are saturated.}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH2})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{b1} - V_x - V_{TH1})^2$$

$$V_x = V_{b1} - V_{TH1} - (V_{b2} - V_{TH2}) \sqrt{\frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}}$$

$$C_1 \frac{dV_{C1}}{dt} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH2})^2 \rightarrow V_{C1} = V_{DD} - \frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH2})^2 t$$

$$V_y = V_{C1} + V_{b1} = V_{DD} + V_{b1} - \frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH2})^2 t$$

@  $t=t_1$ , we have  $V_y = V_{b1} - V_{TH1}$ , polarity of voltage across  $C_1$  has already changed.

$$V_{DD} + V_{b1} - \frac{1}{2} \mu_n \frac{C_{ox}}{C_1} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH2})^2 t_1 = V_{b1} - V_{TH1}$$

$$t_1 = \frac{2(V_{DD} + V_{TH1}) C_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH2})^2}$$

For  $t > t_1$ ,  $M_1$  enters triode region. We assume that still  $M_2$  is saturated.

$$V_y = V_{DD} + V_{b1} - \frac{1}{C_1} I_{D2} \cdot t \quad \text{where } I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH2})^2$$


$$\text{and } I_{D2} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ (V_{b1} - V_x)(V_{DD} + V_{b1} - \frac{1}{C_1} I_{D2} \cdot t - V_x) - \frac{(V_{DD} + V_{b1} - \frac{1}{C_1} I_{D2} \cdot t - V_x)^2}{2} \right]$$

$$\rightarrow V_x \text{ is obtained}$$

When  $V_x = V_{b2} - V_{TH2}$ ,  $M_2$  enters the triode region, too.


$$\mu_n C_{ox} \left(\frac{W}{L}\right)_2 \left[ (V_{b2} - V_{TH2}) V_x - \frac{V_x^2}{2} \right] = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ (V_{b1} - V_x - V_{TH1})(V_y - V_x) - \frac{(V_y - V_x)^2}{2} \right] = -C_1 \frac{dV_y}{dt}$$

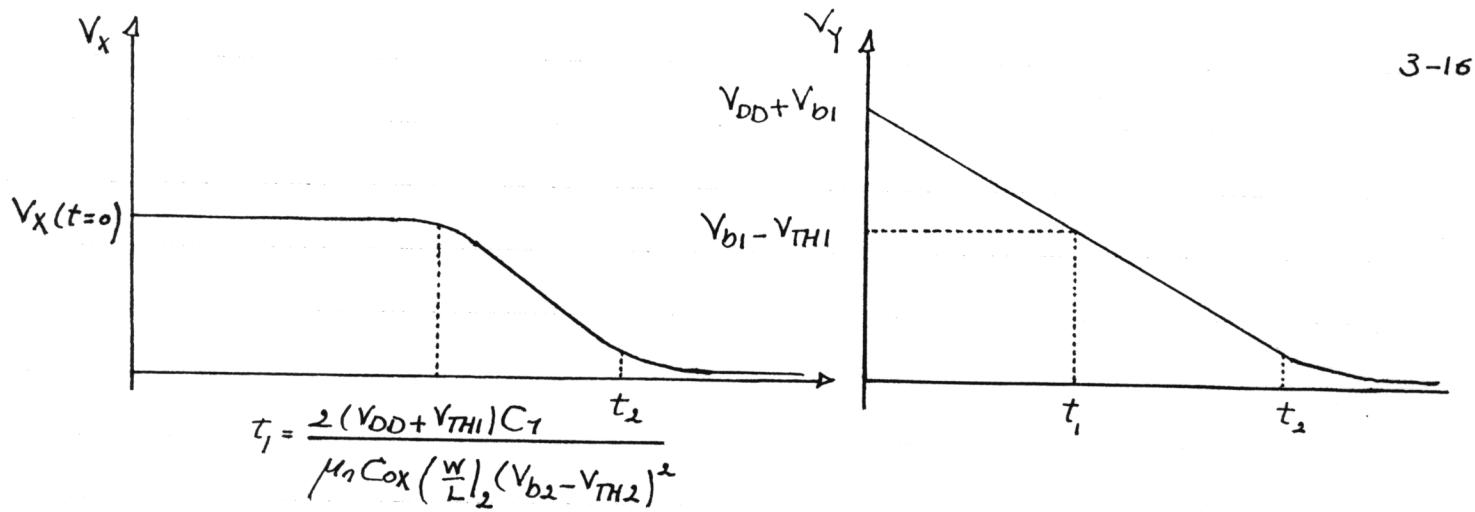$V_x$  and  $V_y$  are obtained. This regime continues until  $V_x$  and  $V_y$  drop to zero, and  $C_1$  charges up to  $-V_{b1}$ .



For  $0 < t < t_1$ ,  $M_1$  Sat.,  $M_2$  Sat. For  $t_1 < t < t_2$ ,  $M_1$  Triode,  $M_2$  Sat.  
 For  $t_2 < t$ ,  $M_1$  Triode,  $M_2$  Triode

3.8

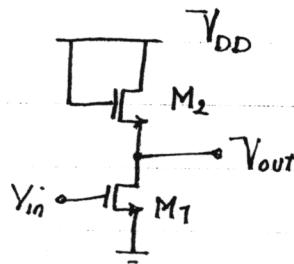

$$\left(\frac{W}{L}\right)_1 = \frac{50}{0.5}, \quad \left(\frac{W}{L}\right)_2 = \frac{10}{0.5}, \quad I_{D1} = I_{D2} = 0.5 \text{ mA}$$

$$\mu_n C_{ox} = 350 \frac{\text{Cm}^2}{\text{V.S}} \times \frac{8.85 \times 10^{-14} \text{ Farad/Cm}}{9 \times 10^7 \text{ Cm}} =$$

$$1.34225 \times 10^{-4} \text{ A/V}^2$$

$$\mu_p C_{ox} = \frac{100 \text{ Cm}^2}{\text{V.S}} \times \frac{8.85 \times 10^{-14} \text{ Farad/Cm}}{9 \times 10^7 \text{ Cm}} =$$

$$3.835 \times 10^{-5} \text{ A/V}^2$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda_N I_D} = 20 \text{ k}, \quad I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TH2})^2 (1 + \lambda_N V_{DS2}),$$

$$0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \times 20 \left[ 3 - V_o - 0.7 - 0.45 (\sqrt{0.9 + V_o} - \sqrt{0.9}) \right]^2 [1 + 0.1(3 - V_o)]$$

$$2.3 - 0.45 (\sqrt{0.9 + V_o} - \sqrt{0.9}) - \sqrt{\frac{1}{2.6845 (1.3 - 0.1 V_o)}} = V_o \rightarrow V_o = 1.466 \text{ V}$$


$$g_{m1} = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 0.5 \times 10^{-3}} = 3.66 \times 10^{-3} \text{ A/V}$$

$$g_{m2} = \sqrt{2 \times 1.34225 \times 10^{-4} \times 20 \times 0.5 \times 10^{-3}} = 1.63 \times 10^{-3} \text{ A/V}$$

$$g_{m2} = \frac{g_m g_{m2}}{2\sqrt{2\phi_F + V_{GS}}} = \frac{0.45}{2\sqrt{0.9 + 1.466}} \times 1.63 \times 10^{-3} = 2.3843 \times 10^{-4} \text{ A/V}$$

$$R_{out} = \frac{1}{g_m + g_{mb2} + r_o^{-1}} \parallel r_o = \frac{1}{1.63 \times 10^{-3} + 2.3843 \times 10^{-4} + (20 \times 10^3)^{-1}} \parallel 20 \times 10^3 \quad 3.17$$
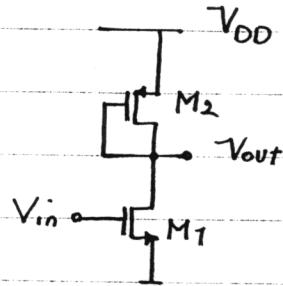
$$R_{out} = 508 \Omega \quad A_v = -g_m \cdot R_{out} = -3.66 \times 10^{-3} \times 508 = -1.85$$



$$g_m = \sqrt{2 \times 3.835 \times 10^{-5} \times 20 \times 0.5 \times 10^{-3}} = 8.7578 \times 10^{-4}$$

$$r_o = \frac{1}{\lambda_p I} = \frac{1}{0.2 \times 0.5 \times 10^{-3}} = 10K$$

$$R_{out} = \frac{1}{g_m + r_o^{-1}} \parallel r_o = 974.8628 \Omega$$

$$A_v = -g_m \cdot R_{out} = -0.8537$$

3.9.

$$(W/L)_1 = 50/0.5, \quad (W/L)_2 = 50/2, \quad I_{D1} = I_{D2} = 0.5mA$$

$$r_o = \frac{1}{\lambda_N I} = \frac{1}{0.1 \times 0.5 \times 10^{-3}} = 20K, \quad r_o = \frac{1}{\lambda_p I} = \frac{1}{0.2 \times 0.5 \times 10^{-3}} = 40K$$

$$g_m = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 0.5 \times 10^{-3}} = 3.6636 \times 10^{-3}$$

$$A_v = -g_m (r_o \parallel r_o) = -48.84$$

If we assume that M<sub>1</sub> is in the edge of the triode region, then, we have:

$$V_{GS} - V_{TH1} = V_{DS1} = V_{out}, \quad I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH1})^2 (1 + \lambda_N V_{DS})$$

$$0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \times 100 V_{DS}^2 (1 + 0.1 V_{DS}) \rightarrow \sqrt{\frac{1}{13.4225 (1 + 0.1 V_{DS})}} = V_{DS}$$

$$V_{DSmin} = V_{min} = 0.2693$$


If we assume that M<sub>2</sub> is in the edge of the triode region, then, we have:

$$I_D = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{SG} - V_{TH2})^2 (1 + \lambda_p V_{SD}), \quad 0.5 \times 10^{-3} = \frac{1}{2} \times 3.835 \times 10^{-5} \times 25 V_{SD}^2 (1 + \lambda_p V_{SD})$$

$$\sqrt{\frac{1}{0.95875 (1 + 0.05 V_{SD})}} = V_{SD} \rightarrow V_{SDmin} = 0.9967V, \quad V_{max} = V_{DD} - V_{SDmin},$$

$$V_{max} = 2V$$

3.10.

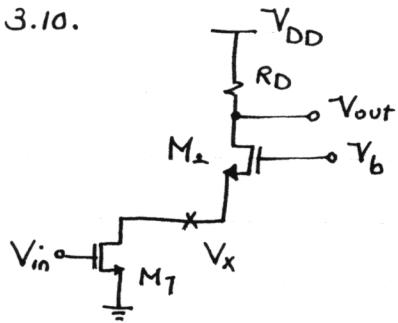

$$\left(\frac{W}{L}\right)_1 = 50/0.5, \quad \left(\frac{W}{L}\right)_2 = 10/0.5 \quad I_{D1} = I_{D2} = 0.5 \text{ mA}$$

$R_D = 1\text{ k}\Omega$

3-18

$$V_{DS,sat1} = V_{GS1} - V_{TH1} = \left( \frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1} \right)^{1/2} = \left( \frac{2 \times 0.5 \times 10^{-3}}{1.34225 \times 10^{-4} \times 100} \right)^{1/2}$$

$$V_{DS,sat1} = 0.2729 \text{ V}$$

$$V_{X,Bias} = 0.2729 + 50 \times 10^{-3} = 0.3229 \text{ V}$$

$$V_{TH2} = V_{TH0} + 8 \left( \sqrt{2\phi_F + V_{BS}} - \sqrt{2\phi_F} \right) = 0.7 + 0.45 (\sqrt{0.9 + 0.3229} - \sqrt{0.9})$$

$$V_{TH2} = 0.77073 \text{ V}$$

$$V_{GS2} = V_{TH2} + \left( \frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2} \right)^{1/2} = 0.77073 + \left( \frac{2 \times 0.5 \times 10^{-3}}{1.34225 \times 10^{-4} \times 20} \right)^{1/2} = 1.38107 \text{ V},$$

$$V_b = V_{GS2} + V_x$$

$$V_b = 1.38107 + 0.3229 = 1.7 \text{ V}, \quad g_{m1} = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 0.5 \times 10^{-3}} = 3.6636 \times 10^{-3} \text{ A/V}$$

$$g_{m2} = \sqrt{2 \times 1.34225 \times 10^{-4} \times 20 \times 0.5 \times 10^{-3}} = 1.6384 \times 10^{-3} \text{ A/V}$$

$$g_{m2e} = \frac{0.45}{2 \sqrt{0.9 + 0.3229}} \quad 1.6384 \times 10^{-3} = 3.3336 \times 10^{-4}, \quad r_o = r_{o2} = \frac{1}{\lambda_N I} = \frac{1}{0.1 \times 0.5 \times 10^{-3}} = 20 \text{ k}\Omega$$

$$R_{out} = R_D \parallel \left\{ \left[ 1 + (g_{m2} + g_{m2e})r_{o2} \right] r_{o1} + r_{o2} \right\} = 10 \parallel \left\{ \left[ 1 + (1.6384 \times 10^{-3} + 3.3336 \times 10^{-4}) \frac{1}{20 \times 10^3} \right] \frac{1}{20 \times 10^3} + \frac{1}{20 \times 10^3} \right\}$$

$$R_{out} = 998.7947 \Omega, \quad G_m = \frac{g_{m1} \cdot r_{o1} [r_{o2}(g_{m2} + g_{m2e}) + 1]}{r_{o1} \cdot r_{o2} (g_{m2} + g_{m2e}) + r_{o1} + r_{o2}}$$

$$G_m = \frac{3.6636 \times 10^{-3} \left( \frac{1}{20 \times 10^3} (1.6384 \times 10^{-3} + 3.3336 \times 10^{-4}) + 1 \right)}{(20 \times 10^3)^2 (1.6384 \times 10^{-3} + 3.3336 \times 10^{-4}) + 2 \times 20 \times 10^3} = 3.5751 \times 10^{-3} \text{ A/V}$$

$$A_V = -G_m \quad R_{out} = -3.57$$

We obtain the small signal voltage gain from input to node X.

$$R_{out}@X = r_{o1} \parallel \frac{R_D + r_{o2}}{1 + (g_{m2} + g_{m2e})r_{o2}} = 20 \times 10^3 \parallel \frac{10^3 + 20 \times 10^3}{1 + (1.6384 \times 10^{-3} + 3.3336 \times 10^{-4}) \frac{1}{20 \times 10^3}}$$

$$R_{out}@X = 506.2$$

$$A_{VX} = -G_m \cdot R_{out}@X = -1.8545$$

$$I \quad V_x = V_{Xmin} = V_{DS,sat1}, \quad \Delta V_x = -50 \text{ mV} \rightarrow \Delta V_{in} = \frac{-50 \times 10^{-3}}{-1.8545} = 26.96 \times 10^{-3}$$

$$\Delta V_{out} = 26.96 \times 10^{-3} \times (-3.57) = -96.25 \times 10^{-3}$$

3.19

$$V_{out, min} = V_{DD} - R_D I_D + \Delta V_0 = 3 - 1 \times 0.5 - 96.25 \times 10^{-3} = 2.41V$$


$$V_{out, max} = 3V, \Delta V_0 = 3 - 2.5 = 0.5V, \Delta V_{in} = \frac{0.5}{-3.57} = -0.14V$$

$$\Delta V_x = -1.8545 (-0.14) = 0.2597$$

$$V_{x, max} = V_{x, Bias} + 0.2597 = 0.3229 + 0.2597 = 0.5826V$$

If we take  $V_{out, min} = V_b - V_{TH2} = 1.7 - 0.77073 = 0.92921V$ ,  $\Delta V_0 = -1.57$  which translates into a huge negative swing at x that makes the final voltage at node x negative. Therefore,  $M_1$  limits the negative going output swing because the voltage gain from input to node x is quite large.

3.11

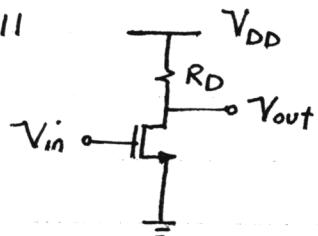

$$(\frac{W}{L})_1 = 50/0.5, R_D = 2k\Omega, \lambda = 0$$

$$r_o = \frac{1}{\lambda N I_D} = \frac{1}{0.1 \times 10^{-3}} = 10k$$

$$R_{out} = r_o \parallel R_D = 10k \parallel 2k = \frac{5000}{3} \Omega$$

$$g_m = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 10^{-3}} = 5.1812 \times 10^{-3}$$

$$A_v = -g_m \cdot R_{out} = -5.1812 \times 10^{-3} \times \frac{5000}{3} = -8.6353$$

At the edge of the triode region:  $V_{out} = V_{GS} - V_{TH} = V_{GS} - 0.7$ ,  $I_D = \frac{V_{DD} - V_{out}}{R_D} = \frac{3 - V_{GS} + 0.7}{2 \times 10^3}$ ,  $I_D = \frac{1}{2} \mu_n C_{ox} (\frac{W}{L})_1 (V_{GS} - V_{TH})^2$

$$\frac{3 - V_{GS}}{2 \times 10^3} = \frac{3.7 - V_{GS}}{2 \times 10^3}, \frac{3.7 - V_{GS}}{2 \times 10^3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \times 100 (V_{GS} - 0.7)^2$$

$$13.4225 V_{GS}^2 - 17.7915 V_{GS} - 10.277025 = 0 \rightarrow V_{GS} = 1.137V$$

$$I_D @ \text{the edge of the triode} = \frac{1}{2} \times 1.34225 \times 10^{-4} \times 100 (1.137 - 0.7)^2 = 1.2815 \times 10^{-3}$$

$$g_m @ \text{the edge of the triode} = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 1.2815 \times 10^{-3}} = 5.8653 \times 10^{-3}$$

$$r_o = \frac{1}{0.1 \times 1.2815 \times 10^{-3}} = 7.8 \times 10^3$$

$$A_v @ \text{the edge of the triode} = -g_m (r_o \parallel R_D) = -5.8653 \times 10^{-3} (7.8 \times 10^3 \parallel 2 \times 10^3)$$

$$A_v = -9.3374$$

$$V_o @ \text{the edge of the triode} = V_{DD} - R_D \times I_D = 3 - 2 \times 1.2815 \times 10^{-3} = 0.4369 V \quad 3-20$$

$$V_{DS} = V_{DS, \text{sat}} - 50 \times 10^{-3} = 0.4369 - 50 \times 10^{-3} = 0.3869 V$$

$$I_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{3 - 0.3869}{2 \times 10^3} = 1.3065 \times 10^{-3}$$

$$I_D = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 \left[ (V_{GS} - V_{TH1}) V_{DS} - \frac{V_{DS}^2}{2} \right] \\ 1.3065 \times 10^{-3} = 1.34225 \times 10^{-4} \times 100 \left[ (V_{GS} - 0.7) 0.3869 - \frac{(0.3869)^2}{2} \right] \Rightarrow V_{GS} = 1.145$$


$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 \cdot V_{DS}$$

$$g_m @ \text{the point where } 50 \text{ mV into the triode} = 1.34225 \times 10^{-4} \times 100 \times 0.3869 = 5.1942 \times 10^{-3}$$

$$R_o^{-1} = \frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH1} - V_{DS}) \Rightarrow R_o = \frac{1}{1.34225 \times 10^{-4} \times 100 (1.145 - 0.7 - 0.3869)} \\ R_o = 1.2835 \times 10^3 \Omega$$

$$A_v @ 50 \text{ mV into the triode region} = -5.1942 \times 10^{-3} \cdot (1.2835 \times 10^3 / 1.2 \times 10^3) = -4$$

3.12.

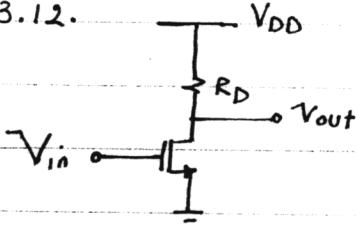

$$\left( \frac{W}{L} \right)_1 = 50 / 0.5 \quad R_D = 2k, \lambda = 0$$

$$I_{D1} @ V_{out} = 7V = \frac{V_{DD} - V_o}{R_D} = \frac{3 - 1}{2 \times 10^3} = 10^{-3} A$$

$$V_{in} = V_{TH1} + \left( \frac{2 I_{D1}}{\mu_n C_{ox} \left( \frac{W}{L} \right)_1} \right)^{1/2} = 0.7 + \left( \frac{2 \times 10^{-3}}{1.34225 \times 10^{-4} \times 100} \right)^{1/2} \Rightarrow V_{in} @ V_{out} = 1V = 1.086V$$

$$I_{D1} @ V_{out} = 2.5V = \frac{3 - 2.5}{2 \times 10^3} = 2.5 \times 10^{-4}, V_{in} @ V_{out} = 2.5V = 0.7 + \left( \frac{2 \times 2.5 \times 10^{-4}}{1.34225 \times 10^{-4} \times 100} \right)^{1/2} = 0.893V$$

$$g_m @ V_{out} = 7V = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 10} = 5.1812 \times 10^{-3}$$

$$g_m @ V_{out} = 2.5V = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 2.5 \times 10} = 2.59 \times 10^{-3}$$

$$r_o @ V_{out} = 7V = \frac{1}{0.1 \times 10^{-3}} = 10K, R_{out} = r_o // R_D = 10000 // 2000 = \frac{5000}{3} \Omega \quad 3-21$$

$$A_v @ V_{out} = -g_m \cdot R_{out} = -5.1812 \times 10^{-3} \times \frac{5000}{3} = -8.6353$$

$$r_o @ V_{out} = 2.5V = \frac{1}{0.1 \times 2.5 \times 10^{-4}} = 40K, R_{out} = r_o // R_D = 40000 // 2000 = 1.7 \times 10^3 \Omega$$

$$A_v @ V_{out} = -g_m \cdot R_{out} = -2.59 \times 10^{-3} \times 1.7 \times 10^3 = -4.9221$$

3.13.  $(\frac{W}{L}) = 50/0.5 / I_D = 0.5 \text{ mA}$   
 $\frac{1}{100/1}$

For NMOS device with  $(\frac{W}{L}) = 50/0.5, r_o = \frac{1}{\lambda_N I_D} = \frac{1}{0.1 \times 0.5 \times 10^{-3}} = 20K$

$$g_m = \sqrt{2 \times 1.34225 \times 10^{-4} \times 100 \times 0.5 \times 10^{-3}} = 3.6636 \times 10^{-3}$$

$$g_m r_o = 73.27$$

For PMOS device with  $(\frac{W}{L}) = 50/0.5, r_o = \frac{1}{\lambda_P I_D} = \frac{1}{0.2 \times 0.5 \times 10^{-3}} = 10K$

$$g_m = \sqrt{2 \times 3.835 \times 10^{-5} \times 100 \times 0.5 \times 10^{-3}} = 1.9583 \times 10^{-3}$$

$$g_m r_o = 19.5831$$

For NMOS device with  $(\frac{W}{L}) = 100/1, r_o = \frac{1}{\frac{0.1 \times 0.5 \times 10^{-3}}{2}} = 40K$

$$g_m = 3.6636 \times 10^{-3}, g_m r_o = 146.5169$$

For PMOS device with  $(\frac{W}{L}) = 100/1, r_o = \frac{1}{\frac{0.2 \times 0.5 \times 10^{-3}}{2}} = 20K$

$$g_m = 1.9583 \times 10^{-3}, g_m r_o = 39.1663$$

3.14.  $I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad ①$


$$g_m = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) \quad ②$$

Substituting  $(1 + \lambda V_{DS})$  from ① in ②, we have,

3-22



$$g_m = \mu_n C_{ox} \left( \frac{w}{L} \right) (V_{GS} - V_{TH}) \frac{I_D}{\frac{1}{2} \mu_n C_{ox} \left( \frac{w}{L} \right) (V_{GS} - V_{TH})^2} = \frac{2 I_D}{V_{GS} - V_{TH}}$$
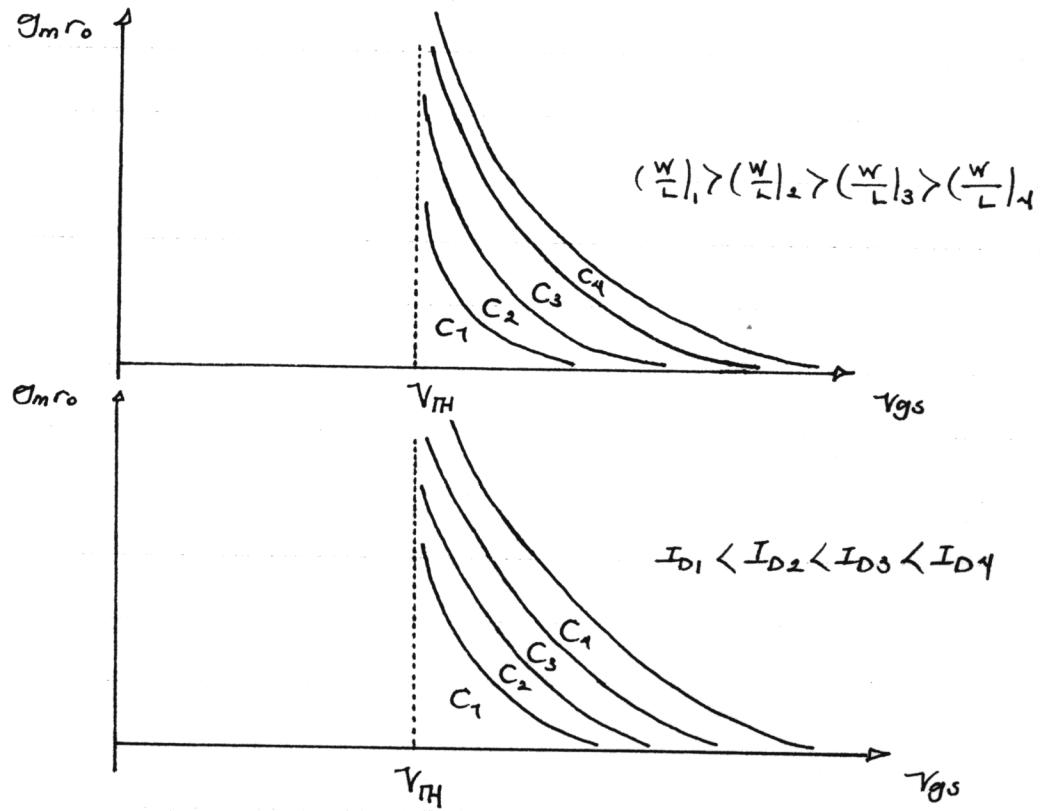
$$g_m r_0 = \frac{2 I_D}{V_{GS} - V_{TH}} \frac{1 + \lambda V_{DS}}{\lambda I_D} = \frac{2(1 + \lambda V_{DS})}{\lambda (V_{GS} - V_{TH})} = \frac{4 I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^3 \lambda \left( \frac{w}{L} \right)}$$



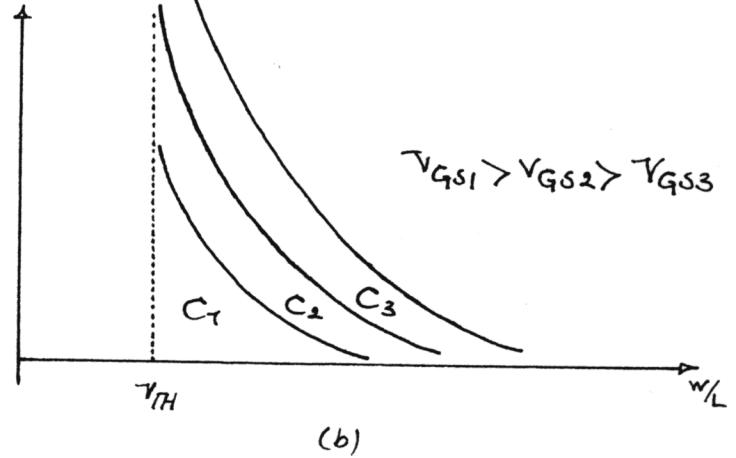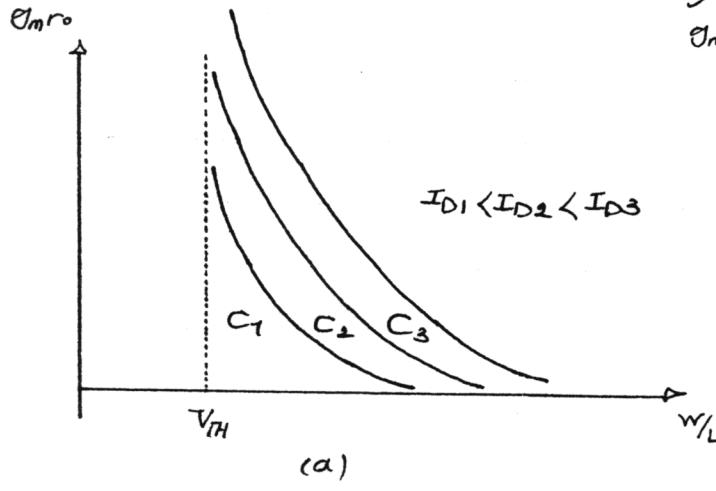3.15. From 3.14. we have:

$$g_m r_0 = \frac{4 I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^3 \lambda \left( \frac{w}{L} \right)}$$



$$3.16. \frac{W}{L} = 50/0.5 \quad V_G = +1.2V \quad V_S = 0 \quad 0 < V_D < 3 \quad V_{bulk} = 0$$

$$V_{Dsat} = V_{GS} - V_{TH} = 1.2 - 0.7 = 0.5V, \text{ for a saturated device } g_m r_0 = \frac{2(1+\lambda V_{DS})}{\lambda(V_{GS}-V_{TH})}$$

@ the edge of the triode region  $g_m r_0 = \frac{2(1+0.5 \times 0.1)}{0.1(1.2-0.7)} = 42$

We cannot neglect the channel-length modulation in the triode region, because it would lead to a discontinuity at the transition point between the saturation and the triode region.

@ triode region

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \left(\frac{W}{L}\right) V_{DS} (1 + \lambda V_{DS})$$


$$g_o = \frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \left(\frac{W}{L}\right) \left\{ (V_{GS} - V_{TH} - V_{DS})(1 + \lambda V_{DS}) + \lambda \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right] \right\}$$

in the triode region  $g_m r_0 = \frac{(1 + \lambda V_{DS}) / V_{DS}}{(V_{GS} - V_{TH} - V_{DS})(1 + \lambda V_{DS}) + \lambda \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]}$

In Saturation  $g_m r_0 = \frac{2(1+0.1 V_{DS})}{0.1(1.2-0.7)} = 40 + 4V_{DS} \quad V_{DS} > 0.5V$

In triode  $g_m r_0 = \frac{(1 + 0.1 V_{DS}) / V_{DS}}{(0.5 - V_{DS})(1 + 0.1 V_{DS}) + 0.1 \times 0.5 V_{DS} (1 - V_{DS})}$
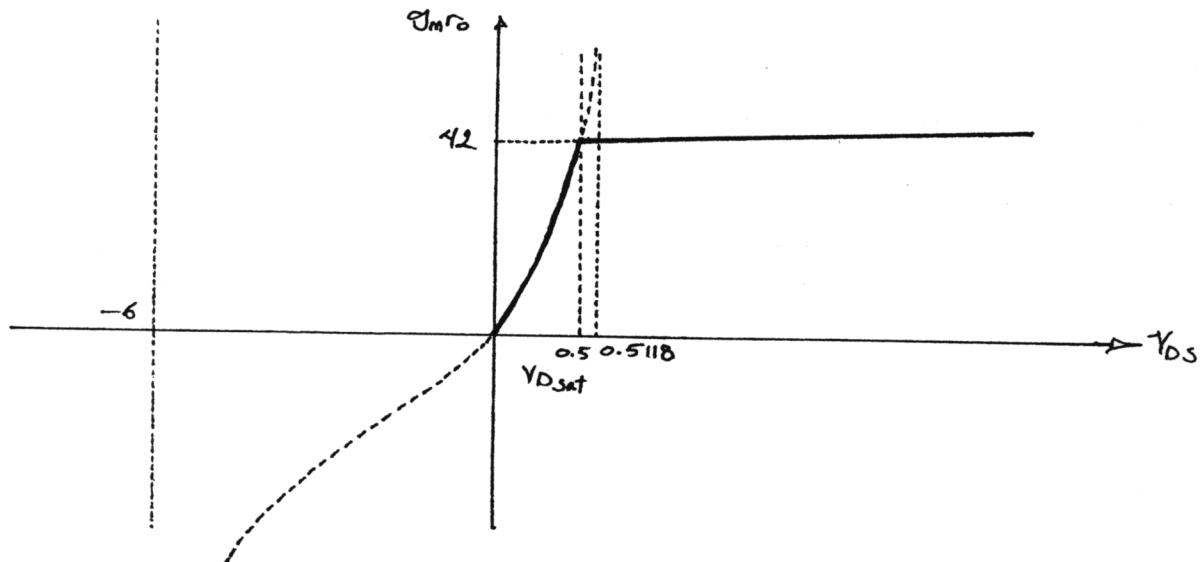
$$g_m r_0 = \frac{0.1 V_{DS} + V_{DS}}{-0.15 V_{DS}^2 - 0.9 V_{DS} + 0.5}$$



$$V_{bulk} = -7V, V_{SB} = +7V$$

$$V_{TH} = V_{TH0} + \lambda \left( \sqrt{2|\phi_F| + V_{SB}} - \sqrt{2|\phi_F|} \right) = 0.7 + 0.45 (\sqrt{0.9+1} - \sqrt{0.9}) = 0.8933V$$

$$\text{In Saturation } g_m r_o = \frac{2(1+0.1V_{DS})}{0.1(1.2-0.8933)} = 65.2262 + 6.5226 V_{DS}$$




$$V_{DS,sat} = V_{GS} - V_{TH} = 1.2 - 0.8933 = 0.3066V, \text{ @ the edge of the triode } g_m r_o = 67.2262$$

$$g_m r_o = \frac{(1+0.1V_{DS})V_{DS}}{(1.2-0.8933-V_{DS})(1+0.1V_{DS})+0.1[(1.2-0.8933)V_{DS}-0.5V_{DS}^2]}$$


$$g_m r_o = \frac{(1+0.1V_{DS})V_{DS}}{-0.15V_{DS}^2 - 0.9386V_{DS} + 0.3066}$$

$$3.17. \quad I_m = \mu_n C_{ox} \left( \frac{W}{L} \right) \left[ V_{GS} - V_{TH0} - \lambda \left( \sqrt{2|\phi_F| + V_{SB}} - \sqrt{2|\phi_F|} \right) \right] (1 + \lambda V_{DS})$$
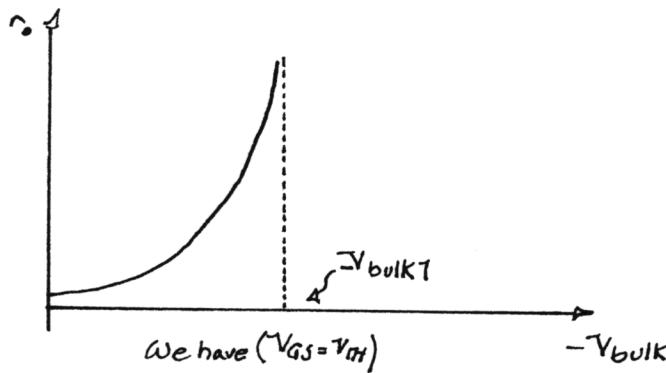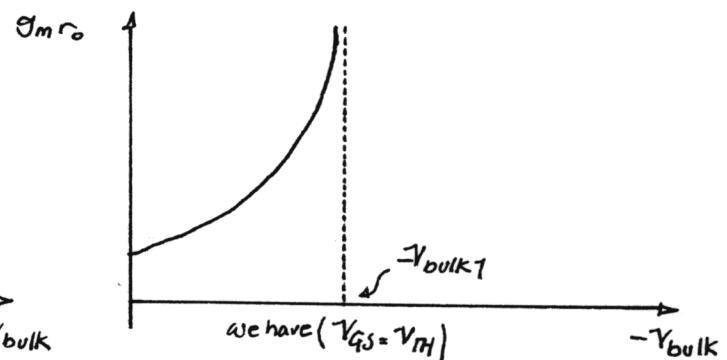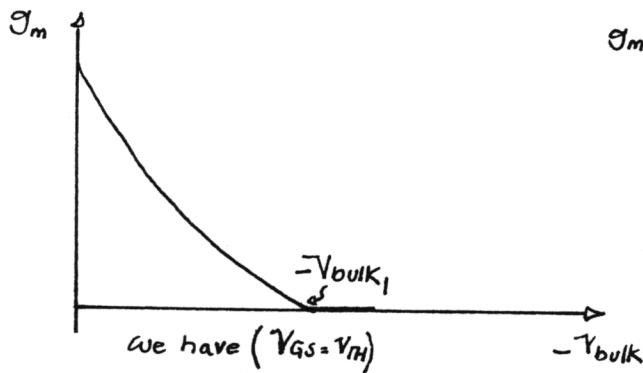
$$r_o = \frac{1}{\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TH})^2 / \lambda}, \quad g_m r_o = \frac{2(1+\lambda V_{DS})}{\lambda(V_{GS} - V_{TH})}$$



3.18.

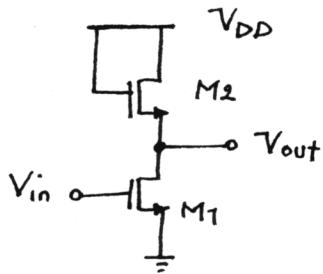

$$\left(\frac{W}{L}\right)_1 = 50/0.5 \quad \left(\frac{W}{L}\right)_2 = 10/0.5 \quad , \quad \lambda = \delta = 0$$

$M_T$  at the edge of the triode region,  $\rightarrow V_{out} = V_{in} - V_{TH1}$

$$I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} + V_{TH1} - V_{TH2})^2$$

$$\left(\frac{W}{L}\right)_1^{1/2} (V_{in} - V_{TH1}) = \left(\frac{W}{L}\right)_2^{1/2} (V_{DD} - V_{in}) \rightarrow (V_{in} - V_{TH1}) = \sqrt{\frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}} (V_{DD} - V_{in})$$

$$V_{in} = \left( \sqrt{\frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}} V_{DD} + V_{TH1} \right) / \left( 1 + \sqrt{\frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}} \right) = \left[ \left( \frac{10}{50} \right)^{1/2} \times 3 + 0.7 \right] / \left[ 1 + \left( \frac{10}{50} \right)^{1/2} \right] = 1.41V$$

$$A_V = - \sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}} = - \sqrt{\frac{50}{10}} = -2.236 .$$

At the edge of the triode region  $V_{out} = 1.41 - 0.7 = 0.71V$

50 mV into the triode region  $V_{out} = 0.71 - 50 \times 10^{-3} = 0.66V$


$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{TH2})^2 = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ (V_{in} - V_{TH1}) V_{out} - \frac{V_{out}^2}{2} \right]$$

$$V_{in} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \frac{(V_{DD} - V_{out} - V_{TH2})^2}{V_{out}} + \frac{V_{out}}{2} + V_{TH1} = \frac{10}{50} \frac{(3 - 0.66 - 0.7)^2}{0.66} + \frac{0.66}{2} + 0.7$$

$$V_{in} = 1.843V, \quad I_D = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ (V_{in} - V_{TH1}) V_{out} - \frac{V_{out}^2}{2} \right], \quad \frac{\partial I_D}{\partial V_{in}} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \cdot V_{out}$$

$$A_V = - \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \cdot V_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{TH2})} = - \frac{\frac{50}{0.5} \times 0.66}{\frac{10}{0.5} \times (3 - 0.66 - 0.7)} = -2.015$$

3.19.

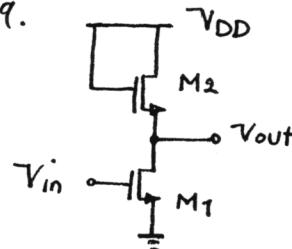

$$\left(\frac{W}{L}\right)_1 = 50/0.5 \quad \left(\frac{W}{L}\right)_2 = 10/0.5 \quad \lambda = 0$$

$$V_{out} = V_{in} - V_{TH1}, \quad V_{TH2} = V_{TH2,0} + \sqrt{2|f_F| + V_{SB}} - \sqrt{2|f_F|}$$

$$I_{D1} = I_{D2} \Rightarrow \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} + V_{TH1} - V_{TH2,0} - 0.45(\sqrt{0.9} + V_{out} - \sqrt{0.9}))^2$$

$$\left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \left(\frac{W}{L}\right)_2 \left[ V_{DD} - V_{in} - 0.45(\sqrt{0.9} + V_{in} - 0.7) - \sqrt{0.9} \right]^2$$

$$V_{in} = \sqrt{\frac{1}{5} \left[ 3 - V_{in} - 0.45(\sqrt{0.2 + V_{in}} - \sqrt{0.9}) \right]} + 0.7 \rightarrow \text{After enough iterations} \rightarrow$$

$$V_{in} = 1.3685, \quad V_{out} = 0.6685, \quad \eta = \frac{\sqrt{2}}{2(2|f_F| + V_{SB})^{1/2}} = \frac{0.45}{2(0.9 + 0.6685)^{1/2}} = 0.1796$$

$$A_V = -\frac{g_{m1}}{g_{m2}(1+\eta_2)} = -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}} \frac{1}{1+\eta_2} = -\sqrt{\frac{50}{10}} \frac{1}{1+0.1796} = -1.8955$$

$$V_{out} = 0.6685 - \frac{50 \times 10^{-3}}{50 \times 10^{-3}} = 0.6185$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{TH2})^2 = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ (V_{in} - V_{TH1}) V_{out} - \frac{V_{out}^2}{2} \right]$$

$$V_{TH2} = V_{TH2,0} + \sqrt{2|f_F| + V_{SB}} - \sqrt{2|f_F|} = 0.7 + 0.45(\sqrt{0.9 + 0.6185} - \sqrt{0.9}) = 0.8276$$


$$24.1453 = \frac{50}{0.5} \left[ (V_{in} - 0.7) 0.6185 - \frac{0.6185^2}{2} \right] \rightarrow V_{in} = 1.3996$$

$$\eta = \frac{0.45}{2(0.9 + 0.6185)^{1/2}} = 0.1825 \quad A_V = -\frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \cdot V_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TH2})(1+\eta_2)} =$$

$$\frac{\left(\frac{W}{L}\right)_1 V_{out}}{\left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - V_{TH2})(1+\eta_2)} = \frac{50 \times 0.6185}{10(3 - 0.6185 - 0.8276)(1+0.1825)} = -1.6829$$

3-26

3.20.

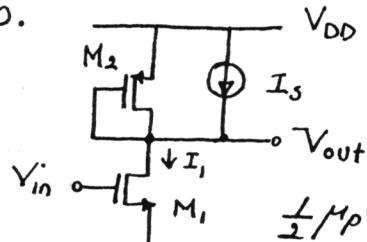

$$\left(\frac{W}{L}\right)_1 = 20/0.5, I_1 = 1 \text{ mA}, I_S = 0.75 \text{ mA}, \lambda = 0 \quad 3.27$$

$M_1$  at the edge of the triode region  $V_{out} = V_{in} - V_{TH1}$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{out} - |V_{TH2}|)^2 + I_S = \frac{1}{2} \mu_n C_{ox} (V_{in} - V_{TH1})^2 - 3$$


$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} + V_{TH1} - |V_{TH2}|)^2 + I_S = \frac{1}{2} \mu_n C_{ox} (V_{in} - V_{TH1})^2 - 3$$

$$(V_{in} - V_{TH1})^2 = \frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1} \rightarrow V_{in} = \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + V_{TH1} = 0.7 + \sqrt{\frac{2 \times 10^{-3}}{1.34225 \times 10^{-4} \times 20/0.5}} = 1.31$$


$$\frac{1}{2} \times 3.835 \times 10^{-5} \left(\frac{W}{L}\right)_2 (3 - 1.31 + 0.7 - 0.8)^2 + 0.75 \times 10^{-3} = 10^{-3}, \left(\frac{W}{L}\right)_2 = 5.159$$

$$A_V = - \frac{g_m 1}{g_m 2} = - \sqrt{\frac{\mu_n C_{ox}}{\mu_p C_{ox}} \times \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2} \times \frac{I_1}{I_2}} = - \sqrt{\frac{1.34225 \times 10^{-4}}{3.835 \times 10^{-5}} \times \frac{20/0.5}{5.159} \times \frac{10}{2.5 \times 10^{-4}}} = -10.418$$
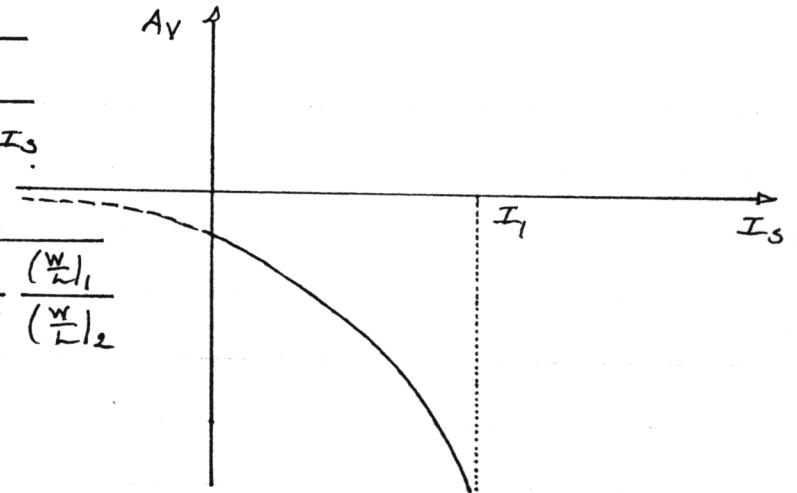
$$3.21. \quad A_V = - \sqrt{\frac{\mu_n C_{ox}}{\mu_p C_{ox}} \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2} \frac{I_1}{I_1 - I_S}}$$



3.22.

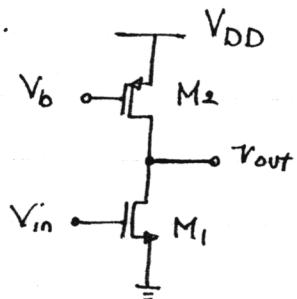

output voltage swing = 2.2

$$I_{D1} = I_{D2} = 1 \text{ mA}$$

$$A_V = 100$$

$$V_{out, min} = \left( \frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1} \right)^{1/2}, V_{out, max} = V_{DD} - \left( \frac{2I_{D2}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} \right)^{1/2}$$

3-28


$$V_{DD} - \left( \frac{2I_D}{\mu_p C_{ox} \left( \frac{W}{L} \right)_1} \right)^{1/2} - \left( \frac{2I_D}{\mu_n C_{ox} \left( \frac{W}{L} \right)_1} \right)^{1/2} = 2.2, \quad r_o = \frac{1}{\lambda_1 I_D} = \frac{1}{0.1 \times 10^{-3}} = 10K$$

$$r_{o2} = \frac{1}{\lambda_2 I_D} = \frac{1}{0.2 \times 10^{-3}} = 5K, \quad r_o // r_{o2} = \frac{10}{3}, \quad G_m, (r_o // r_{o2}) = 100 \rightarrow G_m = \frac{100 \times 3}{107} = 0.03$$

$$2\mu_n C_{ox} \left( \frac{W}{L} \right)_1 \times 10^{-3} = 9 \times 10^{-4} \rightarrow \left( \frac{W}{L} \right)_1 = \frac{9 \times 10^{-4}}{2 \times 1.34225 \times 10^{-4} \times 10^{-3}} = 3352.5796$$

$$3 - \left( \frac{2 \times 10^{-3}}{1.34225 \times 10^{-4} \times 3352.5796} \right)^{1/2} - 2.2 = \left( \frac{2 \times 10^{-3}}{3.835 \times 10^{-5} \left( \frac{W}{L} \right)_2} \right)^{1/2} \rightarrow \left( \frac{W}{L} \right)_2 = 96.97$$

3.23

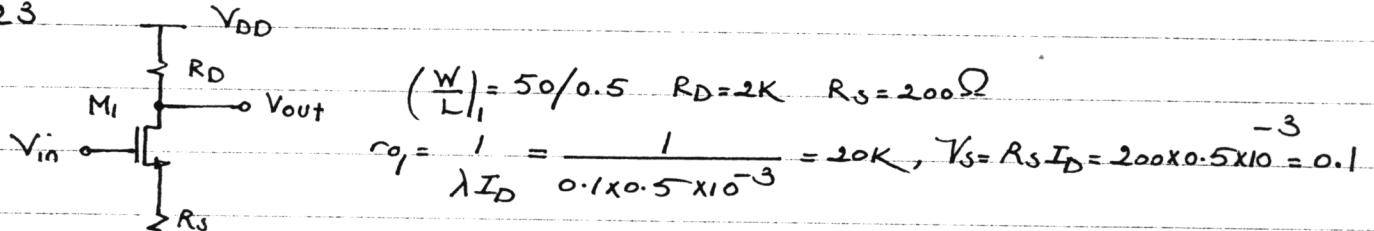

$$V_{TH1} = V_{TH1,0} + \lambda (\sqrt{2I_f f_l + V_{SB}} - \sqrt{2I_f f_l}) = 0.7 + 0.15 (\sqrt{0.9 + 0.1} - \sqrt{0.9})$$

$$V_{TH1} = 0.723, \quad V_{out} = V_{DD} - R_D \cdot I_D = 3 - 2 \times 10^3 \times 0.5 \times 10^{-3} = 2$$

$$V_{DS} = 2 - 0.1 = 1.9$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$G_m = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) = \sqrt{2\mu_n C_{ox} \left( \frac{W}{L} \right)_1 (1 + \lambda V_{DS}) I_D}$$

$$G_{m1} = \sqrt{2 \times 1.34225 \times 10^{-4} \times \frac{50}{0.5}} (1 + 0.1 \times 0.9) \times 0.5 \times 10^{-3} = 3.8249 \times 10^{-3}$$

$$\gamma_1 = \frac{0.45}{2(0.1+0.9)^{1/2}} = 0.225 \quad G_m = \frac{G_{m1} \cdot r_{o1}}{R_S + [1 + (1 + \gamma_1) G_{m1} \cdot R_S] r_{o1}} =$$

$$G_m = \frac{3.8249 \times 10^{-3} \times 20 \times 10^{-3}}{200 + [1 + (1 + 0.225) 3.8249 \times 10^{-3} \times 200] 20 \times 10^{-3}} = 1.9644 \times 10^{-3}$$

$$R_{out} = \left[ 1 + (G_m + G_{m1}) r_o \right] R_S + r_o$$

Seen looking down at the drain of M1

$$R_{out} = \left[ 1 + (1+0.225) 3.8249 \times 10^{-3} \right] 200 + 20 \times 10^3 = 20.2 \times 10^3 \quad 3-29$$

$$R_{out, total} = R_{out} // R_D = 1819.8274, A_V = -G_m \cdot R_{out, total} = -1.96 \times 10^{-3} \times 1819.8 \quad 3-30$$

$$A_V = -3.57$$

$V_{out} = V_{in} - V_{THI}$  @ the edge of the triode region

$$V_{in} = V_{GS1} + R_S I_D$$

$$V_{DD} - R_D I_D = V_{out}, V_{DD} - R_D I_D = V_{GS1} + R_S I_D - V_{THI}, V_{DD} - (R_S + R_D) I_D = V_{GS1} - V_{THI}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS1} - V_{THI})^2 = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 [V_{DD} - (R_S + R_D) I_D]^2 = \frac{1}{2} \times 1.34225 \times 10^{-4} \times \frac{50}{0.5} \left[ 3 - (2000 + 200) I_D \right]^2$$

$$I_D = 6.71125 \times 10^{-3} (3 - 2200 I_D)^2 \rightarrow 32482.15 I_D^2 - 89.5885 I_D + 60.40125 \times 10^{-3} = 0 \quad 3-31$$


$$I_{D1} = 1.5844 \times 10^{-3} \text{ (not acceptable)}, I_{D2} = 1.17355 \times 10^{-3} \text{ (acceptable!)} \quad 3-32$$

$$V_{in} = V_{DD} - R_D I_D + V_{THI} = 3 - 2000 \times 1.17355 \times 10^{-3} + 0.7 = 1.35285 V \quad 3-33$$

$$G_{m1} = \sqrt{2 \times 1.34225 \times 10^{-4} \times \frac{50}{0.5} \times 1.17355 \times 10^{-3}} = 5.6128 \times 10^{-3} \quad 3-34$$

$$G_m = \frac{G_{m1}}{1 + G_{m1} \cdot R_S} = 2.6443 \times 10^{-3} \quad A_V = -G_m R_D = -2.6443 \times 10^{-3} \times 2000 = -5.2887 \quad 3-35$$

3.24

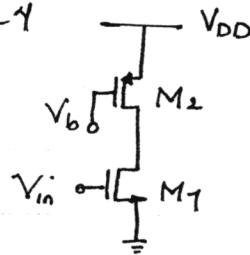

$$A_V = -5, \left( \frac{W}{L} \right)_1 = 20/0.5, I_{D1} = 0.5 mA, V_b = 0$$

$$G_{m1} = 2 \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (1 + \lambda V_{DS}) I_D \quad 3-36$$

$$G_{m1} = \sqrt{2 \times 1.34225 \times 10^{-4} \times \frac{20}{0.5} (1 + 0.1 V_{DS}) \times 0.5 \times 10^{-3}} \quad 3-37$$

$$r_{o1} = \frac{1}{\lambda n I} = \frac{1}{0.1 \times 0.5 \times 10^{-3}} = 20K, r_{o2} = \frac{1}{\lambda p I} = \frac{1}{0.2 \times 0.5 \times 10^{-3}} = 10K$$

The key point here is that the channel length modulation effect in M<sub>1</sub> cannot be neglected because its drain-source voltage is quite large. We take this effect into account with a few iterations.

First we let  $V_{DS1} = 0$ , then, we have,  $g_{m1} = 2.3171 \times 10^{-3}$  (as  $A_v = -5$ )

3-31

$$R_{out, total} = 2157.86 \Omega$$

$$r_{o2} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{TH2}| - V_{SD})} = 2168.835 \Omega$$

$$0.5 \times 10^{-3} = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ (V_{SG} - |V_{TH2}|) V_{SD} - \frac{V_{SD}^2}{2} \right], \text{ by dividing these two relations together.}$$

$$1.2094 = \frac{(3-0.8)V_{SD} - 0.5V_{SD}^2}{3-0.8-V_{SD}} = \frac{4.4V_{SD} - V_{SD}^2}{4.4 - 2V_{SD}}, V_{SD}^2 - 6.8188V_{SD} + 5.3214 = 0$$

$V_{SD} = 0.8909$ , now second iteration starts, with the aid of the value we obtain for  $V_{SD}$  (or  $V_{DS1}$ ) from the first iteration, we have:

$$g_{m1} = 2.5489 \times 10^{-3}, R_{out} = 1961.6020 \Omega$$

$$r_{o2} = 2174.9182, 1.087459 = \frac{4.4V_{SD} - V_{SD}^2}{4.4 - 2V_{SD}}, V_{SD}^2 - 6.5749V_{SD} + 4.7848 = 0$$

$$V_{SD} = 0.8336V$$

Third iteration starts now:

By substituting the value of  $V_{SD}$  from the second iteration in the relation for  $g_{m1}$ , we get:

$$g_{m1} = 2.5558 \times 10^{-3}, R_{out} = 1956.3119, r_{o2} = 2168.4169 \Omega$$

$$1.0842 = \frac{4.4V_{SD} - V_{SD}^2}{4.4 - 2V_{SD}}, V_{SD}^2 - 6.5681V_{SD} + 4.77051 = 0$$

$$V_{SD} = 0.8315 \frac{4.4 - 2V_{SD}}$$

By doing the forth iteration:

$$g_{m1} = 2.5560 \times 10^{-3}$$

$$R_{out} = 1956.1662, r_{o2} = 2168.2379, 1.0841189 = \frac{4.4V_{SD} - V_{SD}^2}{4.4 - 2V_{SD}}$$

$$V_{SD}^2 - 6.5682V_{SD} + 4.77012 = 0$$

$$\boxed{V_{SD} = 0.8315}$$

$$I = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ (V_{GS} - |V_{TH2}|) V_{SD} - \frac{V_{SD}^2}{2} \right] \cdot \left(\frac{W}{L}\right)_2 = \frac{0.5 \times 10^{-3}}{3.835 \times 10^{-5} \left[ (3 - 0.8) / 0.8315 - \frac{0.8315^2}{2} \right]} \\ \left(\frac{W}{L}\right)_2 = 8.7878$$

If M<sub>1</sub> is at the edge of the triode region: V<sub>out</sub> = V<sub>in</sub> - V<sub>TH1</sub> = V<sub>in</sub> - 0.7

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH1}) = I_{D2} = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ (V_{DD} - |V_{TH2}|)(V_{DD} - V_0) - \frac{(V_{DD} - V_0)^2}{2} \right] \times \\ V_{out} = \sqrt{\frac{2 \times 3.835 \times 10^{-5}}{1.34225 \times 10^{-4}} \frac{8.7878}{40} \left[ 2.2(3 - V_0) - \frac{(3 - V_0)^2}{2} \right] (1.6 - 0.2V_0)} \quad (1 + 0.2(V_{DD} - V_0))$$

$$V_0 = 0.6663, V_{in} = 1.3663, I_{m1} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH1}) = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_{out} = \\ 1.34225 \times 10^{-4} \times \frac{20}{0.5} \times 0.6663 = 3.5773 \times 10^{-3}$$

However, M<sub>2</sub> is no longer in triode region because V<sub>0</sub> = 0.66 < V<sub>b</sub> + |V<sub>TH2</sub>| = 0.8

Therefore, we should recalculate V<sub>0</sub> with the assumption that M<sub>2</sub> is saturated

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_0^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_0 - |V_{TH2}|)^2 (1 + \lambda_p (V_{DD} - V_0)) \\ 536.9 V_0^2 + 32.623 V_0 - 260.9845 = 0, V_{out} = 0.6674, V_{in} = 1.3674$$

$$I_{m1} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH}) = 3.5837 \times 10^{-3}, I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 V_0^2 = 1.196 \times 10^{-3}$$

$$r_{out} = r_0, \text{ if } r_{out} = \frac{1}{(\lambda_p + \lambda_n) I} = 2786.962 \Omega$$

$$A_V = -I_{m1} \cdot r_{out} = -9.9877$$

$$V_{out} = 0.8, \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2 (1 + \lambda_p (V_{DD} - V_0))$$

$$1.34225 \times 10^{-4} \times 40 \times (V_{GS} - 0.7)^2 = 3.835 \times 10^{-5} \times 8.7878 (3 - 0.8)^2 (1 + 0.2(3 - 0.8))$$

$$V_{in} = 1.3614$$

3-32



$$g_{m1} = \mu_n C_{ox} \left( \frac{w}{L} \right)_1 (V_{GS} - V_{TH1}) = 3.5512 \times 10^{-3}$$

$$I = \frac{1}{2} \mu_n C_{ox} \left( \frac{w}{L} \right)_1 (V_{GS} - V_{TH1})^2 = 1.1744 \times 10^{-3}$$

$$r_{out} = \frac{1}{(\lambda_P + \lambda_N) I} = 2838.2553$$

$$A_V = - g_{m1} \cdot r_{out} = -10.08$$

3.25 &amp; 3.32

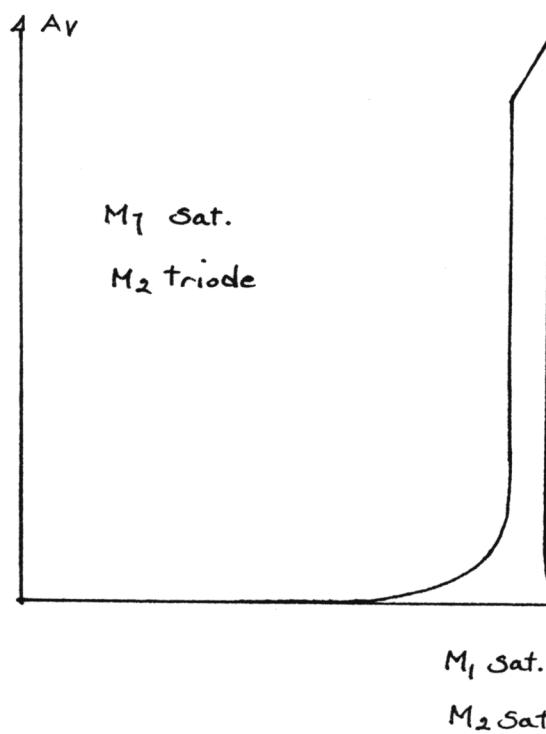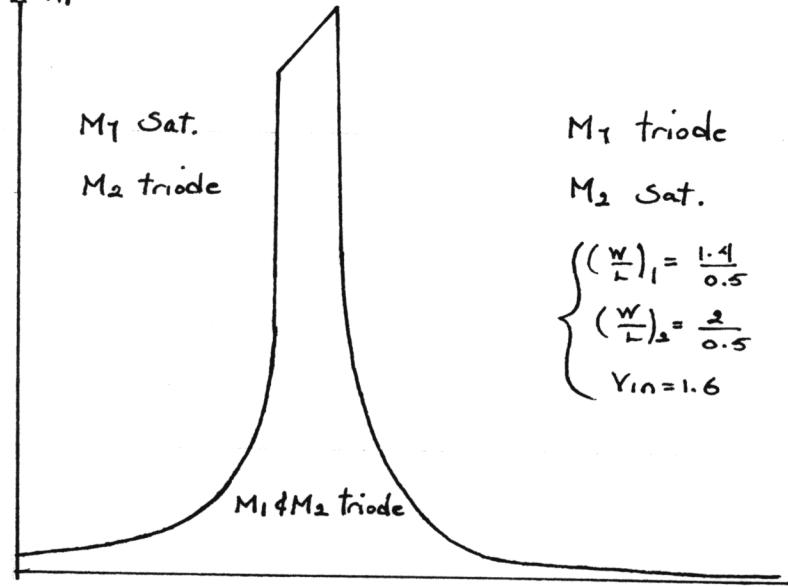

M<sub>1</sub> triode      voltage gain in (a) is  
M<sub>2</sub> sat.      less than that in (b),

$\left\{ \begin{array}{l} \left( \frac{w}{L} \right)_1 = \frac{1.4}{0.5} \\ \left( \frac{w}{L} \right)_2 = \frac{2}{0.5} \\ V_{in} = 0.8938 \end{array} \right.$  because when V<sub>b</sub> sweeps all the way from 0 to V<sub>DD</sub>, nowhere are both devices simultaneously in the saturation region.

3.26.

$V_{in} - V_{out} = 1V, I_{D1} = I_{D2} = 0.5 \text{ mA}, V_{GS2} - V_{GS1} = 0.5$

 $\lambda = 0$ 
 $I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{out} - V_{TH1})^2 =$ 
 $\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_b - V_{TH2})^2$ 
 $0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \left( \frac{W}{L} \right)_1 (1 - 0.7)^2$ 
 $\left( \frac{W}{L} \right)_1 = 82.77 \quad V_{GS2} = 0.5 + 1 = 1.5$ 
 $0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \left( \frac{W}{L} \right)_2 (1.5 - 0.7)^2 \rightarrow \left( \frac{W}{L} \right)_2 = 11.64$

3.39

$\gamma = 0.45 \text{ V}^{-1}, V_{in} = 2.5 \text{ V}, V_{in} - V_{out} = 1, I_{D1} = I_{D2} = 0.5 \text{ mA}, V_{GS2} - V_{GS1} = 0.5$ 
 $V_{out} = V_{in} - 1 = 2.5 - 1 = 1.5, V_{GS2} = 0.5 + (2.5 - 1.5) = 1.5 \text{ V}$ 
 $V_{TH1} = V_{THO} + \gamma (\sqrt{2|f_f| + V_0} - \sqrt{2|f_f|}) = 0.7 + 0.45 (\sqrt{0.9 + 1.5} - \sqrt{0.9}) = 0.97022$

$I_{D1} = I_{D2} = 0.5 \times 10^{-3} = \frac{1}{2} \mu_n C_{ox} S_1 (V_{GS1} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} S_2 (V_{GS2} - V_{TH2})^2$ 
 $0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} S_1 (1 - 0.97)^2 = \frac{1}{2} \times 1.34225 \times 10^{-4} S_2 (1.5 - 0.7)^2$ 
 $S_1 = \left( \frac{W}{L} \right)_1 = 82.78$ 
 $S_2 = \left( \frac{W}{L} \right)_2 = 11.64$


$V_{out} = V_b - V_{TH2} = 1.5 - 0.7 = 0.8$

$V_{TH1} = 0.7 + 0.45 (\sqrt{0.9 + 0.8} - \sqrt{0.9}) = 0.8598$

$0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \times 82.78 (V_{in} - 0.8 - 0.8598)^2$

$V_{in} = 1.6897$

3.26.

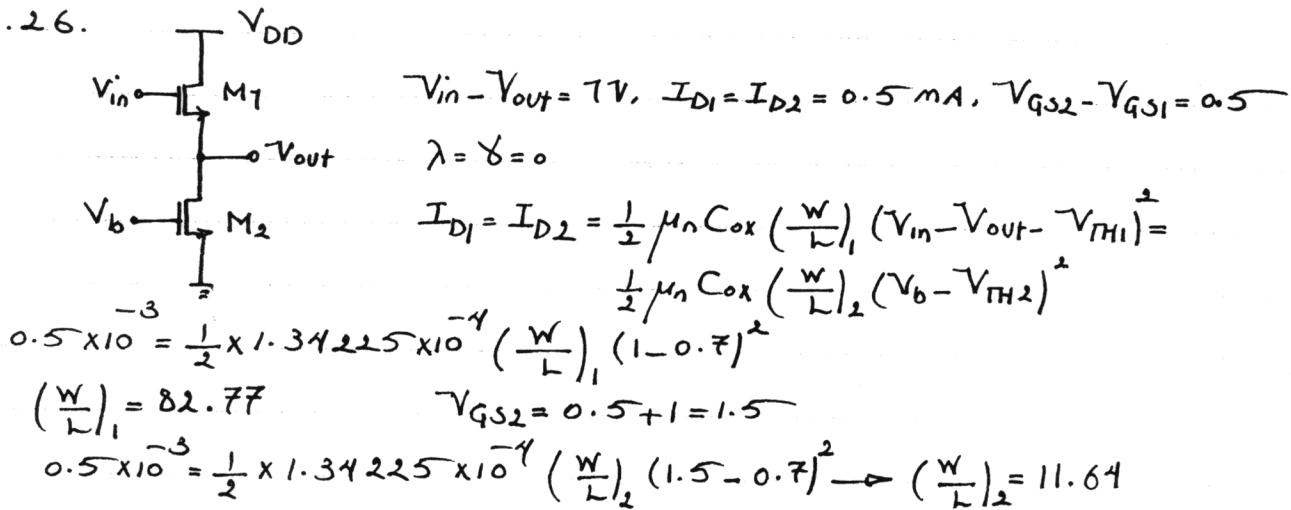

3.33

$$\gamma = 0.45V^{-1}, V_{in} = 2.5V, V_{in} - V_{out} = 1, I_{D1} = I_{D2} = 0.5mA, V_{GS2} - V_{GS1} = 0.5$$

$$V_{out} = V_{in} - 1 = 2.5 - 1 = 1.5, V_{GS2} = 0.5 + (2.5 - 1.5) = 1.5V$$

$$V_{TH1} = V_{TH0} + \gamma (\sqrt{2|f_f| + V_0} - \sqrt{2|f_f|}) = 0.7 + 0.45 (\sqrt{0.9 + 1.5} - \sqrt{0.9}) = 0.97022$$

$$I_{D1} = I_{D2} = 0.5 \times 10^{-3} = \frac{1}{2} \mu_n C_{ox} S_1 (V_{GS1} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} S_2 (V_{GS2} - V_{TH2})^2$$

$$0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} S_1 (1 - 0.97)^2 = \frac{1}{2} \times 1.34225 \times 10^{-4} S_2 (1.5 - 0.7)^2$$

$$S_1 = \left( \frac{W}{L} \right)_1 = 82.78$$

$$S_2 = \left( \frac{W}{L} \right)_2 = 11.64$$



$$V_{out} = V_b - V_{TH2} = 1.5 - 0.7 = 0.8$$

$$V_{TH1} = 0.7 + 0.45 (\sqrt{0.9 + 0.8} - \sqrt{0.9}) = 0.8598$$

$$0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \times 82.78 (V_{in} - 0.8 - 0.8598)^2$$

$$V_{in} = 1.6897$$


3.27.

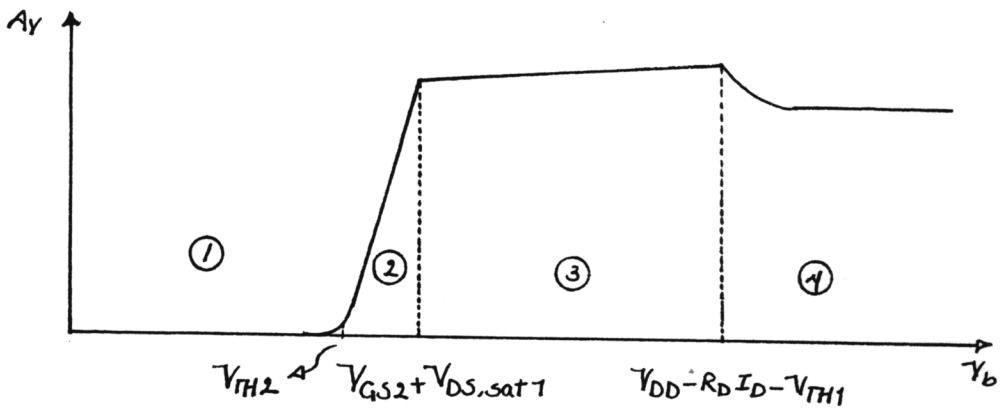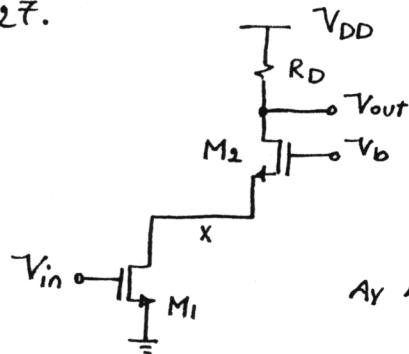

- ① In this region  $V_b$  is less than  $V_{TH2}$ , so  $M_1$  and  $M_2$  are off. It is worth mentioning that  $M_2$  is saturated off and  $M_1$  is off in triode region.
- ②  $V_b$  is increasing above  $V_{TH2}$ , as a result, a current establishes in circuit.  $M_1$  operates in triode region and  $M_2$  does in saturation. The higher  $V_b$ , the higher the drain-source voltage of  $M_1$ , increasing the output impedance of  $M_1$  which, in turn, Causes the small signal voltage gain of the circuit increases.
- ③ Both devices are in Saturation region and the maximum gain is attainable in this region. The slight increase in  $Av$  is because of increasing the transconductance of  $M_1$  with increasing  $V_x$  (or  $V_b$ ).
- ④  $M_2$  enters the triode region, as a result, the total output impedance decreases down to the limit of  $r_o \parallel R_D$ . Consequently, the small signal voltage gain experiences a similar change.

3-34

3.28

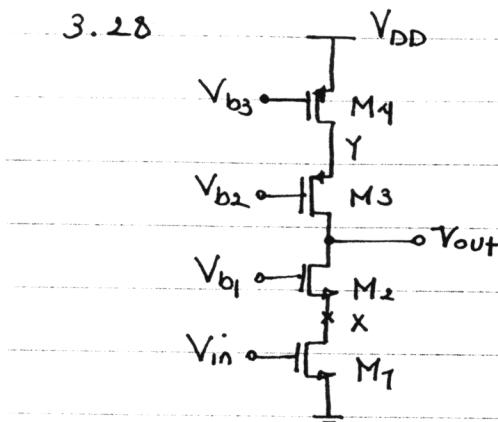

$$\text{output swing} = 1.9 \text{ V}$$

$$I_{bias} = 0.5 \text{ mA}$$

$$Y = 0 \quad \left(\frac{W}{L}\right)_{1-4} = \left(\frac{W}{L}\right)$$

$$V_{b_1} - V_{TH1} < V_{out} < V_{b_2} + V_{TH3}$$

$$V_{b_2} + V_{TH3} - (V_{b_1} - V_{TH1}) = 1.9$$

$$V_{b_2} + 0.8 - V_{b_1} + 0.7 = 1.9, \quad V_{b_2} - V_{b_1} = 0.4$$

$$0.5 \times 10^{-3} = \frac{1}{2} \mu_n C_{ox} S (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} S (V_{b_1} - V_x - V_{TH2})^2 = \\ \frac{1}{2} \mu_p C_{ox} S (V_y - V_{b_2} - |V_{TH3}|)^2 = \frac{1}{2} \mu_p C_{ox} S (V_{DD} - V_{b_3} - |V_{TH4}|)^2$$

$$V_{DD} - V_{SDmin,4} - V_{SDmin,3} - V_{SDmin,2} - V_{SDmin,1} = 1.9$$

$$1.1 = \left( \frac{2I_D}{\mu_p C_{ox} S} \right)^{1/2} + \left( \frac{2I_D}{\mu_p C_{ox} S} \right)^{1/2} + \left( \frac{2I_D}{\mu_n C_{ox} S} \right)^{1/2} + \left( \frac{2I_D}{\mu_n C_{ox} S} \right)^{1/2}$$

$$1.1 = 2 \sqrt{2I_D} \left( \frac{1}{\sqrt{\mu_p C_{ox}}} + \frac{1}{\sqrt{\mu_n C_{ox}}} \right) \frac{1}{\sqrt{S}} \rightarrow S = \frac{8I_D (\sqrt{\mu_p C_{ox}} + \sqrt{\mu_n C_{ox}})^2}{1.1^2}$$

$$S = \frac{8 \times 0.5 \times 10^{-3} \left( \frac{1}{\sqrt{1.34225 \times 10^{-4}}} + \frac{1}{\sqrt{3.835 \times 10^{-5}}} \right)^2}{1.1^2} = 202.98 \rightarrow S = 203$$

$$V_{DSmin,1} = \left( \frac{2I_D}{\mu_n C_{ox} S} \right)^{1/2} = \left( \frac{2 \times 0.5 \times 10^{-3}}{1.34225 \times 10^{-4} \times 203} \right)^{1/2} = 0.1915$$

$$V_{SDmin,4} = \left( \frac{2 \times 0.5 \times 10^{-3}}{3.835 \times 10^{-5} \times 203} \right)^{1/2} = 0.3584$$

$$0.5 \times 10^{-3} = \frac{1}{2} \times 1.34225 \times 10^{-4} \times 203 (V_{b_1} - V_x - 0.7)^2$$

$$V_{b_1} - V_x = 0.8915$$

$$0.5 \times 10^{-3} = \frac{1}{2} \times 3.835 \times 10^{-5} \times 203 (V_y - V_{b_2} - 0.8)^2$$

3.35

$$V_y - V_{b2} = 1.1584$$

$$V_{b2} - V_{b1} = 0.4$$

$$\text{If } V_x = 0.1915 \rightarrow V_{b1} = 1.083, V_{b2} = 1.483, V_y = 2.6414$$

$V_{SD4} = V_{DD} - V_y = 0.3586$ , as a result,  $M_1$  and  $M_2$  are at the edge of the triode region.

$$g_{m1} = \sqrt{2\mu_n C_{ox} S (1 + \lambda V_{DS}) I_D} = \sqrt{2 \times 1.34225 \times 10^{-4} \times 203 \times 0.5 \times 10^{-3}}$$

$$g_{m1} = g_{m2} = 5.2199 \times 10^{-3}$$

$$r_{o1} = r_{o2} = \frac{1}{0.1 \times 0.5 \times 10^{-3}} = 20K \quad r_{o3} = r_{o4} = \frac{1}{0.2 \times 0.5 \times 10^{-3}} = 10K$$

$$G_m = \frac{g_{m1} \cdot r_{o1} \cdot (1 + g_{m2} \cdot r_{o2})}{r_{o1} \cdot r_{o2} g_{m2} + r_{o1} + r_{o2}} = \frac{5.2199 \times 10^{-3} \times 20 \times 10^3 \times (20 \times 10^3 \times 5.2199 \times 10^{-3} + 1)}{(20 \times 10^3)^2 \times 5.2199 \times 10^{-3} + 2 \times 20 \times 10^3}$$

$$G_m = 5.17 \times 10^{-3}, \text{ neglecting the body effect.}$$

$$R_{out} = \left[ (1 + g_{m2} r_{o2}) r_{o1} + r_{o2} \right] / \left[ (1 + g_{m3} r_{o3}) r_{o1} + r_{o3} \right]$$

$$R_{out} = \left[ (1 + 5.2199 \times 10^{-3} \times 20 \times 10^3) 20 \times 10^3 + 20 \times 10^3 \right] / \left[ (1 + 2.79 \times 10^{-3} \times 10 \times 10^3) 10 \times 10^3 + 10 \times 10^3 \right]$$

$$R_{out} = 262.1766 \times 10^3, \quad A_V = -G_m R_{out} = -5.17 \times 10^{-3} \times 262.1766 \times 10^3$$

$$A_V = -1355.45$$

$$g_{m3} = g_{m4} = \sqrt{2 \times 3.835 \times 10^{-5} \times 203 \times 0.5 \times 10^{-3}} = 2.79 \times 10^{-3}$$

## Chapter 4: Differential Amplifiers.

4.1

$$(a) A_v \equiv - \frac{g_{mn}}{g_{mp}} = - \sqrt{\frac{\mu_n (W/L)_N}{\mu_p (W/L)_P}} \quad (4.52)$$

$$A_v = - \sqrt{\frac{350}{100} \times \frac{50/0.5}{50/1}} = - \sqrt{7} = - 2.65$$

$$(b) A_v = - g_{mn} (r_{on} \parallel r_{op}) \quad (4.53)$$

$$I_D = \frac{I_{SS}}{2} = 0.5 \text{ mA} \quad \mu_n C_{ox} = 350 \times \frac{8.85 \times 10^{-14} \times 3.9}{9 \times 10^7} = 0.134 \text{ mA/V}^2$$

$$g_{mn} = \sqrt{2 I_D \mu_n C_{ox} \frac{W}{L}} = \sqrt{2 \times 0.5 \text{ mA} \times 0.134 \text{ mA/V}^2 \times 100} = 3.66 \text{ mS}^{-1}$$

$$L_N = 0.5 \mu \Rightarrow \lambda_n = 0.1 \Rightarrow r_{on} = \frac{1}{\lambda_n I_D} = \frac{1}{0.1 \times 0.5 \text{ mA}} = 20 \text{ k}\Omega$$

$$L_P = 1 \mu ; \lambda_P = 0.2 \text{ for } L = 0.5 \mu ; \lambda \propto \frac{1}{L} \Rightarrow \lambda_P = 0.1$$

$$r_{op} = \frac{1}{\lambda_P I_D} = \frac{1}{0.1 \times 0.5 \text{ mA}} = 20 \text{ k}\Omega$$

$$A_v = - g_{mn} (r_{on} \parallel r_{op}) = - 3.66 \left( 20^k \parallel 20^k \right) = - 36.6$$

$$(V_{in,cm})_{min} = 0.4 + V_{GSI} \quad \text{for both circuits}$$


$$V_{GSI} = V_{TH} + \sqrt{\frac{2 I_D}{\mu_n C_{ox} (W/L)_N}} = 0.7 + \sqrt{\frac{2 \times 0.5 \mu \text{A}}{0.134 \text{ mA} \times 100}} = 0.7 + 0.27 = 0.97 \text{ V}$$

$$\rightarrow (V_{in, CM})_{min} = 0.4 + 0.97 = 1.37^v$$

max output voltage swing:

$$(a) (V_{out1,2})_{max} = V_{DD} - |V_{TH,P}| = 3 - 0.8 = 2.2^v$$

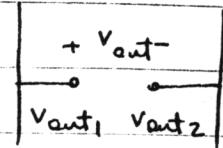There are two constraints for  $(V_{out1,2})_{min}$ :



$$1) M_1 \text{ enters triode: } (V_{out1,2})_{min} = 0.4 + V_{GS1} - V_{TH,n} \\ = 0.4 + 0.97 - 0.7 = 0.67^v$$

2) all of  $I_{SS}$  goes through  $M_3$ :

$$(V_{out1,2})_{min} = V_{DD} - |V_{GS3}| = V_{DD} - |V_{TH,P}| + \sqrt{\frac{2 I_{SS}}{\mu_p C_{ox} (\frac{W}{L})_3}}$$

$$= 3 - 0.8 - \sqrt{\frac{2 \times 1^m}{38.3 \mu \times 50}} = 3 - 0.8 - 1.02 = 1.18^v$$

$$\mu_p C_{ox} = 100 \times \frac{8.85 \times 10^{-14} \times 3.9}{9 \times 10^{-7}} = 38.3 \mu A/v^2 \Rightarrow (V_{out1,2})_{min} = 1.18^v$$

$$\text{Max swing of } V_{out1,2} = 2.2 - 1.18 = 1.02^v$$

$$\text{Max swing of } V_{out} = 2 \times 1.02 = 2.04^v$$

$$(b) (V_{out1,2})_{max} = V_{DD} - |V_{GS3} - V_{TH,P}| = 3 - 0.72 = 2.28^v$$

$$(V_{out1,2})_{min} = 0.4 + V_{GS1} - V_{TH,n} = 0.67^v$$

$$\text{Max swing of } V_{out} = 2(2.28 - 0.67) = 3.22^v$$

$$4.2 \quad I_{SS} = 1 \text{ mA}$$

(a)

$$A_v = -g_m (\frac{1}{g_m} \| r_o \| r_o \| r_o ) \approx -\frac{g_m}{g_m} = \sqrt{\frac{\mu_n}{\mu_p} \times \frac{I_{D1}}{I_{D3}}} \\ = \sqrt{\frac{350}{100} \cdot \frac{\frac{1}{2} I_{SS}}{0.2 \frac{I_{SS}}{2}}} = -4.18$$

$$(b) \quad I_{D5} = I_{D6} = 0.8 \left( \frac{I_{SS}}{2} \right) = 0.4 \text{ mA}$$


$$|V_{GS5}| = V_{DD} - V_b \Rightarrow V_b = V_{DD} - |V_{GS5}| = V_{DD} - |V_{TH,P}| - \sqrt{\frac{2I_{D5}}{\mu_p C_{ox} \frac{W}{L}}}$$

$$V_b = 3 - 0.8 - \sqrt{\frac{2 \times 0.4}{38.3 \mu_p \times 100}} = 1.74$$

(c)

$$(V_{out1,2})_{max} = \min(V_b + |V_{TH,P}|, V_{DD} - |V_{TH,P}|)$$

$$= (1.74 + 0.8, 3 - 0.8) = 2.2^v$$

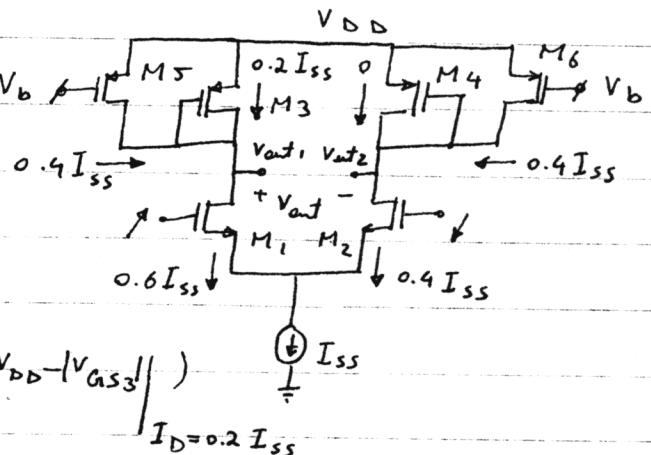

$$(V_{out1,2})_{min} = \max(V_{I_{SS},min} + |V_{GS1}| - |V_{TH,n}|, V_{DD} - |V_{GS3}|) \quad I_D = 0.6 I_{SS}$$

$$\frac{|V_{GS1}|}{I_D = 0.6 I_{SS}} = V_{TH,n} + \sqrt{\frac{2 \times 0.6 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = V_{TH,n} + 0.299^v$$

$$\frac{|V_{GS3}|}{I_D = 0.2 I_{SS}} = |V_{TH,P}| + \sqrt{\frac{2 \times 0.2 I_{SS}}{\mu_p C_{ox} \frac{W}{L}}} = 0.8 + 0.323^v = 1.12^v$$

$$(V_{out1,2})_{min} = \max(0.4 + 0.299, 3 - 1.12) = 1.88^v$$

$$\text{Max swing of } V_{out} = 2(2.2 - 1.88) = 0.64^v$$

$$4.2 \quad I_{SS} = 1 \text{ mA}$$

(a)

$$A_v = -g_m (\frac{1}{g_{m3}} \parallel r_o \parallel r_{o3} \parallel r_{o5}) \approx -\frac{g_m}{g_{m3}} = \sqrt{\frac{\mu_n}{\mu_p} \times \frac{I_{D1}}{I_{D3}}} \\ = \sqrt{\frac{350}{100} \cdot \frac{\frac{1}{2} I_{SS}}{0.2 \frac{I_{SS}}{2}}} = -4.18$$

$$(b) \quad I_{D5} = I_{D6} = 0.8 \left( \frac{I_{SS}}{2} \right) = 0.4 \text{ mA}$$


$$|V_{GS5}| = V_{DD} - V_b \Rightarrow V_b = V_{DD} - |V_{GS5}| = V_{DD} - |V_{TH,P}| - \sqrt{\frac{2I_{D5}}{\mu_p C_{ox} \frac{W}{L}}}$$

$$V_b = 3 - 0.8 - \sqrt{\frac{2 \times 0.4 \text{ mA}}{38.3 \mu_A \times 100}} = 1.74$$

(c)

$$(V_{out1,2})_{max} = \min(V_b + |V_{TH,P}|, V_{DD} - |V_{TH,P}|)$$
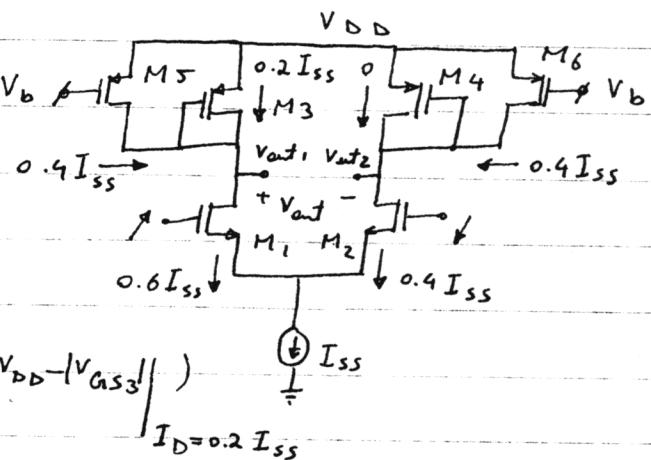
$$= (1.74 + 0.8, 3 - 0.8) = 2.2 \text{ V}$$



$$(V_{out1,2})_{min} = \max(V_{I_{SS},min} + V_{GS1} \Big|_{I_D=0.6 I_{SS}}, V_{DD} - |V_{GS3}| \Big|_{I_D=0.2 I_{SS}})$$

$$\frac{|V_{GS1}|}{I_D=0.6 I_{SS}} = V_{TH,n} + \sqrt{\frac{2 \times 0.6 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = V_{TH,n} + 0.299 \text{ V}$$



$$\frac{|V_{GS3}|}{I_D=0.2 I_{SS}} = |V_{TH,P}| + \sqrt{\frac{2 \times 0.2 I_{SS}}{\mu_p C_{ox} \frac{W}{L}}} = 0.8 + 0.323 \text{ V} = 1.12 \text{ V}$$

$$(V_{out1,2})_{min} = \max(0.4 + 0.299, 3 - 1.12) = 1.88 \text{ V}$$



$$\text{Max swing of } V_{out} = 2(2.2 - 1.88) = 0.64 \text{ V}$$

4.3



(a)

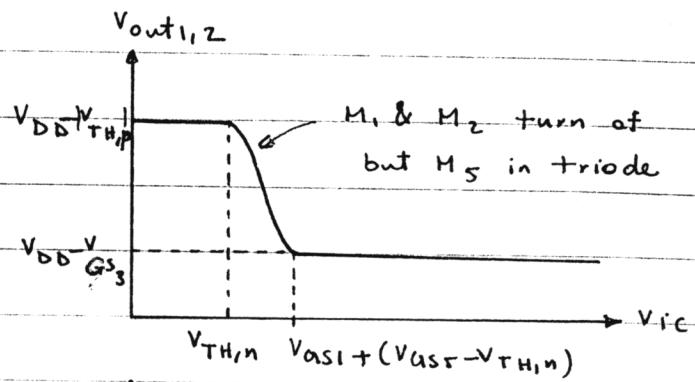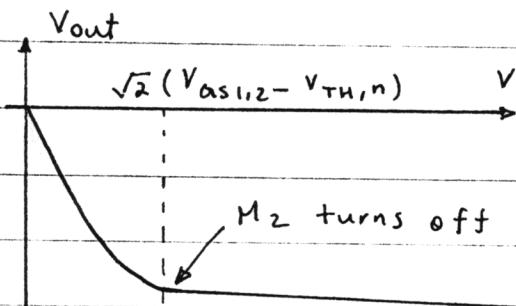



(b)

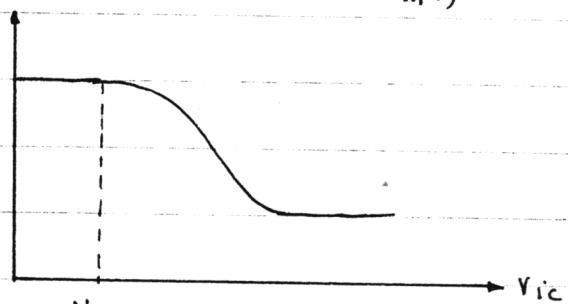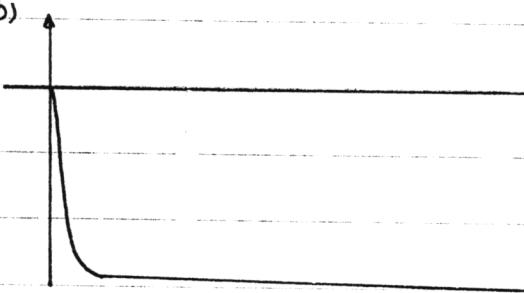



(c)

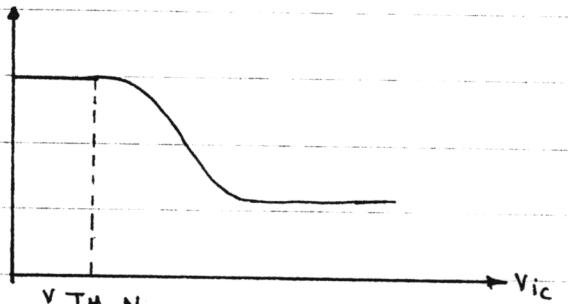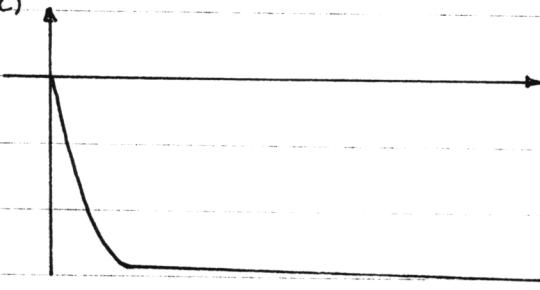

(d)

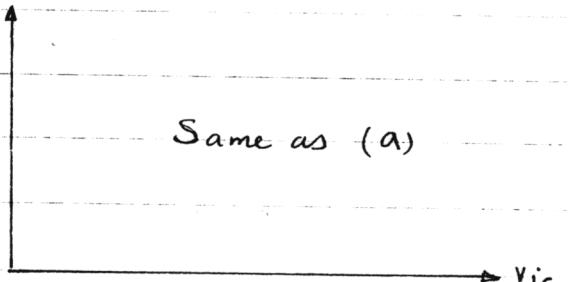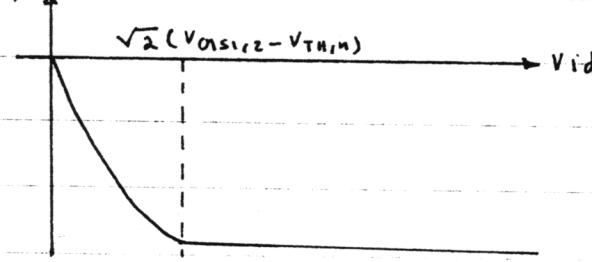


(e)

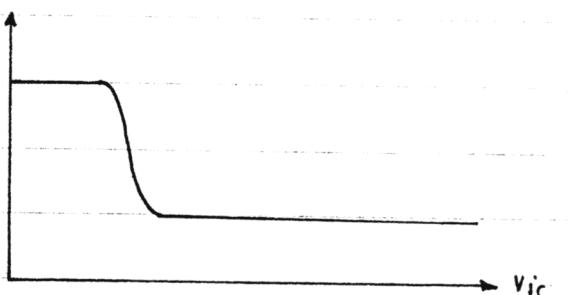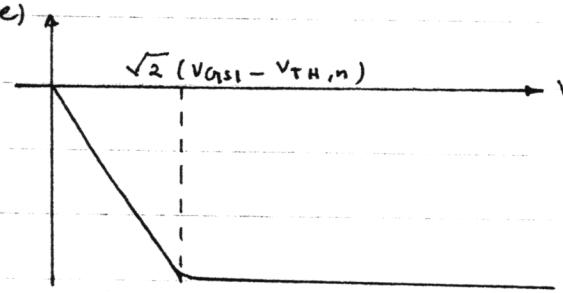


4.4


(a)

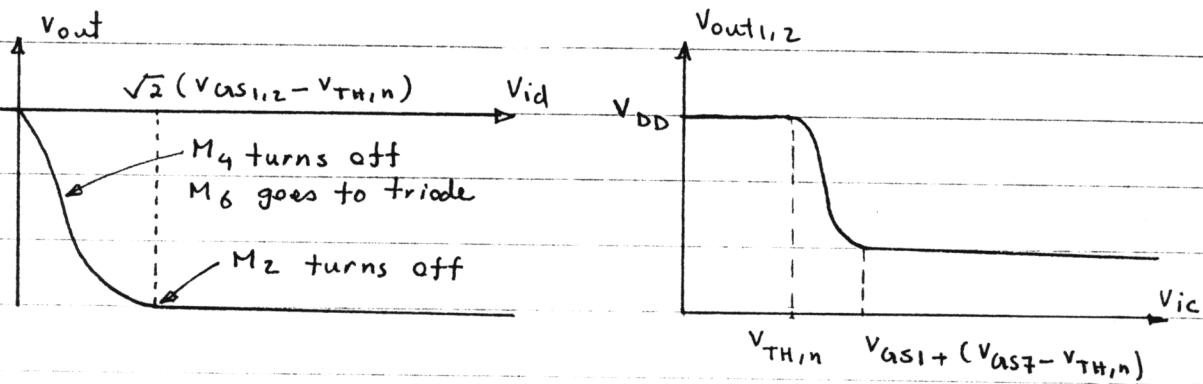

(b)

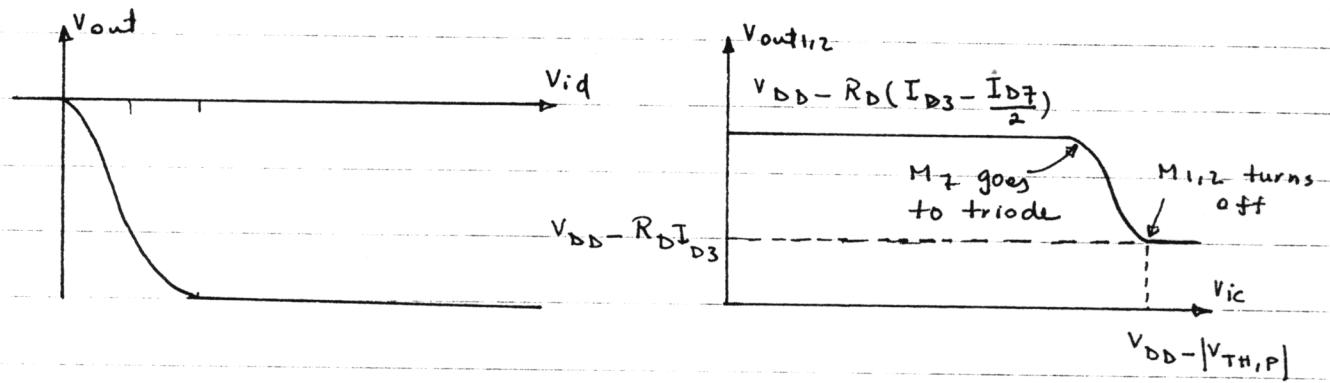

(c)

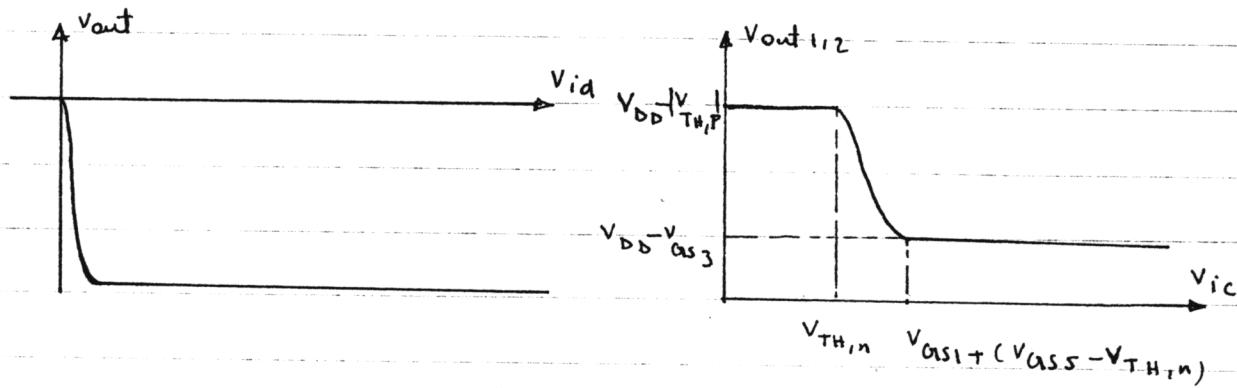


4.5

Fig. 4.35 Using half circuit we have:

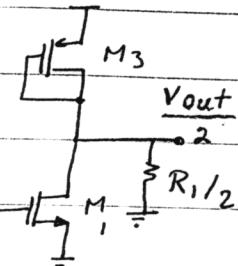(a) we define  $V_{id} = V_{in_1} - V_{in_2}$

$$A_v = \frac{V_{out}}{V_{id}} = g_{m_1} \left( \frac{1}{g_{m_3}} \parallel \frac{R_1}{2} \parallel r_{o_1} \parallel r_{o_3} \right)$$


$$\approx -g_{m_1} \left( \frac{1}{g_{m_3}} \parallel \frac{R_1}{2} \right) = -\frac{g_{m_1} R_1}{2 + g_{m_3} R_1}$$



(b)


$$A_v = -g_{m_1} \left[ r_{o_1} \parallel (R_1 g_{m_3} r_{o_3} + R_1 + r_{o_3}) \right]$$
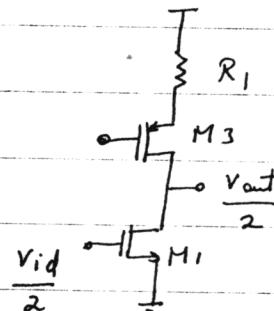
$$\approx -g_{m_1} (r_{o_1} \parallel R_1 g_{m_3} r_{o_3})$$




(c)
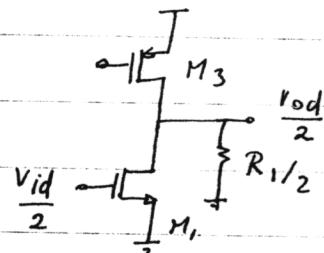
$$A_v = -g_{m_1} (r_{o_1} \parallel r_{o_3} \parallel \frac{R_1}{2})$$





(d)
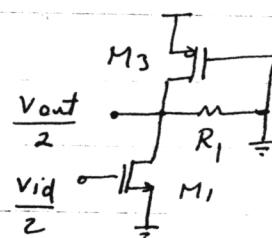
$$A_v = -g_{m_1} (r_{o_1} \parallel r_{o_3} \parallel R_1)$$



(e)

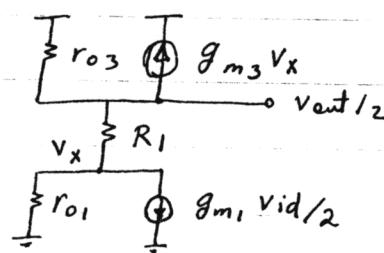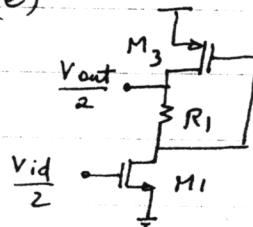

$$KCL: \frac{V_x}{r_{o1}} + \frac{V_x - V_{out/2}}{R_1} + g_{m1} \frac{V_{id}}{2} = 0$$

$$\frac{V_{out/2}}{r_{o3}} + \frac{V_{out/2} - V_x}{R_1} + g_{m3} V_x = 0 \Rightarrow V_x = \frac{(r_{o3} + R_1) V_{out}}{2 r_{o3} (1 - R_1 g_{m3})}$$

$$\left( \frac{R_1 + r_{o1}}{R_1 r_{o1}} \frac{r_{o3} + R_1}{r_{o3} (1 - R_1 g_{m3})} - \frac{1}{R_1} \right) V_{out} + g_{m1} V_{id} = 0$$

$$\frac{(R_1 + r_{o1})(R_1 + r_{o3}) - r_{o1} r_{o3} (1 - R_1 g_{m3})}{R_1 r_{o1} r_{o3} (1 - R_1 g_{m3})} V_{out} + g_{m1} V_{id} = 0$$

$$\frac{R_1 + r_{o1} + r_{o2} + r_{o1} r_{o3} g_{m3}}{r_{o1} r_{o3} (1 - R_1 g_{m3})} V_{out} + g_{m1} V_{id} = 0$$

$$\Rightarrow A_V = \frac{V_{out}}{V_{id}} = - \frac{g_{m1} r_{o1} r_{o3} (1 - R_1 g_{m3})}{R_1 + r_{o1} + r_{o3} + r_{o1} r_{o3} g_{m3}} \approx - \frac{g_{m1}}{g_{m3}} (1 - R_1 g_{m3})$$


$$R_1 g_{m3} < 1$$

Fig. 4.36.

(a)


$$A_V = - g_{m1} \left( \frac{1}{g_{m3}} \parallel r_{o1} \parallel r_{o3} \parallel r_{o5} \right)$$

$$\approx - \frac{g_{m1}}{g_{m3}}$$

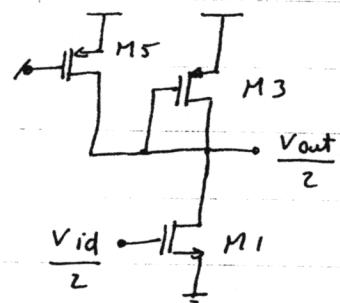


(b)
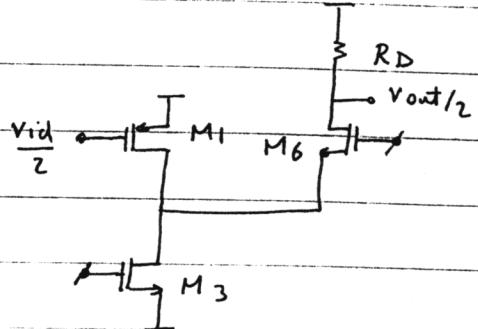
$$A_v = -g_{m_1} \left( R_D \parallel [r_{o6} g_{m_6} (r_{o1} \parallel r_{o3})] \right)$$



(c)

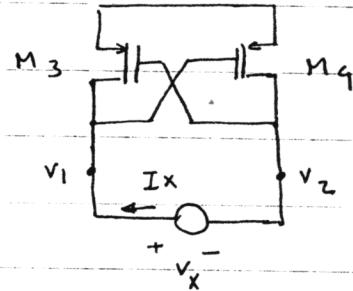if we neglect  $r_{o3}$  &  $r_{o4}$  at the moment,  
we have:




$$I_x = g_{m_3} V_x \quad g_{m_3} = g_{m_4} = g_{m_{3,4}}$$

$$I_x = -g_{m_4} V_1$$

$$2I_x = -g_{m_{3,4}} (V_1 - V_2) = -g_{m_{3,4}} V_x$$
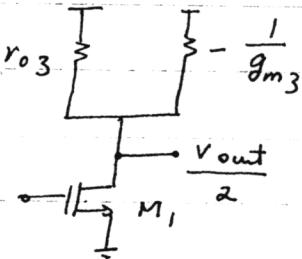
$$\Rightarrow \frac{V_x}{I_x} = -\frac{2}{g_{m_{3,4}}}$$




$$A_v = -g_{m_1} \left( r_{o1} \parallel r_{o3} \parallel \frac{-1}{g_{m_3}} \right)$$

$$A_v = -\frac{g_{m_1}}{\frac{1}{r_{o1}} + \frac{1}{r_{o3}} - g_{m_3}} \quad \left( \frac{1}{r_{o1}} + \frac{1}{r_{o3}} > g_{m_3} \right)$$

if  $g_{m_3} \geq \frac{1}{r_{o1}} + \frac{1}{r_{o3}}$  then the circuit is not stable and small signal model is not valid.

4.6


(a)

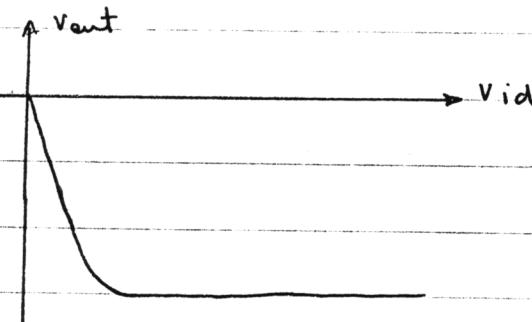

(b)

Similar to what we had in the previous problem (Fig 4.36 (c)),

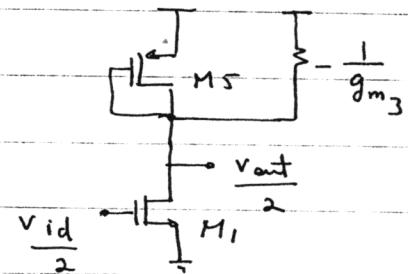$M_3$  gives a negative resistance at the output.



$$A_v = - g_{m1} \left( \frac{1}{g_{m5}} \parallel \frac{-1}{g_{m3}} \right) \quad (\lambda = \infty)$$

$$A_v = - \frac{g_{m1}}{g_{m5} - g_{m3}} \quad (g_{m3} \text{ must be less than } g_{m5})$$



$$g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_T) \quad V_{GS\ 3,4} = V_{GS\ 5,6}$$

$$\Rightarrow \frac{g_{m3,4}}{g_{m5,6}} = \frac{(W/L)_{3,4}}{(W/L)_{5,6}} = 0.8$$

$$\Rightarrow A_v = - \frac{g_{m1}}{g_{m5} - 0.8 g_{m5}} = - \frac{5 g_{m1}}{g_{m5}}$$

4.7

(a)

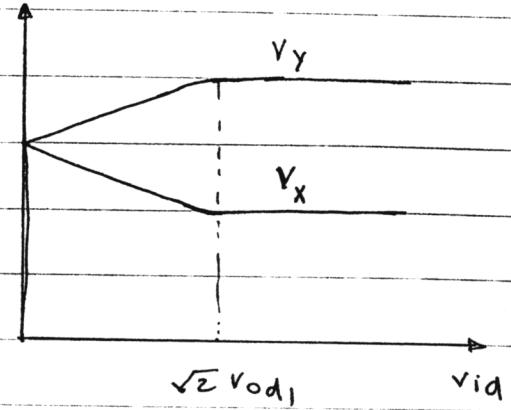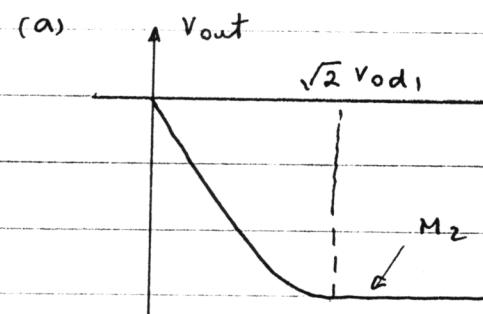


$$V_{od1} = V_{GS1} - V_{TH,n}$$

$$I_D = \frac{I_{SS}}{2}$$

(b)

$$A_v = \frac{V_{out}}{V_{id}} = -g_{m1} \left( \frac{R_1}{2} \parallel \frac{1}{g_{m3}} \right) g_{m3} g_{m5}^{-1}$$
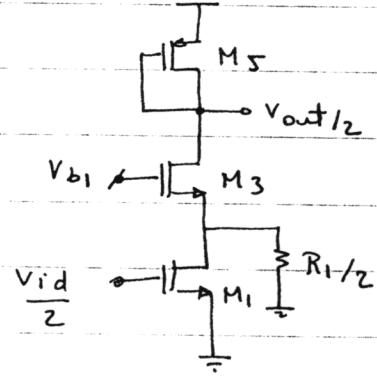
$$= - \frac{g_{m1}}{g_{m5} \left( 1 + \frac{2}{R_1 g_{m3}} \right)}$$




4.8

By using Superposition, we have:


$$G_{m1} = \frac{I_1}{V_{in1}} \quad \left|_{V_{in2}=0} \quad = \quad \frac{g_{m1}}{1 + (g_{m1} + g_{mb1})(R_{S1} + R_{S2} + \frac{1}{g_{m2} + g_{mb2}})} \right.$$

(Transconductance of cs)

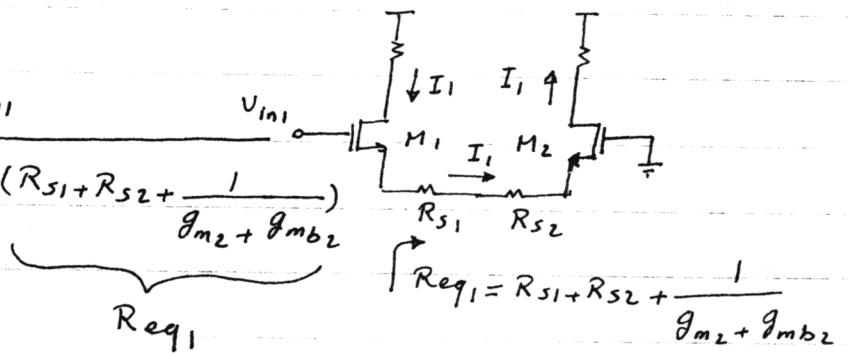


Similarly:

$$G_{m2} = \frac{I_2}{V_{in2}} \Big|_{V_{in1}=0} = \frac{g_{m2}}{1 + (g_{m2} + g_{mb2})(R_{s1} + R_{s2} + \frac{1}{g_{m1} + g_{mb1}})}$$

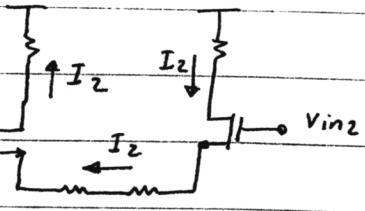

$$I_{out1} = I_1 - I_2$$

$$I_{out2} = I_2 - I_1$$

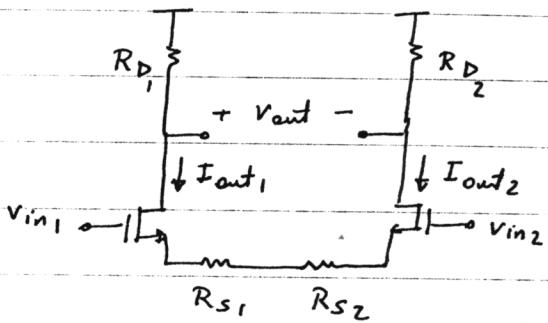

$$V_{out} = V_{out1} - V_{out2} = -R_{D1} I_{out1} + R_{D2} I_{out2}$$

$$V_{out} = -R_{D1}(I_1 - I_2) - R_{D2}(I_1 - I_2)$$


$$V_{out} = -(R_{D1} + R_{D2})(I_1 - I_2)$$

$$V_{out} = -(R_{D1} + R_{D2})(G_{m1}V_{in1} - G_{m2}V_{in2})$$

or equivalently:

$$V_{out} = -(R_{D1} + R_{D2}) \left[ (G_{m1} + G_{m2}) \frac{V_{in1} - V_{in2}}{2} + (G_{m1} - G_{m2}) \frac{V_{in1} + V_{in2}}{2} \right]$$

4.9

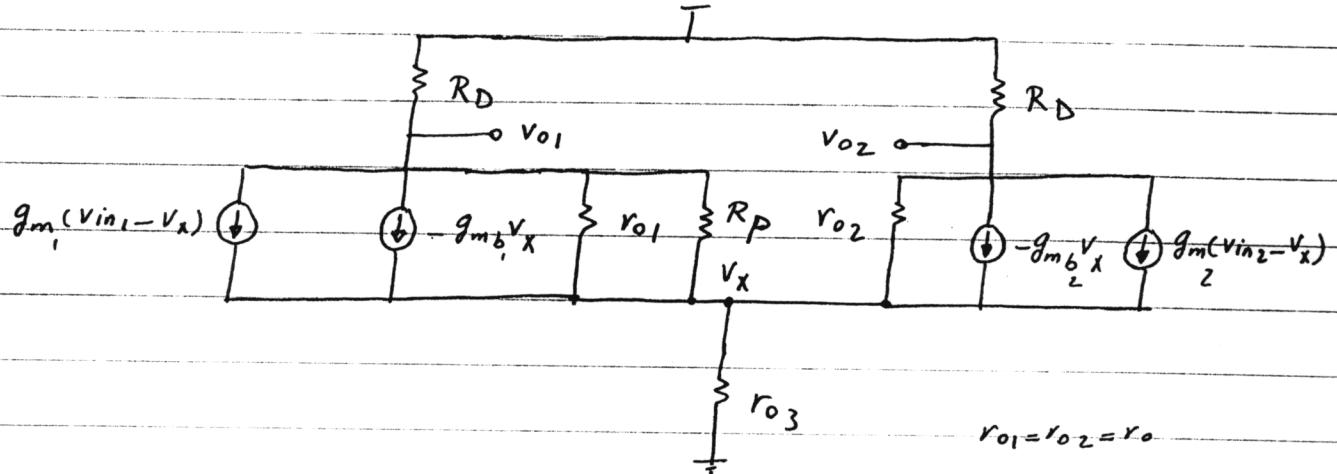

KCL:

$$g_{mb1} = g_{mb2} = g_{mb}$$

$$\left. \begin{array}{l} \textcircled{1} \\ \textcircled{2} \end{array} \right\} \begin{aligned} \frac{V_{o1}}{R_D} + \frac{V_{o1}-V_X}{r_o} + g_m(V_{in1}-V_X) - g_{mb}V_X + \frac{V_{o1}-V_X}{R_P} &= 0 \\ \frac{V_{o2}}{R_D} + \frac{V_{o2}-V_X}{r_o} + g_m(V_{in2}-V_X) - g_{mb}V_X &= 0 \\ \frac{V_{o1}}{R_D} + \frac{V_{o2}}{R_D} + \frac{V_X}{r_{o3}} &= 0 \Rightarrow V_X = -r_{o3} \frac{V_{o1} + V_{o2}}{R_D} \end{aligned}$$

we define :  $\begin{cases} V_{od} = V_{o1} - V_{o2} \\ V_{oc} = \frac{V_{o1} + V_{o2}}{2} \end{cases} \Rightarrow \begin{cases} V_{o1} = V_{oc} + \frac{V_{od}}{2} \\ V_{o2} = V_{oc} - \frac{V_{od}}{2} \end{cases}$

Now by substituting  $V_{o1}$ ,  $V_{o2}$  and  $V_X$  in  $\textcircled{1}$  and  $\textcircled{2}$  we have:

$$\left. \begin{array}{l} (V_{oc} + \frac{V_{od}}{2})(\frac{1}{R_D} + \frac{1}{R_P} + r_o) + g_m V_{in1} - (\frac{1}{R_P} + g_m + g_{mb} + \frac{1}{r_o})(-\frac{2r_{o3}}{R_D} V_{oc}) = 0 \\ (V_{oc} - \frac{V_{od}}{2})(\frac{1}{R_D} + \frac{1}{r_o}) + g_m V_{in2} - (g_m + g_{mb} + \frac{1}{r_o})(-\frac{2r_{o3}}{R_D} V_{oc}) = 0 \end{array} \right\}$$

or:

$$\left[ \frac{1}{R_D} + \frac{1}{R_P} + r_o + (\frac{1}{R_D} + \frac{1}{r_o} + g_m + g_{mb})(\frac{2r_{o3}}{R_D}) \right] V_{oc}$$

$$+ \frac{1}{2} (\frac{1}{R_D} + \frac{1}{R_P} + \frac{1}{r_o}) V_{od} + g_m V_{in1} = 0$$

(3)

$$\left[ \frac{1}{R_D} + \frac{1}{r_o} + (g_m + g_{mb} + \frac{1}{r_o}) \left( \frac{2r_o}{R_D} \right) \right] V_{OC} - \frac{1}{2} \left( \frac{1}{R_D} + \frac{1}{r_o} \right) V_{OD}$$

$$+ g_m V_{IN2} = 0 \quad (4)$$

From equation ③ and ④  $V_{OD}$  and  $V_{OC}$  can be solved in terms of  $V_{IN1}$  and  $V_{IN2}$ .

Now if  $\lambda = \gamma = 0$ , we have:

$$(5) \quad \begin{cases} \frac{V_{O1}}{R_D} + g_m (V_{IN1} - V_x) + \frac{V_{O1} - V_x}{R_P} = 0 \\ \frac{V_{O2}}{R_D} + g_m (V_{IN2} - V_x) = 0 \Rightarrow V_x = V_{IN2} + \frac{V_{O2}}{g_m R_D} \\ V_{O1} + V_{O2} = 0 \quad , \quad V_{out} = V_{O1} - V_{O2} \Rightarrow V_{O1} = \frac{V_{out}}{2} \quad V_{O2} = -\frac{V_{out}}{2} \end{cases}$$

$$\Rightarrow \frac{V_{out}}{2R_D} + g_m V_{IN1} - g_m V_{IN2} + \frac{V_{out}}{2R_D} + \frac{V_{out}}{2R_P} - \frac{V_{IN2}}{R_P} + \frac{V_{out}}{2R_P g_m R_D} = 0$$

$$V_{out} \left( \frac{1}{R_D} + \frac{1}{2R_P} + \frac{1}{2g_m R_P R_D} \right) = -g_m (V_{IN1} - V_{IN2}) + \frac{V_{IN2}}{R_P}$$

$$V_{IN2} = \frac{V_{IN1} + V_{IN2}}{2} - \frac{V_{IN1} - V_{IN2}}{2}$$

$$\Rightarrow V_{out} \left( \frac{1}{R_D} + \frac{1}{2R_P} + \frac{1}{2g_m R_D R_P} \right) = - \left( g_m + \frac{1}{2R_P} \right) (V_{IN1} - V_{IN2}) + \frac{(V_{IN1} + V_{IN2})}{2R_P}$$


$$V_{out} = \left[ - \left( g_m + \frac{1}{2R_P} \right) (V_{IN1} - V_{IN2}) + \frac{V_{IN1} + V_{IN2}}{2R_P} \right] (R_D \parallel 2R_P \parallel 2g_m R_D R_P)$$

$$CMRR = \frac{g_m + \frac{1}{2R_P}}{\frac{1}{R_P}} = \frac{2R_P g_m + 1}{2}$$

$$A_{dm-dm} = - \left( g_m + \frac{1}{2R_P} \right) (R_D \parallel 2R_P \parallel 2g_m R_D R_P) \quad A_{cm-dm} = - \frac{R_D \parallel 2R_P \parallel 2g_m R_D R_P}{R_P}$$

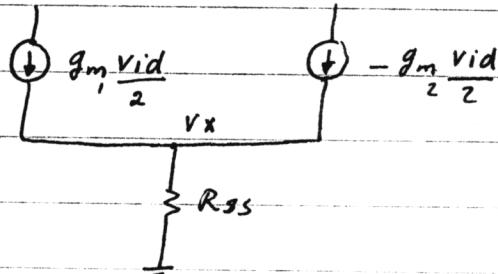4.10


$\lambda = 0$ , so for a differential input, symmetry in the input is enough to force the tail node to be grounded. In other words:



$$g_{m1} \frac{Vid}{2} - g_{m2} \frac{Vid}{2} = R_{ss} V_x$$

$$g_{m1} = g_{m2} \Rightarrow V_x = 0$$
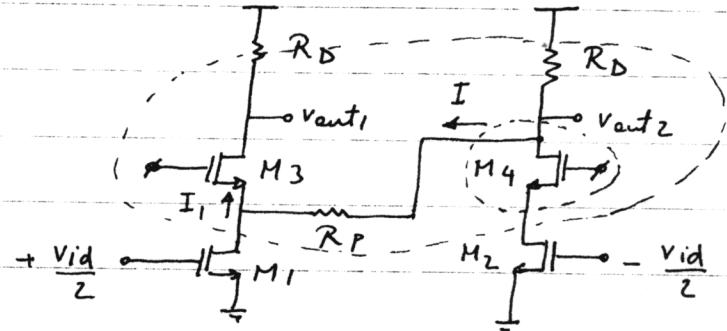
$$(V_{GS1} = V_{GS2} \Rightarrow g_{m1} = g_{m2} \\ \text{but } g_{m3} \neq g_{m4})$$



For the cutsets shown:

$$\frac{V_{out1}}{R_D} + \frac{V_{out2}}{R_D} + \frac{Vid}{2} g_{m1} - \frac{Vid}{2} g_{m2} = 0 \Rightarrow V_{out1} + V_{out2} = 0 \quad (1)$$

$$\text{KCL: } \frac{V_{out2}}{R_D} + I - \frac{Vid}{2} g_{m2} = 0 \quad g_{m1} = g_{m2} \Rightarrow I = \frac{Vid g_{m1}}{2} - \frac{V_{out2}}{R_D} \quad (2)$$

$$\text{KVL: } V_{out2} = IR_P + \frac{I_1}{g_{m3}}, \quad \text{but } I_1 = \frac{V_{out1}}{R_D}$$

$$\Rightarrow V_{out2} = IR_P + \frac{V_{out1}}{R_D g_{m3}} \quad (3)$$

$$(2), (3) \Rightarrow V_{out2} = \left( \frac{Vid g_{m1}}{2} - \frac{V_{out2}}{R_D} \right) R_P + \frac{V_{out1}}{R_D g_{m3}}$$

$$V_{out1} = -V_{out2} \Rightarrow -V_{out1} \left( 1 + \frac{R_P}{R_D} + \frac{1}{R_D g_{m3}} \right) = \frac{g_{m1} R_P}{2} V_{id}$$

$$A_{vd} = \frac{V_{out1} - V_{out2}}{V_{id}} = 2 \frac{V_{out1}}{V_{id}} = - \frac{g_m, R_p}{1 + \frac{R_p}{R_d} + \frac{1}{R_d g_m}} \\ = - \frac{g_m, R_d}{1 + \frac{R_d}{R_p} + \frac{1}{R_p g_m}} = - \frac{g_m, R_d}{1 + \frac{1}{R_p} (R_d + \frac{1}{g_m})}$$

Since  $\lambda = 0 \Rightarrow r_{os} = \infty \Rightarrow A_{cm} = 0 \Rightarrow CMRR = \infty$

4.11

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} [2(v_{GS} - v_{TH,P})v_{DS} - v_{DS}^2] \approx \mu_p C_{ox} \frac{W}{L} (v_{GS} - v_{TH,P})v_{DS}$$

$$R_{on} = \frac{|V_{DS}|}{I_D} = \frac{1}{\mu_p C_{ox} (v_{GS} - v_{TH,P}) \frac{3}{2}}$$

$$\text{if } R_{on} = 2^{k-2} \Rightarrow |V_{GS3} - v_{TH,P}| = \frac{1}{2^k \times 38.3 \times 100} = 0.131^V$$


$$I_{SS} = 20 \mu A \Rightarrow V_{GS1} = v_{TH,N} + \sqrt{\frac{2 I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.7 + \sqrt{\frac{2 \times 10^{-6}}{0.134 \times 100}} = 0.739^V$$

$$V_{DD} = |V_{GS3}| - V_{GS1} + V_{in,cm}$$



$$\Rightarrow V_{in,cm} = 3 - (0.131 + 0.8) + 0.739 = 2.81^V$$

$$|V_{DS3}| = R \frac{I_{SS}}{2} = 2^k \times 10^k = 20^m V \Rightarrow |V_{DS3}| < |V_{GS3} - v_{TH,P}| \Rightarrow M_3 \& M_4 \text{ are in triode}$$
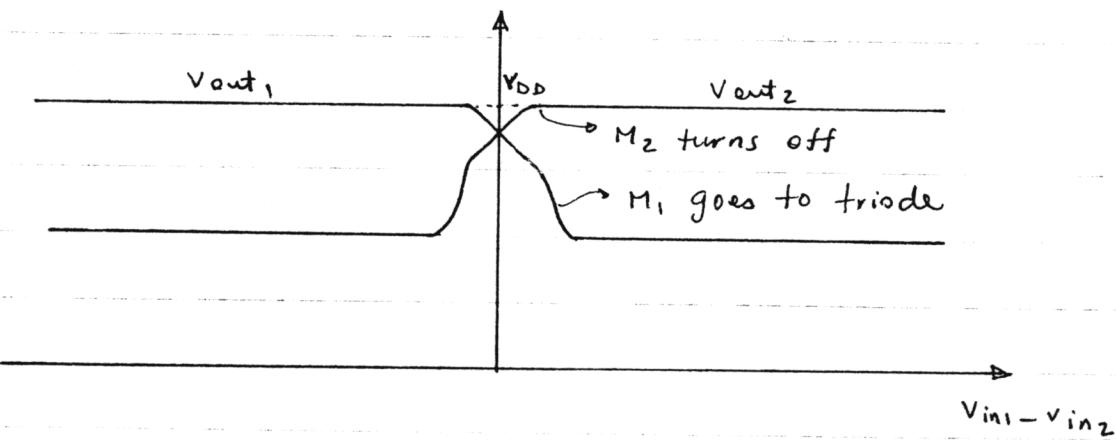
$$V_{D1} - V_{G1} = (3 - 20^m) - 2.81 = 0.17^V > -v_{TH,n} \Rightarrow M_1 \& M_2 \text{ are in Sat.}$$



4.12

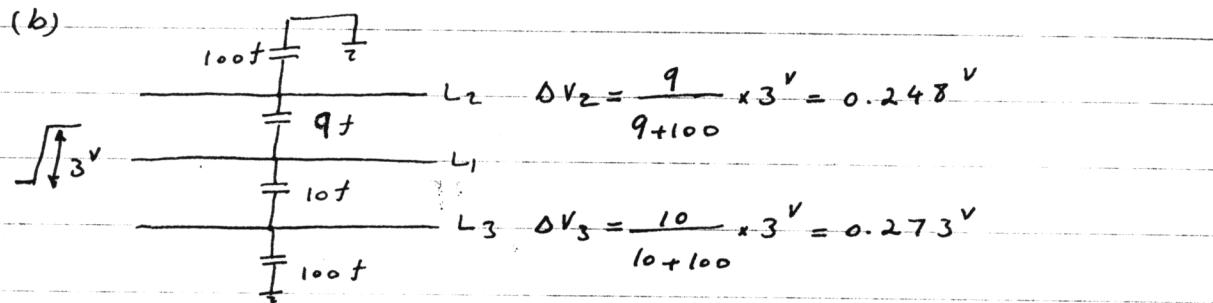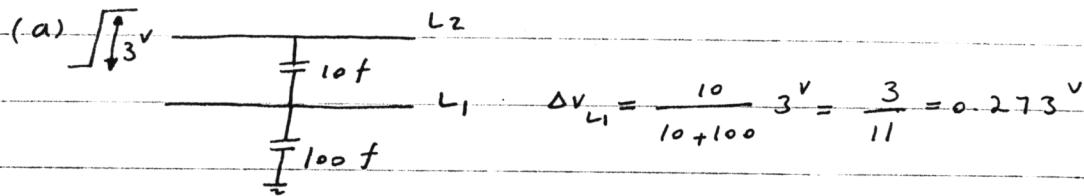


$$\Rightarrow \Delta V_{L_3} - \Delta V_{L_2} = 0.273 - 0.248 = 25^mV$$


4.13

Fig. 4.8 (a)  $I_{SS} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_3 (V_{GS3} - V_{TH,n})^2$
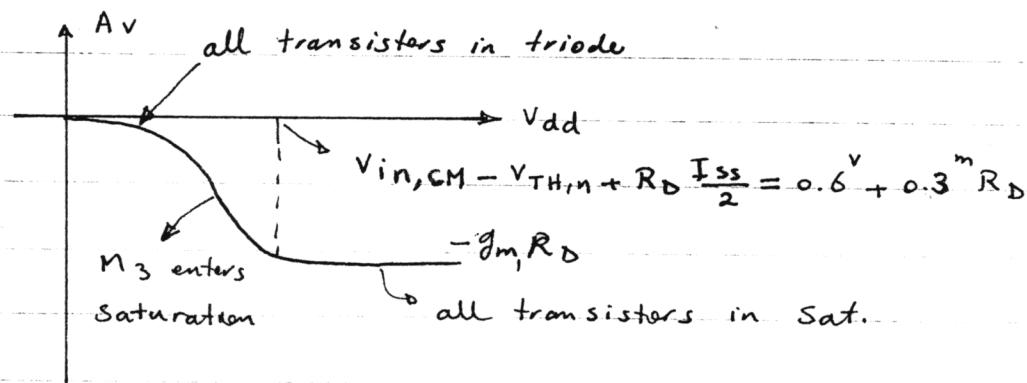
$$V_{GS3} = V_B = 1^V \Rightarrow I_{SS} = 0.5 \times 0.134^m \times 100 (1 - 0.7)^2 = 0.603^mA$$



4.14

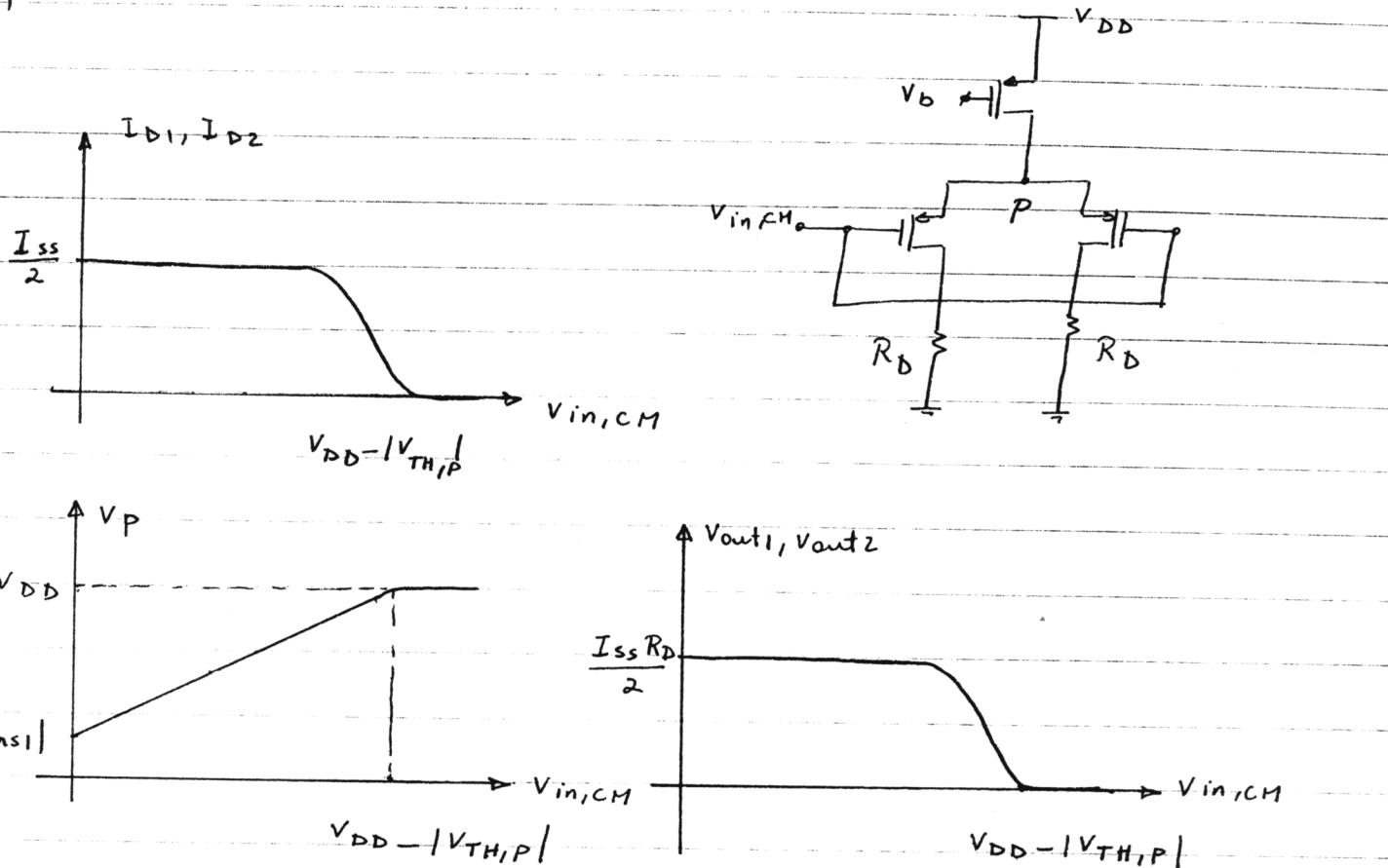

$$I_{D1,2} = \frac{V_{out1,2}}{R_D}$$

$$4.15 \text{ (a)} \quad (V_{out1,2})_{\max} = V_{DD} = 3^V$$

$$(V_{out1,2})_{\min} = V_{in,CM} - V_{TH,N} = 1.2 - 0.7 = 0.5^V$$

$$\text{Max swing of } V_{out} = 2(3 - 0.5) = 5^V$$

$$(b) \quad A_V = -g_m R_D \quad g_m = \sqrt{2 \mu_n C_0 \times \left(\frac{W}{L}\right)_D} = \sqrt{2 \times 0.134^m \times 100 \times \frac{0.5^m}{2}} = 2.59^m$$

$$\text{to get max swing: } R_D \frac{I_{ss}}{2} = \frac{(V_{out1,2})_{\max} - (V_{out1,2})_{\min}}{2} = 1.25$$

$$\Rightarrow R_D = 5^{kR} \quad \Rightarrow \quad A_V = -2.59^m \times 5^k = -13$$

4.16

$$(a) V_{GS} - V_{TH} = \sqrt{\frac{2ID}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2 \times 0.5^m}{0.134^m \times 100}} = 0.273V$$

$$(b) \Delta I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

(4.9)

$$\Delta I_D = \frac{1}{2} \times 0.134^m \times \frac{50}{0.5} \times 50^m \sqrt{\frac{4 \times 1^m}{0.134^m \times \frac{50}{0.5}} - (50^m)^2}$$

$$\Delta I_D = 182 \text{ mA} \Rightarrow \begin{cases} I_{D1} = 0.5^m + \frac{0.182^m}{2} = 0.591^m \\ I_{D2} = 0.5^m - \frac{0.182^m}{2} = 0.409^m \end{cases}$$

(c)

$$G_m = \frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2 \Delta V_{in}}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - \Delta V_{in}^2}} \quad (4.10)$$

$$\Delta V_{in} = 50^mV \Rightarrow G_m = 3.61 \text{ mSR}^{-1}$$

$$(d) \Delta V_{in} = 0 \Rightarrow G_{m_0} = 3.66 \text{ mSR}^{-1}$$

$$G_m = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2 \Delta V_{in}}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - \Delta V_{in}^2}}$$

$$\text{if we define } A = \frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}}, \quad B = \left( \frac{G_m}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right)^2$$

$$\Rightarrow B = \frac{(A - 2 \Delta V_{in})^2}{A - \Delta V_{in}^2} \quad 4 \Delta V_{in}^2 - (4A - B) \Delta V_{in}^2 + A^2 - AB = 0$$

$$\Delta V_{in}^2 = \frac{4A - B \pm \sqrt{(4A - B)^2 - 16(A^2 - AB)}}{8}$$

taking the smaller value:  $\Delta V_{in}^2 = \frac{4A - B - \sqrt{8AB + B^2}}{8}$

So for different value of  $Gm$ , B can be calculated and then  $\Delta V_{in}$  is found.

$$Gm_{10\%} = 0.9 \times 3.66^m = 3.294 \text{ m}\Omega^{-1} \Rightarrow |\Delta V_{in}| = 139 \text{ mV } 10\% \text{ drop}$$

$$Gm_{90\%} = 0.1 \times 3.66^m = 0.366 \text{ m}\Omega^{-1} \Rightarrow |\Delta V_{in}| = 372 \text{ mV } 90\% \text{ drop}$$

4.17

$$(a) V_{od} = V_{GS} - V_{TH} = 0.386 \text{ V}$$

$$(b) \Delta I_D = 0.129 \text{ mA} \Rightarrow I_{D1} = 0.565 \text{ mA}$$

$$I_{D2} = 0.435 \text{ mA}$$

$$(c) Gm = 2.57 \text{ m}\Omega^{-1}$$

$$(d) \Delta V_{in} = 0 \Rightarrow Gm_0 = 2.59 \text{ m}\Omega^{-1}$$

$$Gm_{10\%} = 0.9 \times Gm_0 = 0.9 \times 2.59^m \Rightarrow \Delta V_{in} = 197 \text{ mV}$$

$$Gm_{90\%} = 0.1 \times Gm_0 = 0.1 \times 2.59^m \Rightarrow \Delta V_{in} = 526 \text{ mV}$$

For a given current, by reducing  $\frac{W}{L}$ , overdrive voltage

increases while  $G_m$  decreases. In this case for a fixed  $\Delta V_{in}$ ,  $I_D$  and  $G_m$  change less so the circuit has a wider linear range.

4.18

$$(a) \quad V_{od} = 0.386 \text{ V}$$

$$(b) \quad \Delta I_D = 0.258 \text{ mA} \quad \left\{ \begin{array}{l} I_{D1} = 1.13 \text{ mA} \\ I_{D2} = 0.87 \text{ mA} \end{array} \right.$$

$$(c) \quad G_m = 5.14 \text{ mS}^{-1}$$

$$(d) \quad \Delta V_{in} = 0 \Rightarrow G_{m0} = 5.18 \text{ mS}^{-1}$$

$$G_{m10\%} = 0.9 \times 5.18 \text{ m} \Rightarrow \Delta V_{in} = 197 \text{ mV}$$

$$G_{m90\%} = 0.1 \times 5.18 \text{ m} \Rightarrow \Delta V_{in} = 526 \text{ mV}$$

In this case  $V_{od}$  and  $G_m$  have increased but

the linearity range of  $G_m$  is same as (p. 4.17)

$$4.19 \quad I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{TH,n})^2$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{2W}{L} (V_{in2} - V_{TH,n})^2$$


$$I_{D1} + I_{D2} = I_{SS}$$

if  $I_{D1} = I_{D2}$  then:

$$I_{D1} = \frac{I_{SS}}{2} \Rightarrow V_{in1} = V_{TH,n} + \sqrt{\frac{I_{SS}}{2\mu_n C_{ox} \frac{W}{L}}}$$

$$I_{D2} = \frac{I_{SS}}{2} \Rightarrow V_{in2} = V_{TH,n} + \sqrt{\frac{I_{SS}}{2\mu_n C_{ox} \frac{W}{L}}}$$
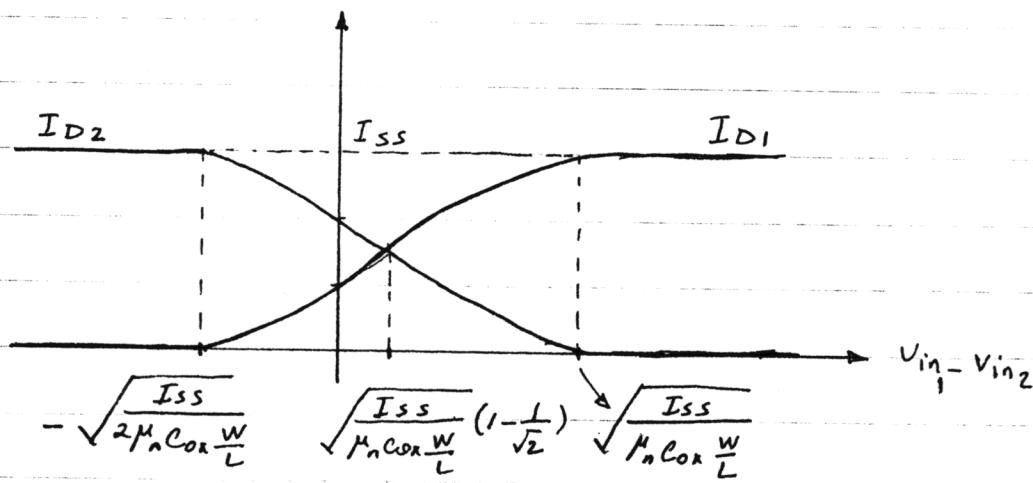
$$V_{in1} - V_{in2} = \sqrt{\frac{I_{SS}}{2\mu_n C_{ox} \frac{W}{L}}} \left(1 - \frac{1}{\sqrt{2}}\right)$$



$$\text{if } V_{in1} = V_{in2} \Rightarrow I_{D1} = \frac{I_{SS}}{3}, \quad I_{D2} = \frac{2I_{SS}}{3}$$

4.20

$$A_{dm-dm} = -g_m R_D$$

$$A_{cm-dm} = \frac{g_m}{1 + 2g_m R_{SS}} R_D - \frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$

$$A_{cm-dm} = - \frac{g_m}{1 + 2g_m R_{ss}} \Delta R_D$$

$$SNR = \frac{(A_{dm-dm} \cdot V_{in,dm})^2}{(A_{cm-dm} \cdot V_{in,cm})^2} = \left( \frac{g_m R_D \times 10^m}{\frac{g_m}{1 + 2g_m R_{ss}} \Delta R_D \times 100^m} \right)^2$$

$$SNR = \frac{(1 + 2g_m R_{ss})^2}{(\frac{\Delta R}{R})^2} \cdot \left( \frac{1}{10} \right)^2$$

$$g_m = \sqrt{2 \mu_n C_o \times \frac{W}{L} I_D} = 3.66 \text{ m.s}^{-1} \quad (I_D = 0.5 \text{ mA})$$

$$L_{ss} = 0.5 \mu m \Rightarrow \lambda = 0.1 \text{ m}^{-1} \Rightarrow R_{ss} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 1 \text{ mA}} = 10 \text{ k}\Omega$$

$$\Rightarrow SNR = \left( \frac{1 + 2 \times 3.66^m \times 10^k}{0.05} \right)^2 \left( \frac{1}{10} \right)^2 = 22000$$

$$\text{or } SNR = 10 \log 22000 = 43.4 \text{ dB}$$

$$CMRR = \left| \frac{A_{dm-dm}}{A_{cm-dm}} \right| = \frac{\frac{g_m R_D}{g_m \Delta R_D}}{\frac{1 + 2g_m R_{ss}}{1 + 2g_m R_{ss}}} = \frac{1 + 2g_m R_{ss}}{\Delta R_D / R_D}$$

$$CMRR = 1484 \quad \text{or} \quad CMRR = 20 \log 1484 = 63.4 \text{ dB}$$

4.21  $A_{cm-dm} = - \frac{\Delta g_m R_D}{(g_{m1} + g_{m2}) R_{ss} + 1} \quad g_{m1} + g_{m2} = 2g_m$

$$SNR = \left( \frac{A_{dm-dm} \cdot V_{in-dm}}{A_{cm-dm} \cdot V_{in-cm}} \right)^2 = \left( \frac{\frac{g_m R_D}{(g_{m1} + g_{m2}) R_{ss} + 1}}{\frac{\Delta g_m R_D}{(g_{m1} + g_{m2}) R_{ss} + 1}} \right)^2 \left( \frac{10^m}{100^m} \right)^2$$

$$SNR = \left( \frac{2g_m R_{SS} + 1}{\frac{\Delta g_m}{g_m}} \right)^2 \times \left( \frac{1}{I_0} \right)^2$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \Rightarrow \Delta g_m = -\mu_n C_{ox} \frac{W}{L} \Delta V_{TH}$$

$$|\Delta g_m| = 0.134^m \times 100 \times 1^{mv} = 13.4 \text{ } \mu\text{A}^{-1}$$

$$\Rightarrow SNR = \frac{(2 \times 3.66^m \times 10^6 + 1)^2}{\left(\frac{13.4 \mu}{3.66^m}\right)^2} \times \left(\frac{1}{I_0}\right)^2 = 4.1 \times 10^6$$

$$\text{or } SNR = 10 \log 4.1 \times 10^6 = 66.1 \text{ dB}$$

$$CMRR = \left| \frac{A_{dm-dm}}{A_{cm-dm}} \right| = \frac{1 + 2g_m R_{SS}}{\Delta g_m / g_m} = 20300$$

$$\text{or } CMRR = 20 \log 20300 = 86.1 \text{ dB}$$

4.22 (a)

$$\left(\frac{W}{L}\right)_{SS} = \frac{50}{0.5}, I_{SS} = 0.5 \text{ mA}$$

$$V_{od_{SS}} = V_{GS3} - V_{TH} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{SS}}} = 0.273 \text{ V}$$

$$I_{D1} = \frac{I_{SS}}{2} = 0.25 \text{ mA} \Rightarrow V_{od_1} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = 0.193 \text{ V}$$

$$(V_{in,cm})_{min} = V_{GS1} + V_{od_{SS}} = 0.7 + 0.193 + 0.273 = 1.17 \text{ V}$$


$$(V_{in,cm})_{max} = V_{DD} - |V_{GS3}| + V_{TH,N}$$

4.25

$$|V_{GS3}| = |V_{TH,P}| + \sqrt{\frac{2ID_3}{\mu_p C_{ox}(\frac{W}{L})_3}} = 1.61 V$$

$$(V_{in,cm})_{max} = 3 - 1.61 + 0.7 = 2.09 V$$

$$(b) V_{in,cm} = 1.2 V$$

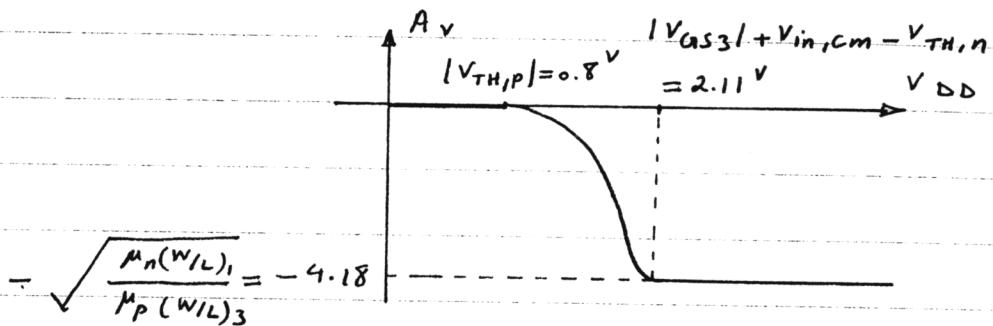

4.23

This mismatch in  $V_{TH}$  of  $M_1$  and  $M_2$  makes  $I_{D1}$  and  $I_{D2}$  unequal. Therefore  $g_{m1} \neq g_{m2}$ ,  $g_{m3} \neq g_{m4}$ . Using the equivalent circuit below to calculate  $A_{cm-dm}$ , we have:


$$i_{D1} = g_{m1} (V_{in,cm} - v_p)$$

$$i_{D2} = g_{m2} (V_{in,cm} - v_p)$$

$$V_{out1} = - \frac{i_{D1}}{g_{m3}} = - \frac{g_{m1}}{g_{m3}} (V_{in,cm} - v_p)$$

$$V_{out2} = - \frac{i_{D2}}{g_{m4}} = - \frac{g_{m2}}{g_{m4}} (V_{in,cm} - v_p)$$
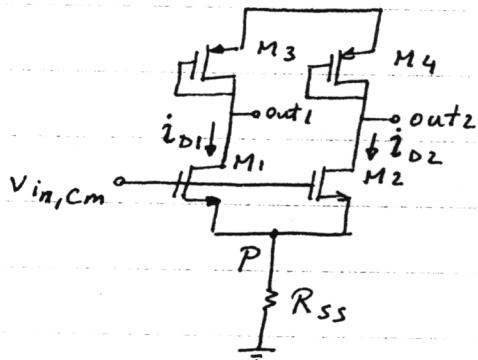
$$\frac{g_{m1}}{g_{m3}} = \frac{\sqrt{2ID_1\mu_nC_{ox}(\frac{W}{L})_{1,2}}}{\sqrt{2ID_3\mu_pC_{ox}(\frac{W}{L})_{3,4}}} = \sqrt{\frac{\mu_n(\frac{W}{L})_{1,2}}{\mu_p(\frac{W}{L})_{3,4}}}, \text{ Similarly } \frac{g_{m2}}{g_{m4}} = \sqrt{\frac{\mu_n(\frac{W}{L})_{1,2}}{\mu_p(\frac{W}{L})_{3,4}}}$$



$$\Rightarrow V_{out1} = V_{out2} \Rightarrow A_{cm-dm} = 0, CMRR = \infty$$

4.26

4.24

$$P \quad 4.20 \quad CMRR = \frac{1 + 2g_m R_{SS}}{\Delta R_D / R_D}$$

$$R_{D1} = \frac{1}{g_{m3}}, \quad R_{D2} = \frac{1}{g_{m4}}$$

$$\frac{\Delta R_D}{R_D} = \frac{R_{D1} - R_{D2}}{R_{D1}} = 1 - \frac{R_{D2}}{R_{D1}} = 1 - \frac{g_{m3}}{g_{m4}} = 1 - \frac{\sqrt{2\mu_p C_{ox}(\frac{W}{L})_3} I_D}{\sqrt{2\mu_p C_{ox}(\frac{W}{L})_4} I_D}$$

$$\frac{\Delta R_D}{R_D} = 1 - \sqrt{\frac{10}{11}} = 0.0465$$

$$\Rightarrow CMRR = 2248 \quad \text{or} \quad CMRR = 20 \log 2248 = 67 \text{ dB}$$

4.25

$$(a) \quad A_v = -g_{m1} (r_{o1} \parallel r_{o3})$$

$$g_{m1} = 3.66 \text{ } \frac{mV}{A} \quad r_{o1} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 0.5 \text{ } m} = 20 \text{ } k\Omega$$

$$r_{o3} = \frac{1}{\lambda I_D} = \frac{1}{0.2 \times 0.5 \text{ } m} = 10 \text{ } k\Omega \quad \Rightarrow \quad A_v = -3.66^m (10^k \parallel 20^k) = -24.4$$

$$(b) \quad (V_{out1,2})_{min} = 1.5 - V_{TH,n} = 1.5 - 0.7 = 0.8^V$$

$$(V_{out1,2})_{max} = V_{DD} - (|V_{OSS3}| - |V_{TH,P}|)$$

$$= V_{DD} - \sqrt{\frac{2 I_D}{\mu_p C_{ox}(\frac{W}{L})_3}} = 3 - \sqrt{\frac{2 \times 0.5 \text{ } m}{38.3 \text{ } \mu, 100}} = 2.49^V$$

$$\text{Max swing of } V_{out} = 2(2.49 - 0.8) = 3.38^V$$

4.26

$$P \quad 4.20 : \quad CMRR = \frac{1 + 2g_m R_{SS}}{\Delta R_D / R_D}$$

$$R_D = \frac{1}{g_m} || r_{o1} || r_{o3} || r_{o5} \approx \frac{1}{g_m}$$

$$I_{D3} + I_{D5} = I_{D4} + I_{D6} = \frac{I_{SS}}{2} \rightarrow \Delta I_{D3} = -\Delta I_{D5} \quad (1)$$

$$I_{D5} = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_5 (V_{GS5} - V_{TH,P})^2 \Rightarrow \frac{\partial I_{D5}}{\partial V} = -\mu_p C_{ox} \left( \frac{W}{L} \right)_5 (V_{GS5} - V_{TH,P})$$

$$\Delta I_{D5} \approx \mu_p C_{ox} \left( \frac{W}{L} \right)_5 (V_{DD} - V_b - |V_{TH,P}|) \Delta V_{TH,P} \quad (2)$$

$$g_m = \sqrt{2 \mu_p C_{ox} \left( \frac{W}{L} \right)_3 I_{D3}} \quad \frac{\partial g_m}{\partial I_{D3}} = \sqrt{\frac{\mu_p C_{ox} \left( \frac{W}{L} \right)_3}{2 I_{D3}}}$$

$$\Rightarrow \Delta g_m \approx \sqrt{\frac{\mu_p C_{ox} \left( \frac{W}{L} \right)_3}{2 I_{D3}}} \Delta I_{D3} \quad (3)$$

$$R_D = \frac{1}{g_m} \quad \frac{\partial R_D}{\partial g_m} = -\frac{1}{g_m^2} \Rightarrow \frac{\Delta R_D}{R_D} \approx -\frac{\Delta g_m}{g_m}$$


$$(1), (2), (3) \Rightarrow \frac{\Delta R_D}{R_D} = -\frac{\Delta g_m}{g_m} = -\sqrt{\frac{\mu_p C_{ox} \left( \frac{W}{L} \right)_3}{2 I_{D3}}} \cdot \frac{\Delta I_{D3}}{\sqrt{2 \mu_p C_{ox} \left( \frac{W}{L} \right)_3 I_{D3}}} = -\frac{\Delta I_{D3}}{2 I_{D3}}$$

$$= \frac{\Delta I_{D5}}{2 I_{D3}} = \frac{\mu_p C_{ox} \left( \frac{W}{L} \right)_5 (V_{DD} - V_b - |V_{TH,P}|) \Delta V_{TH,P}}{2 I_{D3}} = \frac{I_{D5}}{I_{D3}} \cdot \frac{\Delta V_{TH,P}}{V_{DD} - V_b - |V_{TH,P}|}$$

$$\text{or } \frac{\Delta R}{R_D} = \frac{I_{D5}}{I_{D3}} \cdot \frac{V_{TH,P}}{V_{DD} - V_b - |V_{TH,P}|} \cdot \frac{\Delta V_{TH,P}}{V_{TH,P}}$$

$$\text{but } \frac{I_{D5}}{I_{D3}} = 4$$

$$\Rightarrow \frac{\Delta R_D}{R_D} = 4 \cdot \frac{V_{TH,P}}{V_{DD} - V_b - |V_{TH,P}|} \cdot \frac{\Delta V_{TH,P}}{V_{TH,P}}$$

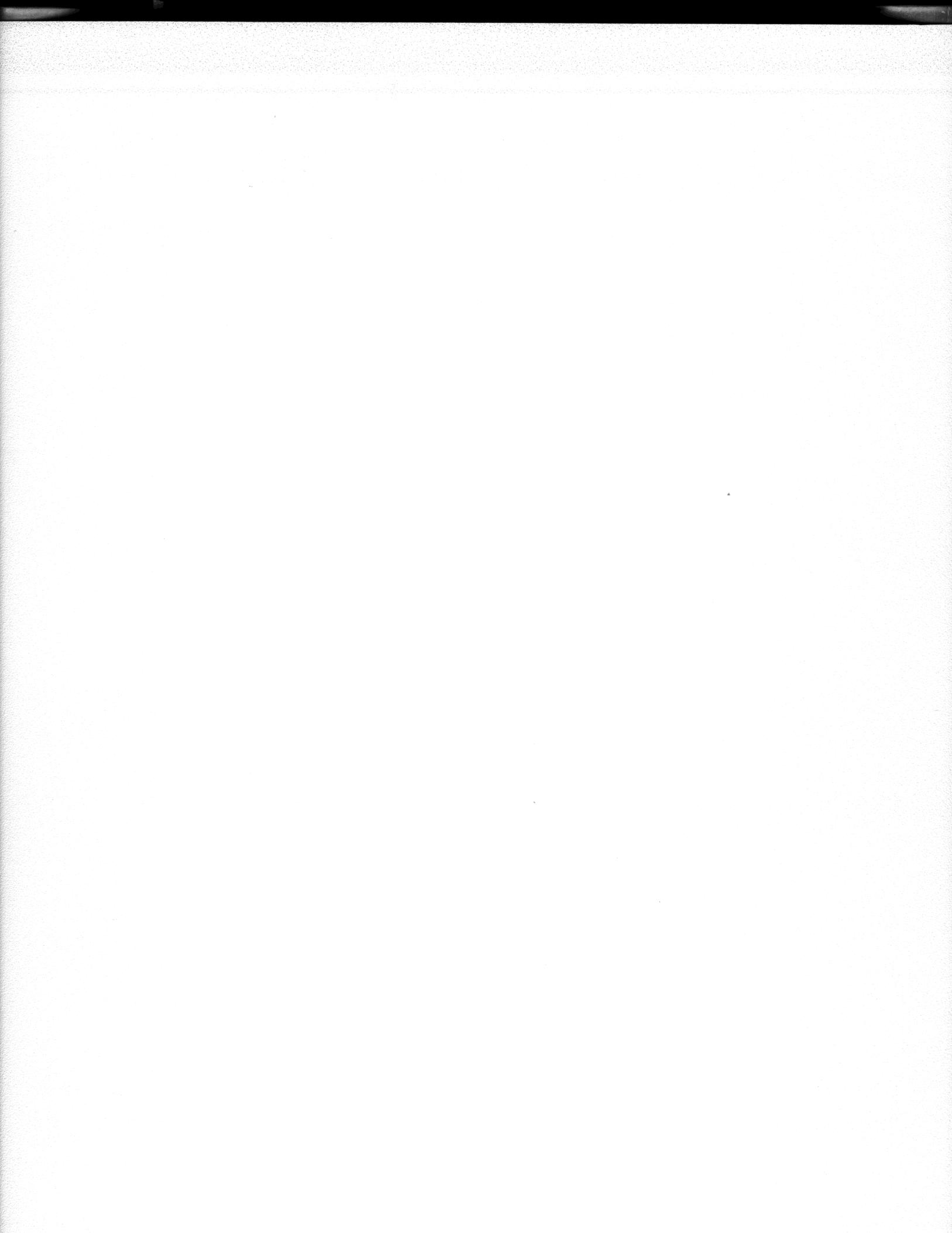

# Chapter 5.

5.1

S.1 (a) M<sub>1</sub> and M<sub>2</sub> are off when  $V_{DD} < V_{TH1,2}$ .

At this time,  $V_{x,y} = V_{DD}$  because  $I_{1,2} = 0$ .


Once  $V_{DD} \geq V_{TH1,2}$ , M<sub>1</sub> and M<sub>2</sub> turn on.

Since M<sub>1</sub> and M<sub>2</sub> are symmetric and the

$V_{GS}$  for both are the same  $I_1 = I_2$  and

$V_x = V_y = V_{GS2,1}$ .  $V_{GS}$  is a quadratic solution as a function off  $V_{DD}$  and follows the below relationship.
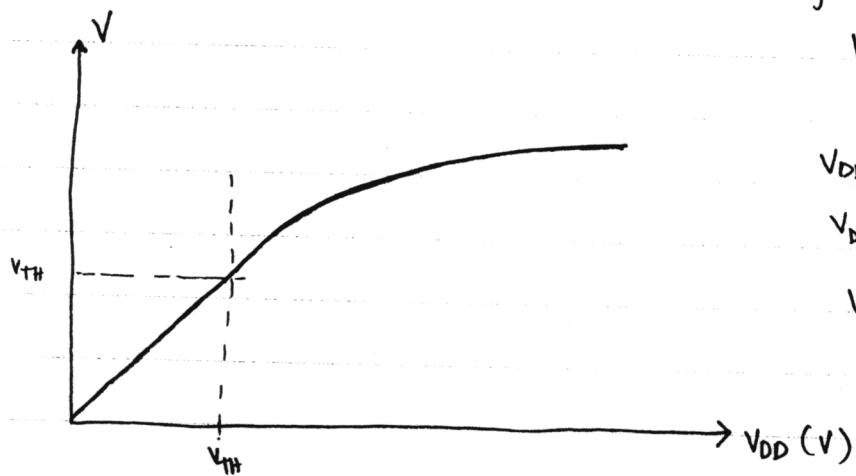
$$\begin{aligned} V_{GS2} &= V_{DD} - I_2 R \\ &= V_{DD} - \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS2} - V_{th})^2 \cdot R \\ K &= \frac{1}{2} \mu C_{ox} \frac{W}{L} \end{aligned}$$




$V_{DD} < V_{TH}$ :  $V_x = V_y = V_{DD}$ .

$V_{DD} \geq V_{TH}$ :

$$V_{GS} = \frac{2V_{th} - \frac{1}{KR} + \sqrt{(2V_{th} - \frac{1}{KR})^2 - 4(V_{th}^2 - \frac{V_{DD}}{KR})}}{2}$$

(b) We have the same solution as S.1(a) because if M<sub>1</sub>, M<sub>2</sub> are symmetric and  $V_{GS1} = V_{GS2}$  then  $V_x = V_y$  and  $I_1 = I_2$ . In this case, no current ever flows through  $R_2$ .

5.1 (c)

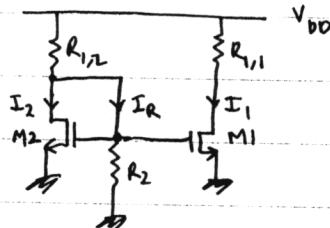


When  $V_{DD} < V_{th1,2}$  no current flows through

M1 and M2. the only current that flows is

$I_R$  through  $R_{1,2}$  and  $R_2$ .  $V_x$  is set by the
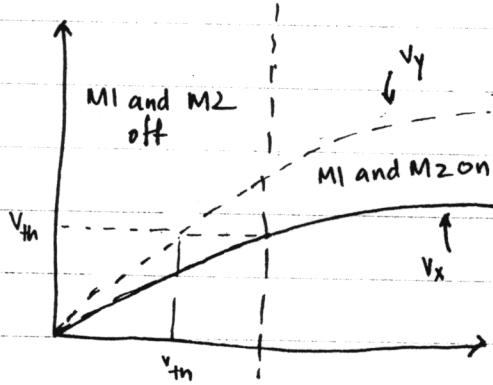
$$V_x = V_{DD} \cdot \frac{R_2}{R_{1,2} + R_2} \quad \text{and} \quad V_y = V_{DD}$$



M1 and M2 turn on only when  $V_x \geq V_{th1,2}$ . Once


M1 and M2 are on,  $I_1$  and  $I_2$  are equal because they have the same  $V_{gs}$ . But  $V_y > V_x$  because

the current through  $R_{1,2}$  consist of  $I_2$  plus  $I_R$  which is greater than the current through  $R_{1,1}$ .

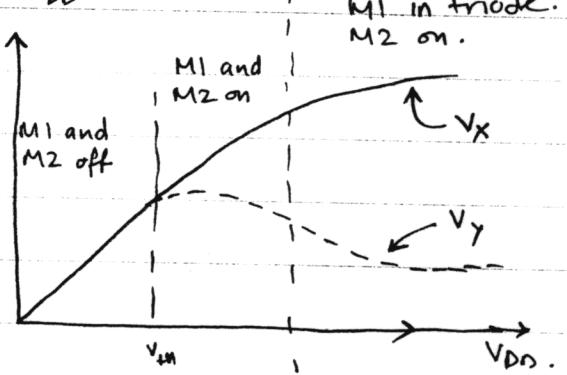(d) When  $V_{DD} < V_{th1,2}$ ,  $I_1 = I_2 = 0$  and  $V_x = V_y = V_{DD}$

Once  $V_{DD} \geq V_{th1,2}$ , M1 and M2 turn on.

the  $R_2$  at the source of M2 causes  $V_{gs2} < V_{gs1}$ . Thus  $I_2 < I_1$  and  $V_x > V_y$ . At some point,  $V_{gs1}$  becomes so large that M1 goes into triode as seen in the graph.




(e) Here when  $V_{DD} > V_{th1,2}$ ,  $V_{gs2} > V_{gs1}$

and  $I_1 < I_2$ . Thus  $V_x < V_y$ ,

but because M2 is diode connected,

M2 never goes into triode.

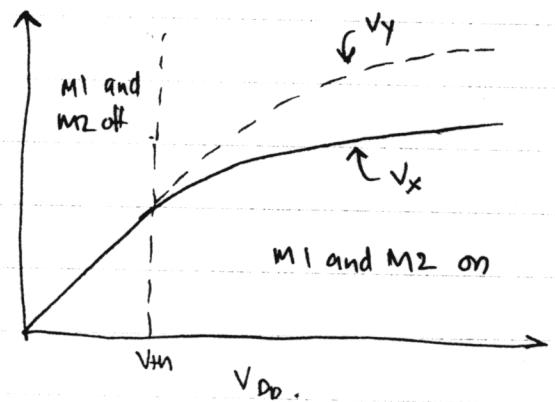

5.2 (a) When  $V_{DD} < V_{th1,2}$ , all transistors are off.  $V_X = V_{DD}$  and  $V_Y$  is floating between GND and  $V_{DD}$  since it is isolated from either node.

Once  $V_{DD} = V_{th1,2}$

all transistors turn on



and the voltages at

nodes are as follows:  $V_X = V_{DD} = V_{th2}$

and  $V_Y = V_{DD} - V_{th3} \approx \emptyset$  if we

assume  $V_{th2} = V_{th3}$ . M1 and M4

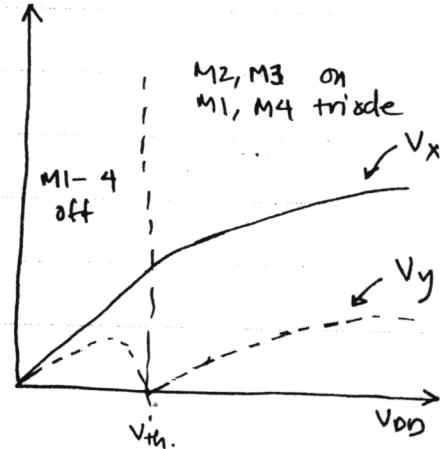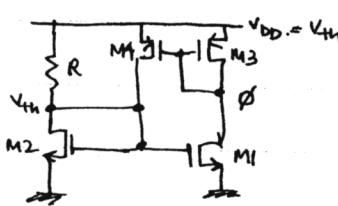are in triode and stay in triode always as  $V_{DD} > V_{th2}$ .




As  $V_{DD} > V_{th2}$ ,  $V_X = V_{gs2}$  and  $V_Y = V_{DD} - V_{gs3} \approx V_{DD} - V_{gs2}$   
 $V_X > V_Y$ .

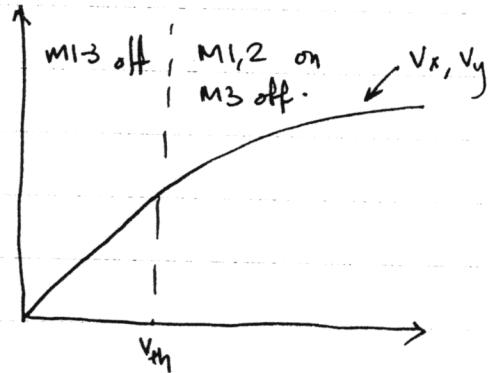
(b) when  $V_{DD} < V_{th1,2}$   $I_1, I_2 = \emptyset$  and  $V_X = V_Y = V_{DD}$

when  $V_{DD} \geq V_{th1,2}$   $I_1 = I_2$  because  $V_{gs1} = V_{gs2}$  and therefore

$V_X = V_Y$ . Since  $V_X \approx V_Y$ ,  $V_{gs3} = 0$  and M3 is always off.



5.3 (a)

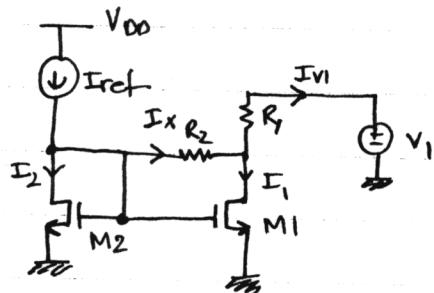

for  $V_i: 0 \leq V_i \leq V_{DD}$  M1 and M2

are always on:  $I_1 = I_2$

$V_y$  and  $V_x$  are related as a function of  $R_1, R_2$  and  $V_i$ .

$$(1) 2I_1 = I_{ref} - I_{V1} = I_{ref} - \frac{V_y - V_i}{R_1}$$


$$(2) I_1 = \frac{V_x - V_y}{R_2} - \frac{V_y - V_i}{R_1}$$

Solving these 2 equations for  $V_y$ , we get


$$V_y = \frac{R_2 V_i + 2R_2 V_x - I_{ref}}{R_1 + R_2}$$

as  $V_i$  increase,  $I_{1,2}$  increase and therefore  $V_x$  and  $V_y$  increase.

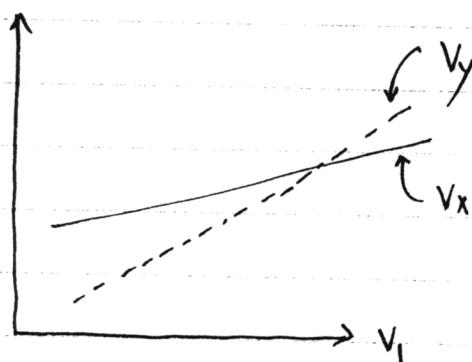The slope of  $V_y$  is greater because it is a linear combination of  $V_x + V_i$ , but  $V_y$  starts off less than  $V_x$  because of the constant subtraction of  $I_{ref}/(R_1+R_2)$ .




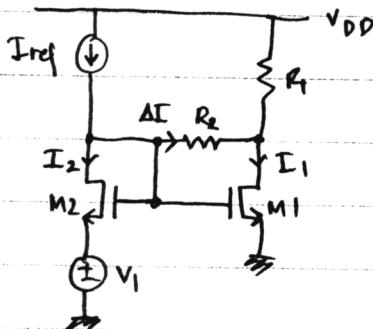
5.3 (b) When  $V_1 = 0$ ,  $I_1 = I_2 \approx I_{ref}$  and  $V_x \approx V_y$ ,  $\Delta I = 0$



As  $V_1$  increases,  $I_2$  gradually decreases and part of  $I_{ref}$  flows through  $R_2$ .  $V_x$  increases and  $V_y = V_x - R_2 \Delta I$ , decreases.

Finally when  $V_1$  is large enough such that  $M_2$  turns off

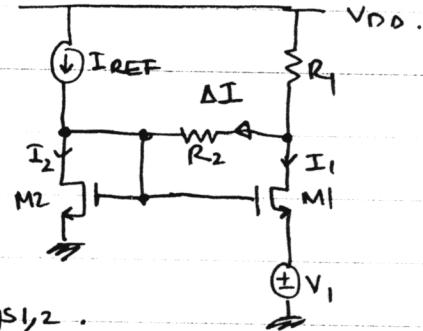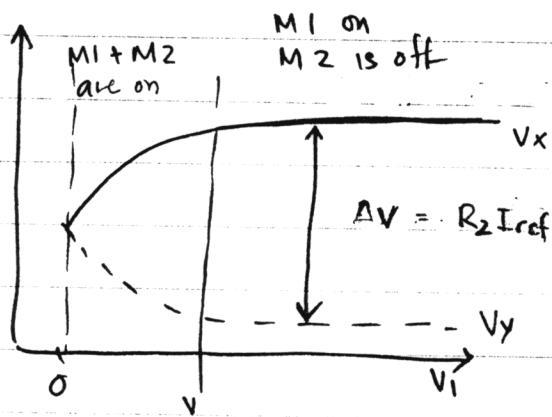$V_y = V_x - R_2 I_{ref}$  and both  $V_x$  and  $V_y$  are set at a constant voltage




(c) When  $V_1 = 0$ ,  $I_1 = I_2$ ,  $V_x \approx V_y$ . there maybe small variations if  $V_{DD} - R_1 I_1 \neq V_{gs1,2}$ .

as  $V_1$  increases,  $I_1$  decreases and the extra current flows through  $M_2$ .  $I_2$  increases.

$$V_y = V_x + \Delta I R_2$$

Once  $V_1$  gets large enough,  $M_1$  shuts off.

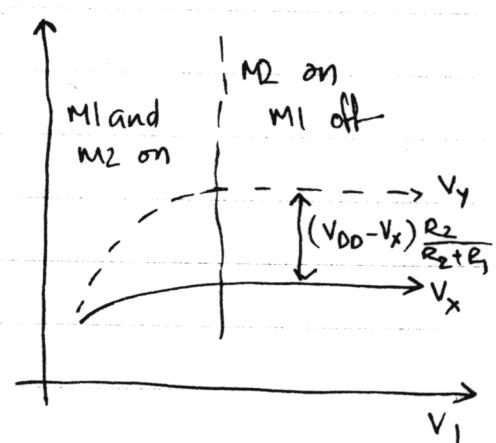
$$V_y = \frac{(V_{DD} - V_x) R_2}{R_1 + R_2} + V_x$$



S.4 (a)  $V_x$  is constant until  $V_i$  gets high enough that  $V_y - V_x$  is greater than  $V_{th3}$ .

Initially M1 is in triode with  $V_y = V_i \frac{1}{1+gm_1 R_2}$  until M1 is in saturation.

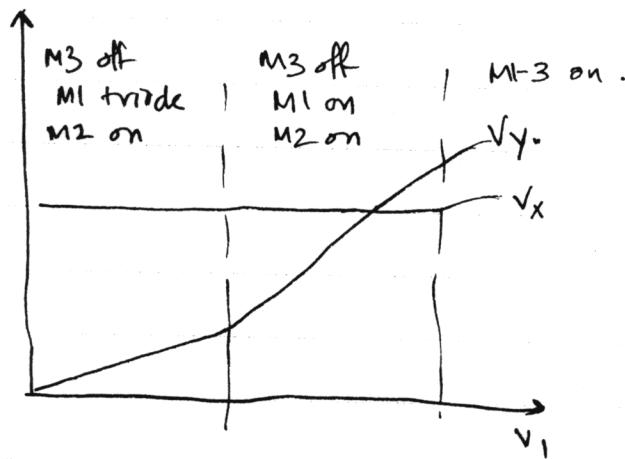When M1 in sat.,  $V_y = V_i - I_{REF} R_1$




(b). When  $V_i = 0$ , M1 and M2 are off and M3 is on, but in a flipped position, Source and drain switch as show below.


$$V_y = V_{DD} \text{ and } V_x = V_i + V_{DS3} \text{ where } V_{DS3} = I_{REF}/gm_3$$

As  $V_i$  increase,  $V_x$  increases in the same amount until  $V_x = V_{th1,2}$ .

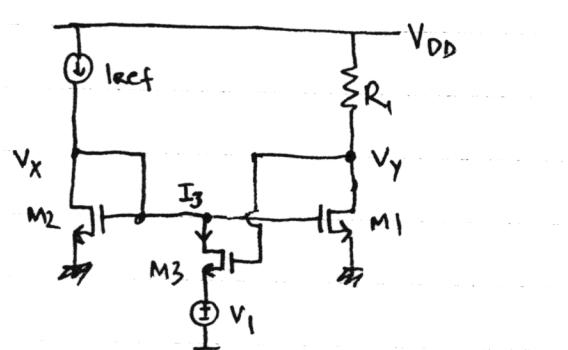
Now that M1 and M2 turn on,  $V_y$  drops down due to  $I_1 R_1$  until M3 turns off. Once M3 is off,  $V_x = V_{GS1,2}$  and  $V_y = V_{DD} - R_1 I_{REF}$ .



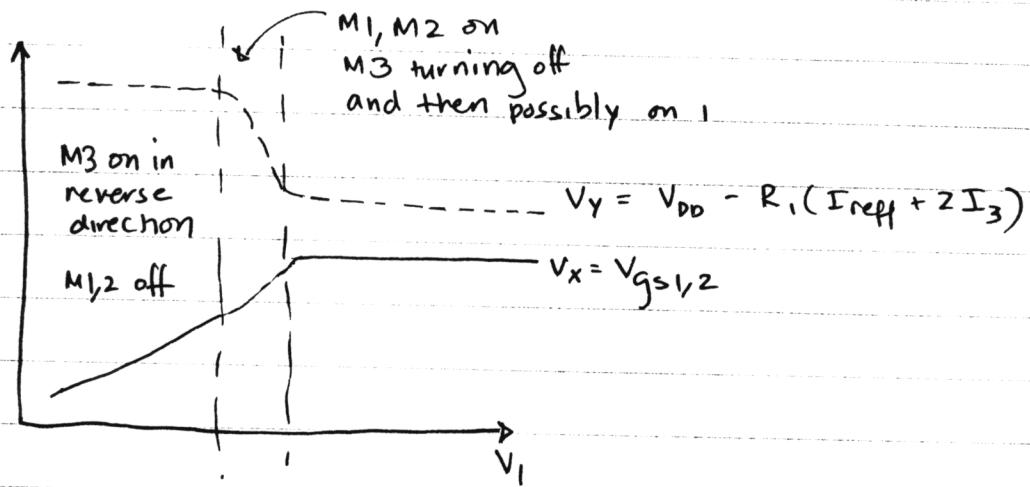If at this point,  $V_{th3} < V_y - V_x$ , M3 will turn on to increase the current through M2 and hence M1 so  $V_y = V_{DD} - R_1(I_{REF} + 2I_3)$



5.5

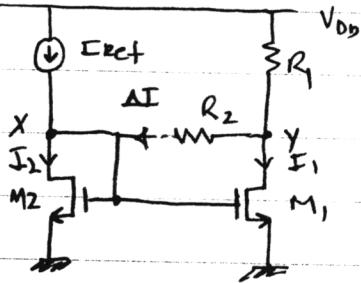

When  $I_{ref} = 0$ , current  $I_1$  and  $I_2$  are supplied by  $V_{DD}$  through  $R_1$


The initial points can be solved with

$$I_{1,2} = \frac{1}{2} MCox \frac{W}{L} (V_{gs1,2} - V_{th})^2 \quad (1)$$

$$V_{gs2,1} = V_{DD} - (2R_1 + R_2) I_{1,2} \quad (2)$$

where  $V_x = V_{gs2,1}$

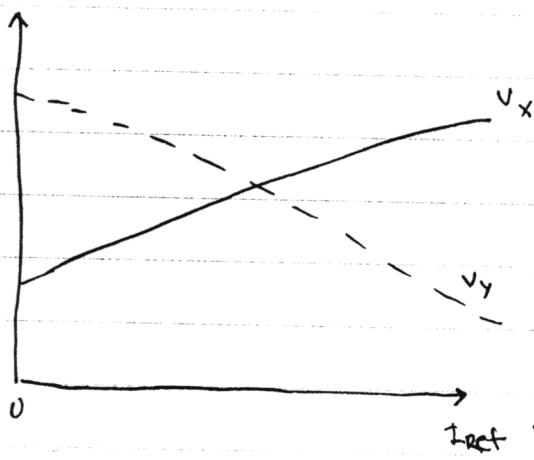
$$V_y = V_x + \frac{V_{DD} - V_x}{2R_1 + R_2} R_2 .$$



As  $I_{ref}$  increases,  $I_2$  increases and hence  $V_{gs2} = V_{gs1} = V_x$  increases. Following KCL, we can find  $V_y$  as a function of  $V_x$ ,  $I_{ref}$


$$V_y = V_{DD} \frac{R_2}{2R_1 + R_2} - I_{ref} \frac{R_1 R_2}{2R_1 + R_2} + \frac{2R_1 V_x}{2R_1 + R_2}$$

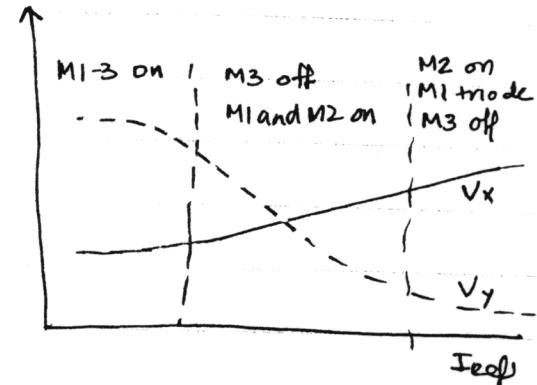
- 5.5(b) Initially when  $I_{ref} = 0$ , this ckt is on with the follow condition  
 $I_1 = I_2 = I_3$  since all transistors are assumed equal and all on.  
 $I_{1-3} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{gs1-3} - V_{th})^2 \quad (1)$   
 $2V_{gs1-3} = V_{dd} - R_i I_{1-3} \quad (2)$   
where  $V_x = V_{gs1-3}$  and  $V_y = 2V_{gs1-3}$ .



Once  $I_{ref}$  increase,  $V_{gs1,2}$  goes up and  $V_y$  drops down, decreasing  $V_{gs3}$  until M3 turns off. Then M1 and M2 act as a typical current mirror for  $I_{ref}$ . Then when  $I_{ref}$  get so large, the  $I_{ref}R_i$  drop increases to a point when M1 goes into triode and can't sustain the  $I_{ref}$  current.

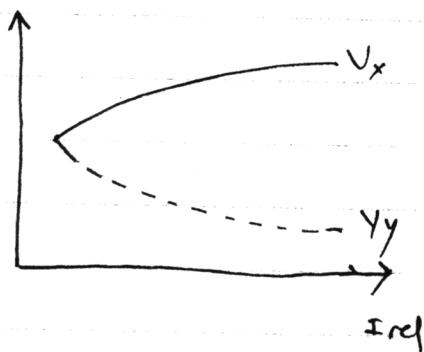- (c) At  $I_{ref}=0$ , all transistors are in saturation mode with  $V_x = V_y$ . Once  $I_{ref}$  turns on, M1 goes into triode and then M4 goes into triode also  
 $V_x \approx V_{gs2}$  and  $V_y = V_{dd} - V_{gs3} \approx V_{dd} - V_{gs2}$



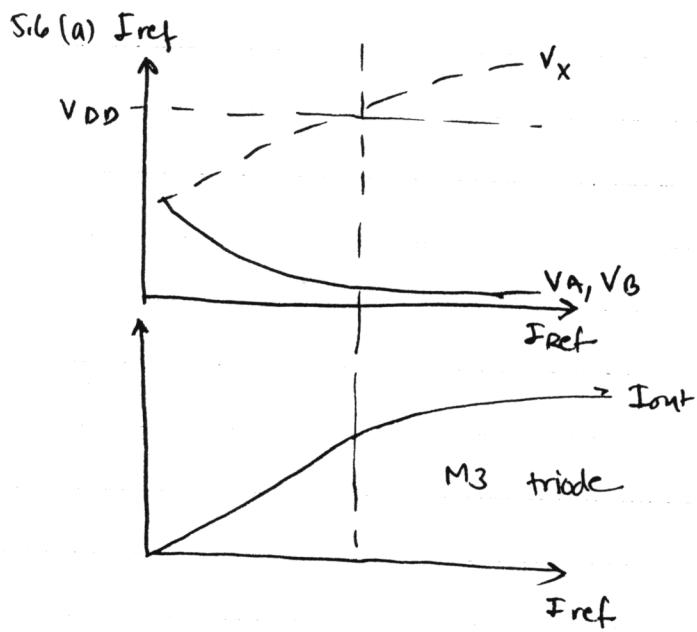

$I_{out}$  follows  $I_{ref}$  for all  $I_{ref}$  until  $V_x > V_{DD}$ . Even if  $M_1$  and  $M_2$  go into triode, they still generate similar currents since  $V_A$  and  $V_B$  match. As  $I_{ref}$  increase,  $V_A, B$  decrease since  $V_{gs1,3}$  increases and  $V_x$  increases since  $V_{gs1,2}$  also increase.

Once  $V_x > V_{DD}$ ,  $M_3$  goes into triode and reduces  $I_{out}$  w.r.t  $I_{ref}$ .



- (b) If  $V_b$  is less than  $1V_{gs}$  for  $I_{REF}$  current,  $V_x$  goes up to a very large voltage to allow for  $I_{REF}$  to flow through  $M_2$  and  $M_4$  if we assume channel resistance.

$$I = \frac{1}{2} \mu_0 \frac{W}{L} (V_{gs} - V_{th}) (1 + \lambda V_{DS})$$

Once  $V_b = 1V_{gs}$ ,  $V_A$  and  $V_B$  are  $\phi V$  and  $I_{out} = I_{ref}$ .

As  $V_b$  increases,  $V_A$  and  $V_B$  increase to turn  $M_1$  and  $M_2$  on.

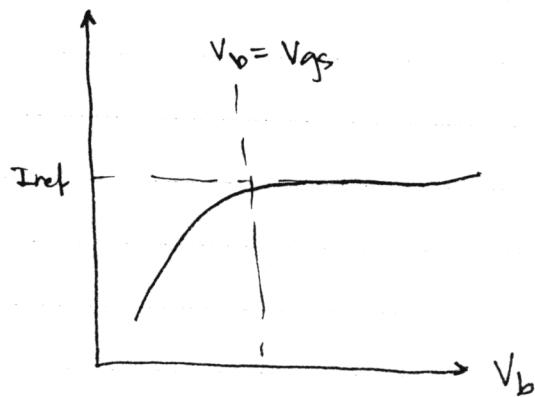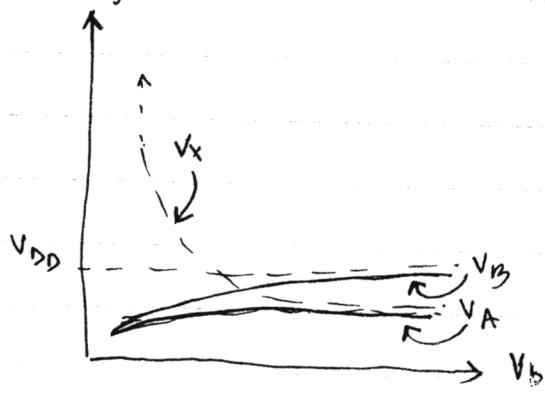$V_x$  is then equal to  $1V_{gs}$ . As  $V_b$  increase further,  $M_3$  and  $M_4$  go into triode while  $M_1$  and  $M_2$  are still in sat.



5.7 (a)  $\sigma=0$

$$K_0 = \frac{1}{2} \mu C_{ox}$$

$$I_{REF} = K_0 \frac{W_0}{L_0} (V_{GS1} - V_{th})^2 (1 + \lambda V_{DS1})$$

$$I_{out} = K_0 \frac{W_0}{L_0} (V_{GS1} - V_{th})^2 (1 + \lambda V_{DS2})$$

where  $V_{DS1} = V_{GS1}$  and  $V_{DS2} = 2V_{GS1} - V_{GS4} - V_{GS3}$

if we assume  $I_{out} \approx I_{REF}$ ,  $V_{GS3} \approx V_{GS1}$ ,

$$\text{so } V_{DS2} = V_{GS1} - V_{GS4}$$

$$V_{GS1} = V_{th} + \sqrt{\frac{I_{REF} L_0}{K_0 W_0}} \quad V_{GS4} = V_{th} + \sqrt{\frac{I_1 L_4}{K_0 W_4}} \quad L' = L - 2L_D$$

$$\frac{I_{out}}{I_{REF}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}} = \frac{1 + \lambda \left( \sqrt{\frac{I_{REF} L_0}{K_0 W_0}} - \sqrt{\frac{I_1 L_4}{K_0 W_4}} \right)}{1 + \lambda \left( V_{th} + \sqrt{\frac{I_{REF} L_0}{K_0 W_0}} \right)}$$

(b)  $\gamma \neq 0$

$$V_{th} = V_{th0} + \gamma (\sqrt{2\phi_f} + V_{SB}) - \sqrt{2\phi_f} \quad \phi_f \approx 4.5 \text{ eV (work func.)}$$

$V_{SB} \equiv \text{Source - substrate voltage}$

Find  $V_{GS1}$ ,  $V_{GS2}$ ,  $V_{GS4}$  and  $V_{GS3}$

$$V_{GS1} = V_{th0} + \sqrt{\frac{I_{REF} L_0}{K_0 W_0}}$$

$$V_{GS2} = V_{th0} + \sqrt{\frac{I_{REF} L_0}{K_0 W_0}} + \gamma (\sqrt{2\phi_f} + V_{GS1}) - \sqrt{2\phi_f}$$

$$V_{GS3} = V_{th0} + \sqrt{\frac{I_{out} L_0}{K_0 W_0}} + \gamma (\sqrt{2\phi_f} + V_{DS2}) - \sqrt{2\phi_f}$$

If we assume  $I_{out} \approx I_{REF}$  and  $V_{DS2} \approx \sqrt{\frac{I_{REF} L_0}{K_0 W_0}} - \sqrt{\frac{I_1 L_4}{K_0 W_4}}$


we can estimate  $V_{GS3}$

$$V_{GS3} \approx V_{th0} + \sqrt{\frac{I_{REF} L_0}{K_0 W_0}} + \gamma \left( \sqrt{2\phi_f} + \sqrt{\frac{I_{REF} L_0}{K_0 W_0}} - \sqrt{\frac{I_1 L_4}{K_0 W_4}} - \sqrt{2\phi_f} \right)$$

$$5.7 \quad V_{GS4} = V_{THO} + \sqrt{\frac{I_1}{k_o} \frac{L_a'}{W_A}} + \gamma (\sqrt{2\phi_f + V_{GS3} + V_{DS2}} - \sqrt{2\phi_f})$$

Now we can plug every thing in to the final solution

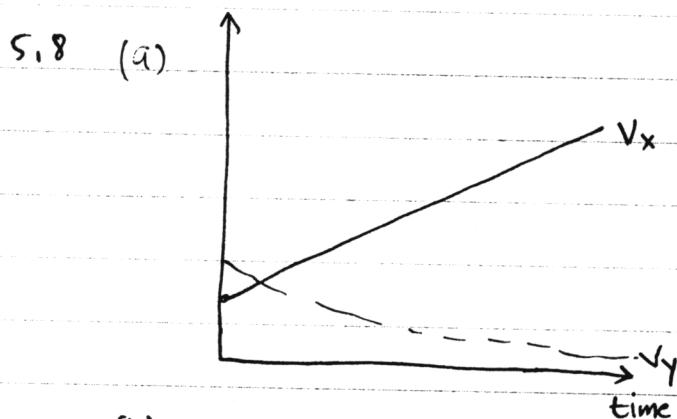
$$\frac{I_{out}}{I_{ref}} \approx \frac{1 + \lambda (V_{GS1} + V_{GS0} - V_{GS4} - V_{GS3})}{1 + \lambda (V_{GS1})}$$



$C_1$  is continuously charged w/  
 $I_{REF}$  so  $V_C$  and  $V_x$  increase with  
time  $V_C = \int_0^t \frac{I_{REF}}{C_1} dt$

$$V_x = V_C + V_{GS2}$$

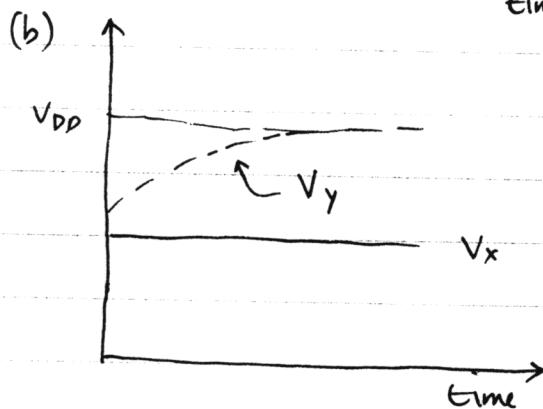
$V_{GS} = V_x$  and  $M_1$  goes into triode



$M_2$  is on with fixed  $V_x = V_{GS2}$   
 $C_1$  is charged with current  $I_1$   
until  $M_1$  turns off.

$$V_y = V_{DD} - I_1 R_y \text{ where}$$

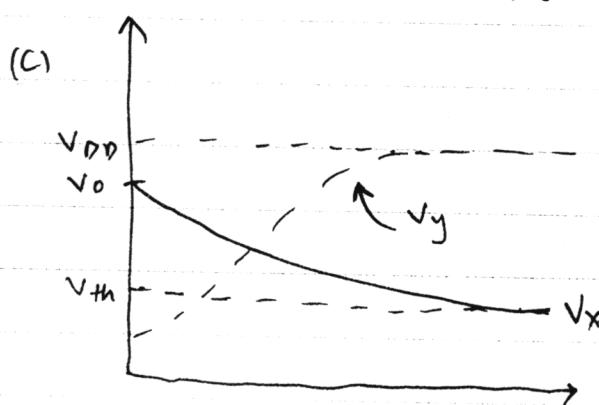
$I_1$  goes from  $I_{ref}$  to  $\emptyset A$ .



With  $C_1$  initially charged w/  $V_0$ ,  
 $M_2$  is on and discharges  $C_1$   
until  $V_x = V_{th}$  and  $I_2 = 0$ .


$$V_y = V_{DD} - R_y I_2 \text{ and as } I_2 \text{ goes to } \emptyset, V_y \text{ goes to } V_{DD}.$$

5.8 (d)

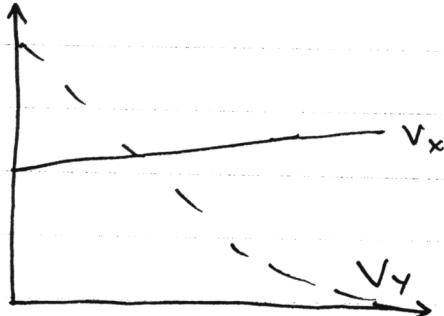

M<sub>2</sub> and M<sub>1</sub> are initially both on, M<sub>1</sub> discharges all the charge in C<sub>1</sub> such that V<sub>y</sub>  $\geq 0$  and M<sub>1</sub> turns off. Since current through M<sub>1</sub> reduces, current through M<sub>2</sub> increases and V<sub>x</sub> increases slightly


(c)

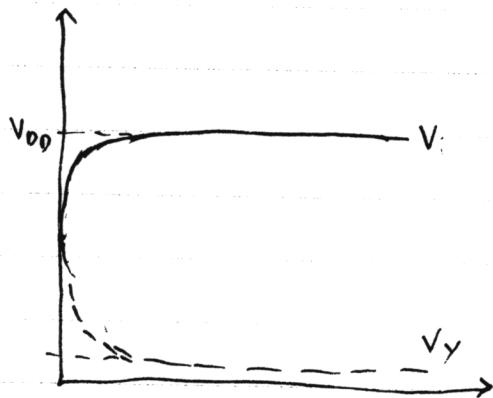


Since M<sub>2</sub> can sustain no current, V<sub>x</sub> goes up to V<sub>DD</sub>. This pushes M<sub>1</sub> into triode and drops V<sub>y</sub> to very small voltage. The voltage across C<sub>1</sub> drops to V<sub>th</sub> to sustain I<sub>2</sub> = 0.

5.9 (a) At t=0, when C<sub>1</sub> is chargedto 0V, V<sub>x</sub> = V<sub>B</sub> - V<sub>gs3</sub> wherethe I<sub>3</sub> = I<sub>ref</sub> and V<sub>y</sub> = V<sub>DD</sub> - R<sub>4</sub>I<sub>ref</sub>.

As the current flows into C<sub>1</sub>, the cap charges up and shuts off M<sub>1</sub>. V<sub>x</sub> is charged up to V<sub>b</sub> - V<sub>th</sub> to sustain I<sub>m</sub> = 0

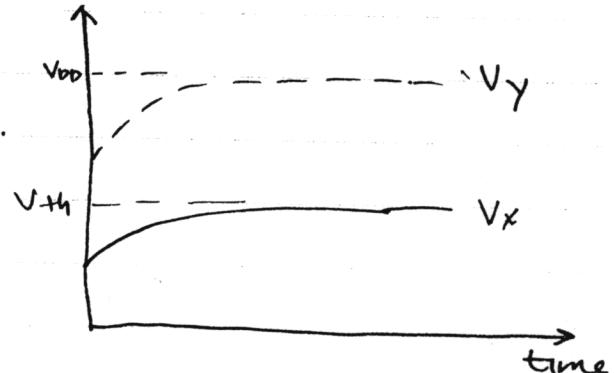
and V<sub>y</sub> = V<sub>DD</sub>

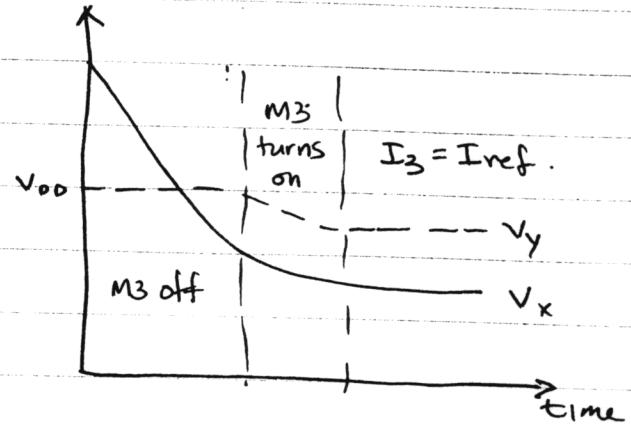5.9 (b) At  $t=0$ ,  $V_x$  is so high that M<sub>3</sub> is off. Current for M<sub>1</sub> and M<sub>2</sub> is generated by  $I_{ref}$  and as  $I_1$  flows through M<sub>1</sub>, C<sub>1</sub> discharges enough to allow current flow through M<sub>3</sub>. Once  $I_3 = I_{REF}$ , C<sub>1</sub> no longer discharges and has a constant set voltage.




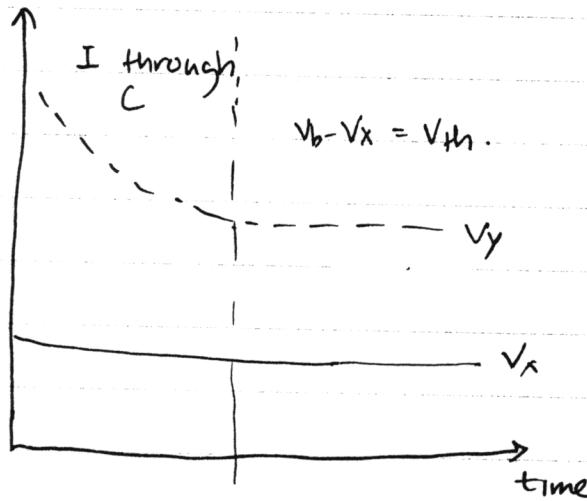(c) At  $t=0$ , all transistors are on.


$V_y = V_{gs3} + V_{dd}$  and  $V_x$  is such that  $I_3 = k \frac{W_3}{L_3} (V_b - V_x - V_{th})^2 \cdot (1 + \lambda V_{bs3})$ . As C<sub>1</sub> discharges,  $V_{bs3}$  decreases and  $V_{gs3}$  increases, lowering  $V_x$ . At the point where  $V_b - V_x = V_{th}$  and  $I_3 = I_{ref} = 0$ ,  $V_y$  stops decreasing.



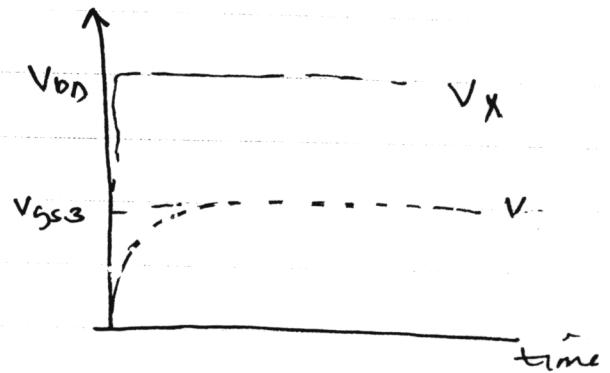
5.10 (a) at  $t=0$ ,  $V_{gs2} = 3V$  and forces current through  $M_2$ . since the source of  $M_2$  is attached to the gate of  $M_1$ , no current can flow and  $V_x = V_{DD}$ .  $C_1$  charges up such that  $I_3 = I_1$  and  $V_y = V_{DD} - V_{gs2}$



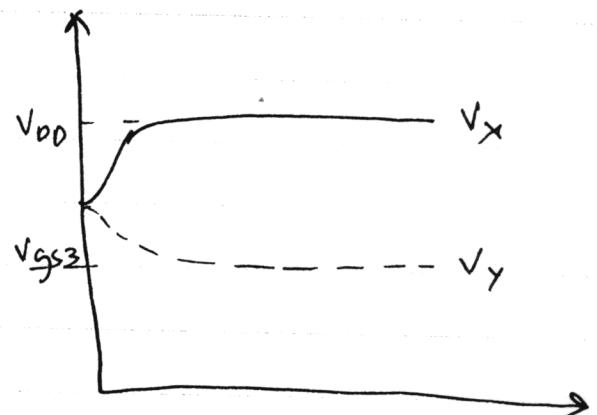(b) Similar to 5.10(a), but since current can flow through  $C_1$  to charge Capacitor.  $V_x$  doesn't instantaneously reach  $V_{DD}$ , but slowly charges to  $V_{DD}$ .  $V_y = V_{DD} - V_{gs3}$  also.



### 5.11 small signal model.

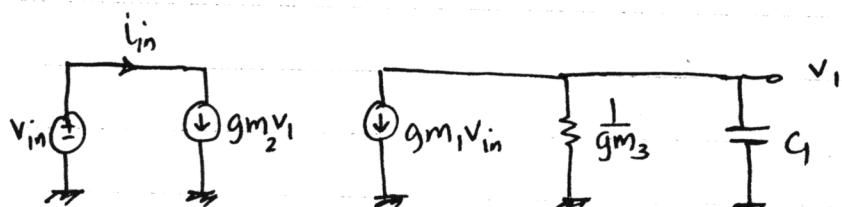


$$\begin{aligned} Z_{in} &= \frac{V_{in}}{I_{in}} = \frac{V_{in}}{g_{m2}v_1} & v_1 &= -g_{m1} \left( \frac{1}{C_s + g_{m3}} \right) v_{in} \\ &= -\frac{C_s + g_{m3}}{g_{m2}g_{m1}} & \text{if all transistors are equal} \\ & \qquad \qquad \qquad g_{m1} = g_{m2} = g_{m3}. \end{aligned}$$

$$Z_{in} = -\frac{C_s}{g_{m2}^2} - \frac{1}{g_{m1}}$$



negative  $C = -\frac{C_s}{g_{m2}^2}$  and negative  $R = -\frac{1}{g_{m1}}$ .

5.12 (a)

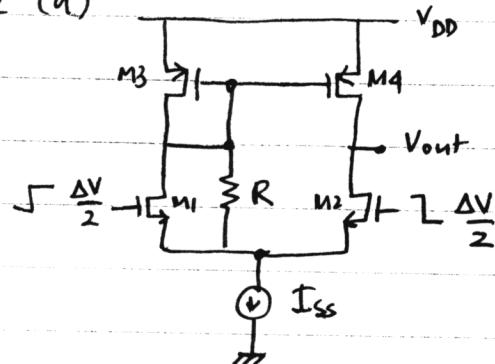

Solve for gain by superposition

$$v_{in} = \Delta V = \frac{\Delta V}{2} - \left(-\frac{\Delta V}{2}\right) = v_{in1} + v_{in2}$$

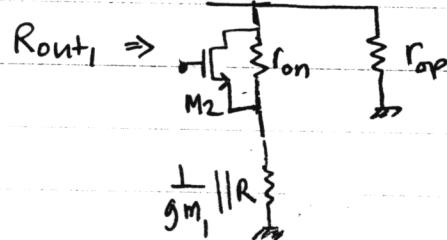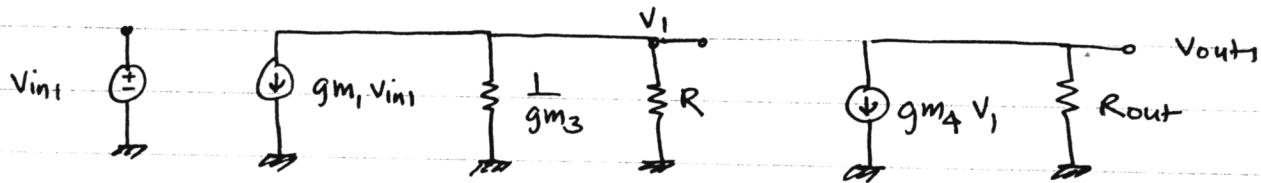1. for  $+\frac{\Delta V}{2}$ , ground M2 gate and find gain.

$$\begin{aligned} R_{out1} &\Rightarrow r_{on} \parallel R \\ R_{out1} &= r_{on} \parallel \left( \frac{1}{g_{m1}} + r_{on} + \frac{g_{m2}}{g_{m1}} r_{on} \right) \\ &\approx r_{on} \parallel 2r_{on} \approx \frac{2}{3} r_{on} = \frac{2}{3} \frac{1}{\lambda I_0} = \frac{4}{3} \frac{1}{\lambda I_{SS}} \end{aligned}$$


$$\frac{v_{out1}}{v_{in1}} = +g_{m1} \left( \frac{1}{g_{m3}} \parallel R \right) g_{m4} R_{out1}$$

2. for  $-\frac{\Delta V}{2}$ 


$$v_{out} = -g_{m2} v_{in2} R_{out1}$$

assume  $g_{m1} = g_{m2}$  and  $g_{m3} = g_{m4}$ 

$$\text{Gain} = \frac{v_{out1} + v_{out2}}{\Delta V} = \frac{g_{m1}}{2} R_{out1} \left[ 1 + \frac{R g_{m3}}{1 + R g_{m3}} \right]$$

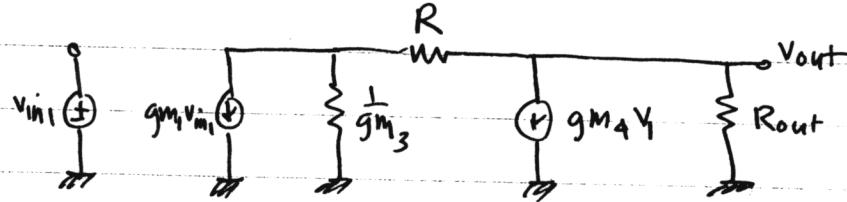(b) for  $v_{in1} = + \frac{\Delta V}{2}$ 

$$\frac{v_{out}}{v_{in1}} = g_{m1} R_{out} \left[ \frac{R g_{m3} - 1}{R g_{m3} + 2 R_{out} + 1} \right]$$

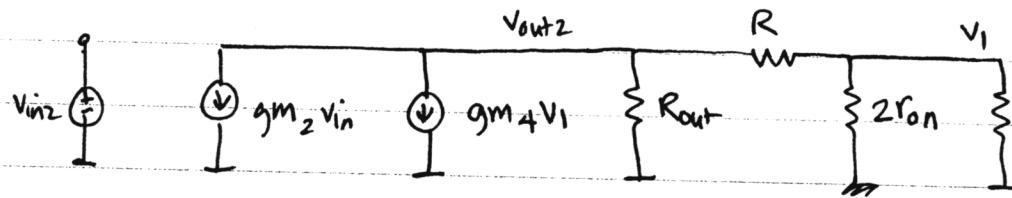for  $v_{in2} = - \frac{\Delta V}{2}$ 

$$v_1 = v_{out2} \cdot \frac{2r_{on} \parallel \frac{1}{g_{m3}}}{R + 2r_{on} \parallel \frac{1}{g_{m3}}} = v_{out2} \cdot \frac{2r_{on}}{R + 2r_{on} + 2g_{m3}r_{on}R}$$


$$v_{out2} = \left( g_{m2}v_{in2} - g_{m4}v_{out2} \right) \frac{2r_{on}}{R + 2r_{on} + 2g_{m3}r_{on}R} \left[ R_{out} \parallel \left( R + 2r_{on} \parallel \frac{1}{g_{m3}} \right) \right]$$

$$\frac{v_{out2}}{v_{in2}} = \frac{-g_{m2} \left[ R_{out} \parallel \left( R + 2r_{on} \parallel \frac{1}{g_{m3}} \right) \right]}{1 + \frac{g_{m4} + 2r_{on}}{R + r_{on} + 2g_{m3}r_{on}R} \cdot \left[ R_{out} \parallel \left( R + 2r_{on} \parallel \frac{1}{g_{m3}} \right) \right]}$$


$$\text{Gain} = \frac{v_{out1} + v_{out2}}{\Delta V}$$

$$S.13 \quad V_{min} = V_p + V_{DSat,2} \quad V_p = V_{CM1,2} - V_{GS1,2}$$


$$= V_{CM1,2} - V_{GS1,2} + V_{DS1,2}$$

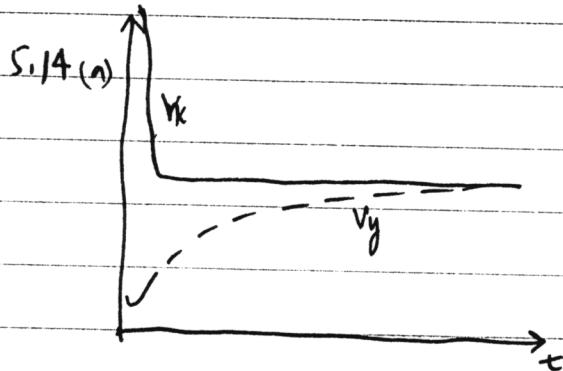

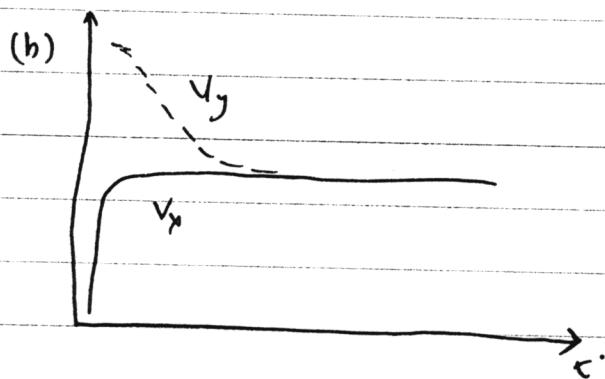$M_3$  and  $M_4$  are initially off.  $M_1$  is on and  $M_2$  is in triode. the current through  $M_1$  initially comes from the  $C_1$  charge until  $V_x$  drops in voltage and  $M_3$  and  $M_4$  turn on.  $M_2$  is still in triode until the current from  $M_4$  charges up  $V_y$  to the same voltage as  $V_x$ .




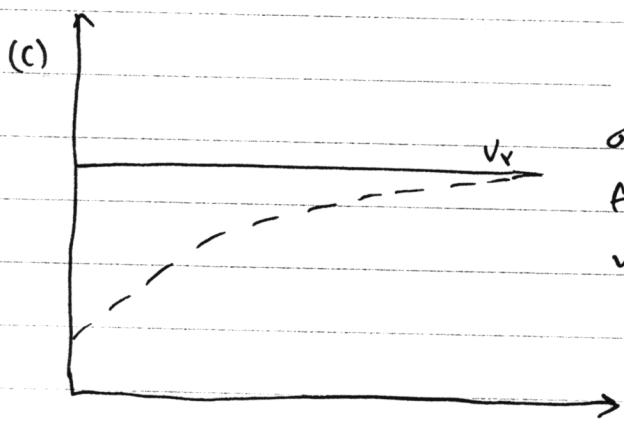$V_x$  starts at  $1.5V - V_{GS1,2}$  where  $M_1$  is in triode and  $M_3$  is on strong.  $M_4$  and  $M_2$  can't sustain that high current w/ tail current =  $I_{SS}$  so  $V_y$  goes up enough to put  $M_4$  in triode and reduce current. Current through  $M_3$  charge  $C_1$  and  $V_y$  reduced its voltage w/ discharge in parasitics.



Initial: short between source & drain of  $M_2$  puts  $M_2$  in triode w/ minimal current flow. Current from  $M_4$  is used to charge up  $C_1$ . As  $C_1$  charges up, some current starts flowing through  $M_2$  until  $V_{DS2}$  is high enough that  $M_2$  is in sat and all current is diverted to  $M_2$ .

S. 15

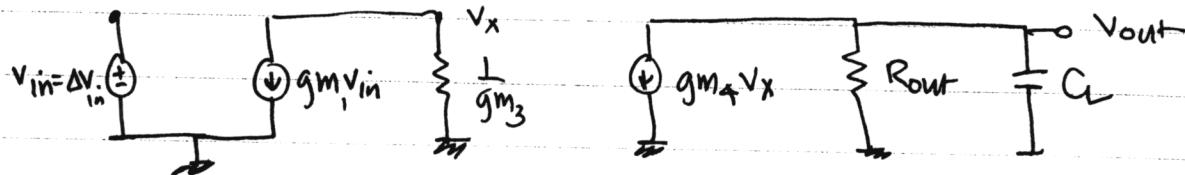
Initial value  $\Rightarrow V_{in} = V_1 \quad V_{out} = V_x$ 

$$\Delta V_{out} = g_{m1} \Delta V_{in} \frac{1}{g_{m2}} g_{m2} R_{out} \quad (\text{final})$$

final value  $\Rightarrow V_{in} = V_1 - \Delta V_{in} \quad V_{out} = V_x - \Delta V_{out}$ 

$$T_C = R_{out} C_L$$

S. 16

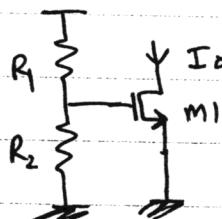

$$\frac{W}{L} = \frac{50\mu}{1.5\mu}, \lambda = 0; I = 0.5mA; k_p = \mu C_{ox} = 137 \times 10^{-9} \frac{A}{V}; L_D = 90nm$$

$$\text{a) } R_2/R_1$$

$$V_{GS1} = V_{DD} \frac{R_2}{R_1 + R_2} = \sqrt{\frac{2I}{k_p \frac{W}{L'}}} + V_{th} \quad L' = L - 2L_D$$

$$\text{Let } R_X = R_2/R_1$$

$$R_X = \frac{\sqrt{\frac{2I}{k_p \frac{W}{L'}}} + V_{th}}{V_{DD} - (\sqrt{\frac{2I}{k_p \frac{W}{L'}}} + V_{th})} = 0.4386$$

$$\text{b) } I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} \left( V_{DD} \frac{R_X}{1+R_X} - V_{th} \right)^2$$

$$\frac{\left( \frac{\partial I_D}{\partial V_{DD}} \right)}{I_D} = \frac{\mu C_{ox} \frac{W}{L} \left( V_{DD} \frac{R_X}{1+R_X} - V_{th} \right) \frac{R_X}{1+R_X}}{\frac{1}{2} \mu C_{ox} \frac{W}{L} \left( V_{DD} \frac{R_X}{1+R_X} - V_{th} \right)^2}$$

$$= \frac{2}{V_{DD} - V_{th} \left( 1 + \frac{1}{R_X} \right)} = 2.84$$

$$5.16 \quad (c) \quad \frac{\partial I_o}{\partial V_{th}} = -u_C \omega \frac{W}{L} \left( V_{DD} \frac{R_x}{1+R_x} - V_{th} \right)$$

$$\Delta I_o \approx -u_C \omega \frac{W}{L} \left( V_{DD} \frac{R_x}{1+R_x} - V_{th} \right) \Delta V_{th} = -233 \mu A$$

$$\Delta I_o = I_o (V_{th} = .75) - I_o (V_{th} = .7) = -205 \mu A$$

$$(d) \quad \frac{\partial I_o}{\partial T} = -\frac{3}{2} \left( \frac{T}{T_0} \right)^{-3/2} \cdot \frac{1}{T} \cdot I_o \quad * \quad T = T_0 + \Delta T$$

$$\Delta I_o \approx -\frac{3}{2} \left( \frac{T}{T_0} \right)^{-3/2} \frac{1}{T} \cdot I_o \Delta T = -103 \mu A \quad *$$

$$\Delta I_o \approx I_o (T=370K) - I_o (T=300K) = -135 \mu A \quad *$$

$$(e) \quad \Delta I_{\text{worst-case}} = I_{\text{worst-case}} - I_o$$


$$I_{\text{worst-case}} = \frac{1}{2} u_C \left( \frac{T_0 + \Delta T}{T_0} \right)^{-3/2} ((V_{DD} - \Delta V_{DD}) \frac{R_x}{1+R_x} - (V_{th} + \Delta V_{th}))$$

$$= 43 \mu A$$

$$\Delta I_{\text{worst case}} = -457 \mu A$$


\* Note as temperature changes, so does  $V_{th}$ . In this calculation, we do not include the temperature effects on threshold voltage.

5.17

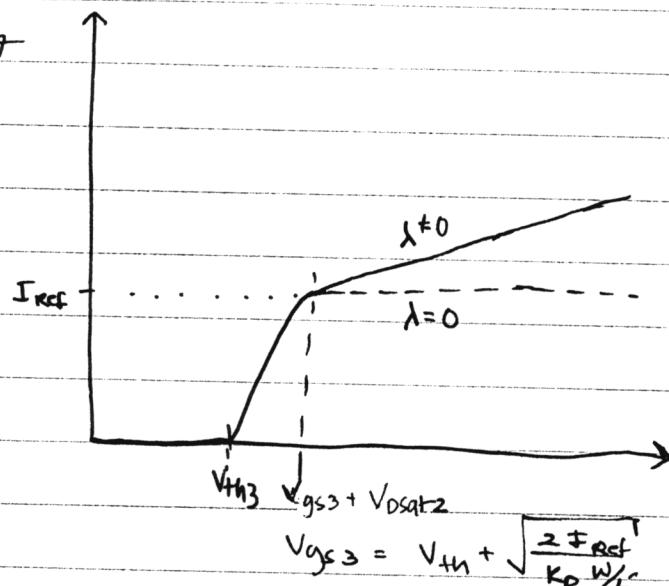

$$V_{gs3} = V_{th} + \sqrt{\frac{2 \cdot I_{Ref}}{K_p W/L}}$$

5.18

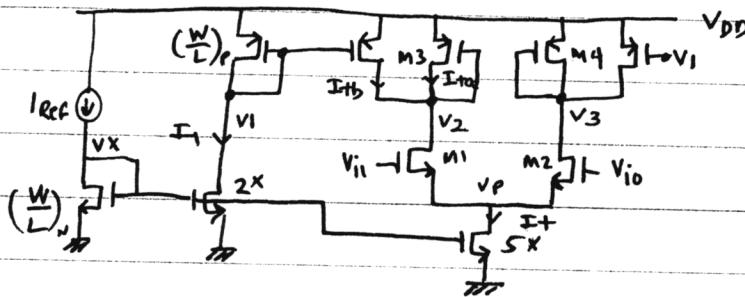

$$(W/L)_N = \frac{10}{.5} \quad (W/L)_{1,2}$$

$$(W/L)_P = \frac{10}{.5} \quad \text{arbitrary}$$

$$I_{Ref} = 100 \mu A$$

$$K_p = 38 \frac{\mu A}{V^2} \quad K_n = 139 \frac{\mu A}{V^2}$$

(a)  $\lambda = 0$ 

$$\frac{1}{2} = \frac{1}{2} K_p \frac{W}{L-2L_0} (V_{gs} - V_t)^2$$

$$V_t = V_{DD} - V_{gs(P)} = V_{DD} - V_{tp} - \sqrt{\frac{2 \cdot 2 \cdot I_{Ref}}{K_p \frac{W}{L-2L_0}}} = 1.619 V$$

$$V_2 = V_3 = V_{DD} - V_{gs(3)} = V_{DD} - V_{tp} - \sqrt{\frac{I_{Ref}}{K_p \frac{W}{L-2L_0}}} = 1.909 V$$

$$V_p = V_{cm} - V_{gs(1)} = 1.3 - V_{th} - \sqrt{\frac{2 \cdot 5 \cdot I_{ref}}{K_n W}} = .3747 V \quad (\gamma = 0)$$

$V_p$  for  $\gamma = .45$  is found iteratively by finding  $V_{th}$  iteratively also.

$$V_{th} (V_p = .3747) = V_{tp} + \gamma \sqrt{2\phi + V_{SB}} - \gamma \sqrt{2\phi} \quad \gamma = .45, \phi = .45$$

$$= .78$$

$$V_p (V_{th} = .78) = .29 \text{ until } V_{th}(\text{final}) = .767$$

$$V_p(\text{final}) = .307$$

5.18 (b)  $\lambda = 2$ 

$$V_{GS}(0) = V_{TN} + \sqrt{\frac{2I_{ref}}{K_n \cdot \frac{W}{L-2L_0}}} = 0.9253$$

for  $I_T$ , initially assume  $V_p = .307$  from part (a)  
iterate with

$$\left\{ \begin{array}{l} I_T = I_{ref} \cdot 5 \cdot \frac{1 + \lambda V_p}{1 + \lambda V_{GS}(0)} \\ \text{and} \end{array} \right.$$

$$V_p = V_{CM1,2} - V_{GS(1,2)} \quad \text{with} \quad V_{TN1,2} = V_{TO} + \sqrt{2\phi + V_p} - \gamma\sqrt{2\phi}$$

$$I_T = 448 \mu A \quad \text{and} \quad V_p = 0.317$$

for  $V_1$ , iterate also

$$\left\{ \begin{array}{l} I_1 = I_{ref} \cdot 2 \cdot \frac{1 + \lambda V_1}{1 + \lambda V_{GS}(0)} \end{array} \right.$$

$$V_1 = V_{DD} - |V_{GS1}| = V_{DD} - V_{TP} - \sqrt{\frac{2 \cdot I_1}{K_p \frac{W}{L-2L_0}}}$$

$$\text{final } I_1 = 222 \mu A, \quad V_1 = 1.59 V$$

for  $V_2, V_3$ , iterate also.


$$\left\{ \begin{array}{l} I_{Ta} = I_T / 2 - I_{Tb} \\ V_{2,3} = V_{DD} - |V_{GS3,6}| = V_{DD} - V_{TP} - \sqrt{\frac{2 \cdot I_{Ta}}{K_p \frac{W}{L-2L_0}}} \\ I_{Tb} = I_1 \cdot \frac{1 + \lambda |V_{GS3,6}|}{1 + \lambda |V_{GS1}|} \end{array} \right.$$

$$I_{Ta} = 17.3 \mu A; \quad I_{Tb} = 207 \mu A; \quad V_{2,3} = 2.029 V$$

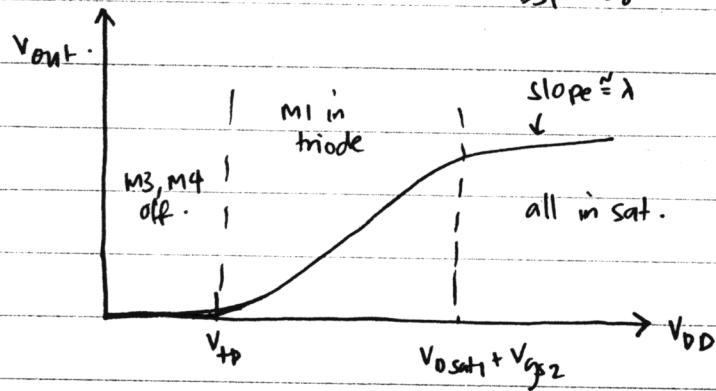5.19  $V_{DD} < V_{TP}$  : M2 and M3 off,  $I_3 = 0$ ,  $V_{out} = 0$

$V_{TP} \leq V_{DD} < V_{DSAT1} + V_{GS2}$  : M1 in triode, linearly approaching saturation. M2 and M3 are on with  $V_{out}$  increasing linearly.

$V_{DD} > V_{DSAT1} + V_{GS2}$  : All transistors are on and as  $V_{DD}$  increases,  $V_{DS1}$  increases so current increases as  $\lambda V_{DS1} \cdot I_0$ .



$$5.20 \quad \gamma = 0 \quad \left(\frac{W}{L}\right)_{1-3} = \frac{10}{5} \quad I_{ref} = .3 \text{ mA} \quad K_n = 138 \frac{\mu\text{A}}{\text{V}^2} \quad L_D = 80 \text{ nm}$$

$$(a) \quad V_b = 2V_{GS1} \quad V_{GS1} = V_{TN} + \sqrt{\frac{2I_{ref}}{K_n} \frac{W}{L^2 L_D}} = .892 \text{ V}$$

$$V_b = 1.78 \text{ V}$$

$$(b) \quad I_{out} = I_{ref} \cdot \frac{(1 + \lambda(V_{GS1} + \Delta V_b))}{1 + \lambda V_{GS1}} = 295 \mu\text{A} \quad \Delta V_b = -.100 \text{ V}$$

$$\Delta I_{out} = \frac{I_{ref} \cdot \lambda \Delta V_b}{1 + \lambda V_{GS1}}$$

5.20 (c)  $V_p$  increases by 1V

$V_y$  increases by  $\Delta x$

solve for 2 unknowns and 2 equations

$$\left\{ \begin{array}{l} I_{out} = I_{ref} \left( \frac{1 + \lambda (V_{gs1} - \Delta x)}{1 + \lambda V_{gs1}} \right) \quad (M2) \\ \end{array} \right. \quad \text{eq 1.}$$

$$\left\{ \begin{array}{l} I_{out} = \frac{1}{2} k_n \frac{w}{L-2L_D} (V_{gs1} - \Delta x)^2 \left( \frac{1 + \lambda (V_{gs1} + 1V - \Delta x)}{1 + \lambda V_{gs1}} \right) \quad (M3) \end{array} \right. \quad \text{eq 2.}$$

$$\Delta x = 13 \text{ mV}$$

$$V_y = V_{gs1} + \Delta x = .905 \text{ V}$$

$$5.21 (a) V_x = V_{gs1} = V_{th} + V_{dsat1} = .863$$

$$V_{dsat1} = \sqrt{\frac{2I_{ref}}{k_n \frac{w}{L-2L_D}}} = .163 \quad V_{th} = .7 \text{ V}$$

$$V_b = V_{dsat1} + V_{gs2}$$

$$\begin{aligned} V_{gs2} &= V_{th} + \sigma \sqrt{2\phi + V_{dsat1}} - \sigma \sqrt{2\phi} + \sqrt{\frac{2I_{ref}}{k_n \frac{w}{L-2L_D}}} \\ &= .7 + .037 + .163 = .900 \text{ V} \end{aligned}$$

As  $V_b$  increases, M2 and M4 go into triode and  $V_A \approx V_x$

and  $V_B \approx V_{M4,drain}$ . As long as  $V_{M4,drain}$  does not drop

Below  $V_{dsat1}$ ,  $I_{out}$  will reasonably follow  $I_{ref}$ .


b)  $V_{M4,drain} \uparrow 1V$ ,  $V_B \uparrow \Delta x$

use eq 1 and 2. from 5.20 to solve for change in current.

$$I_{out} = 301.1 \mu A \quad \Delta x = 21 \text{ mV}$$

5.22 Assume  $\lambda=0$  for bias purpose and  $\lambda=.2$  for small signal analysis.

(a) DC Bias

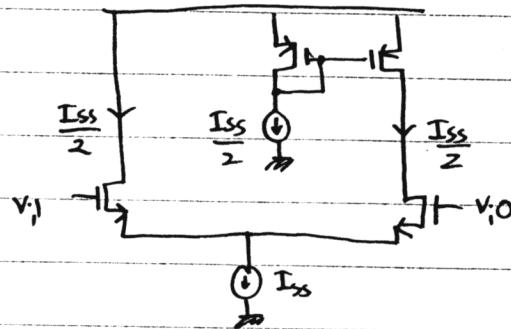

$$g_{m1,2} = \frac{I_{ss}}{V_{dsat1,2}} = 3.18 \text{ mS}$$

$$V_{dsat1,2} = \sqrt{\frac{I_{ss}/K_n}{W/L-2L_D}} = .157$$

$$r_{on} = r_{op} = \frac{1}{\lambda I_{ss}} = 20 \text{ K}$$

Small signal: Gain =  $\frac{v_{out}}{v_{i1} - v_{i0}} = \frac{1}{2} g_{m1,2} R_{out} = 21.2$

$$R_{out} = r_{op} \parallel (2r_{on} + \frac{1}{g_{m1}}) \approx \frac{2}{3} r_o = 13.33 \text{ K}$$

(b) Maximum output voltage swing.

$$\begin{aligned} v_{out(\min)} &= V_{cm} - V_{gs1,2}(I = \frac{I_{ss}}{2}) + V_{dsat1,2} \\ &= V_{cm} - V_{tn1,2} \\ &= 1.3 - .778 = .522 \text{ V} \end{aligned}$$

$$v_{out(\max)} = V_{dd} \quad (\text{M4 in triode})$$

$$\begin{aligned} v_{out(\max)} - v_{out(\min)} &= V_{ds} - V_{cm} + V_{tn1,2} \\ &= 3.1V - 1.3V + .778 = 2.48V \end{aligned}$$

$$V_{tn} = V_{to} + \delta \sqrt{2\phi + 3.6} - \delta \sqrt{2\phi} = .778$$

S.23. Assume  $I_3 = I_4$  though  $V_{th3} \neq V_{th4}$

$$(a) \quad I_3 = \frac{1}{2} k_p \frac{w}{L-2L_0} (V_{gs3} - V_{th3})^2 (1 + \lambda |V_{gs3}|)$$

$$I_4 = \frac{1}{2} k_p \frac{w}{L-2L_0} (V_{gs4} - V_{th4})^2 (1 + \lambda (|V_{gs4}| - \Delta x))$$

$$K' = \frac{1}{2} k_p \frac{w}{L-2L_0}$$

$$K' (V_{dsat3})^2 (1 + \lambda |V_{gs3}|) = K' (V_{dsat3} | - ImV )^2 (1 + \lambda |V_{gs3}| + \lambda \Delta x)$$

$$\Delta x \stackrel{\approx}{=} \frac{ImV \cdot (1 + \lambda |V_{gs3}|)}{\lambda |V_{dsat3}|}$$

$$V_F = V_{gs3} - \Delta x.$$

$$(b) \quad CMRR \stackrel{\triangle}{=} \left| \frac{A_{dm}}{A_{cm}} \right|$$

$$A_{dm} = g_{m1,2} (r_{o3,4} || r_{o1,2})$$


$$= g_{m1,2} (\frac{1}{2} r_o)$$

$$A_{cm} \stackrel{\approx}{=} \frac{-1}{1 + 2 g_{m1,2} r_o} \cdot \frac{g_{m1,2}}{g_{m3,4}}$$

$$CMRR = (1 + 2 g_{m1,2} r_o) g_{m3,4} (r_{o1,2} || r_{o2,4})$$

## Chapter 6

6. 1 (a)

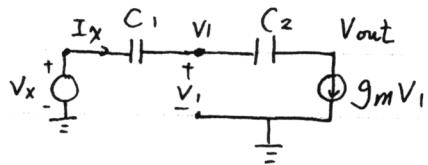
 $g_m$ : transconductance of M<sub>1</sub>.

$$I_x = SC_1(V_x - V_1) = SC_2(V_1 - V_{out}) = g_m V_1$$

$$\therefore SC_1 V_x = (g_m + SC_1) V_1 \Rightarrow V_1 = \left[ \frac{SC_1}{g_m + SC_1} \right] V_x$$

$$\Rightarrow I_x = g_m V_1 = \left[ \frac{g_m SC_1}{g_m + SC_1} \right] V_x$$
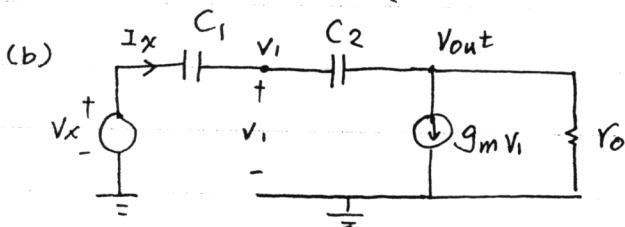
$$\Rightarrow Z_{in} = \frac{V_x}{I_x} = \frac{g_m + SC_1}{g_m SC_1}$$



$$g_m = g_{m1} + g_{m2}$$

$$r_o = r_{o1} // r_{o2}$$

 $g_{m1}, g_{m2}$ : transconductance for M<sub>1</sub>, M<sub>2</sub> $r_{o1}, r_{o2}$ : output resistance for M<sub>1</sub>, M<sub>2</sub>

$$\therefore \overbrace{I_x = SC_1(V_x - V_1)}^{\textcircled{2}} = \underbrace{SC_2(V_1 - V_{out})}_{\textcircled{1}} = g_m V_1 + \frac{V_{out}}{r_o}$$

from  $\textcircled{1}$ :

$$\frac{V_{out}}{V_1} = \frac{SC_2 - g_m}{SC_2 + \frac{1}{r_o}}$$

from  $\textcircled{2}$ :

$$(SC_1 + SC_2)V_1 = SC_1 V_x + SC_2 V_{out}$$

$$= SC_1 V_x + \frac{S^2 C_2^2 - g_m S C_2}{SC_2 + \frac{1}{r_o}} V_1$$

$$\Rightarrow \left[ SC_1 + SC_2 - \frac{S^2 C_2^2 - g_m S C_2}{SC_2 + \frac{1}{r_o}} \right] V_1 = SC_1 V_x$$

6.2


pg 2

$$\Rightarrow \left[ \frac{SC_1C_2 + \frac{SC_1}{r_o} + \frac{SC_2}{r_o} + g_m s C_2}{SC_2 + \frac{1}{r_o}} \right] V_I = SC_1 V_x$$

$$\therefore V_I = \left[ \frac{SC_1C_2 + \frac{C_1}{r_o}}{SC_1C_2 + \frac{C_1}{r_o} + \frac{C_2}{r_o} + g_m C_2} \right] V_x$$

$$I_X = SC_1(V_x - V_I) = SC_1 \cdot \left[ \frac{\frac{C_2}{r_o} + g_m C_2}{SC_1C_2 + \frac{C_1}{r_o} + \frac{C_2}{r_o} + g_m C_2} \right] V_x$$
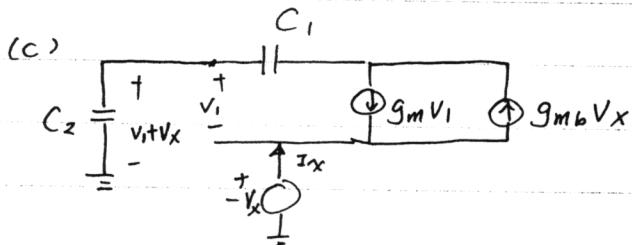
$$Z_{in} = \frac{V_x}{I_X} = \frac{SC_1C_2 + \frac{C_1}{r_o} + \frac{C_2}{r_o} + g_m C_2}{SC_1C_2(\frac{1}{r_o} + g_m)} \quad \times$$



$$SC_2(V_I + V_x) + g_m V_I = g_{mb} V_x$$

$$\Rightarrow (SC_2 + g_m)V_I = (g_{mb} - SC_2)V_x$$


$$\frac{V_x}{V_I} = \frac{SC_2 + g_m}{g_{mb} - SC_2}$$

$$I_X = -g_m V_I + g_{mb} V_x$$

$$= \left[ -g_m \cdot \frac{g_{mb} - SC_2}{SC_2 + g_m} + g_{mb} \right] V_x = \left[ \frac{(g_m + g_{mb})SC_2}{SC_2 + g_m} \right] V_x$$

$$Z_{in} = \frac{V_x}{I_X} = \frac{SC_2 + g_m}{SC_2(g_m + g_{mb})} \quad \times$$

6.2 (a)

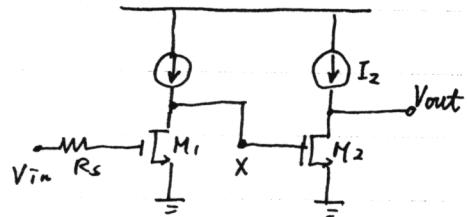

There are three poles associated with this circuit.

The first pole @  $V_{out}$

$$\omega_{p, \text{out}} = \frac{1}{R_o \cdot (C_{gd2} + C_{db2})}$$

The pole @ the input

$$\omega_{p, \text{in}} = \frac{1}{R_s \cdot [(1+g_m r_o) C_{gd1} + (g_s)_1]}$$


The pole @ node X

$$\omega_{p, X} = \frac{1}{R_o \cdot [(C_{gd1} + C_{db1} + (g_s)_2) + (1+g_m r_o) \cdot C_{gd2}]}$$


Please note that the above approximation is based on Miller effect.

In order to get more accuracy approximation, transfer function has to be derived.

(b) Small signal model

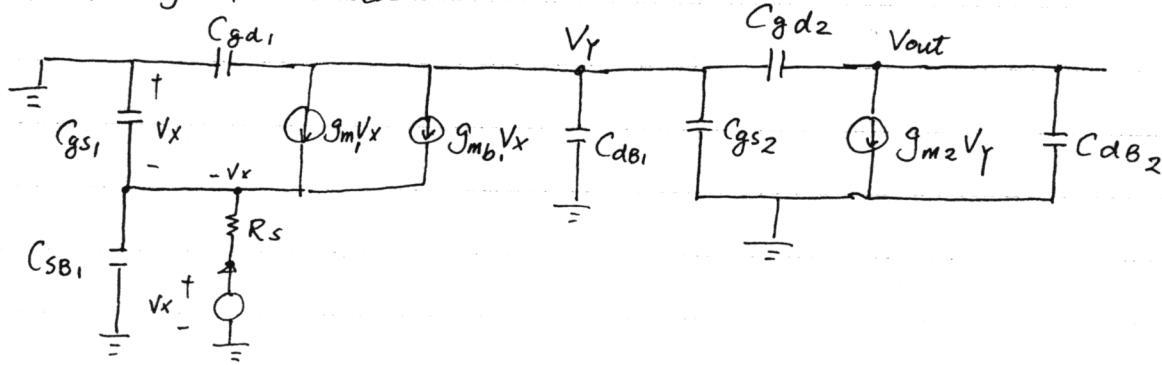

Redraw small signal model

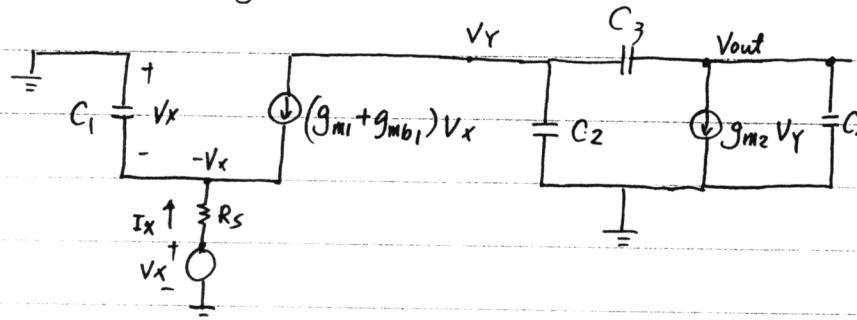

$$C_1 = C_{gs1} + C_{SB1}$$

$$C_2 = C_{gs2} + C_{dB1} + C_{gd1}$$

$$C_3 = C_{gd2}$$

$$C_4 = C_{dB2}$$

$$\text{KCL at } V_{out} : SC_3(V_Y - V_{out}) = g_{m2}V_Y + SC_4V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_Y} = \frac{-g_{m2} + SC_3}{S(C_3 + C_4)}$$

$$\text{KCL at } V_Y : (g_{m1} + g_{mb1})V_X + SC_2V_Y + SC_3(V_Y - V_{out}) = 0$$

$$(g_{m1} + g_{mb1})V_X = -V_Y \left( SC_2 + \frac{S^2C_3C_4 + SC_3 \cdot g_{m2}}{S(C_3 + C_4)} \right)$$

$$\frac{V_Y}{V_X} = -\frac{g_{m1} + g_{mb1}}{S(C_2C_3 + C_2C_4 + C_3C_4) + C_3g_{m2}} / (C_3 + C_4)$$

$$\text{KCL at } V_X : \frac{V_{in} + V_X}{R_s} + SC_1V_X + (g_{m1} + g_{mb1})V_X = 0$$

$$\frac{V_X}{V_{in}} = -\frac{1}{SC_1R_s + (1 + (g_{m1} + g_{mb1}) \cdot R_s)}$$



Thus, there are three poles

$$\omega_{p0} = 0$$

$$\omega_{p1} = \frac{-C_3g_{m2}}{C_2C_3 + C_2C_4 + C_3C_4} *$$

$$\omega_{p2} = \frac{-(1 + (g_{m1} + g_{mb1}) \cdot R_s)}{C_1R_s} *$$

6.3 (a) Small signals

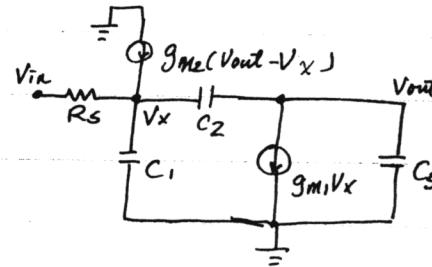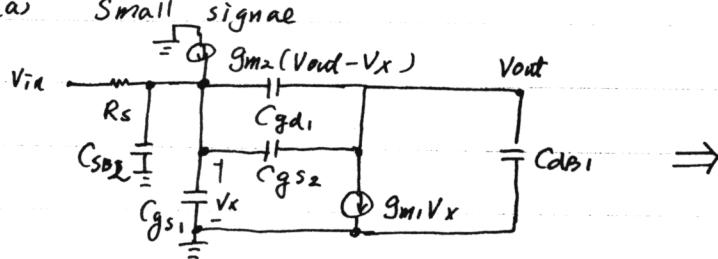

$$C_1 = C_{gs1} + C_{sb2}$$

KCL @ V\_oud:

$$C_2 = C_{gd1} + C_{gs2}$$

$$SC_2(V_x - V_{oud}) = g_{m1}V_x + SC_3V_{out}$$

$$C_3 = C_{db1}$$


$$\therefore \frac{V_{out}}{V_x} = \frac{SC_2 - g_{m1}}{S(C_2 + C_3)} - \Phi$$

$$\text{KCL @ } V_x: \frac{V_{in} - V_x}{R_s} + g_{m2}(V_{out} - V_x) = SC_1V_x + SC_2(V_x - V_{out})$$

$$\Rightarrow \frac{V_{in}}{R_s} = V_x \left( \frac{1}{R_s} + g_{m2} + SC_1 + SC_2 \right) - (g_{m2} + SC_2) \cdot \left[ \frac{SC_2 - g_{m1}}{S(C_2 + C_3)} \right] V_x$$

$$= V_x \cdot \frac{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S \left( \frac{1}{R_s}(C_2 + C_3) + g_{m1}C_2 + g_{m2}C_3 \right) + g_{m1}g_{m2}}{S(C_2 + C_3)}$$
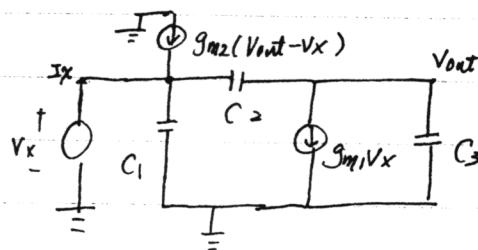
$$\therefore \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}} = \frac{\frac{1}{R_s}(SC_2 - g_{m1})}{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S \left[ \frac{1}{R_s}(C_2 + C_3) + g_{m1}C_2 + g_{m2}C_3 \right] + g_{m1}g_{m2}}$$




$$I_x = SC_1V_x + SC_2(V_x - V_{out}) + g_{m2}(V_x - V_{out})$$

$$\text{from } \Phi: V_x - V_{out} = \left( \frac{SC_3 + g_{m1}}{S(C_2 + C_3)} \right) V_x$$

$$\therefore I_x = \left[ SC_1 + \frac{S^2C_2C_3 + g_{m1}SC_2 + g_{m2}SC_3 + g_{m1}g_{m2}}{S(C_2 + C_3)} \right] V_x$$

$$= \left[ \frac{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S(g_{m1}C_2 + g_{m2}C_3) + g_{m1}g_{m2}}{S(C_2 + C_3)} \right] V_x$$
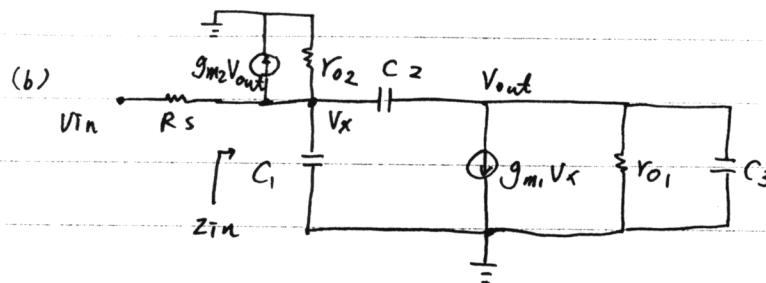
$$Z_{in} = \frac{V_x}{I_x} = \frac{S(C_2 + C_3)}{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S(g_{m1}C_2 + g_{m2}C_3) + g_{m1}g_{m2}}$$



$$C_1 = C_{gs1} + C_{dB2}$$

$$C_2 = C_{gd1} + C_{gd2}$$

$$C_3 = C_{dB1} + C_{gs2}$$

$$\text{KCL at } V_{out} : SC_2(V_x - V_{out}) = g_{m1}V_x + V_{out}\left(\frac{1}{r_{o1}} + sC_3\right)$$

$$\frac{V_{out}}{V_x} = \frac{SC_2 - g_{m1}}{s(C_2 + C_3) + \frac{1}{r_{o1}}}$$

$$\text{KCL at } V_x : \frac{V_{in} - V_x}{R_S} = g_{m2}V_{out} + V_x\left(\frac{1}{r_{o2}} + sC_1\right) + SC_2(V_x - V_{out})$$

$$\frac{V_{in}}{R_S} = \left(SC_1 + s(C_2 + \frac{1}{r_{o2}} + \frac{1}{R_S})V_x - \frac{(g_{m2} + sC_2)(SC_2 - g_{m1})}{s(C_2 + C_3) + \frac{1}{r_{o1}}} \cdot V_x\right)$$

$$= \frac{s^2(C_1C_2 + C_1C_3 + C_2C_3) + s\left[\left(\frac{1}{r_{o2}} + \frac{1}{R_S}\right)(C_2 + C_3) + \frac{1}{r_{o1}}(C_1 + C_2) + g_{m1}C_2 + g_{m2}C_2\right] - g_{m1}g_{m2} + \frac{1}{r_{o1}}\left(\frac{1}{r_{o2}} + \frac{1}{R_S}\right)}{s(C_2 + C_3) + \frac{1}{r_{o1}}}$$


$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{R_S}(SC_2 - g_{m1})}{s^2(C_1C_2 + C_1C_3 + C_2C_3) + s\left[\left(\frac{1}{r_{o2}} + \frac{1}{R_S}\right)(C_2 + C_3) + \frac{1}{r_{o1}}(C_1 + C_2) + g_{m1}C_2 + g_{m2}C_2\right] - g_{m1}g_{m2} + \frac{1}{r_{o1}}\left(\frac{1}{r_{o2}} + \frac{1}{R_S}\right)}$$

For  $Z_{in}$

$$I_X = g_{m2}V_{out} + V_x\left(\frac{1}{r_{o2}} + sC_1\right) + SC_2(V_x - V_{out})$$

$$= \left[ \frac{s^2(C_1C_2 + C_1C_3 + C_2C_3) + s\left[\frac{1}{r_{o2}}(C_2 + C_3) + \frac{1}{r_{o1}}(C_1 + C_2) + g_{m1}C_2 + g_{m2}C_2\right] + (g_{m1}g_{m2} + \frac{1}{r_{o1}}\frac{1}{r_{o2}})}{s(C_2 + C_3) + \frac{1}{r_{o1}}} \right] V_x$$
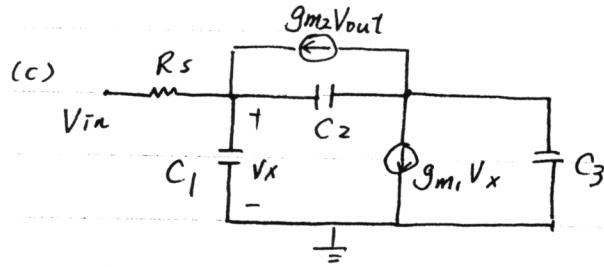
$$Z_{in} = \frac{V_x}{I_X} = \frac{s(C_2 + C_3) + \frac{1}{r_{o1}}}{s^2(C_1C_2 + C_1C_3 + C_2C_3) + s\left[\frac{1}{r_{o2}}(C_2 + C_3) + \frac{1}{r_{o1}}(C_1 + C_2) + g_{m1}C_2 + g_{m2}C_2\right] + (-g_{m1}g_{m2} + \frac{1}{r_{o1}}\frac{1}{r_{o2}})}$$



$$C_1 = C_{gs1} + C_{d\theta 2} + C_{gd2}$$

$$C_2 = C_{gd1}$$

$$C_3 = C_{d\theta 1} + C_{s\theta 2} + C_{gs2}$$

KCL @ Vout :  $SC_2(V_x - V_{out}) = g_{m1}V_x + SC_3V_{out} + g_{m2}V_{out}$

$$\Rightarrow \frac{V_{out}}{V_x} = \frac{SC_2 - g_{m1}}{SC_2 + C_3 + g_{m2}}$$

KCL @ Vx :  $\frac{V_{in} - V_x}{R_s} + g_{m2}V_{out} = SC_1V_x + SC_2(V_x - V_{out})$

$$\frac{V_{in}}{R_s} = \left( \frac{1}{R_s} + SC_1 + SC_2 \right) V_x - (g_{m2} + SC_2) V_{out} = \left( \frac{1}{R_s} + SC_1 + SC_2 \right) V_x - \frac{(g_{m2} + SC_2)(SC_2 - g_{m1})}{S(C_2 + C_3) + g_{m2}}$$

$$\frac{V}{V} = \frac{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S \left[ \frac{1}{R_s}(C_2 + C_3) + g_{m2}C_1 + g_{m1}C_2 \right] + \left[ \frac{g_{m2}}{R_s} + g_{m1}g_{m2} \right]}{S(C_2 + C_3) + g_{m2}}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$$

$$= \frac{\frac{1}{R_s}[SC_2 - g_{m1}]}{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S \left[ \frac{1}{R_s}(C_2 + C_3) + g_{m2}C_1 + g_{m1}C_2 \right] + \left( \frac{g_{m2}}{R_s} + g_{m1}g_{m2} \right)}$$


For  $Z_{in}$

$$I_x = SC_1V_x - g_{m2}V_{out} + SC_2(V_x - V_{out})$$

$$= \left[ \frac{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S(g_{m2}C_1 + g_{m1}C_2) + g_{m1}g_{m2}}{S(C_2 + C_3) + g_{m2}} \right] V_x$$

$$Z_{in} = \frac{S(C_2 + C_3) + g_{m2}}{S^2(C_1C_2 + C_2C_3 + C_1C_3) + S(g_{m2}C_1 + g_{m1}C_2) + g_{m1}g_{m2}}$$

(d)

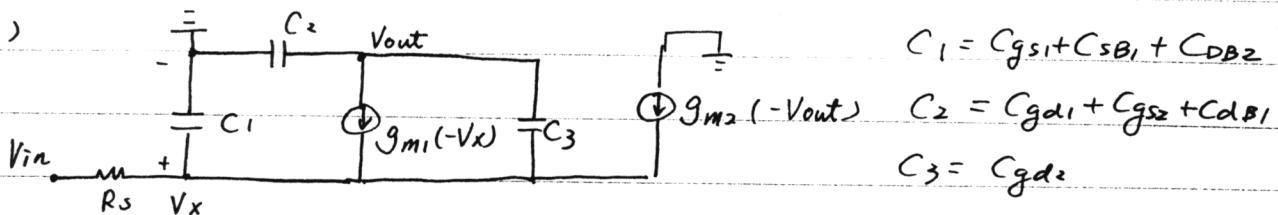

$$C_1 = C_{gs1} + C_{SB1} + C_{DB2}$$

$$C_2 = C_{gd1} + C_{gs2} + C_{dB1}$$

$$C_3 = C_{gd2}$$

$$\text{KCL at } V_{out} : -SC_2 V_{out} = -g_{m1} V_x + SC_3 (V_{out} - V_x)$$

$$\frac{V_{out}}{V_x} = \frac{SC_3 + g_{m1}}{S(C_2 + C_3)}$$

$$\text{KCL at } V_x : \frac{V_{in} - V_x}{R_s} = SC_1 V_x + g_{m1} V_x + SC_3 (V_x - V_{out}) + g_{m2} V_{out}$$

$$\begin{aligned} \frac{V_{in}}{R_s} &= \left[ \frac{1}{R_s} + S(C_1 + C_3) + g_{m1} \right] V_x + \frac{(SC_3 + g_{m1})(g_{m2} - SC_3)}{S(C_2 + C_3)} V_x \\ &= V_x \left[ \frac{S^2(C_1 C_2 + C_1 C_3 + C_2 C_3) + S \left[ \frac{C_1}{R_s} + \frac{C_3}{R_s} + g_{m1} C_2 + g_{m2} C_3 \right] + g_{m1} g_{m2}}{S(C_2 + C_3)} \right] \end{aligned}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{SC_3 + g_{m1}}{S^2 R_s (C_1 C_2 + C_2 C_3 + C_1 C_3) + S[C_2 + C_3 + R_s(g_{m1} C_2 + g_{m2} C_3)] + g_{m1} g_{m2} R_s}$$


For  $Z_{in}$ 

$$I_x = SC_1 V_x + g_{m1} V_x + SC_3 (V_x - V_{out}) - g_{m2} V_{out}$$

$$= \left[ \frac{S^2(C_1 C_2 + C_2 C_3 + C_1 C_3) + S(g_{m1} C_2 + g_{m2} C_3) + g_{m1} g_{m2}}{S(C_2 + C_3)} \right] V_x$$

$$\therefore Z_{in} = \frac{S(C_2 + C_3)}{S^2(C_1 C_2 + C_2 C_3 + C_1 C_3) + S(g_{m1} C_2 + g_{m2} C_3) + g_{m1} g_{m2}}$$

(e)

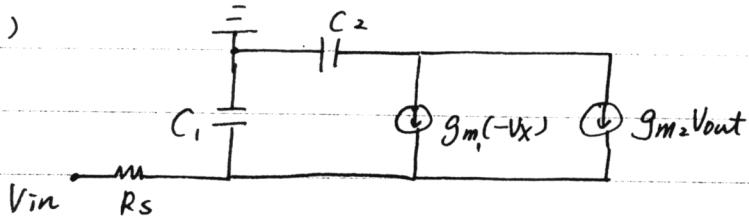

$$C_1 = E_{gs1} + C_{SB1} + C_{dB2} + C_{gd2}$$

$$C_2 = C_{gd1} + C_{SB2} + C_{gs2} + C_{dB1}$$

$$KCL @ Vout \Rightarrow -sC_2 Vout = -g_{m1} V_x + g_{m2} Vout$$

$$\Rightarrow \frac{Vout}{Vx} = \frac{g_{m1}}{sC_2 + g_{m2}}$$

$$KCL @ Vx \Rightarrow \frac{Vin - Vx}{Rs} = sC_1 V_x + g_{m1} V_x - g_{m2} Vout$$

$$\begin{aligned} \Rightarrow \frac{Vin}{Rs} &= \left[ \frac{1}{Rs} + sC_1 + g_{m1} \right] V_x - \frac{g_{m1} g_{m2}}{(sC_2 + g_{m2})} V_x \\ &= \frac{s^2 C_1 C_2 + s \left[ \left( \frac{1}{Rs} + g_{m1} \right) C_2 + g_{m2} C_1 \right]}{sC_2 + g_{m2}} + \frac{g_{m2}}{Rs} \end{aligned}$$

$$\therefore \frac{Vout}{Vin} = \frac{g_{m1}}{s^2 R_s C_1 C_2 + s \left[ (1 + g_{m1} R_s) C_2 + g_{m2} R_s C_1 \right] + g_{m2}}$$


For  $Z_{in}$ 

$$I_x = sC_1 V_x + g_{m1} V_x - g_{m2} Vout$$

$$= \left[ \frac{s^2 C_1 C_2 + s [g_{m1} C_2 + g_{m2} C_1]}{sC_2 + g_{m2}} \right]$$

$$\therefore Z_{in} = \frac{sC_2 + g_{m2}}{s^2 C_1 C_2 + s (g_{m1} C_2 + g_{m2} C_1)}$$

(f)

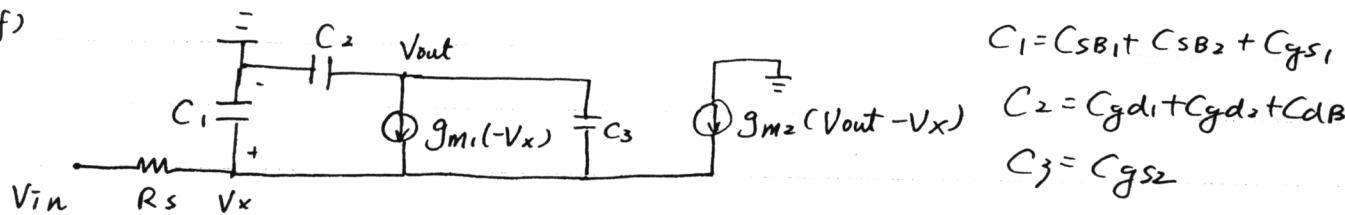

$$C_1 = C_{SB1} + C_{SB2} + C_{gs1},$$

$$C_2 = C_{gd1} + C_{gd2} + C_{dB1},$$

$$C_3 = C_{gs2}$$

$$\text{KCL at } V_{out}: SC_2(-V_{out}) = g_{m1}(-V_x) + SC_3(V_{out} - V_x)$$

$$\Rightarrow \frac{V_{out}}{V_x} = \frac{g_{m1} + SC_3}{S(C_2 + C_3)}$$

$$\text{KCL at } V_x: \frac{V_{in} - V_x}{R_s} + g_{m1}(-V_x) + g_{m2}(V_{out} - V_x) = SC_1 V_x + SC_3(V_x - V_{out})$$

$$\frac{V_{in}}{R_s} = V_x \left( \frac{1}{R_s} + g_{m1} + g_{m2} + SC_1 + SC_3 \right) - \frac{(g_{m2} + SC_3)(g_{m1} + SC_3)}{S(C_2 + C_3)} \cdot V_x$$

$$= \frac{s^2(C_1C_2 + C_2C_3 + C_1C_3) + s \left[ \frac{C_2}{R_s} + \frac{C_3}{R_s} + g_{m1}C_2 + g_{m2}C_2 \right] - g_{m1}g_{m2}}{S(C_2 + C_3)}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} + SC_3}{S^2 R_s (C_1C_2 + C_2C_3 + C_1C_3) + S[C_2 + C_3 + R_s(g_{m1}C_2 + g_{m2}C_2)] - g_{m1}g_{m2}R_s}$$


For  $Z_{in}$ 

$$I_X = g_{m1}V_x + g_{m2}(V_x - V_{out}) + SC_1 V_x + SC_3(V_x - V_{out})$$

$$= \left[ \frac{s^2(C_1C_2 + C_2C_3 + C_1C_3) + s[g_{m1}C_2 + g_{m2}C_2] - g_{m1}g_{m2}}{S(C_2 + C_3)} \right] V_x$$

$$Z_{in} = \frac{V_x}{I_X} = \frac{S(C_2 + C_3)}{S^2(C_1C_2 + C_2C_3 + C_1C_3) + s(g_{m1}C_2 + g_{m2}C_2) - g_{m1}g_{m2}}$$

6.4 (a)

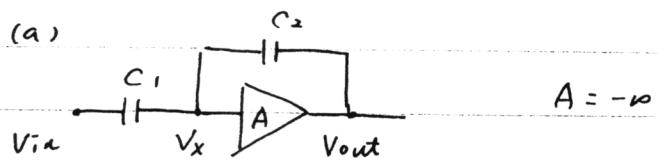

$$A = -\infty$$

(i) At low frequency,  $V_x$  is like virtual ground


$$SC_1 V_{in} = -SC_2 V_{out}$$

$$\frac{V_{out}}{V_{in}} = -\frac{C_1}{C_2}$$

(ii) At high frequency,  $C_1, C_2$  is like a short circuit


$$\frac{V_{out}}{V_{in}} = 1$$

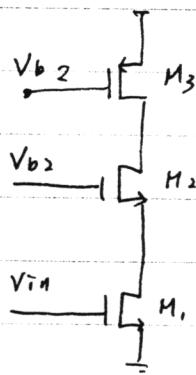(b) At low frequency, the equivalent circuit is shown as




$$Av \approx -g_m r_{o3} \rightarrow \infty, \text{ if } \lambda = 0$$

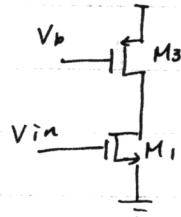(ii) At high frequency, the equivalent circuit




$$Av = -g_{m1} (r_{o1}/r_{o3}) \rightarrow 0 \text{ if } \lambda = 0$$

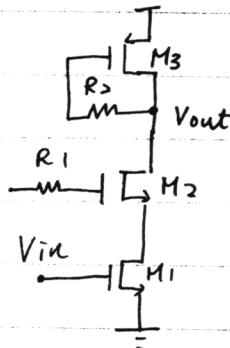(c) (i) At low frequency, the equivalent circuit




$R_1, R_2$  can be ignored

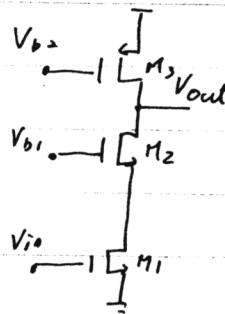

The impedance @  $V_{out}$  =  $\frac{1}{g_{m3}}$

$$Av \approx -g_{m1} \cdot \frac{1}{g_{m3}} = -\frac{g_{m1}}{g_{m3}}$$

(ii) At high frequency.

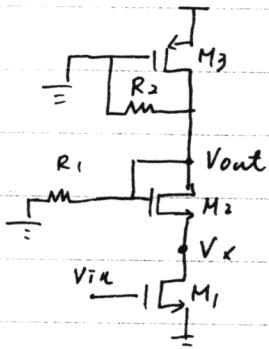

$$\frac{V_x}{V_{in}} = -g_{m1} \cdot \frac{1}{g_{m2}}$$


L the impedance looking into  $V_x$

The impedance @  $V_{out}$  =  $R_1 // R_2$

$$\therefore Av = \left( -g_{m1} \cdot \frac{1}{g_{m2}} \right) \cdot g_{m2} \cdot (R_1 // R_2) = -g_{m1} (R_1 // R_2)$$

X

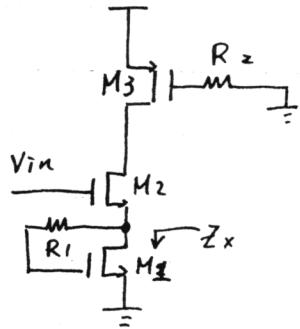
(d) (i) At low frequency, the equivalent circuit is




$$\frac{V_{out}}{V_{in}} = \frac{g_{m2}(r_{o3} / (1 + g_{m2}r_{o2})Z_x)}{1 + g_{m2}Z_x} \approx \frac{g_{m2}(r_{o3} / r_{o2})}{1 + \frac{g_{m2}}{g_{m1}}} \rightarrow \infty \text{ if } \lambda = 0$$

$$Z_x = \frac{1}{g_m}$$

(ii) At high frequency

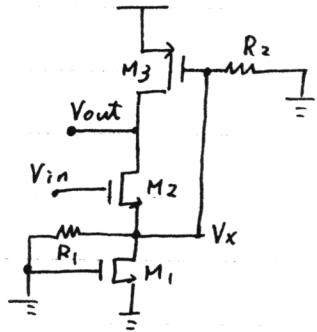

Small-signal model

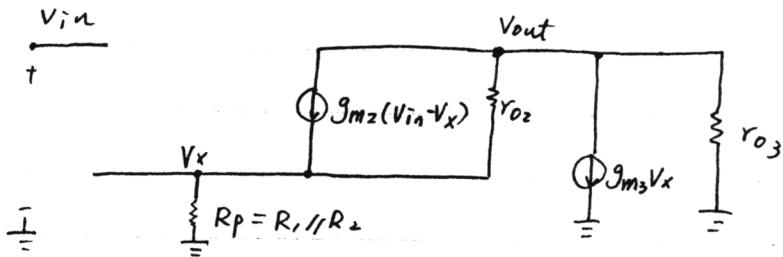

$$KCL @ V_x, V_{out} : \frac{V_x}{R_p} = g_{m2}(V_{in} - V_x) + \frac{V_{out} - V_x}{r_{o2}} = -(g_{m3}V_x + \frac{V_{out}}{r_{o3}})$$


$$\frac{V_x}{R_p} = -(g_{m3}V_x + \frac{V_{out}}{r_{o3}}) \Rightarrow \frac{V_{out}}{V_x} = -r_{o3}(g_{m3} + \frac{1}{R_p})$$

$$g_{m2}(V_{in} - V_x) + \frac{V_{out} - V_x}{r_{o2}} = \frac{V_x}{R_p} \Rightarrow g_{m2}V_{in} = (\frac{1}{R_p} + \frac{1}{r_{o2}} + g_{m2})V_x + \frac{V_{out}}{r_{o2}}$$

$$\Rightarrow g_{m2}V_{in} = \left[ -(\frac{1}{R_p} + \frac{1}{r_{o2}} + g_{m2}) \frac{1}{r_{o3}(g_{m3} + \frac{1}{R_p})} + \frac{1}{r_{o2}} \right] V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-g_{m2}r_{o3}(g_{m3} + \frac{1}{R_p})}{(\frac{1}{R_p} + \frac{1}{r_{o2}} + g_{m2}) - \frac{r_{o3}}{r_{o2}}(g_{m3} + \frac{1}{R_p})} \rightarrow \infty \text{ if } \lambda = 0$$


6.5(a) (i) At low frequency

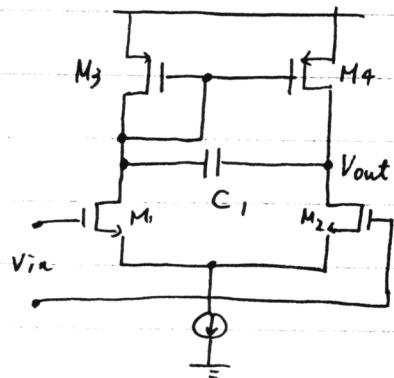

$C_1$  is like an open circuit @ very low frequency


$$\Rightarrow \frac{V_{out}}{V_{in}} = -g_m (R_{o2} // R_{o4}) \rightarrow \infty \text{ if } \lambda = 0$$

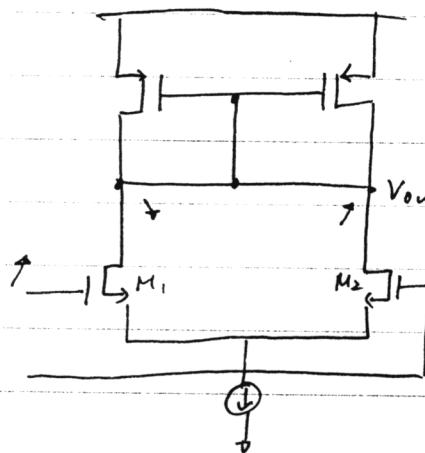(ii) At very high frequency,  $C_1$  is like a short circuit



$$Gain = 0$$

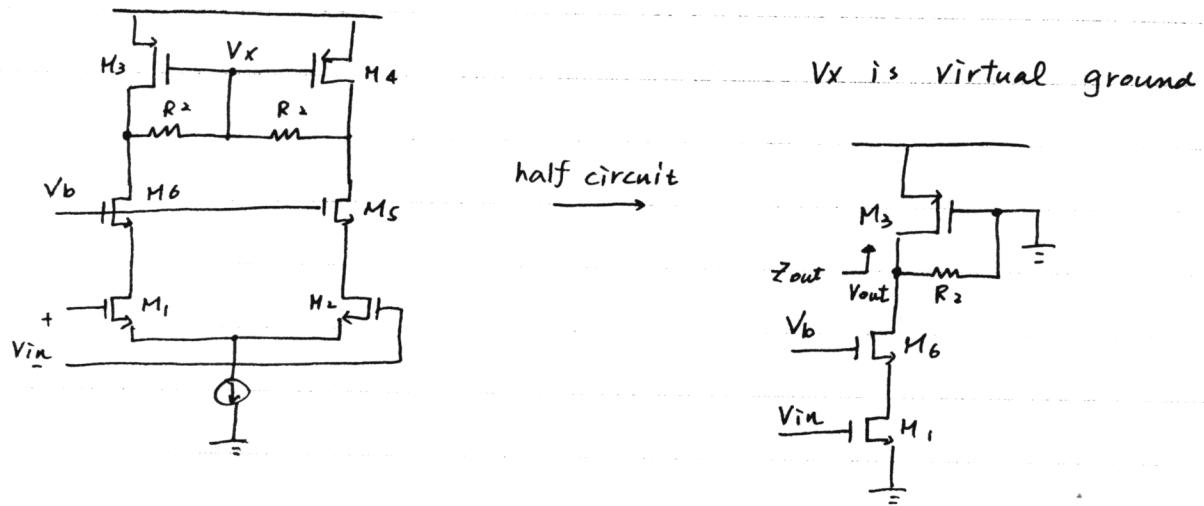
(b) (i) At low frequency, the equivalent circuit is



$$Z_{out} \cong R_3 // R_2 \cong R_2$$

$$AV = -g_{m1} \cdot (R_2 // R_3) \cong -g_{m1} R_2$$


(ii) At high frequency

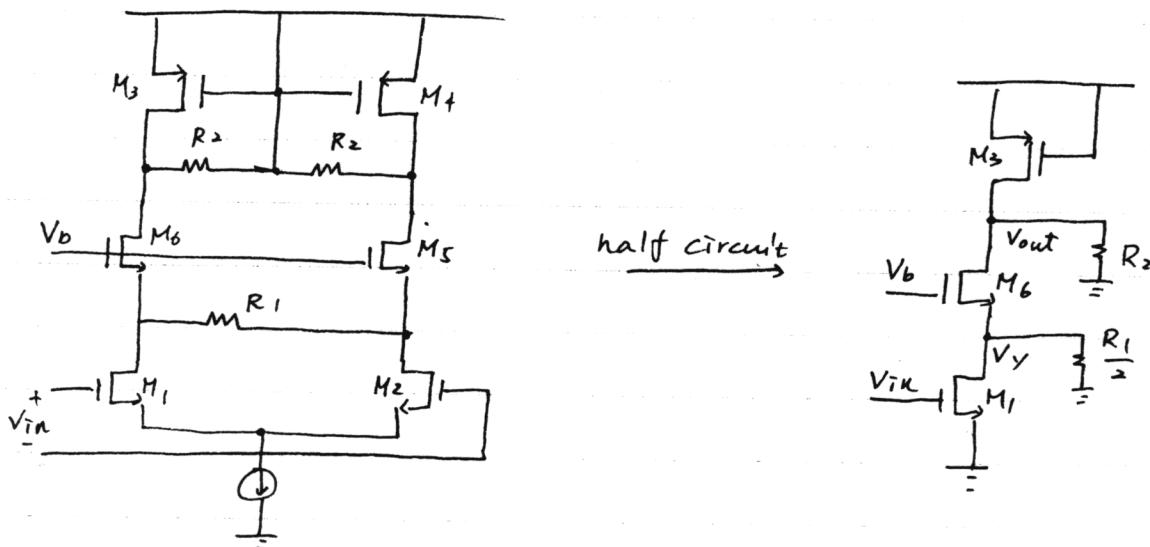

$$\frac{V_y}{V_{in}} = -g_{m1} \left( \frac{1}{g_{m6}} // \frac{R_1}{2} \right), \quad \frac{V_{out}}{V_y} \cong +g_{m6} \cdot R_2$$


$$\frac{V_{out}}{V_{in}} = -\frac{g_{m1} g_{m6} R_1 R_2}{(2 + g_{m6} \cdot R_1)}$$

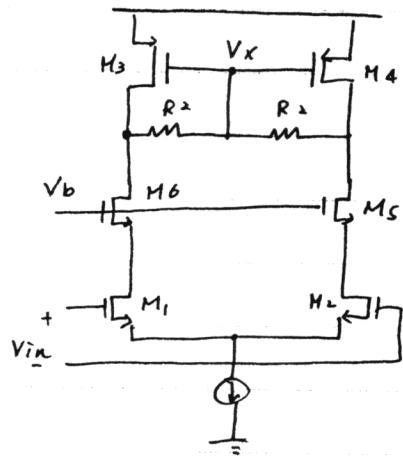(b) (i) At low frequency, the equivalent circuit is



half circuit


$V_x$  is virtual ground

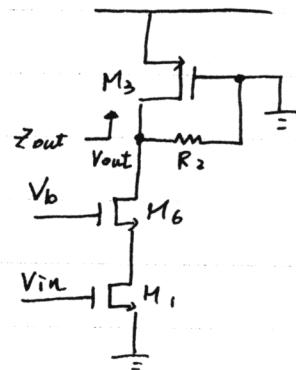


$$Z_{out} \approx r_{o3} // R_2 \approx R_2$$

$$AV = -g_m1 \cdot (R_2 // r_{o3}) \approx -g_m1 R_2 \quad *$$

(ii) At high frequency

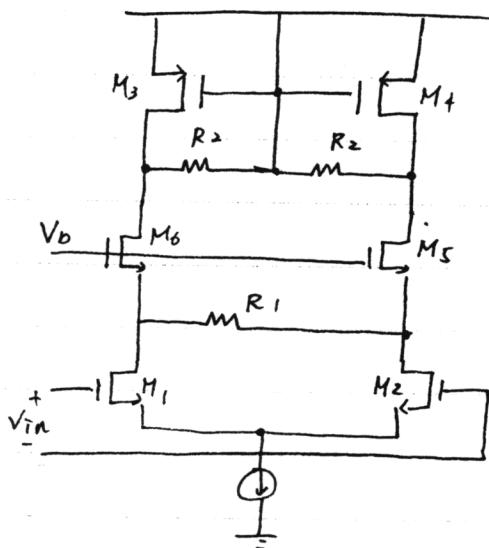


half circuit

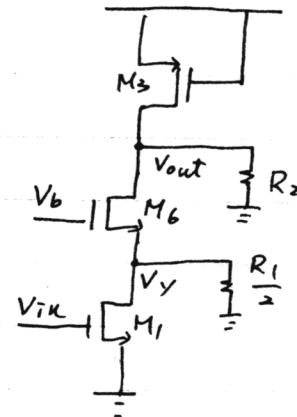


$$\frac{V_y}{V_{in}} = -g_m1 \left( \frac{1}{g_m6} // \frac{R_1}{2} \right), \quad \frac{V_{out}}{V_y} \approx +g_m6 \cdot R_2$$

$$\frac{V_{out}}{V_{in}} = -\frac{g_m1 g_m6 R_1 R_2}{(2 + g_m6 \cdot R_1)} \quad *$$

6.6

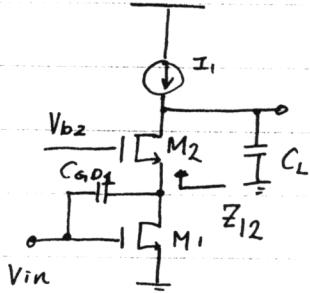

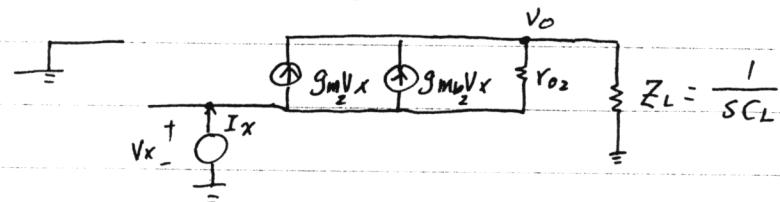The impedance  $Z_{12}$  can be derived from the following small signal model



$$\text{KCL at } V_o : \frac{V_o}{Z_L} + \frac{V_o - V_x}{R_{o2}} = (g_{m2} + g_{mb2})V_x \Rightarrow \left( \frac{1}{Z_L} + \frac{1}{R_{o2}} \right) V_o = (g_{m2} + g_{mb2} + \frac{1}{R_{o2}})V_x$$

$$\Rightarrow V_o = \left( \frac{g_{m2} + g_{mb2} + \frac{1}{R_{o2}}}{1 + \frac{Z_L}{R_{o2}}} \right) V_x$$

$$\Rightarrow I_x = \frac{V_o}{Z_L} = \left[ \frac{g_{m2} + g_{mb2} + \frac{1}{R_{o2}}}{1 + \frac{Z_L}{R_{o2}}} \right] V_x \Rightarrow \frac{V_x}{I_x} = Z_{12} = \frac{1 + \frac{Z_L}{R_{o2}}}{g_{m2} + g_{mb2} + \frac{1}{R_{o2}}}$$

$$\Rightarrow Z_{12} = \frac{R_{o2} + Z_L}{1 + (g_{m2} + g_{mb2})R_{o2}}$$


The Miller multiplication for  $C_{GD1} = 1 + g_{m1}Z_{12}$

$$= 1 + \frac{g_{m1}(R_{o2} + Z_L)}{1 + (g_{m2} + g_{mb2})R_{o2}} \quad \text{--- (1)}$$


If  $C_L$  is relatively large  $\Rightarrow |\frac{1}{sC_L}| \ll R_{o2}$

$$\text{eg (1) can be approximated as } \approx 1 + \frac{g_{m1}R_{o2}}{1 + (g_{m2} + g_{mb2})R_{o2}} \approx 1 + \frac{g_{m1}}{g_{m2} + g_{mb2}}$$


6.7 (a)

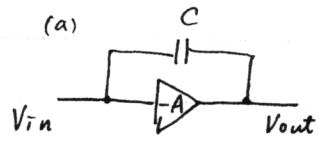Assume the amplifier output resistance  $R_{out}$ 

The small signal model is as follows

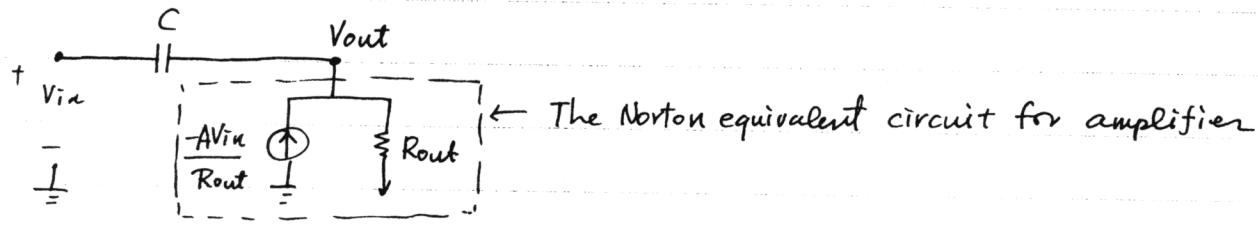

As we can see, the above circuit forms a high pass network

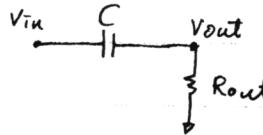Thus, when there is a step  $\Delta V$  at the input, output will follow input, a step  $\Delta V$ , first.Then, it will settle down to  $-AV_{in}$  as the steady state(b) KCL @  $V_{out}$ :

$$-\frac{AV_{in}}{R_{out}} = \frac{V_{out}}{R_{out}} + sC(V_{out} - V_{in})$$

$$\Rightarrow \left(sC - \frac{A}{R_{out}}\right)V_{in} = \left(\frac{1}{R_{out}} + sC\right)V_{out} \Rightarrow \frac{V_{out}}{V_{in}} = \frac{sCR_{out} - A}{1 + sCR_{out}}$$

\*

for the step response,  $X(t) = u(t)$ ,  $t \geq 0 \rightarrow X(s) = \frac{1}{s}$ 


$$Y(s) = \frac{1}{s} \cdot \frac{V_{out}(s)}{V_{in}(s)} = \frac{sCR_{out} - A}{s(1 + sCR_{out})} = \frac{-A}{s} + \frac{(A+1) \cdot R_{out} \cdot C}{1 + sCR_{out}}$$

$$\Rightarrow y(t) = -A u(t) + (A+1) e^{-\frac{t}{R_{out}C}}, t \geq 0$$

For a  $\Delta V$  input step, output =  $-A \cdot \Delta V + (A+1) \cdot \Delta V \cdot e^{-\frac{t}{R_{out}C}}$ 

\*

## 6.8 (a) Small-signal circuit model

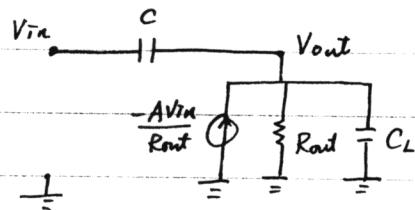

when input has  $\Delta V$  jump,  $V_{out}$  will follow  
and the output jump =  $\left(\frac{C}{C_L + C}\right) \Delta V$

(b) The transfer function  $H(s)$ 

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} : \text{KCL at } V_{out}$$

$$\Rightarrow -\frac{AV_{in}}{R_{out}} = \frac{V_{out}}{R_{out}} + sC(V_{out} - V_{in}) + sC_L V_{out}$$

$$\Rightarrow V_{in} \left( sC - \frac{A}{R_{out}} \right) = V_{out} \left( \frac{1}{R_{out}} + sC + sC_L \right)$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{sCR_{out} - A}{1 + sR_{out}(C + C_L)}$$

## Step response


$$Y(s) = \frac{1}{s} \cdot \frac{sCR_{out} - A}{1 + sR_{out}(C + C_L)} = \frac{-A}{s} + \frac{(A+1)C + AC_L}{s + \frac{1}{R_{out}(C + C_L)}} = \frac{-A}{s} + \frac{\frac{(A+1)C + AC_L}{C + C_L}}{s + \frac{1}{R_{out}(C + C_L)}}$$

$$y(t) = -A u(t) + \frac{(A+1)C + AC_L}{C + C_L} e^{-\frac{t}{R_{out}(C + C_L)}} u(t)$$

For a step  $\Delta V$  @ the input

$$\text{output} = -A \Delta V + \left[ \frac{(A+1)C + A \cdot C_L}{C + C_L} \right] \cdot \Delta V \cdot e^{-\frac{t}{R_{out}(C + C_L)}}$$

6.9.

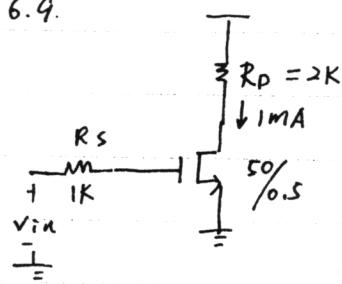

$$\lambda = 0.1$$

$$C_{ox} = \frac{E_{SiO_2}}{t_{ox}} = \frac{3.9 \times 8.85 \times 10^{-14}}{9 \times 10^{-7}} = 3.835 \times 10^{-7}$$

$$\mu_n = 350$$

$$I_D = 10^{-3} = \frac{1}{2} \times 350 \times 3.835 \times 10^{-7} \times \left( \frac{50}{0.5 - 2 \times 0.08} \right) (V_{gs} - V_T)^2 (1 + 0.1 \times V_{ds}) \\ = 67.113 \times 10^{-6} \times \frac{50}{0.34} \times 1.1 \times (V_{in} - 0.7)^2$$

$$\Rightarrow V_{in} = 1.0035$$

$$g_m = \frac{2I_D}{(V_{gs} - V_T)} = 6.59 \times 10^{-3}$$

$$C_{gs} = \frac{2}{3} C_{ox} w L + C_{ov} \cdot w$$

$$= \frac{2}{3} \times 3.835 \times 10^{-7} \times 50 \times (0.5 - 0.08 \times 2) \times 10^{-8} + 3.835 \times 10^{-7} \times 0.08 \times 10^{-4} \times 50 \times 10^{-4} \\ = 53.7 \times 10^{-15}$$

$$C_{gd} = C_{gdo} \cdot w = 0.4 \times 10^{-11} \times 50 \times 10^{-6} = 2 \times 10^{-16}$$

$$C_{dB} = \frac{0.56 \times 10^{-3} \times 75 \times 10^{-12}}{\left(1 + \frac{1}{0.9}\right)^{0.6}} + \frac{0.35 \times 10^{-11} \times 103 \times 10^{-6}}{\left(1 + \frac{1}{0.9}\right)^{0.2}} = 2.714 \times 10^{-14}$$

According to eq (20)

$$\text{Zero} = \frac{g_m}{C_{gd}} = \frac{6.59 \times 10^{-3}}{2 \times 10^{-6}} = 3.3 \times 10^{13} \text{ rad/sec} *$$

pole is the root of  $R_s R_D (C_{gs} C_{gd} + C_{gs} C_{dB} + C_{gd} C_{dB}) s^2$


$$+ [R_s (1 + g_m R_D) C_{gd} + R_s C_{gs} + R_D (C_{gd} + C_{dB})] s + 1 \dots \text{from eq (6.20)}$$

$$\Rightarrow 2.95 \times 10^{-21} s^2 + 1.112 \times 10^{-10} s + 1 = 0$$

$$\omega_{p1} = -14.82 \times 10^9 \text{ rad/sec} *$$

$$\omega_{p2} = 22.88 \times 10^9 \text{ rad/sec} *$$

6.10

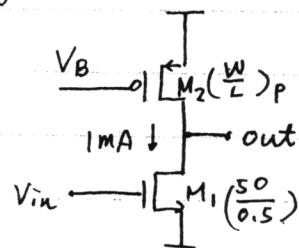

(a) The maximum output level = 2.6 V

 $\rightarrow V_B$  can be as low as  $2.6 - |V_{THP}| = 2.6 - 0.8 = 1.8 V$ 

Let's choose output DC bias @ 1.5 V, such that

 $M_1, M_2$  are both in saturation region

$$\text{Thus, } I_{D1} = 10^{-3} = \frac{1}{2} \times 350 \times 3.835 \times 10^{-7} \times \left( \frac{50}{0.5 - 2 \times 0.08} \right) (V_{in} - 0.7)^2 (1 + 0.1 \times 1.5)$$

$$\Rightarrow V_{in} = 0.997 \approx 1 V$$

$$\text{Also, } I_{D2} = 10^{-3} = \frac{1}{2} \times 100 \times 3.835 \times 10^{-7} \times \left( \frac{W_p}{0.5 - 2 \times 0.09} \right) (3 - 1.8 - 0.8)^2 (1 + 0.2 \times 1.5)$$

$$W_p \approx 80.5 \mu m = 81 \mu m$$

Therefore, we can choose  $(\frac{W}{L})_p = (\frac{81 \mu m}{0.5 \mu m})$ , with gate bias 1.8 Vso that  $M_1, M_2$  are both in saturation region and  $V_{out} \approx 1.5 V$ 

$$V_{out, low} = V_{in} - |V_{THN}| = 0.3 V$$

Thus, the maximum output peak-to-peak swing =  $2.6 - 0.3 = 1.3 V$  \*

(b) This problem is similar to problem 6.9 except

$$R_D \rightarrow (r_o, // r_{on})$$

$$C_{DB} = C_{DB1} + C_{DB2} + C_{gd2}$$

$$\therefore g_{m1} = \frac{2I_D}{V_{gs} - V_t} = 2 \times 10^{-3} / 0.297 = 6.73 \times 10^{-3}$$

$$r_{op} = \frac{1}{(\lambda_p I_D / (1 + \lambda_p V_{ds}))} \approx 6.5 K$$

$$r_{on} = \frac{1}{(\lambda_n I_D / (1 + \lambda_n V_{ds}))} = 11.5 K$$

$$\therefore R_D = r_{op} // r_{on} = 4.1 K$$

$$R_S = 1 K$$

$$C_{gs1} = \frac{2}{3} C_{ox} W_1 L_1 + C_{ox} W_1 \cdot \Delta L = 58.8 \times 10^{-15} F$$

$$C_{gd1} = 2 \times 10^{-16}$$

$$C_{dB1} = \frac{0.56 \times 10^{-3} \times 75 \times 10^{-12}}{\left(1 + \frac{1.5}{0.9}\right)^{0.6}} + \frac{0.35 \times 10^{-11} \times 10^3 \times 10^{-6}}{\left(1 + \frac{1.5}{0.9}\right)^{0.2}} = 23.38 \times 10^{-15} F$$

$$C_{dB2} = \frac{0.94 \times 10^{-3} \times 121.5 \times 10^{-12}}{\left(1 + \frac{1.5}{0.9}\right)^{0.5}} + \frac{0.32 \times 10^{-11} \times 165 \times 10^{-6}}{\left(1 + \frac{1.5}{0.9}\right)^{0.3}} = 70.33 \times 10^{-15} F$$

$$C_{gdz} = 81 \times 0.3 \times 10^{-11} \times 10^{-6} = 0.243 \times 10^{-15} F$$

$$\omega_3 = -\frac{g_m}{C_{gd1}} = -\frac{6.59 \times 10^{-3}}{2 \times 10^{-16}} = -3.3 \times 10^{13} \text{ rad/sec}$$


$\omega_{p1}, \omega_{p2}$  is the root of the equation

$$R_s R_o (C_{gs1} C_{gd1} + C_{gs1} C_{dB} + C_{gd1} C_{dB}) + [R_s (1 + g_m, R_o) C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_{dB})] + 1$$

$$\Rightarrow \omega_{p1} = -2.2 \times 10^9 \text{ rad/sec}$$

$$\omega_{p2} = -17.36 \times 10^9 \text{ rad/sec}$$

6.11

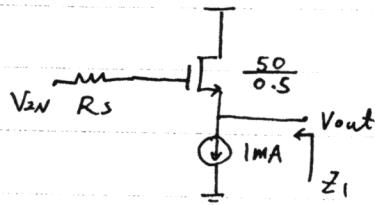Assume  $\delta = 0$ 

$$g_m = \frac{2}{(V_{gs} - V_t)} \\ = \frac{2 \times 10^{-3}}{0.3} = 6.67 \times 10^{-3}$$

From eq (6.49)  $Z_1 = \frac{R_s C_{gs} s + 1}{g_m + C_{gs} s}$

Since  $\frac{1}{g_m} < R_s$

, thus  $Z_1$  is inductive and the equivalent inductance is


$$= \frac{C_{gs}}{g_m} \left( R_s - \frac{1}{g_m} \right)$$

$$C_{gs} = 58 \times 10^{-15} F$$

$$\therefore L = 8.56 \times 10^{-8} H$$

&amp;

6.12 (a)

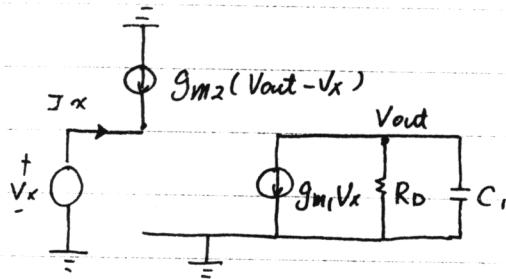


$$V_{\text{out}} = -g_{m1}V_x \left( R_D \parallel \frac{1}{SC_1} \right)$$

$$I_x = -g_{m2}(V_{\text{out}} - V_x) = -g_{m2}V_{\text{out}} + g_{m2}V_x = \left[ g_{m2}g_{m1} \left( R_D \parallel \frac{1}{SC_1} \right) + g_{m2} \right] V_x$$


$$Z_x = \frac{V_x}{I_x} = \frac{1}{g_{m2}g_{m1} \frac{R_D/SC_1}{R_D + 1/SC_1} + g_{m2}} = \frac{1}{g_{m2} \left[ \left( \frac{g_{m1}R_D}{1 + g_{m1}R_D} \right) + 1 \right]} \quad \times$$

$$\text{Thus, } Z_x(S \rightarrow 0) = \frac{1}{g_{m2}(1 + g_{m1}R_D)}$$
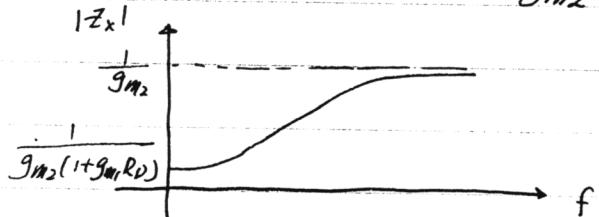
$$Z_x(S \rightarrow \infty) = \frac{1}{g_{m2}}$$




(b)

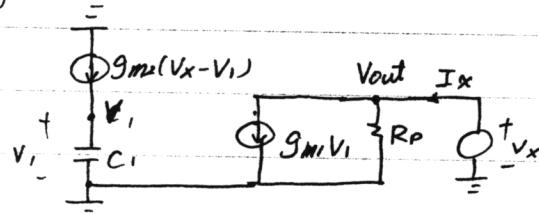

$$\text{KCL at } V_1 : g_{m2}(V_x - V_1) = SC_1 V_1,$$

$$\Rightarrow V_1 = \left( \frac{g_{m2}}{SC_1 + g_{m2}} \right) V_x$$

|Z\_x|

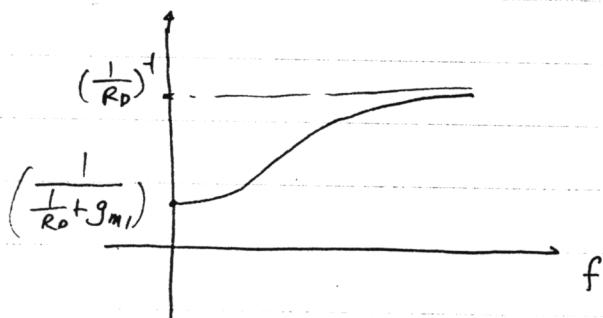


$$\text{KCL at } V_{\text{out}} : I_x = \frac{V_x}{R_D} + g_{m1}V_1,$$


$$= \frac{V_x}{R_D} + \frac{g_{m1}g_{m2}}{SC_1 + g_{m2}} V_x$$

$$\Rightarrow Z_x = \frac{1}{\frac{1}{R_D} + \frac{g_{m1}g_{m2}}{SC_1 + g_{m2}}} \quad \times$$

6.13

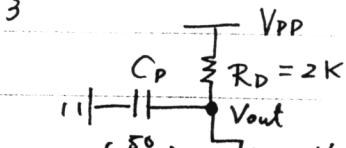

from eq (6.53)

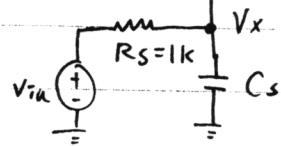

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(g_m + g_{mb}) R_D}{1 + (g_m + g_{mb}) R_s} \cdot \frac{1}{\left(1 + \frac{C_s}{g_m + g_{mb} + R_s^{-1}} \cdot s\right)(1 + R_D C_D s)}$$

Assume  $V_b$  is chosen appropriately such that  $V_x \approx 0$  (no body effect)

$$g_m \approx 6.59 \times 10^{-3}$$

$$g_{mb} = \left[ \frac{\partial}{\partial V_D} \right] g_m = 1.563 \times 10^{-3}$$

$$\left. \begin{aligned} C_s &= C_{SB} + C_{gs} = 42.4 \times 10^{-15} + 58.8 \times 10^{-15} \\ C_D &= C_{DB} = 27.14 \times 10^{-15} \end{aligned} \right\} \text{from problem 9}$$


$$A_v(\text{low frequency}) = \frac{(g_m + g_{mb}) R_D}{1 + (g_m + g_{mb}) R_s} = 1.44$$

$$\omega_{p1} = - \frac{g_m + g_{mb} + R_s^{-1}}{C_s} = - \frac{6.59 \times 10^{-3} + 1.563 \times 10^{-3} + 10^{-3}}{42.4 \times 10^{-15} + 58.8 \times 10^{-15}} = -9.044 \times 10^{10} \text{ rad/s}$$

$$\omega_{p2} = - \frac{1}{R_D C_D} = - \frac{1}{2 \times 10^3 \times 2.714 \times 10^{-14}} = -1.84 \times 10^{10} \text{ rad/s}$$

Compared with the pole locations in problem 9, the poles for common-gate configuration are much larger because there is no Miller-effect for  $g_{fa}$  in this case

6.14

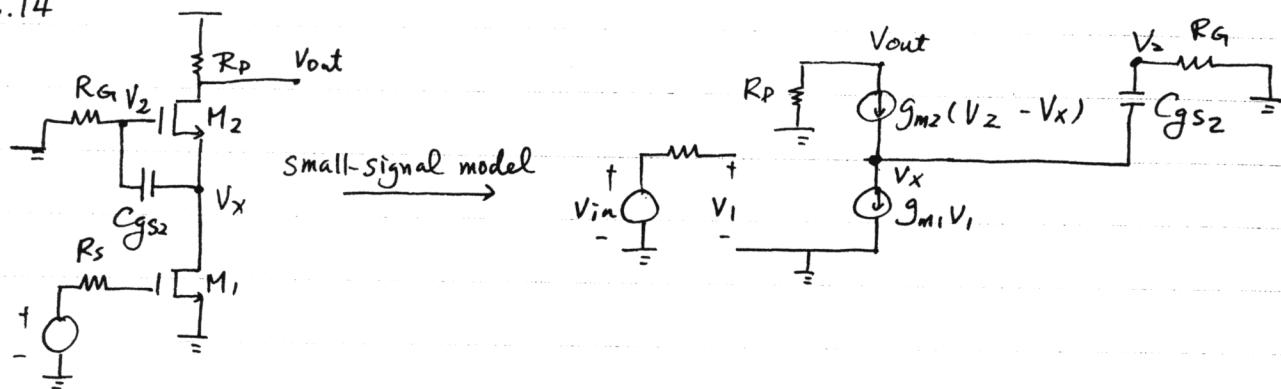

$$\text{KCL at } V_2 : \frac{V_2}{R_g} = sC_{gs2}(V_x - V_2)$$

$$\Rightarrow \frac{V_2}{V_x} = \frac{sC_{gs2}}{\frac{1}{R_g} + sC_{gs2}} = \frac{sR_g C_{gs2}}{1 + sR_g C_{gs2}} - \Phi$$


$$\text{KCL at } V_{\text{out}} : V_{\text{out}} = -g_{m2}(V_2 - V_x)R_p = \left[ \frac{g_{m2}R_p}{1 + sR_g C_{gs2}} \right] V_x - \Theta$$

$$\text{KCL at } V_x : g_{m1}V_1 = g_{m1}V_{\text{in}} = (g_{m2} + sC_{gs2})(V_2 - V_x)$$

$$= \frac{-(g_{m2} + sC_{gs2})}{1 + sR_g C_{gs2}} V_x - \Theta$$

$$\text{From } \Theta, \Theta, \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-g_{m1}g_{m2}R_p}{g_{m2} + sC_{gs2}} *$$

6.15

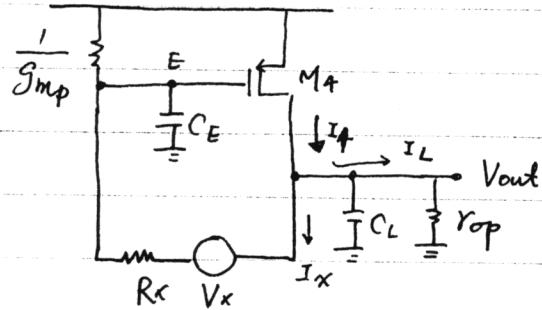

For zero frequency,  $I_L = 0$  &  $I_4 = I_X$


$$I_4 = -g_{mp} V_E$$

$$I_X = V_E (g_{mp} + sC_E)$$

$$\therefore I_4 = I_X \Rightarrow -g_{mp} = g_{mp} + sC_E$$

$$s_3 = \frac{-2g_{mp}}{C_E}$$

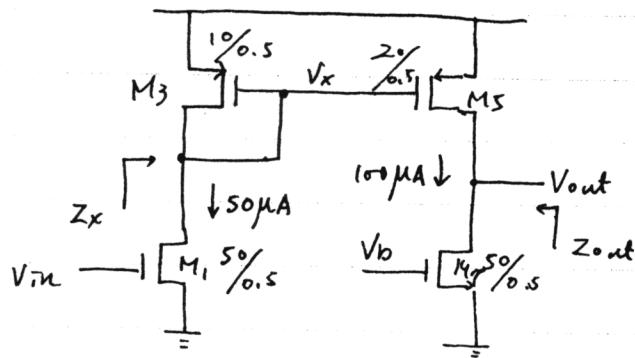6.15 Half circuit can be drawn as follows



Since  $R_s = 0$ , According to (6.20) & (6.76)

$$\frac{V_{out}}{V_{in}}(s) = - \frac{\frac{(C_{gd1} \cdot s - g_{m1}) \cdot \frac{1}{g_{m3}}}{\frac{1}{g_{m3}} (C_{gd1} + C_x) s + 1}}{g_{m5} \cdot (r_{os1}/r_{o2}) \cdot \frac{1}{1 + (r_{os1}/r_{o2}) \cdot C_L \cdot s}}$$

$$Z_x = C_{d87} + C_{gdr7} + C_{db5}$$

$$C_x = C_{gs3} + C_{d81} + C_{gss} + C_{db3} + C_{gas} (1 + g_{m5} (r_{os1}/r_{o2}))$$

$$Z_{out} = (r_{os1}/r_{o2})$$

$$Z_x = \frac{1}{g_{m3}}$$

First of all, let's calculate  $V_x$  operating point

$$I_{d3} = 50 \times 10^{-6} = \frac{1}{2} \times 100 \times 3.835 \times 10^{-7} \times \frac{10}{0.5 - 0.09 \times 2} (3 - V_x - 0.8)^2 (1 + 0.2(3 - V_x))$$

$$V_x \approx 1.94 V$$

For  $V_{in}$  operating point

$$I_{d1} = 50 \times 10^{-6} = \frac{1}{2} \times 50 \times 3.835 \times 10^{-7} \times \frac{50}{0.5 - 0.08 \times 2} (V_{gs1} - 0.7)^2 (1 + 0.1 \cdot 1.94)$$

$$V_{gs1} \approx 0.765 V$$

$$\Rightarrow g_{m1} = \frac{2 I_{d1}}{(V_{gs1} - V_t)} \approx 1.54 \times 10^{-3}$$

$$g_{m3} = \frac{2 I_{d1}}{(3 - 1.94 - 0.8)} \approx 3.73 \times 10^{-4} \Rightarrow g_{m5} = 2 \cdot g_{m3} = 7.46 \times 10^{-4}$$

$$g_{dss} = 2 \times 50 \times 10^{-6} \cdot \lambda / (1 + \lambda \cdot 1.06) = 10^{-4} \cdot 0.2 / 1.212 \approx 1.649 \times 10^{-5}$$

$$g_{ds7} = 10^{-4} \times 0.1 / (1 + 0.196) \approx 8.36 \times 10^{-6}$$

$$r_{05} / r_{07} = 40290$$

$$C_L = C_{BBS} + C_{B7} + C_{gd1} = \left[ \frac{0.94 \times 10^{-3} \times 30 \times 10^{-12}}{\left(1 + \frac{1.06}{0.9}\right)^{0.5}} + \frac{0.32 \times 10^{-11} \times 43 \times 10^{-6}}{\left(1 + \frac{1.06}{0.9}\right)^{0.3}} \right]$$

$$+ \left[ \frac{0.56 \times 10^{-3} \times 75 \times 10^{-12}}{\left(1 + \frac{1.94}{0.9}\right)^{0.6}} + \frac{0.35 \times 10^{-11} \times 103 \times 10^{-6}}{\left(1 + \frac{1.94}{0.9}\right)^{0.2}} \right] + 50 \times 0.4 \times 10^{-17}$$

$$= 19.22 \times 10^{-15} + 21.36 \times 10^{-15} + 2 \times 10^{-16} = 40.78 \times 10^{-15}$$

$$C_{gs3} = \frac{2}{3} \times 3.835 \times 10^{-7} \times 10 \times 0.32 + 3.835 \times 10^{-7} \times 10 \times 0.09 = 11.633 \times 10^{-15}$$

$$C_{dB1} \approx C_{dB7} \approx 21.36 \times 10^{-15}$$

$$C_{gs5} = 2 \cdot C_{gs3} = 23.266 \times 10^{-15}$$

$$C_{dB3} = \frac{1}{2} \cdot C_{BBS} = 9.61 \times 10^{-15}$$

$$C_{gds} = 6.3 \times 10^{-11} \times 20 \times 10^{-6} = 6 \times 10^{-17}$$


$$C_x = [11.633 + 21.36 + 23.266 + 9.61 + 0.06 (1 + g_{MS} \cdot (r_{05} / r_{07}))] \times 10^{-15} = 67.732 \times 10^{-15}$$

$$\therefore \omega_3 = \frac{g_{m1}}{C_{gd1}} = 7.7 \times 10^{12} \text{ rad/sec}$$


$$\omega_{p1} = -\frac{1}{C_L \cdot (r_{05} / r_{07})} = -\frac{1}{40290 \times 40.78 \times 10^{-15}} = 6.08 \times 10^8 \text{ rad/sec}$$

$$\omega_{p2} = -\frac{g_{m3}}{(C_{gd1} + C_x)} = -\frac{-3.73 \times 10^{-4}}{2 \times 10^{-16} + 67.732 \times 10^{-15}} = 5.5 \times 10^9 \text{ rad/sec}$$

6.17 (a)

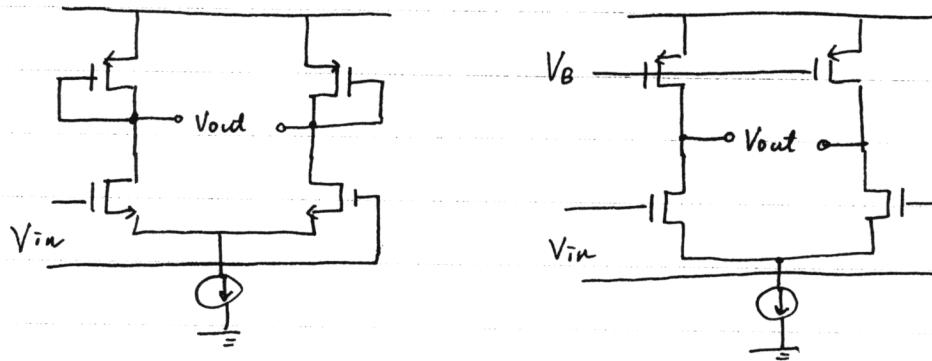

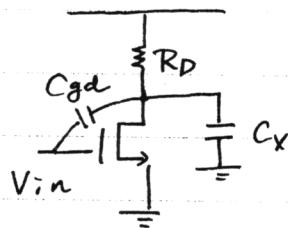Both of these two differential pair can be simplified as common-source amplifier with different load resistance and capacitance



Since  $R_s = 0$ , equation (6.20) can be simplified as

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{(C_{gd}s - g_m)R_D}{s[R_D(C_{gd} + C_x)] + 1}$$


where  $\begin{cases} R_D = \frac{1}{g_{mp}} \text{ for diode connected load} \\ C_x = C_{dBN} + C_{dop} + C_{gsp} \end{cases}$

$$\begin{cases} R_D \approx (r_{on}'' / r_{op}) \text{ for current mirror load} \\ C_x = C_{dBN} + C_{dop} + C_{gdp} \end{cases}$$


Although there is right-half-plane zero, however this zero is much larger than the dominant pole.

Therefore, the maximum phase shift it can achieve is  $\sim 90^\circ$  before the gain is down to unity.


(b)

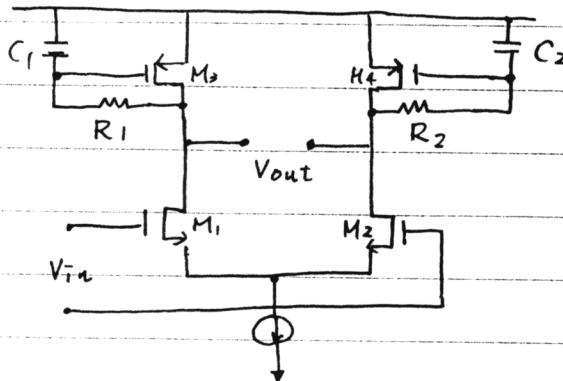

half-circuit

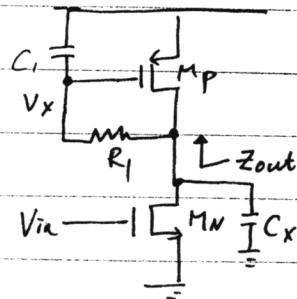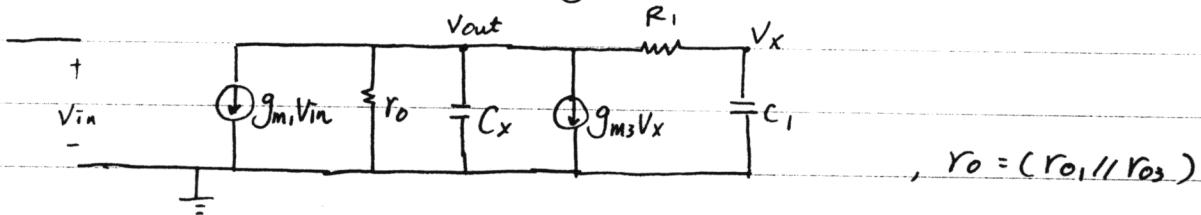(i) At low frequency,  $C_1$  is open circuit. $M_p$  is like a diode-connected device  $\rightarrow Z_{out} \sim \frac{1}{g_{mp}}$ (ii) At high frequency,  $C_1$  is short circuit. $M_p$  is like a current source device  $\rightarrow Z_{out} \sim (r_{on} // r_{op})$ Since  $(r_{on} // r_{op}) \gg \frac{1}{g_{mp}}$ ,  $Z_{out}$  exhibits an inductive behavior

For transfer function, small-signal model



KCL @  $V_x$  :  $\frac{V_{out} - V_x}{R_1} = SC_1 V_x \Rightarrow V_{out} = (1 + s R_1 C_1) V_x$

$$\Rightarrow V_x = \frac{V_{out}}{1 + s R_1 C_1}$$

KCL @  $V_{out}$  :  $-g_{m1} V_{in} = V_{out} \left( \frac{1}{R_o} + s C_x \right) + \frac{1}{R_1} (V_{out} - V_x) + g_{m3} V_x$

$$= V_{out} \left( \frac{1}{R_o} + s C_x + \frac{1}{R_1} \right) + \left( g_{m3} - \frac{1}{R_1} \right) \cdot \frac{V_{out}}{1 + s R_1 C_1}$$

$$-g_m V_{in} = V_{out} \left( \frac{\frac{1}{R_o} + \frac{1}{R_1} + SC_x + \left( \frac{R_1}{R_o} + 1 \right) SC_1 + S^2 R_1 C_1 C_x + g_m z - \frac{1}{R_1}}{1 + SR_1 C_1} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m (1 + SR_1 C_1)}{S^2 R_1 C_1 C_x + S(C_1 + \frac{R_1 C_1}{R_o} + C_x) + (g_m z + \frac{1}{R_o})}$$

From the above transfer function,

$$\omega_z = -\frac{1}{R_1 C_1}$$

$$\text{the sum of two poles} = -\frac{1}{R_1 C_1 C_x} (C_1 + \frac{R_1 C_1}{R_o} + C_x) = -\frac{1}{R_1 C_1} \left( 1 + \frac{C_1}{C_x} \left( 1 + \frac{R_1}{R_o} \right) \right)$$

usually  $C_1 > C_x$ ,  $C_1$  at least  $= C_{gs3}$

Thus, the sum of two poles  $> -\frac{2}{R_1 C_1}$ , which means that at least one of the poles are larger than zero  $\Rightarrow$  It's quite impossible to produce  $135^\circ$  phase shift

Thus, this circuit still can't produce  $135^\circ$  phase shift.

However, it's more likely for it to generate  $90^\circ$  phase shift

@ unity-gain frequency.

8.1

$$V_{in} = I_{in} (Z_{in} + G_{22}) + G_{21} V_{out}$$

$$\frac{V_{out} - A_o I_{in} Z_{in}}{Z_{out}} = -G_{11} V_{out} - G_{12} I_{in}$$

$$\Rightarrow I_{in} \left( \frac{A_o Z_{in}}{Z_{out}} - G_{12} \right) = V_{out} \left( \frac{1}{Z_{out}} + G_{11} \right)$$



$$V_{in} = V_{out} \left[ G_{21} + \frac{(Z_{in} + G_{22})(\frac{1}{Z_{out}} + G_{11})}{\frac{A_o Z_{in}}{Z_{out}} - G_{12}} \right]$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{A_o Z_{in} - G_{12} Z_{out}}{Z_{out}}}{G_{21} \left( \frac{A_o Z_{in}}{Z_{out}} - G_{12} \right) + (Z_{in} + G_{22})(\frac{1}{Z_{out}} + G_{11})}$$

$$\begin{aligned} A_{v_{open}} &= \frac{1}{Z_{out}} (A_o Z_{in} - G_{12} Z_{out}) \cdot \frac{1}{Z_{in} + G_{22}} \cdot \frac{1}{\frac{1}{Z_{out}} + G_{11}} \\ &= \frac{G_{11}^{-1}}{G_{11}^{-1} + Z_{out}} \cdot \frac{1}{Z_{in} + G_{22}} (A_o Z_{in} - G_{12} Z_{out}) \end{aligned}$$

if  $G_{12} \ll A_o Z_{in}/Z_{out}$  then the second term can be neglected

8.2

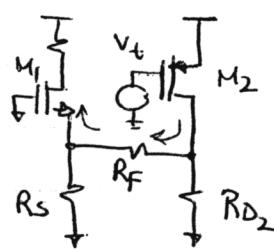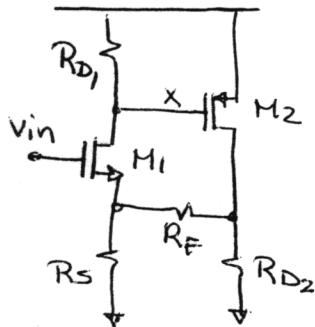

The current through  $R_S$ :

$$- \frac{g_m2 \cdot V_t R_{D2}}{R_{D2} + R_F + (R_S \parallel \frac{1}{g_m2})}$$

The current through  $M_1$ :

$$- \frac{g_m2 V_t R_{D2}}{R_{D2} + R_F + (R_S \parallel \frac{1}{g_m2})} \cdot \frac{R_S}{R_S + \frac{1}{g_m2}}$$


This current is multiplied by  $R_{D1}$  to produce  $V_f$

loop gain:  $\frac{g_{m_2} R_{D_2} R_S R_{D_1}}{(R_{D_2} + R_F)(R_S + \frac{1}{g_{m_2}}) + R_S \cdot \frac{1}{g_{m_2}}}$

This result is accurate, whereas  $A_{v1} A_{v\text{open}}$  is approximate because it neglects the signal propagating thru the feedback network from the input to the output.

8.3

Voltage-current

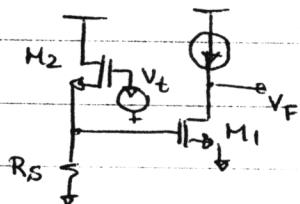

loop gain:  $\frac{R_S}{R_S + \frac{1}{g_{m_2}}} \cdot g_{m_1} r_{o_1}$

$$\frac{V_{in}}{R_S} \times \left( R_S \parallel \frac{1}{g_{m_2}} \right) g_{m_1} r_{o_1} = V$$


$$\Rightarrow \frac{\frac{V_{out}}{V_{in}}}{\left| \frac{V_{in}}{R_S} \right|_{\text{open}}} = g_{m_1} r_{o_1} \left( R_S \parallel \frac{1}{g_{m_2}} \right)$$

$$Z_{in \text{ open}} = \frac{1}{g_{m_2}} \\ Z_{out \text{ open}} = r_{o_1}$$

$$\frac{\frac{V_{out}}{V_{in}}}{\left| \frac{V_{in}}{R_S} \right|_{closed}} = \frac{1}{g_{m_2}} \Rightarrow A_{v \text{ closed}} = \frac{1}{g_{m_2} R_S}$$

$$Z_{in \text{ closed}} = 0 \\ r_{o_1} \rightarrow \infty$$
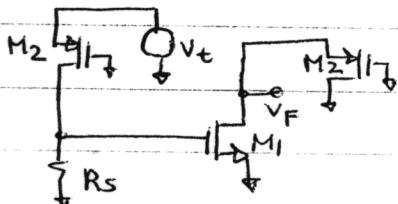
$$Z_{out \text{ closed}} = \frac{R_S + \frac{1}{g_{m_2}}}{g_{m_1} R_S} = \frac{1}{g_{m_1}} + \frac{1}{g_{m_1} g_{m_2} R_S}$$



$$\frac{V_F}{V_t} = g_{m_2} R_S \frac{g_{m_1}}{g_{m_2}} = g_{m_1} R_S$$

$$Z_{in \text{ open}} = r_{o_2}$$


$$Z_{out \text{ open}} = \frac{1}{g_{m_2}}$$

$$\frac{\frac{V_{out}}{V_{in}}}{\left| \frac{V_{in}}{R_S} \right|_{\text{open}}} = R_S \cdot \frac{g_{m_1}}{g_{m_2}}$$

$$A_{v \text{ closed}} = \frac{g_{m_1}/g_{m_2}}{1 + g_{m_1} R_S}$$

$$Z_{in \text{ closed}} = \infty$$
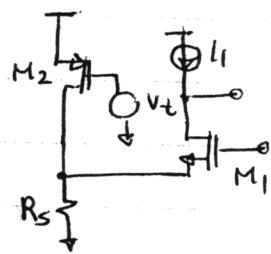
$$Z_{out \text{ closed}} = \frac{1}{g_{m_2}(1 + g_{m_1} R_S)}$$



$$R_S g_{m_2} V_t \frac{r_{o_1}}{R_S + \frac{1}{g_{m_1}}} = V_F \Rightarrow \text{loop gain: } \frac{R_S g_{m_2} r_{o_1}}{R_S + \frac{1}{g_{m_1}}}$$

$$R_{out\ open} = g_{m_1} r_{o_1} R_S + r_{o_1} + R_S \approx g_{m_1} r_{o_1} R_S$$


$$R_{in\ open} = \frac{1}{g_{m_1}}$$

$$\left. \frac{V_{out}}{V_{in}} \right|_{open} = \frac{r_{o_1}}{R_S + \frac{1}{g_{m_1}}}$$

$$r_{o_1} \rightarrow \infty \quad A_V = \frac{1}{R_S g_{m_2}}$$

$$R_{in} = 0$$
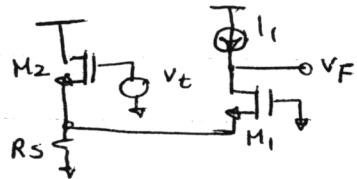
$$R_{out} = \frac{g_{m_1} (R_S + \frac{1}{g_{m_1}})}{g_{m_2}}$$



$$\text{loop gain: } V_t \cdot \frac{R_S \parallel \frac{1}{g_{m_1}}}{\frac{1}{g_{m_2}} + R_S \parallel \frac{1}{g_{m_1}}} \cdot g_{m_1} r_{o_1} = V_F$$

$$R_{in\ open} = \frac{1}{g_{m_1} + g_{m_2}}$$

$$R_{out\ open} = g_{m_1} r_{o_1} (R_S \parallel \frac{1}{g_{m_2}})$$


$$A_V \Rightarrow \frac{V_{in}}{R_S} (R_S \parallel \frac{1}{g_{m_2}}) \times g_{m_1} r_{o_1} = V_{out} \Rightarrow A_{v\ open} = \frac{g_{m_1} r_{o_1} (R_S \parallel \frac{1}{g_{m_2}})}{R_S}$$

$$r_o \rightarrow \infty$$

$$A_{v\ closed} = \frac{(R_S \parallel \frac{1}{g_{m_2}})(\frac{1}{g_{m_2}} + R_S \parallel \frac{1}{g_{m_1}})}{R_S (R_S \parallel \frac{1}{g_{m_1}})}$$


$$R_{in\ closed} = 0$$
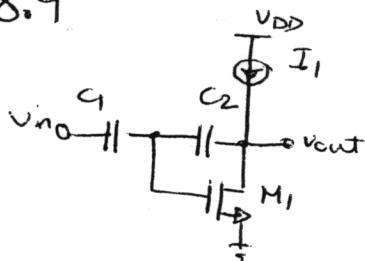
$$R_{out\ closed} = \frac{(R_S \parallel \frac{1}{g_{m_2}})(\frac{1}{g_{m_2}} + R_S \parallel \frac{1}{g_{m_1}})}{R_S \parallel \frac{1}{g_{m_1}}}$$



$$R_{in} = \frac{1}{C_1 \delta} + \frac{1}{g_m}$$

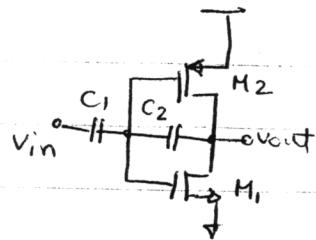
$$R_{out} = \frac{r_o}{1 + \frac{C_2}{C_1 + C_2} g_{m_1} r_o} = \frac{C_1 + C_2}{g_{m_1} C_2}$$



using the results in part (a)

$$R_{in} = \frac{1}{g_s s} + \frac{1}{g_{m1} + g_{m2}}$$
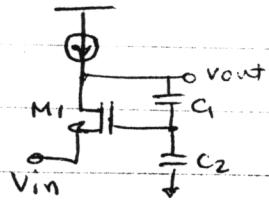
$$R_{out} = \frac{C_1 + C_2}{(g_{m1} + g_{m2}) C_2}$$



$$\text{loop gain} = g_{m1} r_o \frac{C_1}{C_1 + C_2}$$

$$R_{in\ closed} = \frac{1}{g_{m1}} + \frac{1}{C_2 s}$$

$$R_{out\ closed} = \frac{r_o}{1 + g_{m1} r_o \frac{C_1}{C_1 + C_2}} = \frac{C_1 + C_2}{g_{m1} C_1}$$

8.5

$$-\frac{1}{\left(1 + \frac{1}{g_{m_1} r_o}\right) \frac{C_2}{C_1} + \frac{1}{g_{m_1} r_o}} = -0.95 \frac{C_1}{C_2} \Rightarrow \frac{C_1}{C_2} = 1.63$$

$g_{m_1} r_o = 50$

Open loop output impedance:  $r_o$ 

$$\text{loop gain: } \frac{C_2}{C_1 + C_2} g_{m_1} r_o$$

$$\text{closed loop } R_{out} = \frac{r_o}{1 + \frac{C_2}{C_1 + C_2} g_{m_1} r_o} = 0.49 r_o$$

8.6

$$\begin{aligned} R_{in, \text{closed}} &= \frac{1}{g_{m_1}} \cdot \frac{1}{1 + g_{m_2} R_D \frac{C_1}{C_1 + C_2}} & I_1 = I_2 \Rightarrow g_{m_2} = \sqrt{2} g_{m_1} \\ &= \frac{1}{g_{m_1}} \cdot \frac{1}{1 + 1000\sqrt{2} g_{m_1}} = 50 \Rightarrow g_{m_1} = 3.42 \text{ mV} \end{aligned}$$

$$g_m = \sqrt{2 \mu_n C_o \frac{W}{L} I_D} \Rightarrow I_D = \frac{(3.42 \times 10^{-3})^2}{2 \times 1.342 \times 10^{-4} \times 100} = 435 \text{ mA}$$

8.7

$$\frac{V_x}{I_x} = \frac{R_D}{1 + \frac{g_{m_2} R_S (g_{m_1} + g_{mb_1}) R_D}{(g_{m_1} + g_{mb_1}) R_S + 1} \cdot \frac{C_1}{C_1 + C_2}} \xrightarrow{R_D \rightarrow \infty} = \frac{(g_{m_1} + g_{mb_1}) R_S + 1}{g_{m_2} R_S (g_{m_1} + g_{mb_1})} \cdot \frac{C_1 + C_2}{C_1}$$

$$\text{if } (g_{m_1} + g_{mb_1}) R_S \gg 1 \Rightarrow \frac{V_x}{I_x} = \frac{1}{g_{m_2}} \cdot \frac{C_1 + C_2}{C_1}$$

8.8

If  $f_{-3dB}$  of each stage is  $\omega_0$ 

$$\left| \frac{1}{\left(1 + \frac{s}{\omega_0}\right)^n} \right| = \frac{1}{\sqrt{2}} \Rightarrow \left(1 + \left(\frac{\omega}{\omega_0}\right)^2\right)^n = 2$$

if we indicate the Gain  $f_{-3dB}$  as  $K = \text{const}$

$$\Rightarrow \left(\frac{K}{\omega_0}\right)^n = 500$$

$$\Rightarrow \frac{\ln 2}{\ln(1 + (\frac{\omega}{\omega_0})^2)} = \frac{\ln 500}{\ln(\frac{K}{\omega_0})} \Rightarrow 1 + (\frac{\omega}{\omega_0})^2 = \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}}$$


$$\Rightarrow \omega = \omega_0 \sqrt{\left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1}$$

$$\frac{d\omega}{d\omega_0} = 0 \Rightarrow \sqrt{\left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1} + \frac{\omega_0}{2} \cdot \frac{1}{\sqrt{\left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1}} \cdot \left(-\frac{\ln 2}{\ln 500} \cdot \frac{1}{\omega_0} \cdot \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}}\right)$$

$$\Rightarrow \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} - 1 - \frac{1}{2} \frac{\ln 2}{\ln 500} \left(\frac{K}{\omega_0}\right)^{\frac{\ln 2}{\ln 500}} = 0 \Rightarrow \frac{K}{\omega_0} = 1.67$$

$$\Rightarrow \text{Gain per stage} = 1.67 \quad \text{Stage BW} = 598 \text{ MHz}$$

8.9

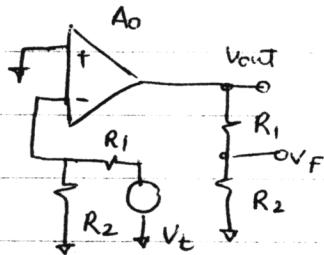

$$A_{v\text{open}} = A_o \frac{R_2}{R_1 + R_2 + R_o}$$

Loop gain:

$$\left(\frac{R_2}{R_1 + R_2}\right) A_o \left(\frac{R_2}{R_o + R_1 + R_2}\right)$$

$$R_{out\text{ open}} = R_o \parallel (R_1 + R_2)$$

$$A_{v\text{closed}} = \frac{A_o \frac{R_2}{R_o + R_1 + R_2}}{1 + \left(\frac{R_2}{R_1 + R_2}\right) A_o \left(\frac{R_2}{R_o + R_1 + R_2}\right)}$$

$$R_{out\text{ closed}} = \frac{R_o \parallel (R_1 + R_2)}{1 + \left(\frac{R_2}{R_1 + R_2}\right) A_o \left(\frac{R_2}{R_o + R_1 + R_2}\right)}$$

B.10


$$\frac{1 + \frac{C_2}{C_1}}{(1 + \frac{C_2}{C_1}) \frac{1}{g_m (r_{o2} \parallel r_{o4})} + 1} = 0.95 \left(1 + \frac{C_2}{C_1}\right)$$

$\uparrow$   
5% gain error

$$g_m (r_{o2} \parallel r_{o4}) \approx 24.4$$

$$\Rightarrow 1 + \frac{C_2}{C_1} \leq 1.28$$

B.11

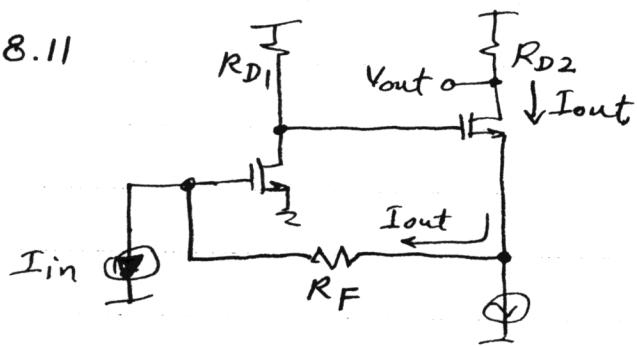

$I_{out}$  fully flows through  $R_F \Rightarrow I_{out} = I_{in}$   
and  $V_{out} = I_{out} \cdot R_{D2}$ .

Thus, the transimpedance is equal to  $R_{D2}$ .  
(continued on next page)

8.11 (c'n'td)

$$-(\underbrace{I_{out} R_s + V_{nRS} + V_{nRF} + V_{n1}}_{V_Y} \underbrace{\partial m_1 R_D}_{+V_{nRD} + V_{n2}}) = V_X$$

$$(V_X - V_Y) \partial m_2 = I_{out}$$

$$\Rightarrow g_m \left[ (I_{out} R_s + V_{nRS} + V_{nRF} + V_{n1}) (-\partial m_1 R_D) + V_{nRD} + V_{n2} - (I_{out} R_s + V_{nRS}) \right] = I_{out}$$

$$\Rightarrow I_{out} \left[ 1 + \partial m_2 R_s (\partial m_1 R_D + 1) \right] = \partial m_2 \left[ (-\partial m_1 R_D - 1) V_{nRS} - \partial m_1 R_D V_{nRF} \right.$$

$$\left. - \partial m_1 R_D V_{n1} + V_{nRD} + V_{n2} \right]$$

$$\Rightarrow I_{out} = \frac{\partial m_2 \left[ -(1 + \partial m_1 R_D) V_{nRS} - \partial m_1 R_D V_{nRF} - \partial m_1 R_D V_{n1} + V_{nRD} + V_{n2} \right]}{1 + \partial m_2 R_s (1 + \partial m_1 R_D)}$$


If we apply a current of  $I_{in}$  to the input, the resulting output current is obtained as :

$$\left\{ \underbrace{[(I_{in} + I_{out}) R_s + I_{in} R_F] (-\partial m_1 R_D)}_{V_X} - \underbrace{(I_{in} + I_{out}) R_s}_{V_Y} \right\} \partial m_2 = I_{out}$$


$$\frac{I_{out}}{I_{in}} = \frac{[-\partial m_1 R_D (R_s + R_F) - R_s] \partial m_2}{1 + \partial m_2 R_s (1 + \partial m_1 R_D)}$$

Dividing the output noise current by the gain yields the input-referred noise current:
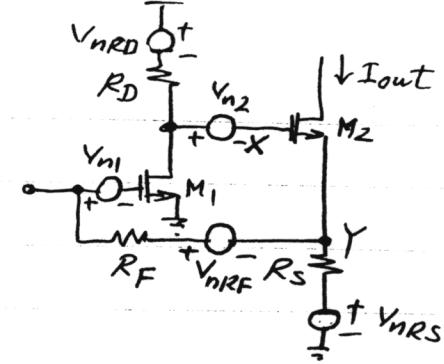
$$I_{n,in} = \frac{-(1 + \partial m_1 R_D) V_{nRS} - \partial m_1 R_D V_{nRF} - \partial m_1 R_D V_{n1} + V_{nRD} + V_{n2}}{-\partial m_1 R_D (R_s + R_F) - R_s}$$



8.12

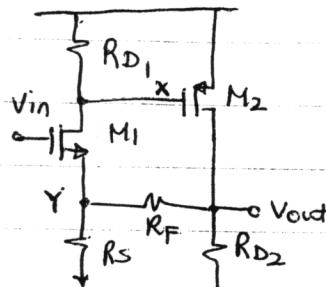

$$I_{D2} = 1 \text{ mA} \Rightarrow \frac{1}{2} M_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_x - |V_{TP}|)^2 = 1 \text{ mA}$$

$$\Rightarrow V_x = 1.478$$

$$I_{D1} = 761 \mu\text{A}$$

$$\begin{cases} \frac{V_y}{2k} + \frac{V_y - V_{out}}{2k} = 761 \mu\text{A} \Rightarrow V_{out} = 1.841 \\ \frac{V_{out}}{2k} + \frac{V_{out} - V_y}{2k} = 1 \text{ mA} \Rightarrow V_y = 1.681 \end{cases}$$

$$I_{D1} = 0.761 \text{ mA} \Rightarrow \frac{1}{2} \times 1.342 \times 10^{-4} \times 100 (V_{in} - V_y - V_{TN})^2 = 0.761 \text{ mA}$$

$$V_{in} - V_y = 1.037 \Rightarrow V_{in} = 2.717 \text{ V}$$

$$G_{21} = 0.5$$

$$\begin{cases} g_m = \frac{2 \times 0.761 \text{ mA}}{1.037 - 0.7} = 4.52 \text{ mV} \\ g_m = \frac{2 \times 1 \text{ mA}}{1.522 - 0.8} = 2.77 \text{ mV} \end{cases} \quad A_{v_{open}} = \frac{-2k}{1k + \frac{1}{4.52 \text{ mV}}} \left[ -2.77 \left[ 2k \parallel 4k \right] \right] = 6.048$$

$$A_{v_{closed}} = \frac{6.048}{1 + 3.024} = 1.503$$

8.13

problem 8.9


$$R_{out} = \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2 + \frac{R_2^2}{R_1 + R_2} \cdot \frac{A_o}{1 + \frac{S}{\omega_0}}}$$

Zero:  $\omega_0$ 

$$\text{pole: } \omega_0 + \frac{A_o R_2^2}{(R_1 + R_2)(R_o + R_1 + R_2)} \omega_0$$


$$\text{DC value: } \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2 + A_o R_2^2 / R_1 + R_2}$$
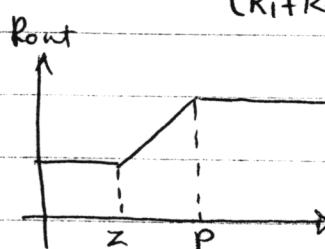
$$\text{final value: } R_o \parallel (R_1 + R_2)$$



The output impedance is less reduced, as the loop gain gets smaller.

8.12

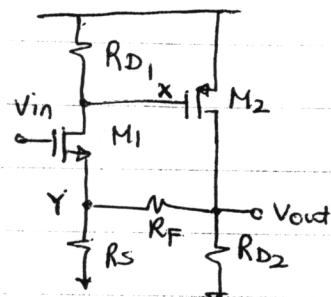

$$I_{D2} = 1 \text{ mA} \Rightarrow \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_x - |V_{TP}|)^2 = 1 \text{ mA}$$

$$\Rightarrow V_x = 1.478$$

$$I_{D1} = 761 \text{ }\mu\text{A}$$

$$\begin{cases} \frac{V_y}{2k} + \frac{V_y - V_{out}}{2k} = 761 \text{ mA} \Rightarrow V_{out} = 1.841 \\ \frac{V_{out}}{2k} + \frac{V_{out} - V_y}{2k} = 1 \text{ mA} \Rightarrow V_y = 1.681 \end{cases}$$

$$I_{D1} = 0.761 \text{ mA} \Rightarrow \frac{1}{2} \times 1.342 \times 10^{-4} \times 100 (V_{in} - V_y - V_{Tn})^2 = 0.761 \text{ mA}$$

$$V_{in} - V_y = 1.037 \Rightarrow V_{in} = 2.717 \text{ V}$$

$$G_{21} = 0.5$$

$$\begin{cases} g_{m1} = \frac{2 \times 0.761 \text{ mA}}{1.037 - 0.7} = 4.52 \text{ mV} \\ g_{m2} = \frac{2 \times 1 \text{ mA}}{1.522 - 0.8} = 2.77 \text{ mV} \end{cases} \quad A_{v_{open}} = \frac{-2k}{1k + \frac{1}{4.52 \text{ mV}}} \left[ -2.77 \left[ 2k \parallel 4k \right] \right] = 6.048$$

$$A_{v_{closed}} = \frac{6.048}{1 + 3.024} = 1.503$$

8.13

problem 8.9


$$R_{out} = \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2 + \frac{R_2^2}{R_1 + R_2} \cdot \frac{A_o}{1 + \frac{s}{\omega_0}}}$$

Zero:  $\omega_0$ 

$$\text{pole: } \omega_0 + \frac{A_o R_2^2}{(R_1 + R_2)(R_o + R_1 + R_2)} \omega_0$$


$$\text{DC value: } \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2 + A_o R_2^2 / R_1 + R_2}$$
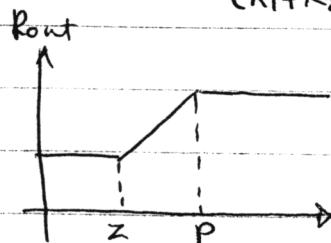
$$\text{final value: } R_o / (R_1 + R_2)$$




The output impedance is less reduced, as the loop gain gets smaller.

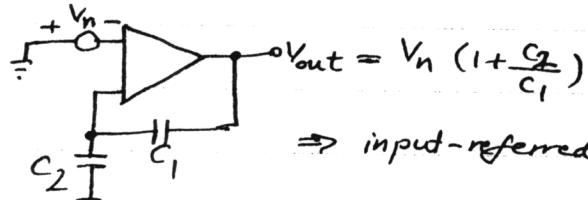8.14 The input-referred noise voltage of the circuit is the same as that of the open-loop circuit:


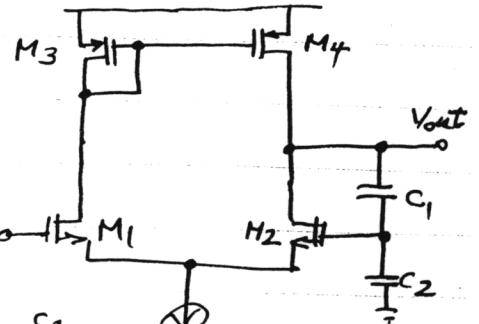
$$\Rightarrow \text{input-referred noise} = \frac{V_n \left(1 + \frac{C_2}{C_1}\right)}{1 + \frac{C_2}{C_1}} = V_n$$



The noise produced by M<sub>1</sub>-M<sub>4</sub> referred to the input is :

$$\overline{V_n^2} = 4kT \left( \frac{2}{3g_{m1,2}} + 2 \frac{2g_{m3,4}}{3g_{m1,2}^2} \right) + 2 \frac{Kn}{(\omega L)_{1,2} C_{oxf}} + 2 \frac{K_p}{(\omega L)_{3,4} C_{oxf}} \times \frac{g_{m3,4}^2}{g_{m1,2}^2}$$

8.15

a)  $Z_{in\ open} = R_o$


$$Z_{in\ closed} = \frac{R_o}{1 + G_{m1}G_{m2}R_o \frac{R_o}{1 + R_o C_{IS}}} = \frac{R_o(1 + R_o C_{IS})}{R_o C_{IS} + 1 + G_{m1}G_{m2}R_o^2}$$

$$\text{Zero: } \frac{1}{R_o C_{IS}}$$

$$\text{pole: } \frac{1 + G_{m1}G_{m2}R_o^2}{R_o C_{IS}}$$

$$\text{DC: } \frac{R_o}{1 + G_{m1}G_{m2}R_o^2}$$

final:  $R_o$

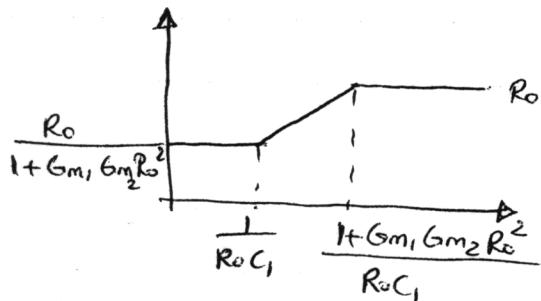

b) Heavy feedback at lower frequency. As frequency increases, feedback weakens since the output impedance of the feedforward amplifier reduces

8.15 (C) For input-referred noise voltage, we short the input,


$$\text{hence } \overline{V_{n,\text{out}}}^2 = 4kT \times 2 \left( \frac{2}{3} g_m + \frac{1}{R_o} \right) \left( R_o \parallel \frac{1}{C_{i,S}} \right).$$

Dividing this by the voltage gain,  $g_m^2 (R_o \parallel \frac{1}{C_{i,S}})^2$ , we have

$$\overline{V_{n,\text{in}}}^2 = 8kT \left( \frac{2}{3} g_m + \frac{1}{g_m^2 R_o} \right).$$

For the input noise current, we leave the input open.

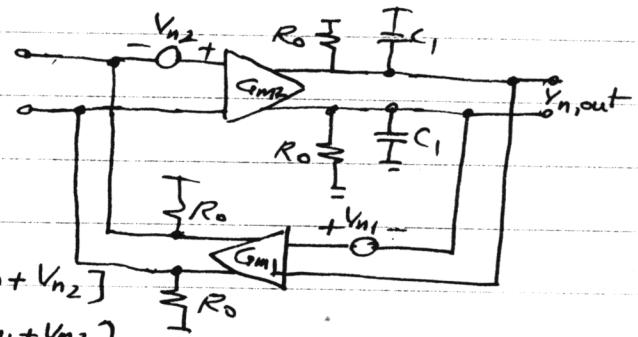Here,  $V_{n_1}$  and  $V_{n_2}$  represent the input noise of each differential pair (including the noise of resistors).



$$\begin{aligned} -V_{n,\text{out}} &= G_{m2} (R_o \parallel \frac{1}{C_{i,S}}) [V_{n_1,\text{out}} + V_{n_2}] G_{m1} R_o + V_{n_2} \\ \Rightarrow V_{n,\text{out}} &= -\frac{G_{m2} (R_o \parallel \frac{1}{C_{i,S}}) (G_{m1} R_o V_{n_1} + V_{n_2})}{1 + G_{m2} (R_o \parallel \frac{1}{C_{i,S}})} G_{m1} R_o \end{aligned}$$

If we apply current between the two input terminals with value  $I_{\text{in}}$ , the output voltage is obtained as:

$$\begin{aligned} -V_{\text{out}} &= (V_{\text{out}} G_{m1} + I_{\text{in}}) R_o \cdot G_{m2} (R_o \parallel \frac{1}{C_{i,S}}) \\ \Rightarrow \frac{V_{\text{out}}}{I_{\text{in}}} &= -\frac{G_{m2} R_o (R_o \parallel \frac{1}{C_{i,S}})}{1 + G_{m1} G_{m2} R_o (R_o \parallel \frac{1}{C_{i,S}})} \end{aligned}$$

Dividing  $V_{n,\text{out}}$  by this gain gives the input-referred noise

$$\text{current: } I_{n,\text{in}} = \frac{G_{m1} R_o V_{n_1} + V_{n_2}}{R_o} \Rightarrow \overline{I_{n,\text{in}}}^2 = G_{m1}^2 \overline{V_{n_1}}^2 + \frac{\overline{V_{n_2}}^2}{R_o^2}$$



8.16

a) Due to symmetry of the  $\pi$  network, no current flows through  $R_F$ .

$$\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - R_{S1} \cdot I_{D1} - V_{TN})^2 = 0.5 \text{ mA}$$

$$(V_{in} - 2.2)^2 = \frac{2 \times 0.5 \times 10^{-3}}{1.342 \times 10^{-4} \times 100} \Rightarrow V_{in} = 2.473 \text{ V}$$
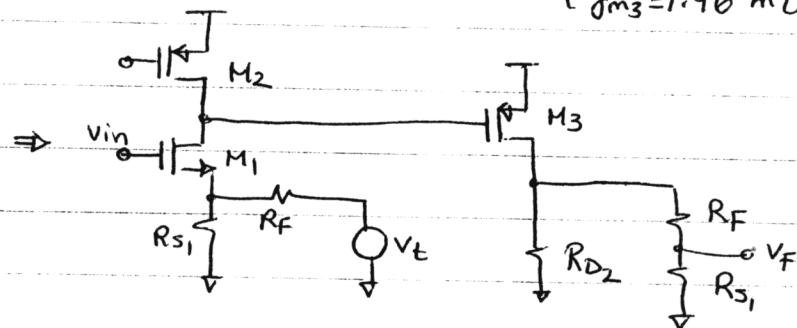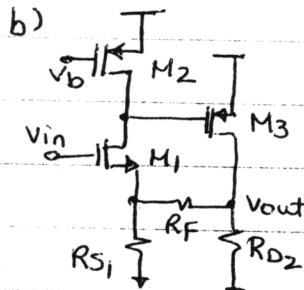
$$\begin{cases} g_{m1} = 3.66 \text{ mV} \\ g_{m2} = 1.96 \text{ mV} \\ g_{m3} = 1.96 \text{ mV} \end{cases} \quad \begin{cases} r_{o1} = 20 \text{ k} \\ r_{o2} = 10 \text{ k} \\ r_{o3} = 10 \text{ k} \end{cases}$$



$$A_{v_{open}} = \frac{r_{o2}}{R_{S1} \parallel R_F + \frac{1}{g_{m1}}} \times g_{m3} [r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1})] = 18.42$$

$$R_{out_{open}} = r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1}) = 1.667 \text{ k}\Omega$$


$$\text{Loop gain: } \frac{V_t}{R_F} \times (R_F \parallel R_{S1}) \times \frac{r_{o2}}{R_{S1} \parallel R_F + \frac{1}{g_{m1}}} \times g_{m3} [r_{o3} \parallel R_{D2} \parallel (R_F + R_{S1})] \times \frac{R_{S1}}{R_F + R_{S1}}$$

$$= V_F \Rightarrow \text{loop gain} = 4.605$$

$$A_v = \frac{18.42}{1 + 4.605} = 3.286$$

$$R_{out} = \frac{1.667 \text{ k}}{1 + 4.605} = 297 \Omega$$

8.17

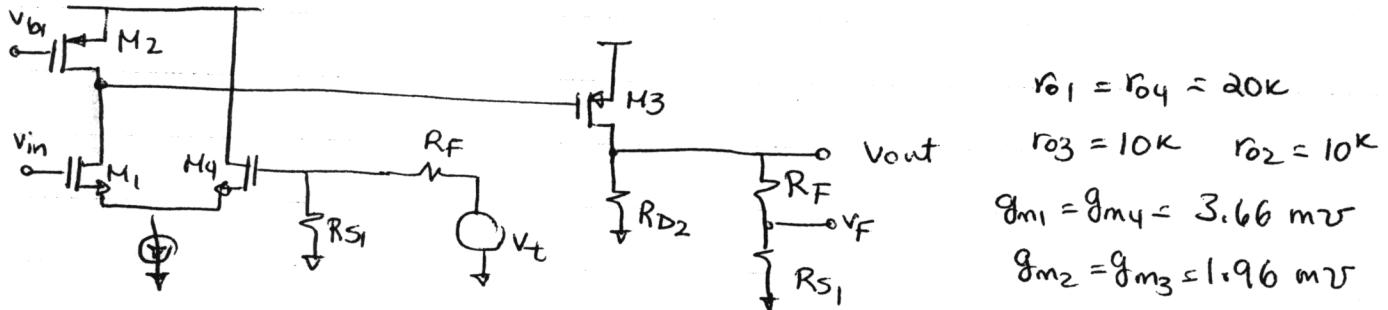

$$A_{v_{open}} = \frac{1}{2} g_{m1} (r_{01} \parallel r_{02}) g_{m3} (r_{03} \parallel R_{D2} \parallel (R_F + R_{S1})) = 39.85$$

$$R_{out} = r_{03} \parallel R_{D2} \parallel (R_F + R_{S1}) = 1.667k$$

$$V_t \frac{R_{S1}}{R_{S1} + R_F} \times \frac{g_{m1}}{2} \times (r_{01} \parallel r_{02}) g_{m3} (r_{03} \parallel R_{D2} \parallel (R_F + R_{S1})) \frac{R_{S1}}{R_{S1} + R_F} = V_F$$

$$\text{loop gain} = 9.96$$

$$A_v = \frac{39.85}{1 + 9.96} = 3.63$$

$$R_{out} = \frac{1.667k}{1 + 9.96} = 153\Omega$$


Smaller output impedance compared to 8.16.

8.18

a)  $I_{Dn} = \frac{1}{2} \mu_n C_o x \frac{W}{L} (V_{GSn} - V_{THn})^2 \Rightarrow V_{GSn} = 0.973 \text{ V}$

$V_{GSp} = 1.311 \Rightarrow 3 - V_b = 1.311 \Rightarrow V_b = 1.69$

$V_{in} = R_1 \cdot I + V_{GSn}$

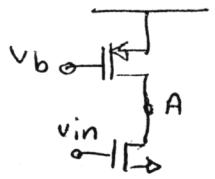


$M_3: \text{saturation} \Rightarrow -V_A + V_b > |V_{THp}| \Rightarrow V_A < 1.689 - 0.8 = 0.889$

$M_4: \text{saturation} \Rightarrow -V_{out} + V_b > V_{THp} \Rightarrow V_{out} < 0.889 \Rightarrow R_1 \cdot I < 0.889 \Rightarrow R_1 < 177$

$M_1: \text{saturation} \Rightarrow V_A > R_1 \cdot I + (V_{GS1} - V_{THn}) \Rightarrow 0.273 + R \times 0.5m < 0.889$ 
 $\Rightarrow R_1 < 1232$

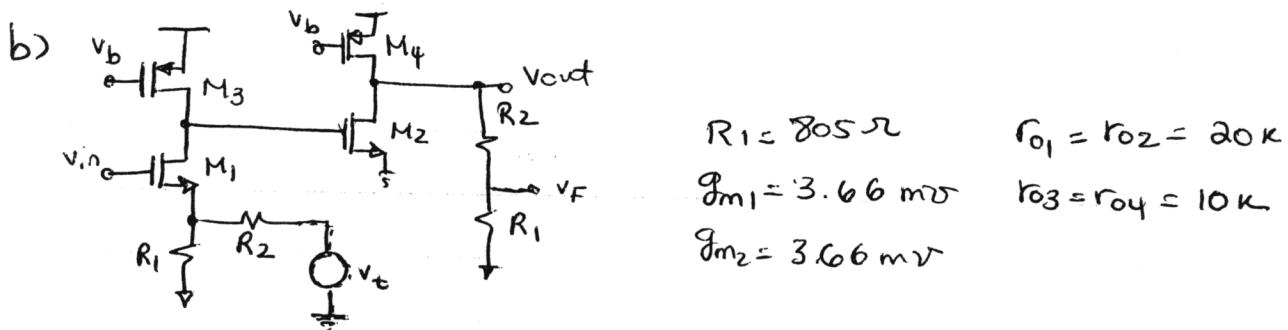$M_2: \text{saturation: } V_{out} = R_1 \cdot I > V_A \rightarrow V_{tn} \Rightarrow R_1 > \frac{0.889 - 0.7}{0.5 \times 10^{-3}} = 378 \Omega$ 
 $378 \leq R_1 \leq 1232 \Rightarrow 1.162 \leq V_{in} \leq 1.589$



$\text{Open loop gain} = \frac{r_{o3}}{R_1 \parallel R_2 + \frac{1}{g_{m1}}} \times g_{m2} (r_{o4} \parallel (R_1 + R_2) \parallel r_{o2}) = 97.6$

$\text{Output impedance} = r_{o4} \parallel (R_1 + R_2) \parallel r_{o2} = 2422 \Omega$


$\text{Loop gain: } \frac{V_t}{R_2} \times (R_1 \parallel R_2) \times \frac{r_{o3}}{R_1 \parallel R_2 + \frac{1}{g_{m1}}} \times g_{m2} (r_{o4} \parallel (R_1 + R_2) \parallel r_{o2}) \frac{R_1}{R_1 + R_2} = V_F$

$\Rightarrow \text{loop gain} = \frac{1}{3000} \times 635 \times 97.6 \times \frac{805}{3805} = 4.37$


$A_v = \frac{97.6}{1 + 4.37} = 18.17$

$R_{out} = \frac{2422}{1 + 4.37} = 451 \Omega$


8.19

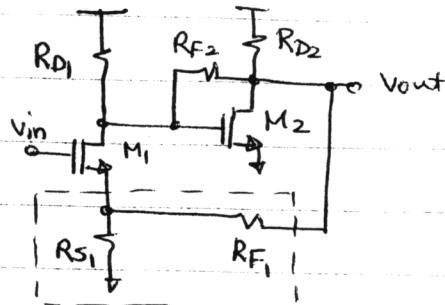

Voltage - Voltage

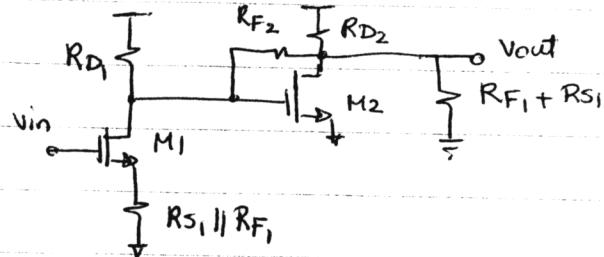

next we consider

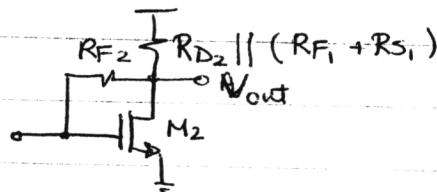

$$R_{in_2} = \frac{RF_2}{1 + g_m_2 [RD_2 || (RF_1 + RS_1)]} = 261 \Omega$$

$$R_{out_2} = \frac{RD_2 || (RF_1 + RS_1)}{1 + g_m_2 [RD_2 || (RF_1 + RS_1)]} = 174 \Omega$$


$$AV_2 = \frac{RD}{RD + RF_2} (-g_m_2 RF_2 + 1) = -3.6$$

$$RD = RD_2 || (RF_1 + RS_1) = 1333$$

$$\text{Open loop gain} = - \frac{RD_1 || R_{in_2}}{RS_1 || RF_1 + \frac{1}{g_m_1}} \cdot AV_2 = \frac{231}{1000 + 200} \times 3.6 = 0.69$$

$$\text{Open loop output impedance} = R_{out_2} = 174 \Omega$$

loop gain:

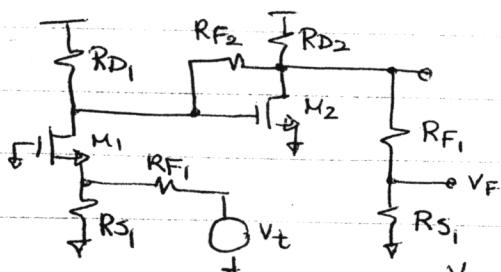

$$\frac{V_t}{R_{F_1}} \times (RS_1 || RF_1) \times \frac{RD_1}{RS_1 || RF_1 + \frac{1}{g_m_1}} \times AV_2 \times \frac{RS_1}{RS_1 + RF_1} = V_F$$

$$\frac{V_F}{V_t} = \frac{1}{2000} \times 1000 \times \frac{1000}{1200} \times 3.6 \times \frac{1}{2} = 0.75$$

$$AV_{closed} = \frac{0.69}{1 + 0.75} = 0.394$$

$$R_{out_{closed}} = \frac{174}{1 + 0.75} = 99.5 \Omega$$

8.20

$$I_{D_1} = I_{D_2} \Rightarrow V_{in} = 1.2538 \Rightarrow I_D = 2.316 \text{ mA}$$

$$g_{m_1} = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS_1} - V_{THn}) = 1.342 \times 10^{-4} \times 100 \times (1.2538 - 0.7) = 7.432 \text{ mV}$$

$$g_{m_2} = \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS_2} - V_{THp}) = 3.835 \times 10^{-5} \times 100 \times (3 - 1.2538 - 0.8) = 3.628 \text{ mV}$$

$$r_{o1} = \frac{1}{\lambda_1 I_1} = \frac{1}{0.1 \times 2.316 \times 10^{-3}} = 4.347 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_2 I_2} = \frac{1}{0.2 \times 2.316 \times 10^{-3}} = 2.159 \text{ k}\Omega$$

(a)

$$a) A_V = -(g_{m_1} + g_{m_2})(r_{o1} \parallel r_{o2}) = -(7.432 + 3.628) 1.439 = 15.91$$

$$R_{out} = r_{o1} \parallel r_{o2} = 1439 \Omega$$

$$b) A_V = \frac{1}{R_1} \cdot \frac{(R_1 \parallel R_2)(g_{m_1} + g_{m_2})(R_2 \parallel r_{o1} \parallel r_{o2})}{1 + (g_{m_1} + g_{m_2})(R_2 \parallel r_{o1} \parallel r_{o2}) \frac{R_1}{R_1 + R_2}}$$


$$(\text{eq. 8.70}) = \frac{1}{1} \times \frac{0.909 (7.432 + 3.628) 1.258}{1 + (7.432 + 3.628) 1.258 \times \frac{1}{11}} = 5.58$$

$$R_{out} = \frac{R_2 \parallel r_{o1} \parallel r_{o2}}{1 + (g_{m_1} + g_{m_2})(R_2 \parallel r_{o1} \parallel r_{o2}) \frac{R_1}{R_1 + R_2}} = 1.258 \text{ k}\Omega / 2.26 = 556 \Omega$$

$$R_{out} = 1.258 \text{ k}\Omega / 2.26 = 556 \Omega$$

(b) We figure out sensitivity for (b), (a) is a special case where

$$R_1 = 0 \quad R_2 = \infty$$

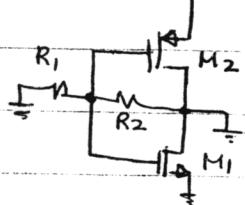 $V_{DD}$ 

$$G_m = g_{m_2}$$

$R_{out}$  = same as before

$$A_V = \frac{g_{m_2} (R_2 \parallel r_{o1} \parallel r_{o2})}{1 + (g_{m_1} + g_{m_2})(R_2 \parallel r_{o1} \parallel r_{o2}) \frac{R_1}{R_1 + R_2}} = \frac{3.628 \times 1.258}{1 + 13.913 \times 1.258} = 1.76$$

if  $R_1 = 0$  and  $R_2 = \infty$

$$A_V = g_{m_2} (r_{o1} \parallel r_{o2}) = 3.628 \times 1.439 = 5.217$$

8.21



$$a) \overline{V_{out}^2} = 4kT \frac{2}{3} (g_{m1} + g_{m2}) (r_o / (r_o)^2)$$

$$\overline{V_{in}^2} = \frac{4kT \frac{2}{3}}{g_{m1} + g_{m2}} =$$

$$b) \overline{V_{in}^2} = 4kT R_1 + \left[ \frac{4kT}{R_2} + 4kT \frac{2}{3} (g_{m1} + g_{m2}) \right] \frac{R_o^2}{A_V^2} = 4kT R_1 + \frac{\frac{4kT}{R_2} + 4kT \frac{2}{3} (g_{m1} + g_{m2})}{\left( \frac{R_2}{R_1 + R_2} \right)^2 (g_{m1} + g_{m2})}$$

$$= 4kT R_1 + \frac{4kT \frac{2}{3}}{g_{m1} + g_{m2}} + \frac{4kT / R_2}{\left( \frac{R_2}{R_1 + R_2} \right)^2 (g_{m1} + g_{m2})^2}$$

8.22

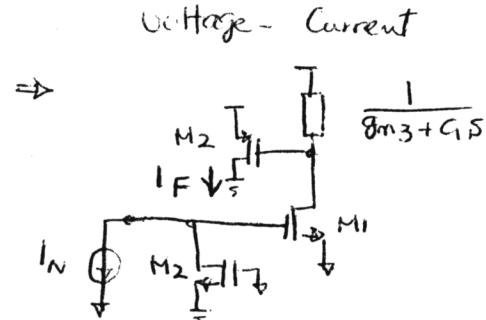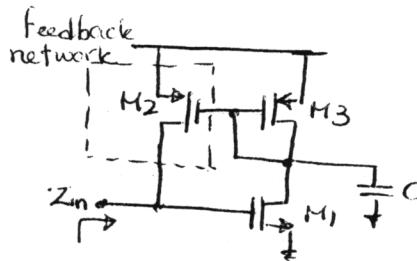

$$\left| \frac{I_F}{I_N} \right| = r_{o2} \cdot g_{m_1} \cdot \frac{1}{g_{m_3} + C_1 s} \cdot g_{m_2}$$

 $r_{o2} \rightarrow \infty$ 


$$Z_{in \text{ open}} = r_{o2}$$

$$Z_{in \text{ closed}} = \frac{r_{o2}}{1 - r_{o2} g_{m_1} g_{m_2} \frac{1}{g_{m_3} + C_1 s}} = - \frac{g_{m_3} + C_1 s}{g_{m_1} g_{m_2}}$$

$$= - \frac{g_{m_3}}{g_{m_1} g_{m_2}} - \underbrace{\frac{C_1}{g_{m_1} g_{m_2}}}_{} s$$

8.23

Very low freq.

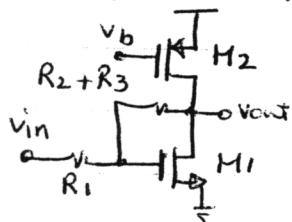


eq. (8.70)

$$A_V = \frac{1}{R_1} \cdot \frac{-(R_1 || (R_2 + R_3)) g_{m_1} (R_2 + R_3)}{1 + g_{m_1} (R_2 + R_3) \frac{R_1}{R_1 + R_2 + R_3}}$$

$$= -\frac{1}{2^k} \frac{(2^{114}) \frac{1}{200} \times 4^k}{1 + \frac{1}{200} \times 4^k \times \frac{1}{3}}$$

$$= -1.739$$

Very high freq.

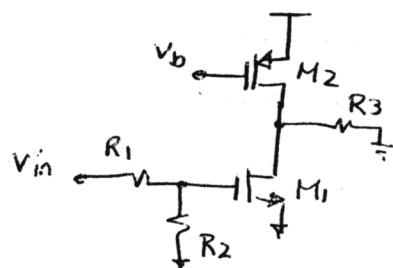

$$A_V = \frac{R_2}{R_1 + R_2} (-g_{m_1} R_3)$$

$$= \frac{1}{2} \left( -\frac{1}{200} \times 2000 \right) = -5$$