

# Network Analysis & Systems

Koshy George



Dept. of Elect. & Comm. Engineering,  
PES University;  
PES Centre for Intelligent Systems

UE18EC201: Network Analysis & Systems



# Disclaimer (1)

- **Errors and Omissions:** The author assumes no responsibility or liability for any errors or omissions in the contents of this file. The information is provided on an “as is” basis with no guarantees of completeness, accuracy, usefulness or timeliness and without any warranties of any kind whatsoever, express or implied.
- **Breach of Confidentiality:** The information in this file are confidential and intended solely for the non-commercial use of the individual or entity to whom this file has been given, who accepts full responsibility for its use. You are not permitted to disseminate, distribute, or copy this file. If you are not the intended recipient you are notified that disclosing, copying, distributing or taking any action in reliance on the contents of this information is strictly prohibited.



## Disclaimer (2)

- **Fair Use:** This file contains copyrighted material the use of which has not always been specifically authorised by the copyright owner.
- **Copyright:** No part of this file may be reproduced, stored in a retrieval system or transmitted in any form or by any means, mechanical, electronic, photocopying, recording or otherwise without the written permission of the author. Copyright ©2019 K. George. All rights reserved.



# Network Analysis and Synthesis

## *Part V: Network Synthesis*



# Network Functions (1)

- Let  $H(s)$  be a network function:

$$H(s) = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)}$$

where  $M_1$  and  $M_2$  are the even parts, and  $N_1$  and  $N_2$  are the odd parts.

- Also,

$$\begin{aligned} H(s) &= \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)} \frac{M_2(s) - N_2(s)}{M_2(s) - N_2(s)} \\ &= \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2} + \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2} \\ &\triangleq \text{Even } [H(s)] + \text{Odd } [H(s)] \end{aligned}$$



## Network Functions (2)

- On the imaginary axis,

$$H(j\omega) = \text{Re} [H(j\omega)] + j\text{Im} [H(j\omega)]$$

- Clearly,

$$\text{Re} [H(j\omega)] = \text{Even} [H(s)]|_{s=j\omega}$$

and

$$j\text{Im} [H(j\omega)] = \text{Odd} [H(s)]|_{s=j\omega}$$

That is, the even part is real and the odd part is imaginary.



# LC Immittance Functions (1)

- Let  $Z(s)$  be the impedance of a passive one-port.



# LC Immittance Functions (1)

- Let  $Z(s)$  be the impedance of a passive one-port.
- For a pure reactive network, the average power dissipated is zero.
- Therefore,

$$\operatorname{Re} [Z(j\omega)] = \operatorname{Even} [Z(j\omega)] = 0$$

where

$$\operatorname{Even} [Z(s)] = \frac{M_1(s)M_2(s) - N_1(s)N_2(s)}{M_2^2(s) - N_2^2(s)}$$

- Clearly,  $\operatorname{Even} [Z(j\omega)] = 0$  implies,

$$M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega) = 0$$





## LC Immittance Functions (2)

$$M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega) = 0$$

implies

- $Z(s) = \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2} + \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2} = \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}.$
- Either  $M_1 = 0 = N_2$  or  $M_2 = 0 = N_1$ .



## LC Immittance Functions (2)

$$M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega) = 0$$

implies

- $Z(s) = \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2} + \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2} = \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}.$
- Either  $M_1 = 0 = N_2$  or  $M_2 = 0 = N_1$ .

Thus,

- If  $M_1 = 0 = N_2$ , then  $Z(s) = \frac{N_1(s)}{M_2(s)}.$



## LC Immittance Functions (2)

$$M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega) = 0$$

implies

- $Z(s) = \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2} + \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2} = \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}$ .
- Either  $M_1 = 0 = N_2$  or  $M_2 = 0 = N_1$ .

Thus,

- If  $M_1 = 0 = N_2$ , then  $Z(s) = \frac{N_1(s)}{M_2(s)}$ .
- If  $M_2 = 0 = N_1$ , then  $Z(s) = \frac{M_1(s)}{N_2(s)}$ .



## LC Immittance Functions (2)

$$M_1(j\omega)M_2(j\omega) - N_1(j\omega)N_2(j\omega) = 0$$

implies

- $Z(s) = \frac{M_1 M_2 - N_1 N_2}{M_2^2 - N_2^2} + \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2} = \frac{N_1 M_2 - M_1 N_2}{M_2^2 - N_2^2}$ .
- Either  $M_1 = 0 = N_2$  or  $M_2 = 0 = N_1$ .

Thus,

- If  $M_1 = 0 = N_2$ , then  $Z(s) = \frac{N_1(s)}{M_2(s)}$ .
- If  $M_2 = 0 = N_1$ , then  $Z(s) = \frac{M_1(s)}{N_2(s)}$ .
- Thus LC immittance functions are a ratio of odd to even polynomials or even to odd polynomials.
- All poles and zeros lie on the imaginary axis.



## LC Immittance Functions (3)

Consider an  $LC$  immittance function

$$H(s) = \frac{a_4 s^4 + a_2 s^2 + a_0}{b_5 s^5 + b_3 s^3 + b_1 s}$$

- All coefficients are real and positive.
- All poles and zeros lie on the imaginary axis.
- There are no multiple poles or zeros on the imaginary axis.



## LC Immittance Functions (3)

Consider an  $LC$  immittance function

$$H(s) = \frac{a_4 s^4 + a_2 s^2 + a_0}{b_5 s^5 + b_3 s^3 + b_1 s}$$

- All coefficients are real and positive.
- All poles and zeros lie on the imaginary axis.
- There are no multiple poles or zeros on the imaginary axis.
- The highest powers must differ by unity: If  $2n$  is the degree of the numerator, then the denominator has degree either  $2n - 1$  or  $2n + 1$ .
- If the degree of denominator is  $2n - 1$ , then  $H(s)$  has a simple pole at  $s = \infty$ .
- If the degree of denominator is  $2n + 1$ , then  $H(s)$  has a simple zero at  $s = \infty$ .



## LC Immittance Functions (4)

$$H(s) = \frac{a_4s^4 + a_2s^2 + a_0}{b_5s^5 + b_3s^3 + b_1s}$$

- The lowest terms of numerator and denominator must differ by one; otherwise, there would be multiple poles or zeros at  $s = 0$ , a contradiction.



## LC Immittance Functions (4)

$$H(s) = \frac{a_4 s^4 + a_2 s^2 + a_0}{b_5 s^5 + b_3 s^3 + b_1 s}$$

- The lowest terms of numerator and denominator must differ by one; otherwise, there would be multiple poles or zeros at  $s = 0$ , a contradiction.
- If the polynomial is even, it should contain all even powers.
- If the polynomial is odd, it should contain all odd powers.
- Otherwise, there would be poles or zeros not on the imaginary axis, a contradiction.





# LC Immittance Functions (5)

Therefore,

$$\begin{aligned}
 H(s) &= \frac{K(s^2 + \omega_1^2)(s^2 + \omega_3^2) \cdots (s^2 + \omega_i^2) \cdots}{s(s^2 + \omega_2^2)(s^2 + \omega_4^2) \cdots (s^2 + \omega_j^2) \cdots} \\
 &= \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s
 \end{aligned}$$

- The residues must be real and positive.
- Clearly,  $H(j\omega)$  is a pure reactance  $jX(\omega)$ , where

$$X(\omega) = -\frac{k_0}{\omega} + \frac{2k_2\omega}{-\omega^2 + \omega_2^2} + \frac{2k_4\omega}{-\omega^2 + \omega_4^2} + \cdots + k_\infty \omega$$

- Moreover,

$$\frac{dX(\omega)}{d\omega} = \frac{k_0}{\omega^2} + k_\infty + \frac{2k_2(\omega^2 + \omega_2^2)}{(\omega^2 - \omega_2^2)^2} + \cdots \geq 0$$



## LC Immittance Functions (6)

Let

$$H(s) = \frac{Ks(s^2 + \omega_3^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2)}$$

Therefore,

$$H(j\omega) = jX(\omega) =$$



## LC Immittance Functions (6)

Let

$$H(s) = \frac{Ks(s^2 + \omega_3^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2)}$$

Therefore,

$$H(j\omega) = jX(\omega) = j \frac{K\omega(-\omega^2 + \omega_3^2)}{(-\omega^2 + \omega_2^2)(-\omega^2 + \omega_4^2)}$$

- What is the plot of  $X(\omega)$  vs.  $\omega$ ?



## LC Immittance Functions (6)

Let

$$H(s) = \frac{Ks(s^2 + \omega_3^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2)}$$

Therefore,


$$H(j\omega) = jX(\omega) = j \frac{K\omega(-\omega^2 + \omega_3^2)}{(-\omega^2 + \omega_2^2)(-\omega^2 + \omega_4^2)}$$

- What is the plot of  $X(\omega)$  vs.  $\omega$ ?
- Recall that  $\frac{dX(\omega)}{d\omega} \geq 0$ .
- $\omega_2$ ,  $\omega_3$ , and  $\omega_4$  are called internal critical frequencies.
- $s = 0$  and  $s = \infty$  are called external critical frequencies.




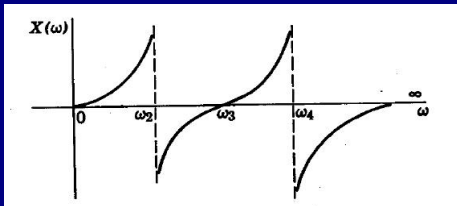
# LC Immittance Functions (7)

$$H(s) = \frac{Ks(s^2 + \omega_3^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2)}$$


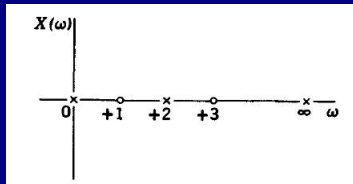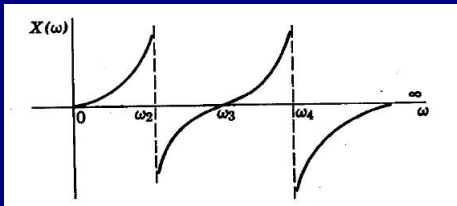
# LC Immittance Functions (7)

$$H(s) = \frac{Ks(s^2 + \omega_3^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2)}$$



# LC Immittance Functions (8)

## Summary of Properties:

- It is the ratio of odd to even polynomials or even to odd polynomials.
- The poles and zeros are simple and lie on the imaginary axis.
- The poles and zeros interlace on the imaginary axis.
- The highest powers of numerator and denominator must differ by unity; the lowest powers also differ by unity.
- There must be a zero or a pole at the origin and infinity.



# LC Immittance Functions (9)

■

$$H(s) = \frac{Ks(s^2 + 4)}{(s^2 + 1)(s^2 + 3)}$$





# LC Immittance Functions (9)

■

$$H(s) = \frac{Ks(s^2 + 4)}{(s^2 + 1)(s^2 + 3)}$$

■

$$H(s) = \frac{s^5 + 4s^3 + 5s}{3s^4 + 6s^2}$$



## LC Immittance Functions (9)

■

$$H(s) = \frac{Ks(s^2 + 4)}{(s^2 + 1)(s^2 + 3)}$$

■

$$H(s) = \frac{s^5 + 4s^3 + 5s}{3s^4 + 6s^2}$$

■

$$H(s) = \frac{K(s^2 + 1)(s^2 + 9)}{(s^2 + 2)(s^2 + 10)}$$



## LC Immittance Functions (10)

$$H(s) = \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s$$

Let  $H(s)$  be an impedance.

- The first term is a  $1/k_0$  F capacitor and the last term is a  $k_\infty$  H inductor.



# LC Immittance Functions (10)

$$H(s) = \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s$$

Let  $H(s)$  be an impedance.

- The first term is a  $1/k_0$  F capacitor and the last term is a  $k_\infty$  H inductor.
- The term  $\frac{2k_i s}{s^2 + \omega_i^2}$  is a parallel tank circuit with  $1/2k_i$  F capacitor in parallel with a  $2k_i/\omega_i^2$  H inductor.
- This is known as **Foster series network**.




# LC Immittance Functions (10)

$$H(s) = \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s$$

Let  $H(s)$  be an impedance.

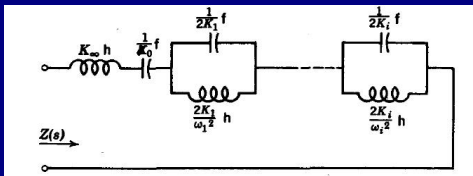- The first term is a  $1/k_0$  F capacitor and the last term is a  $k_\infty$  H inductor.
- The term  $\frac{2k_i s}{s^2 + \omega_i^2}$  is a parallel tank circuit with  $1/2k_i$  F capacitor in parallel with a  $2k_i/\omega_i^2$  H inductor.
- This is known as **Foster series network**.



# LC Immittance Functions (11)

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} =$$




# LC Immittance Functions (11)

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} = 2s + \frac{9/2}{s} + \frac{15s/2}{s^2 + 4}$$


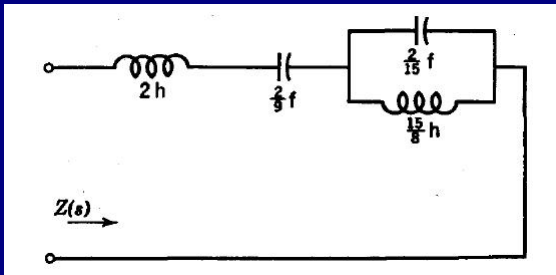
# LC Immittance Functions (11)

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} = 2s + \frac{9/2}{s} + \frac{15s/2}{s^2 + 4}$$





## LC Immittance Functions (12)

$$H(s) = \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s$$

Let  $H(s)$  be an admittance.

- The first term is a  $1/k_0$  H inductor and the last term is a  $k_\infty$  F capacitor.



## LC Immittance Functions (12)

$$H(s) = \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s$$

Let  $H(s)$  be an admittance.

- The first term is a  $1/k_0$  H inductor and the last term is a  $k_\infty$  F capacitor.
- The term  $\frac{2k_i s}{s^2 + \omega_i^2}$  is a series circuit with  $1/2k_i$  H inductor in series with a  $2k_i/\omega_i^2$  F capacitor.
- This is known as **Foster parallel network**.




# LC Immittance Functions (12)

$$H(s) = \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s$$

Let  $H(s)$  be an admittance.

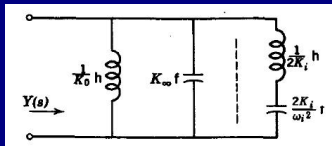- The first term is a  $1/k_0$  H inductor and the last term is a  $k_\infty$  F capacitor.
- The term  $\frac{2k_i s}{s^2 + \omega_i^2}$  is a series circuit with  $1/2k_i$  H inductor in series with a  $2k_i/\omega_i^2$  F capacitor.
- This is known as **Foster parallel network**.



# LC Immittance Functions (13)

$$Y(s) = \frac{s(s^2 + 2)(s^2 + 4)}{s(s^2 + 1)(s^2 + 3)} =$$




## LC Immittance Functions (13)

$$Y(s) = \frac{s(s^2 + 2)(s^2 + 4)}{s(s^2 + 1)(s^2 + 3)} = s + \frac{3s/2}{s^2 + 1} + \frac{s/2}{s^2 + 3}$$


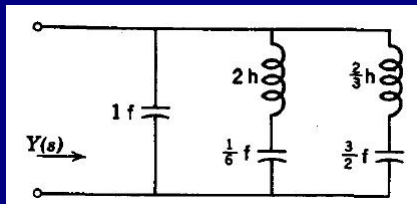
# LC Immittance Functions (13)

$$Y(s) = \frac{s(s^2 + 2)(s^2 + 4)}{s(s^2 + 1)(s^2 + 3)} = s + \frac{3s/2}{s^2 + 1} + \frac{s/2}{s^2 + 3}$$



## LC Immittance Functions (14)

- Recall: the degrees of the numerator and denominator always differ by unity.
- Therefore, there is always a pole or zero at  $s = \infty$ .



## LC Immittance Functions (14)

- Recall: the degrees of the numerator and denominator always differ by unity.
- Therefore, there is always a pole or zero at  $s = \infty$ .
- Thus, for an impedance function  $Z(s)$ , the degree of the numerator is  $2n$  and the degree of the denominator is  $2n - 1$ , implying that there is a pole at  $s = \infty$ .
- Clearly, we can remove an impedance  $L_1s$  so that  $Z_2(s) \triangleq Z(s) - L_1s$  is still an LC impedance function.





## LC Immittance Functions (14)

- Recall: the degrees of the numerator and denominator always differ by unity.
- Therefore, there is always a pole or zero at  $s = \infty$ .
- Thus, for an impedance function  $Z(s)$ , the degree of the numerator is  $2n$  and the degree of the denominator is  $2n - 1$ , implying that there is a pole at  $s = \infty$ .
- Clearly, we can remove an impedance  $L_1s$  so that  $Z_2(s) \triangleq Z(s) - L_1s$  is still an LC impedance function.
- The degree of the denominator of  $Z_2(s)$  is  $2n - 1$  making the degree of the numerator  $2n - 2$ !



## LC Immittance Functions (14)

- Recall: the degrees of the numerator and denominator always differ by unity.
- Therefore, there is always a pole or zero at  $s = \infty$ .
- Thus, for an impedance function  $Z(s)$ , the degree of the numerator is  $2n$  and the degree of the denominator is  $2n - 1$ , implying that there is a pole at  $s = \infty$ .
- Clearly, we can remove an impedance  $L_1s$  so that  $Z_2(s) \triangleq Z(s) - L_1s$  is still an LC impedance function.
- The degree of the denominator of  $Z_2(s)$  is  $2n - 1$  making the degree of the numerator  $2n - 2$ !
- Clearly  $Z_2(s)$  has a zero at  $s = \infty$ ; or  $1/Z_2(s)$  has a pole at  $s = \infty$ .
- This process can be continued, leading to a CFE with a ladder network.



# LC Immittance Functions (15)

$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$$

Therefore,



# LC Immittance Functions (15)

$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$$

Therefore,

$$\begin{array}{r}
 s^4 + 4s^2 + 3 \overline{) 2s^5 + 12s^3 + 16s} \quad (2s \leftrightarrow Z) \\
 \underline{2s^5 + 8s^3 + 6s} \phantom{0} \\
 4s^3 + 10s \quad (4s^3 + 10s) \overline{) s^4 + 4s^2 + 3} \quad (\frac{1}{4}s \leftrightarrow Y) \\
 \underline{s^4 + \frac{5}{2}s^2} \phantom{0} \\
 \frac{3}{2}s^2 + 3 \quad (\frac{3}{2}s^2 + 3) \overline{) 4s^3 + 10s} \quad (\frac{2}{3}s \leftrightarrow Z) \\
 \underline{4s^3 + 8s} \phantom{0} \\
 2s \quad (2s) \overline{) \frac{3}{2}s^2 + 3} \quad (\frac{3}{4}s \leftrightarrow Y) \\
 \underline{\frac{3}{2}s^2} \phantom{0} \\
 3 \quad (3) \overline{) 2s} \quad (\frac{2}{3}s \leftrightarrow Z) \\
 \underline{2s} \\
 0
 \end{array}$$



# LC Immittance Functions (16)

$$Z(s) = 2s + \frac{1}{\frac{s}{4} + \frac{1}{\frac{8s}{3} + \frac{1}{\frac{3s}{4} + \frac{1}{2s/3}}}}$$





# LC Immittance Functions (17)

- If the initial function is an impedance, the first quotient is an impedance, the second is an admittance (due to the expansion of the reciprocal), and so on.
- This is a **Cauer ladder network**.



## LC Immittance Functions (17)

- If the initial function is an impedance, the first quotient is an impedance, the second is an admittance (due to the expansion of the reciprocal), and so on.
- This is a **Cauer ladder network**.
- In contrast, if  $H(s)$  has a pole at  $s = 0$ , the aforementioned procedure can be used to successively remove the poles at  $s = 0$ .
- For this the polynomials are arranged in ascending order.





# LC Immittance Functions (18)

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$

Therefore,



# LC Immittance Functions (18)


$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$

Therefore,

$$\begin{array}{r}
 2s + s^3 \overline{) 3 + 4s^2 + s^4} \quad 3/2s \leftrightarrow Z \\
 \underline{3 + \frac{3}{2}s^2} \\
 \frac{5}{2}s^2 + s^4 \quad 2s + \frac{4}{5}s^3 \leftrightarrow Y \\
 \underline{2s + \frac{4}{5}s^3} \\
 \frac{1}{5}s^3 \quad \frac{5}{2}s^2 + s^4 \quad 25/2s \leftrightarrow Z \\
 \underline{\frac{5}{2}s^2} \\
 s^4 \quad \frac{1}{5}s^3 \quad 1/5s \leftrightarrow Y \\
 \underline{\frac{1}{5}s^3} \\
 \underline{\underline{0}}
 \end{array}$$



# LC Immittance Functions (19)

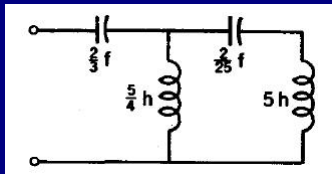

- This is also a Cauer ladder network.



# LC Immittance Functions (20)

## Canonical Forms

- Foster Series Network or Foster I form: PFE of an impedance function.
- Foster Parallel Network or Foster II form: PFE of an admittance function.
- Cauer I form: CFE when the polynomials are arranged in descending order.
- Cauer II form: CFE when the polynomials are arranged in ascending order.
- Cauer I and II forms result in ladder networks and are applicable for an immittance function.

