

9.1 (p325)

 $\alpha = 1000 \text{ s}^{-1}$ and $\omega_o = 800 \text{ rad/s}$, with $R = 100 \Omega$.

$$(a) \quad \alpha = \frac{1}{2RC} \quad \text{so} \quad C = \frac{1}{2R\alpha} = \underline{5 \mu\text{F}}$$

$$(b) \quad \omega_o = \frac{1}{\sqrt{LC}} \quad \text{so} \quad L = \frac{1}{C\omega_o^2} = \underline{312.5 \text{ mH}}$$

$$(c) \quad s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2} = \underline{-400 \text{ s}^{-1}}$$

$$(d) \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_o^2} = \underline{-1600 \text{ s}^{-1}}$$

9.2 (p329)

$$(a) \quad i_L(0^-) = 3 \times \frac{24}{24+48} = \underline{1 \text{ A}}$$

$$(b) \quad v_C(0^-) = 48i_L(0^-) = \underline{48 \text{ V}}$$

(c) Since the capacitor voltage cannot change in zero time, $v_C(0^+) = v_C(0^-) = 48 \text{ V}$. Thus,

$$i_R(0^+) = \frac{48}{24} = \underline{2 \text{ A}}$$

(d) $i_L(0^+) = i_L(0^-)$. With the source off at $t = 0^+$, $i_C(0^+) + i_L(0^+) + i_R(0^+) = 0$ so

$$i_C(0^+) = -1 - 2 = \underline{-3 \text{ A}}$$

$$(e) \quad \alpha = \frac{1}{2RC} = 5 \text{ s}^{-1} \text{ (48-}\Omega \text{ ohm resistor shorted)} \text{ and } \omega_o = \frac{1}{\sqrt{LC}} = 4.899 \text{ rad/s}$$

$$v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [1]$$

where $s_1 = -4 \text{ s}^{-1}$ and $s_2 = -6 \text{ s}^{-1}$

$$\begin{aligned} i_C(t) &= C \frac{dv_C}{dt} = C [A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}] \\ &= \frac{1}{240} [-4 A_1 e^{-4t} - 6 A_2 e^{-6t}] \end{aligned}$$

$$i_C(0^+) = -3 = \frac{1}{240}(-4A_1 - 6A_2) \quad [2]$$

also, from Eq. [1]

$$v_C(0^+) = 48 = A_1 + A_2 \quad [3]$$

Solving Eqns. [2] and [3], we find that $A_1 = -216$ V and $A_2 = 264$ V

so $v_C(t) = -216e^{-4t} + 264e^{-6t}$ V and hence $v_C(0.2) = \underline{-17.54 \text{ V}}$

9.3 (p331)

We have a parallel RLC circuit with

$$\alpha = \frac{1}{2RC} = 41.67 \times 10^9 \text{ s}^{-1} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}} = 20 \times 10^9 \text{ rad/s.}$$

Since $\alpha > \omega_0$, the circuit is overdamped, so we compute $s_1 = -5.113 \times 10^9 \text{ s}^{-1}$ and $s_2 = -78.23 \times 10^9 \text{ s}^{-1}$.

Thus, we expect a resistor current $i_R(t) = Ae^{s_1 t} + Be^{s_2 t} = Ae^{-5.113 \times 10^9 t} + Be^{-78.23 \times 10^9 t}$ A.

Noting that $v_C = 3i_R$ and $v_C(0) = 0$, we can write $3A + 3B = 0$. [1]

Define i_C as flowing out of the top node. Then,

noting that $i_C(0^+) = -i_R(0^+) - i_L(0^+) = 0/3 + 6 = 6$ and


$$\text{that } i_C(0^+) = C \left. \frac{dv}{dt} \right|_{t=0^+} = 4 \times 10^{-12} [3As_1 e^{s_1 t} + 3Bs_2 e^{s_2 t}]_{t=0^+} = 4 \times 10^{-12} [3As_1 + 3Bs_2] = -6 \quad [2]$$

we can solve these two equations for $A = 6.838$ and $B = -A$.

Therefore, $i_R(t) = \underline{6.838(e^{-78.23 \times 10^9 t} - e^{-5.113 \times 10^9 t})}$ amperes.

9.4 (p333)

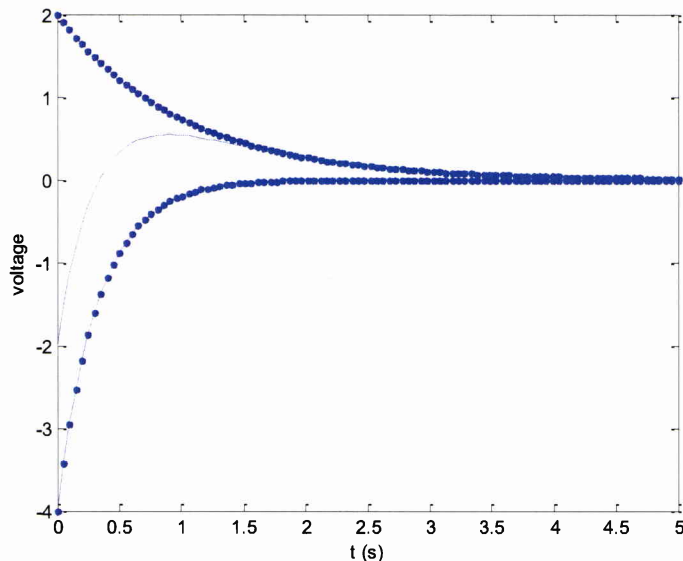- (a) We begin by sketching the two terms independently, then adding graphically, as shown below (the total is drawn in a solid line).



- (b) The maximum value of this function is 544.3 mV (see part (c), or estimate from graph).

Solving using MATLAB for the time at which this value drops to 5.443 mV,

```
>> solve('2*exp(-ts) - 4*exp(-3*ts) = 5.443e-3')
```

from which the only sensible answer is 5.906 s.

- (c) Using MATLAB, we find the time at which the maximum occurs by setting the derivative of the function equal to zero:

```
>> solve('-2*exp(-t) + 12*exp(-3*t) = 0','t')
```

ans =

0.8959

```
>> 2*exp(-1/2*log(6))-4*exp(-3*1/2*log(6))
```

ans =

0.5443

So the maximum value of 544.3 mV occurs at t = 895.9 ms.

9.5 (p338)

- (a) At $t = 0$, resistor R_2 is shorted.

$$\omega_o = \frac{1}{\sqrt{LC}} = 500 \text{ rad/s.}$$

$$\alpha = \frac{1}{2RC} = 500 \text{ s}^{-1}, \text{ so } R_1 = \underline{1000 \Omega}$$

- (b) The voltage across the capacitor cannot change in zero time, so $v(0^+) = v(0^-)$.

$$\text{Looking at the circuit for } t = 0^-, v(0^-) = 0.5 \frac{(1000)}{1000 + R_2} R_2 = 100$$

$$\text{Solving, } R_2 = \underline{250 \Omega}$$

- (c) $v(t) = e^{-500t}(At + B)$. Define i_C, i_{R_1}, i_L flowing downwards.

$$v(0^+) = v(0^-) = 100 = B, \text{ so } v(t) = e^{-500t}(At + 100)$$

$$i_L(0^-) = 0.5 \frac{1000}{1000 + 250} = 0.4 \text{ amperes} = i_L(0^+)$$

$$i_{R_1}(0^+) = \frac{100}{1000} = 0.1 \text{ amperes so } i_C(0^+) = -0.4 - 0.1 = -0.5 \text{ amperes}$$

$$i_C(t) = C \frac{dv}{dt} = 10^{-6} [(-500)e^{-500t}(At + 100) + Ae^{-500t}]$$

$$i_C(0^+) = -0.5 = 10^{-6} [(-500)(100) + A]$$

$$\text{so } A = -450\,000 \text{ V} \cdot \text{s}^{-1}$$

$$\text{Thus, } v(t) = e^{-500t}(-4.5 \times 10^5 t + 100)$$

$$\text{and } v(0.1) = \underline{-212.3 \text{ V}}$$

9.6 (p344)

$$\alpha = \frac{1}{2RC} = 100 \text{ s}^{-1}, \omega_o = \frac{1}{\sqrt{LC}} = 224 \text{ rad/s}, \text{ so } \omega_d = 200 \text{ rad/s}$$

$$\text{For } t < 0, v = 3 \left(\frac{100}{100 + 50} \right) = 2 \text{ V} = v(0^-) = v(0^+)$$

$$\text{For the inductor, defining } i_L \text{ as flowing downward, } i_L(0^-) = \frac{5}{500} = 0.01 \text{ A} = i_L(0^+)$$

$$(a) \text{ For } t > 0, i_C = C \frac{dv}{dt}$$

$$\text{where } v(t) = e^{-100t}(A \cos 200t + B \sin 200t)$$

$$v(0^+) = 2 = A$$

Define i_C and i_R flowing downward. Then $i_C + i_L + i_R = 0$

$$\begin{aligned}\text{At } t = 0^+, \quad i_C(0^+) &= -i_L(0^+) - i_R(0^+) \\ &= -0.01 - \frac{v(0^+)}{500} \\ &= -0.01 - \frac{2}{500} = -0.014 \text{ A}\end{aligned}$$

$$\begin{aligned}i_C(t) &= C \frac{dv}{dt} \\ &= 10 \times 10^{-6} \left[-100 e^{-100t} (2 \cos 200t + B \sin 200t) + e^{-100t} (-400 \sin 200t + 200B \cos 200t) \right]\end{aligned}$$

$$i_C(0^+) = -0.014 = 10 \times 10^{-6} [-100(2) + (200B)]$$

Solving, $B = -6$

$$\text{Thus, } \left. \frac{dv}{dt} \right|_{t=0^+} = \frac{-0.014}{10 \times 10^{-6}} = -1400 \frac{\text{V}}{\text{s}}$$

$$(b) \quad v(t) = e^{-100t} (2 \cos 200t - 6 \sin 200t) \quad \text{so } v(1 \text{ ms}) = \underline{0.695 \text{ V}}$$

(c) These are several ways to solve this, including graphically. Using the iterative routine on a calculator, we find that $t = \underline{1.609 \text{ ms}}$ is the first zero for $t > 0$. $\left(t = \frac{1}{200} \tan^{-1} \left(\frac{1}{3} \right) \text{ exactly} \right)$

9.7 (p349)

$$(a) \quad \alpha = \frac{R}{2L} = \underline{100 \text{ s}^{-1}}$$

$$(b) \quad \omega_o = \frac{1}{\sqrt{LC}} = \underline{223.6 \text{ rad/s}} \quad \therefore \text{ underdamped with } \omega_d = 200 \text{ rad/s}$$

$$(c) \quad i(0^-) = 1 \text{ A}$$

since $i(0^+) = i(0^-)$, $i(0^+) = \underline{1 \text{ A}}$

$$(d) \quad \bullet \text{ define } v_C, v_L \text{ with '+' on top.}$$

$$v_C(0^+) = v_C(0^-) = 100 \times 1 = 100 \text{ V}$$

$$v_L(0^+) = v_C(0^+) - 100i(0^+) = 100 - 100 = 0. \quad \text{Since } v_L = L \frac{di}{dt}, \left. \frac{di}{dt} \right|_{t=0^+} = \underline{0}$$

$$(e) \quad i(t) = e^{-100t} (A \cos 200t + B \sin 200t)$$

$$i(0) = 1 = A$$

$$\frac{di}{dt} = e^{-100t} (-200A \sin 200t + 200B \cos 200t) - 100e^{-100t} (A \cos 200t + B \sin 200t)$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = (200B) - 100A = 0 \quad \text{so} \quad B = \frac{100}{200} = 0.5$$

$$\text{Thus, } i(t) = e^{-100t} (\cos 200t + 0.5 \sin 200t) \text{ and } i(12 \text{ ms}) = \underline{-120.4 \text{ mA}}$$

9.8 (p351)

We're given a hint that "plug and chug" might not be a good route to try here, so instead let's simply note that as we have a series circuit, the inductor current (the quantity of interest) flows through each element. Further, $i_L = i_C = -3v_C$ (the last term coming from the dependent source).

Armed with the knowledge that $i_C = C \frac{dv_C}{dt}$, we can then write $C \frac{dv_C}{dt} = -3v_C$. Rewriting,

$$0.01 \frac{dv_C}{dt} + 3v_C = 0 \quad \text{or} \quad \frac{dv_C}{dt} + 300v_C = 0, \text{ which as a solution of the form}$$

$$v_C = v_C(0^+) e^{-300\alpha} = 10e^{-300\alpha} \text{ V, } t > 0. \text{ Since we can obtain } i_C(t) \text{ by differentiation and multiplying by } C, \underline{i_L = i_C = -30e^{-300\alpha} \text{ A, } t > 0.}$$

9.9 (p355)

$$(a) \quad i_L(0^+) = i_L(0^-) = \underline{10 \text{ A}} \quad (i_s = 10 \text{ A, } t < 0)$$

$$(b) \quad v_C(0^+) = v_C(0^-) = 20(10) = \underline{200 \text{ V}}$$

$$(c) \quad \text{Since the inductor current cannot change in zero time, } v_R(0^+) = 20(10) = \underline{200 \text{ V}}$$

$$(d) \quad i_L(\infty) = \underline{-20 \text{ A}} \text{ due to } i_s \rightarrow -20 \text{ A}$$

$$(e) \quad \alpha = \frac{R}{2L} = 10\,000 \text{ s}^{-1} \text{ and } \omega_o = \frac{1}{\sqrt{LC}} = 10\,000 \text{ rad/s}$$

\therefore circuit is critically damped. So,

$$i_L(t) = e^{-10^4 t} (A_1 t + A_2) - 20$$

Applying initial conditions,

$$i_L(0^+) = 10 = A_2 - 20 \quad [1]$$

and so $A_2 = 30$

$$\frac{di_L}{dt} = -10^4 e^{-10^4 t} (A_1 t + A_2) + A_1 e^{-10^4 t}$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = -10^4 A_2 + A_1 = \frac{1}{L} [v_C(0^+) - v_R(0^+)]$$

$$\text{or } A_1 - 30 \times 10^4 = 10^3 (200 - 200)$$

$$\text{so } A_1 = 30 \times 10^4$$

$$\text{Thus, } i_L(t) = e^{-10^4 t} (30 \times 10^4 t + 30) - 20 \\ = \underline{2.073 \text{ A}}$$

9.10 (p359)

$$(a) \quad i_L(0^+) = i_L(0^-) = \frac{10}{50} = \underline{0.2 \text{ A}} \quad (v_S = 10 \text{ V}, t < 0)$$

$$(b) \quad v_C(0^+) = v_C(0^-) = 50 \times \frac{10}{50} = \underline{10 \text{ V}}$$

$$(c) \quad i_L(\infty) = \frac{30}{50} = \underline{0.6 \text{ A}} \quad (v_S \rightarrow 30 \text{ V})$$

$$(d) \quad \alpha = \frac{1}{2RC} = 10 \text{ s}^{-1} \quad \text{and} \quad \omega_o = \frac{1}{\sqrt{LC}} = 8 \text{ rad/s}$$

Thus, the circuit is overdamped and

$$i_L(t) = Ae^{s_1 t} + Be^{s_2 t} + 0.6$$

where $s_1 = -4 \text{ s}^{-1}$ and $s_2 = -16 \text{ s}^{-1}$

$$i_L(0) = 0.2 = A + B + 0.6 \quad [1]$$

$$\frac{di_L}{dt} = -4Ae^{-4t} - 16Be^{-16t}$$

$$\text{so } \left. \frac{di_L}{dt} \right|_{t=0^+} = -4A - 16B = \frac{1}{L}[-v_C(0) + 30] \text{ or } -4A - 16B = \frac{20}{15.625} \quad [2]$$

Solving Eqns. [1] and [2] simultaneously, $A = -0.4267$ and $B = 0.02667$

$$\text{so that } i_L(t) = -426.7e^{-4t} + 26.67e^{-16t} + 600 \text{ mA}$$

$$\text{Thus, } i_L(0.1) = \underline{319.4 \text{ mA}}$$

9.11 (p361)

$$i_L(0^-) = \frac{12}{1+5} = 2 \text{ A} = i_L(0^+)$$

$$v(0^-) = 12 \frac{5}{1+5} = 10 \text{ V} = v(0^+)$$

- define i flowing out of “+” reference of $v(t)$.

$$v = L \frac{di}{dt} \text{ and } i = -C \frac{dv}{dt} \quad \text{Thus, } v = -LC \frac{d^2v}{dt^2} \text{ or } \frac{d^2v}{dt^2} = -25v$$

$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{-i_L(0^+)}{C} = \frac{-2}{0.005} = -400 \text{ V}$$

so an initial voltage of +400 V is required where -6 V was needed previously. At the $v(t)$ node, an initial voltage of +10 V is required where 0 V was previously needed. Previously a gain of -9 was obtained using $R_1 = 10 \text{ k}\Omega$ and $R_f = 90 \text{ k}\Omega$. Now we require a gain of -25 , so replace R_f with 250 kΩ.

