

# Network Analysis & Synthesis

Koshy George



Dept. of Elect. & Comm. Engineering,  
PES University;  
PES Centre for Intelligent Systems

UE18EC201: Network Analysis & Synthesis



# Disclaimer (1)

- **Errors and Omissions:** The author assumes no responsibility or liability for any errors or omissions in the contents of this file. The information is provided on an “as is” basis with no guarantees of completeness, accuracy, usefulness or timeliness and without any warranties of any kind whatsoever, express or implied.
- **Breach of Confidentiality:** The information in this file are confidential and intended solely for the non-commercial use of the individual or entity to whom this file has been given, who accepts full responsibility for its use. You are not permitted to disseminate, distribute, or copy this file. If you are not the intended recipient you are notified that disclosing, copying, distributing or taking any action in reliance on the contents of this information is strictly prohibited.



## Disclaimer (2)

- **Fair Use:** This file contains copyrighted material the use of which has not always been specifically authorised by the copyright owner.
- **Copyright:** No part of this file may be reproduced, stored in a retrieval system or transmitted in any form or by any means, mechanical, electronic, photocopying, recording or otherwise without the written permission of the author. Copyright ©2019 K. George. All rights reserved.



# Network Analysis and Synthesis

## *Part IV: Two-Ports*



# Overview of Syllabus

## Unit IV (7+2 hours) Two Ports:

- Review of one-ports.
- $z$ -parameters: open circuit analysis;  
 $y$ -parameters: short circuit analysis.
- $h$ -parameters and  $t$ -parameters.
- Deriving two port network parameters from one another.
- Interconnection of two port networks.

**Ref. A:** Chapter 11.

**Ref. B:** Chapter 17.

**Ref. C:**<sup>1</sup> Chapter 9.

---

<sup>1</sup>F. F. Kuo, *Network Analysis and Synthesis*, 2nd edn., John Wiley, 2006.



# One-Port — Review (1)

- Suppose that we have bought an amplifier and speakers separately.




# One-Port — Review (1)

- Suppose that we have bought an amplifier and speakers separately.
- The speaker system consists of woofers, mid-range speakers and tweeters.
- Filters are to be designed to direct the specific range of audio frequencies to the speakers, low frequency to woofer, and high-frequency to tweeter.
- The design of these filters requires only the following data — Thévenin equivalent circuit of the amplifier and the input impedance of the speakers.
- That is, for this application, we need not know what happens inside the amplifier, but only what happens at the terminals.



## One-Port — Review (2)

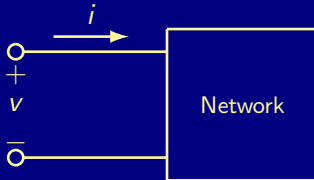

- Equivalently, we treat the amplifier and the speaker as a two-terminal network or a one-port as we are interested only in the port properties.
- Or, the inside is treated as a black box.
- We have so far considered only one-ports.
- The pair of terminals is customarily connected to an energy source which is the driving force of the network.
- Hence, the pair of terminals is called the driving point of the network.





## One-Port— Review (3)

- The transform impedance at a port is the ratio of the voltage transform to current transform for a network in a zero-state and no independent sources:

$$Z(s) = \frac{V(s)}{I(s)}$$


- Similarly, the transform admittance is the ratio

$$Y(s) = \frac{I(s)}{V(s)}$$

- The impedance or admittance at a port is called a driving-point impedance or admittance.
- Often referred to as immittance.




# Two-Ports (1)

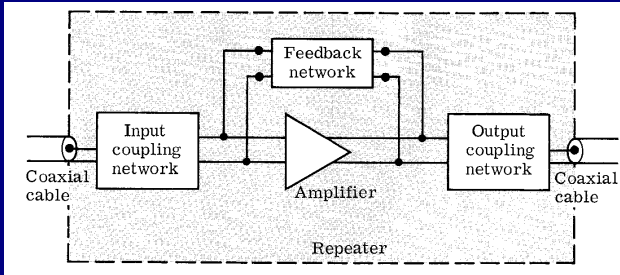

- Many practical examples fall into the category wherein one is interested in accessing two pairs of terminals; that is, two ports.
- The specifics or details of the network between these two ports are not relevant.




# Two-Ports (2)

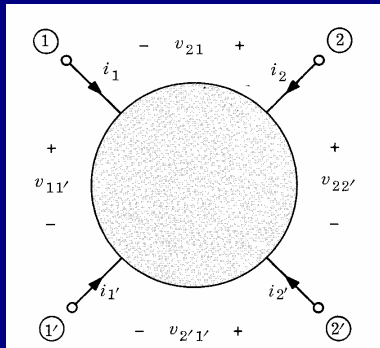

- The figure shows a network with four terminals.



# Two-Ports (3)

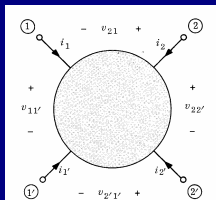

- In general, the four terminals must satisfy KVL and KCL:


$$i_1(t) + i_{1'}(t) + i_2(t) + i_{2'}(t) = 0$$

$$v_{11'}(t) + v_{21}(t) - v_{22'}(t) - v_{2'1'} = 0$$

for all instants  $t$  and all possible connections of the four-terminal network.



# Two-Ports (3)

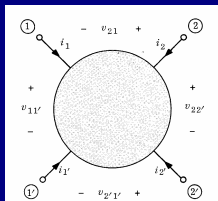

- In general, the four terminals must satisfy KVL and KCL:

$$i_1(t) + i_1'(t) + i_2(t) + i_2'(t) = 0$$

$$v_{11'}(t) + v_{21}(t) - v_{22'}(t) - v_{2'1'} = 0$$

for all instants  $t$  and all possible connections of the four-terminal network.

- The four-terminal network becomes a two-port only if the following conditions are imposed for all  $t$ :

$$i_1'(t) = -i_1(t), \quad i_2'(t) = -i_2(t)$$



# Two-Ports (4)



- The four-terminals are paired into ports 1-1' and 2-2'.



## Two-Ports (4)



- The four-terminals are paired into ports 1–1' and 2–2'.
- Everything between these four terminals is a black box.



## Two-Ports (4)




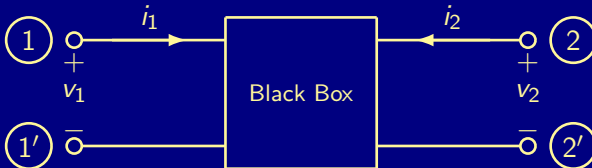
- The four-terminals are paired into ports 1–1' and 2–2'.
- Everything between these four terminals is a black box.
- A two-port is any four-terminal network such that
  - At every instant of time  $t$ , the current entering terminal 1 (i.e.,  $i_1$ ) is equal to the current leaving the terminal 1'.










- The four-terminals are paired into ports 1–1' and 2–2'.
  - Everything between these four terminals is a black box.
  - A two-port is any four-terminal network such that
    - At every instant of time  $t$ , the current entering terminal 1 (i.e.,  $i_1$ ) is equal to the current leaving the terminal 1'.
    - Similarly, at every instant of time  $t$ , the current entering terminal 2 (i.e.,  $i_2$ ) is equal to the current leaving the terminal 2'.
- 



## Two-Ports (5)

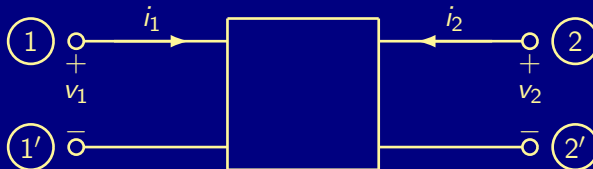


Network vs. Two-ports:

- To solve a network implies that all branch voltages and branch currents are calculated.
- In a two-port, the only variables of interest are the port variables —  $v_1$ ,  $v_2$ ,  $i_1$  and  $i_2$ .
- Also, in a two-port, the only places independent sources are connected are the ports.




## Two-Ports (6)

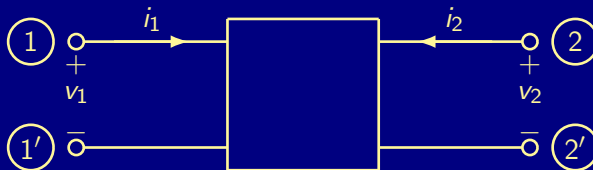

- The port at the left is usually referred to as the input port and has voltage  $v_1$  and current  $i_1$ .
- The port at the right is usually referred to as the output port and has voltage  $v_2$  and current  $i_2$ .
- Two-ports are completely characterised by all possible waveforms  $v_1(\cdot)$ ,  $v_2(\cdot)$ ,  $i_1(\cdot)$  and  $i_2(\cdot)$ .




# Two-Ports (7)

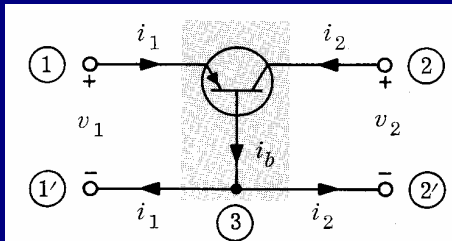

- Common-base transistor: An example of a two-port.



## Two-Ports (8)

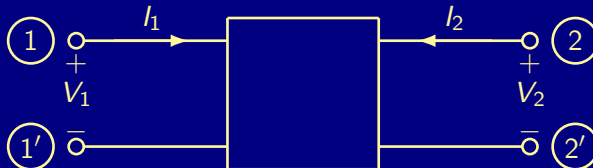

- Port 1 is the input port with transform quantities  $V_1$  and  $I_1$ .
- Port 2 is the output port with transform quantities  $V_2$  and  $I_2$ .
- Only two of these four variables are independent.
- The dependence of the other two variables on the independent variables can be expressed in a number of ways.
- Here, we consider six such combinations.



# Two-Ports (9)

Name	Dependent Variables	Independent Variables
Open-circuit impedance	$V_1, V_2$	$I_1, I_2$
Short-circuit admittance	$I_1, I_2$	$V_1, V_2$
Transmission	$V_1, I_1$	$V_2, I_2$
Inverse transmission	$V_2, I_2$	$V_1, I_1$
Hybrid	$V_1, I_2$	$I_1, V_2$
Inverse hybrid	$I_1, V_2$	$V_1, I_2$



# Two-Ports (10)

Short-Circuit Admittance Parameters: Assuming no dependent (controlled) sources,

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$





## Two-Ports (10)

**Short-Circuit Admittance Parameters:** Assuming no dependent (controlled) sources,

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

Observe that the four parameters may be defined as follows:



$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

- The conditions  $V_1 = 0$  or  $V_2 = 0$  is equivalent to shorting port 1 or port 2, respectively.





# Two-Ports (11)

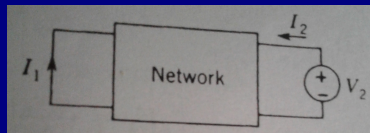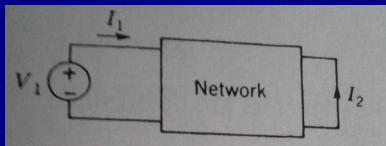

- (a):  $y_{11}$  and  $y_{21}$ .
- (b):  $y_{12}$  and  $y_{22}$ .
- The terminology “short-circuit admittance” is obvious.



# Two-Ports (11)

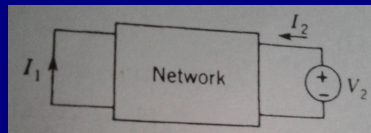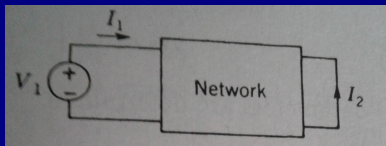

- (a):  $y_{11}$  and  $y_{21}$ .
- (b):  $y_{12}$  and  $y_{22}$ .
- The terminology “short-circuit admittance” is obvious.
- For a reciprocal network,

$$y_{12} = y_{21}$$



# Two-Ports (12)

Open-Circuit Impedance Parameters: Assuming no dependent (controlled) sources,

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$



## Two-Ports (12)

**Open-Circuit Impedance Parameters:** Assuming no dependent (controlled) sources,

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

Observe that the four parameters may be defined as follows:



$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

- The conditions  $I_1 = 0$  or  $I_2 = 0$  is equivalent to open circuits at port 1 or port 2, respectively.





# Two-Ports (13)

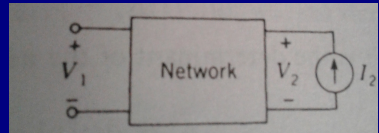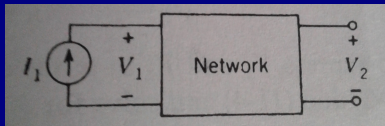

- (a):  $z_{11}$  and  $z_{21}$ .
- (b):  $z_{12}$  and  $z_{22}$ .
- The terminology “open-circuit impedance” is obvious.



# Two-Ports (13)

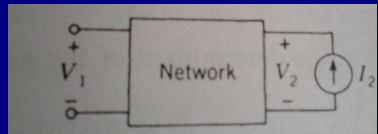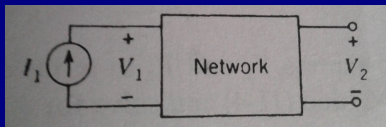

- (a):  $z_{11}$  and  $z_{21}$ .
- (b):  $z_{12}$  and  $z_{22}$ .
- The terminology “open-circuit impedance” is obvious.
- For a reciprocal network,

$$z_{12} = z_{21}$$



## Two-Ports (14)

Note that for short-circuit admittance parameters,

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

or

$$I = YV$$





## Two-Ports (14)

Note that for short-circuit admittance parameters,

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

or

$$I = YV$$

Similarly, for open-circuit impedance parameters,

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

or

$$V = ZI$$



## Two-Ports (14)

Note that for short-circuit admittance parameters,

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

or

$$I = YV$$

Similarly, for open-circuit impedance parameters,

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$


or

$$V = ZI$$

- Clearly,  $YZ = ZY = I$ .
- Also,  $y_{11}z_{11} = y_{22}z_{22}$ .



## Two-Ports (15)

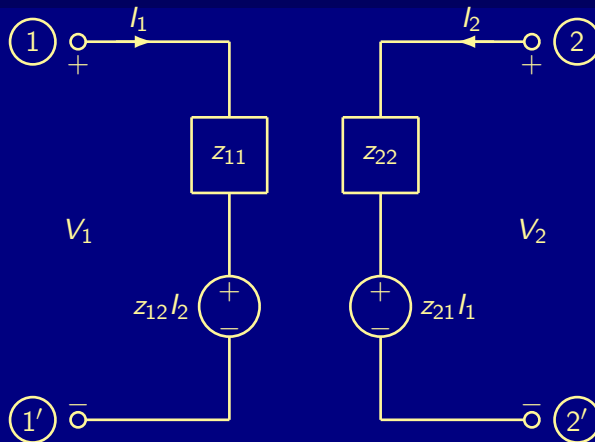

- Two-generator equivalent in terms of open-circuit impedance parameters.



# Two-Ports (16)

Recall:

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$



# Two-Ports (16)

Recall:

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$


Equivalently,

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{12}I_1 + z_{22}I_2 + (z_{21} - z_{12})I_1$$

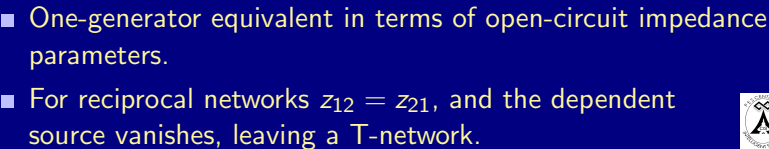- The latter leads to the one-generator equivalent in terms of the open-circuit impedance parameters.





# Two-Ports (18)

Recall:

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$



# Two-Ports (18)

Recall:

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

Equivalently,

$$I_1 = (y_{11} + y_{12}) V_1 - y_{12} (V_1 - V_2)$$


$$I_2 = (y_{21} - y_{12}) V_1 + (y_{12} + y_{22}) V_2 - y_{12} (V_2 - V_1)$$

- The latter leads to the one-generator equivalent in terms of the short-circuit admittance parameters.






# Two-Ports (19)

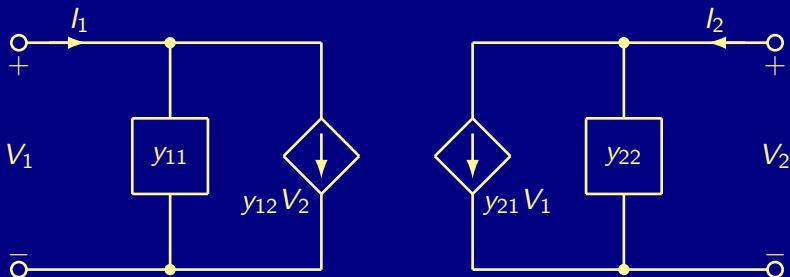

- Two-generator equivalent in terms of short-circuit admittance parameters.



# Two-Ports (20)

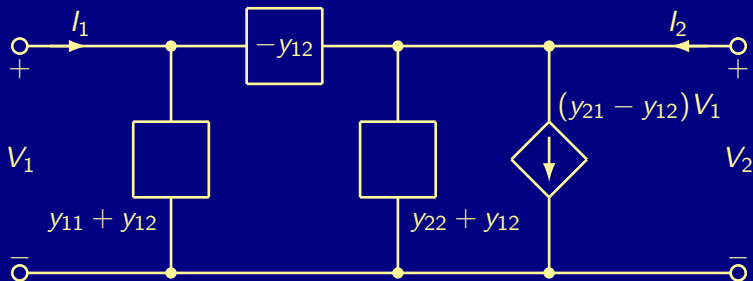

- One-generator equivalent in terms of short-circuit admittance parameters.
- For reciprocal networks  $y_{12} = y_{21}$ .

