

Network Analysis & Systems

Koshy George



Dept. of Elect. & Comm. Engineering,
PES University;
PES Centre for Intelligent Systems

UE18EC201: Network Analysis & Systems



Disclaimer (1)

- **Errors and Omissions:** The author assumes no responsibility or liability for any errors or omissions in the contents of this file. The information is provided on an “as is” basis with no guarantees of completeness, accuracy, usefulness or timeliness and without any warranties of any kind whatsoever, express or implied.
- **Breach of Confidentiality:** The information in this file are confidential and intended solely for the non-commercial use of the individual or entity to whom this file has been given, who accepts full responsibility for its use. You are not permitted to disseminate, distribute, or copy this file. If you are not the intended recipient you are notified that disclosing, copying, distributing or taking any action in reliance on the contents of this information is strictly prohibited.



Disclaimer (2)

- **Fair Use:** This file contains copyrighted material the use of which has not always been specifically authorised by the copyright owner.
- **Copyright:** No part of this file may be reproduced, stored in a retrieval system or transmitted in any form or by any means, mechanical, electronic, photocopying, recording or otherwise without the written permission of the author. Copyright ©2019 K. George. All rights reserved.



Network Analysis and Synthesis

Unit IV: Two-Ports



Examples (1)

- Example 1, Valkenburg, p. 328.



Examples (1)

- Example 1, Valkenburg, p. 328.
- Example 2, Valkenburg, p. 330.



Examples (1)

- Example 1, Valkenburg, p. 328.
- Example 2, Valkenburg, p. 330.
- Example 3, Valkenburg, p. 330.



Examples (1)

- Example 1, Valkenburg, p. 328.
- Example 2, Valkenburg, p. 330.
- Example 3, Valkenburg, p. 330.
- Problem 11-1, Valkenburg, p. 342.



Examples (1)

- Example 1, Valkenburg, p. 328.
- Example 2, Valkenburg, p. 330.
- Example 3, Valkenburg, p. 330.
- Problem 11-1, Valkenburg, p. 342.
- Problem 11-3, Valkenburg, p. 342.



Examples (1)

- Example 1, Valkenburg, p. 328.
- Example 2, Valkenburg, p. 330.
- Example 3, Valkenburg, p. 330.
- Problem 11-1, Valkenburg, p. 342.
- Problem 11-3, Valkenburg, p. 342.
- Problem 11-4, Valkenburg, p. 342.



Two-Ports (21)

Transmission Parameters:

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$



Two-Ports (21)

Transmission Parameters:

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Observe that the four parameters may be defined as follows:

$$\begin{aligned} \frac{1}{A} &= \left. \frac{V_2}{V_1} \right|_{I_2=0} & \frac{1}{C} &= \left. \frac{V_2}{I_1} \right|_{I_2=0} \\ -\frac{1}{B} &= \left. \frac{I_2}{V_1} \right|_{V_2=0} & -\frac{1}{D} &= \left. \frac{I_2}{I_1} \right|_{V_2=0} \end{aligned}$$

- These are called chain parameters or $ABCD$ parameters or t parameters or general circuit parameters (power transmission lines).



Two-Ports (22)

- The negative signs are due to a different conventions for the direction of I_2 in power transmission problems.



Two-Ports (22)

- The negative signs are due to a different conventions for the direction of I_2 in power transmission problems.

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

- $1/A$ is the open-circuit gain.
- $1/C$ is the open-circuit transfer impedance.
- $-1/B$ is the short-circuit transfer admittance.
- $-1/D$ is the short-circuit gain.



Two-Ports (23)

Suppose that there are two two-ports: Then

$$\begin{pmatrix} V_{1a} \\ I_{1a} \end{pmatrix} = \begin{pmatrix} A_a & B_a \\ C_a & D_a \end{pmatrix} \begin{pmatrix} V_{2a} \\ -I_{2a} \end{pmatrix}$$

and

$$\begin{pmatrix} V_{1b} \\ I_{1b} \end{pmatrix} = \begin{pmatrix} A_b & B_b \\ C_b & D_b \end{pmatrix} \begin{pmatrix} V_{2b} \\ -I_{2b} \end{pmatrix}$$

If these are two are in cascade or chain, then for the composite network

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$



Two-Ports (23)

When the two ports are in cascade,

$$\begin{aligned}V_1 &= V_{1a} & I_1 &= I_{1a} \\V_2 &= V_{2b} & I_2 &= I_{2b} \\I_{2a} &= -I_{1b} & V_{2a} &= V_{1b}\end{aligned}$$

Then

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} =$$



Two-Ports (23)

When the two ports are in cascade,

$$\begin{aligned}V_1 &= V_{1a} & I_1 &= I_{1a} \\V_2 &= V_{2b} & I_2 &= I_{2b} \\I_{2a} &= -I_{1b} & V_{2a} &= V_{1b}\end{aligned}$$

Then

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} A_a & B_a \\ C_a & D_a \end{pmatrix} \begin{pmatrix} A_b & B_b \\ C_b & D_b \end{pmatrix}$$

- This can be generalised to any number of two-ports.



Two-Ports (24)

Inverse Transmission Parameters:

$$V_2 = A'V_1 - B'I_1$$

$$I_2 = C'V_1 - D'I_1$$



Two-Ports (24)

Inverse Transmission Parameters:

$$V_2 = A'V_1 - B'I_1$$

$$I_2 = C'V_1 - D'I_1$$

Observe that the four parameters may be defined as follows:

$$\begin{aligned} \frac{1}{A'} &= \left. \frac{V_1}{V_2} \right|_{I_1=0} & \frac{1}{C'} &= \left. \frac{V_1}{I_2} \right|_{I_1=0} \\ -\frac{1}{B'} &= \left. \frac{I_1}{V_2} \right|_{V_1=0} & -\frac{1}{D'} &= \left. \frac{I_1}{I_2} \right|_{V_1=0} \end{aligned}$$

- These parameters apply for transmission in the opposite direction.
- The properties of the inverse transmission $A'B'C'D'$ parameters are similar to the transmission $ABCD$ parameters.



Two-Ports (25)

Recall:

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

Compare this with

$$\frac{1}{A} = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad \frac{1}{C} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

■ Thus, $A = z_{11}/z_{21}$ and $C = 1/z_{21}$.



Two-Ports (25)

Recall:

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

Therefore,

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \frac{1}{\Delta} \begin{pmatrix} z_{22} & -z_{12} \\ -z_{21} & z_{11} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$-\frac{1}{B} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \quad -\frac{1}{D} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

- Thus, $B = \Delta/z_{21}$ and $D = z_{22}/z_{21}$, where $\Delta = z_{11}z_{22} - z_{12}z_{21}$.



Two-Ports (26)

Transmission parameters in terms of z -parameters:

$$A = \frac{z_{11}}{z_{21}}, \quad B = \frac{\Delta}{z_{21}}, \quad C = \frac{1}{z_{21}}, \quad D = \frac{z_{22}}{z_{21}}$$

- Clearly, $AD - BC = z_{12}/z_{21}$.
- For a reciprocal network,

$$AD - BC = 1$$

- Similarly for the inverse transmission parameters, reciprocity implies

$$A'D' - B'C' = 1$$



Two-Ports (27)

Hybrid, or h , parameters:

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

Observe that the four parameters may be defined as follows:

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$


$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

- h_{11} and h_{21} are respectively the s.c. input impedance and current gain.
- h_{12} and h_{22} are respectively the o.c. reverse voltage gain and output admittance.



Two-Ports (28)

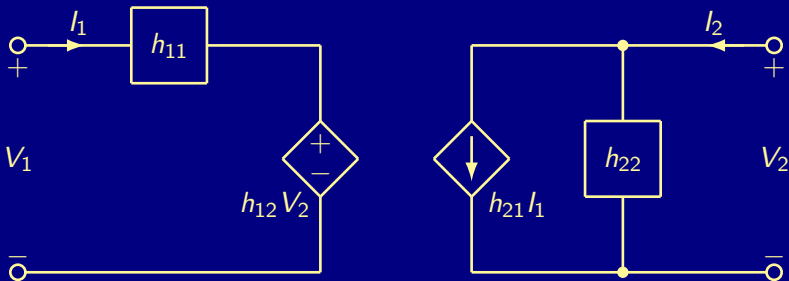- Note that the parameters are dimensionally mixed; hence, the term 'hybrid'.
- Useful for modelling transistors.



Inverse Hybrid, or g , Parameters:

$$V_2 = g_{21} V_1 + g_{22} I_2$$



Observe that the four parameters may be defined as follows:

$$\begin{aligned} g_{11} &= \left. \frac{l_1}{V_1} \right|_{l_2=0} & g_{21} &= \left. \frac{V_2}{V_1} \right|_{l_2=0} \\ g_{12} &= \left. \frac{l_1}{l_2} \right|_{V_1=0} & g_{22} &= \left. \frac{V_2}{l_2} \right|_{V_1=0} \end{aligned}$$

- g_{11} and g_{21} are respectively the o.c. input admittance and voltage gain.
- g_{12} and g_{22} are respectively the s.c. reverse current gain and output impedance.



Two-Ports (30)

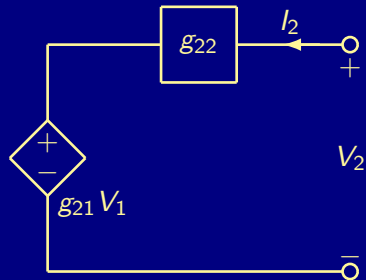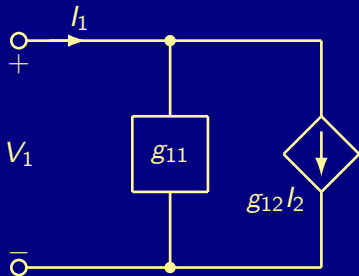

Examples (2)

- Example 4, Valkenburg, p. 335.



Examples (2)

- Example 4, Valkenburg, p. 335.
- Problem 11-10, Valkenburg, p. 343.



Examples (2)

- Example 4, Valkenburg, p. 335.
- Problem 11-10, Valkenburg, p. 343.
- Problem 11-11, Valkenburg, p. 343.



Examples (2)


- Example 4, Valkenburg, p. 335.
- Problem 11-10, Valkenburg, p. 343.
- Problem 11-11, Valkenburg, p. 343.

Reading Assignment: Section 11-6: Relationships Between Parameter Sets.



Two-Ports (31)

Parallel Connection of Two-Ports:

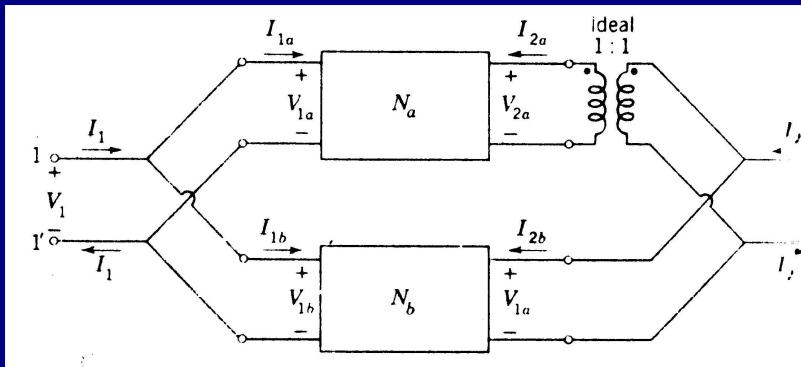

Two-Ports (32)

- Assumption: The parallel connection will not alter the nature of the networks.
- For example, T -networks shorts out the lowest resistor, and hence the network is altered.
- This is circumvented by the 1:1 turns ratio ideal transformer.
- Or, when the two networks have a common ground. In this case, the ideal transformer is not required.



Two-Ports (33)

- Short-circuit admittance functions are useful in characterising parallel two-ports.
- For Network A,

$$I_{1a} = y_{11a} V_{1a} + y_{12a} V_{2a}$$

$$I_{2a} = y_{21a} V_{1a} + y_{22a} V_{2a}$$

- For Network B,

$$I_{1b} = y_{11b} V_{1b} + y_{12b} V_{2b}$$

$$I_{2b} = y_{21b} V_{1b} + y_{22b} V_{2b}$$



Two-Ports (34)

- Assuming parallel connection can be made,

$$V_1 = V_{1a} = V_{1b}, \quad V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b}, \quad I_2 = I_{2a} + I_{2b}$$



Two-Ports (34)

- Assuming parallel connection can be made,

$$V_1 = V_{1a} = V_{1b}, \quad V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b}, \quad I_2 = I_{2a} + I_{2b}$$

- Therefore, from KCL,

$$I_1 = (y_{11a} + y_{11b})V_1 + (y_{12a} + y_{12b})V_2$$

$$I_2 = (y_{21a} + y_{21b})V_1 + (y_{22a} + y_{22b})V_2$$



Two-Ports (34)

- Assuming parallel connection can be made,

$$V_1 = V_{1a} = V_{1b}, \quad V_2 = V_{2a} = V_{2b}$$

$$I_1 = I_{1a} + I_{1b}, \quad I_2 = I_{2a} + I_{2b}$$

- Therefore, from KCL,

$$I_1 = (y_{11a} + y_{11b})V_1 + (y_{12a} + y_{12b})V_2$$


$$I_2 = (y_{21a} + y_{21b})V_1 + (y_{22a} + y_{22b})V_2$$

- This can be extended to any number of networks.



Two-Ports (35)

Twin T -networks with a common ground:

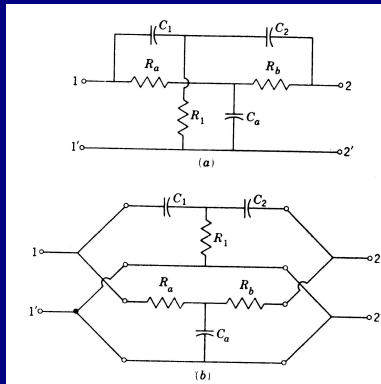

Two-Ports (36)

A bridged- T -network and its equivalent as a parallel two-port:

