Network Analysis & Systems

Koshy George





Dept. of Elect. & Comm. Engineering,
PES University;
PES Centre for Intelligent Systems

UE18EC201: Network Analysis & Systems





Disclaimer (1)

- Errors and Omissions: The author assumes no responsibility or liability for any errors or omissions in the contents of this file. The information is provided on an "as is" basis with no guarantees of completeness, accuracy, usefulness or timeliness and without any warranties of any kind whatsoever, express or implied.
- Breach of Confidentiality: The information in this file are confidential and intended solely for the non-commercial use of the individual or entity to whom this file has been given, who accepts full responsibility for its use. You are not permitted to disseminate, distribute, or copy this file. If you are not the intended recipient you are notified that disclosing, copying, distributing or taking any action in reliance on the contents of this information is strictly prohibited.



Disclaimer (2)

- Fair Use: This file contains copyrighted material the use of which has not always been specifically authorised by the copyright owner.
- Copyright: No part of this file may be reproduced, stored in a retrieval system or transmitted in any form or by any means, mechanical, electronic, photocopying, recording or otherwise without the written permission of the author. Copyright ©2019 K. George. All rights reserved.





Network Analysis and Synthesis

Part V: Network Synthesis





■ In a passive network, no voltage can appear across any pair of terminals before a current or voltage source is applied between another pair of terminals.





- In a passive network, no voltage can appear across any pair of terminals before a current or voltage source is applied between another pair of terminals.
- More generally, a network (or a system) cannot respond before it is excited.





- In a passive network, no voltage can appear across any pair of terminals before a current or voltage source is applied between another pair of terminals.
- More generally, a network (or a system) cannot respond before it is excited.
- Recall that the response of a network function is

$$Y(s) = H(s)U(s)$$

where H(s) could be associated with a one-port or a two-port.





- In a passive network, no voltage can appear across any pair of terminals before a current or voltage source is applied between another pair of terminals.
- More generally, a network (or a system) cannot respond before it is excited.
- Recall that the response of a network function is

$$Y(s) = H(s)U(s)$$

where H(s) could be associated with a one-port or a two-port.

■ Since $\mathcal{L}\{\delta(t)\}=1$, if $u(t)=\delta(t)$,

$$Y(s) = H(s)$$

■ Accordingly, the network function H(s) is also referred to as the Laplace transform of the impulse response.





The convolution of two signals are defined by

$$f(t)*g(t) = \int_{-\infty}^{\infty} f(\tau)g(t-\tau)d\tau$$





The convolution of two signals are defined by

$$f(t)*g(t) = \int_{-\infty}^{\infty} f(\tau)g(t-\tau)d\tau$$

In particular for the network function if $H(s) = \mathcal{L}\{h(t)\}$, and u(t)is an applied voltage or current,

$$y(t) = h(t) * u(t) = \int_{-\infty}^{\infty} u(\tau)h(t-\tau)d\tau$$





The convolution of two signals are defined by

$$f(t)*g(t) = \int_{-\infty}^{\infty} f(\tau)g(t-\tau)d\tau$$

In particular for the network function if $H(s) = \mathcal{L}\{h(t)\}$, and u(t) is an applied voltage or current,


$$y(t) = h(t) * u(t) = \int_{-\infty}^{\infty} u(\tau)h(t-\tau)d\tau$$

By definition of causality, for all t < 0,

$$h(t) = 0$$





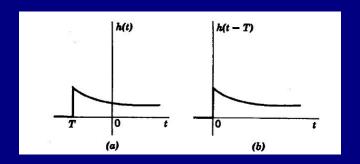

- If the impulse response is causal or non-anticipative, then it is realisable using passive components.
- If the impulse response is non-causal or anticipative, then it is not realisable using passive components.





Theorem (Payley-Wiener)

A necessary and sufficient condition for a function to be realisable (i.e., causal) is that its magnitude function is such that

$$\int_{-\infty}^{\infty} \frac{|\ln|H(j\omega)|}{1+\omega^2} d\omega < \infty$$

- This implies that the amplitude cannot be zero over a finite range of frequencies. For example, the ideal low-pass filter.
- Equivalently, the amplitude function cannot fall off to zero faster than exponential order. For example, $|H(j\omega)| = e^{-\omega^2}$, resulting in $\int_{-\infty}^{\infty} \frac{\omega^2}{1+\omega^2} d\omega = \infty$.





Definition

A network function is said to bounded-input bounded-output (BIBO) stable if the response of the network is bounded for every bounded applied voltage or current.

That is for any u(t) s.t.

$$|u(t)| < m_1 \Longrightarrow |y(t)| < m_2 \quad \forall \ t \in [0, \infty)$$



Definition

A network function is said to bounded-input bounded-output (BIBO) stable if the response of the network is bounded for every bounded applied voltage or current.

That is for any u(t) s.t.

$$|u(t)| < m_1 \Longrightarrow |y(t)| < m_2 \quad \forall \ t \in [0, \infty)$$

Since for a realisable system h(t) = 0 for t < 0,

$$|y(t)| \leq m_1 \int_0^\infty |h(\tau)| d\tau < \infty$$

- That is the impulse response must be absolutely integrable.
- An important requirement for this is

$$\lim_{t \to \infty} h(t) = 0$$

■ Functions like $\sin \omega t$ are not absolutely integrable.





- Functions like $\sin \omega t$ are not absolutely integrable.
- More generally, the impulse responses of network functions with poles on the imaginary axis or in the right-half of s-plane are not absolutely integrable.





- Functions like $\sin \omega t$ are not absolutely integrable.
- More generally, the impulse responses of network functions with poles on the imaginary axis or in the right-half of s-plane are not absolutely integrable.
- Network functions with poles in the left-half of *s*-plane and simple poles on the imaginary axis are called marginally stable.





- Functions like $\sin \omega t$ are not absolutely integrable.
- More generally, the impulse responses of network functions with poles on the imaginary axis or in the right-half of s-plane are not absolutely integrable.
- Network functions with poles in the left-half of *s*-plane and simple poles on the imaginary axis are called marginally stable.
- Otherwise, they are said to be unstable.





- \blacksquare Functions like $\sin \omega t$ are not absolutely integrable.
- More generally, the impulse responses of network functions with poles on the imaginary axis or in the right-half of s-plane are not absolutely integrable.
- Network functions with poles in the left-half of s-plane and simple poles on the imaginary axis are called marginally stable.
- Otherwise, they are said to be unstable.
- For network functions of passive linear time-invariant networks with lumped parameters, stability implies causality.





Definition (Kuo, p. 295)

A polynomial with real coefficients is said to be Hurwitz if all its poles have real parts which are zero or negative.

■ This is an archaic definition.





Definition (Kuo, p. 295)

A polynomial with real coefficients is said to be Hurwitz if all its poles have real parts which are zero or negative.

This is an archaic definition.

More correctly.

Definition (Van Valkenburg, Network Synthesis, 1960, p. 86)

A polynomial with real coefficients is said to be Hurwitz if all its poles have real parts which are negative.





Definition (Kuo, p. 295)

A polynomial with real coefficients is said to be Hurwitz if all its poles have real parts which are zero or negative.

■ This is an archaic definition.

More correctly,

Definition (Van Valkenburg, Network Synthesis, 1960, p. 86)

A polynomial with real coefficients is said to be Hurwitz if all its poles have real parts which are negative.

- This definition shall be used here.
- The class of polynomials following Kuo's definition can be called as modified Hurwitz polynomials.
- The class of polynomials following the latter definition can be called strictly Hurwitz polynomials.



- A necessary condition for a polynomial to be Hurwitz is that none of the coefficients should be zero.
- A necessary condition for a polynomial to be modified Hurwitz is that none of the coefficients should be zero. If any coefficient is zero, then the coefficients of all the even powers of the odd powers are zeros.





- A necessary condition for a polynomial to be Hurwitz is that none of the coefficients should be zero.
- A necessary condition for a polynomial to be modified Hurwitz is that none of the coefficients should be zero. If any coefficient is zero, then the coefficients of all the even powers of the odd powers are zeros.
- Specifically, the odd and even parts of a modified Hurwitz polynomial have roots on the imaginary axis.





■ Let P(s) be a polynomial. Then

$$P(s) = p_o(s) + p_e(s)$$

where $p_o(s)$ contains all the odd powers of P(s) and $p_e(s)$ contains all the even powers of P(s).





■ Let P(s) be a polynomial. Then

$$P(s) = p_o(s) + p_e(s)$$

where $p_o(s)$ contains all the odd powers of P(s) and $p_e(s)$ contains all the even powers of P(s).

■ Observe that $p_o(s)$ is an odd function and $p_e(s)$ an even function.





■ Let P(s) be a polynomial. Then

$$P(s) = p_o(s) + p_e(s)$$

where $p_o(s)$ contains all the odd powers of P(s) and $p_e(s)$ contains all the even powers of P(s).

- Observe that $p_o(s)$ is an odd function and $p_e(s)$ an even function.
- Consider the continued fraction expansion of either $\frac{p_o(s)}{p_o(s)}$ or $\frac{p_e(s)}{p_o(s)}$.





■ Let P(s) be a polynomial. Then

$$P(s) = p_o(s) + p_e(s)$$

where $p_o(s)$ contains all the odd powers of P(s) and $p_e(s)$ contains all the even powers of P(s).

- Observe that $p_o(s)$ is an odd function and $p_e(s)$ an even function.
- Consider the continued fraction expansion of either $\frac{p_o(s)}{p_e(s)}$ or $\frac{p_e(s)}{p_o(s)}$.
- The polynomial is modified Hurwitz if all the quotient polynomials are positive.
- The CFE is finite in length.





$$P(s) = s^4 + s^3 + 5s^2 + 3s + 4:$$





$$P(s) = s^4 + s^3 + 5s^2 + 3s + 4$$
:

$$P(s) = s + rac{1}{rac{s}{2} + rac{1}{2s + rac{1}{s/4}}}$$





$$P(s) = s^4 + s^3 + 5s^2 + 3s + 4$$
:

$$P(s) = s + rac{1}{rac{s}{2} + rac{1}{2s + rac{1}{s/4}}}$$

$$P(s) = s^4 + s^3 + 2s^2 + 3s + 2:$$





$$P(s) = s^4 + s^3 + 5s^2 + 3s + 4:$$

$$P(s) = s + rac{1}{rac{s}{2} + rac{1}{2s + rac{1}{s/4}}}$$

$$P(s) = s^4 + s^3 + 2s^2 + 3s + 2:$$

$$P(s) = s + \frac{1}{-s + \frac{1}{-\frac{s}{5} + \frac{1}{5s/2}}}$$





■ More generally, if the CFE of P(s) yields positive quotient terms, then P(s) is modified Hurwitz to within a multiplicative factor W(s):

$$P(s) = W(s)P_1(s)$$

where $P_1(s)$ is modified Hurwitz and W(s) is a factor common between $p_e(s)$ and $p_o(s)$.





 \blacksquare More generally, if the CFE of P(s) yields positive quotient terms, then P(s) is modified Hurwitz to within a multiplicative factor W(s):

$$P(s) = W(s)P_1(s)$$

where $P_1(s)$ is modified Hurwitz and W(s) is a factor common between $p_e(s)$ and $p_o(s)$.

Example:
$$P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$$
:





■ More generally, if the CFE of P(s) yields positive quotient terms, then P(s) is modified Hurwitz to within a multiplicative factor W(s):

$$P(s) = W(s)P_1(s)$$


where $P_1(s)$ is modified Hurwitz and W(s) is a factor common between $p_e(s)$ and $p_o(s)$.

 Example:
$$P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$$
:

$$P(s) = \frac{s}{2} + \frac{1}{\frac{4s}{3} + \frac{1}{\frac{3s}{2}(s^4 + 4)}}$$







$$P(s) = s^3 + 2s^2 + 3s + 6$$
:





 $P(s) = s^3 + 2s^2 + 3s + 6$: The CFE terminates after the first step with quotient term s/2. Note that

$$W(s) = s^3 + 3s = s(s^2 + 3)$$

is modified Hurwitz and hence P(s) is also modified Hurwitz.



 $P(s) = s^3 + 2s^2 + 3s + 6$: The CFE terminates after the first step with quotient term s/2. Note that

$$W(s) = s^3 + 3s = s(s^2 + 3)$$

is modified Hurwitz and hence P(s) is also modified Hurwitz.

■ What if P(s) is an odd or even function?





■ $P(s) = s^3 + 2s^2 + 3s + 6$: The CFE terminates after the first step with quotient term s/2. Note that

$$W(s) = s^3 + 3s = s(s^2 + 3)$$

is modified Hurwitz and hence P(s) is also modified Hurwitz.

- What if P(s) is an odd or even function?
- Determine the CFE of P(s)/P'(s), and draw appropriate conclusions.
- **Example:** $P(s) = s^7 + 3s^5 + 2s^3 + s$.





Definition

A function H(s) is positive real (PR) if


- **1** H(s) is real for real s.
- **2** For all s with Re $s \ge 0$,

Re
$$H(s) \geq 0$$

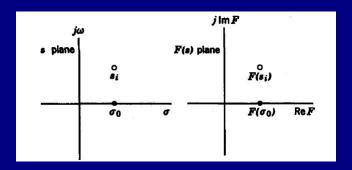- These represent physically realisable passive driving-point immittances.
- The first condition is obvious if H(s) has real coefficients.







- The first condition indicates that the real axis of the s-plane maps onto the real axis of the F(s)-plane.
- The second condition indicates that the right half of the s-plane maps onto the right half of the F(s)-plane.





Examples:

■ Ls.





Examples:

- Ls.
- *R*.





Examples:

- Ls.
- *R*.
- $\blacksquare \frac{1}{Cs}$.





- If H(s) is PR, so is $\frac{1}{H(s)}$.
- Therefore, if a driving point admittance is PR, then the corresponding driving-point impedance is PR.





- If H(s) is PR, so is $\frac{1}{H(s)}$.
- Therefore, if a driving-point admittance is PR, then the corresponding driving-point impedance is PR.
- If $H_1(s)$ and $H_2(s)$ are PR, so is $H_1(s) + H_2(s)$.
- Examples: Two impedances in series or two admittances in parallel.





- If H(s) is PR, so is $\frac{1}{H(s)}$.
- Therefore, if a driving-point admittance is PR, then the corresponding driving-point impedance is PR.
- If $H_1(s)$ and $H_2(s)$ are PR, so is $H_1(s) + H_2(s)$.
- Examples: Two impedances in series or two admittances in parallel.
- The poles and zeros are real or complex conjugate pairs.
- The poles and zeros cannot have positive real parts.
- Only simple poles are permitted on the imaginary axis, and with real and positive residues.





- If H(s) is PR, so is $\frac{1}{H(s)}$.
- Therefore, if a driving-point admittance is PR, then the corresponding driving-point impedance is PR.
- If $H_1(s)$ and $H_2(s)$ are PR, so is $H_1(s) + H_2(s)$.
- Examples: Two impedances in series or two admittances in parallel.
- The poles and zeros are real or complex conjugate pairs.
- The poles and zeros cannot have positive real parts.
- Only simple poles are permitted on the imaginary axis, and with real and positive residues.
- The relative degree can be -1, 0, or +1.
- The lowest powers of the denominator and numerator polynomials may differ at most by unity. This prevents multiple poles or zeros at the origin.





Fact

The necessary and sufficient conditions for a real-rational function H(s) to be PR are

- 1 H(s) must have no poles in the right-half of s-plane.
- \blacksquare H(s) may have simples poles on the imaginary axis with real and positive residues.
- **3** Re $H(j\omega) \geq 0$ for all ω .
 - The denominator polynomial of H(s) must be modified Hurwitz.





Examples:

$$H_1(s) = \frac{s+2}{s^2 + 3s + 2}$$





Examples:

$$H_1(s) = \frac{s+2}{s^2 + 3s + 2}$$

$$H_2(s)=\frac{s+1}{s^2+2}$$





Examples:

$$H_1(s) = \frac{s+2}{s^2 + 3s + 2}$$

$$H_2(s)=\frac{s+1}{s^2+2}$$

$$H_3(s) = \frac{s+4}{s^2+2s+1}$$





Examples:

$$H_4(s) = \frac{3s^2 + 5}{s(s^2 + 1)}$$





Examples:

$$H_4(s) = \frac{3s^2 + 5}{s(s^2 + 1)}$$

$$H_6(s) = \frac{s^2 + 2s + 25}{s^2 + 5s + 16}$$





Examples:

$$H_4(s) = \frac{3s^2 + 5}{s(s^2 + 1)}$$

$$H_6(s) = \frac{s^2 + 2s + 25}{s^2 + 5s + 16}$$





Basic Philosophy:

- Driving-point functions are broken into a sum of simpler PR functions.
- The simpler PR functions are synthesised.





Basic Philosophy:

- Driving-point functions are broken into a sum of simpler PR functions.
- The simpler PR functions are synthesised.

$$H(s) = H_1(s) + H_2(s) + \cdots + H_n(s)$$

- Each H_i must be PR.
- Given the RHS, the synthesis procedure is easier.
- Given the LHS, the following can be attempted:
 - PFE of H(s) or 1/H(s) (cleverly done!).
 - Removing min Re $H(j\omega)$ so that the remainder is PR.





Examples:

$$H_1(s) = \frac{s^2 + 2s + 6}{s(s+3)} =$$





Examples:

$$H_1(s) = \frac{s^2 + 2s + 6}{s(s+3)} = \frac{2}{s} + \frac{s}{s+3} = \frac{2}{s} + \frac{1}{1 + \frac{3}{s}}$$






Examples:

$$H_1(s) = \frac{s^2 + 2s + 6}{s(s+3)} = \frac{2}{s} + \frac{s}{s+3} = \frac{2}{s} + \frac{1}{1 + \frac{3}{s}}$$

assuming $H_1(s)$ is an impedance.

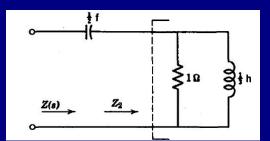





$$H_2(s) = \frac{7s+2}{2s+4} =$$





$$H_2(s) = \frac{7s+2}{2s+4} = \frac{1}{2} + \frac{3s}{s+2}$$





$$H_2(s) = \frac{7s+2}{2s+4} = \frac{1}{2} + \frac{3s}{s+2}$$


after removing the min Re $H(j\omega)$.





$$H_2(s) = \frac{7s+2}{2s+4} = \frac{1}{2} + \frac{3s}{s+2}$$

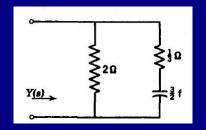after removing the min Re $H(j\omega)$. Assuming $H_2(s)$ is an admittance.







$$H_3(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s} =$$





$$H_3(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s} = 1 + \frac{3s^2 + 1}{6s^3 + 3s}$$





$$H_3(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s} = 1 + \frac{3s^2 + 1}{6s^3 + 3s}$$

after removing the min Re $H(i\omega)$.





$$H_3(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s} = 1 + \frac{3s^2 + 1}{6s^3 + 3s}$$

after removing the min Re $H(j\omega)$. Assuming $H_3(s)$ is an impedance,

$$\frac{6s^3 + 3s}{3s^2 + 1} = 2s + \frac{1}{3s + \frac{1}{s}}$$





$$H_3(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s} = 1 + \frac{3s^2 + 1}{6s^3 + 3s}$$

after removing the min Re $H(j\omega)$. Assuming $H_3(s)$ is an impedance,

$$\frac{6s^3 + 3s}{3s^2 + 1} = 2s + \frac{1}{3s + \frac{1}{s}}$$

