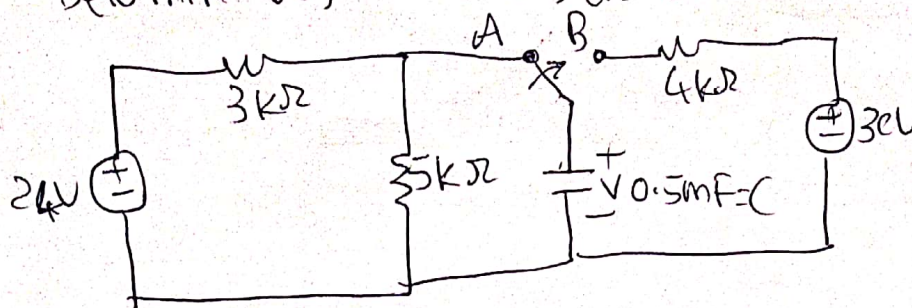


- ① Switch is at position 'A' for a long time. At $t=0$, switch moves to B. Determine $v(t)$ for $t \geq 0$; and calculate $v(t)$ at $t=1s$ and $4sec$.




a) At A: - After a long time 'C' acts like o.c. [at $t \rightarrow \infty$]

$$\therefore V(0^-) = \frac{24 \times 5k}{8k} = 15V = \underline{V(0^+)}$$

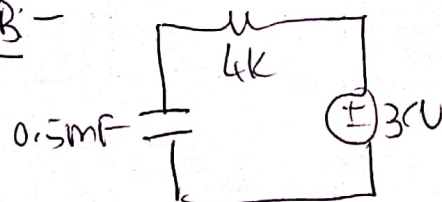b) At $t \rightarrow \infty$ switch at B: -

$$\therefore \underline{V(\infty) = 30V}$$



'C' acts like o.c. at $t \rightarrow \infty$.


$$\therefore V(t) = V(\infty) + [V(0^+) - V(\infty)] e^{-t/RC} \quad RC = 4 \times 10^3 \times 0.5 \times 10^{-3}$$

$$\therefore \underline{V(t) = (30 - 15e^{-0.5t})V}$$


$$\underline{RC = 2sec.}$$

$$\underline{V(1) = 30 - 15e^{-0.5} = 20.9V} \quad \underline{V(4) = 30 - 15e^{-2} = 27.97V}$$

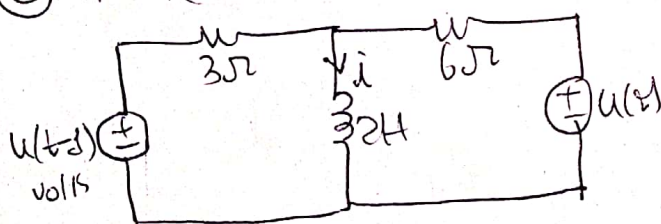- ② For the circuit shown, calculate $i(t)$ if $i(0) = 0A$.


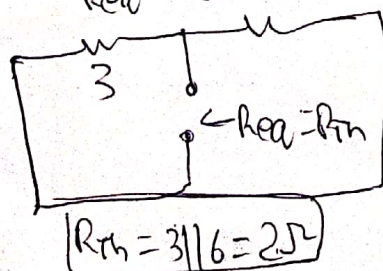
$$\tau = \frac{L}{R_{eq}} = \frac{3}{2} = \underline{1.5sec.}$$



$$\underline{R_{th} = 3 || 6 = 2\Omega}$$

a) For $t < 0$: - $u(t) = 0$ and $u(t) = 0$

$$\therefore \underline{i(0^-) = 0A = i(0^+)}$$

b) For $0 < t < \infty$: - $u(t) = 1V$; $u(t) = 1V$

$$\therefore \underline{i(\infty) = \frac{1}{6}A} \quad ['L' \text{ acts like s.c.}]$$

$$\therefore \underline{i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}} \quad \tau = 1.5sec$$

$$\therefore \underline{i(t) = \frac{1}{6} [1 - e^{-2t}]A}$$


①

c) For $t > 1$: $u(t-1) = 1V$; $u(t) = 1V$

$$i(1) = \frac{1}{6} [1 - e^{-1}] = 0.1053A$$

$$i(\infty) = \frac{1}{3} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2}A$$


'L' acts like s.c.

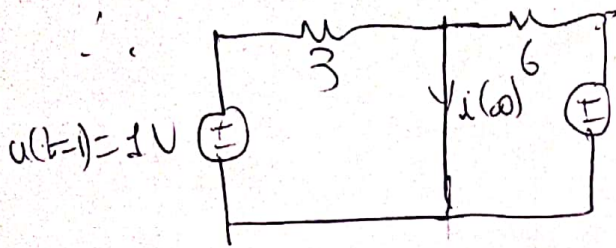

$$i(t) = i(\infty) + [i(1) - i(\infty)] e^{-t/1}$$


$$i(t) = 0.5 - 0.3947 e^{-t} A$$

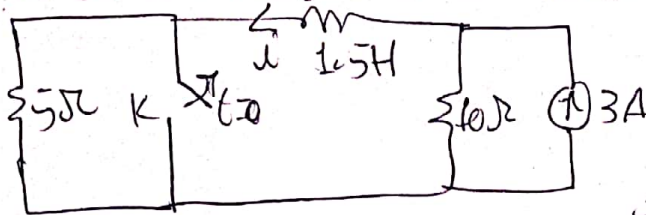3) The switch is closed for a long time, and opened at $t=0$. Find $i(t)$; $t > 0$.



$$i(0^-) = i(0^+) = 3A$$

a) At $t=0^-$: $i(0^-)$

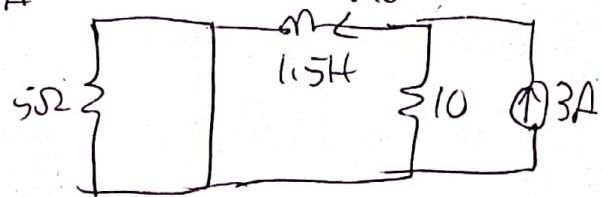


5 ohm shared and 10 ohm also.

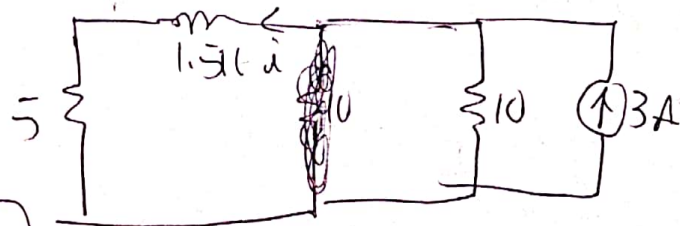5) At $t=0^+$: 'K' is open.

As $t \rightarrow \infty$ 'L' acts like s.c.


$$i(\infty) = \frac{3 \times 10}{5 + 10} = \frac{30}{15} = 2A$$



$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$$

c) $\tau \rightarrow$ time const: - De-activate independent sources and open inductor

Calculate R_{th} at $t=0^+$:

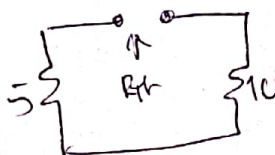


$$R_{th} = 15\Omega$$

$$\tau = \frac{L}{R} = \frac{1.5}{15} = 0.1s$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/0.1}$$


$$i(t) = 2 + [3 - 2] e^{-t/0.1} = 2 + e^{-10t} A$$

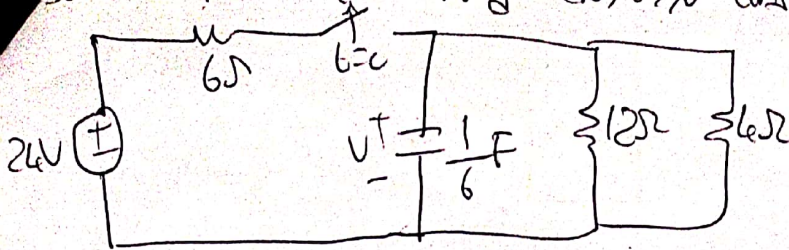switch opens at $t=0$. Find $V_C(t)$, $t > 0$ and $w_C(0)$.



a) When switch 'k' is closed: - $V(0^+) = V(0^-) =$ voltage across C

when s.s. is reached it acts like 0.

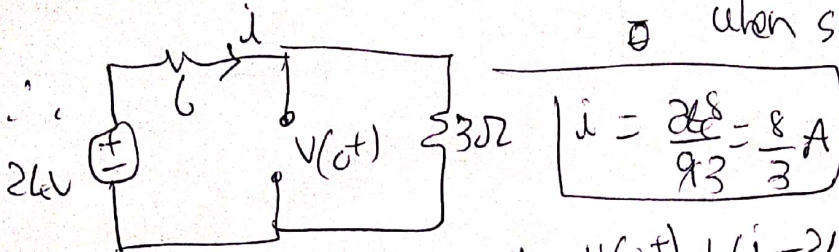


$$i = \frac{24}{9+3} = \frac{8}{3} \text{ A}$$

$$V(0^+) + 6i - 24 = 0$$

$$\therefore V(0^+) = 24 - 6 \times \frac{8}{3} = 24 - 16 = 8 \text{ V}$$

$$\therefore V(0^+) = 24 - 16 = 8 \text{ V}$$

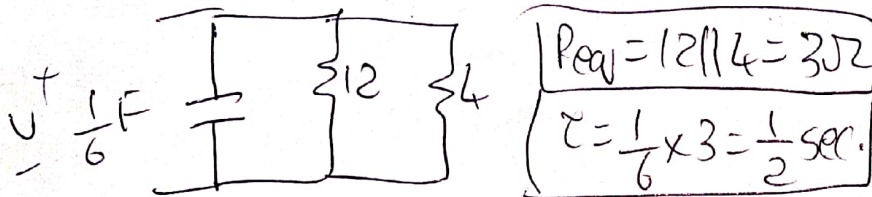b) When 'k' is open: - It is a source-free RC-ckt.



$$R_{eq} = 12 || 12 = 6 \Omega$$


$$\tau = \frac{1}{6} \times 3 = \frac{1}{2} \text{ sec.}$$

$$\therefore V_C(t) = V(0^+) e^{-t/\tau} = 8 e^{-t/1/2} = 8 e^{-2t} \text{ Volts}$$



$$c) w_C(0) = \frac{1}{2} C V(0^+)^2 = \frac{1}{2} \times \frac{1}{6} \times 8^2 = \frac{64}{12} = 5.33 \text{ J}$$

5) The switch is closed for a long time. At $t=0$, the switch is opened.

Calculate $i(t)$, $t > 0$

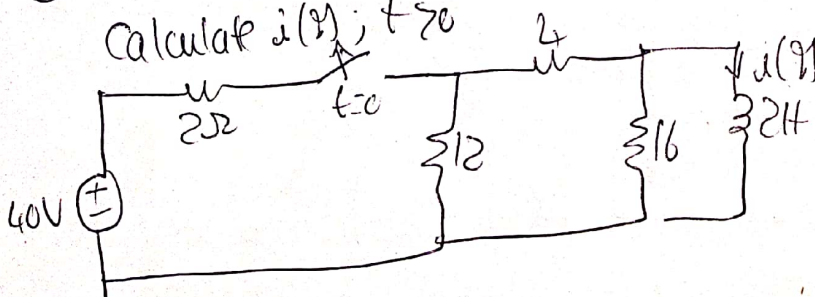


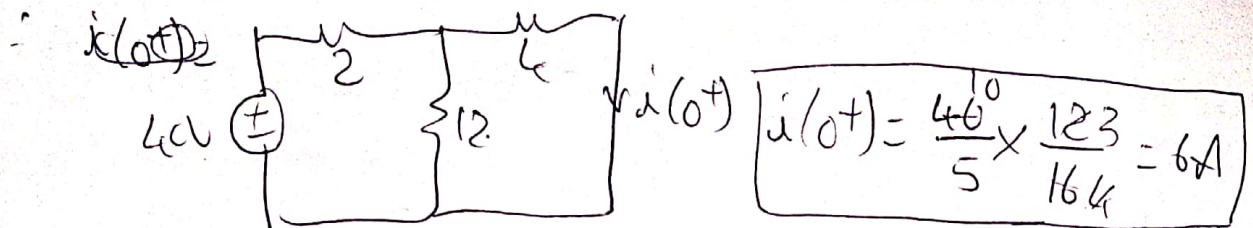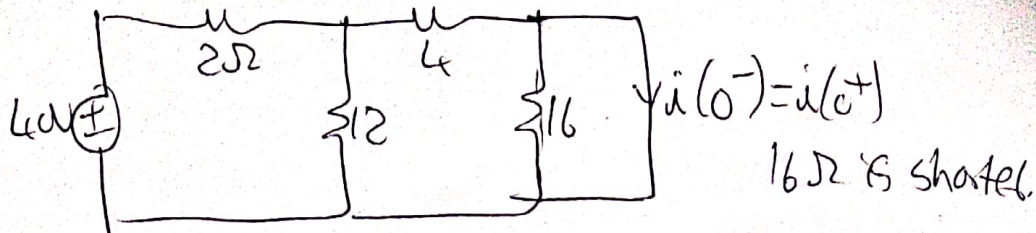a) When 'K' is closed: - For a long time 'L' acts like SC.




$$i(0^+) = \frac{4}{5} \times \frac{123}{164} = 6A$$

b) When 'K' is open: -

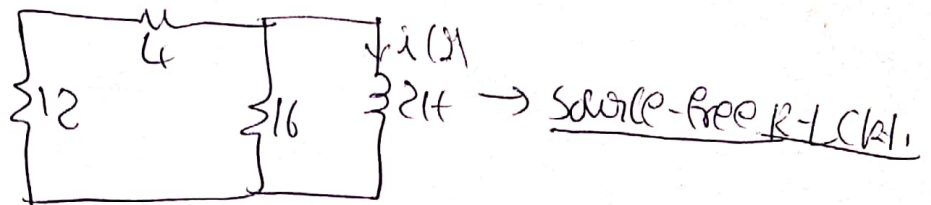


$$\tau = \frac{L}{R_{th}}$$

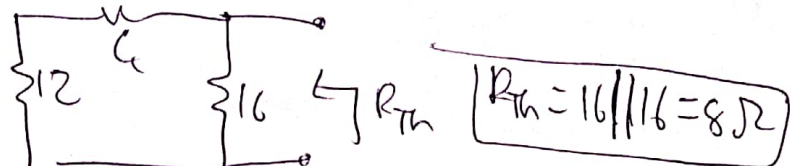

$$\tau = \frac{2}{8} = \frac{1}{4} \text{ sec.}$$

$$i(t) = i(0^+) e^{-t/\tau} = 6 e^{-4t} A$$

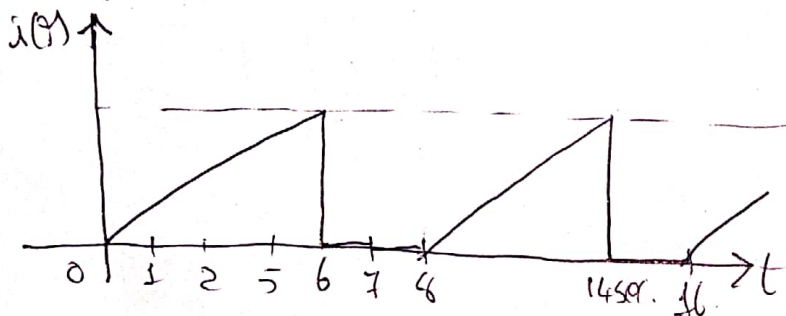6) The current $i(t)$ is as shown in the figure, with a period of 8 sec.
(a) What is the avg. value of current over a single period; (b) If $q(0) = 0$; sketch $q(t)$ $0 \leq t \leq 20s$.



$$T = 8 \text{ sec.}$$

$$(a) i_{avg} = \frac{1}{T} \int_0^T i(t) dt$$

$$\begin{aligned} i(t) &= t; 0 \leq t \leq 6 \text{ sec.} \\ i(t) &= 0; 6 \leq t \leq 8 \text{ sec.} \end{aligned}$$


$$i_{avg} = \frac{1}{8} \int_0^8 i(t) dt = \frac{1}{8} \int_0^6 t dt + \frac{1}{8} \int_6^8 0 dt = \frac{1}{8} \times \frac{t^2}{2} \Big|_0^6$$

$$i_{avg} = \frac{1}{8} \left[\frac{36}{2} \right] = \frac{36}{16} = 2.25 A$$

$$i(t) = \frac{dq(t)}{dt}$$

$$(b) q(t) = \int_0^t i(\tau) d\tau = \int_0^t \tau d\tau = \frac{\tau^2}{2} \Big|_0^t = 0.5 t^2 = 500 t^2 \text{ mC}; 0 \leq t \leq 6$$
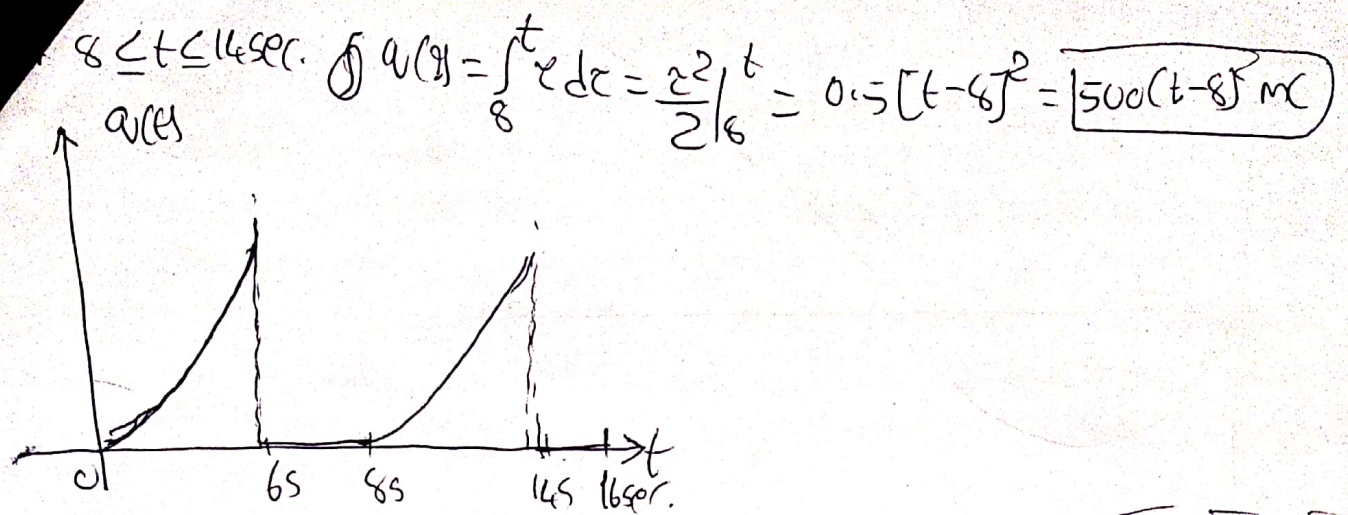
$$= 0; 6 \leq t \leq 8 \text{ sec.} \quad (4)$$



(7) A new type of device accumulates charge according to expression $q(t) = (10t^2 - 22)t \text{ mC}$ (t in sec.) [a] In interval $0 \leq t \leq 5 \text{ sec.}$ at what time does current flow into device is zero.


[b] Sketch $q(t)$ over the interval $0 \leq t \leq 5 \text{ msec.}$ and $i(t)$.


[a] $i(t) = \frac{dq(t)}{dt} = \frac{d}{dt} [10t^2 - 22] \Rightarrow 20t - 22 = 0 \Rightarrow t = 1.1 \text{ sec.}$

[b] $i(t) = (20t - 22) \text{ mA}$


$i(0) = -22 \text{ mA}$	$i(3) = 38 \text{ mA}$
$i(1) = -2 \text{ mA}$	$i(4) = 58 \text{ mA}$
$i(2) = 18 \text{ mA}$	$i(5) = 78 \text{ mA}$

$q(t) = (10t^2 - 22)t \text{ mC}$	
$q(0) = 0$	$q(3) = 24 \text{ mC}$
$q(1) = -12 \text{ mC}$	$q(4) = 72 \text{ mC}$
$q(2) = -4 \text{ mC}$	$q(5) = 100 \text{ mC}$

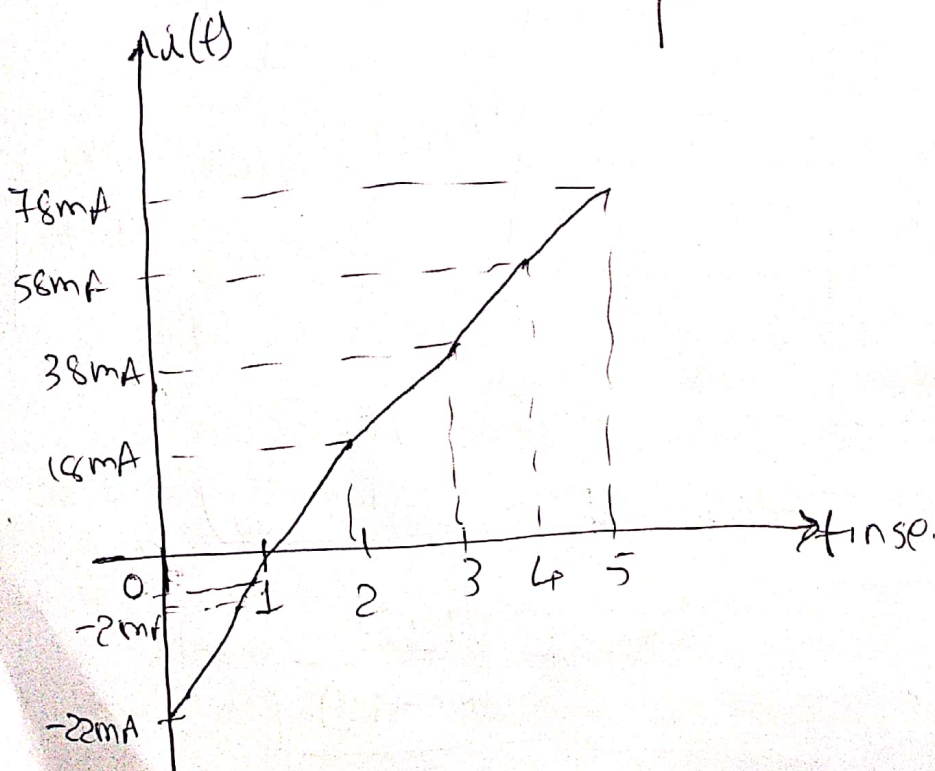

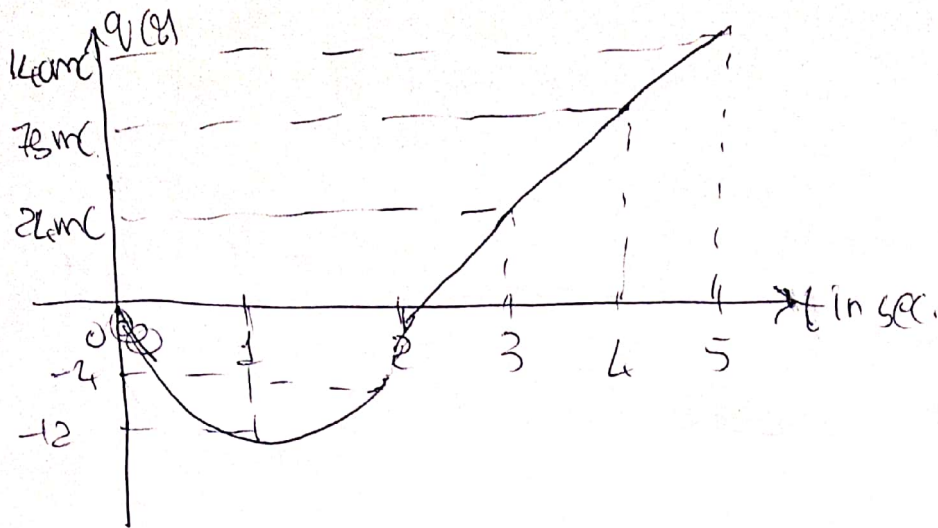


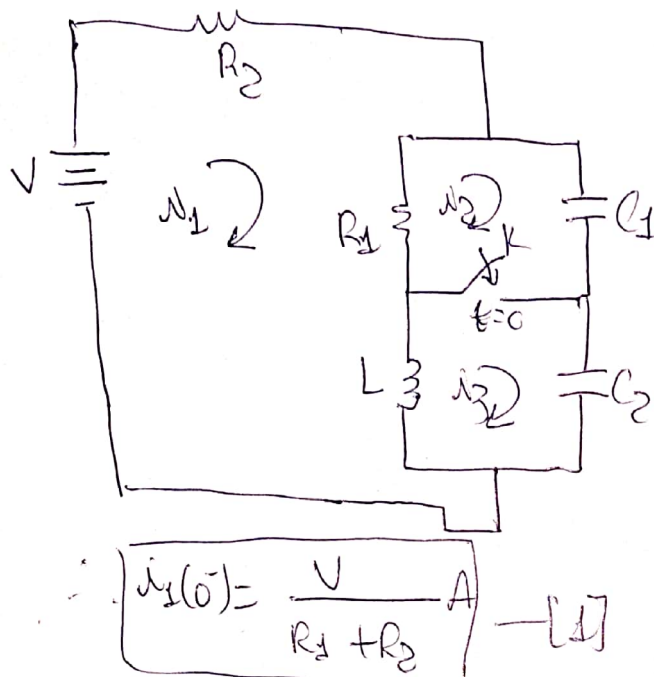Q Find the values of ~~the~~ all loop currents at $t=0^+$, K closed at $t=0$.




$$i_1(0^-) = \frac{V}{R_1 + R_2} \text{ A} \quad \text{--- [1]}$$

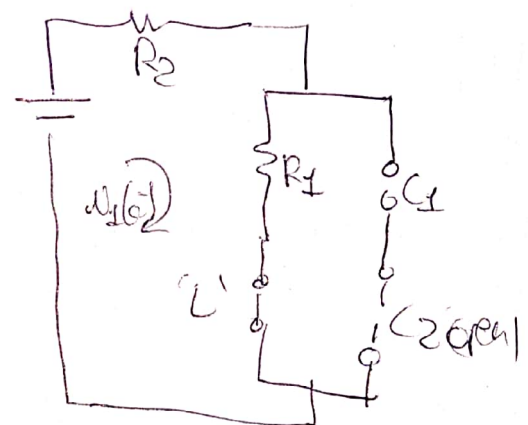a) At $t=0^-$, with steady state reached when 'K' is open
 C_1, C_2 acts like o.c. and 'L' acts like s.c.




b) At $t=0^+$:-

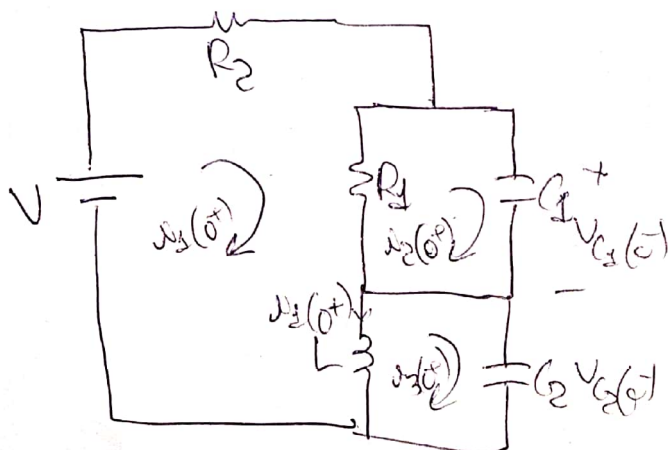

$$V_{C1}(0^-) + V_{C2}(0^-) = \frac{V R_1}{R_1 + R_2} \quad \text{--- [2]}$$

$$V_{C1}(0^+) = \frac{V R_1 C_2}{(C_1 + C_2)(R_1 + R_2)} = V_{C1}(0^-) \quad \text{--- [3] a}$$
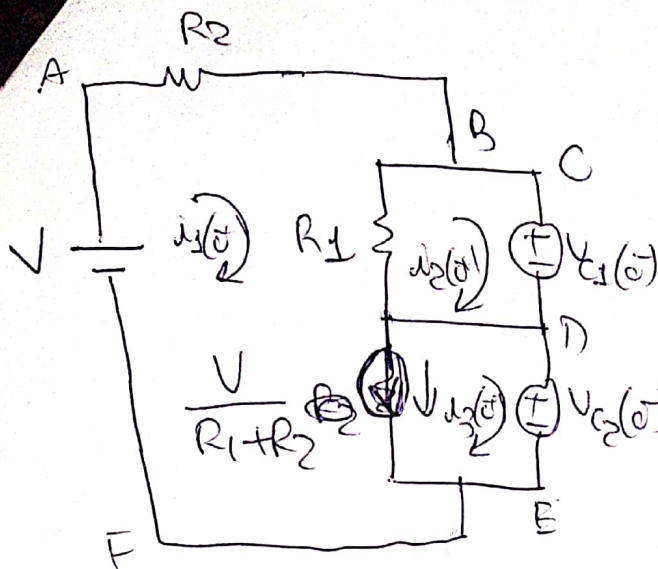
$$V_{C2}(0^+) = \frac{V R_1 C_1}{(C_1 + C_2)(R_1 + R_2)} = V_{C2}(0^-) \quad \text{--- [3] b}$$



Applying KVL for mesh

A-B-C-D-E-F-A :-

$$+V - R_2 i_1(t) - V_{C1}(t) - V_{C2}(t) = 0$$

$$R_2 i_1(t) = V - V_{C1}(t) - V_{C2}(t)$$

~~$$R_2 i_1(t) = V - \frac{V R_1 C_2}{(R_1 + R_2)} - \frac{V R_1 C_1}{R_1 + R_2}$$~~

$$R_2 i_1(t) = V - \frac{V R_1 C_2}{(R_1 + R_2)(C_1 + C_2)} - \frac{V R_1 C_1}{(R_1 + R_2)(C_1 + C_2)}$$

$$\therefore R_2 i_1(t) = \frac{V R_1 C_1 + V R_1 C_2 + V R_2 C_1 + V R_2 C_2 - V R_1 C_2 - V R_1 C_1}{(R_1 + R_2)(C_1 + C_2)}$$

$$\therefore i_1(t) = \frac{V R_2 (C_1 + C_2)}{R_2 (R_1 + R_2)(C_1 + C_2)} = \boxed{\frac{V (C_1 + C_2)}{(R_1 + R_2)(C_1 + C_2)}}$$

$$\therefore i_1(t) - i_3(t) = \frac{V}{R_1 + R_2}$$

$$\therefore i_3(t) = \frac{V}{R_1 + R_2} - \frac{V}{R_1 + R_2} = 0 \text{ A}$$

KVL for mesh-2 :-

$$+V_{C1}(t) + R_1 [i_2(t) - i_1(t)] = 0$$

$$R_1 i_2(t) = R_1 i_1(t) - V_{C_2}(t)$$

$$\therefore R_1 i_2(t) = \frac{R_1 V}{(R_1 + R_2)} - \frac{V R_1 C_2}{(C_1 + C_2)(R_1 + R_2)}$$

$$\therefore R_1 i_2(t) = \frac{V R_1 C_1 + V R_1 C_2 - V R_1 C_2}{(R_1 + R_2)(C_1 + C_2)}$$

$$\therefore \underline{i_2(t)} = \frac{V R_1 C_1}{(R_1 + R_2)(C_1 + C_2) R_1} = \boxed{\frac{V C_1}{(R_1 + R_2)(C_1 + C_2)} A}$$