

Laplace transform:

$$\mathcal{L}[k] = \mathcal{L}[k \cdot u(t)] = \frac{k}{s} \quad \text{LT deals with causal } \rightarrow (\text{from } 0^- \text{ to } \infty) \text{ type function.}$$

$$\mathcal{L}(\cos \omega_0 t \cdot u(t)) \rightarrow \frac{s}{s^2 + \omega_0^2} \quad t \geq 0^-$$

Properties of Laplace transform.

$$f(t) \rightleftharpoons F(s)$$

1) Linearity

$$f_1(t) \rightarrow F_1(s)$$

$$\text{and } f_2(t) \rightarrow F_2(s) \text{ then}$$

$$c_1 f_1(t) + c_2 f_2(t) \rightarrow c_1 F_1(s) + c_2 F_2(s)$$

$\underbrace{\quad}_{\text{Linear comb. of}} f_1(t) + f_2(t)$

2) Differentiation in time domain

$$a) \mathcal{L}\left[\frac{df}{dt}\right]$$

$$\begin{aligned} \int_0^\infty \frac{df}{dt} \cdot e^{-st} \cdot dt &= f(t) \cdot e^{-st} \Big|_0^\infty - \int_0^\infty f(t) \cdot (-s) \cdot e^{-st} \cdot dt \\ &= -f(0^-) e^{0^-} + s \int_0^\infty f(t) \cdot e^{-st} \cdot dt \end{aligned}$$


$$= -f(0^-) + sF(s)$$

$$\mathcal{L}\left[f'(t)\Big|_{t \geq 0^-}\right] = sF(s) - f(0^-) \quad \text{---(i)}$$

$(0^- \text{ to } \infty)$


$$\mathcal{L}\left[f'(t)\Big|_{t \geq 0^+}\right] = sF(s) - f(0^+) \quad \text{---(ii)} \quad (0^+ \text{ to } \infty)$$

Example:

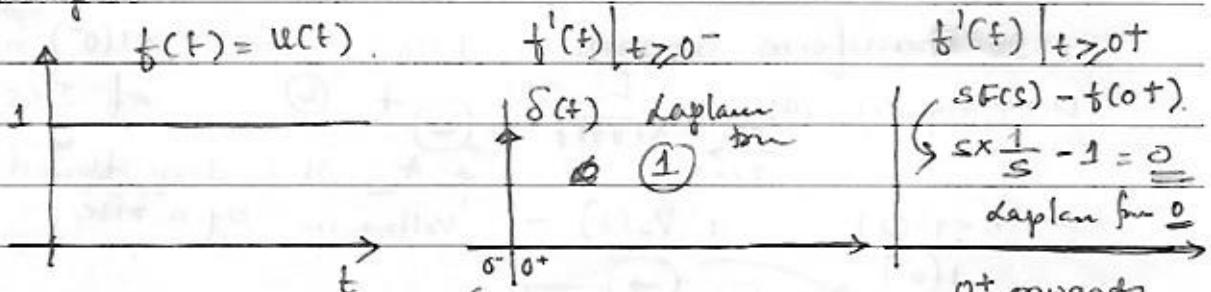

$$\begin{aligned} \mathcal{L}(u(t)) &= \frac{1}{s}, \quad \text{as } F(s) - f(0^-) \\ &= s \cdot \frac{1}{s} - 0 = \underline{\underline{1}} \quad \text{Jumping from } 0^- \text{ to } 0^+; \text{ after } 0^+, \text{ derivative is zero.} \end{aligned}$$

Application

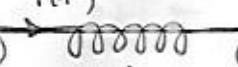$i(t)$ Inductor having L henry carry current $i(t)$
 (a)  (b) and voltage V_L a/c it.
 $+ V_L -$

$$V_L(t) = L \cdot \frac{di}{dt}$$

$$\mathcal{L}(V_L(t)) = L \left[L \cdot \frac{di}{dt} \right] \quad \begin{matrix} \text{Assume } (i(t)) \Rightarrow I(s) \\ \mathcal{L}(V_L(t)) \Rightarrow V_L(s) \end{matrix}$$

$$V_L(s) = L \left[s I(s) - i(0^-) \right]$$

$$V_L(s) = \underbrace{L s I(s)}_{\substack{\uparrow \\ \text{Initial cond.}}} - \underbrace{L i(0^-)}_{\substack{\uparrow \\ \text{Initial cond.}}} \quad \begin{matrix} V_L + i_L - \text{time dom} \\ V_L \& I(s) - s-\text{domain} \\ (\text{LT}) \end{matrix}$$

$V_L(t)$ from
 0^- to ∞

$$L s I(s) = V_L(s) + L i(0^-)$$

$$\left[I(s) = \left(\frac{V_L(s)}{L s} \right) + \frac{i(0^-)}{s} \right] \quad -(2)$$


(1) & (2) Initial cond's of inductor need to be known.

Provided initial current $i(0^-) = 0$.


$$\left. \begin{array}{l} V_L(s) = (L s) I(s) \\ I(s) = \frac{V_L(s)}{(L s)} \end{array} \right\} \quad -(3)$$

If a current $I(s)$ flows through a inductor, then $V_L(s) = (L s)$ times $I(s)$ where $(L s)$ is regarded as generalized impedance of inductance in transform domain.

If a voltage a/c inductor is $V_L(s)$, then its current through inductor is $V_L(s)/(L s)$ where $(\frac{1}{L s})$ is admittance of inductance in transform domain.

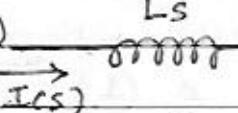In transform domain $L i(0^-)$ $i(0^-)$ is independent w.r.t eq: (1) (a)  (b) of $I(s)$.

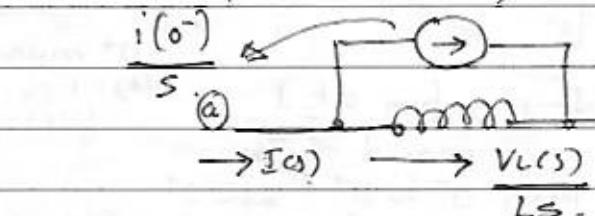w.r.t eq: (2) $+ V_L(s) -$ It is drop flowed voltage rise by a rise.




$(L s)$ - generalized impedance of inductance

DATE

Transform Impedance and admittance

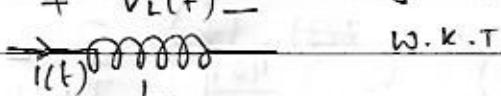a) Inductance : Inductance of L Henry carry current $i(t)$ and voltage acc if $V_L(t)$ [induced voltage]



W.K.T

$$V_L(t) = L \cdot \frac{di}{dt} \quad \text{--- (1)}$$

Laplace transform of $V_L(t)$

$$\mathcal{L}(V_L(t)) = L \mathcal{L}\left(\frac{di}{dt}\right)$$

$$= L \left[s I(s) - i(0^-) \right]$$

$$[V_L(s) = LS I(s) - L i(0^-)] \quad \text{--- (2)}$$

from (2)

$$LS I(s) = V_L(s) + L \cdot i(0^-)$$

$$I(s) = \frac{V_L(s) + L \cdot i(0^-)}{LS}$$

$$\begin{aligned} I(s) &= \frac{V_L(s)}{LS} + \frac{i(0^-)}{S} \\ &= I_L(s) + \frac{i(0^-)}{S} \end{aligned} \quad \text{--- (3)}$$

where $I(s)$ LT of $i(t)$

In eq 2 (2) & (3)

 $V_L(s)$ LT of $V_L(t)$ and $i(0^-)$ is a constant
does not depend on Impedance $i(0^-)$ - Initial current inductor.With practical condⁿ of inductor known $V_L(s)$, $I(s)$ can be computedProvided initial condⁿ are zero, ie $i(0^-) = 0$, eq 2 (2) (3) reduce

$$V_L(s) = LS I(s) \quad \boxed{\quad} \quad \text{--- (4)}$$

$$I(s) = \frac{V_L(s)}{LS} \quad \boxed{\quad} \quad \text{--- (4)}$$


If current $I(s)$ flows through inductor of L Henry, then,
 $V_L(s)$ is LS times $I(s)$ where LS is transform form impedance of inductance

If $V_L(s)$ is voltage acc inductor of L Henry then,
 $I(s)$ is $(\frac{1}{LS})$ times $V_L(s)$ when $\frac{1}{LS}$ is transform form of admittance of inductance.

Impedance of inductor = LS & Admittance of inductor = $\frac{1}{LS}$

DATE

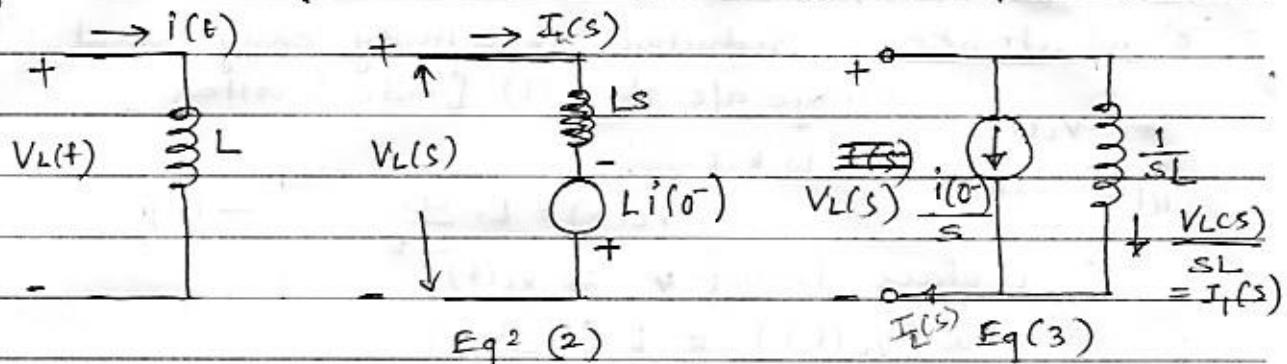Eq(2) and (3) representations using transform diagram.



$$V_L(s) = I_L(s)Ls + L \cdot i(0^-) \quad I_L(s) = \frac{V_L(s)}{Ls} + \frac{i(0^-)}{s}$$

b) Capacitor : A capacitor with capacitance of C Farads, having $V_C(t)$ as the voltage acr. it with charge $q(t)$

$$V_C(t) = \frac{q(t)}{C} = q(0^-) + \int_{0^-}^t i \cdot dt$$

$$= \frac{q(0^-)}{C} + \frac{1}{C} \int_{0^-}^t i \cdot dt$$

$$\boxed{V_C(t) = V_C(0^-) + \frac{1}{C} \int_{0^-}^t i \cdot dt} \quad -(1)$$

$V_C(0^-)$ - is a constant

Voltage due to

definite integral
Extra charge deposited
initial charges on cap at $t=0^-$
(constant)

Now LT on eq 2 (1)

$$V_C(s) = \frac{V_C(0^-)}{s} + \frac{1}{C} \left(\frac{I(s)}{s} \right)$$

$\frac{1}{Cs}$ Impedance
of Cap.

$$\boxed{V_C(s) = \frac{I(s)}{Cs} + \frac{V_C(0^-)}{s}} \quad -(2)$$

Now, $I(s)$ can be derived

Initial voltage

$$I(s) = \frac{V_C(s) - V_C(0^-)}{Cs}$$

$$I(s) = Cs \left[V_C(s) - \frac{V_C(0^-)}{s} \right]$$


$$\boxed{I(s) = Cs V_C(s) - \frac{Cs \cdot V_C(0^-)}{s}} \quad -(3)$$

admittance
of Capacitor

Initial current

DATE

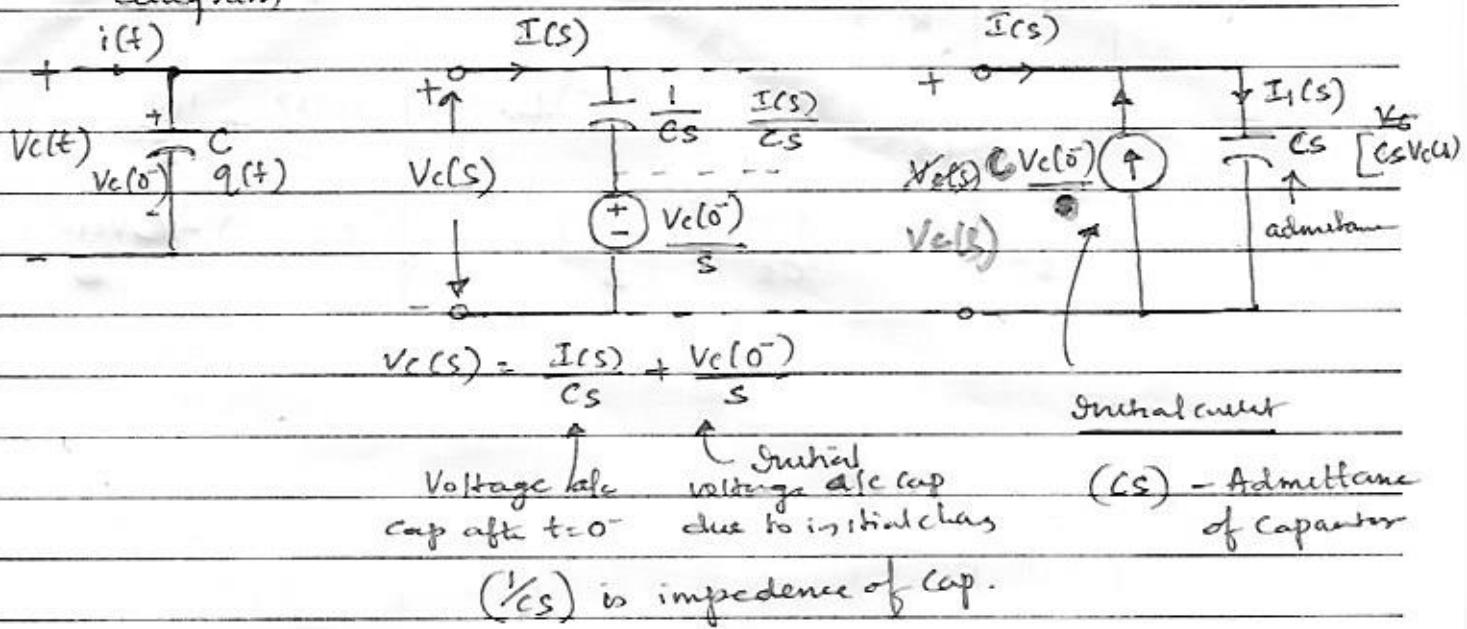Eq 2 (2) and (3) can be pictorially represented by transform diagram




$V_c(s) = \frac{I(s)}{Cs} + \frac{V_c(0)}{s}$

Voltage drop across cap after $t=0^-$ due to initial charge

$(\frac{1}{Cs})$ - Admittance of Capacitor

$(\frac{1}{Cs})$ is impedance of cap.

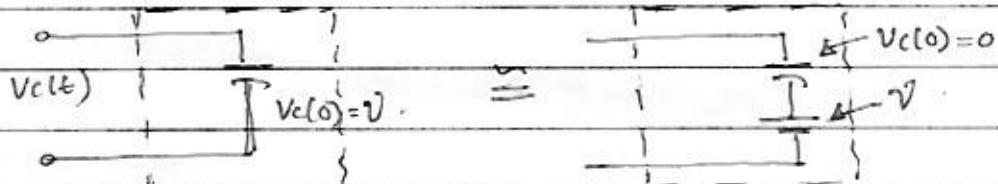

Capacitor with initial voltage $V_c(0) = V$ \equiv Capacitor with initial voltage $V_c(0) = 0$ with a series connected voltage source $= V$.

\rightarrow In transform domain

If 0^- conditions are known, substitution of 0^+ conditions the response can be found directly as it takes care of transition from 0^- to 0^+ automatically. \therefore There is no need to know condns at 0^+ if 0^- condns are known.

c) Resistor : Resistor with resistance R with voltage $V(t)$

across it having $i(t)$ flowing through it

$$\begin{array}{ccc} i(t) & R & I(s) \\ \xrightarrow{\text{LT}} & \xrightarrow{R = \frac{V(t)}{i(t)}} & \xrightarrow{\text{LT}} \\ + V(t) & - & + V(s) \end{array} \quad R = \frac{V(s)}{I(s)}$$


$$\frac{d}{dt} \left| \frac{V(t)}{i(t)} \right|_{\text{zero initial cond.}} = \frac{V(s)}{I(s)} = \begin{cases} R & \text{if } x = \text{Resistor} \\ Ls & \text{if } x = \text{Inductor} \\ \frac{1}{Cs} & \text{if } x = \text{Capacitor} \end{cases}$$

$$\frac{i(t)}{V(t)} \xrightarrow{\text{LT}} \frac{1}{x}$$


DATE

Element	Impedance	Admittance	$V(s)$	$I(s)$
R	R	$\frac{1}{R}$	$I(s) R$	$V_s(s)/R$
L	LS	$\frac{1}{LS}$	$I(s) LS - i(0^+) L$	$\underline{V_L(s)} + \frac{i(0^+)}{S}$
C	$\frac{1}{CS}$	CS	$\frac{I(s)}{CS} + \frac{V_c(0^+)}{S}$	$CS V_c(s) - \underline{C V_c(0^+)}$


DATE _____

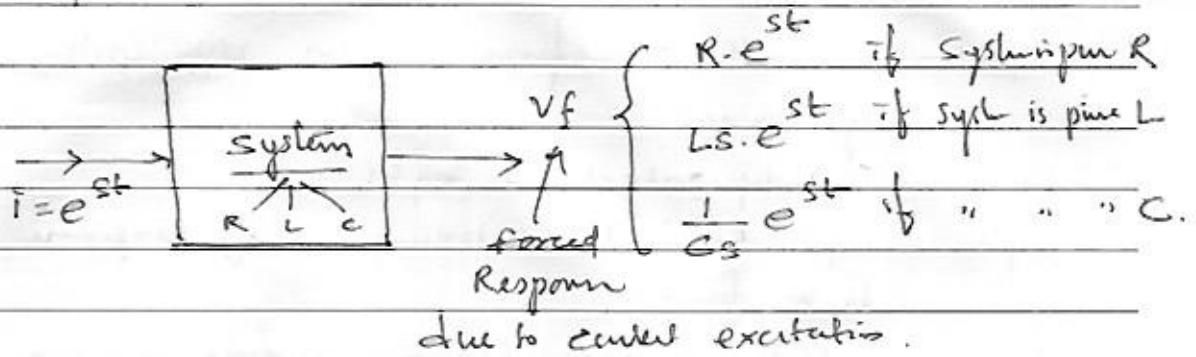

- phasor diagram & B.R.J.W.

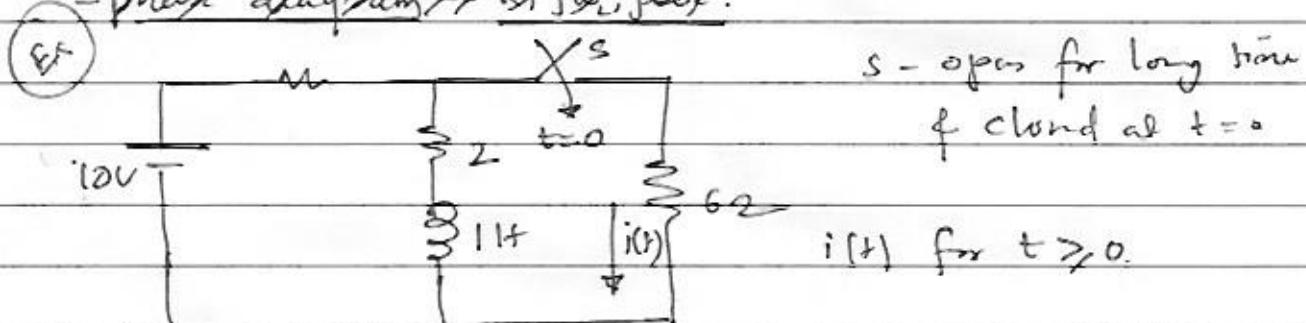

Transformed

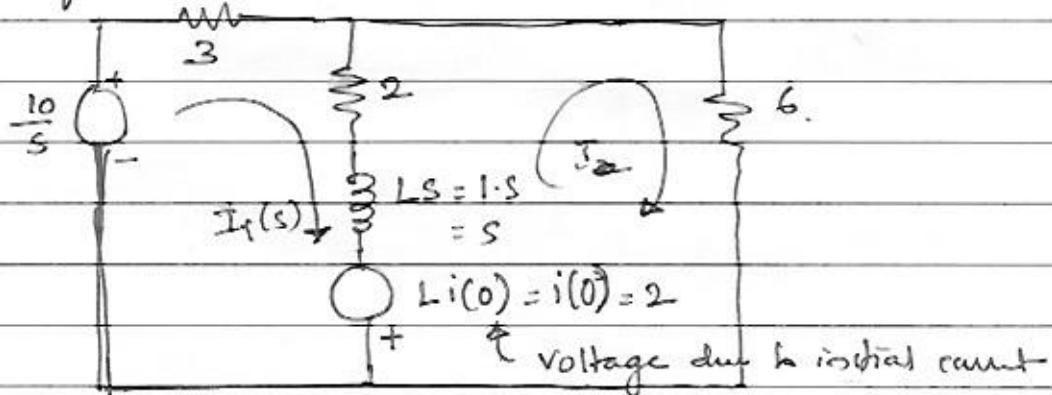

$$\text{Initial current} = \frac{10}{s+2} = 2 \text{ A}$$

$$3I_1(s) + 2[I_1(s) - I_2(s)]$$

$$3I_1(s) + (2+s)[I_1(s) - I_2(s)] - 2 - \frac{10}{s} = 0$$

$$3I_1(s) + 2I_1(s) - 2I_2(s) + sI_1(s) - sI_2 = \frac{10}{s} + 2$$

$$5I_1(s) - sI_2(s)$$

$$(5+s)I_1(s) - (2+s)I_2(s) = \frac{10}{s} + 2 \quad (1)$$

$$(2+s)[I_2(s) - I_1(s)] + 6I_1(s) + 2 = 0$$

$$(8+s)I_1(s) - (2+s)I_2(s) = -2 \quad (2)$$

By solving

$$I_1(s) = \frac{20/s + 4}{9(s+4)} = \frac{4s+20}{9s(s+4)}$$

$$i(t) = \frac{5}{9} - \frac{1}{9}e^{-4t}$$

$$\text{Using partial fraction } \frac{5/9}{s} - \frac{1/9}{s+4}$$


DATE

Step 1 - Setup the transform diagram with initial cond: replaced by sources.


Step 2 - Set up algebraic eq's.

Step 3 - Get the Laplace transform of response quantity to be found

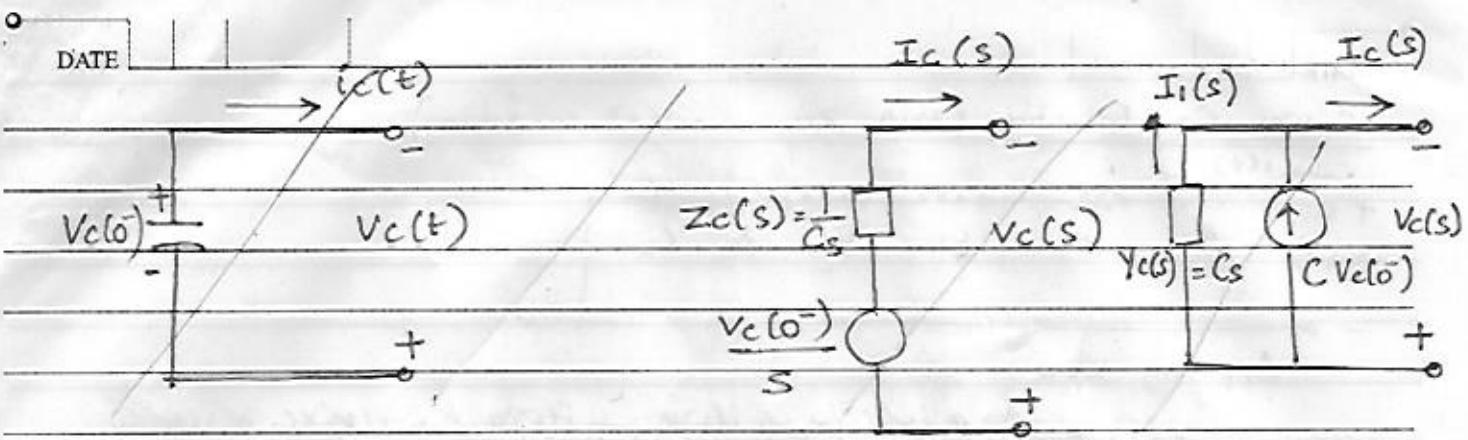Step 4 - ILT to get Response in time domain



Mutual Coupled Coils

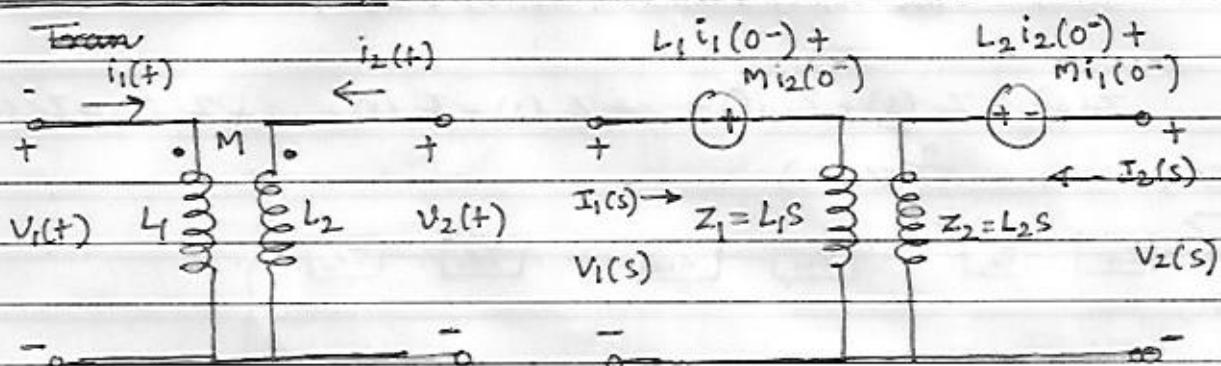

$$V_1(+)=L_1 \cdot \frac{di_1(+)}{dt} + M \cdot \frac{di_2(+)}{dt}$$

$$\begin{aligned} V_1(s) &= L_1(sI_1(s) - i_1(0^-)) + M(sI_2(s) - M i_2(0^-)) \\ &= M s I_2(s) - M i_2(0^-) + L_1 s I_1(s) - L_1 i_1(0^-) \end{aligned}$$

11th

$$V_2(t)=L_2 \cdot \frac{di_2(t)}{dt}+m \cdot \frac{di_1(t)}{dt}$$

$$V_2(s)=L_2(sI_2(s)-i_2(0^-))+m(sI_1(s)-i_1(0^-))$$

$$\therefore = M s I_1(s) - m i_1(0^-) + L_2 s I_2(s) - L_2 i_2(0^-)$$

Remarks


- for single elements, under zero initial conditions, the transform impedance is the ratio of the transform of the element voltage to the transform of the element current

$$Z(s) = \frac{\mathcal{L}[V(t)]}{\mathcal{L}(i(t))} = \frac{V(s)}{I(s)}$$

- Under zero initial conditions, the reciprocal ratio transform admittance
- Initial conditions are represented by transform voltage sources or current sources.

DATE

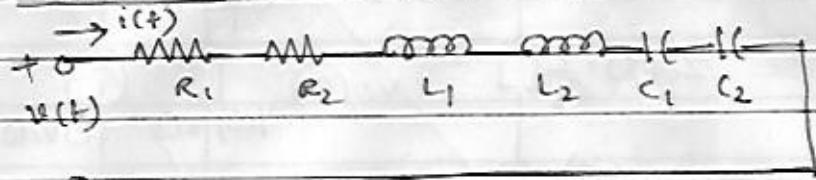Series Combination (with zero initial condition)




Applying KVL

$$V(t) = i(t)R_1 + i(t)R_2 + i(t)L_1 + i(t)L_2 + i(t)C_1 + i(t)C_2$$

$$V(s) = Z_{R1}(V_{R1}(s) + V_{R2}(s) + V_{L1}(s) + V_{L2}(s) + \dots + V_{C1}(s) + V_{C2}(s))$$

$$Z(s) = Z_{R1}(s) + Z_{R2}(s) + \dots + Z_{L1}(s) + Z_{L2}(s) + \dots + Z_{C1}(s) + Z_{C2}(s)$$


$$I(s) = \sum_{k=1}^n Z_k(s)$$

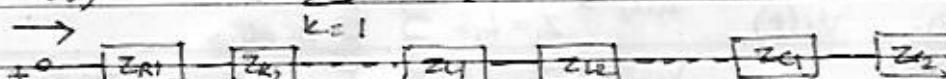

$$V(s)$$

$$\therefore V(s) = I(s) \sum_{k=1}^n Z_k(s) = I(s)(Z_{R1}(s) + Z_{R2}(s) + \dots + Z_{L1}(s) + Z_{L2}(s) + \dots + Z_{C1}(s) + Z_{C2}(s))$$

Parallel comb?

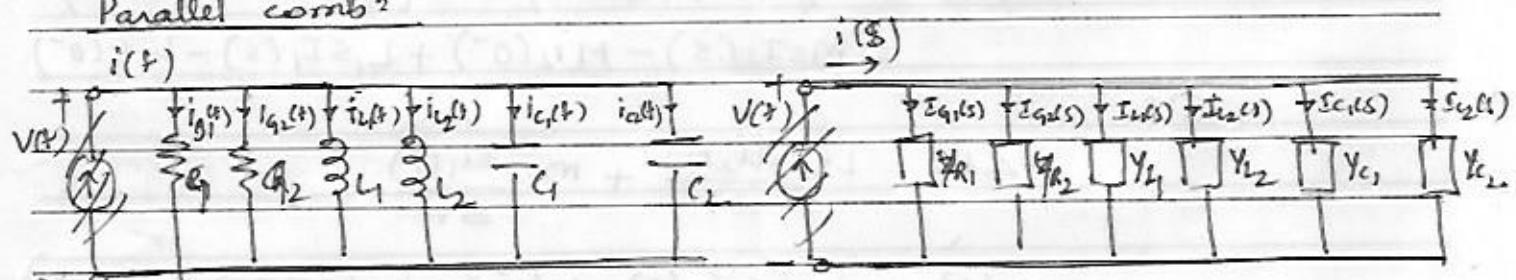

By applying KCL

$$i(t) = I_{g1}(t) + I_{g2}(t) + i_{L1}(t) + i_{L2}(t) + i_{C1}(t) + i_{C2}(t)$$

corresponding transform eq 2

$$I(s) = I_{g1}(s) + I_{g2}(s) + I_{L1}(s) + I_{L2}(s) + I_{C1}(s) + I_{C2}(s)$$

$$= \frac{V(s)}{Z_{R1}(s)} + \frac{V(s)}{Z_{R2}(s)} + \frac{V(s)}{Z_{L1}(s)} + \frac{V(s)}{Z_{L2}(s)} + \frac{V(s)}{Z_{C1}(s)} + \frac{V(s)}{Z_{C2}(s)}$$


$$I(s) = V(s) [Y_{g1}(s) + Y_{g2}(s) + \dots + Y_{L1}(s) + Y_{L2}(s) + \dots + Y_{C1}(s) + Y_{C2}(s)]$$

$$Y(s) = Y_{g1}(s) + Y_{g2}(s) + \dots + Y_{L1}(s) + Y_{L2}(s) + \dots + Y_{C1}(s) + Y_{C2}(s)$$


DATE

- An immittance is an impedance or an admittance.
- A network function relates currents or voltage at different parts of the netw.
- Network functions are therefore immittance or voltage gain or current gain.
- A transfer function is a network function at zero inst initial cond.

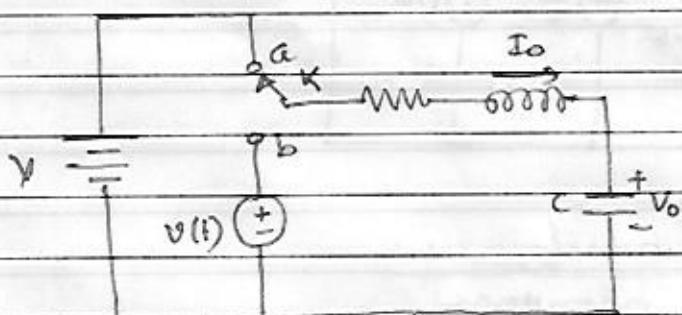Ex(1) : Switch K is ~~closed~~ held in position a until such time that a current I_0 flows in the inductor and the capacitor is charged to voltage V_0 . At that instant, K is thrown to position b, connecting to a voltage source $V(t)$. Find $I(s)$ and so $i(t)$.



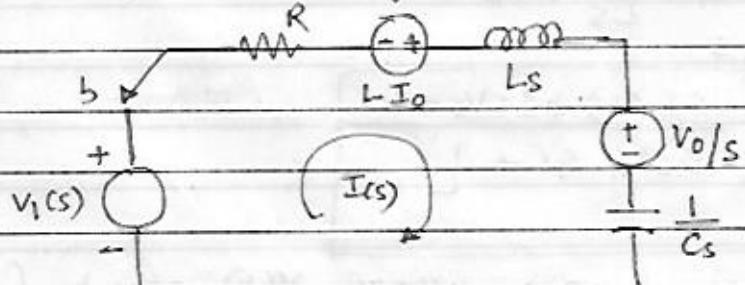Equivalent transform netw with the conditions given with transform impedances.



$$I(s) = \frac{\text{total transform voltage}}{\text{total impedance}} = \frac{V(s)}{Z(s)}$$

$$I(s) = \frac{V(s)}{Z(s)} = \frac{V_1(s) + L I_0 - V_0/s}{R + Ls + \frac{1}{Cs}}$$


xpy nr & Dr by s.

$$\left[I(s) = \frac{sV_1(s) + L I_0 s - V_0}{(Ls^2 + Rs + \frac{1}{C})} \right] \quad -(1)$$


By using partial fractions corresponds $i(t)$ by ILT.

This soln has been found without working differential eq. 2. of system ad automatically incorporates the required initial cond.

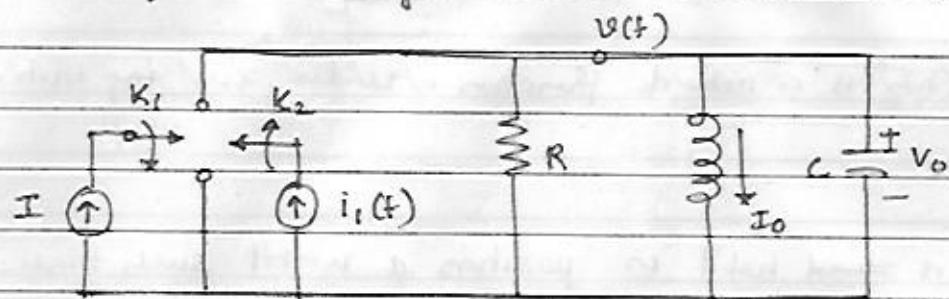(2) Switch K_1 is opened at the instant when inductor current is I_0 and capacitor is charged to V_0 . At the same instant, $t=0$, the switch K_2 is closed. It is required to find the transform of node voltage $V(s)$ so that $v(t)$ can be derived



Transformed n(s)

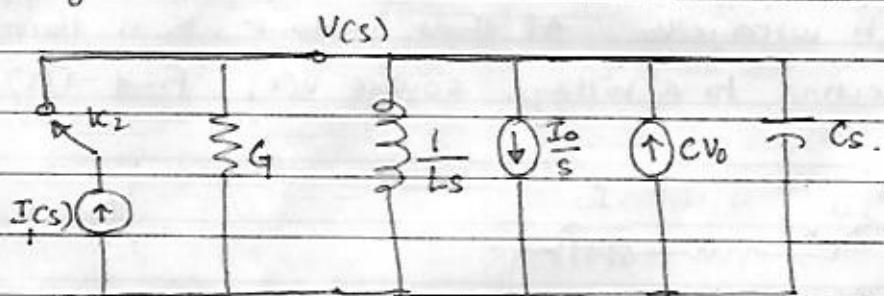

$$V(s) = \frac{I_0(s)}{Y(s)} = \frac{\text{total transform current}}{\text{total admittance}}$$

$$= \frac{I_1(s) + CSV_0 - I_0/s}{G + \frac{1}{sL} + CS}$$


Xplg Nr & Dr by S

$$V(s) = \frac{SI_1(s) + CSV_0 - I_0}{CS^2 + GS + \frac{1}{sL}}$$

The corresponding time domain voltage, $v(t)$ can be found by ILT.

DATE

(3)

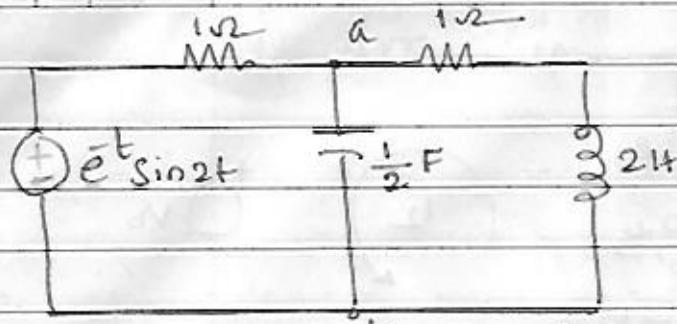

Assume network is initially relaxed (no current, no charge) and switch was closed at $t=0$. find $i(t)$ by finding $I(s)$.

$$Z_{RL} = 1 + 2s \quad Y_{RL} = \frac{1}{1+2s}$$


$$Y_{ab} = Y_C + Y_{RL}$$

$$= \frac{1}{\frac{1}{C}} + \frac{1}{1+2s} = \frac{1}{\frac{1}{0.5s}} + \frac{1}{1+2s} = \frac{s}{0.5s} + \frac{1}{1+2s} = \frac{s(1+2s)+2}{2(1+2s)}$$

$$Y_{ab}(s) = \frac{2s^2 + s + 2}{2(1+2s)}$$

Z_{ab} is reciprocal
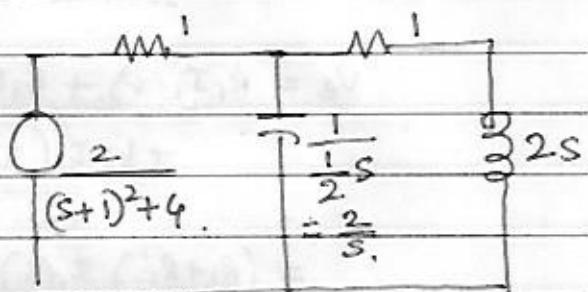
$$Z_{ab}(s) = \frac{2(1+2s)}{2s^2 + s + 2}$$



$$Z_{total}(s) = Z_{ab}(s) + 1$$

$$= \frac{2(1+2s)}{2s^2 + s + 2} + 1 = \frac{2 + 4s + 2s^2 + s + 2}{2s^2 + s + 2}$$


$$Z_{total}(s) = \frac{2s^2 + 5s + 4}{2s^2 + s + 2}$$

W.K.T

$$I(s) = \frac{V(s)}{Z(s)} = \frac{V(s) \cdot Y(s)}{Z(s)}$$


$$V(s) = \frac{2}{(s+1)^2 + 4} \quad Y(s) = \frac{2}{(s+1)^2 + 2^2} = \frac{2}{(s+1)^2 + 4}$$
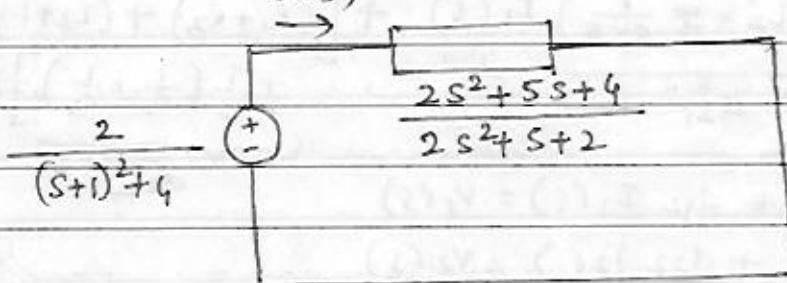
$$\therefore I(s) = \frac{2}{[(s+1)^2 + 4]} \times \frac{2s^2 + s + 2}{(2s^2 + 5s + 4)}$$



DATE

(4)

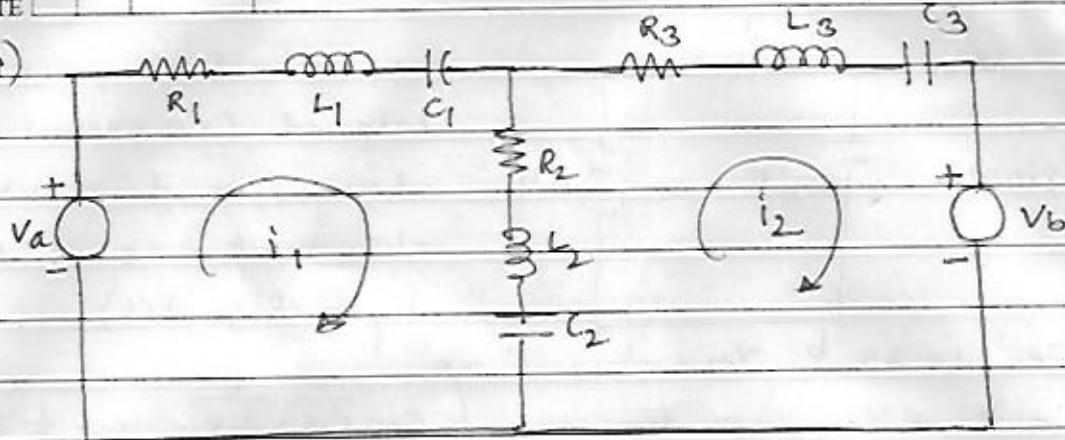

KVL @ Loop 1

$$\begin{aligned}
 V_a &= R_1 I_1(s) + L_1 s I_1(s) + \frac{1}{C_1 s} I_1(s) + R_2 (I_1(s) - I_2(s)) \\
 &\quad + L_2 s (I_1(s) - I_2(s)) + \frac{1}{C_2 s} (I_1(s) - I_2(s)) \\
 &= (R_1 + R_2) I_1(s) + s(L_1 + L_2) I_1(s) + \frac{1}{s} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) I_1(s) \\
 &\quad - R_2 I_2(s) - L_2 s I_2(s) - \frac{1}{C_2 s} I_2(s)
 \end{aligned}$$

$$\begin{aligned}
 V_a &= \underbrace{\left[(R_1 + R_2) + s(L_1 + L_2) + \frac{1}{s} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \right]}_{a_{11}} I_1(s) \\
 &\quad + \underbrace{\left[-R_2 - L_2 s - \frac{1}{C_2 s} \right]}_{a_{12}} I_2(s)
 \end{aligned}$$

KVL @ Loop 2


$$\begin{aligned}
 -V_b &= \underline{-R_3 I_2(s)} + L_3 s I_2(s) + \frac{1}{C_3 s} I_2(s) + \frac{1}{C_2 s} (I_2(s) - I_1(s)) \\
 &\quad + L_2 s (I_2(s) - I_1(s)) + R_2 (I_2(s) - I_1(s)) \\
 -V_b &= \underbrace{+ \left(-R_3 - L_3 s - \frac{1}{C_3 s} \right)}_{a_{21}} I_1(s) + \underbrace{\left[(R_1 + R_3) + (L_2 + L_3)s \right.} \\
 &\quad \left. + \frac{1}{s} \left(\frac{1}{C_2} + \frac{1}{C_3} \right) \right] I_2(s)
 \end{aligned}$$

$$a_{11}(s) I_1(s) + a_{12} I_2(s) = V_1(s)$$


$$a_{21}(s) I_1(s) + a_{22} I_2(s) = V_2(s)$$

DATE

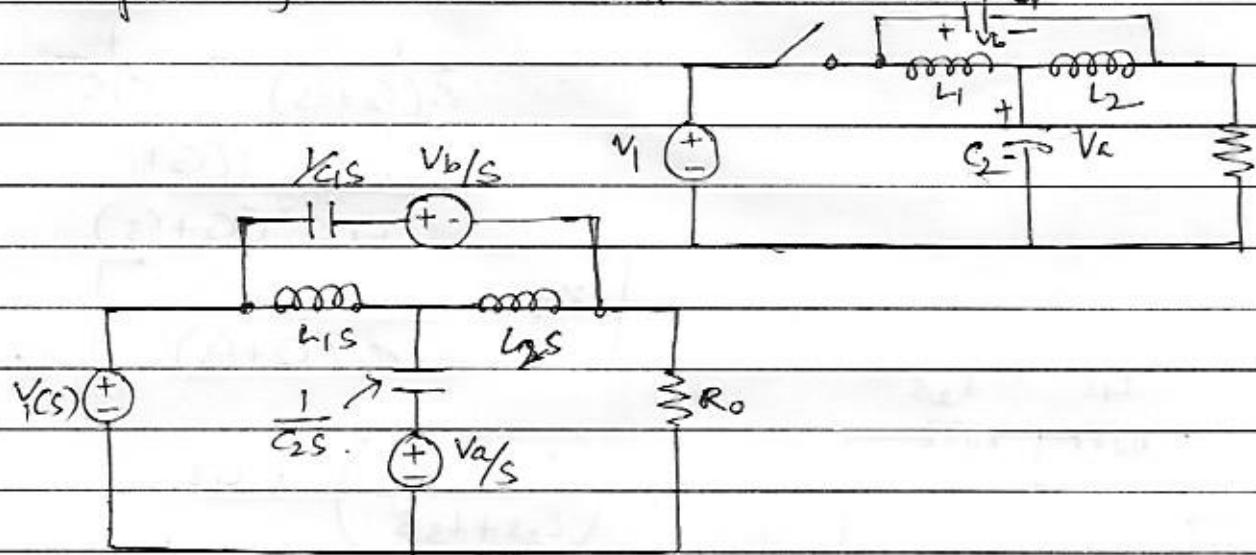- 9.6) In the n/w of the figure, the switch K is closed at $t=0$, and at $t=0^-$ the indicated voltages are on the two capacitors. Draw the transform n/w for the analysis on the loop basis, representing all elements and all initial conditions.



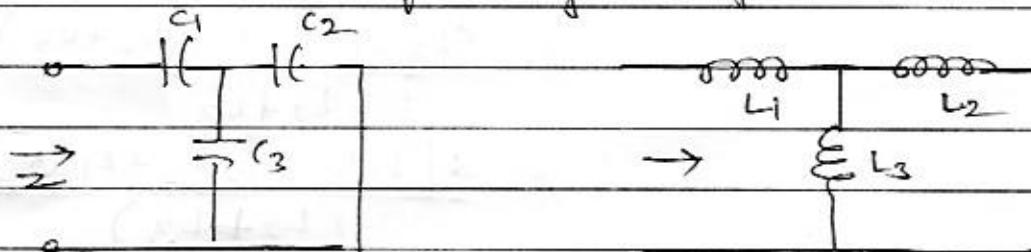- 9.7) Determine the transform impedance for the two networks shown




$$\rightarrow \frac{1}{\frac{1}{c_1 s}} \quad \frac{1}{\frac{1}{c_2 s}} \quad \rightarrow \frac{\left(\frac{1}{c_1 s} + \frac{1}{c_2 s}\right) \times Y_{Cs}}{\frac{1}{c_1 s} + \frac{1}{c_2 s} + \frac{1}{c_3 s}}$$

$$Z_{eq} = \frac{\frac{1}{c_1 c_2 s^2} + \frac{1}{c_1 c_3 s^2}}{\frac{1}{c_1 s} + \frac{1}{c_2 s} + \frac{1}{c_3 s}}$$

$$\frac{\frac{1}{c_2 s} \times \frac{1}{c_3 s}}{\frac{1}{c_2 s} + \frac{1}{c_3 s}} + \frac{1}{c_1 s} = \frac{\frac{1}{c_2 c_3 s^2}}{c_2 + c_3} + \frac{1}{c_1 s}$$

$$= \frac{c_1 s + s(c_2 + c_3)}{c_1 s^2(c_2 + c_3)} = \frac{1}{s(c_2 + c_3)} + \frac{1}{c_1 s}$$

$$\begin{aligned}
 Z_{eq} &= \left(\frac{\frac{1}{C_2 S} * \frac{1}{C_3 S}}{\frac{1}{C_2 S} + \frac{1}{C_3 S}} \right) + \frac{1}{C_1 S} = \frac{\frac{1}{C_2 C_3 S^2}}{\frac{1}{C_2} + \frac{1}{C_3}} + \frac{1}{C_1 S} \\
 &= \frac{1}{S(C_2 + C_3)} + \frac{1}{C_1 S} \\
 &= \frac{C_1 S + S(C_2 + C_3)}{C_1 S^2 (C_2 + C_3)} \\
 Z_{eq} &= \boxed{\frac{C_1 + C_2 + C_3}{C_1 (C_2 + C_3) S}}
 \end{aligned}$$

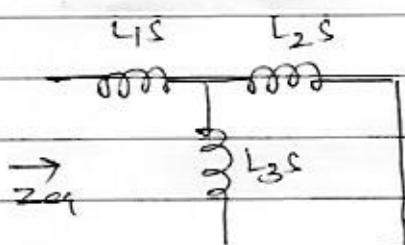

$$\begin{aligned}
 Z_{eq} &= \left(\frac{L_2 L_3 S^2}{L_2 S + L_3 S} \right) + L_1 S \\
 &= \frac{L_2 L_3 S}{L_2 + L_3} + L_1 S
 \end{aligned}$$


$$\begin{aligned}
 &= \frac{S L_2 L_3 + S L_1 (L_2 + L_3)}{L_2 + L_3} \\
 &= \frac{S [L_1 L_2 + L_2 L_3 + L_1 L_3]}{(L_2 + L_3)}
 \end{aligned}$$

block


9.12) Two blocks with two terminals each are externally identical.

It is known that one box contains now shown (a) and other contains info changing (b) with $R = \sqrt{\frac{L}{C}}$.

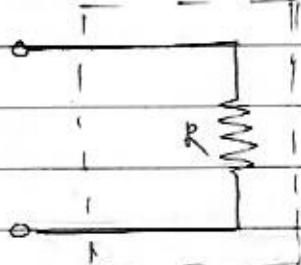(i) show that the input impedance $Z_{in(s)} = \frac{V_{in(s)}}{I_{in(s)}} = R$ for both networks. (ii) Investigate the possibility of distinguishing the purely resistive networks. Any




(a)

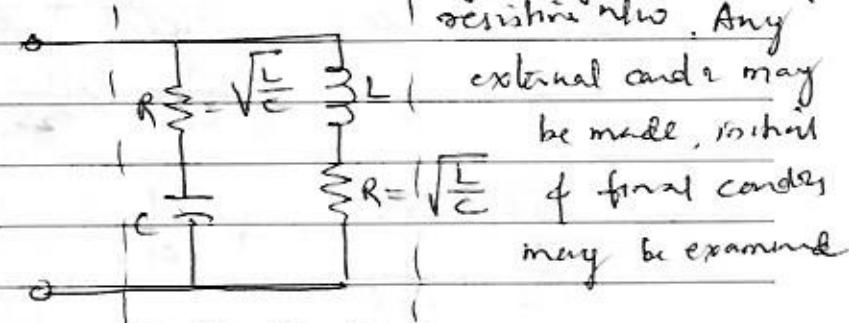

(b)

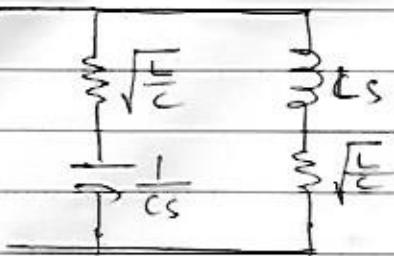external condenser may be made, initial condenser of final condenser may be examined





$$Z_{eq} = \frac{\left(Ls + \frac{1}{cs}\right) \times \left(\frac{1}{cs} + \frac{1}{L}\right)}{\left(Ls + \frac{1}{cs}\right) + \left(\frac{1}{cs} + \frac{1}{L}\right)}$$

$$= \frac{\left(Ls + \sqrt{\frac{L}{c}}\right) \left(\frac{1}{cs} + \sqrt{\frac{L}{c}}\right)}{Ls + \frac{1}{cs} + 2\sqrt{\frac{L}{c}}}$$

$$= \frac{Ls}{cs} + Ls\sqrt{\frac{L}{c}} + \frac{1}{cs}\sqrt{\frac{L}{c}} + \frac{L}{c}$$

$$Ls + \frac{1}{cs} + 2\sqrt{\frac{L}{c}}$$

$$= 2\frac{L}{c} + \sqrt{\frac{L}{c}} \left(Ls + \frac{1}{cs} \right)$$

$$Ls + \frac{1}{cs} + 2\sqrt{\frac{L}{c}}$$

$$= 2\sqrt{\frac{L}{c}}\sqrt{\frac{L}{c}} + \sqrt{\frac{L}{c}} \left(Ls + \frac{1}{cs} \right)$$


$$= \sqrt{\frac{L}{c}} \left[Ls + \frac{1}{cs} + 2\sqrt{\frac{L}{c}} \right]$$

$$\left(Ls + \frac{1}{cs} + 2\sqrt{\frac{L}{c}} \right)$$

$$= \sqrt{\frac{L}{c}}$$


$$= R$$

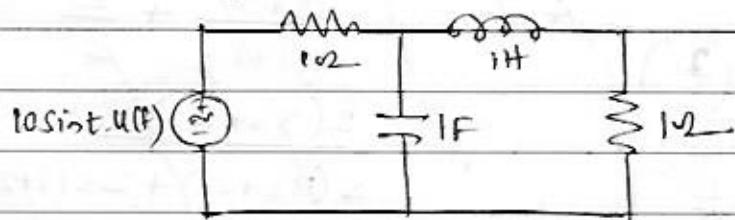9.15) If the capacitors are uncharged and inductor current is zero at $t=0^-$, in the given fig, show that the transform of generator current is




$$I_1(s) = \frac{10(s^2 + s + 1)}{(s^2 + 1)(s^2 + 2s + 2)}$$

DATE

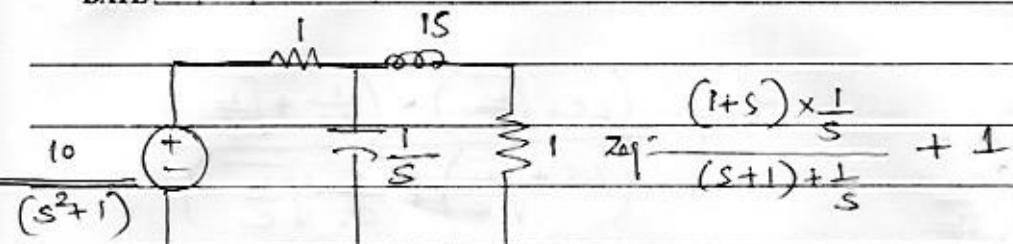



$$= \frac{(s+1)}{(s^2+s+1)} + 1$$

$$= \frac{(s+1)}{s^2+s+1} + (s^2+s+1)$$

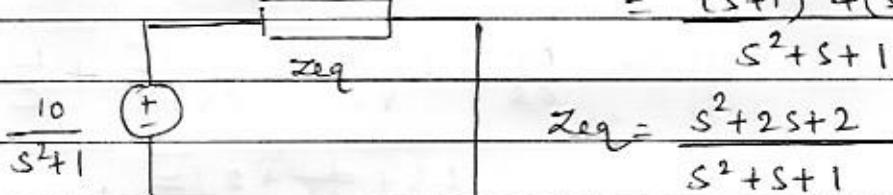

$$I(s) = \frac{10}{(s^2+1)} \times \frac{(s^2+s+1)}{(s^2+2s+2)}$$

(9.16)

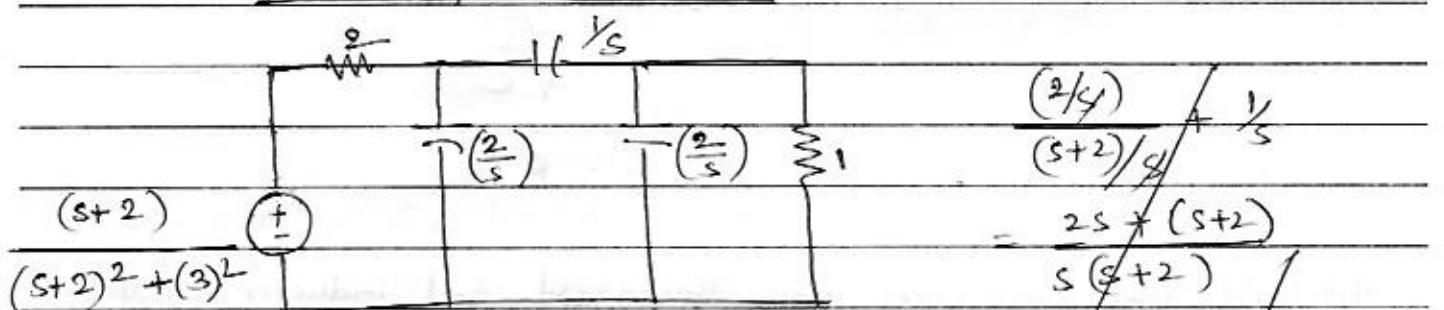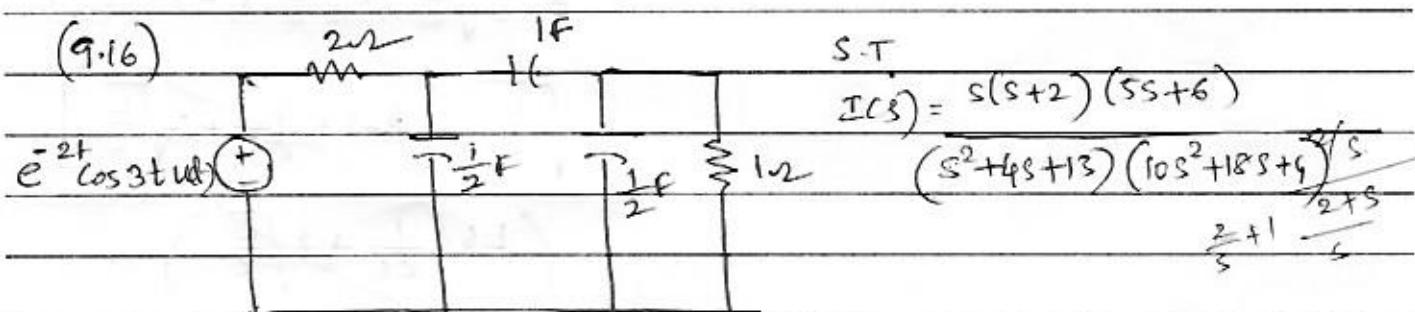

$$Z_{eq} = \left[\frac{\left(\frac{2}{s}\right) + \frac{1}{s}}{\left(\frac{2}{s}+1\right)} \times \frac{2}{s} \right] + \left[\frac{\left(\frac{2}{s}\right) + \frac{1}{s}}{\left(\frac{2}{s}+1\right)} + \frac{2}{s} \right]$$

$$= \frac{2(s+2)}{s(s+2)} \times \frac{2}{s}$$

$$= \frac{3s+2}{s(s+2)} + \frac{2}{s(s+2)}$$

$$= 2 \left(\frac{3s+2}{s(s+2)} \right)$$

$$= \frac{s(3s+2) + 2s(s+2)}{s(s+2)} + 2$$

$$= \frac{2(3s+2)}{3s^2+2s+2s^2+4}$$


DATE _____

$$\rightarrow \frac{\frac{2}{s} \times 1}{\frac{2}{s} + 1} = \frac{\left(\frac{2}{s}\right)}{\left(\frac{2+s}{s}\right)} = \frac{2}{s+2}$$

$$\rightarrow \frac{2}{(s+2)} + \frac{1}{s} = \frac{2s+s+2}{s(s+2)} = \frac{3s+2}{s(s+2)}$$

$$\rightarrow \frac{8s+2}{s(s+2)} \times \frac{2}{s} = \frac{(6s+4)/s^2(s+2)}{(3s+2)+2(s+2)}$$
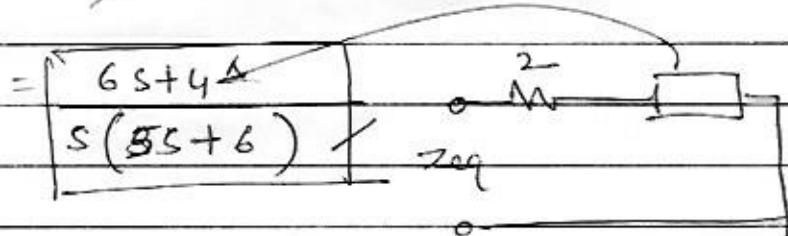
$$= \frac{6s+4}{s^2(s+2)} \times \frac{s(s+2)}{3s+2+2s+4}$$



~~$$\rightarrow \frac{6s+4}{s(5s+6)} + 2 = \frac{6s+4+2(5s+6)}{s(5s+6)}$$~~

~~$$zeq = \frac{6s+4+10s^2+12s}{s(5s+6)}$$~~

$$zeq = \frac{10s^2+18s+4}{s(5s+6)}$$

$$I(s) = \frac{(s+2)}{(s+2)^2+9} \times \frac{s(5s+6)}{10s^2+18s+4}$$

$$I(s) = \frac{s(s+2)(5s+6)}{(s^2+4s+13)(10s^2+18s+4)}$$

DATE

For a L-mesh network with initial cond² sources, the sol² can be more generally written as

$$\sum_{j=1}^L a_{kj}(s) I_j(s) = V_k(s) \quad k=1, 2, \dots, L$$

Ex : L = 3

$$\sum_{j=1}^3 a_{kj}(s) I_j(s) = V_k(s) \quad k=1, 2, 3$$

$$\begin{array}{l|l} k=1 & \begin{bmatrix} a_{11}(s) & a_{12}(s) & a_{13}(s) \\ a_{21}(s) & a_{22}(s) & a_{23}(s) \\ a_{31}(s) & a_{32}(s) & a_{33}(s) \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} V_1(s) \\ V_2(s) \\ V_3(s) \end{bmatrix} \end{array} \quad (1)$$

L → Number of loops

a_{kj} - Coefficient a_{kj} are impedances plus ^{initial} cond² sources.

Similarly for N-Node network with cond² sources, the sol² can be more generally written as

$$\sum_{j=1}^N b_{kj}(s) V_j(s) = I_k(s) \quad k=1, 2, \dots, N$$

Ex : N = 3

$$\sum_{j=1}^3 b_{kj}(s) V_j(s) = I_k(s) \quad k=1, 2, 3$$

$$\begin{array}{l|l} k=1 & \begin{bmatrix} b_{11}(s) & b_{12}(s) & b_{13}(s) \\ b_{21}(s) & b_{22}(s) & b_{23}(s) \\ b_{31}(s) & b_{32}(s) & b_{33}(s) \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \\ V_3(s) \end{bmatrix} = \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} \end{array} \quad (2)$$

where N - Number of Nodes

b_{kj} - Coefficient b_{kj} are admittance plus initial cond² sources

a_{kj}, b_{kj} are coefficients with initial cond² because C & L may be holding energy (inductor having current $I(t)$ & Cap having $V(0)$) which will be moved to RHS side ie Response vector

\therefore Eq(1) can be redefined compactly as

$$[Z][I] = [V] + [V_0] = [V'] \quad \text{for mesh analysis}$$

\uparrow Initial cond² voltages

where $[Z]$ - Impedance matrix

$[I]$ - Loop current matrix I_1, I_2, \dots, I_L

$[V']$ - sum of voltage sources (dependent +
(sources + Initial cond² voltage))

$$V_1 + V_{01}, V_2 + V_{02}, \dots, V_L + V_{0L}$$

$L=3$

$$\begin{bmatrix} Z_{11}(s) & Z_{12}(s) & Z_{13}(s) \\ Z_{21}(s) & Z_{22}(s) & Z_{23}(s) \\ Z_{31}(s) & Z_{32}(s) & Z_{33}(s) \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} V_1'(s) \\ V_2'(s) \\ V_3'(s) \end{bmatrix} \quad \begin{array}{l} V_1'(s) = V_1(s) + V_{01}(s) \\ V_2'(s) = V_2(s) + V_{02}(s) \\ V_3'(s) = V_3(s) + V_{03}(s) \end{array}$$

$$\uparrow V_j'(s) = V_j(s) + V_{0j}(s) \quad \uparrow \text{Initial cond}$$

likewise Eq²(2) can be redefined compactly as

$$[Y][V] = [I] + [I_0] = [I'] \quad \text{for Node Analysis}$$

where $[Y]$ - Admittance matrix

$[V]$ - Node voltage vector V_1, V_2, \dots, V_N

$[I']$ - sum of current sources (sources + Initial cond² curr)

$N=3$

$$\begin{bmatrix} Y_{11}(s) & Y_{12}(s) & Y_{13}(s) \\ Y_{21}(s) & Y_{22}(s) & Y_{23}(s) \\ Y_{31}(s) & Y_{32}(s) & Y_{33}(s) \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \\ V_3(s) \end{bmatrix} = \begin{bmatrix} I_1'(s) \\ I_2'(s) \\ I_3'(s) \end{bmatrix} \quad \begin{array}{l} I_1'(s) = I_1(s) + I_{01}(s) \\ I_2'(s) = I_2(s) + I_{02}(s) \\ I_3'(s) = I_3(s) + I_{03}(s) \end{array}$$

$$\uparrow I_j'(s) = I_j(s) + I_{0j}(s)$$

Δ - Determinant of $[Z]$, $L=3$

the basis form eq²

$$\rightarrow V_j'(s) = V_j(s) + V_{0j}(s)$$

where $V_j'(s)$ - Voltage transform

$V_j(s)$ - transform all sources in loop j

$V_{0j}(s)$ - transform of all initial cond² loop j .

↑ transform of
all current
sources @ node j

↑ transform
of all initial
cond² at node j

DATE Superposition theorem

Now,

$$[Z][I] = [V^1] \neq [V^r], \quad [Y][V] = [I^1] \\ = [V] + [V_0] \quad = [I] + [I_0]$$

Let us consider mesh ($L = 3$)

$$\begin{pmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1^1 \\ V_2^1 \\ V_3^1 \end{pmatrix} \quad \text{--- (1)}$$

Each current is obtained by determining response to a voltage and then summing

$$\begin{pmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1^1 \\ 0 \\ 0 \end{pmatrix} \quad I_{11}^1, I_{21}^1, I_{31}^1 \\ \Delta_{11} \quad \Delta_{12} \quad \Delta_{13}$$

partial responses

for I_2

$$\Delta_{12} = \begin{pmatrix} Z_{21} & Z_{23} \\ Z_{31} & Z_{33} \end{pmatrix} \quad \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} \quad \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ V_2^1 \\ 0 \end{pmatrix} \quad I_{12}^1, I_{22}^1, I_{32}^1 \\ \Delta_{22} = \begin{pmatrix} Z_{11} & Z_{13} \\ Z_{31} & Z_{33} \end{pmatrix} \quad \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} \quad \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ V_3^1 \end{pmatrix} \quad I_{13}^1, I_{23}^1, I_{33}^1 \\ \Delta_{32} = \begin{pmatrix} Z_{11} & Z_{13} \\ Z_{21} & Z_{23} \end{pmatrix} \quad \begin{pmatrix} \cdot \\ \cdot \\ \cdot \end{pmatrix} \quad \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ V_3^1 \end{pmatrix} \quad \Delta_{31}, \Delta_{32}, \Delta_{33}$$

(or)

Ex: $I_2(s) = I_{21}^1(s) + I_{22}^1(s) + I_{23}^1(s)$

In eq² (2), $I_2(s) = \frac{\Delta_{12}}{\Delta_2} V_1^1(s) + \frac{\Delta_{22}}{\Delta_2} V_2^1(s) + \frac{\Delta_{32}}{\Delta_2} V_3^1(s) \quad \text{--- (2)}$

$V_j^1(s) = V_j(s) + V_{0j}(s)$

is summation of voltages, $\Delta_{12} = \begin{pmatrix} Z_{11} & V_1^1 & Z_{13} \\ Z_{21} & 0 & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{pmatrix}$, $\Delta_{22} = \begin{pmatrix} Z_{11} & 0 & Z_{13} \\ Z_{21} & V_2^1 & Z_{23} \\ Z_{31} & 0 & Z_{33} \end{pmatrix}$, $\Delta_{32} = \begin{pmatrix} Z_{11} & 0 & Z_{13} \\ Z_{21} & 0 & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{pmatrix}$

Note: All the current sources are transformed into voltage sources of all the loops. In Eq² (2), we observe that, each of the transform sources one at a time and then add the partial responses to get $I_2(s)$. This is in essence, the superposition principle (or) principle of linearity.

and $V_{0j}(s)$ being the transform voltage across the loop j . This summation, of course, must be made by taking into account the polarity of the various sources w.r.t to reference direction of the loop. We have assumed that any current source in the net is transformed into voltage source before the above formulation.



Two aspects of superposition are important in network analysis.

- i) A given response in a network resulting from a number of independent sources (including initial cond² sources) may be computed by summing the response to each individual source with all other sources reduced to make inoperative (reduced to zero voltage or zero current)

This statement describes additivity property of linear n/w.

- ii) If all sources are multiplied by a constant, the response is multiplied by the same constant. This statement describes the property of homogeneity in a linear n/w.

Eq² (2) is evident for additivity & homogeneity

$$I_2(s) = \frac{1}{\Delta_2} [\Delta_{12} V_1'(s) + \Delta_{22} V_2'(s) + \Delta_{32} V_3'(s)]$$

∴ superposition is combined property of additivity and homogeneity, especially in n/w with initial conditions.

Procedure to find response in a element in n/w using superposition principle



- a) Name the terminals of branch/element where response to be found as A,B
- b) Consider a independent source in n/w and make all other independent sources inoperative (deactivate)
 - Voltage sources are replaced by short circuit (sc) so that voltage strength is zero
 - Current sources are replaced by open circuit (o.c) so that current strength is zero.

Dependent sources (controlled sources) must be left intact.

- c) Using KVL/KCL/network reduction principle find the response due to active source.
- d) Repeat b,e step(b),(c) for all other independent sources one by one
- e) Sum the responses obtained by individual independent sources to get total response


DATE

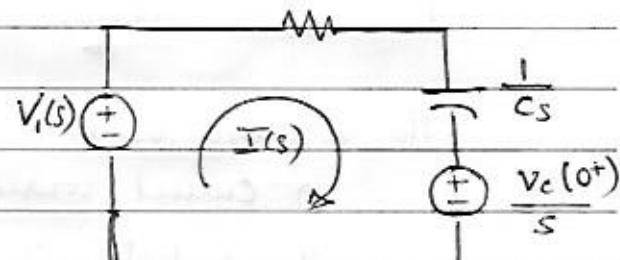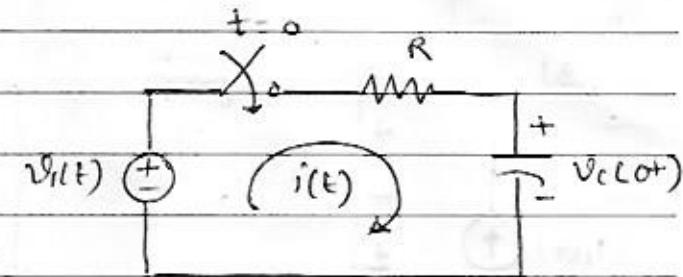- (2) Find $i(t)$ in the net using superposition thm.
 K is closed at $t=0$, where cap is initially has
 $v_c(0^+)$



Step 1:

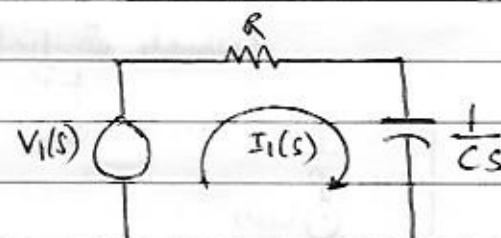
$$I_1(s) = \frac{V_i(s)}{R + \frac{1}{Cs}} \quad (1)$$



Step 2

$$R I_2(s) + I_2(s) \times \frac{1}{Cs} = -\frac{v_c(0^+)}{s}$$

$$I_2(s) = \frac{-v_c(0^+)/s}{R + \frac{1}{Cs}} \quad (2)$$

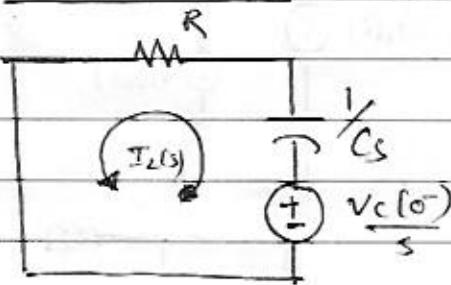Sum of $I_1(s)$ & $I_2(s)$

$$I(s) = I_1(s) + I_2(s)$$

$$= \frac{V_i(s)}{R + \frac{1}{Cs}} = \frac{v_c(0^+)/s}{R + \frac{1}{Cs}}$$

$$I(s) = \frac{V_i(s) - v_c(0^+)/s}{R + \frac{1}{Cs}}$$

Taking 1st
 $i(t)$ can
be found

- The Numerator shows that the response is due to the superimposition of the response due to each of the sources in network.


- Let $V_i(s) = V_0/s$ and $v_c(0) = V_0$ - Two sources are equal and opposite so $i(t) = 0$

if, instead $V_i(s) = 2V_0/s$ & $v_c(0) = V_0$ - then the superimposed responses added to

$$i(t) = \frac{V_0}{R} \cdot e^{-t/Rc} \quad - \text{homogenous aspect of Super}$$




(3)

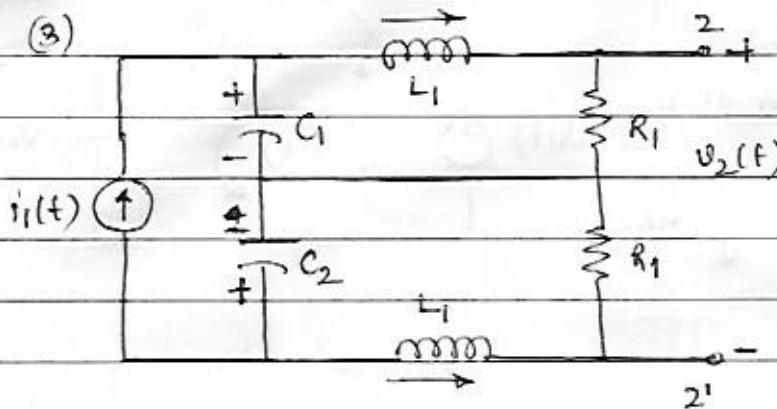



Initial charge on cap is same & current through inductor is same.

The response $v_2(t)$ is due to

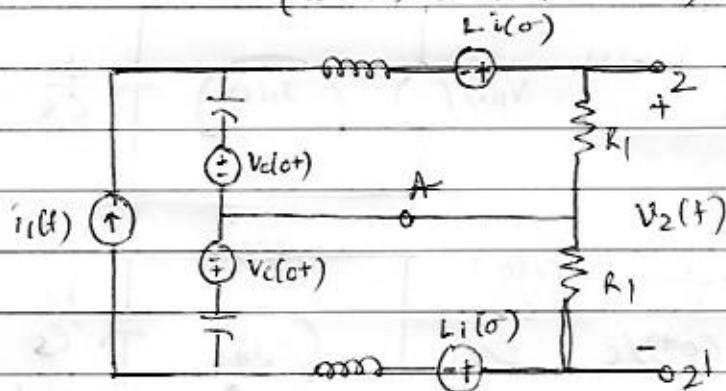
- i) current source $i_1(t)$ and
- ii) initial voltage on cap and current through inductor (which initial cond²) gives.



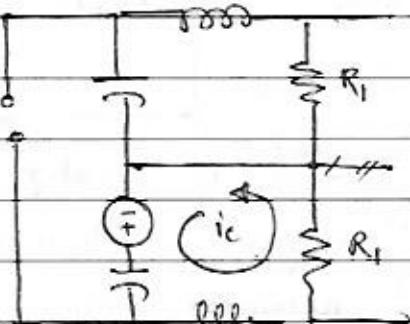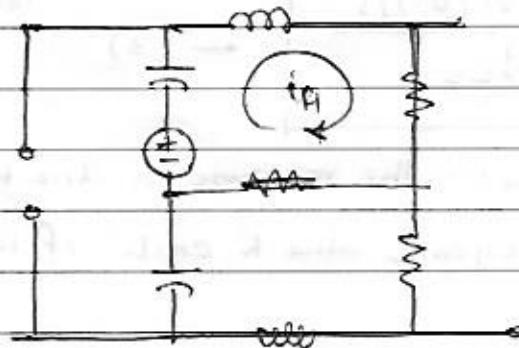In this response due to initial cond² will always cancel, and the response will depend only on the excitation from $i_1(t)$.



DATE

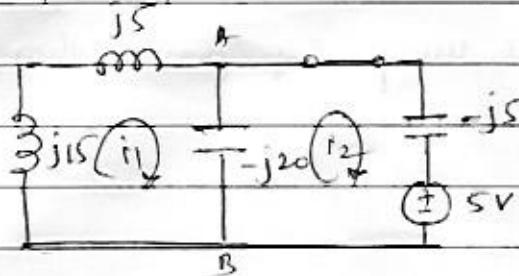

$$j20i_1 - j20(i_1 - i_2) = 0 \\ +j20i_2 = 0 \quad \therefore i_2 = 0.$$

$$-j20(i_2 - i_1) - j5i_2 + 5 = 0$$


$$+j20i_1 - j20i_2 = -5$$

$$V_{AB} = (i_1 - i_2) \times -j20$$

$$= j0.25 \times -j20 \\ = 5V$$


$$i_1 = \frac{-5}{j20} = -j0.25$$
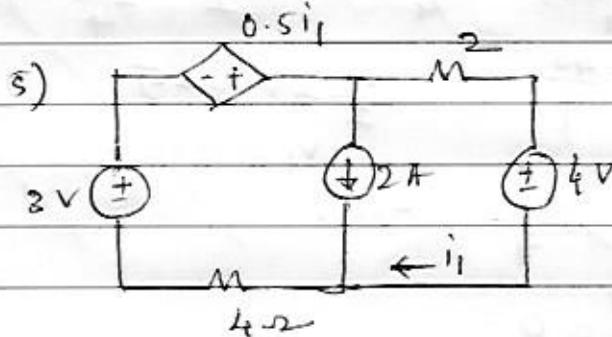
$$V_{AB \text{ total}} = 7.5 - 20 + 5 = -\underline{\underline{7.5V}}$$



Find i_1 using superposition
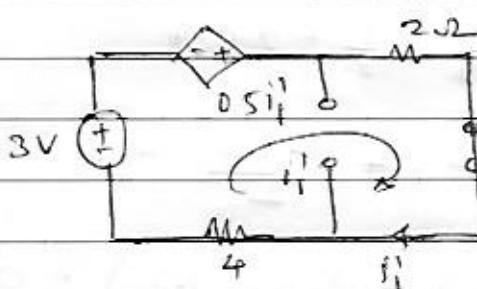
$$\frac{V_1}{2} = \frac{i_1}{1} \\ V_1 = \frac{i_1}{2}$$



$$-3 - 0.5i_1'' + 6i_1'' = 0$$

$$5.5i_1'' = 3 \quad |i_1'' = \underline{\underline{0.545A}}$$


$$\frac{V_1}{2} - 0.5i_1'' + 2 + \frac{V_1}{2} = 0$$

$$\frac{V_1}{4} - \frac{0.5i_1''}{4} + 2 + \frac{V_1}{2} = 0 \\ -(2 + i_1'') - \frac{0.5i_1''}{4} + 2 + i_1'' = 0 \\ 0.875i_1'' - \frac{1}{4} = 0$$

$$\frac{V_1}{4} - \frac{0.5i_1''}{4} + 2 + i_1'' = 0$$

$$\therefore \frac{V_1}{4} - \frac{0.5i_1''}{4} + 2 + i_1'' = 0$$

$$\therefore V_1 = \frac{i_1''}{2}$$

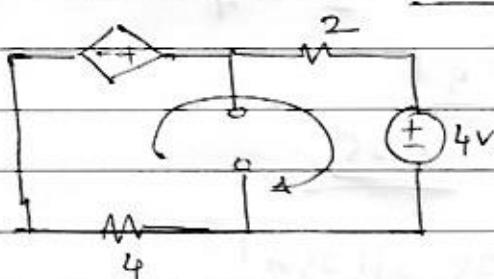

$$+4 + 4i_1''' - 0.5i_1''' + 2i_1''' = 0$$

$$5.5i_1''' = -4$$

$$i_1''' = -0.727$$

$$\therefore \frac{i_1''}{2} - \frac{0.5i_1''}{4} + 2 + i_1'' = 0$$

$$1.375i_1'' = -2$$



$$i_1'' = -1.45$$

$$\therefore i_1 = 0.545 - 1.45 - 0.727 \therefore$$

$$\boxed{i_1 = -1.632}$$

(7) for the given fig find current I using superposition theorem

81

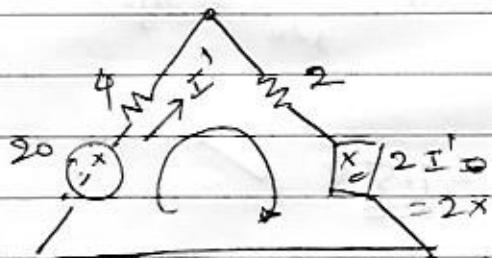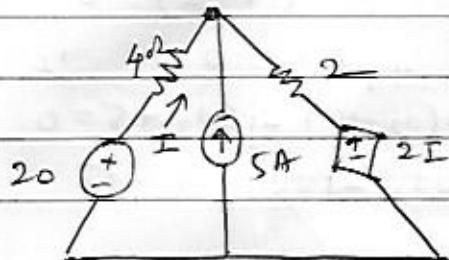

$$\frac{V_1 - 20}{4} + \frac{V_1 - 2(V_1 - 20)}{4} = 0$$

$$\frac{V_1 - 5}{4} + \frac{V_1}{2} - \frac{V_1 + 40}{4} = 0$$


$$\frac{V_1}{2} - 5 = 0$$

$$V_1 = 10V$$

By KVL

$$-20 + 4I' + 2I' + 2I' = 0$$
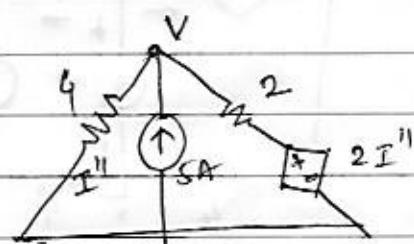
$$8I' = 20 \quad I' = \frac{20}{8} = \frac{5}{2} = 2.5A$$



$$\frac{V}{4} - 5 + \frac{V - 2I''}{2} = 0$$

$$\frac{V}{4} - 5 + \frac{V}{2} - \frac{2}{2} \left(\frac{V}{4} \right) = 0$$

$$\frac{V}{4} - 5 + \frac{V}{2} + \frac{V}{4} = 0$$




$$V = 5$$

$$I'' = -\left(\frac{V}{4}\right) = -\left(\frac{5}{4}\right) = -1.25$$

$$I = I' + I'' = 2.5 - 1.25 = 1.25A$$


DATE

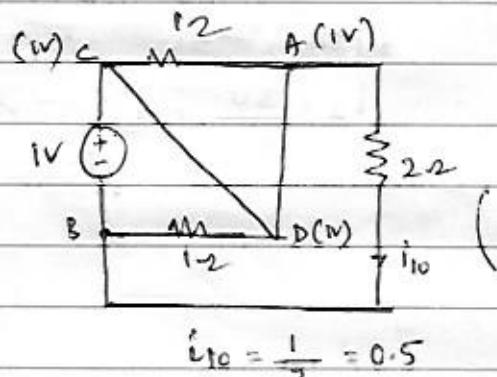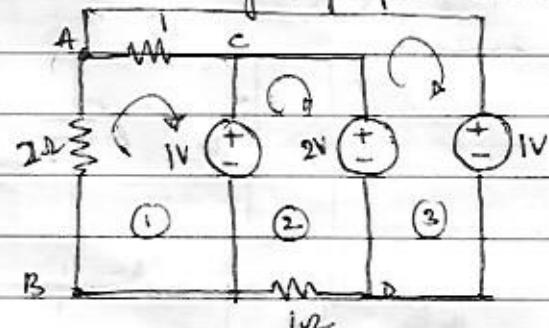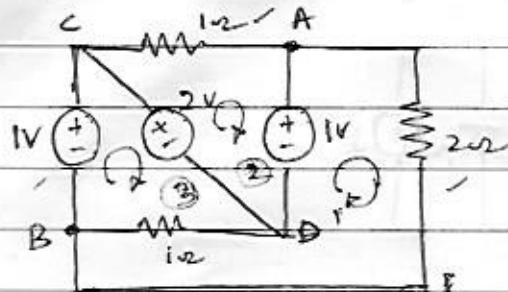(3) Determine the current in 2Ω resistor using superposition theorem.




$$\left(\begin{array}{ccc} 3 & 0 & -1 \\ 0 & 1 & 0 \\ -1 & 0 & 1 \end{array} \right) \left(\begin{array}{c} i_1 \\ i_2 \\ i_3 \end{array} \right) = \left(\begin{array}{c} 1 \\ 2 \\ -1 \end{array} \right)$$
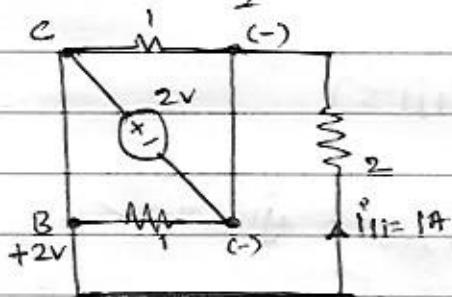
$$\begin{aligned} i_{11} &= 0.5 & i_{21} &= 0 & i_{31} &= +0.5 & \left(\begin{array}{c} 1 \\ 0 \\ 0 \end{array} \right) \\ i_{22} &= 0 & i_{22} &= +1 & i_{23} &= 0 & \left(\begin{array}{c} 0 \\ 1 \\ 0 \end{array} \right) \\ i_{31} &= -0.5 & i_{32} &= 0 & i_{33} &= -3/2 & \left(\begin{array}{c} 0 \\ 0 \\ -1 \end{array} \right) \end{aligned}$$



$$\begin{aligned} i_1 &= 0A & i_2 &= -1 & i_3 &= -\frac{1}{2} - \frac{3}{2} = -\frac{4}{2} = -2A \\ i_1 &= 0A & i_2 &= +1 & i_3 &= -2A \end{aligned}$$


$$i_{10} = \frac{1}{2} = 0.5$$

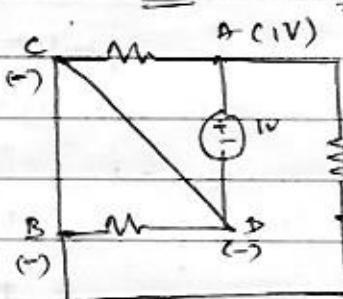


$$i_{13} = \frac{1}{2} = 0.5$$

$$i_{\text{total}} (i_1) = 0.5 + 0.5 - 1 = 0A$$

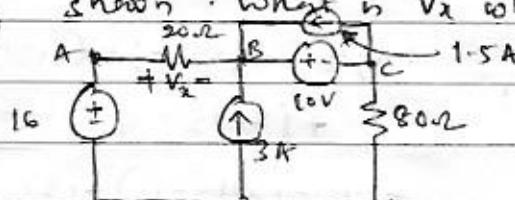(4) find components of V_x caused by each sources acting alone on the shown. What is V_x when all sources are acting.


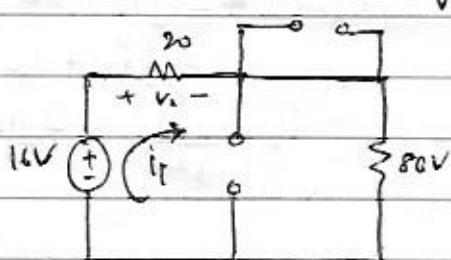
$$i_2 = \frac{80}{80+20} \times 3A = 2.4A$$



$$i_1 = \frac{16}{100} = 0.16$$

$$Vx_1 = 0.16 \times 20 = 3.2V$$

$$Vx = 3.2 - 48 - 2 = -46.8V$$

$$Vx = -(2.4 \times 10) = -48V$$

$$i_3 = \frac{10}{120} = 0.1A$$


$$Vx_3 = -(0.1 \times 20) = -2V$$

$$i_4 = 0$$

$$Vx_4 = 0$$

DATE

(5) Apply superposition theorem. find voltage across capacitor of reactance

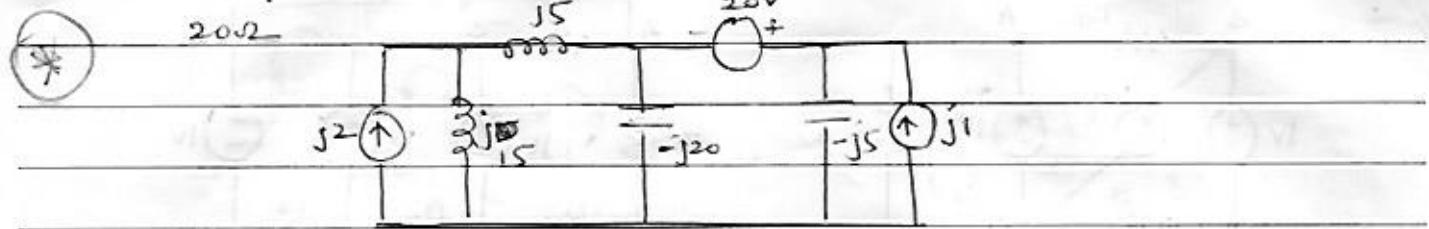

Col 1

$$-j5i_1 + j5i_2 - 20(i_2 - i_1) = 0$$

$$+j20i_2 = -30$$

$$i_2 = \frac{-30}{j20} = -j1.5 \text{ A}$$

$$-j5(i_2) - 20(j(i_2 - i_1)) = 0$$

$$-j5i_2 - 20ji_2 + 20ji_1 = 0$$

$$-j25i_2 + j20i_1 = 0$$

$$j20i_1 = j25i_2$$

$$= j25(+j1.5)$$

$$j20i_1 = -37.5$$

$$i_1 = -37.5/j20 = -j1.875 \text{ A}$$

$$i_{AB} = i_1 - i_2 = +j1.875 - (+j1.5)$$

$$= +j0.375$$

$$V_{AB} = +j0.375 \times -j20$$

$$= +7.5 \text{ V}$$

$$= +7.5 \text{ V}$$

$$+j15i_1 + j5i_1 - j20(i_1 - i_2) = 0$$

$$+j20i_2 = 0 \quad i_2 = 0$$

$$-20 - j20(i_2 - i_1) - j5i_2 = 0$$

$$+j20i_1 + 25j i_2 = 20$$

$$\therefore i_{AB} = i_1 - i_2 = -j4$$

$$V_{AB} = -j4 \times -j20 = j^2 20$$


$$= -20 \text{ V}$$

$$j20i_1 = 25j i_2 + 20$$

$$i_1 = \frac{20}{j20} = -\frac{j4}{j20}$$

DATE

(15)

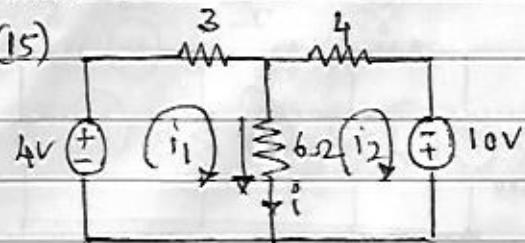

$$\begin{pmatrix} 9 & -6 \\ -6 & 10 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 4 \\ 0 \end{pmatrix}$$


$$i_1^1 = 0.740 \quad i_2^1 = 0.445$$

$$\begin{pmatrix} 9 & -6 \\ -6 & 10 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 10 \end{pmatrix}$$

$$i_1^{II} = 1.112 \quad i_2^{II} = 1.666$$

$$i_1 = 1.852 \text{ A} \quad i_2 = 2.111$$


$$i = i_1 - i_2 = -0.259$$

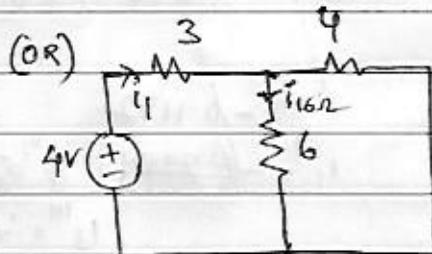

$$R_{eq} = \frac{4 \times 6}{10} + 3 = 2.4 + 3 = 5.4$$

$$i_1 = 4/5.4 = 0.740$$
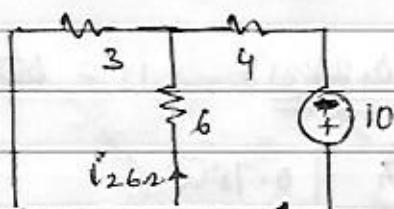
$$i_{16.2} = \left(\frac{4}{4+6} \right) \times 0.740 = 0.296.$$




$$R_{eq} = \frac{3 \times 6}{9} + 4 = 6.2$$

$$i_2 = +\frac{10}{6.2} = 1.6667.$$

$$i_{26.2} = \frac{3}{3+6} \times 1.667 = 0.5556 \text{ A}$$
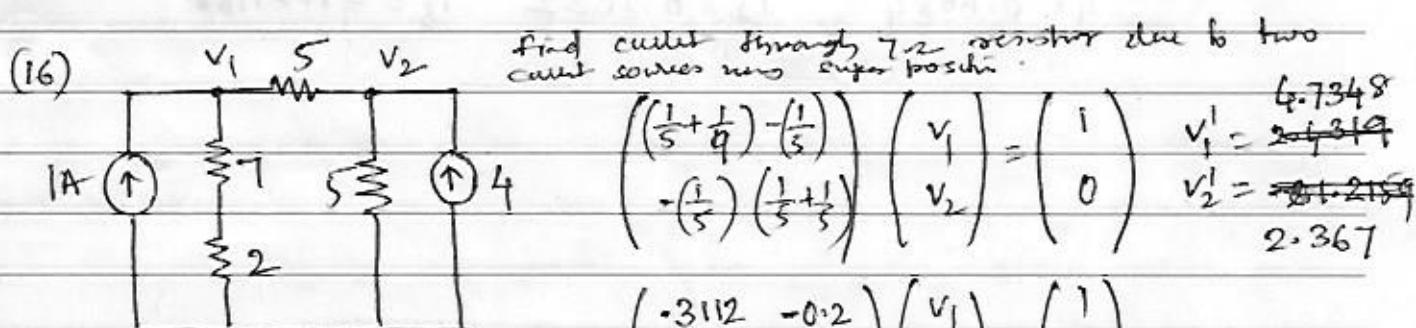
$$i = i_{16.2} - i_{26.2} = +0.296 - 0.5556 = -0.259 \text{ A}$$



find current through 7Ω resistor due to two
current sources using super position

$$\begin{pmatrix} \left(\frac{1}{5} + \frac{1}{4}\right) - \left(\frac{1}{5}\right) \\ -\left(\frac{1}{5}\right) \left(\frac{1}{5} + \frac{1}{4}\right) \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} i \\ 0 \end{pmatrix}$$

$$v_1^1 = \frac{4.7348}{2.367} = 2.045 \text{ V}$$

$$\begin{pmatrix} -0.2 & -0.2 \\ -0.2 & 0.4 \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} 1 \\ 0 \end{pmatrix}$$

$$v_1^{II} = 0.4696 + 9.4696 = 9.9363 \text{ V}$$

$$v_2^{II} = -7.568 + 14.0734 = 6.5056 \text{ V}$$

Curent through 7Ω resistor

$$= \frac{14.2045}{9} = 1.5782 \text{ A}$$


$$\begin{pmatrix} 0.3112 & -0.2 \\ -0.2 & 0.4 \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \end{pmatrix} = \begin{pmatrix} 0 \\ 4 \end{pmatrix}$$

$$v_1 = 4.7348 + 9.4696 = 14.2045 \text{ V}$$

$$v_2 = 2.367 + 14.0734 = 16.4401 \text{ V}$$

$$\therefore v_f = -14.2045 \text{ V}$$

DATE

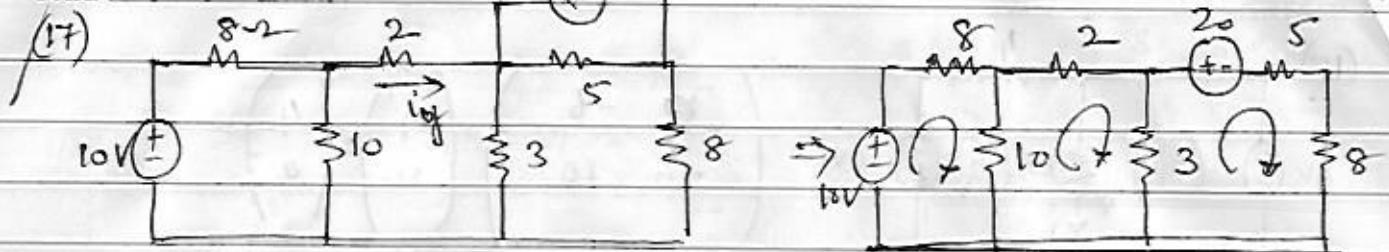

$$\begin{pmatrix} 18 & -10 & 0 \\ -10 & 15 & -3 \\ 0 & -3 & 16 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \\ -20 \end{pmatrix}$$

$$\begin{aligned} i_1' &= 0.9030 & \begin{pmatrix} 18 & -10 & 0 \\ -10 & 15 & -3 \\ 0 & -3 & 16 \end{pmatrix} \begin{pmatrix} i_1' \\ i_2' \\ i_3' \end{pmatrix} &= \begin{pmatrix} 10 \\ 0 \\ 0 \end{pmatrix} & i_1' &= 0.9125 & i_2' &= 0.6684 \\ i_2' &= 0.6254 & & & i_1' &= 0.9030 & i_3' &= 0.1172 \\ i_3' &= 0.1172 & & & i_2' &= 0.6254 & & -0.2111 \\ i_1'' &= i_2'' = i_3'' \\ &= 0 & & & i_1'' &= 0 & i_2'' &= 0 & i_3'' &= 0 \\ i_1''' &= -0.2345 & & & & & & & & & \\ i_2''' &= 0.4222 & & & & & & & & & \\ i_3''' &= -1.3291 & & & & & & & & & \end{aligned}$$

$$\begin{aligned} i_1 &= 0.6684 & i_2 &= 0.2032 & i_3 &= -1.2118 \\ i_1 &= 0.9030 - 0.2345 & & & & \\ &= 0.6685 & i_0 &= i_2 = 0.2032 & 0.7858 & \\ & & & & & \end{aligned}$$


$$i_4 = 0.2033 A$$

$$i_4 = i_2 = 0.6254 - 0.4222 = 0.2032$$

$$i_1 = 0.6684 \quad i_2 = 0.2032 \quad i_3 = -1.2118$$

DATE

(19)

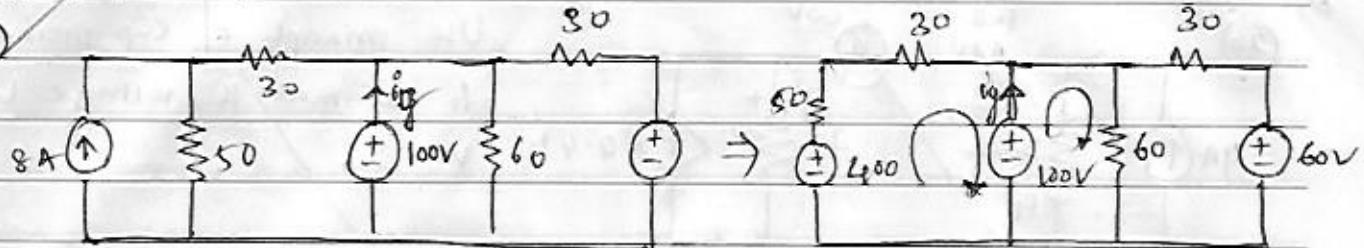

$$\begin{pmatrix} 80 & 0 & 0 \\ 0 & 60 & -60 \\ 0 & -60 & 90 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 300 \\ 100 \\ -60 \end{pmatrix}$$

$i_1 = 3.75$
 $i_2 = 3$
 $i_3 = 1.333$

$$\begin{pmatrix} 80 & 0 & 0 \\ 0 & 60 & -60 \\ 0 & -60 & 90 \end{pmatrix} \begin{pmatrix} i_1' \\ i_2' \\ i_3' \end{pmatrix} = \begin{pmatrix} 200 \\ 0 \\ 0 \end{pmatrix}$$

$i_1' = 3.75 \quad i_2' = 0 \quad i_3' = 0$

$$\begin{pmatrix} 80 & 0 & 0 \\ 0 & 60 & -60 \\ 0 & -60 & 90 \end{pmatrix} \begin{pmatrix} i_1'' \\ i_2'' \\ i_3'' \end{pmatrix} = \begin{pmatrix} 300 \\ 100 \\ 0 \end{pmatrix}$$

$i_1'' = 0, \quad i_2'' = 5 \quad i_3'' = 3.334$


$$\begin{pmatrix} 80 & 0 & 0 \\ 0 & 60 & -60 \\ 0 & -60 & 90 \end{pmatrix} \begin{pmatrix} i_1''' \\ i_2''' \\ i_3''' \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ -60 \end{pmatrix}$$

$i_1''' = 0 \quad i_2''' = -2 \quad i_3''' = -2$


$$i_y = i_2 - i_3 = 3 - 3.75 = \underline{\underline{-0.75A}}$$

$$i_y = i_2 - i_3 = 3 - 3.75 = \underline{\underline{-0.75A}}$$

(or)

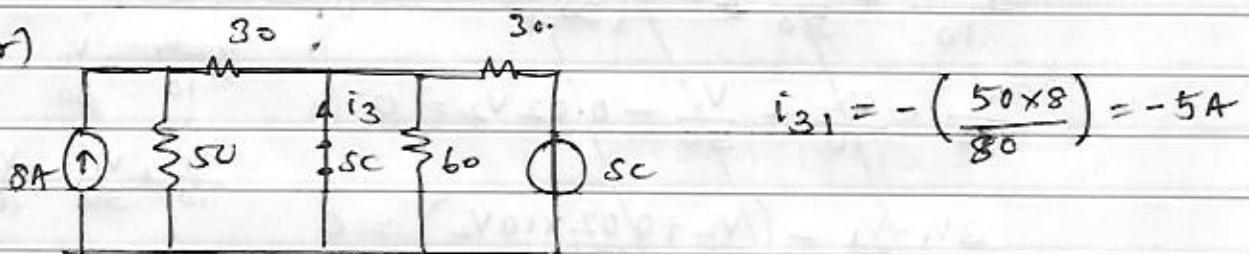

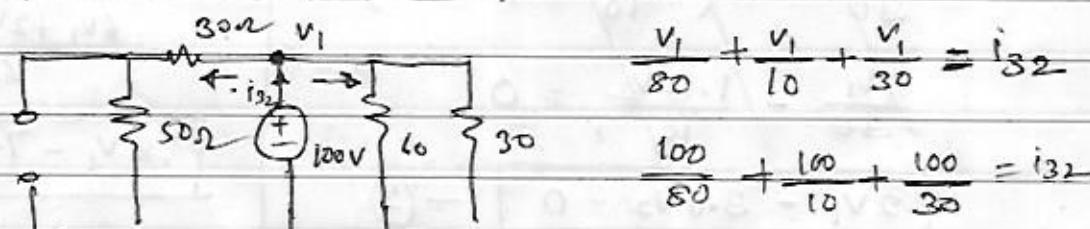
$$i_{31} = -\left(\frac{50 \times 8}{80}\right) = -5A$$



$$\frac{v_1}{80} + \frac{v_1}{10} + \frac{v_1}{30} = i_{32}$$

$$\frac{100}{80} + \frac{100}{10} + \frac{100}{30} = i_{32}$$

$$i_{32} = 6.25A$$

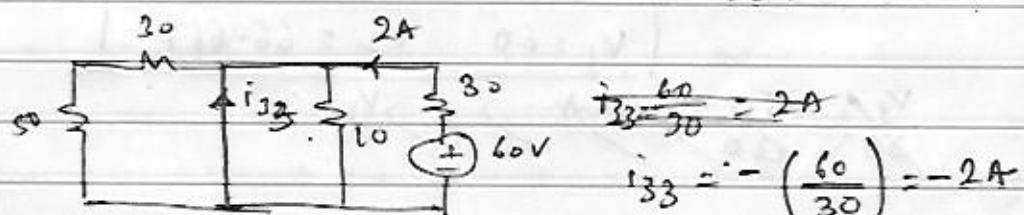


$$\frac{60}{30} = 2A$$

$$i_{33} = -\left(\frac{60}{30}\right) = -2A$$


$$i_3 = -5 - 2 + 6.25 = -0.75A //$$

DATE

(20)

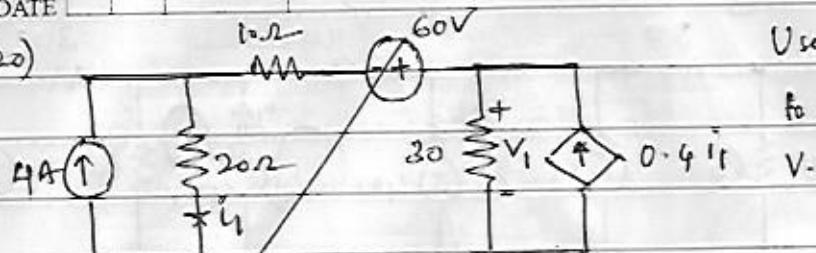

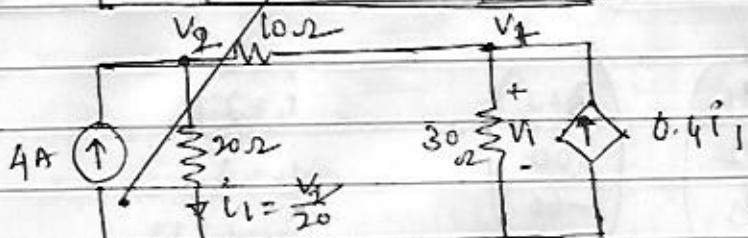Use principle of superposition
to determine the voltage labelled V.



$$-4 + \frac{V_1}{20} + \frac{V_1 - V_2}{10} = 0$$

$$\frac{V_1}{20} + \frac{V_1}{10} - \frac{V_2}{10} = 4$$

$$V_1 + 2V_1 - 2V_2 = 4 \times 20$$

$$3V_1 - 2V_2 = 80 \quad \text{--- (1)}$$

$$\begin{bmatrix} \frac{1}{10} + \frac{1}{20} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{30} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \end{bmatrix}$$

$$\frac{V_2}{30} + \frac{V_2 - V_1}{10} + 0.4i_1 = 0$$

$$\frac{V_2}{30} + 3V_2 - 3V_1 = 0.4 \left(\frac{V_1}{20} \right)$$

$$-3V_1 + 0.4V_1 + 4V_2 = 0$$

$$\therefore i_1 = V_1/20$$

$$\frac{V_2}{20} + \frac{V_2 - V_1}{10} = 4 \Rightarrow V_2 + 2V_2 - 2V_1 = 4 \times 20$$

$$-2V_1 + 3V_2 = 80 \quad \text{--- (1)}$$

$$\frac{V_1 - V_2}{10} + \frac{V_1}{30} + 0.4 \left(\frac{V_2}{20} \right) = 0$$

$$\frac{V_1 - V_2}{10} + \frac{V_1}{30} - 0.4 \times \frac{V_2}{20} = 0$$

$$\frac{V_1}{10} - \frac{V_2}{10} - \frac{V_1}{30} - 0.02V_2 = 0$$

$$\frac{V_1}{10} + \frac{V_1}{30} - \frac{V_2}{10} - 0.4V_2 = 0$$

$$\frac{3V_1 - V_1}{30} - \left(\frac{V_2 + 0.02 \times 10V_2}{10} \right) = 0$$

$$\frac{6V_1 + 2V_1 - 6V_2 - 3 \times 0.4V_2}{60} = 0$$

$$\frac{2V_1}{30} - \frac{1.2V_2}{10} = 0$$


$$8V_1 - 7.2V_2 = 0 \quad \text{--- (2)}$$

$$[2V_1 - 3.6V_2 = 0] \quad \text{--- (2)}$$

$$\boxed{V_1 = 60 \quad V_2 = 66.667}$$

$$\frac{V_1}{30} = \frac{60}{30} \Rightarrow 2A \therefore \therefore V_1 =$$

(18)

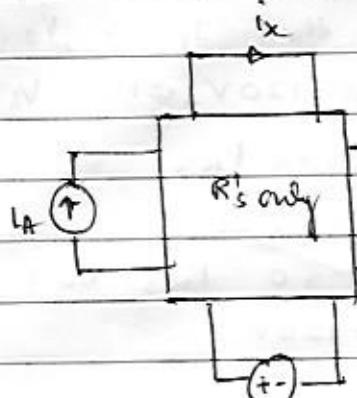With source i_A and V_B on and $V_C = 0$

$$i_x = 20$$

With source i_A and V_C on, $V_B = 0$ $i_x = 5A$ With all sources off, $i_x = 12A$ a) find i_x if only source operating
is a) i_A b) V_B c) V_C .b) find i_x if i_A and V_C are doubledin magnitude and V_B is reversed

$$\text{So (i)} \quad i_A(i_x) + V_B(i_x) = 20 \quad i_x(i_A) + i_x(V_B) = 20 \quad \text{--- (1)}$$

$$\text{ii) } i_A(i_x) + V_C(i_x) = -5 \quad i_x(i_A) + i_x(V_C) = -5 \quad \text{--- (2)}$$

$$\text{iii) } i_A(i_x) + V_B(i_x) + V_C(i_x) = 12A \quad i_x(i_A) + i_x(V_B) + i_x(V_C) = 12 \quad \text{--- (3)}$$

Find \rightarrow

$$\boxed{i_x(i_A) = 8 \quad i_x(V_B) = 17 \quad i_x(V_C) = -8}$$

1	1	0	i_A	20
1	0	1	V_B	-5
1	1	1	V_C	12

By solving
 $i_x(i_A) = 3 \quad i_x(V_B) = 17 \quad i_x(V_C) = -8 A$

if i_A is operating $i_x(i_x) = 12$

$$3 i_x = 12 \quad i_x = 12/3 = 4 A$$

if V_B is operating $V_B(i_x) = 12 \quad i_x = 12/V_B = 12/17 = 0.705A$ if V_C is operating $V_C(i_x) = 12 \quad i_x = 12/V_C = 12/-8 = -1.5$


~~$$b) \quad 2i_x(i_A) + V_B(i_x) + 2i_x(V_C) = 2(3) - 17 + 2(-8) = 0$$~~
~~$$i_x(V_B) = 6 - 17 + 16 = -5$$~~
~~$$2i_x(i_A) - i_x(V_B) + 2i_x(V_C) = -27$$~~

$$i_x(i_A) = 8 \quad i_x(V_B) = -5 \quad i_x(V_C) = -8$$

$$2i_x(i_A) - i_x(V_B) + 2i_x(V_C) = 2(3) - 17 + 2(-8)$$

$$= -27$$

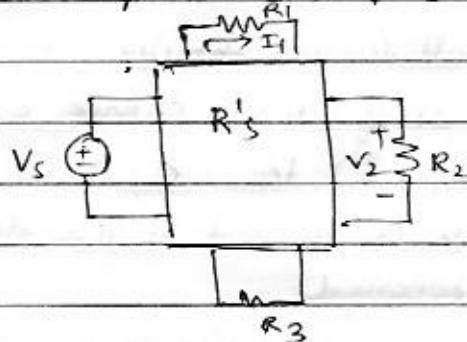1) for linear ckt shown in fig it is found that $I_1 = 3A$, $V_2 = 50V$ and power delivered to $R_3 = 60W$, when $V_s = 120V$. when V_s is changed to $105V$ find new values of I_1 , V_2 , P_{R_3} .



$$I_1 = 3A \quad V_2 = 50 \quad P_{R_3} = 60 \text{ Watts.}$$

$$V_s = 120V$$

If the n/w consists of linear elements the response that is current or voltage is directly proportional to voltage or current same

$$I_1 \propto V_s, \quad I_1 = K_1 V_s \quad 3 = K_1 (120) \quad K_1 = \frac{3}{120} = \frac{1}{40}$$

$$V_2 \propto V_s \quad V_2 = K_2 V_s \Rightarrow 50 = K_2 (120) \Rightarrow K_2 = \frac{50}{120} = \frac{5}{12}$$

$$P_{R_3} = I_3^2 R_3 = \left(\frac{V_s}{R_3}\right)^2 R_3 = \frac{V_s^2}{R_3}$$

$$\therefore P_{R_3} \propto V_s^2 \quad P_{R_3} = K_3 V_s^2$$

$$60 = K_3 (120)^2$$

$$\frac{60}{(120)^2} \quad K_3 = \frac{1}{240}$$

∴ When V_s is changed to $105V$.

$$I_1 = K_1 (V_s) = \left(\frac{1}{40}\right) 105 = 2.625 A$$


$$V_2 = K_2 (V_s) = \left(\frac{5}{12}\right) 105 = 43.75 V$$

$$P_{R_3} = K_3 V_s^2 = \left(\frac{1}{240}\right) \frac{105^2}{\cancel{105}} = \underline{\underline{45.9375 W.}}$$

52.5

DATE

(2a) Use superposition principle find voltage labelled

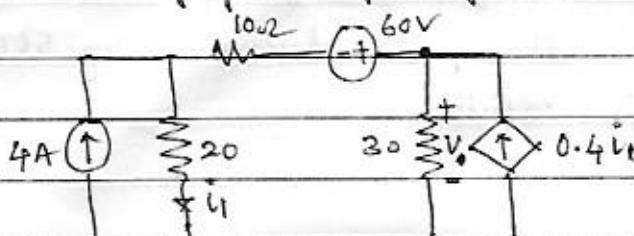

Node 1

$$\frac{V_2}{20} + \frac{V_2 - V_1}{10} - 4 = 0$$

$$V_2 + 2V_2 - 2V_1 = 80$$

$$-2V_1 + 3V_2 = 80 \quad \text{--- (1)}$$

$$\frac{V_1}{30} + \frac{(V_1 - V_2)}{10} - 0.4i_1 = 0$$

$$\frac{V_1}{30} + \frac{V_1}{10} - \frac{V_2}{10} - 0.4 \frac{V_2}{20} = 0$$

$$\frac{2V_1}{60} + 6V_1 - 6V_2 - 0.4(3)V_2 = 0$$

$$\therefore [V_1 = 60]$$

$$V_2 = 66.667$$

$$[8V_1 - 7.2V_2 = 0] \quad \text{--- (2)}$$

 $V_1 = 60V$ due to 4A current source

$$\frac{V_2 - 60}{30} + \frac{V_2}{30} - 0.4 \left(\frac{V_2 - 60}{30} \right) = 0$$

$$2V_2 - 0.4V_2 - 60 + 0.4 \times 60 = 0$$


$$1.6V_2 = 60 - 0.4 \times 60$$

$$[V_2 = 22.5]$$



$$V = V_1 + V_2 = 60 + 22.5 = 82.5V$$

DATE


(21)

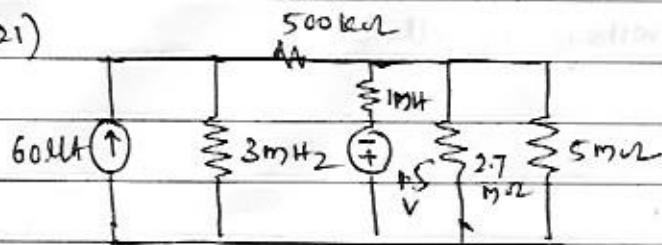

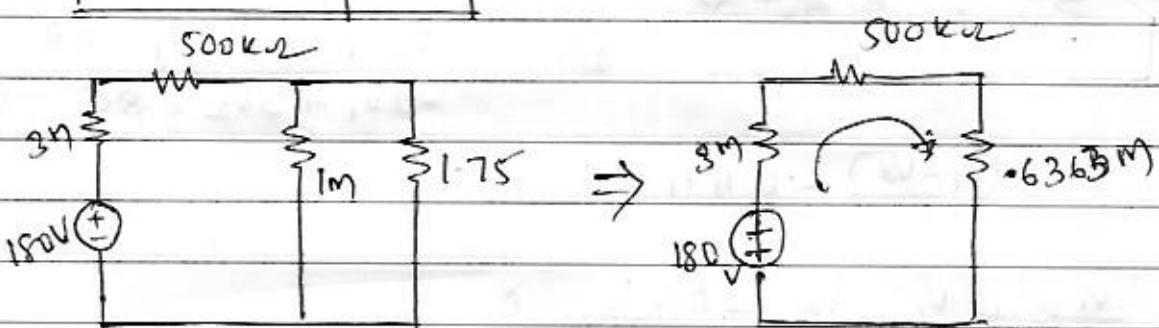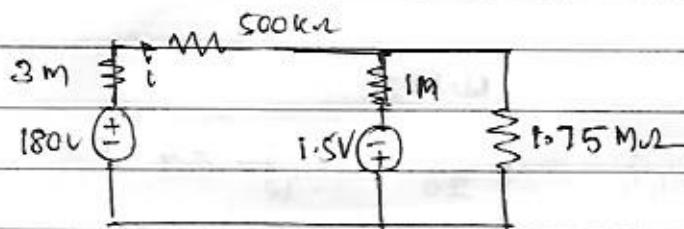Use principle of superposition to find
the power dissipated by $500\text{k}\Omega$
resistor



$$i_1 = 0.0435 = 43.51 \mu A$$

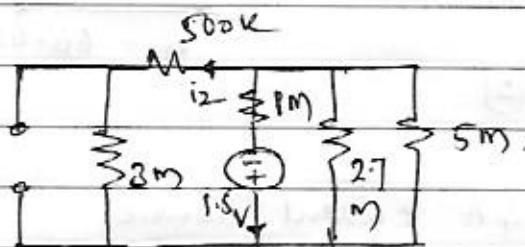

$$i_2 = 0.6998 \mu A$$

$$\begin{aligned} \frac{V_1}{500\text{k} + 3\text{m}} + \frac{V_1 + 1.5V}{1\text{m}} + \frac{V_1}{1.75\text{m}} &= 0 \\ \frac{V_1}{3.5\text{m}} + \frac{V_1}{1\text{m}} + \frac{1.5}{1\text{m}} + \frac{V_1}{1.75\text{m}} &= 0 \\ 1.75\text{m}V_1 + 6.125\text{m}V_1 &= -1.5 \times 6.125\text{m} + V_1 \times 3.5\text{m} \\ 11.375\text{m}V_1 - 9.1875\text{m} &= 0 \\ V_1 &= -0.80769 \end{aligned}$$

$$i_2 = -0.237 \mu A$$

$$\begin{aligned} i &= i_1 - i_2 = 43.51 \mu A - (-0.237 \mu A) \\ i &= 43.747 \mu A \end{aligned}$$

$$\begin{aligned} P_{500\text{k}} &= i^2 R = (43.747 \times 10^{-6})^2 \times 500\text{k} \\ &= 9.56 \times 10^{-4} \end{aligned}$$

$$P_{500\text{k}} = 9.56 \mu W$$

DATE

(X) complete the table given

I_1	I_2	Ex No.	V_1	V_2	I_1	I_2
V_1	V_2	1	50	100	-1	27
		2	100	50	7	24
Bilateral		3	200	0	-	-
		4			20	0
		5			10	30

$I_1' \propto V_1$	$I_2' \propto V_1$	$I_1'' \propto V_2$	$I_2'' \propto V_2$
$I_1' = K_1 V_1$	$I_2' = K_2 V_1$	$I_1'' = K_3 V_2$	$I_2'' = K_4 V_2$

$$I_1 = I_1' - I_1'' = K_1 V_1 - K_3 V_2 \quad \text{--- (1)}$$

$$I_2 = I_2' - I_2'' = K_2 V_1 - K_4 V_2 = -K_2 V_1 + K_4 V_2 \quad \text{--- (2)}$$

$$K_1 V_1 - K_3 V_2 = I_1 \quad \text{--- (1')}$$

$$-K_2 V_1 + K_4 V_2 = I_2 \quad \text{--- (2')}$$

$$\text{can (1) & (2)} \quad V_1 = 50 \quad V_2 = 100 \quad I_1 = -1 \quad I_2 = 27 \quad I_1 = 7$$

Using $50K_1 - 100K_3 = -1$ } Using eq 2 (1)

eq 2 (1) $100K_2 - 50K_4 = 7$ }

$K_1 = 0.1$	$K_3 = 0.06$	$0.1V_1 - 0.06V_2 = I_1$
-------------	--------------	--------------------------

can (1) & (2) for find K_2, K_4 using eq 2 (2).

$$-K_2 V_1 + K_4 V_2 = I_2$$

$$-K_2 50 + K_4 100 = 27$$

$$-K_2 100 + K_4 50 = 24$$

11/4

$$(5) \quad I_1 = 10 \quad \& \quad I_2 = 30$$

$$V_1 = 133.8$$

$K_2 = -0.14$	$K_4 = 0.2$
---------------	-------------

$$V_2 = 56.33V$$

(3) when $V_1 = 200 \quad V_2 = 0$.

$$I_1 = K_1 V_1 - K_3 V_2 = 0.1 \times 200 + 0.14 \times 0 = 20A$$

$$I_2 = -K_2 V_1 + K_4 V_2 = +0.14 \times 200 + 0.2 \times 0 = 28A$$


(4) when $I_1 = 20 \quad I_2 = 0$; $20 = 0.1 V_1 - 0.06 V_2$

$$0 = +0.14 V_1 + 0.2 V_2$$


$$V_1 = 140 \quad V_2 = -98.59$$

DATE


- Q) Determine current through 2Ω resistor of net shown in fig using superposition.

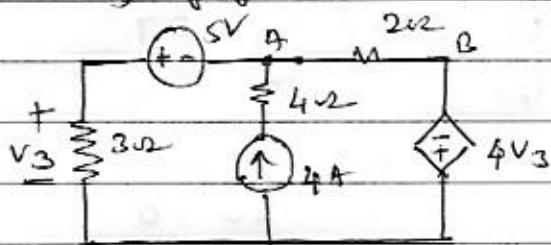

Consider 5V

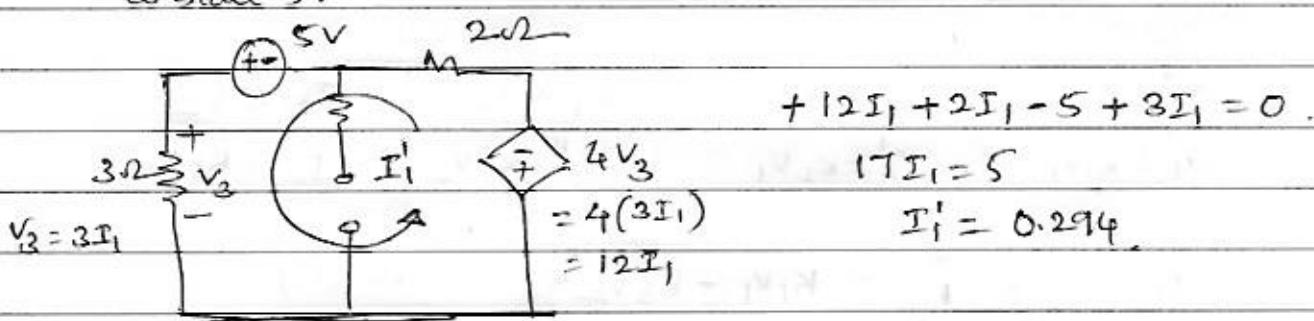

Consider 4A case

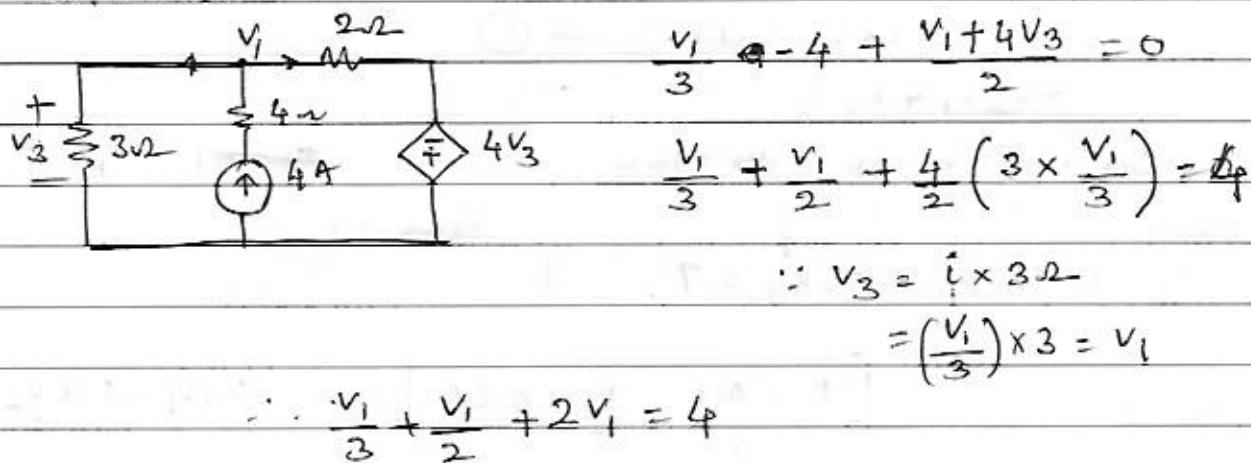


$$5V_1/2 = I'' \quad I'' = 5(1.414)/2 = 3.529$$


$$I = -I'_1 + I''_1 = -0.294 + 3.529$$

$$I = 3.235 \text{ from A to B}$$


DATE _____

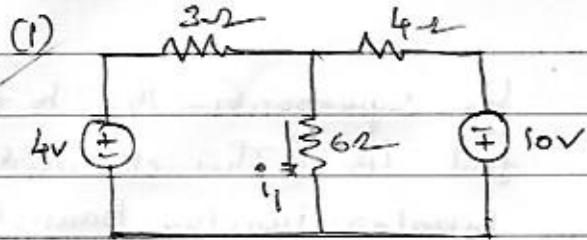

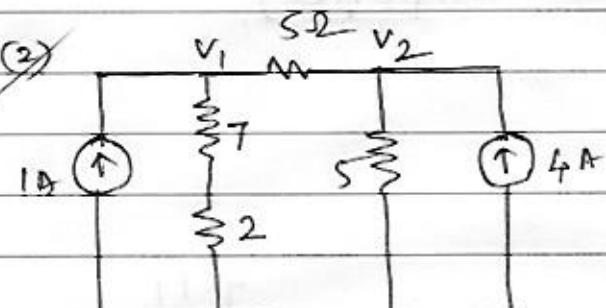
Find Contribution of the 4V and 10V source to the current labelled i_1



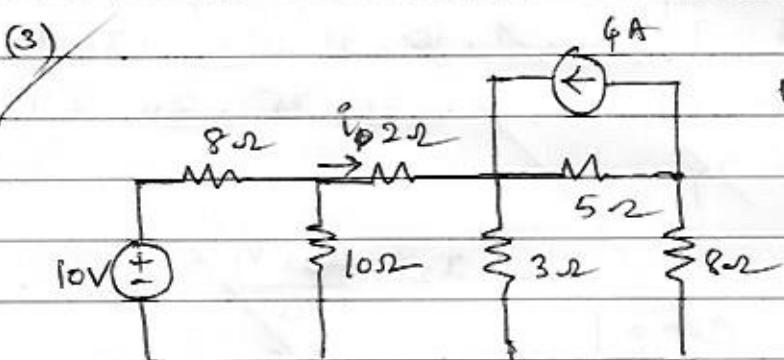
Determine contribution of 1A source to V_1 and calculate total current through the 7Ω resistor



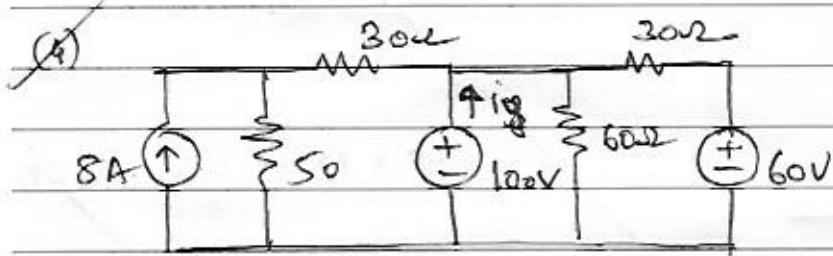
Use principle of superposition to determine the current labelled i_y



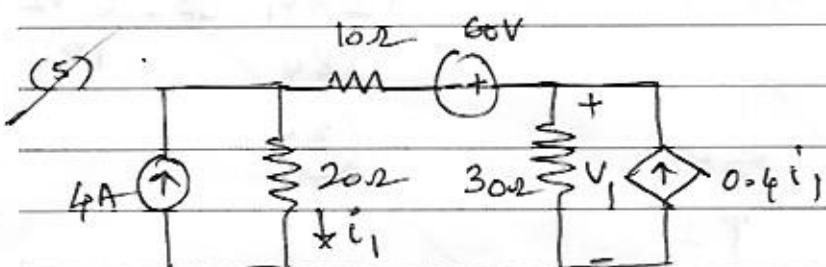Use superposition to determine the current labelled i_3



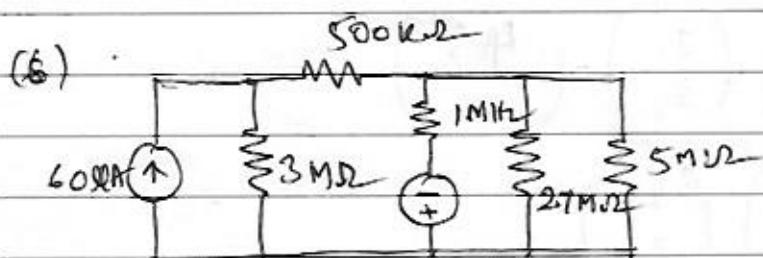
Use principle of superposition to determine the voltage labelled V .



Use principle of superposition to find the power - dissipated by $500\text{k}\Omega$ resistor

DATE

(7)

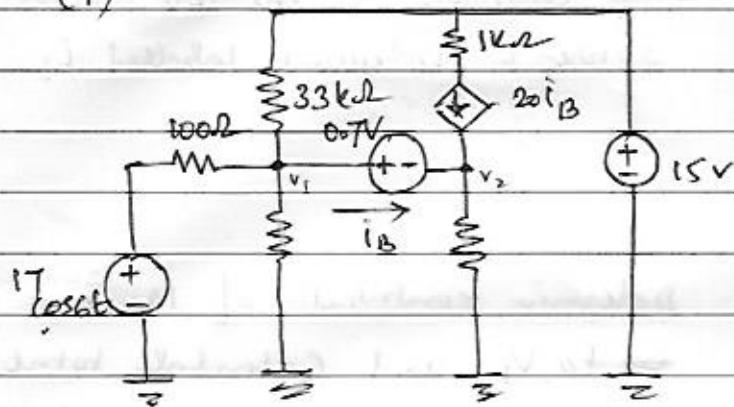

Use superposition to find i_B (This circuit model is bipolar junction transistor amplifier).

Verify

9-17.

~~1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 24, 25, 26, 27, 28, 29, 30, 31, 32, 33, 34.~~

$$I_2 = \frac{A_{21} V_1}{R}$$

[9-17] [9-20] [9-28]

$$= \frac{6}{180} \times 45$$

9-17


9-20

9-28

Thevenins

$$18 \times 72 - 36 = 180$$
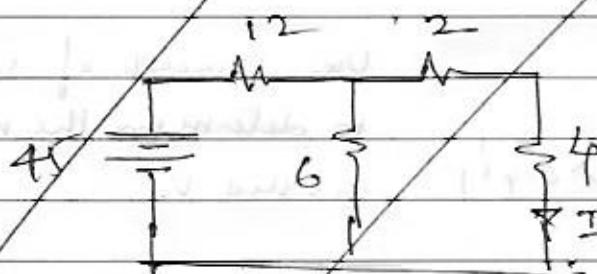
$$\frac{12 \times V_1}{180} - \frac{6 \times V_2}{180}$$



$$\begin{pmatrix} 18 & -6 \\ -6 & 12 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 45 \\ 0 \end{pmatrix}$$

$$\begin{pmatrix} 45 & -6 \\ 0 & 12 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

DATE Reciprocity

Suppose

$$[Z][I] = [V] \quad (1) \quad [V] \rightarrow \text{Independent source excluding initial cond: sources}$$

and

$$\begin{pmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix}$$

where $[Z]$ is symmetric matrix - ie Network having R, L, C and transformer but not dependent sources.

$$\begin{pmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{12} & Z_{22} & Z_{23} \\ Z_{13} & Z_{23} & Z_{33} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} \quad \Delta = \begin{pmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{12} & Z_{22} & Z_{23} \\ Z_{13} & Z_{23} & Z_{33} \end{pmatrix}$$

where Cramus & Expansion by minors.

$$I_k = \frac{D_k}{\Delta} = \frac{V_1 \Delta_{1k} + V_2 \Delta_{2k} + V_3 \Delta_{3k}}{\Delta} \quad \text{where } k=1, 2, \dots \text{ loops}$$

$$k=1 \quad I_1 = \frac{D_1}{\Delta} = \frac{V_1 \Delta_{11} + V_2 \Delta_{21} + V_3 \Delta_{31}}{\Delta} = \frac{\Delta_{11} V_1 + \Delta_{21} V_2 + \Delta_{31} V_3}{\Delta} \quad (1)$$

$$D_1 = \begin{pmatrix} V_1 & Z_{12} & Z_{13} \\ V_2 & Z_{22} & Z_{23} \\ V_3 & Z_{32} & Z_{33} \end{pmatrix} \quad \text{where } \Delta_{11} = \begin{pmatrix} Z_{22} & Z_{23} \\ Z_{23} & Z_{33} \end{pmatrix} \quad \Delta_{21} = \begin{pmatrix} Z_{12} & Z_{13} \\ Z_{23} & Z_{33} \end{pmatrix} \quad \Delta_{31} = \begin{pmatrix} Z_{12} & Z_{13} \\ Z_{22} & Z_{23} \end{pmatrix}$$

$$k=2 \quad I_2 = \frac{D_2}{\Delta} = \frac{\Delta_{12} V_1 + \Delta_{22} V_2 + \Delta_{32} V_3}{\Delta} \quad (2)$$

$$D_2 = \begin{pmatrix} Z_{11} & V_1 & Z_{13} \\ Z_{12} & V_2 & Z_{23} \\ Z_{13} & V_3 & Z_{33} \end{pmatrix} \quad \text{where } \Delta_{12} = \begin{pmatrix} Z_{12} & Z_{23} \\ Z_{13} & Z_{33} \end{pmatrix} \quad \Delta_{22} = \begin{pmatrix} Z_{11} & Z_{13} \\ Z_{13} & Z_{33} \end{pmatrix} \quad \Delta_{32} = \begin{pmatrix} Z_{11} & Z_{13} \\ Z_{12} & Z_{23} \end{pmatrix}$$

$$k=3 \quad I_3 = \frac{D_3}{\Delta} = \frac{\Delta_{13} V_1 + \Delta_{23} V_2 + \Delta_{33} V_3}{\Delta} \quad (3)$$

$$D_3 = \begin{pmatrix} Z_{11} & Z_{12} & \cancel{V_1} \\ Z_{12} & Z_{22} & \cancel{V_2} \\ Z_{13} & Z_{23} & \cancel{Z_{33}} \\ V_3 & & \end{pmatrix} \quad \text{where } \Delta_{13} = \begin{pmatrix} Z_{12} & Z_{22} \\ Z_{13} & Z_{23} \end{pmatrix} \quad \Delta_{23} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{13} & Z_{23} \end{pmatrix} \quad \Delta_{33} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{12} & Z_{22} \end{pmatrix}$$

Now if $V_1 = V_2 = 0$ in eq 2 (1) then

$$I_1 = \frac{\Delta_{31} V_3}{\Delta}$$

If $V_2 = V_3 = 0$ in eq 2 (3) then $I_3 = \frac{\Delta_{13} V_1}{\Delta}$

$$\text{ie } I_1 = \frac{\Delta_{13}}{\Delta} V_3 \quad \text{and } I_3 = \frac{\Delta_{13}}{\Delta} V_1$$

$$\text{where } \Delta_{13} = \begin{vmatrix} Z_{12} & Z_{13} \\ Z_{22} & Z_{23} \end{vmatrix} \quad \Delta_{13} = \begin{vmatrix} Z_{12} & Z_{22} \\ Z_{13} & Z_{23} \end{vmatrix}$$


$$= Z_{12}Z_{23} - Z_{13}Z_{22} \quad = Z_{12}Z_{23} - Z_{13}Z_{22}$$

$$\therefore \Delta_{31} = \Delta_{13}$$

$$\therefore \frac{I_1}{V_3} = \frac{\Delta_{13}}{\Delta} \quad \text{and } \frac{I_3}{V_1} = \frac{\Delta_{13}}{\Delta}$$

In general, for a n/w with ~~k-loops~~ L-loops., L = 1, ..., k.
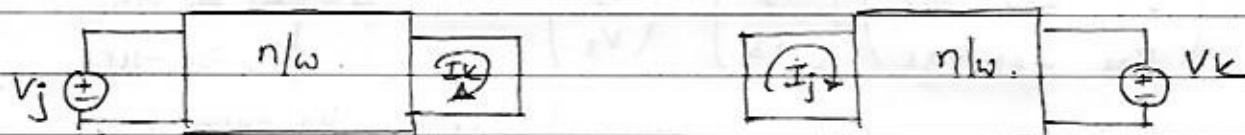
$$\left[\frac{I_k}{V_j} = \frac{I_j}{V_k} \right] \quad \text{if } V_j \neq V_k.$$



- Suppose V_j is the only source in the n/w. This results in the current I_k in the k^{th} loop.
- If the source is now moved to the k^{th} loop, then the current in the j^{th} loop is $I_j = I_k$.
- This is the principle of Reciprocity.
- The ratio of the response transform to excitation transform is invariant to an interchange of the position in the n/w of the excitation and response.
- When the above property holds good, the n/w is reciprocal otherwise the n/w is said to be non reciprocal.


conds of the n/w to be reciprocal

- 1) The impedance matrix should be ~~reciprocal~~ symmetric
ie n/w having R, L, C and transformer as linear elements but not dependent sources. - Network should not have dependent source (Controlled sources)
- 2) There should be only one source of excitation in the n/w.
 \therefore there should be no initial cond's transformed sources, meaning the n/w elements must be initially relaxed or in zero state.

DATE


* Reciprocity theorem.

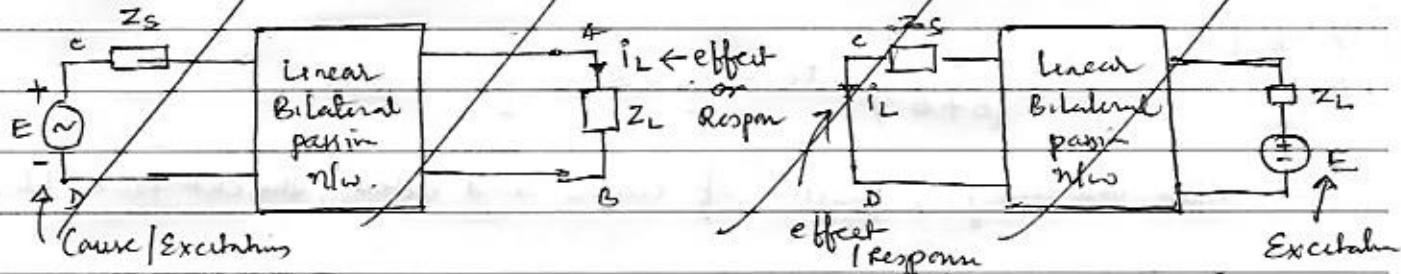The theorem states that in a linear bilateral single source network the ratio of cause to effect or effect to cause remain constant even if positions of cause and effect are interchanged.




Ex(1) In the ckt shown in fig find V_x and prove reciprocity.

$$I = 5 \angle 90^\circ$$

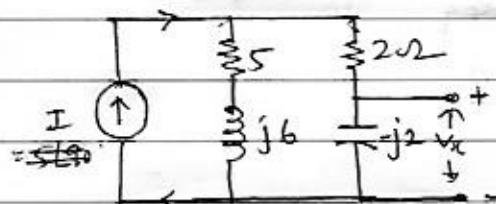

$$\Sigma = 5 \angle 90^\circ$$
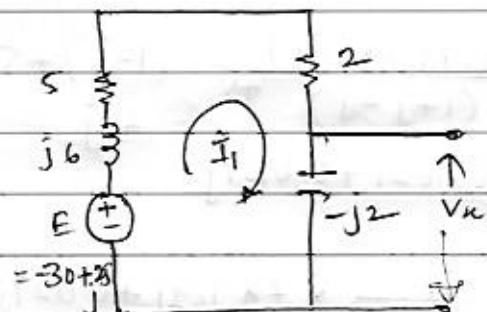
$$E = I \times (s + j6) = js \times (s + j6) = -30 + 25j$$



$$I_1 = \frac{E}{Z} = \frac{-30 + 25j}{(7 + 4j)} = -1.692 + 4.538j$$



$$V_x = I_1 \times -j2$$

$$= (-1.692 + 4.538j) \times -j2$$

$$= 9.076 + 3.384j$$

$$= 9.686 \angle 20.45^\circ$$

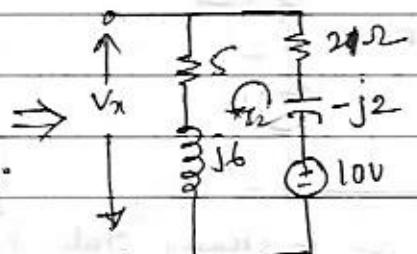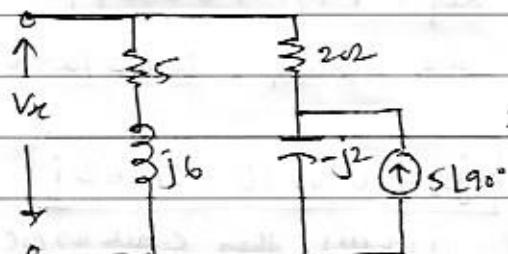To verify reciprocity theorem of cause and effect are interchanged
After interchanging the positions ckt look like



$$I_2 = \frac{10}{7.25 + 4j}$$
 ~~$= 1.076 + 0.6152j$~~
 ~~$= 0.39 + 0.624j$~~


$$V_x = I_2 \times (s + j6)$$

~~$= -1.575 + 2.652j$~~

$$= 1.69 + 9.538j$$

$$V_x = 9.076 + 3.384j = \underline{\underline{9.686 \angle 20.45^\circ}}$$

DATE

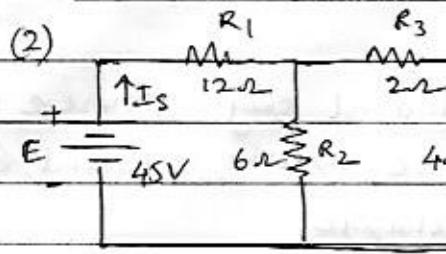


$$R_{eq} = \left(\frac{6 \times 6}{6+6} \right) + 12 = 15\Omega$$

$$I_s = \frac{E}{R_{eq}} = \frac{45}{15} = 3A$$


$$\begin{pmatrix} 12 & 6 \\ 6 & 12 \end{pmatrix} I = \left(\frac{6}{6+6} \right) \times I_s = \frac{6}{12} \times 3 = \frac{3}{2} = 1.5A$$

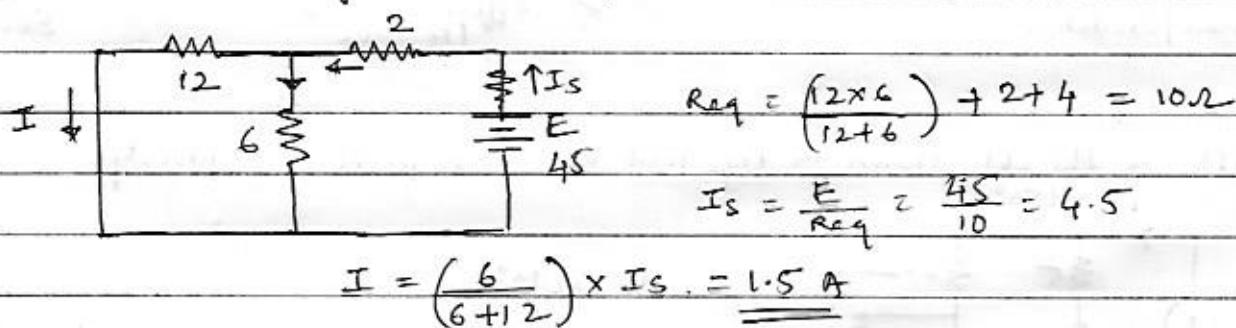After interchanging position of cause and effect, the circuit looks like



$$I_s = \frac{E}{R_{eq}} = \frac{45}{10} = 4.5$$
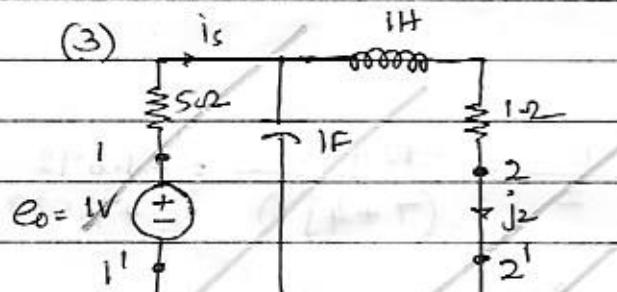
$$I = \left(\frac{6}{6+12} \right) \times I_s = \underline{\underline{1.5A}}$$



$$Z_{eq} = \frac{(1+j) \times (-j)}{(1+j-j)} = \frac{(1-j)}{j} = 6-j$$


$$I_s = 0.1621 + 0.027j$$

$$(i) \quad X_L = \omega L = 1 \times 1 = 1\Omega \quad j_2 = \frac{-j}{(1+j)-j} \times (0.1621 + 0.027j)$$

$$X_C = \omega C = 1 \times 1 = 1 \quad X_C = -j$$

$$j_2 = -0.027 - 0.162j$$

After interchanging


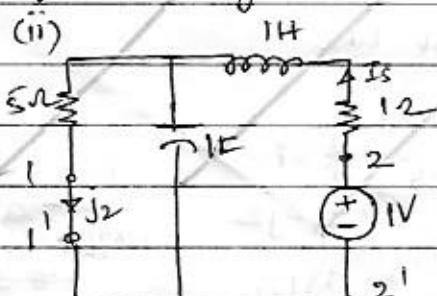


$$Z_{eq} = 1.192 + 0.0384j$$

$$I_s = \frac{1}{Z_{eq}} = 0.8378 - 0.027j$$


$$j_2 = 0.0270 - 0.162j$$

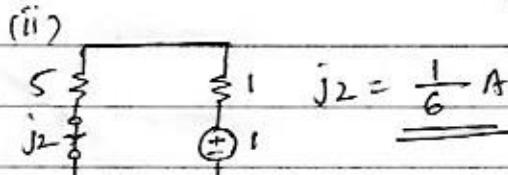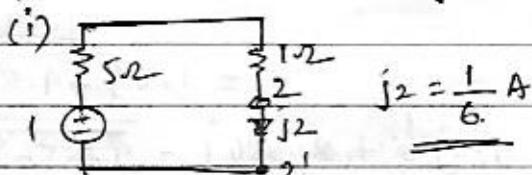If L & C are in steady state for (i) & (ii), they can act as open circuits as S.C



DATE

OR

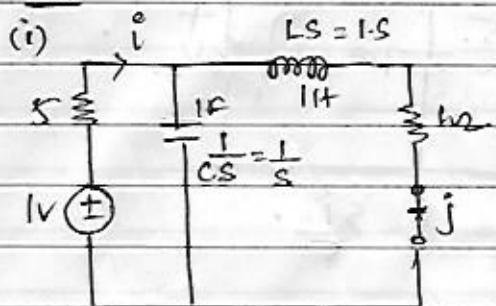

$$Z_{eq} = \left[\frac{(1+s) \times \left(\frac{1}{s}\right)}{\left(1+s+\frac{1}{s}\right)} \right] + s$$

$$= \left[\frac{\left(\frac{1}{s}+1\right)}{\left(s+s^2+1\right)} \right] + s = \left[\frac{(1+s)}{s(s^2+s+1)} \right] s$$

$$Z_{eq} = \left(\frac{1+s}{s^2+s+1} \right) + s = \frac{(1+s)+s(s^2+s+1)}{s^2+s+1}$$

$$= \frac{5s^2+6s+6}{s^2+s+1}$$

~~$$i = \frac{1}{Z_{eq}} = \frac{s^2+s+1}{5s^2+6s+6}$$~~


$$j_2 = \frac{\left(\frac{1}{s}\right)}{\left(\frac{1}{s}+1+s\right)} \times i$$

$$= \frac{\left(\frac{1}{s}\right)}{\left(1+s+s^2\right)} \times \frac{s^2+s+1}{5s^2+6s+6}$$

$$j = \cancel{\frac{5s^2+6s+6}{s}} \quad \text{if } s=0 \quad j = 0+0+6$$



$$= \left(\frac{1}{s}\right) \times \left(\frac{1}{s^2+s+1}\right) \times \cancel{\frac{s^2+s+1}{5s^2+6s+6}}$$
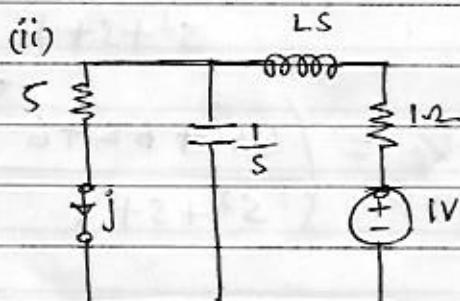
$$j = \frac{1}{5s^2+6s+6} \quad \text{if } s=0 \quad j = \frac{1}{6}$$



$$j = \frac{1}{6}$$

DATE

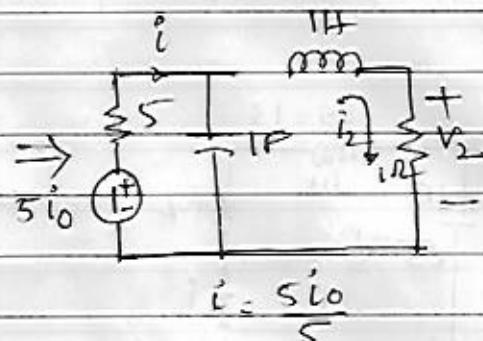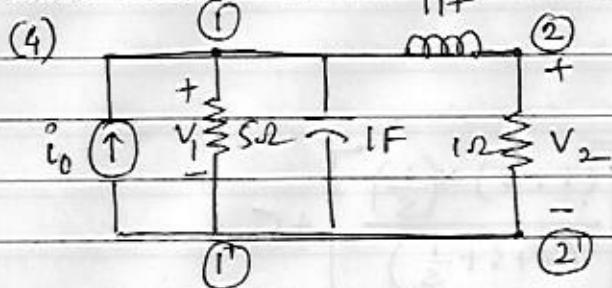

$$i_2 = \frac{(-j)}{(1+j)} \times \frac{5i_0}{s} = -\frac{j}{s} (i_0)$$

$$Z_{eq} = \frac{(1+Ls) \times \frac{1}{Cs}}{(1+Ls + \frac{1}{Cs})} + s$$

$$= \frac{Cs + Ls(\frac{1}{Cs} + \frac{L}{C})}{Cs + LCS^2 + 1} + s$$

$$= \frac{1+Ls}{Cs} \times \frac{Cs}{Cs + LCS^2 + 1} + s$$

$$= \frac{1+Ls + s(Cs + LCS^2 + 1)}{Cs + LCS^2 + 1}$$

$$= \frac{5Cs + 5LCS + 5 + 1 + LS}{LCS^2 + Cs + 1}$$

$$\frac{(s+1) \times \frac{1}{s}}{s+1 + \frac{1}{s}} = \frac{(s+1)}{(s^2 + s + 1)} + s$$


$$= \frac{s+1 + s(s^2 + s + 1)}{s^2 + s + 1}$$

$$Z_{eq} = \frac{(5s^2 + 6s + 6)}{s^2 + s + 1}$$

4

DATE

2) In netw shown find voltage V_x and verify reciprocity thm.

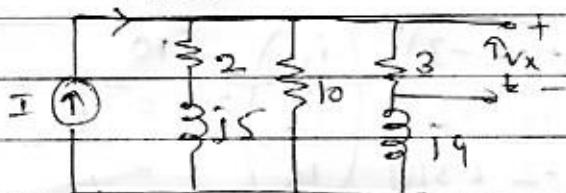 $\Sigma L = 90$ 

$$\begin{array}{c}
 \text{Circuit diagram:} \\
 \text{Top branch: } 2 \parallel 3j5 \parallel 10 \parallel 3 \parallel 9j9 \parallel V_x \\
 \text{Bottom branch: } E + \text{Dep. Source} \\
 \text{Middle branch: } i_1 \\
 \text{Currents: } i_2 \\
 \text{Dep. Sources: } 3j5, 9j9 \\
 \text{Voltage: } V_x
 \end{array}$$

$$\left[\begin{array}{cc|c} 12+j5 & -10 & i_1 \\ -10 & 13+j4 & i_2 \end{array} \right] = \left[\begin{array}{c} 25-j10 \\ 0 \end{array} \right]$$

$$= (25-j10)$$

$$I_2 = \frac{\Delta_{12}}{\Delta} \times V_1$$

$$\Delta = 36 + 113j$$

$$\left[\begin{array}{cc|c} 12+j5 & 25-j10 & \\ -10 & 0 & \end{array} \right]$$

$$\frac{13+j4}{(12+j5)(13+j4)-100} = \frac{13+j4}{36+113j} \\
 = 0.0654 - 0.942j$$

$$I_2 = \frac{-10}{\Delta} \times V_1 = 0.1635$$

$$= 0.5 - 6.76j$$

$$(12+j5)i_1 - 10i_2 = 25-j10 \quad \text{--- (1)}$$


$$(-10i_1 + (13+j4)i_2 = 0 \quad \text{--- (2)}$$

$$I_2 = \frac{D_2}{\Delta} = \frac{\left| \begin{array}{cc|c} 12+j5 & 25-j10 & \\ -10 & 0 & \end{array} \right|}{\left| \begin{array}{cc|c} 12+j5 & -10 & \\ -10 & 13+j4 & \end{array} \right|} = \frac{250-100j}{36+113j}$$

$$I_2 = +0.1635 - j2.26$$

$$V_x = 3i_2 = 6.81 \angle -94.13^\circ$$

$$\Sigma L = 90 = 0-j5$$

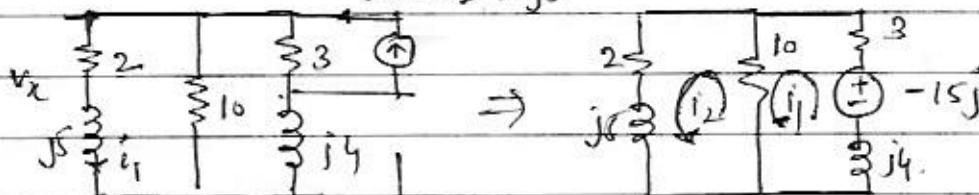


$$I_2 = \frac{D_2}{\Delta} = \frac{\left| \begin{array}{cc|c} 13+j4 & -15j & \\ -10 & 0 & \end{array} \right|}{\left| \begin{array}{cc|c} 13+j4 & -10 & \\ -10 & 12+j5 & \end{array} \right|} = \frac{-15j}{0} \\
 = -1.2 - 0.38j$$

$$\therefore V_x = i_2 \times (2+j5) = \frac{-0.5-6.76j}{6.81 \angle -94.13^\circ}$$

DATE

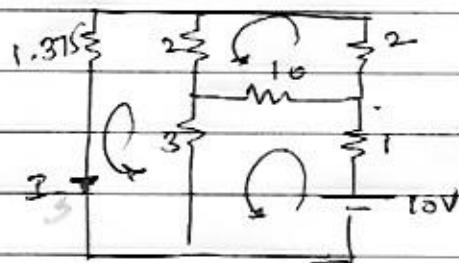③ In the circuit find current I and verify by superposition



$$\begin{pmatrix} 14 & -10 & -3 \\ -10 & 14 & -2 \\ -3 & -2 & 6.375 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \\ 0 \end{pmatrix}$$

$$I_3 = I = \frac{D_3}{\Delta} = \frac{\Delta_{13}}{\Delta} V_1 = \frac{-10 \cdot 14}{-10 \cdot 14 + 10 \cdot 3} \cdot 10$$

$$\begin{aligned} \Delta &= 14(14 \times 6.375 - 4) \\ &\quad + 10(-10 \times 6.375 - 6) \\ &\quad - 3(20 + 14 \times 3) \end{aligned}$$

$$= 310$$


$$= \frac{14 \cdot (-10 \cdot 14 + 10 \cdot 3)}{310}$$

$$= \frac{14(0) + 10(0) + 10(20 + 42)}{310}$$

$$= \frac{620}{310} = 2A$$

$$\boxed{I = 2A}$$

By interchanging the positions

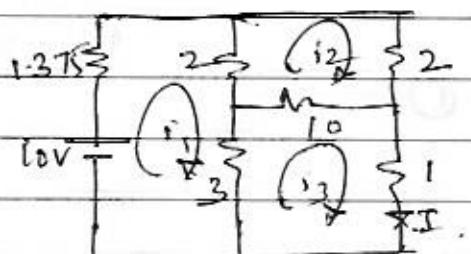

$$\begin{pmatrix} 6.375 & -2 & -3 \\ -2 & 14 & -10 \\ -3 & -10 & 14 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 10 \\ 0 \\ 0 \end{pmatrix}$$

$$I_3 = I = \frac{6.375 \cdot (-2 \cdot 14 + 10 \cdot 3)}{310}$$

$$= \frac{6.375(0) + 2(0) + 10(20 + 14 \times 3)}{310}$$

$$= \underline{\underline{2A}}$$

I.

DATE _____

Millman's Theorem


→ n voltage sources $E_1, E_2, E_3 \dots E_n$ with their series impedance connected in parallel may be replaced by single voltage source E with shunt impedance Z .

i.e Any number of parallel voltage sources reduced to one + voltage source.

→ Steps involved


- Convert voltage source to current sources.
- Combine all these current source and impedances.
- Convert resulting current source to voltage source.

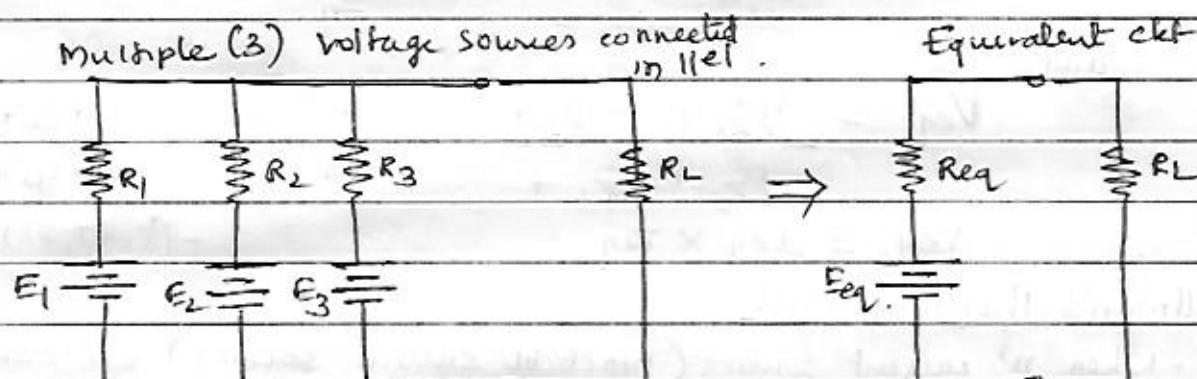Multiple (3) voltage sources connected in parallel.




Equivalent ckt

Step 1:

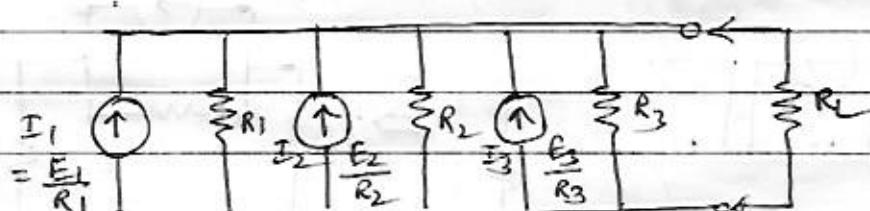

Step 2:

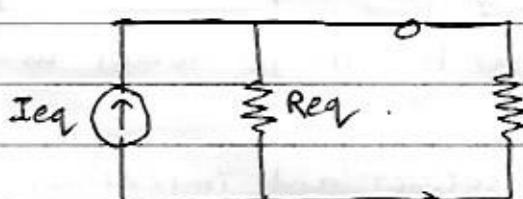

$$I_{eq} = I_1 + I_2 + I_3$$

$$= \frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3}$$

$$[I_{eq} = E_1 G_1 + E_2 G_2 + E_3 G_3] - (1)$$

$$\frac{1}{Req} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$G_T = G_1 + G_2 + G_3 \quad - (2)$$

$$I_{eq} = \sum_{i=0}^n E_i G_i \quad \sum_{i=0}^n \frac{E_i}{R_i}$$

$$\frac{1}{Req} = \sum_{i=0}^n \frac{1}{R_i} \quad - (3)$$

$$G_{eq} = \sum_{i=0}^n G_i$$

Step 3:

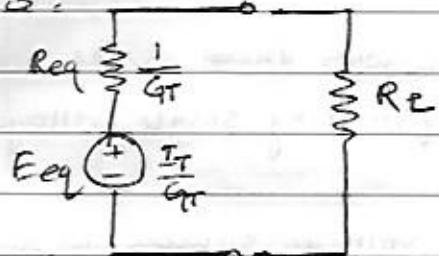

$$E_{eq} = \sum_{i=0}^n I_i G_i$$

$$\sum_{i=0}^n G_i$$

n = 3

$$E_{eq} = \frac{I_1 + I_2 + I_3}{G_1 + G_2 + G_3} = \frac{I_1 + I_2 + I_3}{G_T}$$

More generally,

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_n}$$

$$Z_{eq} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}}$$


and

$$V_{eq} = \frac{V_1/Z_1 + V_2/Z_2 + \dots + V_n/Z_n}{V/Z_1 + V/Z_2 + \dots + V/Z_n} = \frac{I_1 + I_2 + \dots + I_n}{G_1 + G_2 + \dots + G_n}$$

$$V_{eq} = I_{eq} \times Z_{eq} = (I_1 + I_2 + \dots + I_n) Z_{eq}$$

Millman's theorem - Dual

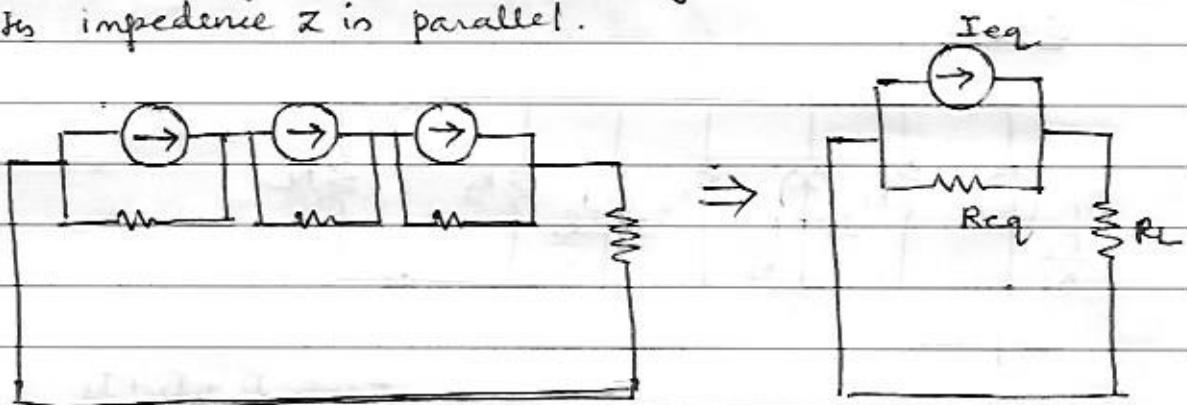- When 'n' current sources (practical current sources) are connected in series, they can be replaced by single current source with impedance Z in parallel.





Step 1: Convert all current sources to voltage sources using source transformation.

Step 2: Combine all voltage sources and impedances.

to get E_{eq} & Z_{eq}

Step 3: Convert E_{eq} & Z_{eq} to equivalent current source I_{eq} and Z_{eq} .

DATE

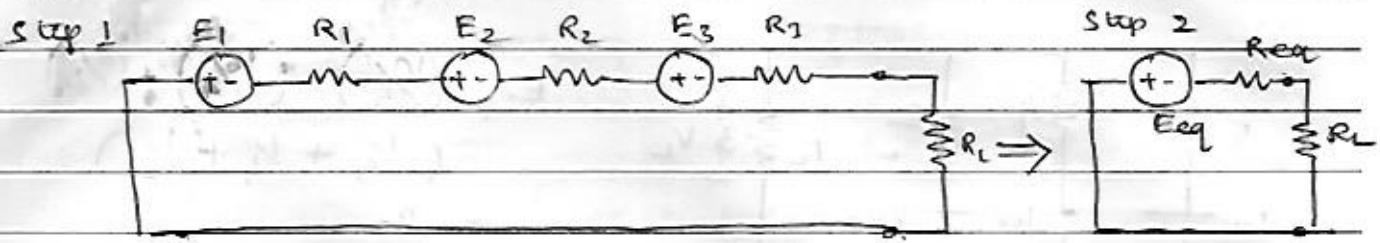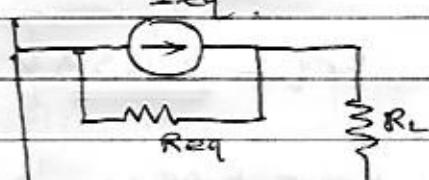Step 3: 

$$E_{eq} = E_1 + E_2 + \dots + E_n \\ = I_1 R_1 + I_2 R_2 + \dots + I_n R_n \\ R_{eq} = R_1 + R_2 + \dots + R_n.$$


$$I_{eq} = \frac{E_{eq}}{R_{eq}} = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$

More generally

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$

$$I_{eq} = \frac{E_1 + E_2 + \dots + E_n}{Z_1 + Z_2 + \dots + Z_n} = \frac{I_1 Z_1 + I_2 Z_2 + \dots + I_n Z_n}{Z_{eq}}$$

Example (1)

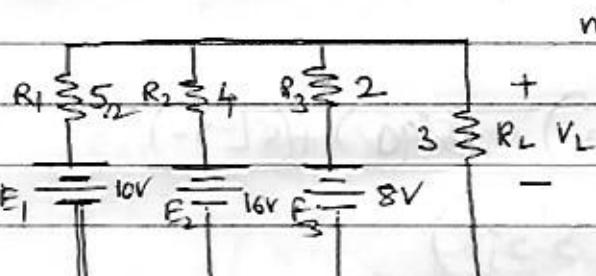


$n = 3$

$E_{eq} = \frac{\sum_{i=0}^3 I_i}{\sum_{i=0}^3 G_i} = \frac{I_1 + I_2 + I_3}{G_1 + G_2 + G_3}$

$E_{eq} = \frac{E_1/R_1 + E_2/R_2 + E_3/R_3}{1/R_1 + 1/R_2 + 1/R_3}$


$E_{eq} = \frac{(10/5) + (16/4) + (8/2)}{(1/5 + 1/4 + 1/2)} = \frac{10}{0.95} = 10.5263$
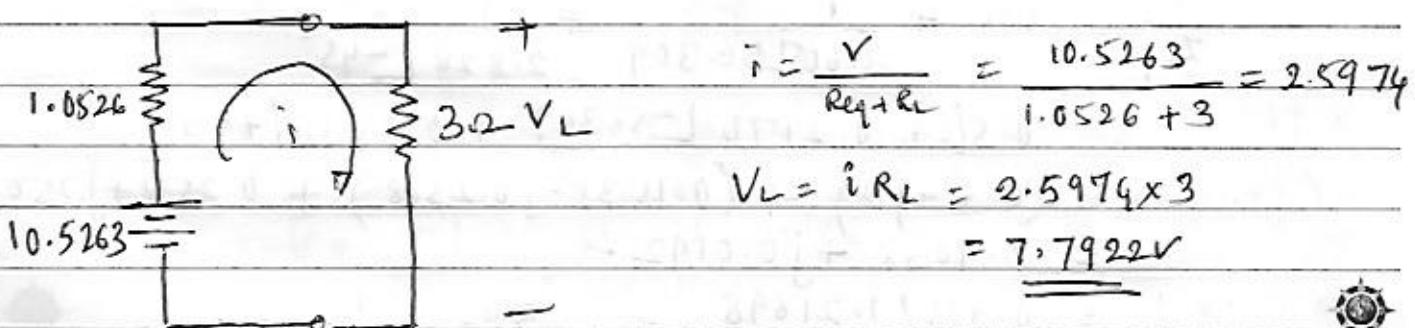
$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{4} + \frac{1}{2} = 0.95 \quad R_{eq} = \frac{1}{0.95} = 1.0526$$



DATE

(2)

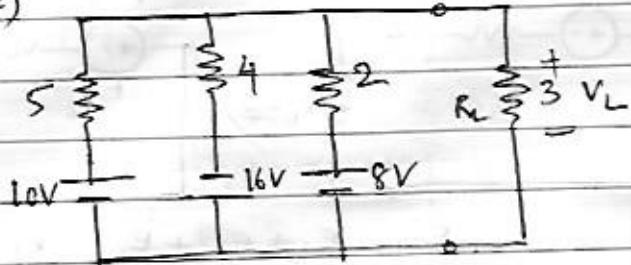


$$E_{eq} = \left(\frac{10}{5}\right) - \left(\frac{16}{4}\right) + \left(\frac{8}{2}\right)$$

$$= \frac{2}{0.95}$$

$$E_{eq} = \underline{2.1053 \text{ V}}$$

$$\frac{R_{eq}}{Z} = \frac{1}{R_{eq}} = 0.95 \quad R_{eq} = \underline{1.0526 \text{ ohm}}$$

(3)

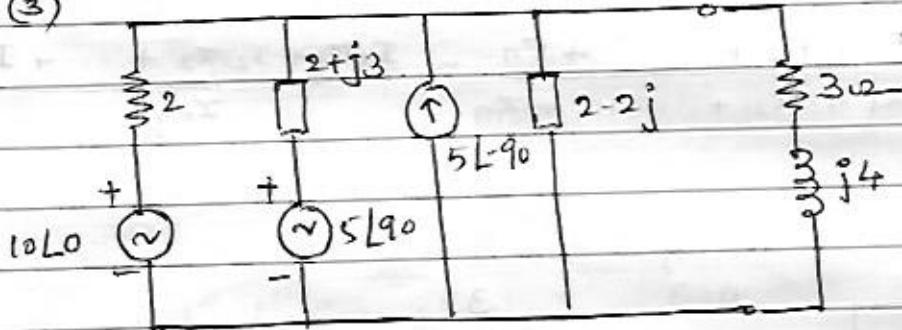

$$E_{eq} = \left(\frac{10L0}{2}\right) + \left(\frac{5L90}{2+j3}\right) + \left(\frac{5L90}{2-2j}\right) + \left(\frac{5L90}{3+j4}\right)$$

$$I_{eq} = (5+j0) + \frac{5L90}{3.6L56.309} + 5L-90$$

$$= 5+j0 + 1.1556+j0.770 + 0-j5$$

$$= (6.1556-j4.23)$$

$$= 7.4688 \angle -34.496^\circ$$

$$\frac{1}{Z_{eq}} = 0.5 + \frac{1}{3.605L56.309} + \frac{1}{2.828L-45}$$

$$= 0.5/0 + 0.2774 \angle -56.309 + 0.3536 \angle +45$$


$$= (0.5+j0) + (0.1538-j0.2308) + 0.250+j.250$$

$$= 0.9038 + j0.0192 -$$

$$\frac{1}{Z_{eq}} = 0.904 \angle 1.21698 - \quad Z_{eq} = \frac{1}{0.904 \angle 1.21698}$$

DATE
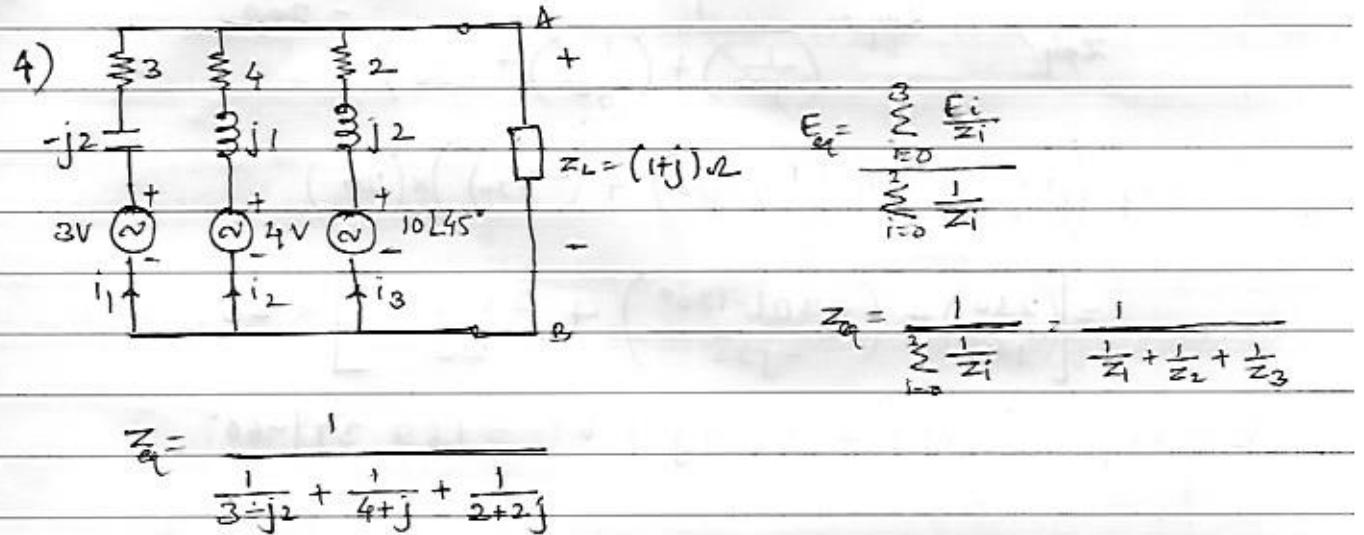
$$E_{eq} = \frac{I_{eq}}{(1/Z_{eq})} = I_{eq} \times Z_{eq} = 7.4688 [-34.496 \times \frac{1}{0.904 [1.21698 }] \\ = 8.2619 [-35.7130] \\ [E_{eq} = 6.708 - j4.8226]$$



$$Z_{eq} = \frac{1}{0.71606 + j0.1549} = 1.334 + j0.2887$$

$$E_{eq} = \left(\frac{E_1}{Z_1} + \frac{E_2}{Z_2} + \frac{E_3}{Z_3} \right) Z_{eq} \quad 10L45^\circ = 7.071 + j7.071$$

$$= \left(\frac{3}{3-j2} + \frac{4}{4+j} + \frac{10L45^\circ}{2+j2} \right) (1.334 + j0.2887)$$

$$[E_{eq} = 6.689 + j1.794] \quad 5.168 + j5.00$$

$$I_L = \frac{E_{eq}}{Z_{eq} + Z_L} = \frac{6.689 + j1.794}{(1.334 + j0.2887) + (1+j)}$$


$$I_L = (2.521 - j0.6236) \text{ Amp.}$$

$$V_{AB} = I_L \times Z_L = (2.521 - j0.6236)(1+j) = 3.1446 + j1.897 \text{ V.}$$

$$i_1 = \frac{V_{AB} - 3}{(3-j2)} = (-0.258 + j0.460) \quad i_2 = \frac{V_{AB} - 4}{(4+j)} = (0.078 - 0.49j) \text{ A} \\ = 0.258 - j0.460$$

$$i_3 = \frac{V_{AB} - 10L45^\circ}{(2+j2)} = (2.26 + 0.32j) \text{ A}$$

DATE

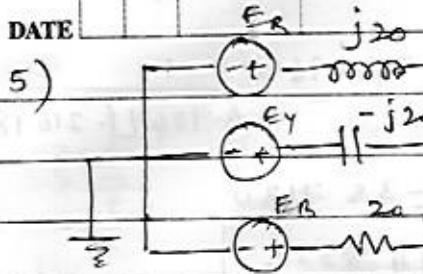

$$E_R = 230 \text{ V}$$

$$E_Y = 236 L - 120^\circ$$

$$E_B = 230 L^{120^\circ}$$

find V_s.

$$\frac{Y}{Z_{eq}} = Z_{eq} = \frac{1}{\left(\frac{1}{j20}\right) + \left(\frac{1}{-j20}\right) + \left(\frac{1}{20}\right)} = 20 \Omega$$

$$E_{eq} = \left(\left(E_R / j20 \right) + \left(E_Y / -j20 \right) + \left(E_B / 20 \right) \right) \times 20$$


$$= \left[\left(\frac{230}{j20} \right) + \left(\frac{230 L - 120^\circ}{-j20} \right) + \frac{230 L^{120^\circ}}{20} \right] \times 20$$

$$V_s = E_{eq} = (84.18 - 145.8j) \text{ V.} = 168.37 L^{-60^\circ}$$

* Reciprocity

More generally, for a network with L-loops

$$\frac{I_k}{V_j} = \frac{I_j}{V_k}$$

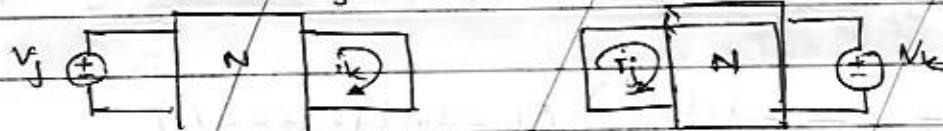

- Suppose V_j is the only source in the net. This results in the current I_k in the k^{th} loop.

- If this source is now moved to the k^{th} loop, then the current in the j^{th} loop is $I_j = I_k$.

- This is the principle of reciprocity.

- The ratio of the response transform to the excitation transform is invariant to an interchange of positions in the network of the excitation and the response.


- When this property holds, we say that the net is reciprocal otherwise the network is non-reciprocal.

Thevenin's Theorem

A 2 terminal network N_A containing linear elements and independent sources is equivalent to simpler network containing an independent voltage source in series with 2-terminal network having an impedance excluding the load.

The source voltage is the open circuit voltage of N_A . i.e. load Z_L disconnected.

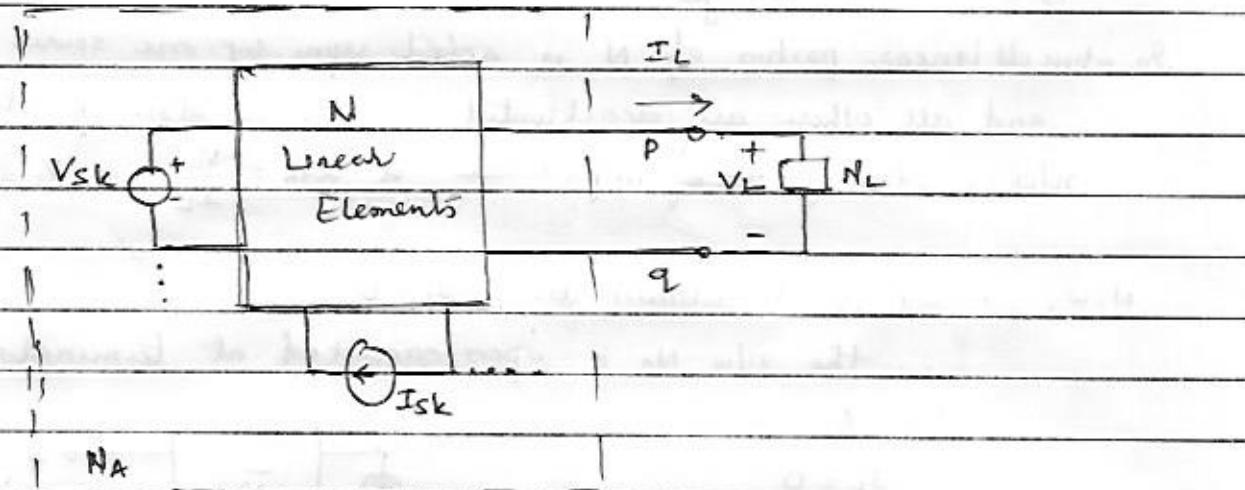The impedance (series impedance) is effective impedance of N_A measured at the terminal after deactivating all independent sources i.e. Reactivating by i_{sk} N_A . i.e. Voltage sources are S.C and current sources are O.C




The network N_A consists of Network N of linear elements - with several independent voltage sources (V_{sk}) and current sources I_{sk} acting on N . The two terminal of network N_A is connected to network N_L . (externally load N_L is connected)

Due to N_A , there is a V_L ac N_L and I_L flowing through N_L .

Now, by substitution method N_L can be replaced by current source I_L (I_L is current flowing through N_L)

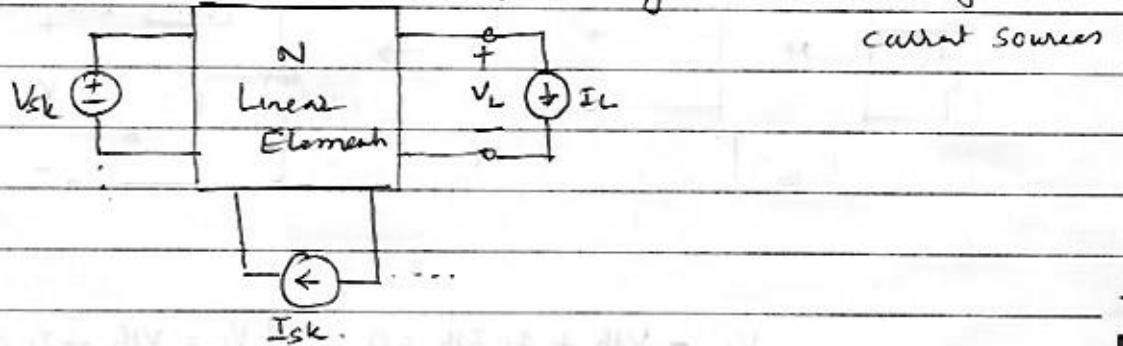- Elements can be replaced by either a voltage source or current sources



Using superposition principle to computing V_L by
superposing the effects of all independent sources & current source


V_L is $\therefore V_L = A_0 I_L + A_1 V_{S1} + A_2 V_{S2} + \dots + A_3 I_{S1} + A_4 I_{S2}$ — (1)

$$V_L = A_0 I_L + B_0 \quad \text{— (2)}$$

Now the effective impedance of N_A can be computed by deactivating all the independent sources in the n/w except I_L source.
ie $B_0 = 0$.

$$\therefore V_L = A_0 I_L$$
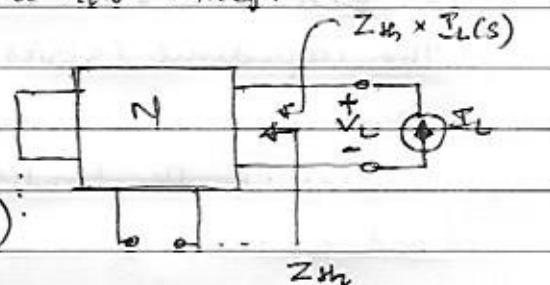
$$\left[A_0 = \frac{V_L}{I_L} = Z_{th} \right] \text{(Effective impedance)}$$



Now, source voltage

In above ckt, linear portion of N is acted upon by one source I_L and all others are deactivated. $\therefore I_L$ is driving the one port n/w. \therefore driving point impedance is $Z_{th} = \frac{V_L}{I_L}$ ie $V_L = I_L \times Z_{th}$.

Now, is eq² (1) to obtain B_0 , $I_L = 0$.


\therefore the n/w N_A is open circuited at terminals pq

$$\therefore V_L = A_0 I_L + B_0.$$


$$I_L = 0$$

$$V_L = B_0 = V_{oc} = V_{th}.$$

↑ Open ckt
Voltage.

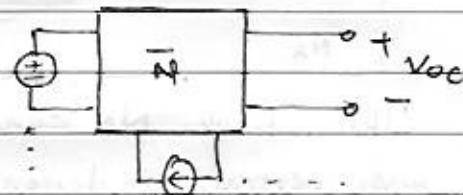

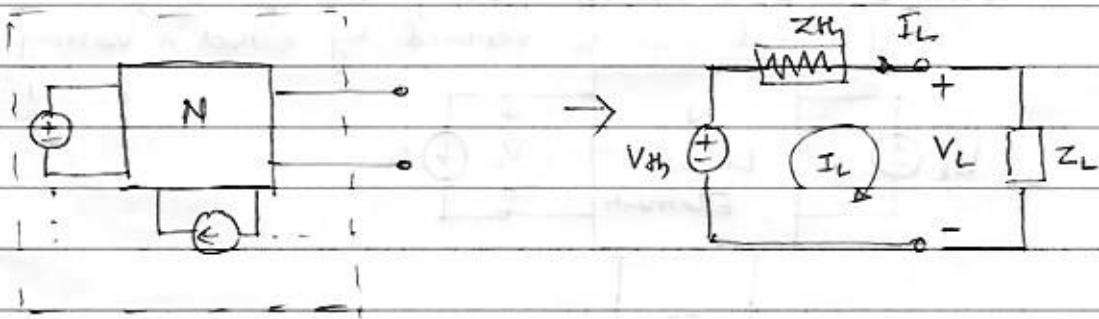Superimposing the two cases discussed above gives the Thevenin's equivalent of network N_A having open ckt Voltage V_{th} in series effective impedance Z_{th} .



$$V_L = V_{th} + I_L Z_{th} = 0 \quad \therefore V_L = V_{th} - I_L Z_{th}$$

DATE

Conditions of Network NA and NL

- Network NA consists of linear elements (n) which may be either passive elements (R, L, C) which are reciprocal and dependent sources which are non-reciprocal.
- Network NA consists of independent sources (either current/voltage sources and initial cond^rs of passive components).
- No coupling between NA and NL
ie No magnetic (or) Controlled sources in NA depending on current/voltage in NL & vice versa.

Similarly, Network NL

- NL can be linear or non linear, μ or time varying element.
- Independent / dependent sources.
- Initial cond^rs for passive components.
- No coupling w^rs NL. (magnetically controlled sources)

Steps to find Effective impedance (Z_{th})


- i) Set all the initial conditions to zero ie $V_C = 0, I_L = 0$ and turn off all independent sources by s.c voltage sources and o.c current sources.
- ii) Controlled ckt in Network are kept intact
- iii) Determine the driving point impedance of (or) admittance.

Steps to find Open ckt voltage $V_{oc} = V_{th}$

- i) Open terminal of network NA with network NL removed.
(ie load removed)
- ii) Find open ckt voltage $V_{oc} = V_{th}$ due to all the sources - acting in the network.
- iii) Replace NA with $V_{oc} = V_{th}$ and series effective impedance Z_{th} .
- iv) Connect the NL (load impedance) and calculate the load current I_L .

DATE

Norton's theorem

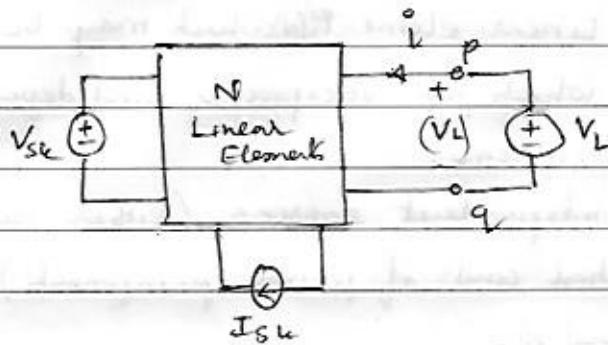

$$i = C_0 V_L + C_1 V_{S1} + C_2 V_{S2} + C_3 I_{S1} + C_3 I_{S2} \quad (1)$$


$$i = C_0 V_L + D_0 \quad (2)$$

If $D_0 = 0$ ie All independent sources made inactive

$$i = C_0 V_L$$

Norton's
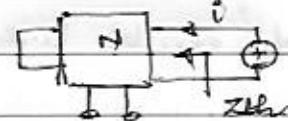
$$\left[C_0 = \frac{i}{V_L} \right] = G_{eq} \text{ (Admittance)}$$





Now, By removing V_L and sc the terminal p,q, the current i can be computed

(ii) If $V_L = 0$, sc the p,q
eq 2 (2) is



$$i = 0 + D_0$$

$$\therefore [D_0 = i] = -I_{SC} = IN.$$

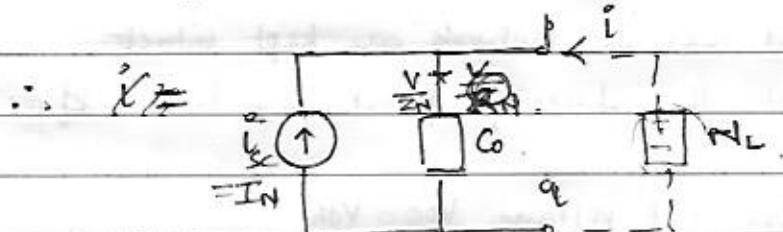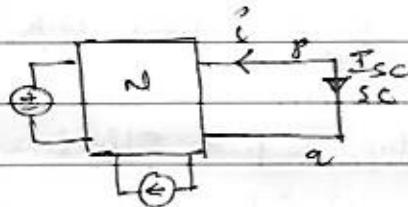

DATE

(1)

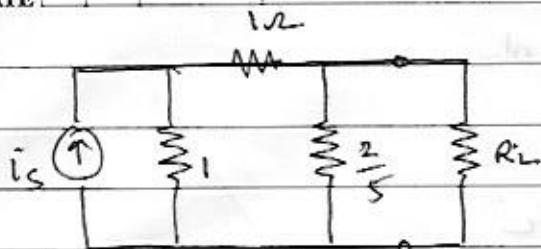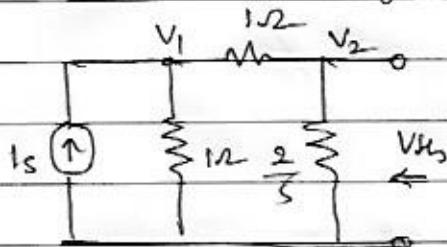find V_{th} and R_{th} .

Using Node analysis.

$$\text{At } N_1, \frac{V_1}{1} + \frac{(V_1 - V_2)}{1} - I_s = 0$$

$$2V_1 - V_2 = I_s \quad \text{---(1)}$$

$$\text{At } N_2, \frac{V_2}{\frac{2}{5}} + \frac{(V_2 - V_1)}{1} = 0$$

$$\frac{5}{2}V_2 - V_1 = 0 \quad \text{---(2)}$$

from (1)

$$2V_1 = I_s + V_2$$

$$V_1 = \frac{(I_s + V_2)}{2} \quad \text{---(3)}$$

(3) in (2)


$$\frac{5}{2}V_2 - \frac{(I_s + V_2)}{2} = 0$$

$$\frac{5}{2}V_2 - \frac{I_s}{2} - \frac{V_2}{2} = 0$$


$$\frac{6}{2}V_2 = \frac{I_s}{2}$$

$$V_2 = \frac{I_s}{2} \times \frac{2}{6} = \frac{I_s}{6}$$



$$\boxed{V_2 = \frac{I_s}{6}} = V_o = V_{th}$$

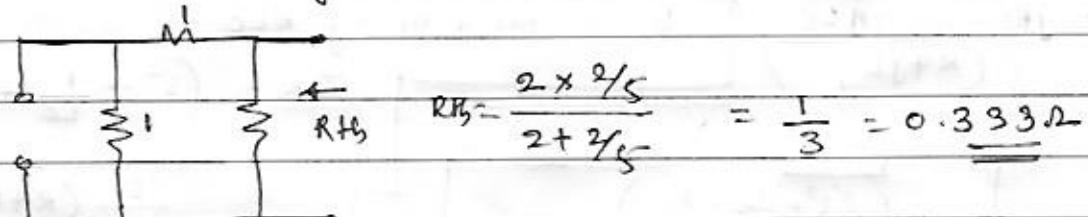 $\chi^{th}(R_{th})$ found by s.c voltage & o.c current source

Thévenin equivalent is

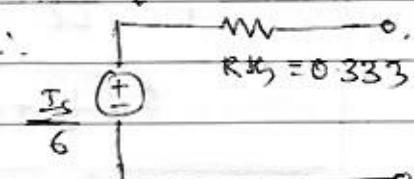

DATE

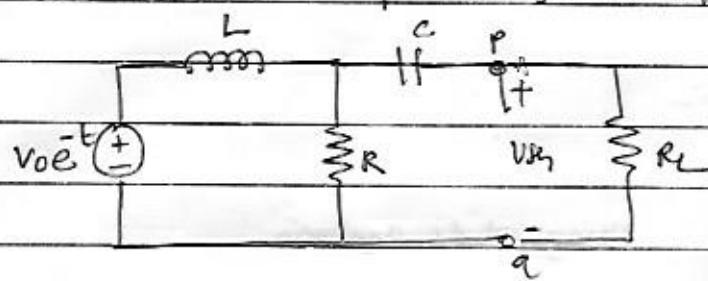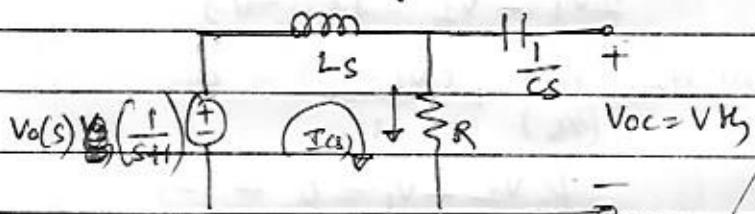2) find thevenins eq² ckt for the n/w.Compute V_{th} by O.C P.Q.

$$\alpha(e^{-t}) = \frac{1}{s+1} \quad (\text{or}) \quad \text{time domain}$$


$$I(s) = \frac{V_o(s)}{(s+1)(R+L_s)}$$

$$V_{oc} = I(s) \times R$$


$$V_{oc} = \frac{V_o(s) R}{(R+L_s)(s+1)}$$

R.H.Y., s.c. Voltage source, initial condns as zero.

L relaxed acts as O.C

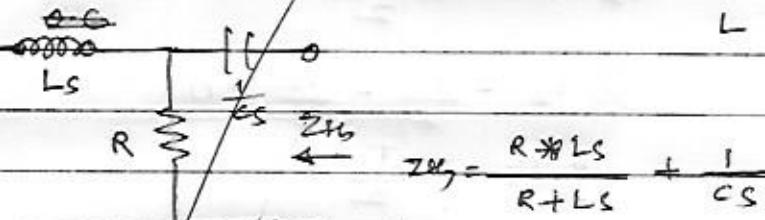
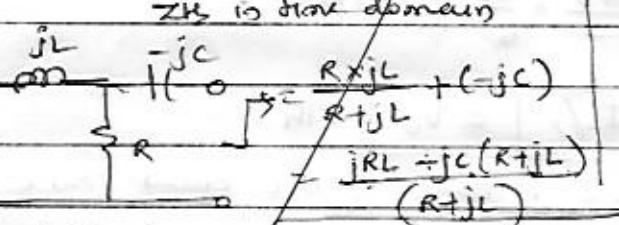
$$= (R+L_s) \frac{RL_s}{CS(R+L_s)} + \frac{1}{CS}$$




$$= \frac{RL_s^2 + R + L_s}{CS(R+L_s)}$$

$$= jRL - jRC + jLC$$

Divide N.R & D.R by RLC
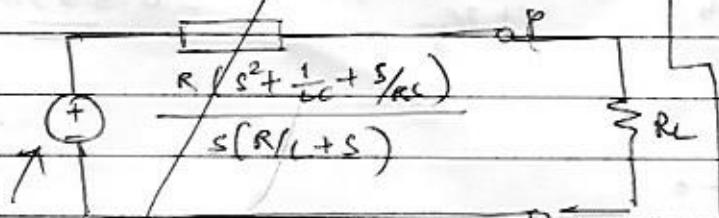
$$Z_{th} = \left(s^2 + \frac{1}{LC} + \frac{s}{RC} \right)$$



$$V_{th} = \frac{V_o(s) R}{(s+1)(R+L_s)}$$

$$= \frac{s}{RL} (R+L_s)$$



$$= \left(s^2 + \frac{1}{LC} + \frac{s}{RC} \right) \times \frac{R}{s \left(\frac{1}{L} + \frac{s}{R} \right)}$$

$$Z_{th} = \frac{R \left(s^2 + \frac{1}{LC} + \frac{s}{RC} \right)}{s(R/L + s)}$$

$$e^{-t} = \frac{V_0}{s+a}$$

32

DATE

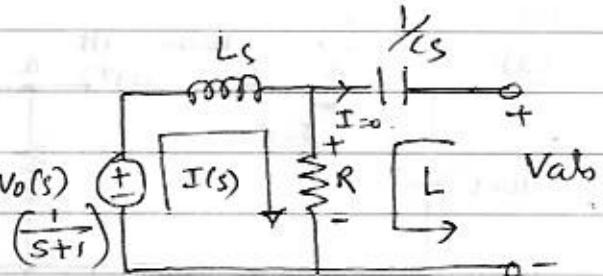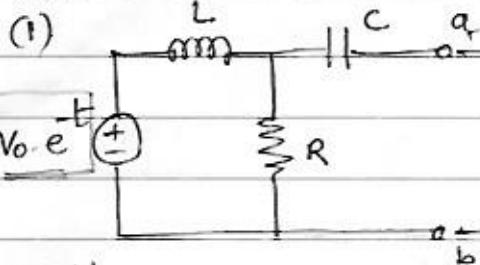


$$\frac{V_0}{s+a}$$

$$\left(\frac{1}{s+1}\right) V_0 \text{ KVL to loop } L$$

$$I(s) = \frac{V_0(s)}{(s+1)(R+Ls)} \quad \text{---(1)}$$

$$-V_{ab} + \frac{V_0(s)}{(s+1)(R+Ls)} \cdot R$$
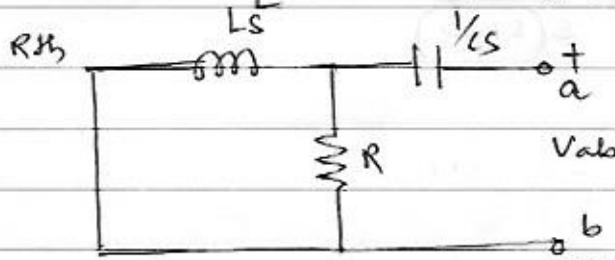
$$V_{ab} = \left[\frac{V_0(s)}{(s+1)(R+Ls)} \cdot R \right] \quad \text{---(2)}$$



$$Z_{eq} = \frac{R \times Ls}{R+Ls} + \frac{1}{Cs}$$

$$= \frac{(RLs)Cs + 1(R+Ls)}{Cs(R+Ls)}$$


$$Z_{eq} = \frac{RLCs^2 + R+Ls}{Cs(R+Ls)}$$

\Rightarrow N.R, D.R by RLC

$$Z_{eq} = \left(s^2 + \frac{1}{Lc} + \frac{s}{RC} \right)$$



$$- \frac{s}{RL}(R+Ls)$$
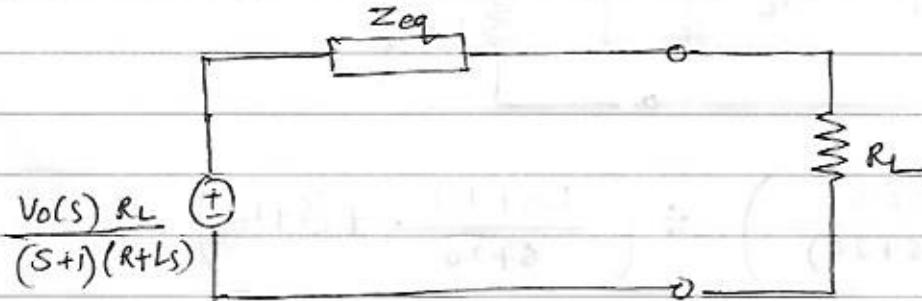
$$Z_{eq} = \frac{(s^2 + 1/Lc + s/RC)}{s(1/L + s/R)} \times \frac{R}{R} = \frac{R(s^2 + 1/Lc + s/RC)}{s(R/L + s)}$$



DATE


K

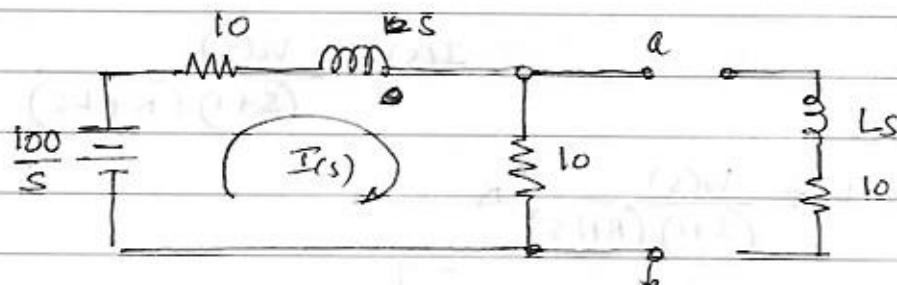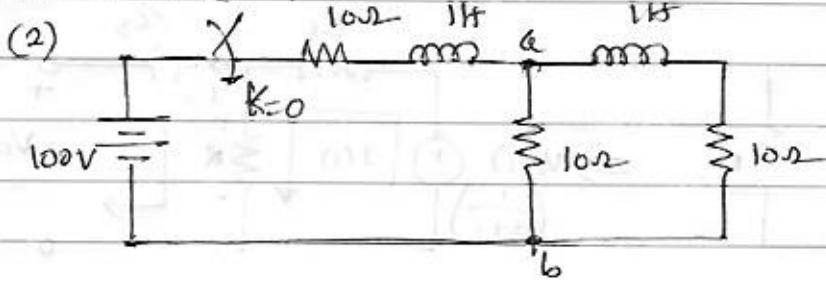

$$I(s) = \frac{100}{(20+s)s} = \frac{100}{s(s+20)}$$

$$V_R = I(s) \times 10$$

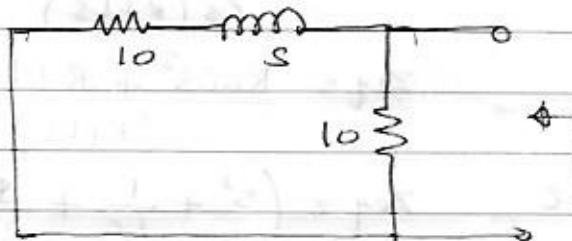
$$\boxed{V_R = \frac{1000}{s(s+20)}} \quad \text{--- (1)}$$



$$Z_R = \frac{(s+10) \times 10}{s+10+10}$$

$$Z_R = \left(\frac{10s+100}{s+20} \right)$$

Thevenins equivalent

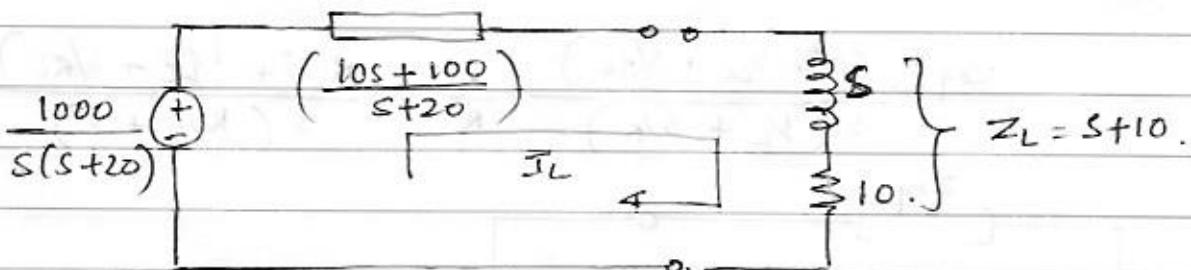

$$I_L = \left(\frac{1000}{s(s+20)} \right) \div \left(\frac{10s+100}{s+20} + (s+10) \right)$$


$$= \frac{1000}{s(s+20)} \times \frac{(s+20)}{(s^2+20s+10s+200)}$$

$$\frac{s^2+20s}{s^2+20s} \times \frac{1000}{s^2+30s+200}$$


$$\boxed{I_L = \frac{1000(s+20)}{2s^2+60s+300}}$$

DATE

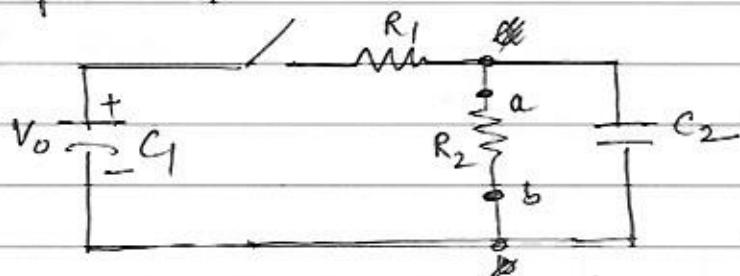- (4) Find current in the resistor R_2 . Initial cond τ s are i.e. voltage across capacitor $C_1 = V_0$ and $C_2 = 0V$




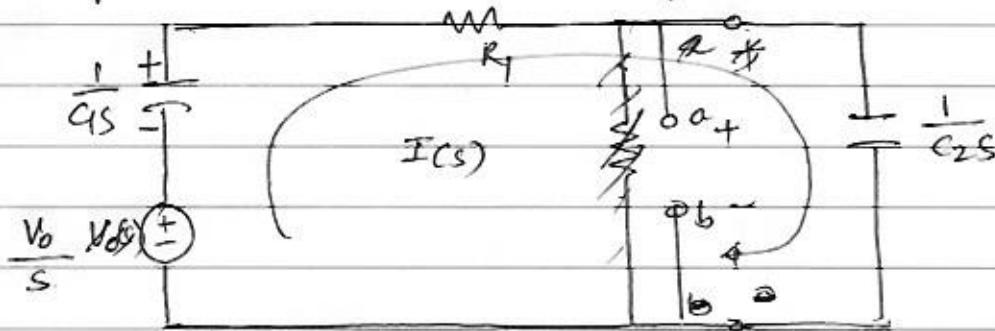
Open ckt τ g (a, b) and transformed ckt τ s



$$I(s) = \frac{(V_0/s)}{R_1 + \frac{1}{C_1 s} + \frac{1}{C_2 s}}$$


$$V_{ab} = I(s) \times \frac{1}{C_2 s} = \frac{(V_0/s)}{R_1 + \frac{1}{C_1 s} + \frac{1}{C_2 s}} \times \frac{1}{C_2 s}$$
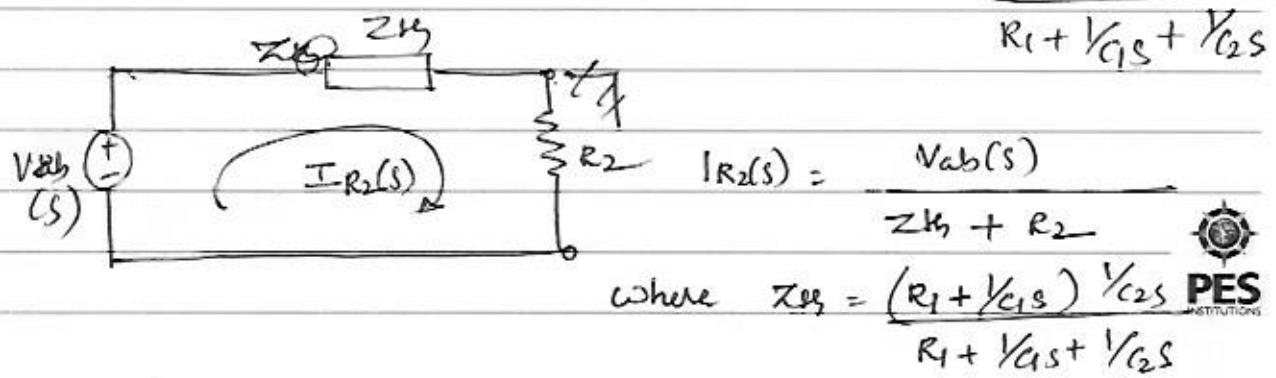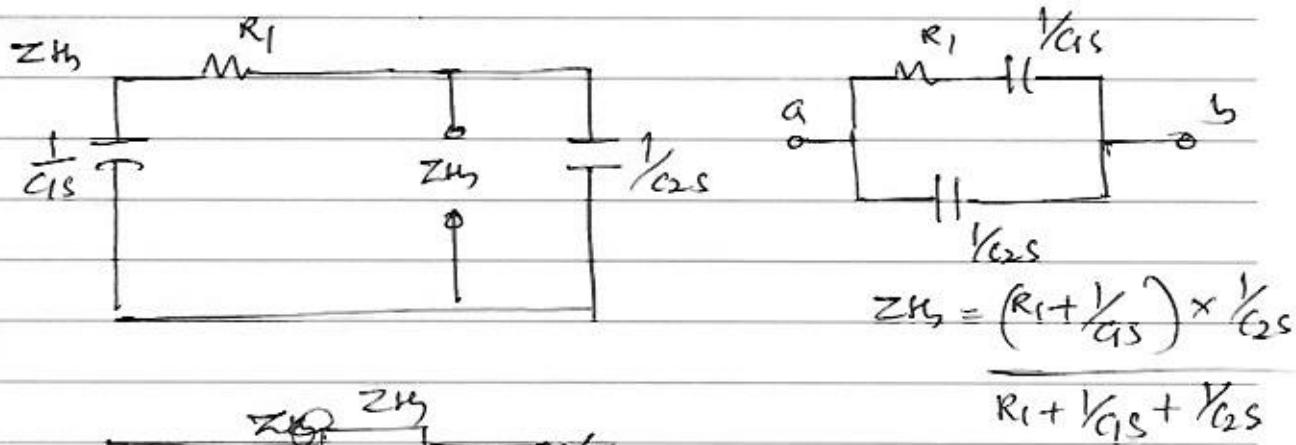
$$V_{ab} = \frac{V_0 / C_2 s^2}{R_1 + \frac{1}{C_1 s} + \frac{1}{C_2 s}}$$



where $Z_H2 = \frac{(R_1 + \frac{1}{C_1 s}) \frac{1}{C_2 s}}{R_1 + \frac{1}{C_1 s} + \frac{1}{C_2 s}}$

DATE

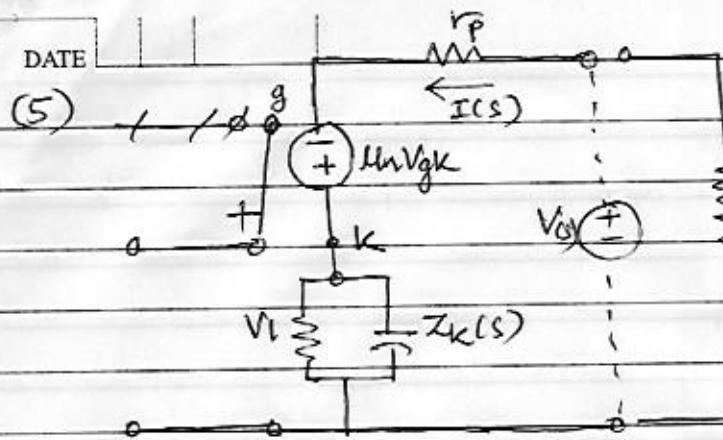


The networks contain a controlled source which depends on the voltage $V_{gk}(s)$

$$V_{gk}(s) \neq 0$$

$$V_{gk}(s) = V_1(s) - V_k(s)$$
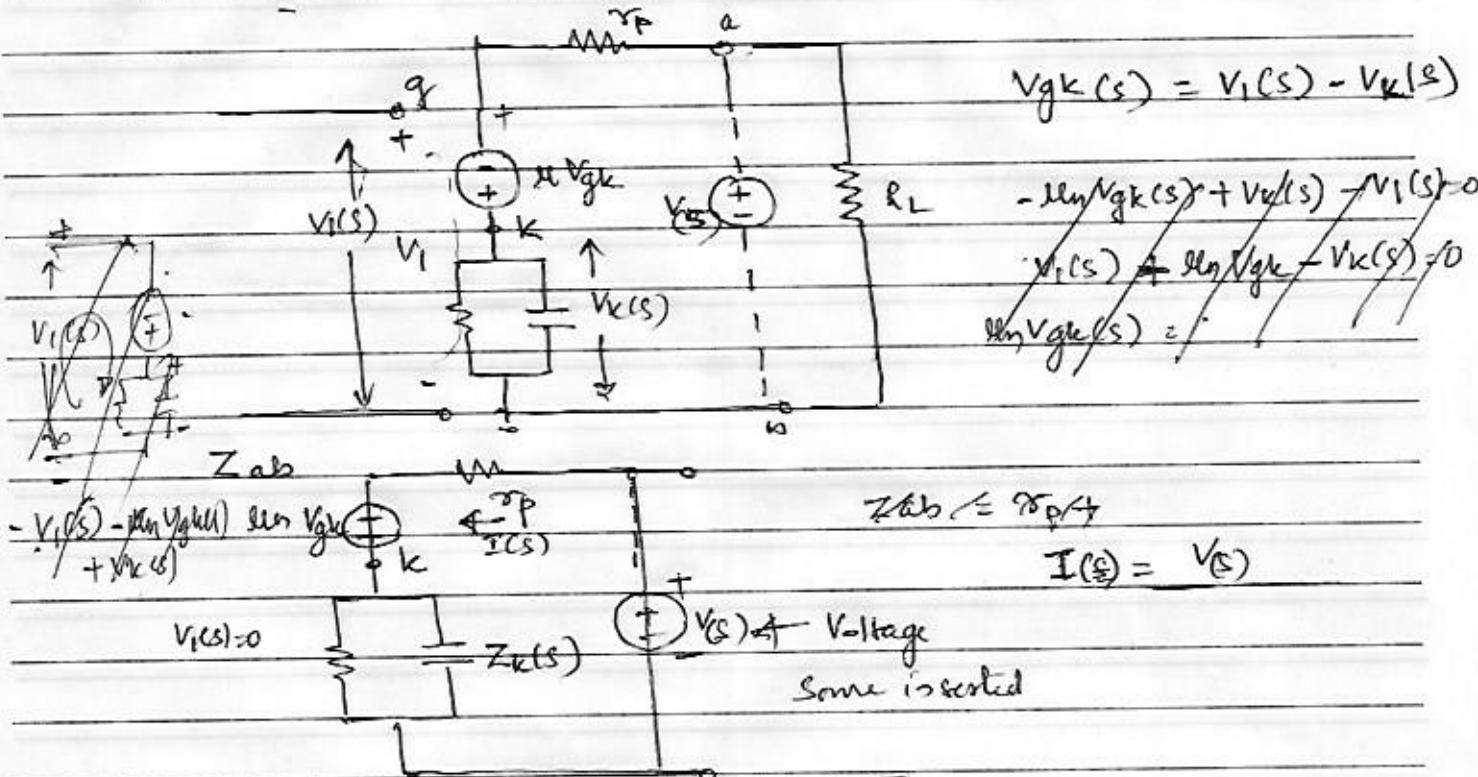
$$\begin{aligned} -\mu V_{gk}(s) + V_k(s) - V_1(s) &= 0 \\ V_1(s) + \mu V_{gk}(s) - V_k(s) &= 0 \\ \mu V_{gk}(s) &= V_k(s) \end{aligned}$$



$$Z_{ab} = r_p +$$

$$I(s) = V(s)$$

Voltage
Some inserted

$$y(s) = I(s) r_p + I(s) \mu V_{gk}(s) + I(s) Z_k(s)$$


$$V(s) = I(s) r_p - \mu (V_1(s) - V_k(s)) + V_k(s)$$

$$= I(s) r_p - \mu (0 - I(s) Z_k(s)) + I(s) Z_k(s)$$

$$= I(s) r_p + \frac{\mu}{n} I(s) Z_k(s) + I(s) Z_k(s)$$

$$Z_{ab}(s) = Z_{ab}(s) = \frac{V(s)}{I(s)} = r_p + \frac{\mu}{n} Z_k(s) + Z_k(s)$$
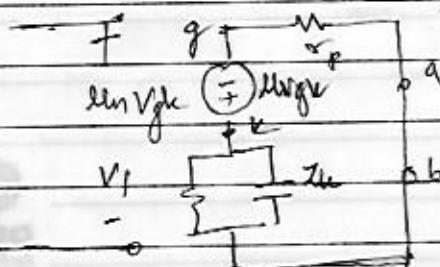
$$Z_{ab}(s) = Z_{ab}(s) = r_p + Z_k(s)(1 + \mu)$$



$$I(s) \cdot Z_k + I(s) \mu V_{gk} + I(s) r_p = 0$$


$$I(s) = V_1(s)$$

$$I(s) = \frac{\mu V_1(s)}{r_p + (1 + \mu) Z_k(s)}$$

$$Z_{ab} = r_p + (1 + \mu) Z_k(s)$$

DATE

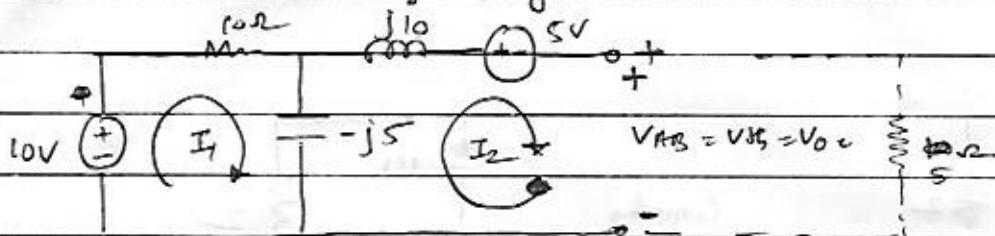- (1) Find current in 5Ω resistor connected between terminals A and B in ckt shown in fig using Thevenin's thm.



KVL for current I_1

$$-10 + 10I_1 - j5(I_1 - I_2) = 0$$

$$(10 - j5)I_1 + j5I_2 = 10 \quad \text{---(1)} \quad I_1 = \frac{10 - j5I_2}{(10 - j5)}$$

$$-j5(I_2 - I_1) + j10I_2 + 5V + V_{AB} = 0 \quad V_{AB} = I_2 \times 5\Omega$$

$$+j5I_1 + j5I_2 = -V_{AB} - 5V \quad \text{---(2)}$$

$$+j5I_1 + j5I_2 + I_2 \times 5 = -5V$$

$$V_{AB} = -5V - j5I_1 - j5I_2$$


$$= -5 - j5 \left(\frac{10 - j5I_2}{(10 - j5)} \right) / j5/I_2 = 0$$

$$+j5I_1 + (5 + j5)I_2 = -5V \quad \text{---(2)}$$


$$10I_1 + (5 + 10j)I_2 = 5$$

DATE

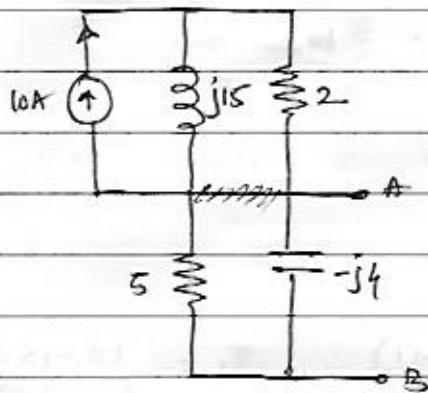(2) find thevenins eq. ck for the net shunt in fig. What imp must be connected between A & B for max power transfer. What is max power



Converting
current into
volt

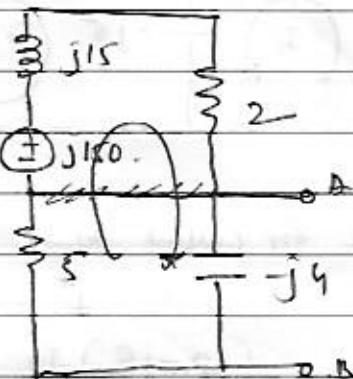

By KVL

$$5I_1 - j150 + j15I_1 + 2I_1 - j4I_1 = 0$$

$$I_1(7 + j11) = -j150.$$

$$I_1 = +j150 / (7 + j11)$$


$$I_1 = 9.7 + 6.17j$$

$$I_1 = 11.5 \angle 32.47^\circ$$

$$V_{AB} = -j4 \times (9.7 + 6.17j)$$

$$= 24.68 - 38.8j$$

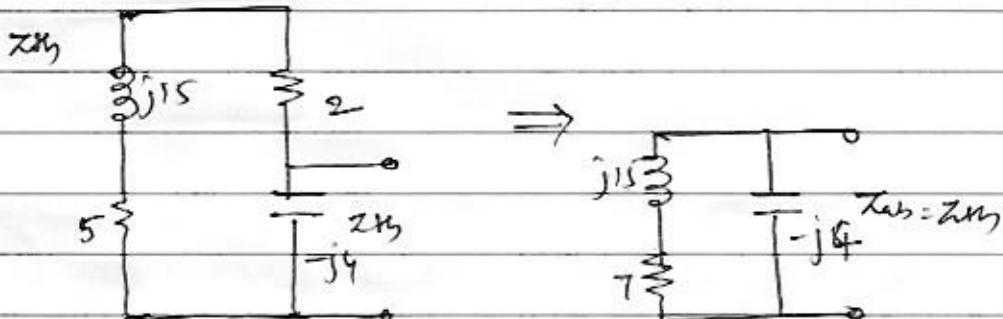
$$\boxed{V_B = 45.98 \angle -57.54^\circ}$$



$$I_L = \frac{V_B}{Z_{AB} + R_L} = 18.731 - 29.45j$$

$$Z_{AB} = (7 + 11j) \times (-j4)$$

$$= 0.6588 - 5.035j$$

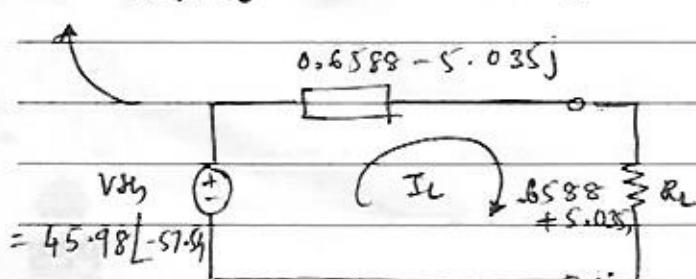


for max power

$$R_L = Z_{AB}^*$$

$$P = |I_L|^2 \times R_L = |18.731 - 29.45j|^2 \times R_L$$

DATE

(3) Using Thvenins thm find current in 2Ω resistor

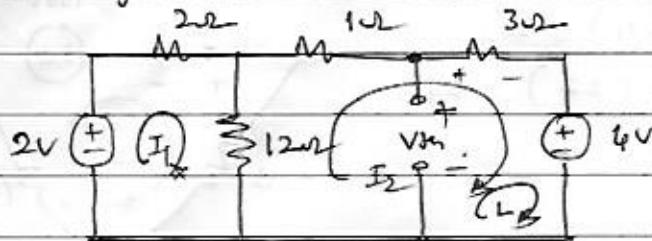KVL @ I_1

$$-2 + 2I_1 + 12(I_1 - I_2) = 0.$$

$$[14I_1 - 12I_2 = 2] \quad \text{--- (1)}$$

$$@ I_2 \quad 4I_2 + 4 + 12(I_2 - I_1) = 0.$$

$$\cancel{4} \quad [-12I_1 + 16I_2 = -4] \quad \text{--- (2)}$$

$$I_1 = -0.2 \text{ A} \quad I_2 = -0.4 \text{ A}$$


∴ ~~KVL~~ KVL at loop L.

$$-V_{Th} + 3(-0.4) + 4 = 0$$

$$V_{Th} = 3 \times 0.4$$

$$V_{Th} = 4 - 1.2 = 2.8 \text{ V}$$


$$V_{Th} = 2.8 \text{ V}$$

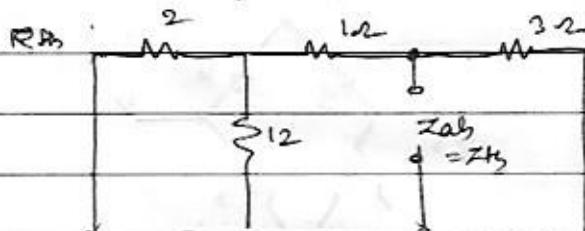

$$\frac{12 \times 2}{17} + 1 = 2.714 \text{ A}$$


$$Z_{Th} = \frac{2.714 \times 3}{2.714 + 3} = \underline{\underline{1.425 \Omega}}$$

$$R_{Th} = 1.425 \Omega$$

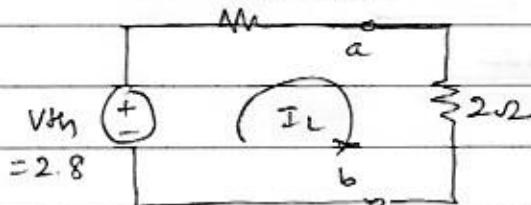

$$I_L = \frac{2.8}{2 + 1.425} = 0.8175 \text{ A}$$

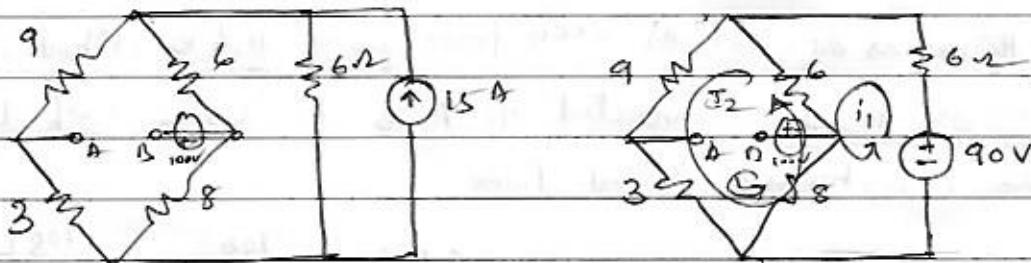(4) Obtain Thvenins eqn w.r.t to terminals A,B.



$$\text{KVL } 1, 28 \text{ A}$$

$$@ 1 \quad -90 + 6i_1 + 6(i_1 - i_2) + 8(i_1 - i_2)$$

$$20i_1 - 14i_2 = 90 \quad \text{--- (1)}$$

$$@ 2 \quad 9i_2 + 3i_2 + 8(i_2 - i_1) + 6(i_2 - i_1) = 0$$

$$-14i_1 + 26i_2 = 0 \quad \text{--- (2)}$$

$$i_1 = 7.222$$

$$i_2 = 3.888$$

DATE


Applying KVL to loop

$$-V_{AB} - 100 + 3i_2 - 8(i_2 - i_1) = 0$$






$$-100 + 3 \times 3.888 + 8(3.888 - 7.22) = V_{AB}$$

$$-100 + 11.664 - 26.656 = V_{AB}$$

$$V_{AB} = -115V$$

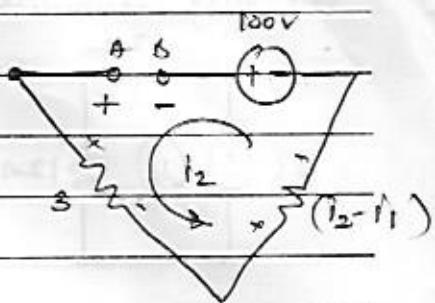

Req (Thevenin Resistance)

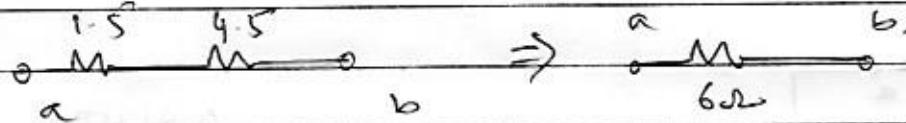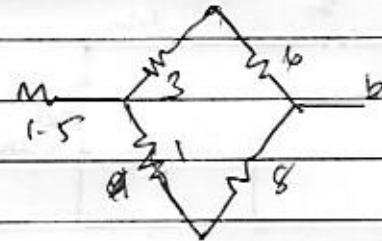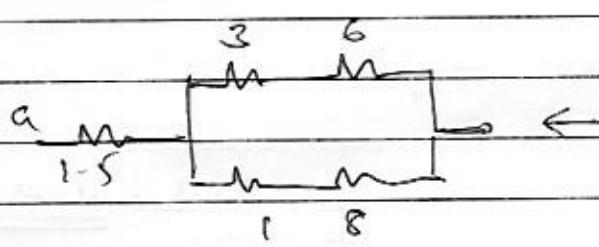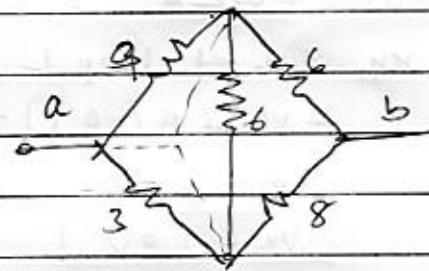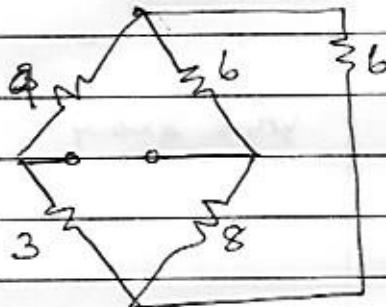

Req 6Ω


Req

V_{AB}

-115V

← Thevenin equivalent ckt

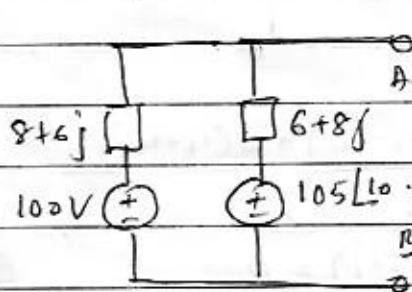- 5) Obtain Thevenin eq² ckt as seen from point A & B. What is the load impedance to be connected b/w A & B for I_{max}. If load impedance is pure resistance what P_{max}



$$E_{eq} = \frac{\sum E_i / Z_i}{\sum Z_i} = \frac{100}{3+6j} + \frac{105L10}{6+8j}$$

$$\frac{1}{3+6j} + \frac{1}{6+8j}$$

$$E_{eq} = 102.96 + 8.86j$$

$$Z_{eq} = 3.57 + 3.57j$$

DATE

$$Z_h = Z_{eq} = 3.57 + j3.57$$

for max power transfer

$$R_L = \frac{Z_h}{Z_h + Z_h}$$

$$E_{eq} (+) 102.96 + j8.86$$

 $= V_{th}$

$$R_L = 3.57 - j3.57$$

$$I_L = \frac{102.96 + j8.86}{Z_h + R_L}$$


$$= \frac{102.96 + j8.86}{2(3.57)}$$

$$= 14.42 + j1.24$$

$$(i) P_{max} = \frac{|V|^2}{R} = \frac{102.96^2}{3.57} \times (3.57)^2 = 747.5 \text{ W. ?}$$

(ii) Load is pure resistive


$$= \sqrt{(3.57)^2 + (3.57)^2}$$

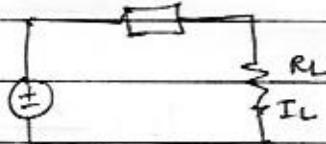

$$R_L = |Z_h| = 5.05$$

=

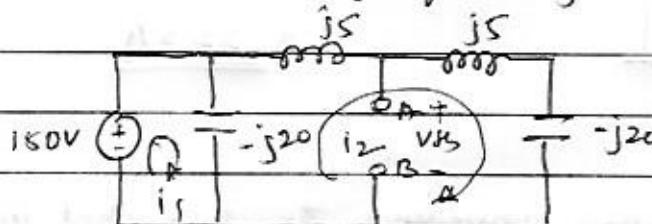6) find shuntless eq w.r.t terminals A & B of ckt. Find current in the load imp of $(10 - j7.5) \Omega$ connected b/w AB



$$-150 - j20 \times I_1 = 0$$

$$\frac{j20}{10 - j7.5} I_1 = 150 \quad I_1 =$$

$$-j10 \times i_2$$

$$-150 - j20(i_1 - i_2) = 0$$

$$-j20(i_2 - i_1) - j10i_2 = 0$$

$$-20j i_1 + 20j i_2 = 150 \quad \text{---(1)}$$

$$-j30i_2 + j20i_1 = 0$$

$$-j30i_2 = -j20i_1$$

$$-20j i_1 + 20j(0.6667i_1) = 150$$

$$i_2 = 0.6667i_1$$

$$i_1 = \frac{150}{-20j} = 22.5i$$


$$i_2 = 15.0075i$$

$$V_{th} = i_2 \times (j5 - j20)$$


$$= 15.0075i \times -j15$$

$$[V_{th} = 225.11 \text{ Volts}]$$

DATE

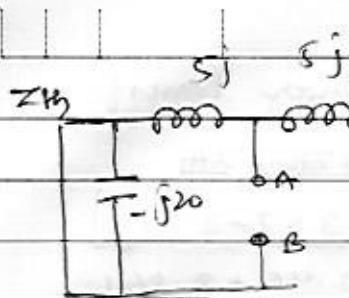


$$Z_{th} = -j20 + j5 =$$

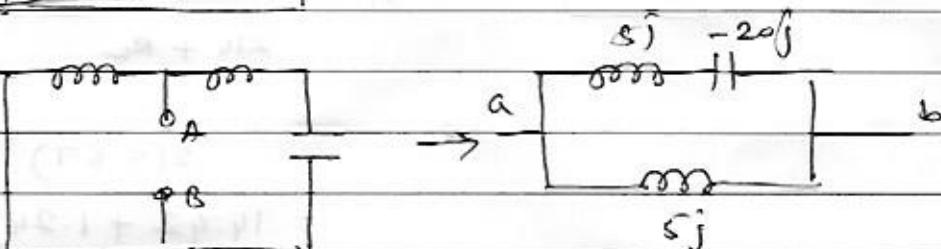

$$Z_{th} = \frac{-15j \times 5j}{-15j + 5j} = 7.5j$$

$$Z_R = 7.5j$$

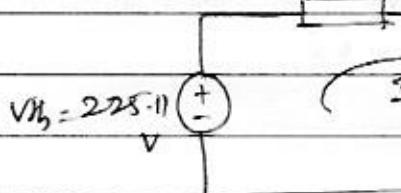


$$I_L = \frac{V_B}{Z_R + Z_L}$$

$$= \frac{225.11}{10 - 7.5j + 7.5j}$$

$$I_L = 22.75$$

$$= 22.5A$$

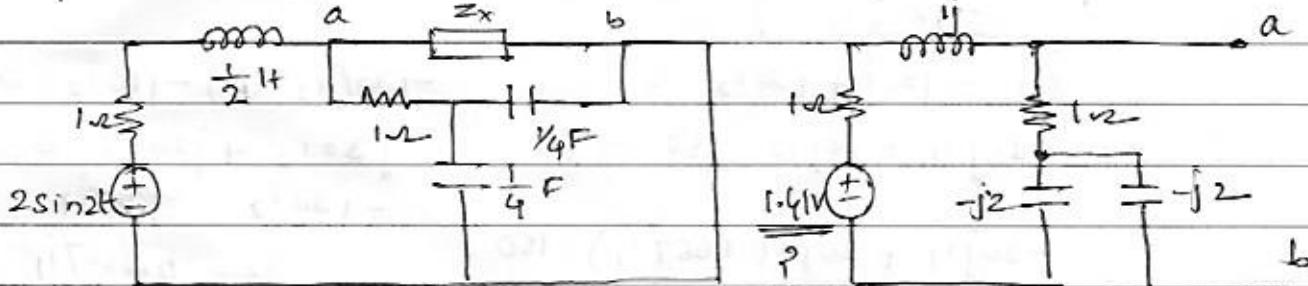Q7) for the n/w shown in fig determine impedance Z_x such that max power is transferred from source to load of imp Z_x . find P_{max}




$$\omega = 2 \quad \therefore x_L = j\omega L = j2 \times \frac{1}{2} = j1.$$

$$x_C = \frac{1}{j\omega C} = \frac{1}{j2 \times \frac{1}{4}} = -2j.$$

$$\omega = 2\pi f$$

$$\frac{2}{\pi} = f$$

$$\frac{-j2 \times j2}{-(j2) + (-j2)}$$

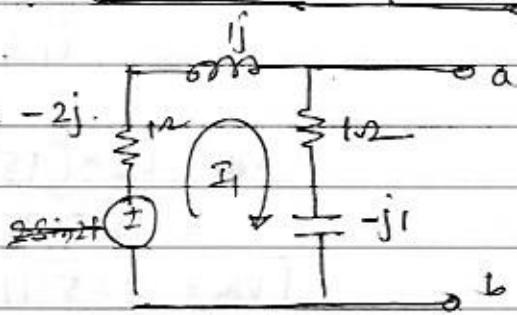


$$KVL: 1.41 - 2i_1 = 0$$

$$2i_1 = 1.41 \quad \therefore i_1 = 0.705$$




$$V_{AB} = i_1 \times (1-j) = 0.705 - 0.705j$$

DATE

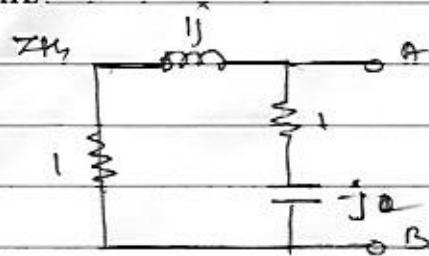
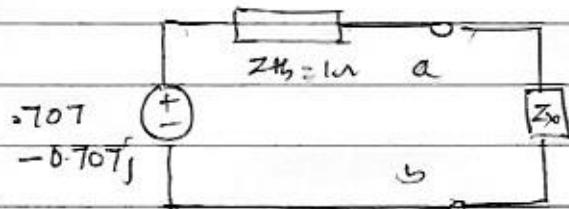
$$Z_{AB} = \frac{(1+j)(1-j)}{1+j+1-j} = \underline{\underline{1\Omega}}$$




$$P_{max} \quad Z_{AB} = Z_X = 1\Omega$$




$$\therefore I_L = \frac{V_{AB}}{1+1} = 0.35(1-j)A \\ = 0.5[-45^\circ]$$

$$P_{max} = |I_L|^2 Z_X = \underline{\underline{0.28W}}$$

DATE _____

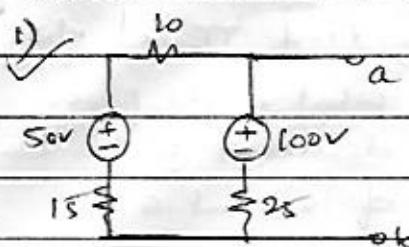

Find Thvenin equivalent at terminals a & b.
How much power is delivered to a resistor
connected to a and b if R_{ab} equals
a) 50Ω b) 12.5Ω

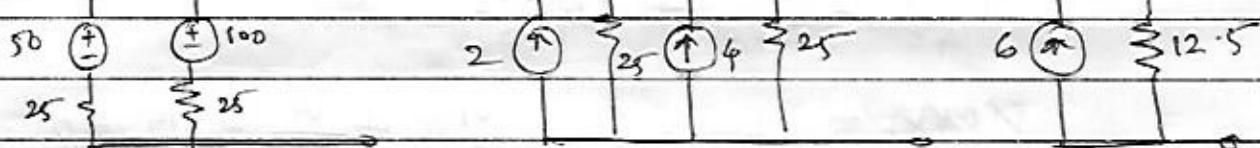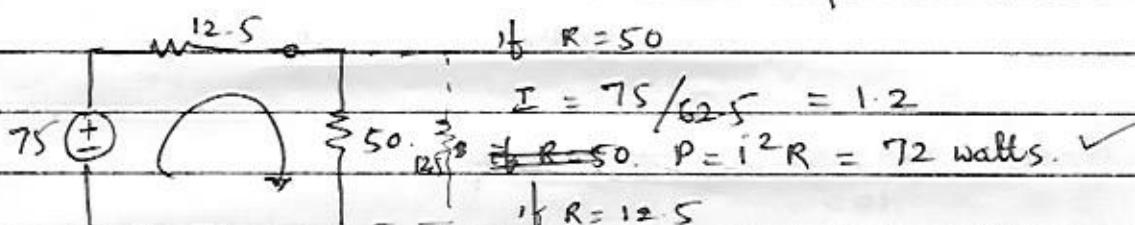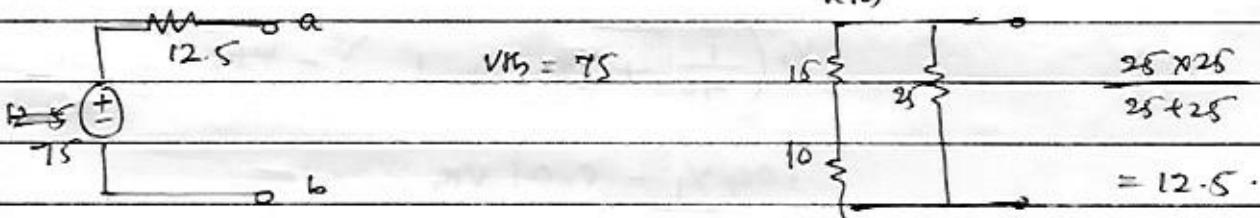
 V_{Th}  R_{Th} 

$$I = 75/25 = 3 \text{ A}$$


$$P = I^2 R = 3^2 \times 12.5 = 112.5 \text{ Watts. } \checkmark$$

2


(2)

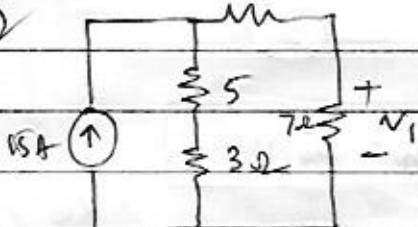

Find Thvenins equivalent of the n/w
connected to 7Ω resistors. Find the
corresponding Nortons equivalent
compute V_1 using both ckt.

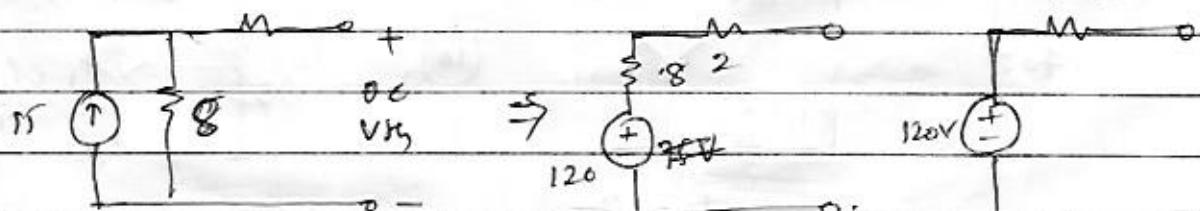
 10Ω 

Thvenins equivalent

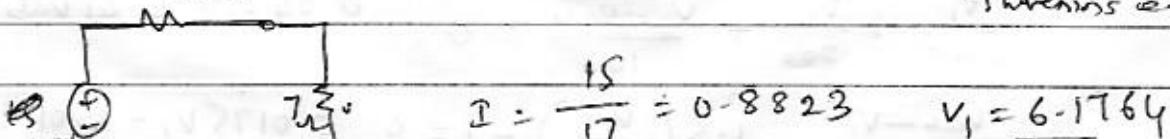


$$I = \frac{15}{17} = 0.8823$$

$$V_1 = 6.1764$$

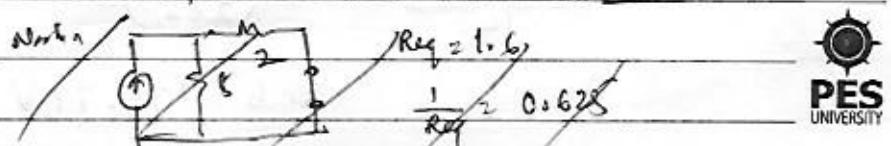 $N_{eq} = 1.6$ $\frac{1}{R_{eq}} = 0.625$

DATE

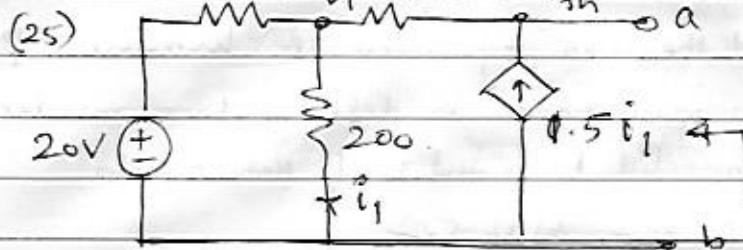40Ω V_1 100Ω V_{th} find TR of nwwhat is the power delivered to the load of 10Ω at a, b.

KCL at Node 1

$$\frac{V_1 - 20}{40} + \frac{V_1}{200} + \frac{V_1 - V_{th}}{100} = 0.$$

$$0.04V_1 - \frac{V_1}{40} - \frac{20}{40} + \frac{V_1}{200} + \frac{V_1}{100} - \frac{V_{th}}{100} = 0.$$

$$V_1 \left(\frac{1}{40} + \frac{1}{200} + \frac{1}{100} \right) - \frac{V_{th}}{100} = \frac{20}{40},$$

$$0.04V_1 - 0.01V_{th} = 0.5.$$

$$\boxed{4V_1 - V_{th} = 50.} \quad \text{--- (1)}$$


Node 2 $\frac{V_{th} - V_1}{100} - 1.5 \frac{V_1}{200} = 0$

$$\frac{V_{th}}{100} = \frac{V_1}{100} - 1.5 \left(\frac{V_1}{200} \right) = 0 \quad \left\langle i_1 = \frac{V_1}{200} \right.$$

$$0.01V_{th} - 0.0175V_1 = 0$$

$$\boxed{-1.75V_1 + V_{th} = 0} \quad \text{--- (2)}$$
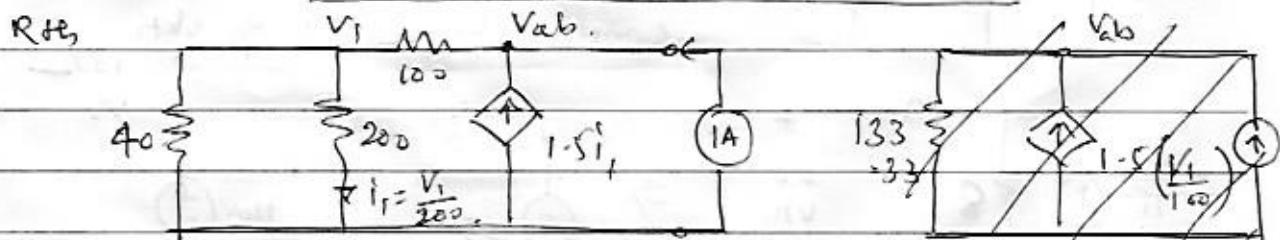
$$\boxed{V_1 = 22.22V \quad V_{th} = 38.88}$$



$$i_1 = \frac{V_1}{100}.$$

$$\frac{V_1}{40} + \frac{V_1}{200} + \frac{V_1 - V_{ab}}{100} = 0. \quad 0.04V_1 - 0.01V_{ab} = 0 \quad \text{--- (1)}$$



$$\frac{V_{ab} - V_1}{100} - 1.5 \left(\frac{V_1}{200} \right) + 1 = 0 \quad 0.0175V_1 - 0.01V_{ab} = 1 \quad \text{--- (2)}$$

$$V_{ab} = 177.77V$$

$$R_{th} = \frac{V_{ab}}{1A} = 177.77 \quad \text{--- (2)}$$

DATE

40

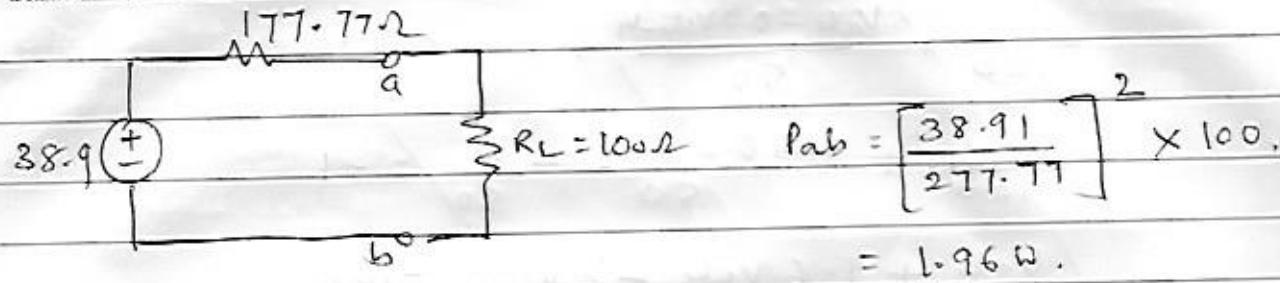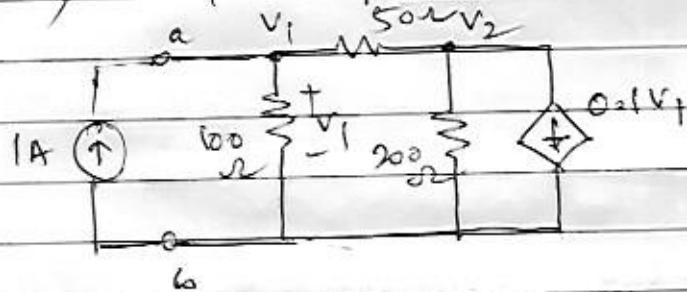26) Find TNE eq² ckt

At Node 1

$$\frac{V_1}{100} + \frac{V_1 - V_2}{50} = 1.$$

$$V_1 + 2V_1 - 2V_2 = 100.$$

$$3V_1 - 2V_2 = 100 \quad (1)$$

$$\frac{V_2}{200} + \frac{V_2 - V_1}{50} + 0.1V_1 = 0$$

$$V_2 + 4V_2 - 4V_1 + 0.1 \times 200V_1 = 0$$

$$16V_1 + 5V_2 = 0 \quad (2)$$


$$a \quad R_{th} = 10.638$$

$$b \quad V_{th} = 10.638$$

$$V_1 = 10.638 \quad V_2 = -34.042.$$

$$V_{th} = 10.638 \quad R_{th} = V_1/I_A = 10.638$$

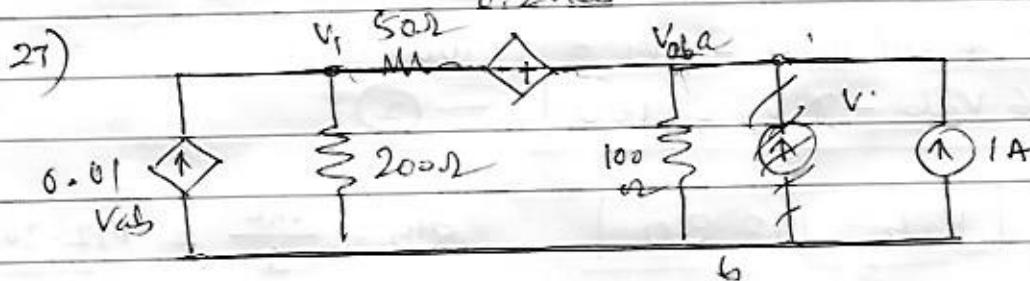$I_{th} = 0A$ As there is no \oplus independent sources $I_{th} = 0$, $V_{th} = 0$.



$$\frac{V_2}{100} + \frac{V_p}{200} + V_1 - V_{ab} + \frac{0.2V_{ab}}{50} - 0.1V_{ab} = 0.$$

$$\frac{V_1}{200} + \frac{V_1}{50} - \frac{0.2V_{ab}}{50} - 0.1V_{ab} = 0.$$

$$5V_1 - 3.2 - 20V_{ab} \quad 5V_1 - 4.8V_{ab} = 0.1 \times 200V_{ab}$$

$$5V_1 - 23.2V_{ab} = 0 \quad (1)$$

$$5V_1 - 24.8V_{ab} = 0 \quad (2)$$

$$\frac{V_{ab}}{100} + \frac{V_{ab} - 0.2V_{ab} - V_1}{50} + 1 = 0$$

$$\frac{V_{ab}}{100} + \frac{0.8V_{ab}}{50} - \frac{V_1}{50} = -1$$

$$V_{ab} + 1.6V_{ab} - 2V_1 = -100$$

$$-2V_1 + 2.6V_{ab} = -100$$

Node V_1

$$\frac{V_1}{200} + \frac{(V_1 + 0.2V_{ab} - V_{ab})}{50} - 0.01V_{ab} = 0$$

$$V_1 + 4V_1 - 0.8V_{ab} - 0.01 \times 200V_{ab} = 0$$

$$5V_1 - 3.2V_{ab} - 20 = 0$$

$$5V_1 - 5.2V_{ab} = 0 \quad \text{--- (1)}$$

Node V_{ab}

$$\frac{V_{ab}}{100} + \frac{V_{ab} - 0.2V_{ab} - V_1}{50} - 1 = 0$$

$$\frac{V_{ab}}{100} + \frac{0.8V_{ab}}{50} - \frac{V_1}{50} = 1$$

$$V_{ab} + 1.6V_{ab} - 4V_1 = 1 \times 100$$

$$2.6V_{ab} - 4V_1 = 100 \quad \text{--- (2)}$$

$$V_{ab} = 192.30$$


$$R_{th} = \frac{V_{ab}}{I} = \frac{192.30}{1} = 192.30 \Omega$$

$$V_2 = 0.1497$$

$$R = 0.1497$$


DATE

(28)

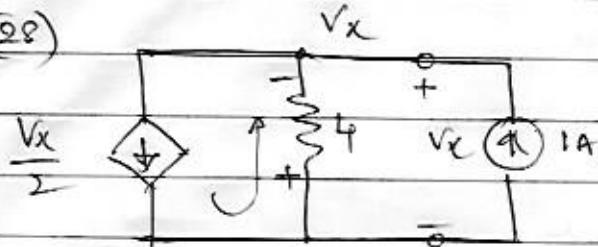

$$\frac{V_x}{2} + \frac{V_x}{4} - 1 = 0$$

$$2V_x + V_x - 4 = 0$$

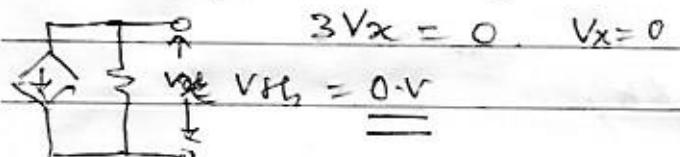


$$3V_x = 0, V_x = 0$$


$$3V_x = 4, V_x = \frac{4}{3} = 1.33$$

$$V_x = 1.33, R_{th} = \frac{V_x}{I} = \frac{1.33}{1} = 1.33$$

(29)

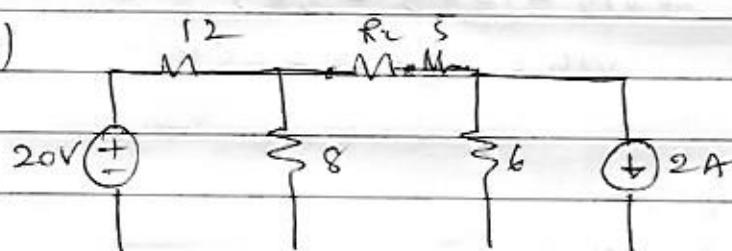

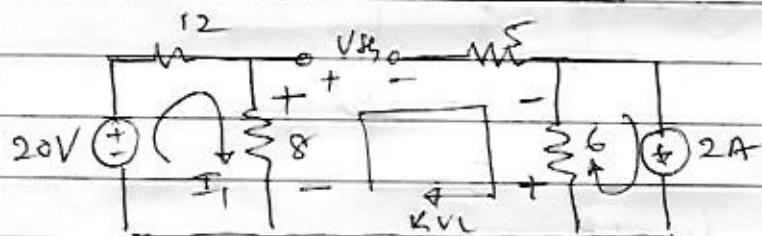
What is the maximum power that could be dissipated in R_L



$$-8I_1 + V_R + 5 \times 0 + 6 \times 2 = 0$$

$$-8(20/R) + V_R - 12 = 0$$

$$V_R = 12 + 8 = \underline{\underline{20V}}$$

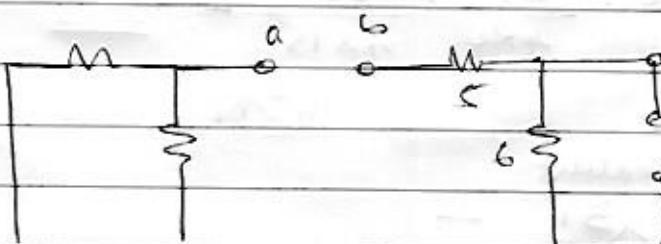 R_{th} 

P_L is max
when $R_L = R_S$

$$\therefore P_L = \frac{V_{th}^2}{4R_L}$$


$$= \frac{V_{th}^2}{4R_L}$$

$$= 20^2$$

$$= 400$$


DATE

(30)

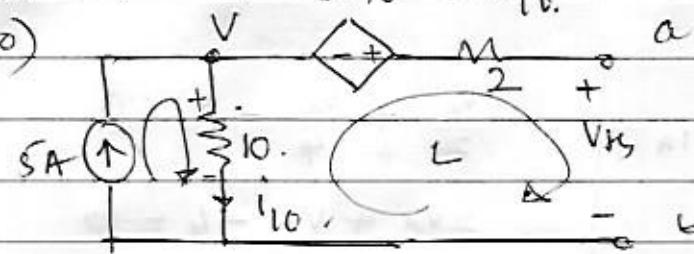


$$i_{10} = 5A$$
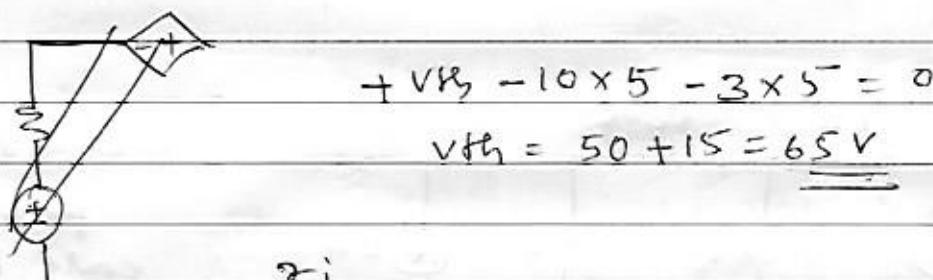
$$\begin{aligned} i_{10} &= 5 \times 10 = 50 \\ \text{KVL loop } L &: +V_{R3} - 10 \times 5 - 3 \times 5 = 0 \\ &+V_{R3} - 50 - 15 = 0 \\ &V_{R3} = 50 + 15 = 65V \end{aligned}$$



$$+V_{R3} - 10 \times 5 - 3 \times 5 = 0$$

$$V_{R3} = 50 + 15 = 65V$$

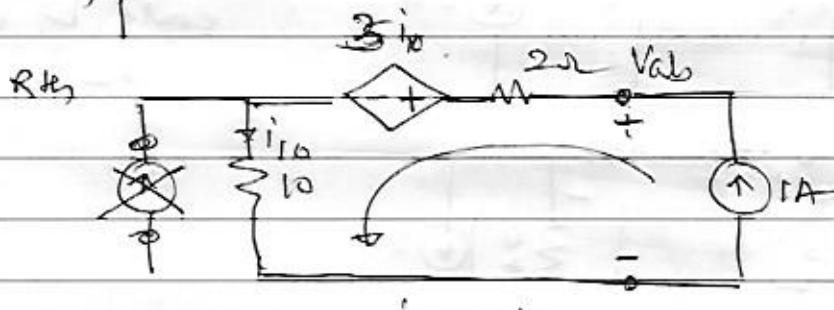

$$i_{10} = 1A$$

$$-V_{ab} + 2 + 3(1) + 10(1) = 0$$


$$V_{ab} = 15V$$

$$\therefore R_L = \frac{15}{1} = 15\Omega$$

$$P_{Lmax} = \frac{V_{R3}^2}{4R_L} = \frac{65^2}{4 \times 15} = 70.41 \text{ Watts}$$

$$I^2/R_L$$

* Norton's equivalent

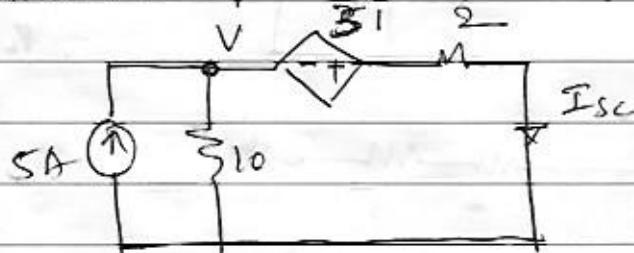

$$\frac{V}{10} + \frac{V + 3i}{2} - 5 = 0$$

$$\frac{V}{10} + \frac{V}{2} + \frac{3}{2} \left(\frac{V}{10} \right) = 5$$

$$\therefore V = 6.667V$$

$$I_{sc} = \left[V + 3 \left(\frac{V}{10} \right) \right] \div 2 = 4.33A$$


$$(2 + 10 + 3)V = 5$$

$$20$$

$$V = 5 \times \frac{20}{15}$$

DATE

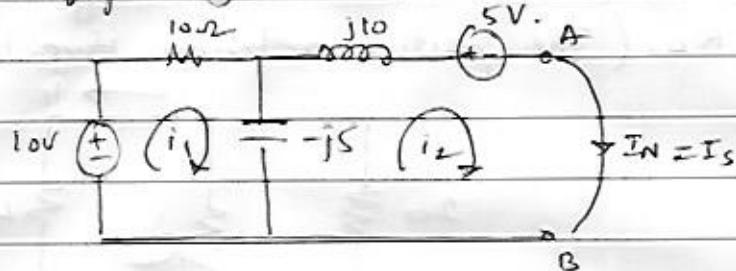
What current is 5Ω resistor connected between A & B in ckt. in fig using Nortons




$$\begin{pmatrix} 10-j5 & +j5 \\ +j5 & j5 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 10 \\ -5 \end{pmatrix} \quad \Delta = j50 + 25 + 25 = 50 + j50$$

$$\begin{pmatrix} 10-j5 & 10 \\ j5 & -5 \end{pmatrix} \quad \Delta_2 = -50 - j25.$$
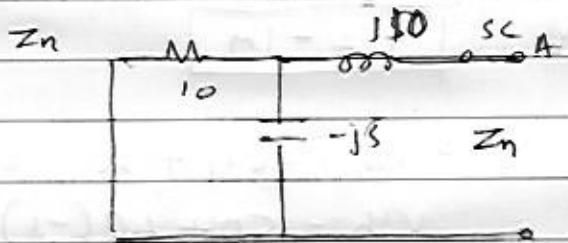
$$\therefore I_2 = \Delta_2 / \Delta = (-0.75 + j0.25)A = I_N.$$



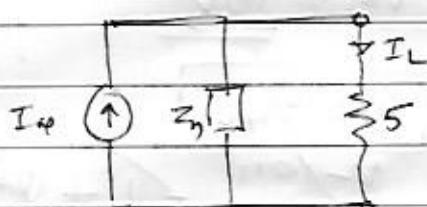
$$\begin{aligned} Z_{eq} &= \frac{10 \times -j5}{10 - j5} + j10 \\ &= \frac{-j50 + j10(10 - j5)}{10 - j5} \\ &= \underline{\underline{2 + 6j}} \end{aligned}$$





$$I_L = \frac{Z_N \times I_N}{Z_N + 5} = \frac{(2 + 6j) \times (-0.75 + j0.25)}{7 + 6j}$$

$$I_L = -0.53 - 0.117j.$$

(2) find Norton's equivalent ckt. What impedance must be connected between A & B for max power

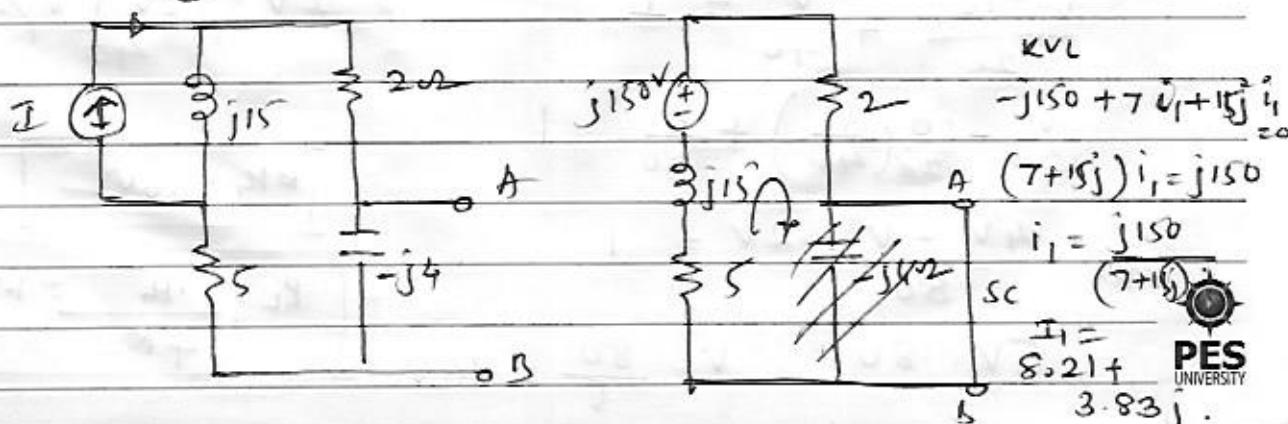10L^{0°}

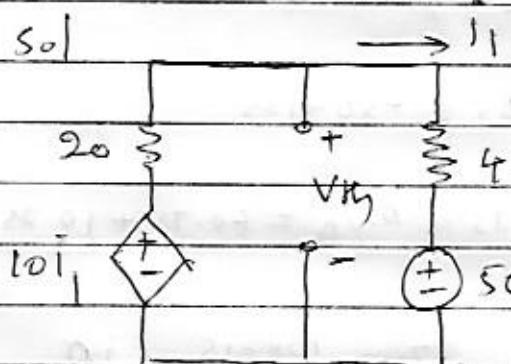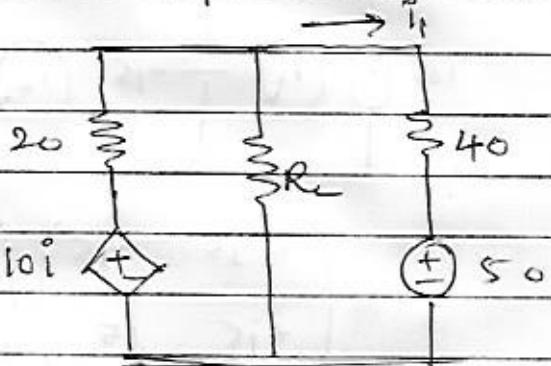(3) Determine the value of R_L to which maximum power can be delivered. Calculate the voltage across the corresponding R_L . (The positive reference direction is at the top)




KVL

$$\begin{aligned} -10i + 20i_1 + 40i_1 + 50 &= 0 \\ 50i_1 + 50 &= 0 \\ i_1 &= -1A \end{aligned}$$

$$-V_{RL} + 40i_1 + 50 = 0$$

$$\begin{aligned} V_{RL} &= 50 + 40(-1) = 0 \\ &= 50 - 40 \end{aligned}$$

$$V_{RL} = 10V$$

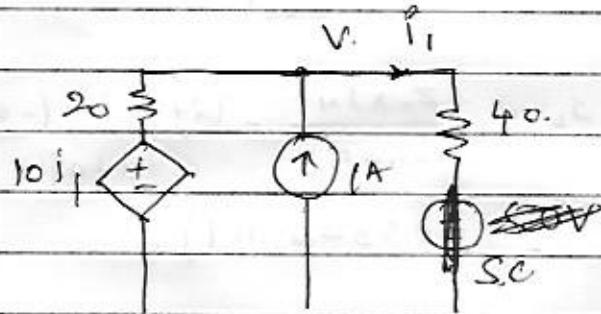

$$i_1 = V/40$$

$$\frac{V - 10i_1}{20} + 1 + \frac{V}{40} = 0$$

$$i_1 = \frac{V}{40}$$

$$\frac{V}{20} - 10\left(\frac{V}{40}\right) + \frac{V}{40} = 1$$

$$\frac{V - 10i_1}{20} + \frac{V}{40} = 1$$

$$\frac{2V - 10V + V}{40} = 1$$

$$\frac{V - 10\left(\frac{V}{40}\right)}{20} + \frac{V}{40} = 1$$

$$R_{RL} = 16\sqrt{2}$$

$$\frac{4V - V + 2V}{80} = 1$$


$$5V = 80$$

$$V = \frac{80}{5} = 16V$$



$$P_L = \frac{V_{RL}^2}{4R_L} = 1.5625 \text{ Watts}$$

DATE

(32)

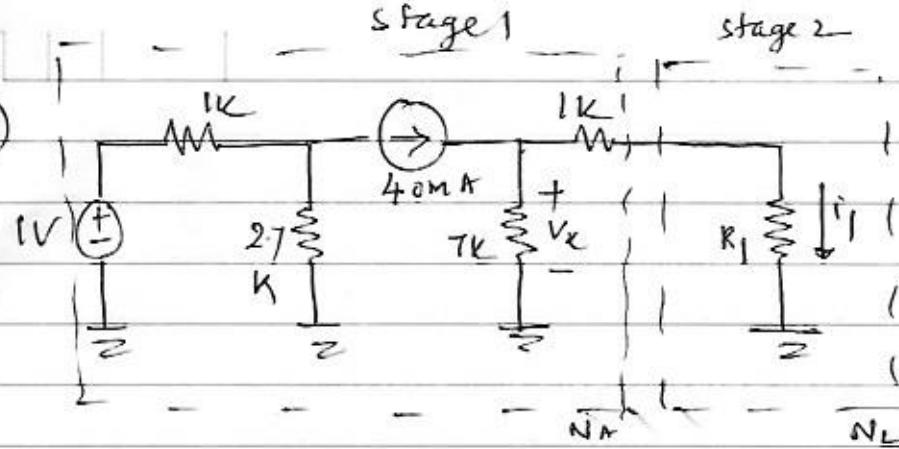

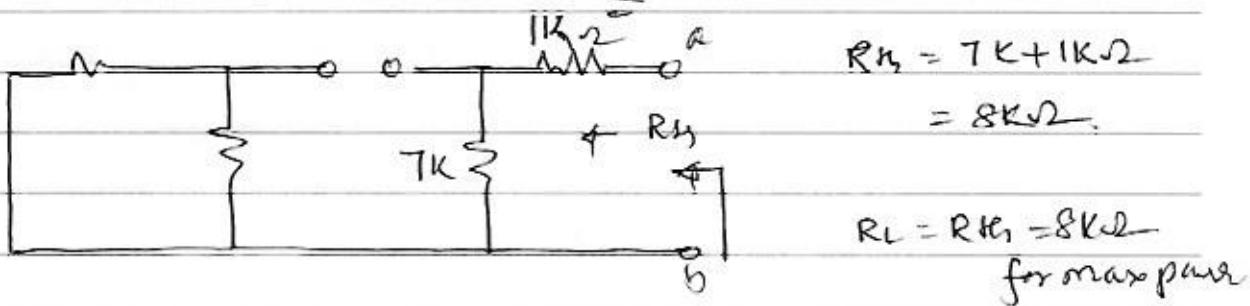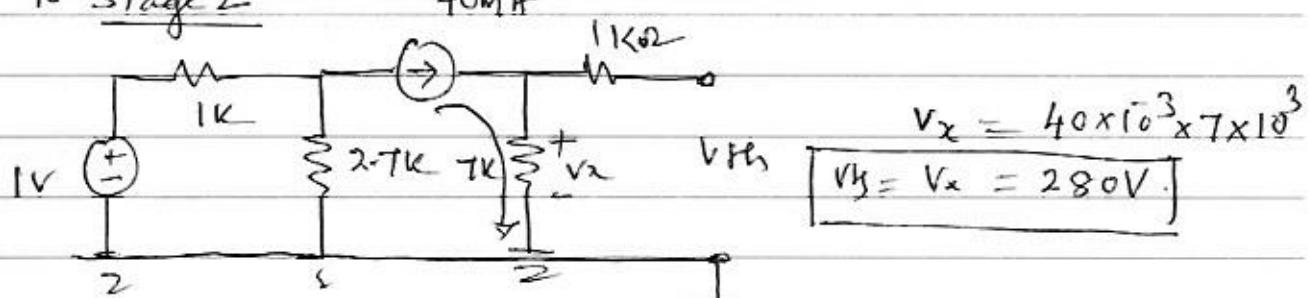
Select R_L so that max power is transferred from stage 1 to stage 2



DATE

* Maximum Power Transfer Theorem.

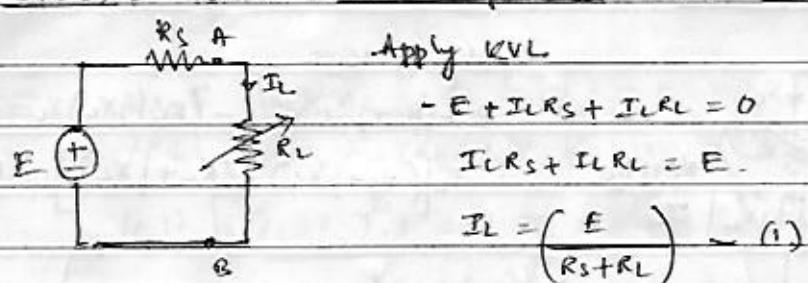Case (i) : When source impedance and load impedance are resistive.



Power received by the load resistance $P_L = |I_L|^2 \cdot R_L$ Watts.

$$P_L = \frac{|E|^2}{(R_s + R_L)^2} \cdot R_L \quad \text{--- (2)}$$

Power received by load resistance is maximum at some value of R_L (0 to ∞)
ie. It maximum when

$$\frac{dP_L}{dR_L} = 0$$

$$\frac{d}{dR_L} \left(\frac{|E|^2}{(R_s + R_L)^2} \cdot R_L \right) = 0$$

$$|E|^2 \left[\frac{(R_s + R_L)^2 \frac{dR_L}{dR_L} - R_L \frac{d}{dR_L} (R_s + R_L)}{(R_s + R_L)^2} \right] = 0$$

$$|E|^2 \left[\frac{(R_s + R_L)^2 - R_L 2(R_s + R_L)(1)}{(R_s + R_L)^3} \right] = 0$$

$$|E|^2 \left[\frac{R_s + R_L - 2R_L}{(R_s + R_L)^3} \right] = 0$$


$$R_s + R_L - 2R_L = 0 \Rightarrow R_s - R_L = 0.$$

$$\therefore [R_s = R_L] \quad \text{--- (3)}$$

for power received by load resistance to be maximum, load resistance must be equal to source resistance ie $R_L = R_s$.


By substituting (3) in (2).

$$P_L = \frac{|E|^2}{(R_s + R_L)^2} (R_L) = \frac{|E|^2 R_L}{4 R_s^2} = \frac{|E|^2}{4 R_s} \text{ watts.}$$

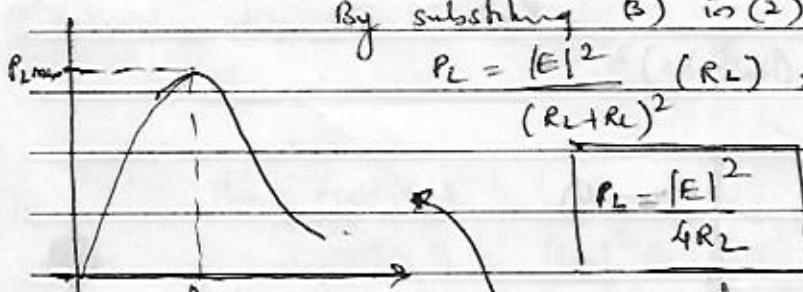

Variation of P_L w.r.t R_L . It is max when $R_L = R_s$.

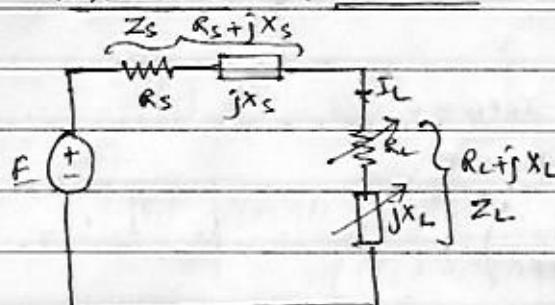Case (ii) : When source impedance and load impedance are complex & where resistance and reactance are variable independently.



Applying KVL

$$E - (R_s + jX_s) I_L - (R_L + jX_L) I_L = 0.$$

$$I_L [(R_s + jX_s) + (R_L + jX_L)] = E.$$

$$I_L = \frac{E}{[(R_s + R_L) + j(X_s + X_L)]} \quad \text{--- (1)}$$

$$|I_L| = \frac{|E|}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$\text{Load power } P_L = |I_L|^2 \cdot R_L$$

$$P_L = \frac{|E|^2}{(R_s + R_L)^2 + (X_s + X_L)^2} \times R_L \quad \text{--- (2)}$$

Keeping load resistance constant & varying X_L . Then power received by load is maximum $\frac{dP_L}{dX_L} = 0$.

$$\frac{dP_L}{dX_L} \left[\frac{|E|^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \right] = 0.$$

$$|E|^2 R_L \left[\frac{(R_s + R_L)^2 + (X_s + X_L)^2 (0) - 1 \cdot (0 + 2(X_s + X_L))}{((R_s + R_L)^2 + (X_s + X_L)^2)^2} \right] = 0$$

$$-2(X_s + X_L) = 0$$

$$-2X_s = 2X_L$$

$$\therefore [X_L = -X_s] \quad \text{--- (3)}$$

It means when $X_L = -X_s$, maximum power is received by load
Substituting (3) in (2)

$$P_L = \frac{|E|^2}{(R_s + R_L)^2 + (X_s - X_s)^2} \times R_L$$

$$\boxed{P_L = \frac{|E|^2 R_L}{(R_s + R_L)^2}} \quad \text{--- (4)}$$

DATE

Keeping X_L constant at $-X_S$ and varying R_L , then power received by load is max $\frac{dP_L}{dR_L} = 0$

$$\frac{dI}{dR_L} \left[\frac{|E|^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} \right] = 0$$

$$|E|^2 \left[\frac{(R_S + R_L) \cdot 1 - R_L \cdot 2(R_S + R_L)}{(R_S + R_L)^3} \right] = 0. \quad \therefore X_S = X_L \quad X_L = -X_S.$$

$$|E|^2 \left[\frac{R_S + R_L - 2R_L}{(R_S + R_L)^3} \right] = 0$$

$$R_S + R_L - 2R_L = 0 \quad R_S - R_L = 0.$$

$$R_L = R_S \quad \text{--- (5)}$$

We have load impedance


$$Z_L = R_L + jX_L$$

By substituting (4) & (5) [max power cond.]

$$\begin{aligned} Z_L &= R_S - jX_S. \\ \therefore Z_L &= Z_S^*. \end{aligned} \quad \text{--- (6)}$$

It means, when source impedance and load impedance are complex, ~~and~~ Maximum power is received by load when load imp and source impedance are complex conjugate.

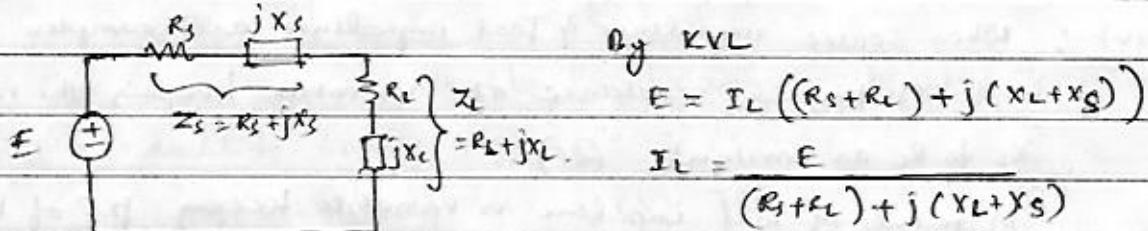Case (iii) - When some of load impedance are complex but only load resistance is varying.



$$|I_L| = \frac{|E|}{\sqrt{(R_S + R_L)^2 + (X_L + X_S)^2}} \quad \text{--- (1)}$$

Power received

$$P_L = \frac{|E_L|^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} \quad \text{--- (2)}$$

When R_L is varied from $(0 \text{ to } \infty)$ Power received by load is max when

$$\frac{dP_L}{dR_L} = 0$$

$$\frac{dI}{dR_L} \left[\frac{|E|^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \right] = 0 |E|$$

$$|E|^2 \left[\frac{(R_s + R_L)^2 + (X_s + X_L)^2 \cdot 1 - R_L (2(R_s + R_L))}{((R_s + R_L)^2 + (X_s + X_L)^2)^2} \right]$$

$$(R_s + R_L)^2 + (X_s + X_L)^2 - 2R_L R_s - 2R_L^2 = 0.$$

$$R_s^2 + R_L^2 + 2R_s R_L + (X_s + X_L)^2 - 2R_s R_L - 2R_L^2 = 0$$

$$R_s^2 - R_L^2 + (X_s + X_L)^2 = 0.$$

$$R_L^2 = R_s^2 + (X_s + X_L)^2.$$

$$R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$$

fixed impedance


$$R_s + j(X_s + X_L)$$

Magnitude of this is

$$\sqrt{R_s^2 + (X_s + X_L)^2}$$


Power received by load is maximum when R_L is equal to magnitude of fixed impedance
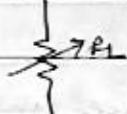
$$Ex: \quad \underline{3+j4} \quad m \quad 6\Omega$$



$$R_L = \sqrt{(3)^2 + (4)^2} = 5\Omega.$$

$$\underline{4+j4} \quad m$$


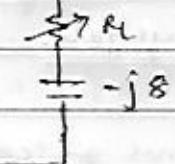


$$R_L = \sqrt{(4)^2 + (X_s + X_L)^2}$$

$$= \sqrt{16 + (4-8)^2} = \sqrt{16+16} = \sqrt{32} \Omega.$$

Case (iv) : When source impedance & load impedance are complex with load resistance & reactance are variable keeping the ratio of $X_L : R_L$ as constant (or)

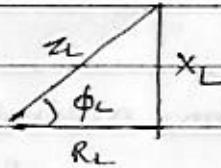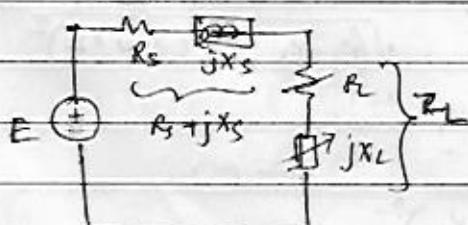Magnitude of load impedance is variable keeping p.f of load as the constant



$$\cos \phi_L = \frac{R_L}{|Z_L|} \quad R_L = |Z_L| \cos \phi_L$$

$$\tan \phi = \frac{X_L}{R_L}$$

$$X_L = |Z_L| \sin \phi_L$$

DATE

By KVL

$$E = [(R_s + jX_s) + (R_L + jX_L)] I_L$$

$$I_L = \frac{E}{(R_s + R_L) + j(X_s + X_L)}$$

$$|I_L| = \frac{|E|}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$P_L = |I_L|^2 R_L = \frac{|E|^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

$$P_L = \frac{|E|^2 |Z_L| \cdot \cos \phi_L}{(R_s + |Z_L| \cos \phi_L)^2 + (X_s + |Z_L| \sin \phi_L)^2}$$

Z_L is varied from 0 to ∞ .

When power received by load is max. $\frac{dP_L}{dZ_L} = 0$.

$$\therefore \frac{d}{dZ_L} \left(\frac{|E|^2 |Z_L| \cos \phi_L}{(R_s + |Z_L| \cos \phi_L)^2 + (X_s + |Z_L| \sin \phi_L)^2} \right) = 0.$$

$$|E|^2 \left[\frac{Dn(\cos \phi_L) - Nn(2() \cos \phi_L + 2() \sin \phi_L)}{\left((R_s + |Z_L| \cos \phi_L)^2 + (X_s + |Z_L| \sin \phi_L)^2 \right)^2} \right] = 0$$

$$\therefore \cos \phi_L = n_n [2() \cos \phi_L + 2() \sin \phi_L]$$

$$R_s^2 + X_s^2 + |Z_L|^2 = 2 |Z_L|^2$$


$$R_s^2 + X_s^2 = |Z_L|^2$$

$$|Z_L| = \sqrt{R_s^2 + X_s^2}$$

$$|Z_L| = |Z_s|$$

for maximum power transfer magnitude of load imp must be equal to magnitude of source impedance.

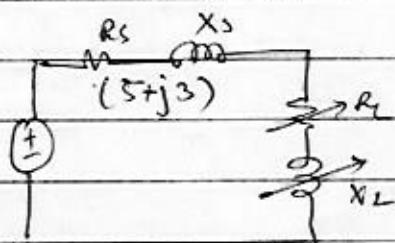Ex: In the ckt shown below find the value of R_L & X_L if the load resistance is reactance variable with ratio $X_L/R_L = 0.2$



As $X_L/R_L = 0.2$ [Ratioed]


for

$$|Z_L| = |Z_s|$$

$$= \sqrt{(5)^2 + (3)^2} = \sqrt{34} = 5.83$$

$$\therefore R_L = |Z_L| \cos \phi_L \quad \tan \phi_L = \frac{X_L}{R_L} = 0.2 \quad \therefore \phi_L = 11.3^\circ$$

$$= 5.83 \cos(11.3^\circ) = 5.71 \quad \text{if } X_L = |Z_L| \sin \phi_L = 1.41 \quad Z_L = 5.71 + j1.41$$

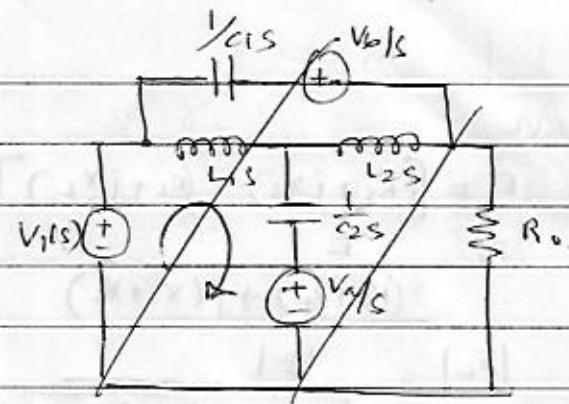

$$\frac{V_1(s)}{V_2(s)} = \frac{(L_1s + \frac{1}{C_2s})}{(L_2s + \frac{1}{C_2s})}$$

DATE

Energy and Power

- Consider a one port network with reference directions for V & i to define power

- The energy absorbed by the n/w from time t_1 to t_2 is
- $$W = \int_{t_1}^{t_2} V(t) \cdot i(t) \cdot dt \text{ Joules} \quad \rightarrow (1)$$
-

The rate at which energy is absorbed is the power (ie instantaneous power)

$$P(t) = \frac{dW}{dt} = \frac{d}{dt} \left(\int_{t_1}^{t_2} V(t) \cdot i(t) \cdot dt \right) = V(t) \cdot i(t) \text{ Watts} \quad \rightarrow (2)$$

Convention : for the voltage & current reference shown in fig,

A positive P indicate flow of energy into the n/w.

If either the voltage / current reference is changed, reversed ; so is the reference of energy

- (i) Let us consider n/w with single linear elements like R, L and C .

a) Resistor (R) :

w.k.t $V = iR$ and energy absorbed is

$$W_R = \int_{t_1}^{t_2} V(t) \cdot i(t) \cdot dt = \int_{t_1}^{t_2} i^2(t) \cdot R \cdot dt = R \int_{t_1}^{t_2} i^2(t) \cdot dt \\ = \frac{1}{R} \int_{t_1}^{t_2} V^2(t) \cdot dt \quad \rightarrow (3)$$

and Instantaneous power (rate at which energy is absorbed)

$$P_R = R i^2(t) = \frac{1}{R} V^2(t) \quad \rightarrow (4)$$

for a sinusoidal current, $i = I_m \sin \omega t$ with $t_1 = 0$, energy absorbed (eq: (3)) can be given by


$$W_R = \int_0^{t_2} i^2(t) \cdot R \cdot dt = R \int_0^{t_2} I_m^2 \sin^2 \omega t \cdot dt \\ = I_m^2 R \int_0^{t_2} \frac{1 - \cos 2\omega t}{2} \cdot dt$$

$$\boxed{W_R = \frac{I_m^2 R}{2} \left(t - \frac{\sin 2\omega t}{2\omega} \right) J} \quad \rightarrow (5)$$


DATE

Instantaneous power eq² (4) can be written as

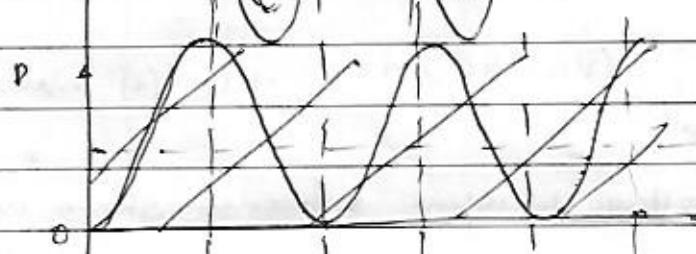
$$P_R = R \cdot I_m^2 \sin^2 \omega t = \frac{R I_m^2}{2} (1 - \cos 2\omega t) \quad \text{Watts} \quad \rightarrow (6)$$



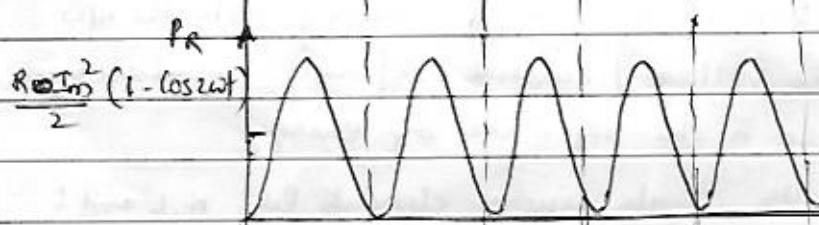P_R varies at twice the freq of V_R, I_R
and ϕ_{P_R} is always zero.


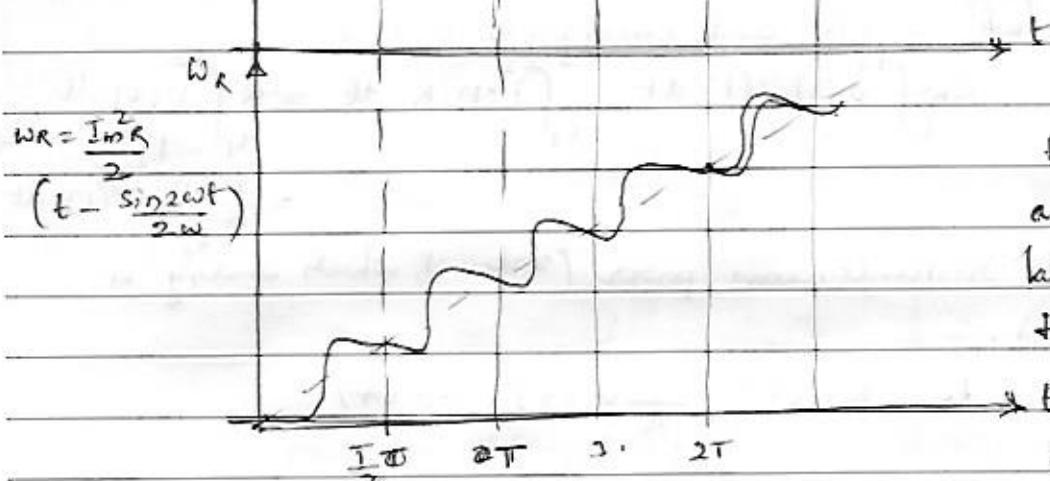
$$P_{av,R} = \frac{R}{2} I_m^2 = R \left(\frac{I_m^2}{2} \right)$$



Energy W_R is always +ve
and increases to very large value with increasing time.

$$\Delta W_R = R \int_0^T i^2(t) dt = \frac{1}{2} R I_m^2 T$$

Energy absorbed per cycle

Conclusion:

- both power and energy varies at twice the freq of voltage or current
- Power and energy are always positive
- Energy increases with time

DATE

b) for an inductor (L)

w.r.t $V = L \frac{di}{dt}$, the energy which enters inductor for storage (energy absorbed) is - from eq²(1)

$$W_L = \int_{t_1}^{t_2} \left(L \frac{di}{dt} \right) V(t) dt$$

$$= \int_{t_1}^{t_2} \left(L \cdot \frac{di}{dt} \right) i \cdot dt = \int_{t_1}^{t_2} L \cdot i \cdot di = L \frac{i^2}{2} \Big|_{t_1}^{t_2}$$

$$\boxed{W_L = \frac{L}{2} (i^2(t_2) - i^2(t_1))} \quad \text{J.} - (7)$$

$i(t_2)$ and $i(t_1)$ are current at t_2 & t_1

If we let $i(t_1) = 0$ at t_1 and if $i(t_2) = I_m \sin \omega t$, then

$$\boxed{W_L = \frac{L}{2} (I_m^2 \sin^2 \omega t) = \frac{L I_m^2}{2} \frac{(1 - \cos 2\omega t)}{2}} - (8)$$

and the power

$$P_L(t) = \frac{d}{dt} \left(\frac{1}{2} L i^2 \right) = L i \frac{di}{dt} - (9)$$

$$\text{If } i(t) = I_m \sin \omega t \quad t \geq 0$$

$$P_L(t) = L I_m^2 \sin \omega t \frac{d(I_m \sin \omega t)}{dt}$$

$$= L I_m^2 \sin \omega t \cos \omega t (\omega)$$

$$= L I_m^2 \omega \sin \omega t \cos \omega t$$

$$\boxed{P_L(t) = \frac{L I_m^2 \omega}{2} \sin 2\omega t} \quad \text{Watt} - (10)$$


From V , i , P_L , and W_L it is clear that

- $V \neq i$ i.e. V leads i by 90°

- P_L & W_L are varying at twice the freq of V & i
but the maximum value of W_L remain ~~same~~ same
for each cycle.

- P_L is (+)ve as well as (-)ve and ω is always (+)ve.

DATE

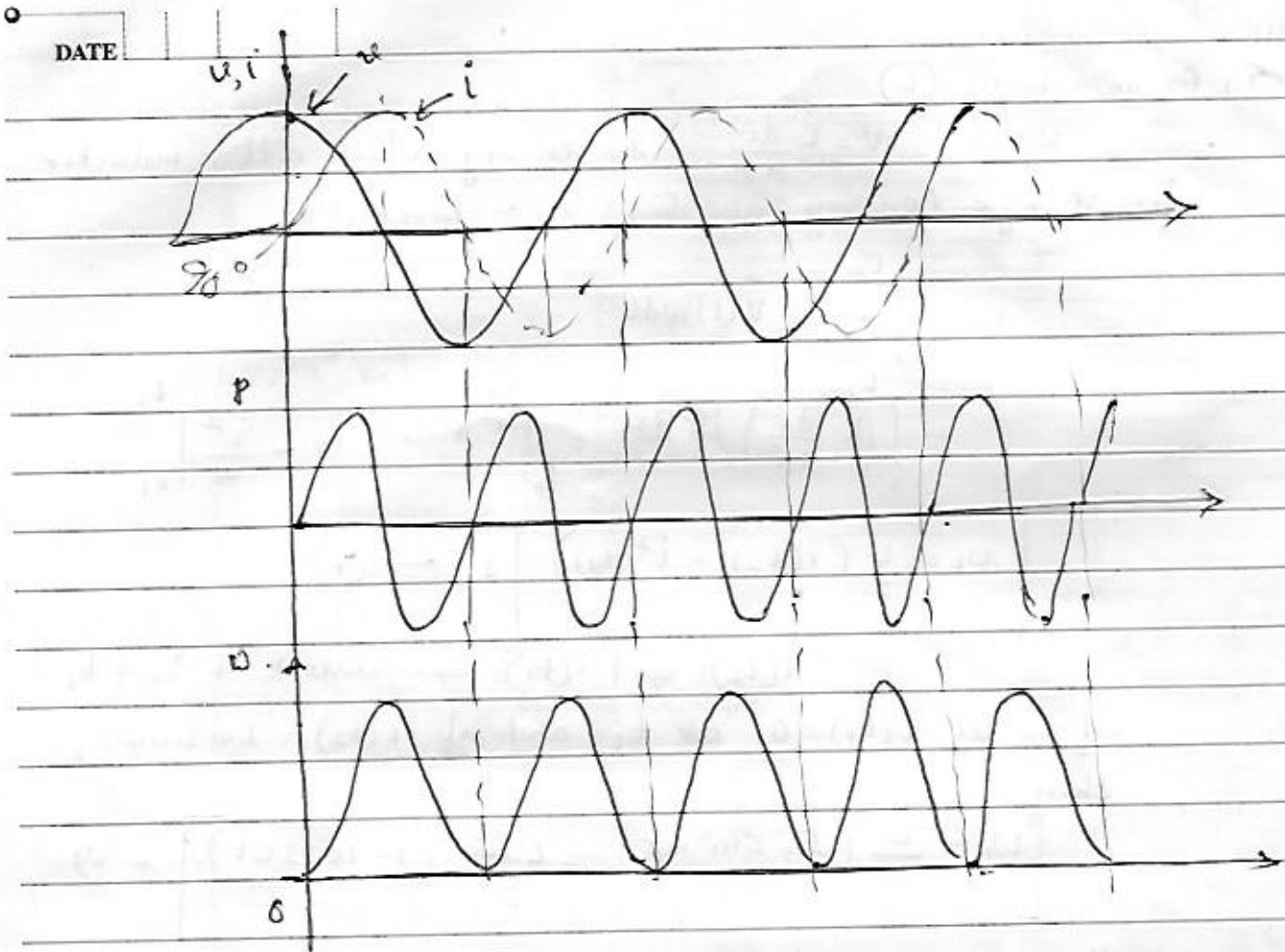

c) for Capacitor,

$$i = C \frac{dv}{dt} \quad -(i)$$

Energy absorbed is

$$w_c = C \int_{t_1}^{t_2} v(t) \cdot \frac{dv(t)}{dt} dt = C \int_{t_1}^{t_2} v dv$$

$$\boxed{w_c = \frac{1}{2} C (v^2(t_2) - v^2(t_1))}$$

$$\text{and } \boxed{P_c(t) = C \cdot v \cdot \frac{dv}{dt}} \quad t > 0 \quad -(ii)$$

for instantaneous sinusoidal voltage $v(t) = V_m \sin \omega t, t > 0$

$$w_c(t) = \frac{1}{2} C V_m^2 \sin^2 \omega t = \frac{1}{4} C V_m^2 (1 - \cos 2\omega t)$$

$$P_c(t) = C V_m^2 \frac{d}{dt} (\sin \omega t) = C \cdot V_m^2 \sin \omega t \cos \omega t (\omega)$$

Only $\frac{1}{2}\pi$ phase shift
charge wrt inductor

$$\boxed{P_c(t) = C V_m^2 \frac{\omega}{2} \sin 2\omega t} \quad -(iii)$$

W_c, P_c behaves similarly as inductor

DATE _____

Average PowerInductor: If T is the period

$$P_{av,L} = \frac{1}{nT} \int_0^{nT} \frac{1}{2} L I_m^2 \omega \sin 2\omega t \cdot dt = 0.$$

similarly for capacitor

$$P_{av,C} = \frac{1}{nT} \int_0^{nT} \frac{1}{2} C V_m^2 \omega \cdot \sin 2\omega t \cdot dt = 0.$$

for Resistor;

$$\begin{aligned} P_{av,R} &= \frac{1}{nT} \int_0^{nT} \frac{1}{2} R I_m^2 (1 - \cos 2\omega t) \cdot dt = \left(\frac{1}{2} R I_m^2 \right) \\ &= R \left(\frac{I_m}{\sqrt{2}} \right)^2 \end{aligned}$$

P_{av,L} and P_{av,C} is equal to zero for each cycle and for a resistor $P_{av,R} = \frac{R}{2} I_m^2 = R \left(\frac{I_m}{\sqrt{2}} \right)^2$

Average Energy

- for each cycle, the energy supplied to a capacitor or inductor is zero. i.e $\frac{W_{av,L}}{\text{cycle}} = \frac{W_{av,C}}{\text{cycle}} = 0$

- for Resistor, the energy absorbed per cycle

$$\Delta W_R = R \int_0^T i^2(t) \cdot dt = \frac{1}{2} R \cdot I_m^2 T.$$

* Effective (or) RMS (Root Mean Square) Value

- Effective value of a periodic current is defined as constant value of current which will produce the same power in a resistor as is produced on the avg by the periodic current
- for constant current I ,

$$P = I^2 R \quad \text{--- (1)}$$

for sinusoidal steady state, the avg power

$$P_{av, R} = \frac{1}{nT} \int_0^{nT} \frac{1}{2} R I_m^2 (1 - \cos 2\omega t) dt = \frac{1}{2} R I_m^2$$

According def² of Effect / RMS value

$$P = P_{av, R}$$

$$I^2 R = R \cdot \left(\frac{I_m}{\sqrt{2}} \right)^2$$

$$\therefore \left[\frac{I_{eff}}{V} = \frac{I_m}{\sqrt{2}} \right] \quad \text{--- (2)}$$

$\therefore P = V^2/R$ ~~and~~ for d.c.

$$\frac{V^2}{R} = \frac{R}{2} (I_m)^2 \times \frac{R}{R} = \frac{(I_m R)^2}{2R} = \frac{V_m^2}{R^2} = \frac{1}{R} \left(\frac{V_m}{\sqrt{2}} \right)^2$$

$$\therefore \left[V_{eff} = \frac{V_m}{\sqrt{2}} \right] \quad \text{--- (3)}$$

finally $P_{av} = I_{eff}^2 R = I_{eff} V_{eff}$

for Non sinusoidal but periodic current $i(t)$ of period T

$$P_{av} = \frac{1}{T} \int_{t_0}^{t_0+T} R i^2(t) \cdot dt$$

$$\therefore I_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) \cdot dt} = I_{rms}$$

$$V_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V^2(t) \cdot dt} = V_{rms}$$

$$P_{av} = I_{rms} V_{rms}$$

Avg Power

$$\frac{\text{Avg Power}}{\text{T in period}}$$

Inductor

$$P_{av, L} = \frac{1}{n\tau_0} \int_{0}^{n\tau_0} \frac{1}{2} L I_m^2 \omega \sin 2\omega t \cdot dt = 0$$

Capacitor

$$P_{av, C} = \frac{1}{n\tau_0} \int_{0}^{n\tau_0} \frac{1}{2} C V_m^2 \omega \sin 2\omega t \cdot dt = 0$$

Resistor

$$P_{av, R} = \frac{1}{n\tau_0} \int_{0}^{n\tau_0} \frac{1}{2} R I_m^2 (1 - \cos 2\omega t) \cdot dt$$

$$= \frac{1}{2} R I_m^2$$

$$P_{av, R} = R \cdot \left(\frac{I_m}{\sqrt{2}} \right)^2$$



Avg Energy

Inductor
+ capacitor

$$\boxed{W_{av, L} = \omega_{av} C = 0}$$

R
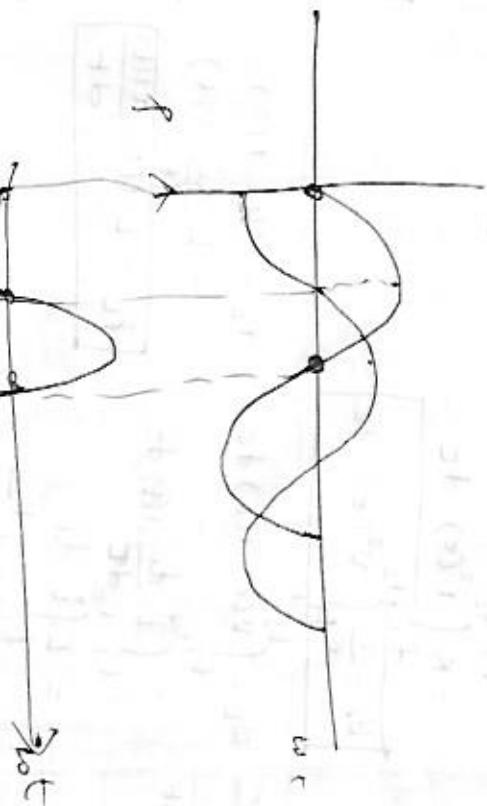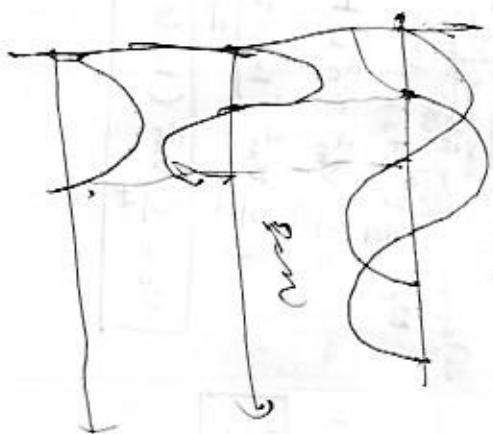
$$\Delta W_R = R \int_0^T i^2(t) \cdot dt$$
$$\boxed{\Delta W_R = \frac{1}{2} R I_m^2 T}$$



RMS Effective Power

$$\text{Resistor } (R) \rightarrow V(t) = i(t) \cdot R$$

$$\text{Power } (P_R) = V(t) \cdot i(t)$$

$$\boxed{P_R = i(t)^2 \cdot R = \frac{V^2(t)}{R}} \quad -(i)$$

(i) If excitation is sinusoidal.

$$i(t) = I_{\text{rms}} \sin \omega t$$

$$\begin{aligned} P_R &= (I_{\text{rms}}^2 \cdot \sin^2 \omega t) \cdot R \\ &= I_{\text{rms}}^2 R \cdot \sin^2 \omega t \\ &= I_{\text{rms}}^2 R \left(1 - \frac{\cos 2\omega t}{2} \right) \\ \boxed{P_R = \frac{I_{\text{rms}}^2 R}{2} (1 - \cos 2\omega t)} \end{aligned}$$

Avg power for one cycle

$$\begin{aligned} P_{\text{av}} &= \frac{I_{\text{rms}}^2 R}{2} \int_0^T (1 - \cos 2\omega t) dt \\ &= \frac{I_{\text{rms}}^2 R}{2} \cdot T \quad T = \pi \\ &= \frac{I_{\text{rms}}^2 R}{2} \left[t \Big|_0^T + \frac{\sin 2\omega t}{2\omega} \Big|_0^T \right] \\ &= \frac{I_{\text{rms}}^2 R}{2} \cdot T \end{aligned}$$

$$\boxed{P_{\text{av}} = \frac{I_{\text{rms}}^2 R}{2}}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \quad I_{\text{rms}} = \frac{I_m}{\sqrt{2}}$$

$$\boxed{P_{\text{av}} = \frac{I_m (V_m)}{2} = V_{\text{rms}} \cdot I_{\text{rms}}}.$$

(ii) Non sinusoidal & periodic

$$P_{\text{av}} = \frac{1}{T} \int_{t_0}^{t_0+T} i^2(\tau) R \cdot d\tau$$

$$I_{\text{eff}} = I_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(\tau) d\tau}$$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V^2(\tau) d\tau}$$

$$\boxed{P_{\text{av}} = V_{\text{rms}} \times V_{\text{rms}}}$$

Avg Power and Complex power

$$P_{\text{av}} = \frac{I_{\text{rms}}^2 R}{2} = \frac{V_{\text{rms}}^2}{2R} \text{ watts.}$$


In terms of rms values

$$P_{\text{av}} = \frac{I_{\text{rms}}^2 R}{2} = \left(\frac{I_{\text{rms}}}{\sqrt{2}} \right)^2 \cdot R = I_{\text{rms}}^2 R$$

$$P_{\text{av}} = \frac{V_{\text{rms}}^2}{2R} = \frac{1}{R} \left(\frac{V_{\text{rms}}}{\sqrt{2}} \right)^2 = \frac{V_{\text{rms}}^2}{R}$$

$$Z(j\omega) = R + jX$$

$$R = \text{Re}(Z(j\omega))$$

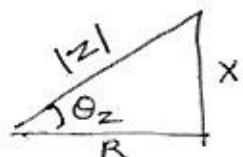

$$\cos \theta = \frac{R}{|Z|}$$

~~$$R = \text{Re}(Z(j\omega)) \quad R = |Z| \cdot \cos \theta \quad \text{--- (a)}$$~~

$$\sin \theta = \frac{X}{|Z|}$$

$$X = |Z| \cdot \sin \theta. \quad \text{--- (b)}$$

$$P_{\text{av}} = I_{\text{rms}}^2 R$$

$$\boxed{P_{\text{av}} = I_{\text{rms}}^2 |Z| \cdot \cos \theta_Z} \quad \text{--- (i)}$$

~~$$R = \text{Re } Z(j\omega)$$~~

$$\boxed{P_{\text{av}} = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos \theta_Z}$$

Power factor (pf) - cosine angle of the impedance

(or) phase difference between ϕ_V & i


p.f. - leading / lagging
I leads V V leads I

Imaginary part of power

$$Q = I_{\text{rms}} V_{\text{rms}} |Z|$$

$$\boxed{Q = I_{\text{rms}}^2 |Z| \cdot \sin \theta}$$
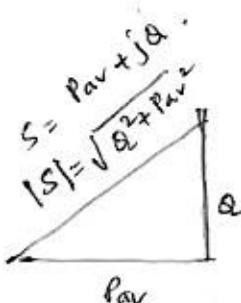
$$\boxed{Q = I_{\text{rms}} V_{\text{rms}} \cdot \sin \theta_Z}$$



$$S^2 = P_{\text{av}}^2 + Q^2 \quad S = \sqrt{P_{\text{av}}^2 + Q^2} = V_{\text{rms}} I_{\text{rms}} \cos \theta_Z$$

$$Ex: V = V_m e^{j\theta_v} \quad I = I_m e^{j\phi_i}$$

$$R_{eq} = \left| Z = \frac{V_m L \theta_v}{I_m L \theta_i} = \frac{V_m}{I_m} L \theta_v - \theta_i \right| \quad \text{when } p_f = \theta_v - \theta_i$$

↳ (a) $\frac{V_{rms}}{\theta_v}$ $[\theta_v]$

$$\text{complete power } S = \text{VarTerms} \cdot L_{\text{Or}} - \theta_i$$

$$S = P_{av} + jQ = V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \cdot \sin(\theta_v - \theta_i)$$


 The diagram illustrates the decomposition of apparent power S into its components. A horizontal bracket under the term $V_{rms} I_{rms} \cos(\theta_v - \theta_i)$ is labeled P_{av} . Another horizontal bracket under the term $j V_{rms} I_{rms} \cdot \sin(\theta_v - \theta_i)$ is labeled Q . A vertical bracket on the left side of the equation, spanning both terms, is labeled \rightarrow Reactiva power.


Note - ① If reactive power is (-)ve it means,


$$f_{\text{ave}} =$$

- i) pf angle is negative..
 - ii) pf is leading and ^{capacitive is}
 - iii) Reactance is ~~Opposite~~ or same


② of a u (+) re

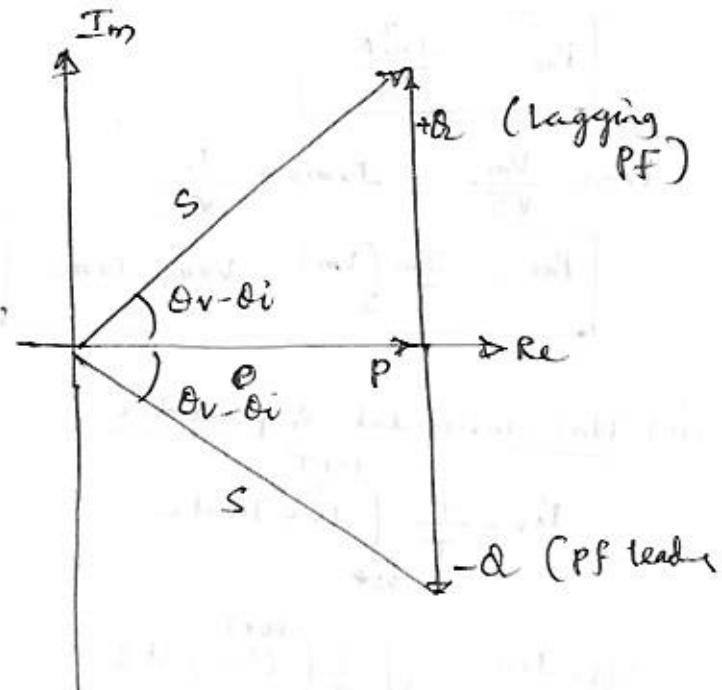- i) pf angle is (+)ve
 - ii) pf is lagging
 - iii) Reactance is Inductor is same



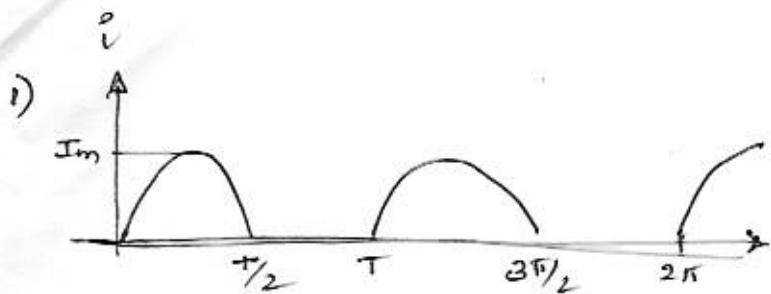

$$I_{rms} = \frac{Im}{2}$$

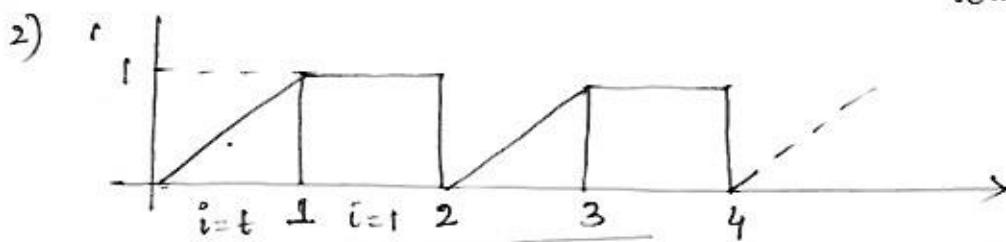

Period Waveform descs

$$i(t) = \begin{cases} 0 & 0 \leq t < 1 \\ 1 & 1 \leq t \leq 2 \end{cases}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt}$$

$$= \sqrt{\frac{1}{2} \left(\int_0^1 t^2 dt + \int_1^2 1^2 dt \right)}$$

$$= \sqrt{\frac{1}{2} \left[\frac{t^3}{3} \Big|_0^1 + 1 \Big|_1^2 \right]}$$

$$= \sqrt{\frac{1}{2} \left[\frac{1}{3} + (2 - 1) \right]} = \sqrt{\frac{1}{2} \times \frac{1}{3} + }$$

$$= \sqrt{\frac{1}{2} \left[\frac{t^3}{3} \Big|_0^1 + t \Big|_1^2 \right]} = \sqrt{\frac{1}{2} \left[\left(\frac{1}{3} - 0\right) + (2 - 1) \right]}$$

$$= \sqrt{\frac{1}{2} \left(\frac{1}{3} + 1 \right)}$$

$$I_{rms} = \underline{0.816}$$

* Resistor (R) - $V_{\text{eff}} i(t) \cdot R$ $v(t) = i(t) \cdot R$ $W_R = \int_{t_1}^{t_2} i^2(t) \cdot R \cdot dt$

Q)

i) Energy $W_R = R \int_{t_1}^{t_2} i^2(t) dt$ $P(t) = i^2(t) \cdot R = \frac{V^2(t)}{R}$

$I(t) = I_m \sin \omega t$ $t > 0$

$$\begin{aligned} W_R &= R \int_{t_1}^{t_2} I_m^2 \sin^2 \omega t \cdot dt \\ &= I_m^2 R \int_{t_1}^{t_2} \left(\frac{1 - \cos 2\omega t}{2} \right) dt \\ &= \frac{I_m^2 R}{2} \int_{t_1}^{t_2} (1 - \cos 2\omega t) dt \\ &= \frac{I_m^2 R}{2} \left[t \Big|_0^{t_2} + \frac{\sin 2\omega t}{2\omega} \Big|_0^{t_2} \right] \end{aligned}$$

$$W_R = \frac{I_m^2 R}{2} \left[t - \frac{\sin 2\omega t}{2\omega} \right]$$

Avg Energy and Power $[0 \text{ to } T]$ - one cycle

$$\begin{aligned} \Delta W_R &= I_m R \frac{2}{2} \int_0^T \left(t - \frac{\sin 2\omega t}{2\omega} \right) dt \\ &= \frac{I_m^2 R}{2} \end{aligned}$$

$$\begin{aligned} \Delta W_R &= \frac{I_m^2 R}{2} \int_0^T (1 - \cos 2\omega t) \cdot dt \\ &= \frac{I_m^2 R}{2} \left[t \Big|_0^T + \frac{\sin 2\omega t}{2\omega} \Big|_0^T \right] \end{aligned}$$

$$\Delta W_R = \frac{I_m^2 R \cdot T}{2}$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{2}} \quad V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$\begin{aligned} P(t) &= I_m^2 \sin^2 \omega t \cdot R \\ &= I_m^2 R \left[\frac{1 - \cos 2\omega t}{2} \right] \end{aligned}$$

$$P(t) = \frac{I_m^2 R}{2} [1 - \cos 2\omega t]$$

one cycle ($0 \text{ to } T$)

$$\begin{aligned} P_{\text{av}} &= \frac{I_m^2 R}{2} \int_0^T (1 - \cos 2\omega t) dt \\ &= \frac{I_m^2 R}{2} \cdot \frac{NT}{2} \end{aligned}$$

$$\begin{aligned} P_{\text{av}} &= \frac{1}{NT} \int_0^{NT} \frac{I_m^2 R}{2} (1 - \cos 2\omega t) dt \\ &= \frac{I_m^2 R \cdot NT}{T^2} \end{aligned}$$

$$P_{\text{av}} = \frac{I_m^2 R}{2}$$

Periodic - Non-Sinusoidal

$$P_{\text{av}} = \frac{1}{T} \int_{t_0}^{t_0+T} R i^2(t) \cdot dt$$

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) \cdot dt}$$

$$V_{\text{eff}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V^2(t) \cdot dt}$$

(1) Network shown

$$i(t) = 4 \cos(100\pi t + 10^\circ)$$

$V(f) = 120 \cos(100\pi t - 20^\circ)$ V. find the apparent power & power factor of the load. Determine the element values that form the series connected load

$$\text{i) } \text{pf}_{1/2} \quad \theta_V - \theta_i = -20 - 10 = -30^\circ \quad \text{pf} = \cos(\theta_V - \theta_i) = \cos(-30^\circ) = \frac{\sqrt{3}}{2}$$

(ii)

$$\text{ii) } S = V_{\text{rms}} I_{\text{rms}} L \theta_V - \theta_i$$

$$= \frac{120}{\sqrt{2}} \cdot \frac{4}{\sqrt{2}} L^{-20-10}$$

$$\boxed{S = 240 L^{-30}}$$

$$\boxed{S = 207.84 + j120} \quad \checkmark$$

$\uparrow P_Av$

$\uparrow Q$

θ is $(-)$ ve \therefore Reactance is ~~+~~ capacitive in nature

$$Z = \frac{V}{I} = \frac{120 L^{-30}}{4 L^{10}} \neq \frac{V_m}{I_m} L \theta_V - \theta_i = \frac{V_{\text{rms}}}{I_{\text{rms}}} L \theta_V - \theta_i \\ = |Z| L \theta_V - \theta_i$$

$$Z = \frac{V_m L \theta_V}{I_m L \theta_i} = \frac{120}{4} L^{-20-10} = 30 L^{-30} \\ = 25.98 - j15\Omega$$

$$= 120^\circ$$

$$R \neq C/L$$


$$\frac{1}{2\pi f C} = 15 \quad X_C = -j15$$

$$X_C = -15 \quad \frac{1}{2\pi f C} = -15$$

$$C = \left(\frac{1}{2\pi f 15} \right) = \frac{1}{100\pi \times 15}$$

$$2\pi f = 100\pi$$

(2)

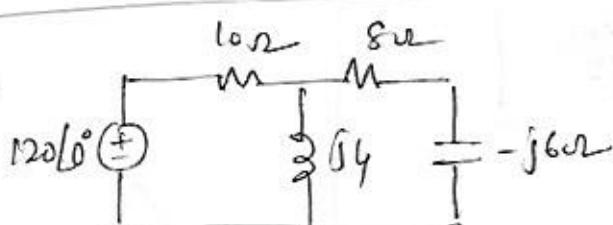

$$\text{pf} =$$

$$Z = \frac{(8-j6) \times j4}{8-2j} + 10$$

$$\boxed{Z = 11.88 + j0.547 \Omega}$$

$$\text{Par} = \text{Vrms} I_{\text{rms}} \cos \theta = 1.062 \text{ kW}$$

$$I = 8.846 - j3.328$$

$$= 9.451 L - 20.58^\circ$$

I lags V

$$\theta_V - \theta_i = 0 - (-20) = 20^\circ$$

$$|\cos(20)| = 0.939$$

$$P_{av} = 60\sqrt{2} \times 6.68 \quad \cancel{\text{Vrms Irons. cos}\theta}$$

$$= 60\sqrt{2} \times 6.68 \times (1/0.889) \times 0.939 = \underline{\underline{63.27}}$$

$$P_{av} = V_{rms} I_{rms} \cos\theta$$


$$P_{av} = \cancel{60\sqrt{2}} 120 \times 9.45 \times 0.939$$

$$= 1064.8 \text{ watts} = \underline{\underline{1.064 \text{ kW}}}$$

$$\frac{\sqrt{2}}{2}$$

$$\underline{\underline{1.064 \text{ kW}}}$$

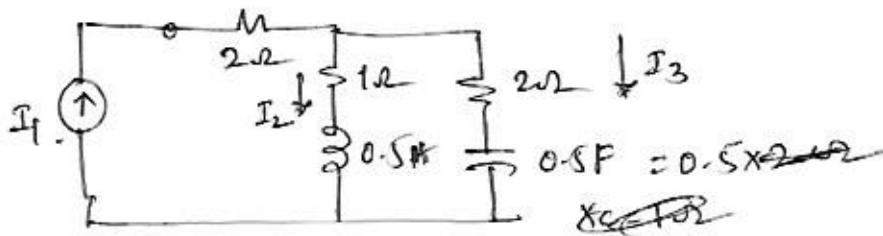- (3) The network shown, current drawn by source is
 $i_1 = 5\sqrt{2} \sin 2t$ and is steady state. find P_{av} & Q



$$I_1 = 5\sqrt{2} \sin 2t$$

$$X_L = 0.5 \times \omega = 0.5 \times 2 = 1$$

$$Z = 2 + j0.333 = 2 + j\frac{1}{3}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2 \times 0.5} = 1$$

$$P_{av} = V_{rms} I_{rms} \cos\theta = 3 + 0.333j$$

$$= I_{rms}^2 |Z| \cos\theta.$$

$$= I_{rms}^2 R.$$

$$P_{av} = I_{rms}^2 R = \left(\frac{5\sqrt{2}}{\sqrt{2}}\right)^2 \times 3 = 5^2 \times 3 = 75 \text{ W.}$$

$$Q = I_{rms}^2 \text{Im}(Z) = 5^2 \times (0.333) = 8.3325$$

$$= \frac{25}{3}$$

$$\boxed{S = P_{av} + jQ = 75 + j8.333} \quad | \quad |S| = \underline{\underline{75.4}}$$

~~$\text{V}_o = V_{rms} I_{rms}$~~

~~$P_{av} = V_{rms} I_{rms} \cos(0) = V_{rms} I_{rms}$~~

~~$\frac{75}{I_{rms}}$~~

~~$|S|$~~

~~$|S| = V_{rms} I_{rms} / 0$~~

~~$75.4 = V_{rms} I_{rms}$~~

~~$I_{rms} = \frac{75.4}{5} = \underline{\underline{15}}$~~

DATE


$$S = \sum_{j=1}^J V_j I_j^*$$

$$V = \sqrt{m} |V| \quad I = \sqrt{n} |I|$$

~~Impedance: V_m / I_n~~ [Doubts]

Tellegen's theorem:

- This theorem is applicable to all types of networks containing
 - Both active and passive elements
 - Linear or non linear and
 - Sources may be time-varying (or) time invariant.
- It states that the summation of all instantaneous or complex powers delivered by the sources and absorbed by the passive elements of the network is zero.
- Resistors present in the net absorb and dissipate power, whereas capacitor and inductor store power in them.

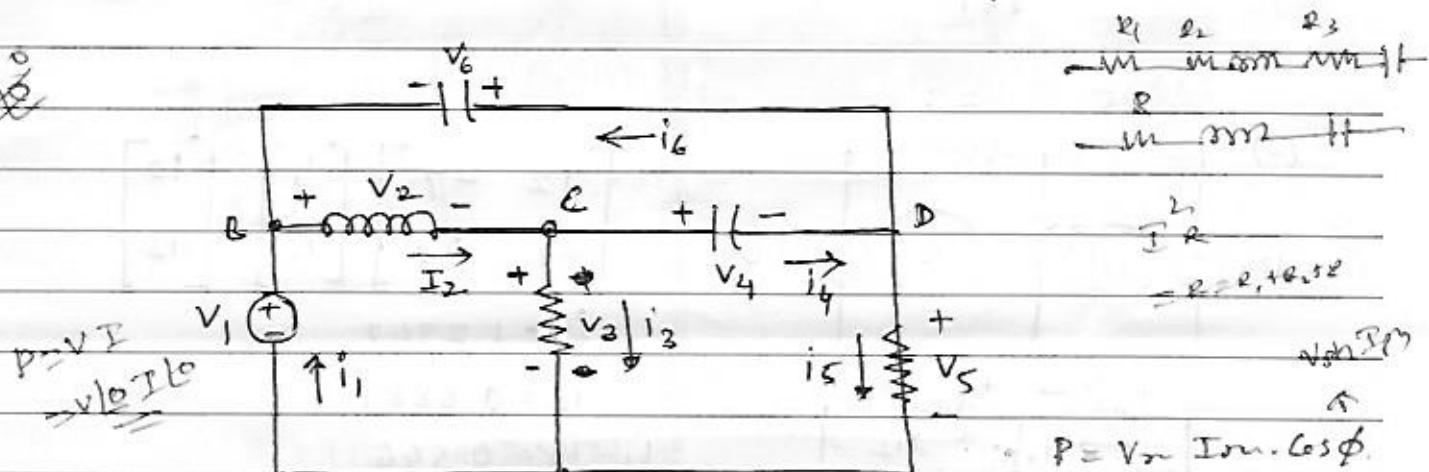

The arbitrarily chosen voltages and currents satisfy eq²

$$\sum_{k=1}^6 V_k i_k = 0 \quad (1)$$

If Kirchhoff's voltage and current laws have been satisfied.

Let us complete the following table for above circuit and verify

	1	2	3	4	5	6	Tellegen's thm
V_k	4	2	—	3	—	—	
I_k	2	2	4	—	—	—	
P_k							$\Sigma P_k = ?$

Using KVL @ loop ABCA', ACDA', ABDA

$$@ ABCA': -V_1 + V_2 + V_3 = 0 \quad \therefore V_3 = V_1 - V_2 = 4 - 2 = 2V$$

$$@ ACDA': -V_3 + V_4 + V_5 = 0 \quad \therefore V_5 = V_3 - V_4 = 2 - 3 = -1V$$

$$@ ABDA': -V_1 - V_6 + V_5 = 0 \quad V_6 = -V_1 + V_5 = -4 - 1 = -5V$$

$V_m \cos \theta \quad \text{if } V_m \text{ is real}$

Using KCL, @ node B, C, and D


$$@ \text{node B} : i_6 = i_1 + i_2 \therefore i_6 = 2+2=4 \text{ A}$$

$$@ \text{node C} \therefore i_2 = i_3 + i_4 \quad i_4 = i_2 - i_3 = 2-4 = -2 \text{ A}$$

$$@ \text{node D} : i_4 = i_5 + i_6 \quad i_5 = i_4 - i_6 = -2-4 = -6 \text{ A}$$

$k \rightarrow$	1	2	3	4	5	6
V_k	4	2	2	3	-1	-5
I_k	2	2	4	-2	-6	4
P_k	8	4	8	-6	6	-20
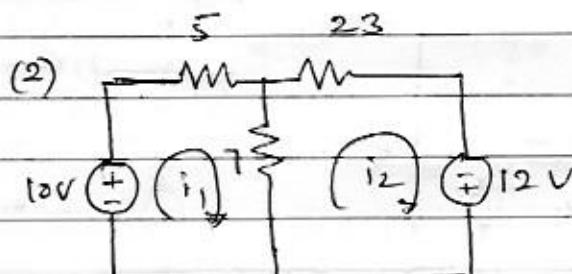
$$\sum_{k=1}^6 V_k I_k = 8+4+8-6+6-20 = 26-26 = 0$$



$$\begin{bmatrix} 12 & -7 \\ -7 & 30 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 12 \end{bmatrix}$$

$$i_1 = 1.2347$$

$$i_2 = 0.6881$$


$$i_1 - i_2 = 0.546$$

$$P_k = P_{\text{generated}} + P_{\text{absorbed}}$$

$$= (10 \times 1.2347) + (12 \times 0.6881)$$

$$+ [-5 \times 1.2347 + 23 \times 0.6881 - 7 \times 0.546]$$

$$= 20.59 - 20.59 = 0$$

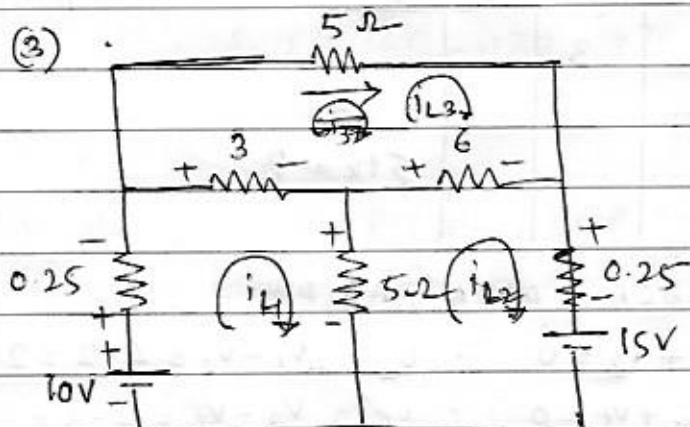

$$\begin{bmatrix} 8.25 & -5 & -3 \\ -5 & 11.25 & -6 \\ -3 & -6 & 14 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ -15 \\ 0 \end{bmatrix}$$


$$i_1 = -0.2829$$

$$i_2 = -1.9333$$

$$i_3 = -0.8891$$

$$i_{3,2} = i_1 - i_3 = 0.6062$$

DATE

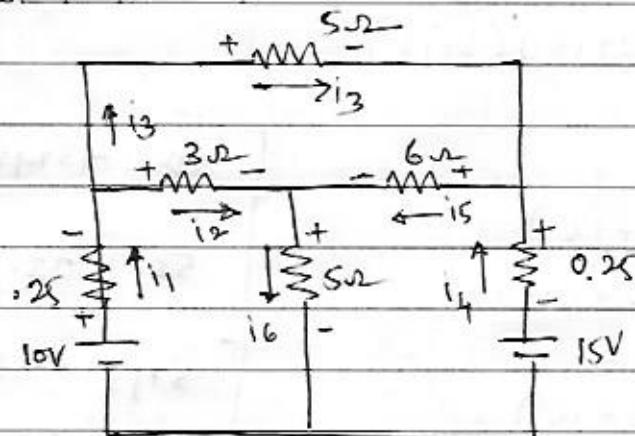

$$i_1 = -0.2829$$

$$i_2 = i_{L1} - i_{L3}$$


$$i_3 = i_{L3} = -0.8891$$

$$i_4 = -i_{L2} = +1.9333$$

$$i_5 = i_{L3} - i_{L2} = 1.0442$$

$$i_6 = i_{L1} - i_{L2} = 1.6504.$$

(OR)

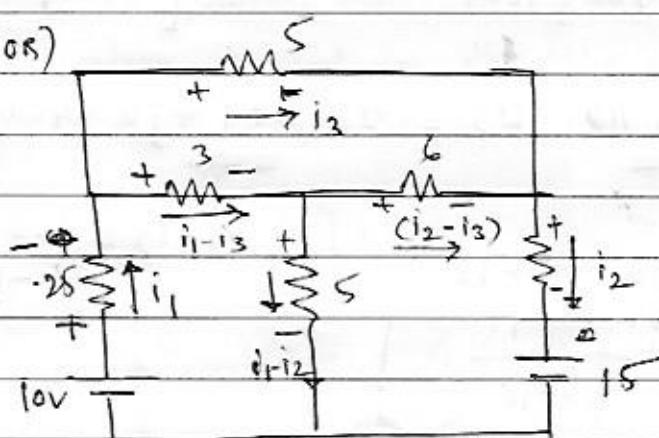

$$i_1 - i_3 = 0.6062$$

$$i_2 - i_3 = -1.6503 + 1.0442$$

$$i_1 - i_2 = 1.6503 -$$

$$P_d = -0.06323, \angle 3.1325$$

$$0.09186 + 3.271 +$$

$$P_{del} = 0.0200 + 1.1024 + 13.6175 + 6.54 + 0.9344 + 3.952$$

$$= 26.166 \cancel{+ 2.829} = \underline{\underline{28.995}} \quad .$$

$$\underline{\underline{P_{del}}} = \underline{\underline{2.829}} + \underline{\underline{28.995}} - \underline{\underline{2.829}} = \underline{\underline{26.170}}$$

by Src

Pd = Pabs Pdelivered = Pabsorbed



for the ckt shown, verify
telegen's thm

$\begin{array}{c} 2 \\ \text{---} \\ \\ \text{---} \\ 30 \\ \\ \text{---} \\ \text{---} \end{array}$	$\begin{array}{c} -j8 \\ \\ \text{---} \\ \\ \text{---} \\ i_1 \\ \\ \text{---} \\ i_2 \\ \\ \text{---} \\ j5 \\ \\ \text{---} \\ \text{---} \end{array}$	$Z = \frac{1}{R} + j\omega C$ $= \frac{1}{2} + j5$ $= 5.31 \angle 76.6^\circ$
$P = \frac{1}{2} R$	$i_1 = 50 \angle 0^\circ$	$\begin{bmatrix} 5+j5 & -(3+j5) \\ -(3+j5) & 23-j3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 50 \\ 50 \end{bmatrix}$

DATE

$$\Delta = (5+j5) \times (33-j3) - (3+j5)(3+j5)$$

$$\Delta = 196 + j120$$

$$50 \times (33-j3) + 50(3+j5) \\ = 1800 + 100j$$

$$\begin{bmatrix} 50 & -(3+j5) \\ 50 & 33-j3 \end{bmatrix}$$


$$50 \times (5+j5) + 50(3+j5) \\ = 400 + 500j$$

$$\begin{bmatrix} 5+j5 & 50 \\ -(3+j5) & 50 \end{bmatrix}$$

$$I_1 = \underline{6.9069 - j3.718} \quad I_2 = \underline{2.6204 + j0.9466}$$

$$i_1 - i_2 = 4.2865$$

$$-j4.6644$$

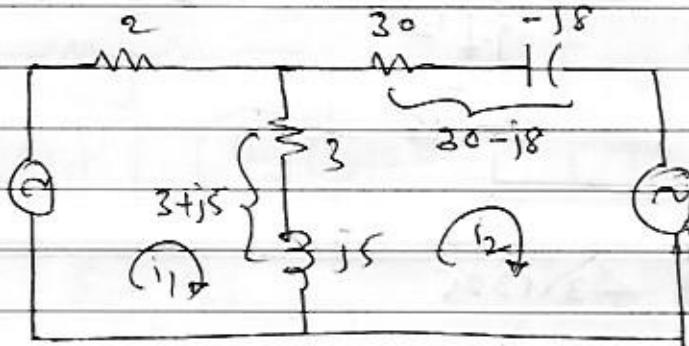

$$P_{ab} = (67.763 - j102.719) + (189.794 - j136.890) \\ + 218.80 + j101.064 \\ = (476.357 - j138.544)$$

$$P_{del} = (345.345 + j185.9) + (131.02 + j7.33j) \\ = (476.365 - j138.57)$$

$$P_{ab} - P_{del} = \boxed{124.833 - j345.625} \text{ (Ans)}$$