

DATE

- \* Power factor is the cosine of  $\angle \theta$  of impedance
- \* Power factor is also the cosine of the angle between  $V$  &  $I$

$$E_v = V_m \sin \omega t \quad V = V_m \sin \omega t$$

$$I = I_m \sin(\omega t + \theta) \quad \text{leads } V_{\parallel}$$

If  $I$  leads  $V$ , power factor is leading

 $P_6$ 18<sup>th</sup> Oct '19

$$Z = |Z|/\theta$$

$$I = V / Z$$

$$Z \angle \theta$$

i) If ' $\theta$ ' is -ve

$$\frac{I}{V} = \frac{V / Z}{1 \angle -\theta} = \frac{V / \theta}{Z} \Rightarrow I \text{ leads } V \rightarrow \text{reactance is capacitive}$$

ii) If ' $\theta$ ' is +ve  $\rightarrow I$  lags  $V \rightarrow$  reactance is Inductive.

- Let  $V = V_m \sin \omega t$ . If pf is leading,  $I = I_m \sin(\omega t + \theta)$   
and if the pf is lagging  $I = I_m \sin(\omega t - \theta)$

## Auxiliary Complex Power

$$V = V_m \angle \theta_v = V_m \sin(\omega t + \theta_v)$$

$$I = I_m \angle \theta_i = I_m \sin(\omega t + \theta_i)$$

$$Z = \frac{V}{I} = \frac{V_m \angle \theta_v}{I_m \angle \theta_i} = \frac{V_m}{I_m} \underbrace{\angle (\theta_v - \theta_i)}_{\theta}$$

$$= \frac{V_m / \sqrt{2}}{I_m / \sqrt{2}} \angle (\theta_v - \theta_i)$$

$$= \frac{V_{rms}}{I_{rms}} \angle (\theta_v - \theta_i) = |Z| / \theta$$

DATE

$$P_{av} = \frac{V_m I_m}{2} \cos(\theta)$$

$$S = \frac{1}{2} V_m | \theta_v - \theta_i | \times I_m | \theta_v - \theta_i |$$

$$= V_{rms} I_{rms} / \theta_v - \theta_i = V_{rms} I_{rms}^*$$

$$S = V_{rms} I_{rms} \cos |\theta_v - \theta_i| + j V_{rms} I_{rms} \sin |\theta_v - \theta_i|$$

real power (Pav)


reactive power (VAR)

Idle power : It absorbs energy


volt ampere reactive.

$$S = P_{av} + jQ$$


- If the reactive power is -ve, power factor angle is negative, power factor is leading & the reactance is capacitive in nature
- If the reactive power is positive, power factor angle is +ve, pf is lagging & the reactance is inductive in nature.

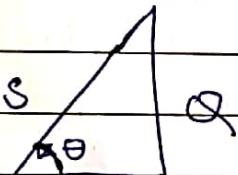APPARENT POWER :  $|S| = V_{rms} I_{rms}$ .


power triangle

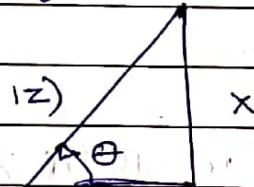

Impedance triangle

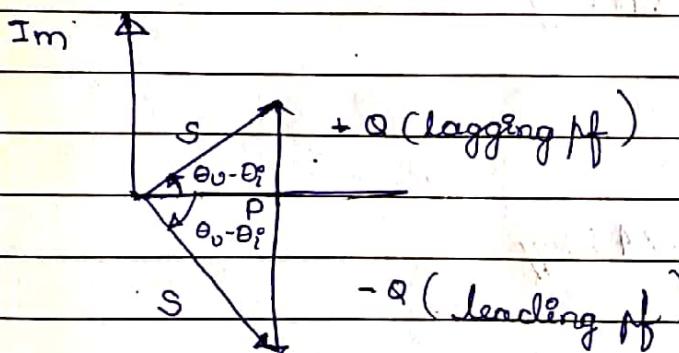

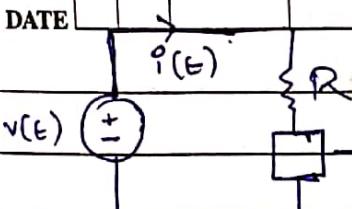- 1) A series connected load draws a current  $i(t) = 4 \cos(100\pi t + 10^\circ)$  A when the applied voltage is  $v(t) = 120 \cos(100\pi t - 20^\circ)$  V. Find the apparent power & the power factor of the load. Determine the element values that form the series connected load



$$(a) \quad V = 120 \angle -20^\circ$$

$I = 4 \angle 10^\circ \rightarrow$  leads  $V =$  Capacitive

$$Z = \frac{V}{I} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 30 \angle -30^\circ = 25.98 - j15$$

$$\theta = -30^\circ$$

$$\text{Power factor} = \cos(-30^\circ) = \frac{\sqrt{3}}{2} \text{ (Leading)}$$

$$(b) \quad S = V_{rms} I_{rms} / \theta_v - \theta_i$$

$$= \frac{120}{\sqrt{2}} \frac{4}{\sqrt{2}} \angle -30^\circ$$

$$= 240 \angle -30^\circ \text{ VAR} //$$

$$= 207.846 - j120 //$$

$$R = 25.98$$

$$X_C = 15$$

$$\frac{1}{\omega C} = 15 \quad \omega = 100\pi //$$

$$C = 2.122 \times 10^{-4} = 212.2 \text{ nF} //$$

Power dissipated in  $R$


$$I_{rms}^2 \Phi$$

$$= \left( \frac{4}{\sqrt{2}} \right)^2 (25.98) = 207.84 \text{ W} //$$

$$\bullet (I_{rms})^2 \times 15 \angle -90^\circ$$

$$= 120 \angle -90^\circ$$

$$= 0 - j120$$

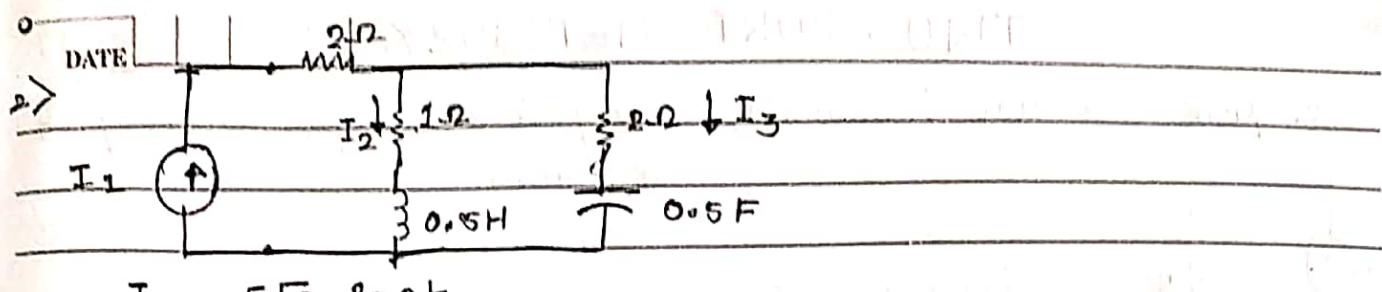

$$\omega = 2$$

$$\text{Impedance of Inductor} = j\omega L = j(2)(0.5) = j\Omega$$

$$\text{Capacitive} = \frac{1}{j\omega C} = \frac{1}{j(2)(0.5)} = -j\Omega/2$$

$$Z = \left[ \frac{1+j}{(1+j)(2-j)} \right] + 2$$

$$= \frac{2-j+2j-j^2}{3} = \frac{3+j}{3} = \frac{1+j}{3} = 1 + 0.33j$$

$$= 3.018 \angle 6.34^\circ$$


$$P_{av} = I_{rms}^2 Z \cos(6.34^\circ)$$

$$= \left(\frac{5\sqrt{2}}{\sqrt{2}}\right)^2 \times 3.018 \times \cos(6.34^\circ)$$

$$= 74.99$$

$$\approx 75 \text{ W}$$
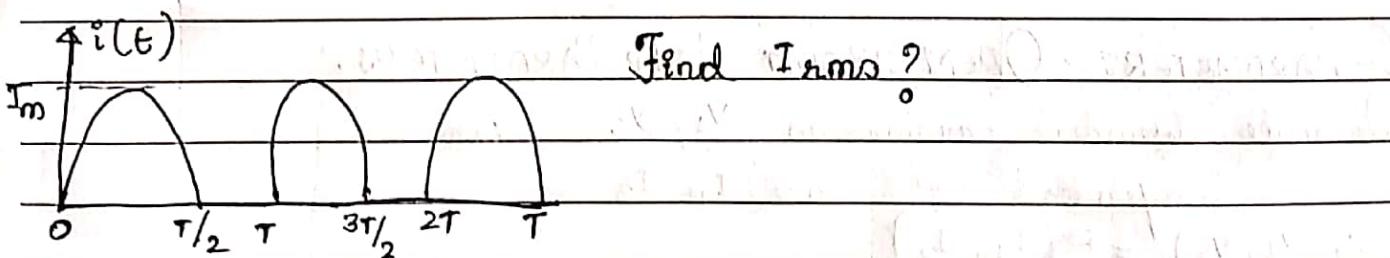
$$Q = 5^2 \times 3.018 \times \sin(6.34^\circ) = 8.35 \text{ VAR}$$



$$I_{rms} = \left[ \frac{1}{T} \int_0^{T/2} I_m^2 \sin^2 \omega t dt \right]^{1/2}$$

$$= \frac{I_m^2}{T} \left[ \frac{1 - \cos 2\omega t}{2} dt \right]^{1/2} = \frac{I_m^2}{2T} \left[ \left( \frac{T}{2} \right) - \frac{\sin 2\omega b}{2} \right]$$



$$= \frac{I_m^2}{2T} \times \frac{T}{2} = \left( \frac{I_m^2}{4} \right)^{1/2} = \frac{I_m}{2}$$

DATE
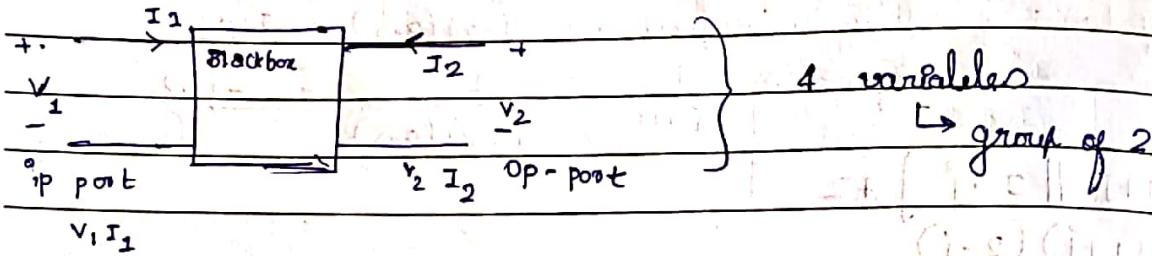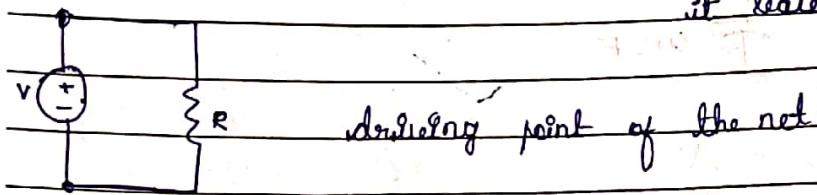
## TWO-PORT NETWORKS:


2<sup>st</sup>  
Oct'19

2 port  $\rightarrow$  two terminals, one port it enters another port it leaves.



\* Convention (Two port network) current goes in

Ex. in

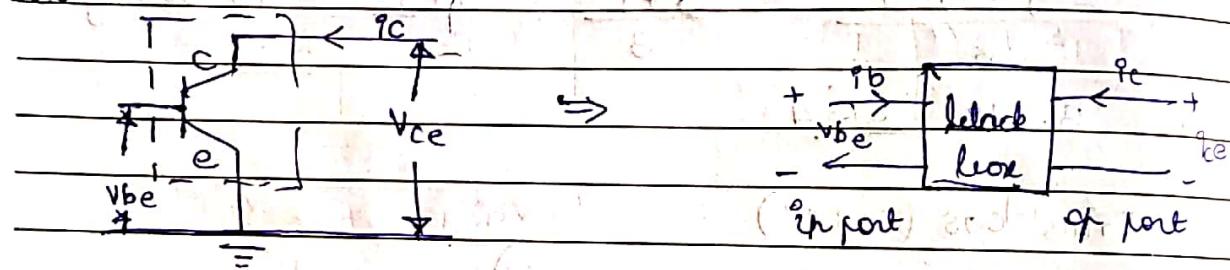4 Variables  $v_1, i_1, v_2, i_2$ 

\* If we make two of each group, four sets will be formed where one set is dependent variable & other set is independent variables.

\* Out of all combinations, 6 combinations we will consider.

### ① Z-PARAMETERS: OPEN CIRCUIT IMP PARAMETERS.

We make dependent variables as  $v_1, v_2$  then

Independent " are  $i_1, i_2$

$$\therefore (v_1, v_2) = f(i_1, i_2)$$

$$v_1 = z_{11} i_1 + z_{12} i_2 \rightarrow ①$$

$$v_2 = z_{21} i_1 + z_{22} i_2 \rightarrow ②$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \rightarrow ③$$

$$\begin{bmatrix} z_{11} = v_1 \\ i_1 = 0 \\ i_2 = 0 \end{bmatrix}$$

Driving point input impedance with op  
open ckt

DATE

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} (\Omega) \rightarrow \text{Forward transfer impedance with op OC}$$


- \* If denominator is input port variable  $\rightarrow$  Forward
- \* If it is output port set by the  $I_p$   $\rightarrow$  Transfer (one input & one output) variable of Impedance.

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} (\Omega) \rightarrow \text{Reverse transfer impedance with ip OC}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} (\Omega) \rightarrow \text{Driving point output impedance with } I_p \text{ OC.}$$


- \* Represent with dependent source which contain both input port and output port also there, otherwise represent it as zero.

## 2 - GENERATOR EQUIVALENT CIRCUIT

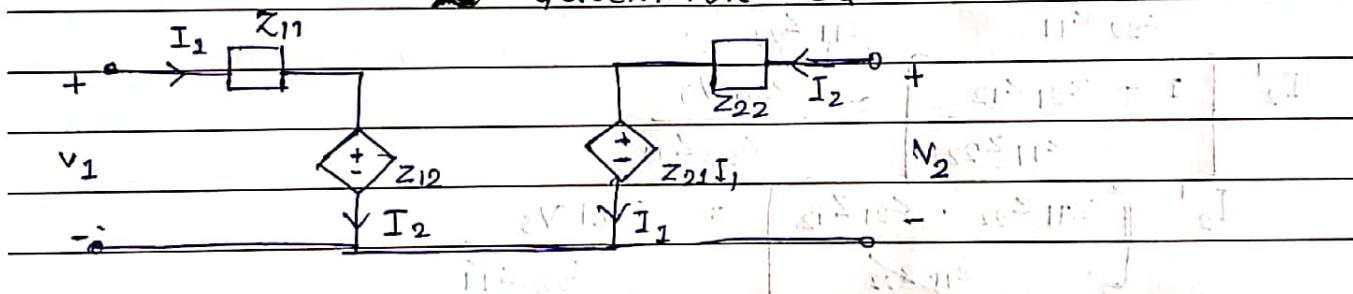

## RECIPROCAL & SYMMETRICAL NETWORKS

### 1.1) RECIPROCAL NETWORKS

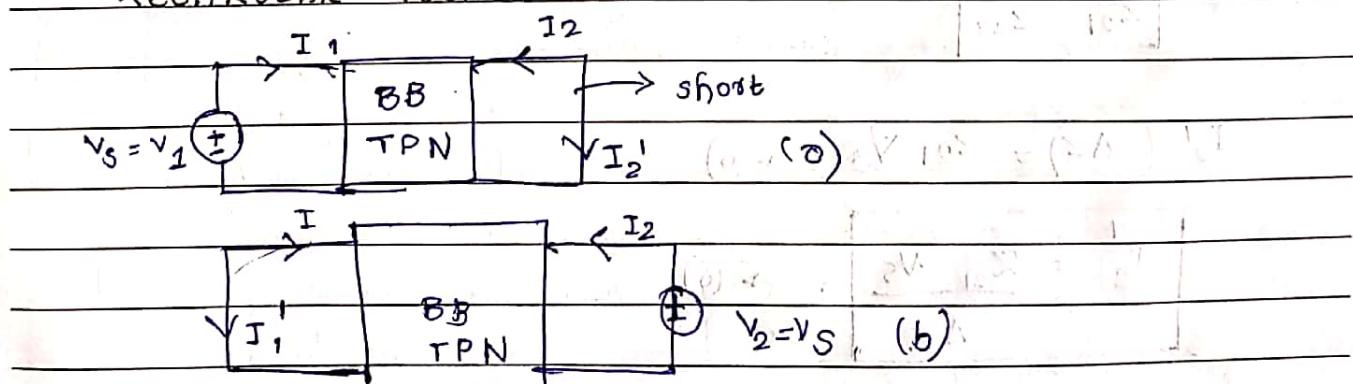

$$I_1' = I_2'$$

DATE

Consider (a) network

$$V_1 = V_S$$

$$V_2 = 0$$

$$I_1 = I_1$$

$$I_2 = -I_1'$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow ①$$

$$V_S = Z_{11} I_1 + Z_{12} (-I_2)' \rightarrow ④$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow ②$$

$$0 = Z_{21} I_1 + Z_{22} (-I_2)'$$

$$Z_{22} I_2' = Z_{22} I_1$$

from ④

$$I_2' = Z_{21} I_1$$

$$Z_{22}$$

$$I_1 = \frac{V_S + Z_{12} I_2'}{Z_{11}} \rightarrow ⑤$$

Rule, 5 in 3

$$I_2' = Z_{21} \left[ \frac{V_S + Z_{12} I_2'}{Z_{11}} \right] = Z_{21} \left[ \frac{V_S + Z_{12} I_2'}{Z_{11}} \right]$$

$$Z_{22}$$

$$\Rightarrow Z_{21} V_S + \frac{Z_{21} Z_{12} I_2'}{Z_{11} Z_{22}}$$

$$I_2' \left[ 1 - \frac{Z_{21} Z_{12}}{Z_{11} Z_{22}} \right] = \frac{Z_{21} V_S}{Z_{22} Z_{11}}$$

$$I_2' \left[ \frac{Z_{11} Z_{22} - Z_{21} Z_{12}}{Z_{11} Z_{22}} \right] = \frac{Z_{21} V_S}{Z_{22} Z_{11}}$$

Wkt

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \Delta Z = Z_{11} Z_{22} - Z_{12} Z_{21}$$

$$I_2' (\Delta Z) = Z_{21} V_S \rightarrow ⑥$$

$$I_2' = \frac{Z_{21} V_S}{\Delta Z}$$

$$\rightarrow ⑥$$

Consider (b) network

$$V_2 = V_S ; V_1 = 0$$

$$0 = -Z_{11} I_1' + Z_{12} I_2$$

$$I_1 = -I_1' ; I_2 = I_2$$

$$V_S = -Z_{21} I_1' + Z_{22} I_2 \rightarrow 8$$

DATE

$$Z_{12} I_2 = Z_{11} I_1$$

$$I_1' = \frac{Z_{12} I_2}{Z_{11}} \rightarrow \textcircled{7}$$

from (8)

$$I_2 = V_S + \frac{Z_{21} I_1'}{Z_{22}}$$

$$I_1' = \frac{Z_{12}}{Z_{11}} \left[ \frac{V_S + Z_{21} I_1'}{Z_{22}} \right] = \frac{Z_{12} V_S + Z_{12} Z_{21} I_1'}{Z_{11} Z_{22}} \frac{1}{Z_{11} Z_{22}}$$

$$\Rightarrow I_1' \left[ 1 - \frac{Z_{12} Z_{21}}{Z_{11} Z_{22}} \right] = \frac{Z_{12} V_S}{Z_{11} Z_{22}}$$

$$\Rightarrow I_1' \left[ \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{11} Z_{22}} \right] = \frac{Z_{12} V_S}{Z_{11} Z_{22}}$$


$$\Rightarrow I_1' [\Delta Z] = V_S Z_{12}$$

$$\Rightarrow I_1' = \frac{V_S Z_{12}}{\Delta Z} \rightarrow \textcircled{9}$$

$$Z_{12} = Z_{21}$$

$$\Rightarrow I_1' = \frac{V_S Z_{21}}{\Delta Z}$$

$$\Rightarrow I_1' = I_2'$$

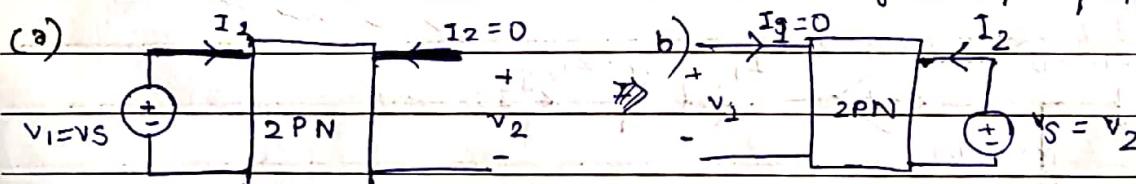1.2) SYMMETRICAL NWS : We can interchange  $\Sigma$  of ports

$$\text{If } \frac{V_S}{I_1} = \frac{V_S}{I_2}$$

$$\text{a) } V_1 = V_S \quad V_2 = V_2$$

$$I_1 = I_1 \quad I_2 = 0$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \Rightarrow V_S = Z_{11} I_1$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \Rightarrow V_2 = Z_{21} I_1$$

$$\frac{V_S}{I_1} = Z_{11} \rightarrow \textcircled{1}$$

DATE

b)  $V_2 = V_S \circ V_1 = V_1$   
 $I_2 = I_1 \circ I_1 = 0$

$\rightarrow V_1 = Z_{12} I_2$

$V_S = Z_{22} I_2$

$V_S = Z_{22}$	$\rightarrow ②$
$I_2$	

Comparing eqno ① & ②  $\Rightarrow Z_{11} = Z_{22}$

### SINGLE GENERATOR EQUIVALENT CIRCUIT:

$V_1 = Z_{11} I_1 + Z_{12} I_2 \rightarrow ①$

$V_2 = Z_{21} I_1 + Z_{22} I_2 \rightarrow ②$

$V_1 = Z_{11} I_1 + Z_{12} I_2 + Z_{12} I_1 - Z_{12} I_1$


$V_1 = Z_{12} (I_1 + I_2) + I_1 (Z_{11} - Z_{12}) = 0 \rightarrow ③$

$V_1 - Z_{12} (I_1 + I_2) - I_1 (Z_{11} - Z_{12}) = 0$


$V_2 = Z_{21} I_1 + Z_{22} I_2 + Z_{12} I_1 - Z_{12} I_1 + Z_{12} I_2 - Z_{12} I_2$

$= Z_{12} (I_1 + I_2) + (Z_{22} - Z_{12}) I_2 + (Z_{21} - Z_{12}) I_1 \rightarrow ④$

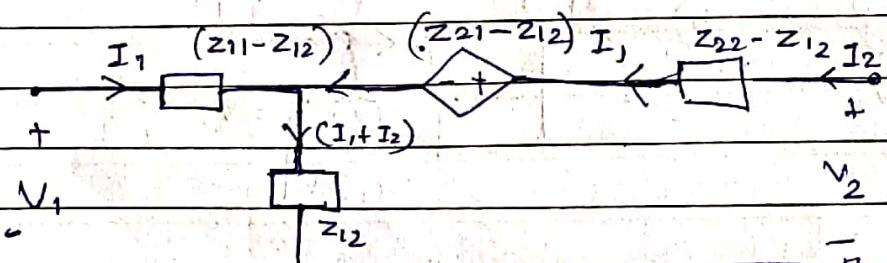$V_2 - Z_{12} (I_1 + I_2) - (Z_{22} - Z_{12}) I_2 - I_1 (Z_{21} - Z_{12}) = 0$



Now of its reciprocal  $Z_{12} = Z_{21}$

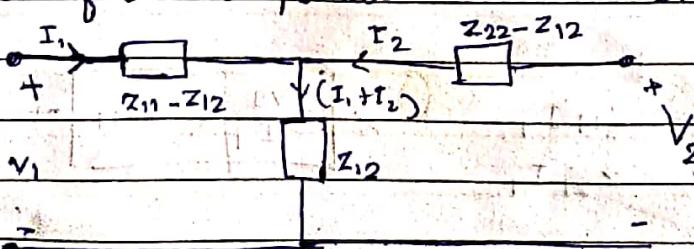

2)  $[Y]$  PARAMETERS : SHORT CIRCUIT ADMITTANCE PARAMETERS.

Dependent Variables  $\rightarrow (I_1, I_2)$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Independent Variables  $\rightarrow (V_1, V_2)$

$$I_2 = Y_{11}V_1 + Y_{12}V_2 \rightarrow (1)$$

$$I_1 = Y_{21}V_1 + Y_{22}V_2 \rightarrow (2)$$

(a) When  $V_2 = 0$

$$\therefore Y_{11} = \frac{I_1}{V_1}, Y_{21} = \frac{I_2}{V_1} \quad (V)(S) \quad \begin{array}{c} I_1 \\ \oplus \\ 2PN \\ \ominus \\ I_2 \end{array} \quad V_1 \quad V_2 = 0$$

1) Driving point  $\varphi_p$  admittance with  $\text{op}$  SC

2) Forward transfer admittance with  $\text{op}$  SC

(b) When  $V_1 = 0$


$$Y_{12} = \frac{I_1}{V_2} = \text{Reverse transfer admittance with } \text{op} \text{ SC}$$

$$Y_{22} = \frac{I_2}{V_2} = \text{Driving point of admittance with } \text{op} \text{ SC}$$

RECIPROCAL  $\Rightarrow Y_{12} = Y_{21}$

SYMMETRICAL  $\Rightarrow Y_{11} = Y_{22}$

### 2 - GENERATOR EQ CKT

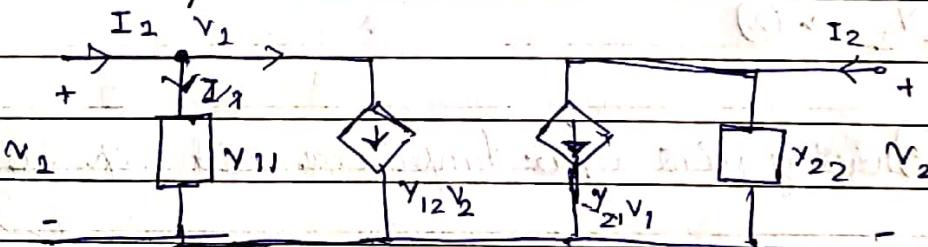


### SINGLE GENERATOR


$$I_1 = Y_{11}V_1 + Y_{12}V_2 + Y_{12}V_1 - Y_{12}V_1$$

$$= -Y_{12}(V_1 - V_2) + (Y_{11} + Y_{12})V_1 \rightarrow (3)$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 + Y_{12}V_1 - Y_{12}V_1 + Y_{12}V_2 - Y_{12}V_2$$
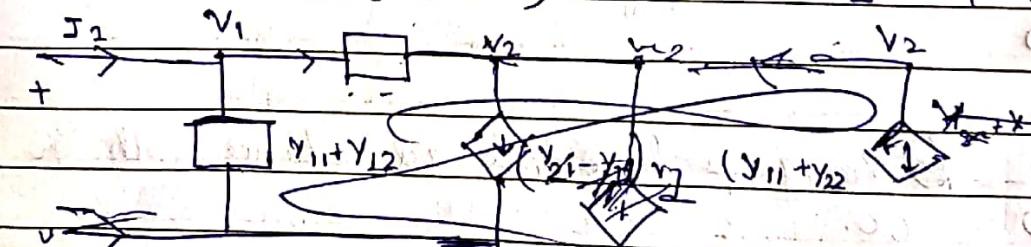
$$= -Y_{12}(V_2 - V_1) + (Y_{22} + Y_{12})V_2 + (Y_{21} - Y_{12})V_1 \rightarrow (4)$$



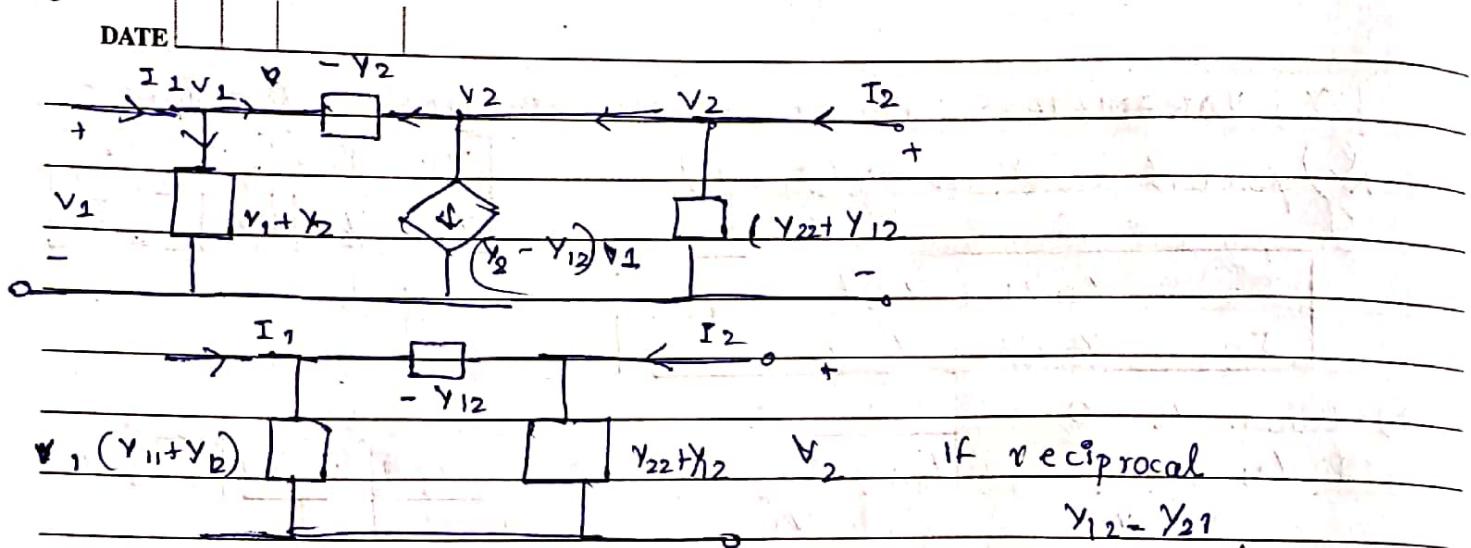

22<sup>nd</sup> Oct '19

### 3) HYBRID [h] PARAMETERS:

Dependent variables : ( $V_1, I_2$ )

Independent " ( $I_1, V_2$ )

$$(V_1, I_2) = f(I_1, V_2)$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11}I_1 + h_{12}V_2 \rightarrow ①$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \rightarrow ②$$

$$h_{11} = \frac{V_1}{I_1} \quad \left. \right|_{V_2=0}$$

Driving point input Impedance with op sc

$$h_{21} = \frac{I_2}{I_1} \quad \left. \right|_{V_2=0}$$

Forward current gain with op sc ( $V_2 = 0$ )

$$h_{12} = \frac{V_1}{V_2} \quad \left. \right|_{I_1=0}$$


Reverse voltage gain in OC

$$h_{22} = \frac{I_2}{V_2} \quad \left. \right|_{I_1=0}$$

Driving point output admittance with ip OC.

DATE

## 2 - Generator equivalent ckt

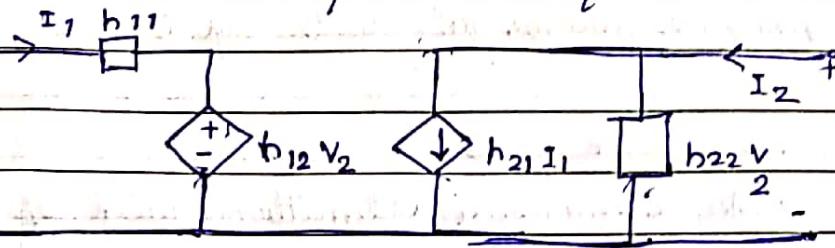

## 1 &gt; (g) PARAMETER [INVERSE h]:

$$(I_1, V_2) = f(V_1, I_2)$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$


$$g_{11} = \frac{I_1}{V_1} \quad \text{Driving point input admittance with op OC}$$

$$g_{12} = \frac{I_1}{I_2} \quad \text{Forward voltage gain with op OC}$$

$$g_{21} = \frac{V_2}{V_1} \quad \text{Reverse current gain with ip SC.}$$

$$g_{22} = \frac{V_2}{I_2} \quad \text{Driving point output impedance with ip SC}$$

## 2 - GENERATOR EQUIVALENT

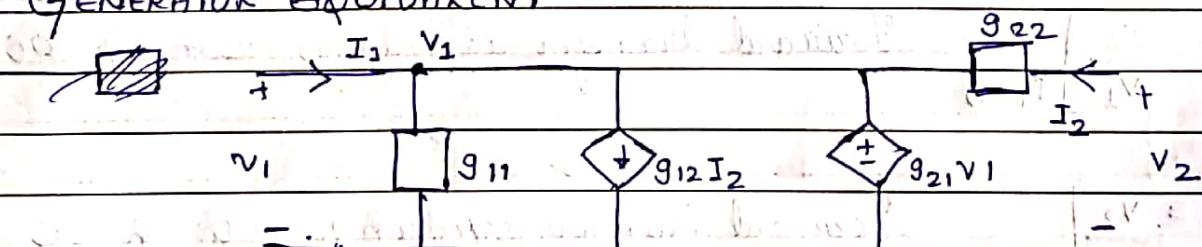

## 3 &gt; TRANSMISSION [T or ABCD] PARAMETERS

$$(V_1, I_1) = f(V_2, I_2)$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

current is going in

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

DATE

$$A = \frac{V_1}{V_2} \quad | \quad I_2 = 0$$

Forward voltage gain with op. OC

$$C_L = \frac{I_1}{V_2} \quad | \quad I_2 = 0$$

Forward transfer admittance with op. OC

$$B = -\frac{V_1}{I_2} \quad | \quad V_2 = 0$$

Forward transfer impedance with op. SC

$$D = -\frac{I_1}{I_2} \quad | \quad V_2 = 0$$

Forward current gain with op. SC

## 6) INVERSE T PARAMETERS

[ T' or A'B'C'D' or abcd parameters )

$$V_2 I_2 = f(V_1, I_1)$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix} \quad \begin{aligned} V_2 &= aV_1 - bI_1 \\ I_2 &= cV_1 - dI_1 \end{aligned}$$

$$a = \frac{V_2}{V_1} \quad | \quad I_1 = 0$$

Forward voltage gain with ip. OC

$$C = \frac{I_2}{V_1} \quad | \quad I_1 = 0$$

Forward transfer admittance with ip. OC

$$-b = \frac{V_2}{I_1} \quad | \quad V_1 = 0$$

Forward transfer impedance with ip. SC

$$-d = \frac{I_2}{I_1} \quad | \quad V_1 = 0$$

Forward current gain with ip. SC

RELATION B/W PARAMETER SETS.

T' in terms of H

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow ①$$

$$V_2 = aV_1 - bI_1$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow ②$$

$$I_2 = cV_1 - dI_1$$

DATE

$$h_{12} V_2 = V_1 - h_{11} I_1$$

$$V_2 = \frac{V_1 - h_{11} I_1}{h_{12}}$$

$$\left[ a = \frac{1}{h_{12}} \quad \text{&} \quad b = \frac{h_{11}}{h_{12}} \right]$$

put  $V_2$  in eqn 2

$$I_2 = h_{21} I_1 + h_{22} \left[ \frac{V_1 - h_{11} I_1}{h_{12}} \right]$$

$$\Rightarrow I_2 = \frac{h_{21} I_1 + h_{22} V_1 - h_{22} h_{11} I_1}{h_{12}}$$

$$I_2 = \left[ \frac{h_{21} - h_{22} h_{11}}{h_{12}} \right] I_1 + \left[ \frac{h_{22}}{h_{12}} \right] V_1$$

$$d = -\left( h_{21} - h_{22} h_{11} \right) \quad \text{&} \quad c = \frac{h_{22}}{h_{12}}$$

$$d = -\left( -\Delta h \right) \quad \text{&} \quad c = \frac{h_{22}}{h_{12}}$$

Z IN TERMS OF Y

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{1}{\Delta Y} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \frac{Y_{22}}{\Delta Y}, \quad Z_{12} = -\frac{Y_{12}}{\Delta Y}, \quad Z_{21} = -\frac{Y_{21}}{\Delta Y}, \quad Z_{22} = \frac{Y_{11}}{\Delta Y}$$

23rd Oct, 19

① Express [y] parameters in terms of [h]

b)

$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow ①$$

$$I_1 = \frac{V_1 - h_{12} V_2}{h_{11}}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow ②$$

$$I_1 = \frac{V_1}{h_{11}} - \frac{h_{12} V_2}{h_{11}}$$

c)

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow ③$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow ④$$

$$Y_{11} = \frac{1}{h_{11}} \quad \text{&} \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

DATE

$$I_2 = h_{21} \left( \frac{v_1 - h_{12} v_2}{h_{11}} \right) + h_{22} v_2$$

$$I_2 = \frac{h_{21} v_1}{h_{11}} - \frac{h_{21} h_{12}}{h_{11}} v_2 + h_{22} v_2$$

$$= \frac{h_{21}}{h_{11}} v_1 + v_2 \left[ \frac{h_{22} - h_{21} h_{12}}{h_{11}} \right]$$

$$\frac{h_{21}}{h_{11}} v_1 + v_2 \left[ \frac{h_{22} h_{11} - h_{21} h_{12}}{h_{11}} \right]$$

$$Y_{21} = \frac{h_{21}}{h_{11}}, \quad Y_{22} = \Delta h$$

Q: Express  $[T]$  in terms of  $[T']$ :

$T'$  <sup>dep</sup>

$T$  <sup>o</sup>

$$\begin{bmatrix} v_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} v_1 \\ -I_1 \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix}$$

ReWriting

$$\begin{bmatrix} v_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} a & -b \\ -c & d \end{bmatrix} \begin{bmatrix} v_1 \\ I_1 \end{bmatrix} \rightarrow \text{Modified } T'$$

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a & -b \\ -c & d \end{bmatrix} \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix}$$


$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = 1 \cdot \begin{bmatrix} d & b \\ c & a \end{bmatrix} \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix} \quad \begin{array}{l} a \neq d \\ \Delta T' \end{array} \quad \begin{array}{l} B = b \\ \Delta T' \end{array}$$

$$c = \frac{c}{\Delta T'} \quad d = \frac{d}{\Delta T'}$$

DATE

## INTERCONNECTION OF 2 PORT NETWORKS:

### 1) CASCADE / TANDEM CONNECTION:

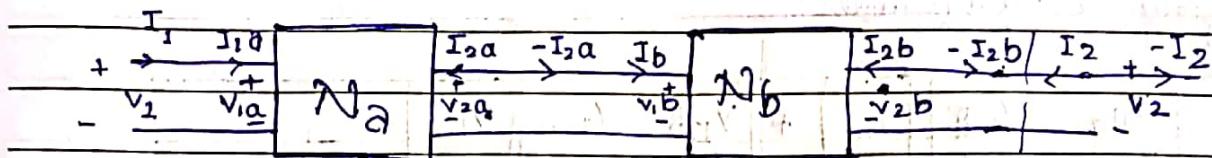

T parameter is helpful for microwave transitions

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix}$$


$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

\* Helpful in finding parameters of a big network by splitting them and lastly multiplication of matrix to be done here.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

### 2) PARALLEL CONNECTION:

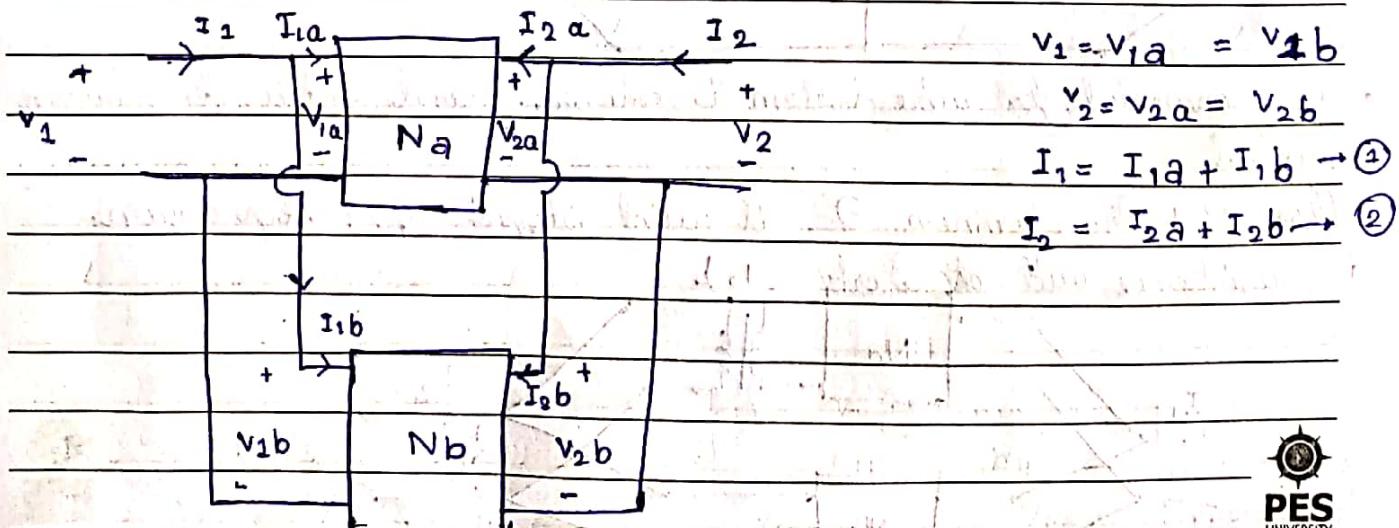

DATE

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} + \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$


applying  $\gamma$ -parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \gamma_{11a} & \gamma_{12a} \\ \gamma_{21a} & \gamma_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} \gamma_{11b} & \gamma_{12b} \\ \gamma_{21b} & \gamma_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \gamma_{11a} + \gamma_{11b} & \gamma_{12a} + \gamma_{12b} \\ \gamma_{21a} + \gamma_{21b} & \gamma_{22a} + \gamma_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

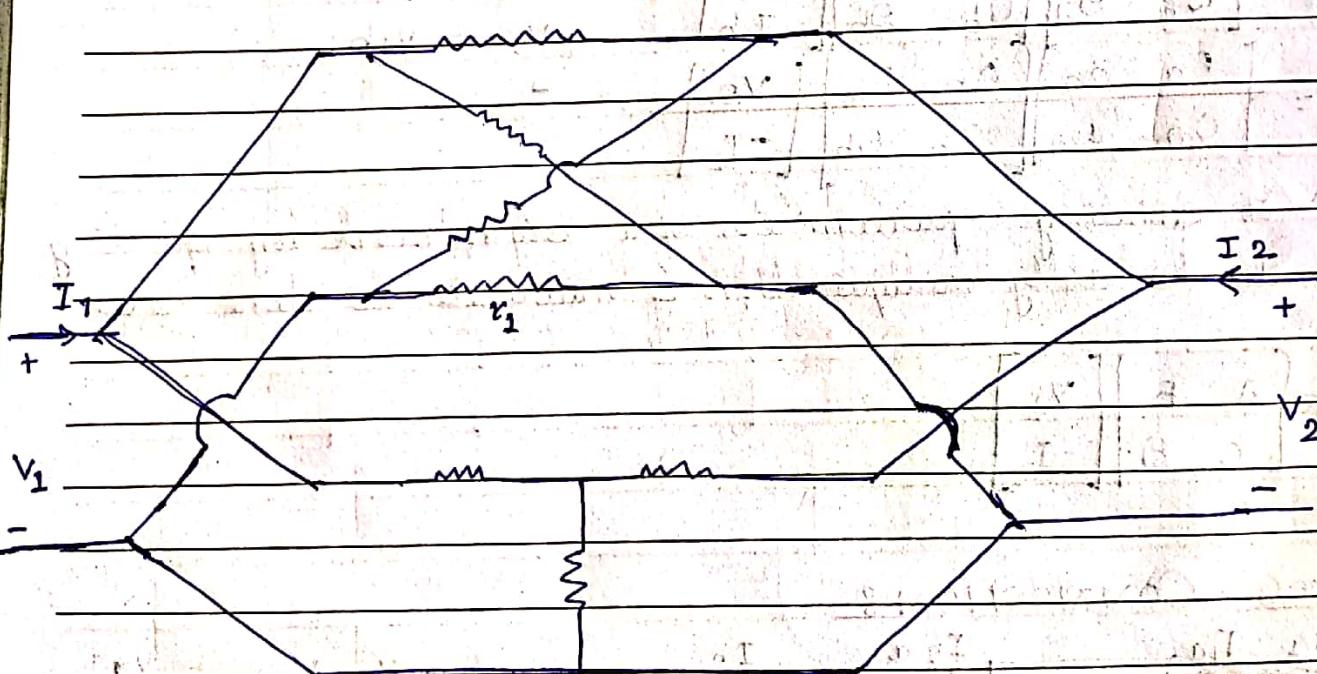\* Everywhere we do addition of the  $\gamma$ -parameters except in Cascade (Multiplication)



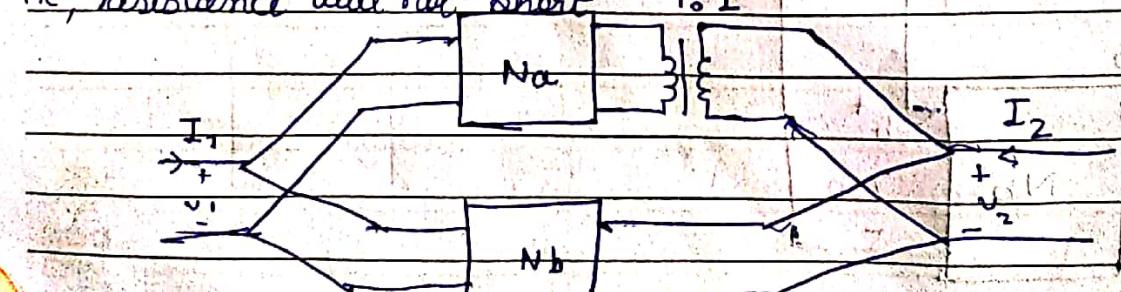- $r_1$  connected to wire bottom is shorted and network remain unaltered.
- Use 1:1 transformers  $\beta$ , it would stepped up / step down i.e., resistance will not short.





DATE


## ISOCATION

1:1

## TRANSFORMER


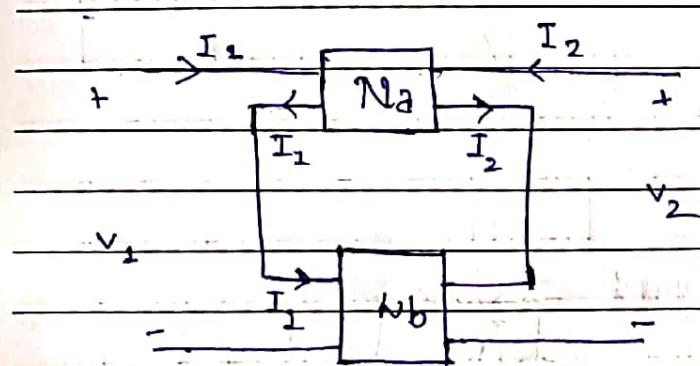
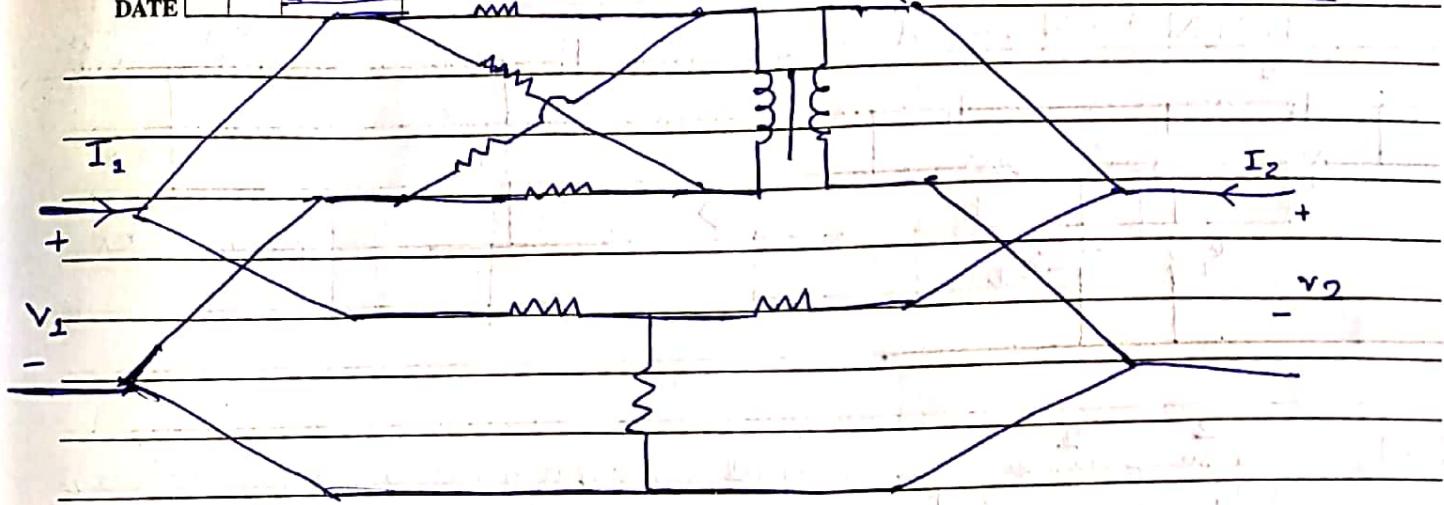


## BRIDGETREE NETWORK

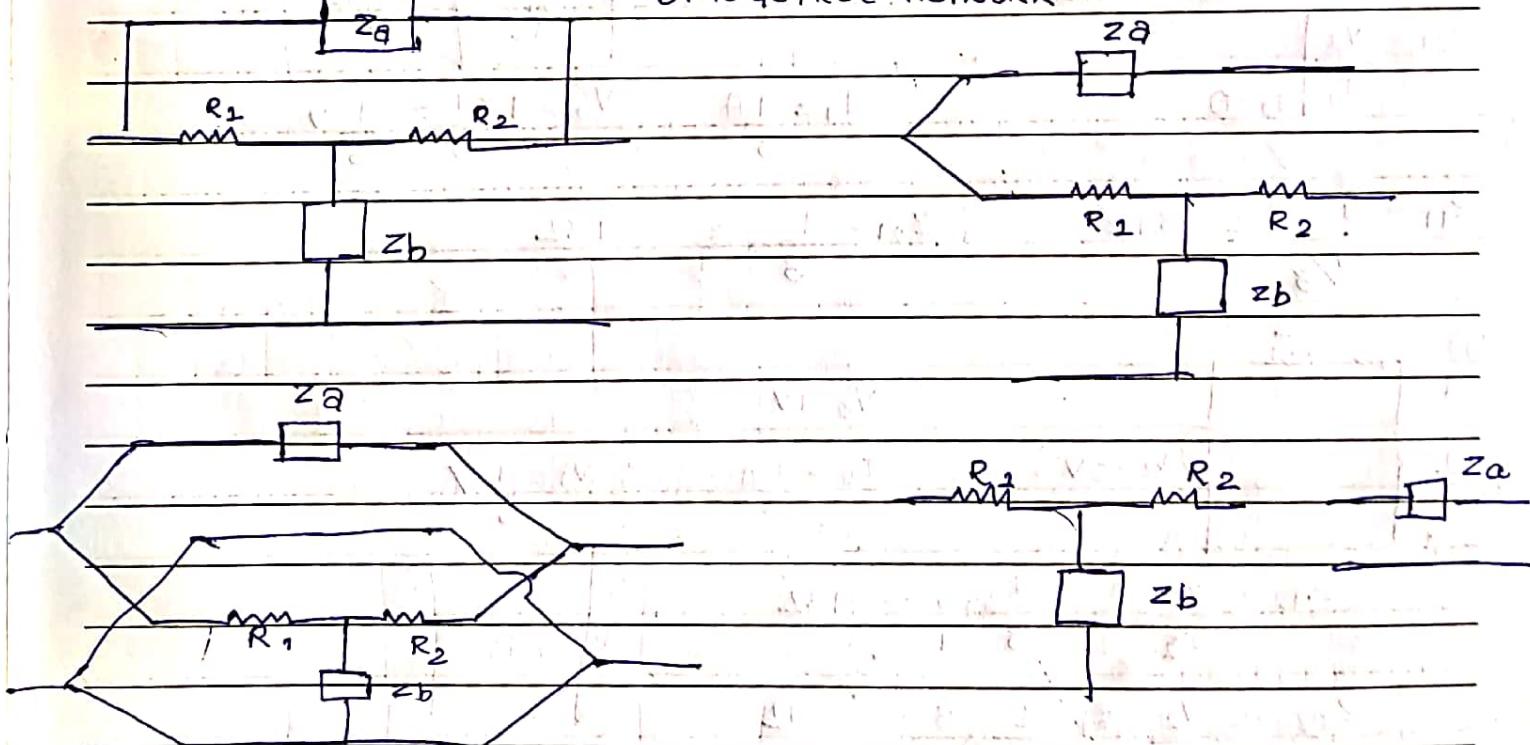

DATE

## TWIN T-NETWORK

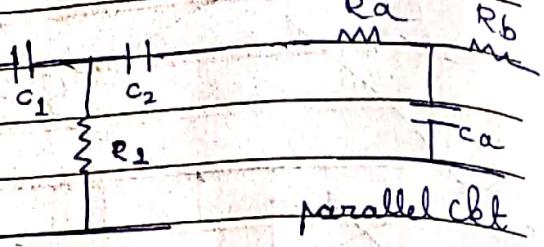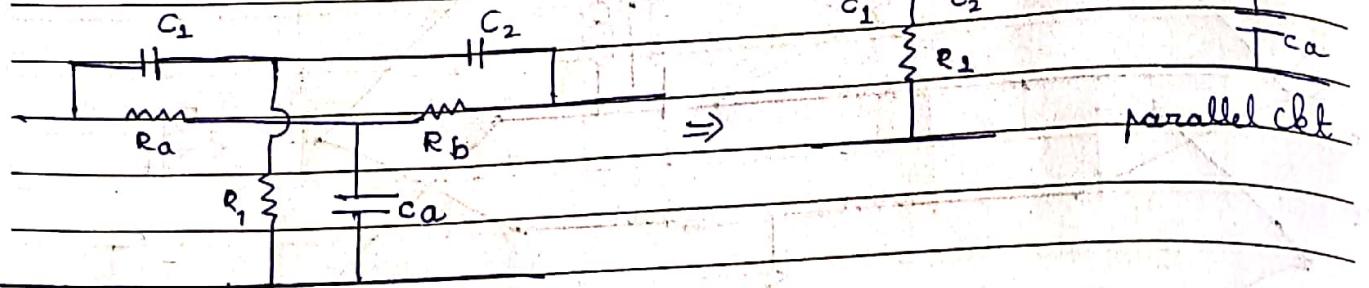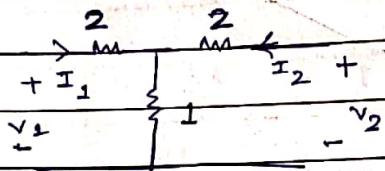Q: 1


Find Z-parameters of this network

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow (1)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow (2)$$

First part:

$$Z_{11} = \frac{V_1}{I_1} \quad |_{I_2=0}$$

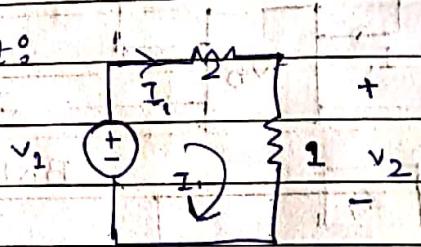

$$Z_{21} = \frac{V_2}{I_1} \quad |_{I_2=0}$$

$$I_1 = \frac{1A}{3} \quad V_2 = 1 \times \frac{1}{3} = \frac{1}{3} V$$

$$Z_{11} = \frac{1}{\frac{1}{3}} = 3 \Omega \quad ; \quad Z_{21} = \frac{1}{3} \times \frac{1}{3} = \frac{1}{9} \Omega$$

b)

$$V_2 = 1V$$

$$I_2 = \frac{1A}{3} \quad ; \quad V_1 = \frac{1}{3} V$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{\frac{1}{3}}{\frac{1}{3}} = 1 \Omega$$

$$Z_{22} = \frac{V_2}{I_2} = \frac{1}{\frac{1}{3}} = 3 \Omega$$


$$[Z] = \begin{bmatrix} 3 & 1 \\ 1 & 3 \end{bmatrix}$$

$$Z_{11} = Z_{22}$$

$$Z_{12} = Z_{21}$$

This network is reciprocal & symmetrical


DATE

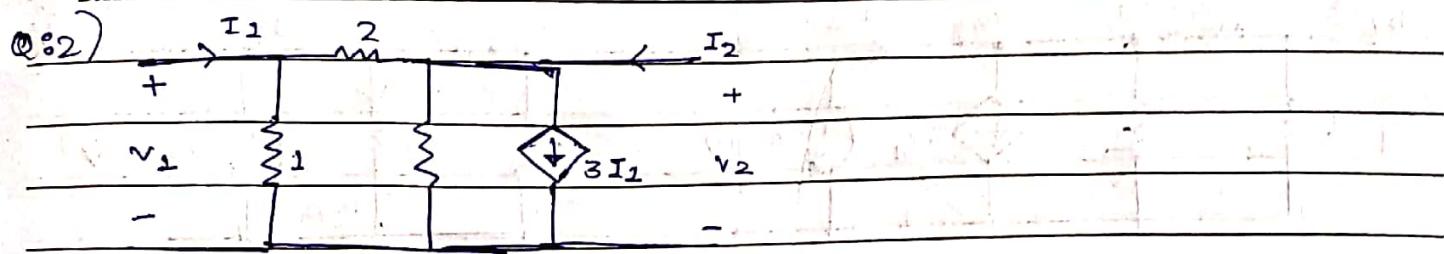

\* Nowhere we can connect the independent sources inside the network  
diff b/w transport network & usual.

- Find  $Z$  &  $Y$ ?

(1)  $Z \approx$  part A:  $I_2 = 0$

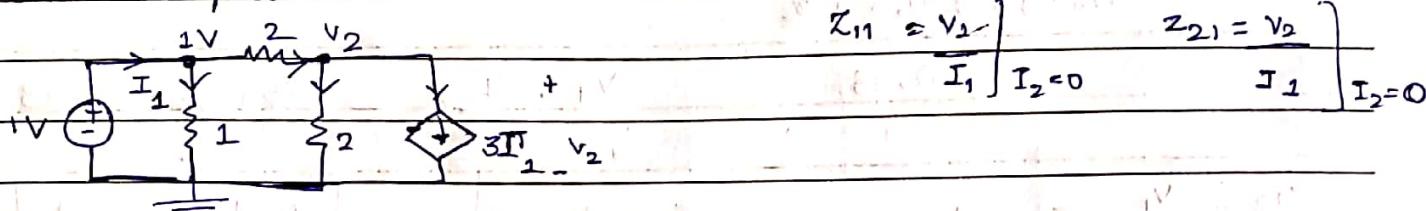

$$\text{apply KCR at node } V_2: \frac{1-V_2}{Z} = \frac{V_2 + 3I_1}{2}$$

$$\frac{V_2 - 1 + V_2}{2} = \frac{1 - V_2}{2} = \frac{V_0 + 1 + 1 - V}{2}$$

$$I_1 = \frac{1 + 1 - V_2}{2}$$

$$\frac{1}{2} \left( \frac{V_1 + V_2 - 1}{2} \right) = \frac{V_1 + 1}{2}$$

$$\frac{V_1}{2} = 1 \quad \Rightarrow \quad V_1 = 2$$

$$\frac{1 - V_2}{2} = \frac{V_2 + 3I_1}{2}$$

$$\frac{\frac{1 - V_2}{2} - V_2}{2} = 3 \left[ \frac{1 + \frac{1 - V_2}{2}}{2} \right] = \frac{1 - V_2}{2} = 3 \left[ \frac{3 - V_2}{2} \right]$$

$$\frac{1}{2} - \frac{9}{2} = \frac{V_2 - V_2}{2} = +\frac{8}{2} = \frac{V_2}{2}$$


$$V_2 = 8V$$

$$I_1 = -2.5$$

$$Z_{11} = \frac{1}{-2.5} = -0.4$$

$$Z_{21} = \frac{8}{-2.5} = 3.2 \Omega$$

DATE

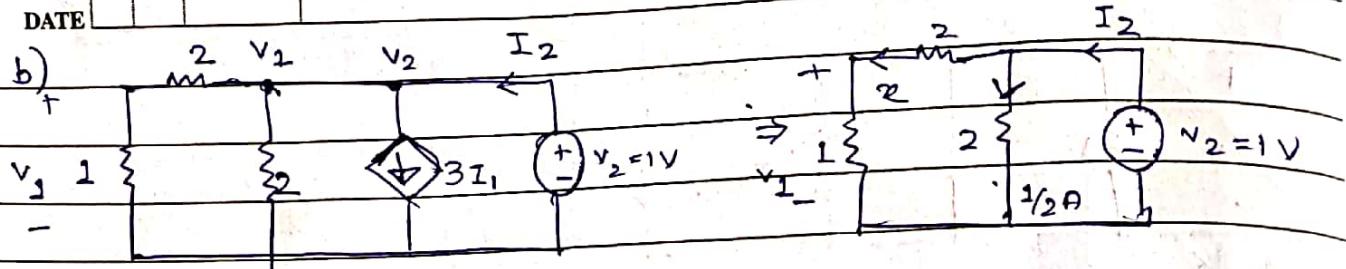

$$I_2 = \frac{1}{\frac{6}{5}} = 0.833$$

$$0.833 = 0.5 + \chi$$

$$\chi = 0.33$$

$$v_1 = \frac{1}{3} V$$

$$I_2 = 0.833$$

$$Z_{12} = \frac{v_1}{I_2} = \frac{1}{3 \times 0.833} = 0.4$$

$$\begin{bmatrix} -0.4 & 0.4 \\ 3.2 & 1.2 \end{bmatrix}$$

$$Z_{22} = \frac{v_2}{I_2} = \frac{1}{0.833} = 1.2$$


(L) dependent sources go then  
which means it is not a  
reciprocal

Y:

$$I_1 = Y_{11}v_1 + Y_{12}v_2$$

$$I_2 = Y_{21}v_1 + Y_{22}v_2$$

$$Y_{11} = \frac{I_1}{v_1}$$

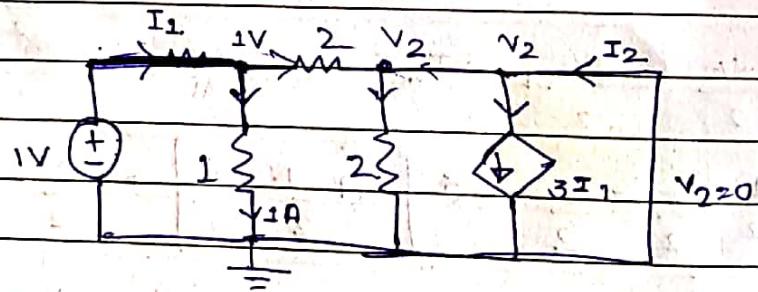

KCL at node v2

$$\frac{1-v_2}{2} + I_2 = \frac{v_2}{2} + 3I_1$$

$$v_2 = 0$$

$$I_1 = \frac{1+1-v_2}{2}$$

$$\frac{1}{2} + I_2 = 3I_1$$

$$= 1 + \frac{1}{2}$$

$$3I_1 - I_2 = \frac{1}{2}$$

$$= 1.5$$


$$3\left(\frac{3}{2}\right) - I_2 = \frac{1}{2}$$

$$\Rightarrow I_2 = 4 \text{ A} //$$

DATE

$$Y_{11} = \frac{1.5}{1} = \frac{3}{2} \text{ S}$$
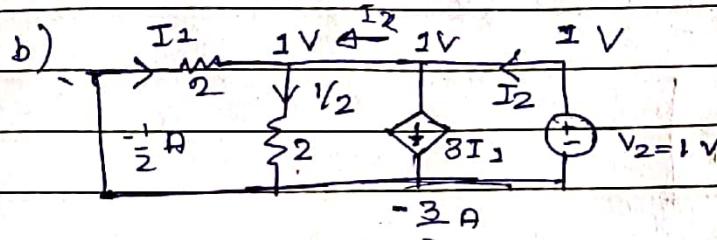
$$Y_{21} = \frac{I_2}{V_1} = \frac{4}{1} = 4 \text{ S}$$




, so will also short circuited

$$I_2 + \left(-\frac{1}{2}\right) = \frac{1}{2} \quad I_2 = \frac{-3}{2} + 1 = -1 \quad 2 //$$

$$I_2 = -1 \text{ A}$$

$$Y_{12} = \frac{I_1}{V_2} = \frac{-1}{2} \text{ S}$$

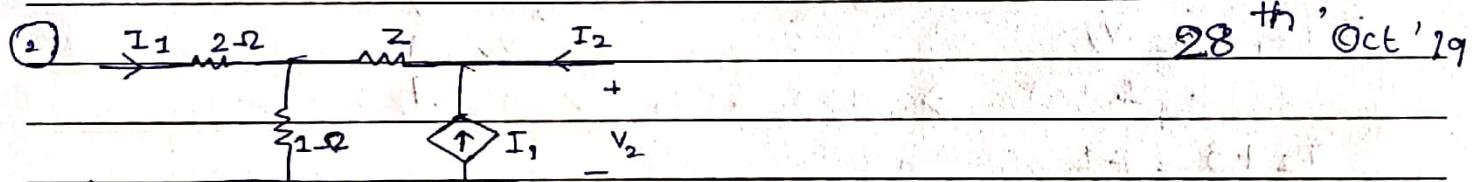
$$Y_{22} = \frac{I_2}{V_2} = -\frac{1}{2} \text{ S}$$



Find  $\eta$ :

$$V_1 = AV_2 - BI_2 \rightarrow ①$$

$$I_1 = CV_2 - DI_2 \rightarrow ②$$

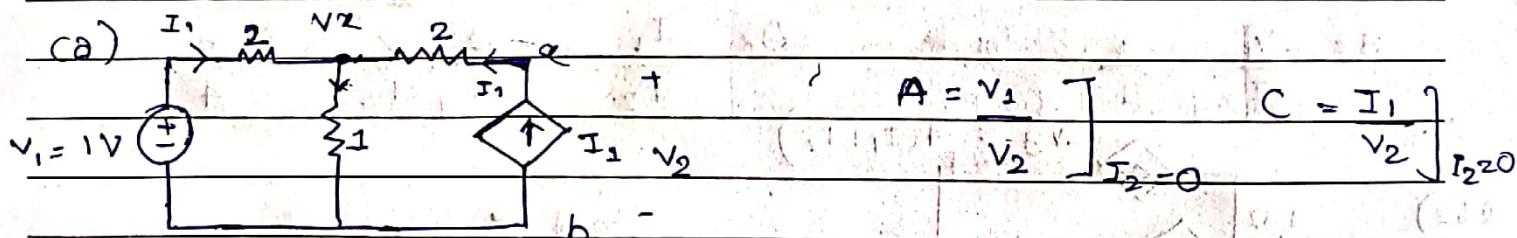

KCL at node  $V_x$ :

$$\frac{1-V_x}{2} + I_x = V_x \Rightarrow \frac{1-V_x}{2} + \frac{1-V_x}{2} = V_x \Rightarrow 1 - V_x = V_x \Rightarrow 1 = 2V_x$$

$$\cancel{\frac{1}{2}} - \cancel{\frac{1}{4}} + I_x = \cancel{\frac{1}{2}} \Rightarrow I_x = \frac{1}{4} \text{ A} \quad V_x = \frac{1}{2} \text{ V}$$

$$I_1 = \frac{1-V_x}{2} = \frac{1}{2} - \frac{1}{4} = \frac{1}{4} \text{ A}$$


DATE

$$V_a - 2I_1 - \frac{V_2}{2} (1) - V_b = 0$$

$$V_{ab} = V_2 = 2I_1 + V_2$$

$$= 2\left(\frac{1}{4}\right) + \frac{1}{2} = \frac{1}{2} + \frac{1}{2} = 1V.$$

$A = V_1 = 1$	$C = I_1 = \frac{1}{4}$
$V_2$	$\frac{1}{4}$

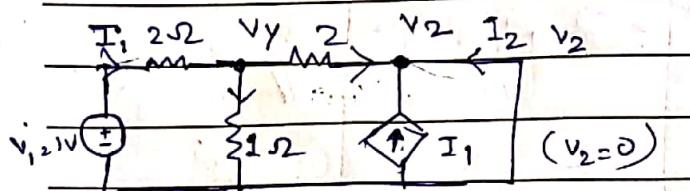KCL at  $V_y$ 

$$\frac{1-V_y}{2} \pm V_y + V_y$$

$$\frac{1-V_y}{2} = V_y + V_y$$

$$I_1 = \frac{1-V_y}{2} = \frac{1-\frac{1}{4}}{2} = \frac{3}{8}$$

$$\frac{1}{2} = V_y + V_y$$

$$\frac{1}{2} = 2V_y$$

$$I_2 + I_1 = \frac{V_2 - V_y}{2}$$


$$V_y = \frac{1}{4}$$

$$I_2 + 3 = -\frac{1}{8}$$

$$I_2 = -\frac{1}{8} - 3 = -\frac{1}{8} - \frac{24}{8} = -\frac{25}{8}$$

$$B = \frac{-V_1}{I_2} = \frac{-1}{1} \times 2 = 2$$
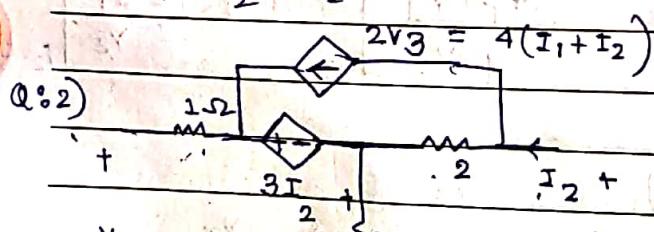
$$D = \frac{-I_1}{I_2} = \frac{3}{8} \times 2 = \frac{3}{4}$$



Find Z parameters


$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

whatever current is entering there must be  $I_1$  current should return back to their respective ports

DATE
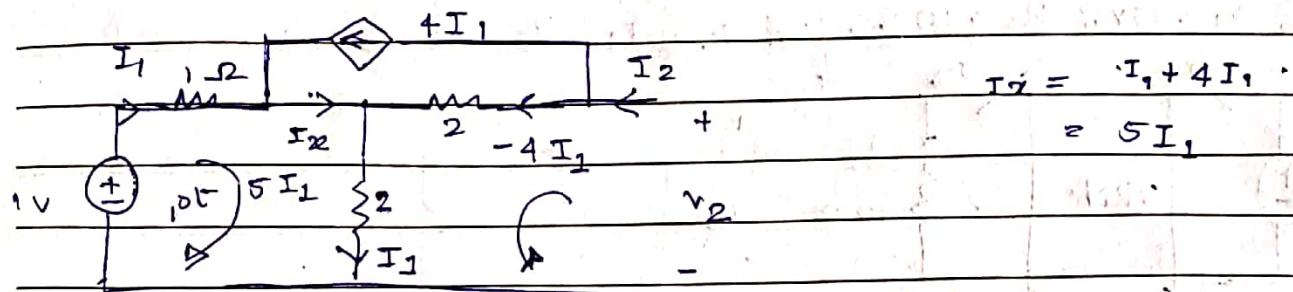
$$(a) \quad z_{11} = v_1 \quad ; \quad z_{21} = v_2 \\ I_1 \quad I_2 = 0 \quad I_1 \quad I_2 = 0$$



KVL for 1st loop

$$v_1 - I_1 - 2I_1 = 0$$

$$1 - 3I_1 = 0$$

$$I_1 = 1/3$$

$$z_{11} = v_1 = 3A$$

$$I_1$$

KVL for 2nd loop

$$v_2 - 2(-4I_1) - 2I_1 = 0$$


$$v_2 + 8I_1 - 2I_1 = 0$$

$$v_2 + 6I_1 = 0$$

$$v_2 = -6 \left(\frac{1}{3}\right) = -2V$$

$$\frac{v_2}{I_1} = -6 \Omega = z_{21}$$

$$(b) \quad I_1 = 0$$

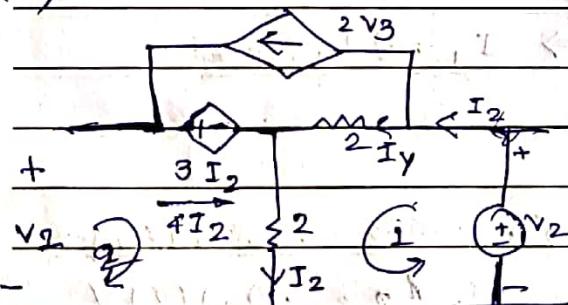

$$I_y + 4I_2 = I_2$$

$$I_y = -3I_2$$

Loop 1

$$v_1 - 2(-3I_2) - 2I_2 = 0 \quad 1 + 6I_2 - 2I_2 = 1 + 4I_2 \quad \text{but } I_2 = -\frac{1}{4}$$

$$4$$

KVL for Loop 2

$$v_1 - 3I_2 - 2I_2 = 0 \Rightarrow v_1 - 5I_2 = 0 \quad v_1 = 5I_2 = 5\left(-\frac{1}{4}\right)$$

$$z_{21} = v_2 = \frac{1}{-1} \times 4 = -4$$

$$z_{12} = \frac{v_1}{I_2} = \frac{5}{4} \times \frac{4}{-1} = -5/4$$

$$z_2 = \begin{vmatrix} 3 & 5 \\ -6 & -4 \end{vmatrix}$$


It is not symmetric & reciprocal

DATE

$$3) I_2 = 0, V_1 = 20V, I_1 = 2A, V_2 = 4V$$

$$ii) I_1 = 0, V_2 = 12V, I_2 = 1.5A, V_1 = 3V$$

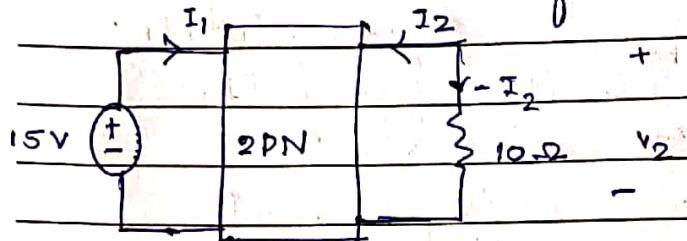When  $V_1 = 15V, R_L = 10\Omega$ , find  $I_2, I_1, V_2$



$$Z_{11} = \frac{V_1}{I_1}$$

$$= 20$$

$$= 2$$

$$Z_{12} = \frac{V_1}{I_2}$$

$$= 10$$

$$= 1.5$$

$$Z_{21} = \frac{V_2}{I_1}$$

$$= 2$$

$$= 4$$

$$Z_{22} = \frac{V_2}{I_2}$$

$$= 8$$

$$= 5$$

$$V_1 = 10I_1 + 2I_2$$

$$V_2 = -10I_2$$

$$V_2 = 2I_1 + 8I_2$$

$$-10I_2 = 2I_1 + 8I_2 \Rightarrow -18I_2 = 2I_1 \Rightarrow I_1 = -9I_2 \quad \text{④}$$

from eqn ①

$$V_1 = 15 = -90I_2 + 2I_2 = -88I_2 = -0.1704$$


$$15 = 1.5336 \cdot 10I_1 + 0.3408$$

$$15.3408 = 10I_1$$

$$I_1 = 1.534 A$$


Parameters	Symmetrical	Reciprocal
$Z$	$Z_{11} = Z_{22}$	$Z_{12} = Z_{21}$
$y$	$y_{11} = y_{22}$	$y_{12} = y_{21}$
$h$	$h_{11} = h_{22}$	$h_{12} = -h_{21}$
$T$	$A = D$	$\Delta T = 1$
$T'$	$A' = D'$	$\Delta T' = 1$
$g$	$g_{11} = g_{22}$	$g_{12} = -g_{21}$

DATE

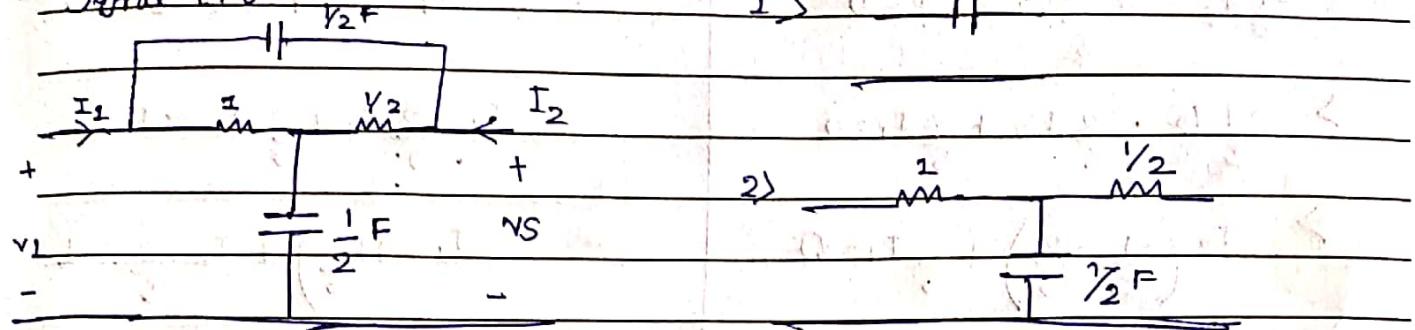Find  $[Y]$ :

$$\Rightarrow \frac{1}{2}F = \frac{2}{s} \Omega$$

(a)

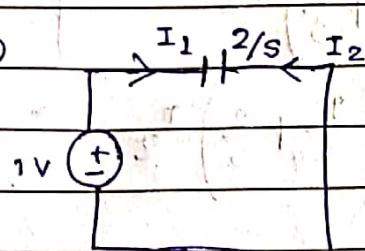


$$I_2 = -\frac{s}{2} A$$

$$Y_{11} = \left[ \begin{array}{c} I_1 \\ v_1 \end{array} \right] \quad v_2 = 0$$

$$Y_{21} = \left[ \begin{array}{c} I_2 \\ v_1 \end{array} \right] \quad v_2 = 0$$

$$= \frac{s}{2} \Omega$$


$$= -\frac{s}{2} \Omega$$

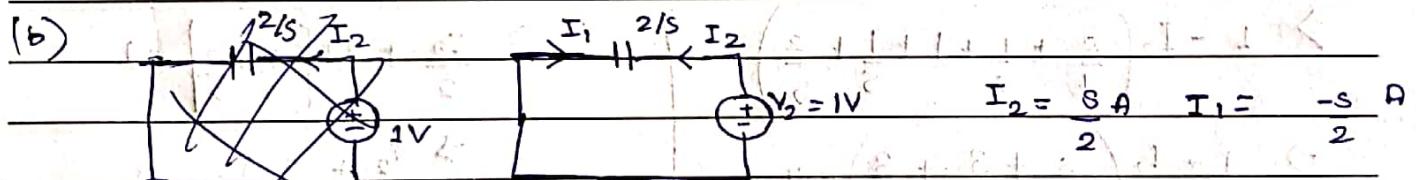

$$Y_{12} = \left[ \begin{array}{c} I_1 \\ v_2 \end{array} \right] = -\frac{s}{2} \Omega$$

$$Y_{21} = \left[ \begin{array}{c} I_2 \\ v_2 \end{array} \right] = \frac{s}{2} \Omega$$
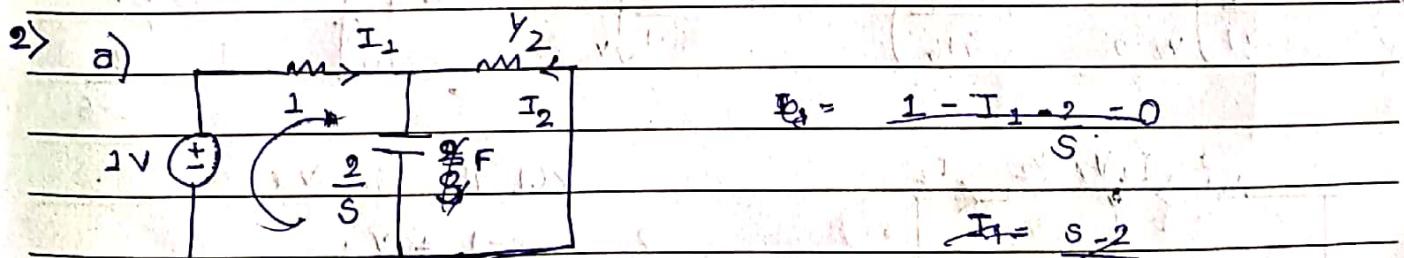
$$Y = \begin{bmatrix} s/2 & -s/2 \\ -s/2 & s/2 \end{bmatrix}$$



$$I_1 = \frac{1 - I_2}{s} = 0$$

$$I_2 = \frac{s - 2}{s}$$

$$\Rightarrow 1 - I_1 - \frac{2}{s} (I_1 - I_2) = 0$$

$$\frac{1 - I_1}{s} - 2 \frac{I_1}{s} + 2 \frac{I_2}{s} = 0 \Rightarrow 1 + I_1 \left( -\frac{1}{s} - \frac{2}{s} \right) + \frac{2}{s} I_2 = 0$$

DATE

$$-\frac{1}{2} I_2 - \frac{2}{S} (I_2 - I_1) = 0$$

$$1 + I_1 - \frac{2}{S} (I_1 + I_2) = 0$$

$$\Rightarrow -\frac{1}{2} I_2 - \frac{2}{S} I_2 + \frac{2}{S} I_1 = 0$$

$$I_1 + 2 I_1 + \frac{2}{S} I_2 = 1$$

$$\Rightarrow I_2 \left( -\frac{1}{2} - \frac{2}{S} \right) + \frac{2}{S} I_1 = 0$$

$$I_1 \left( 1 + \frac{2}{S} \right) + I_2 \cdot \frac{2}{S} = 1$$

$$\frac{2}{S} I_1 = \left( \frac{1}{2} + \frac{2}{S} \right) I_2$$

$$I_1 - I_2 = 1$$

$$I_1 = \frac{s}{2} \left( \frac{1}{2} + \frac{2}{S} \right) I_2 \rightarrow ②$$

$$I_1 = \frac{I_2}{2}$$

$$1 + S I_2 \left( \frac{1}{2} + \frac{2}{S} \right) \left( -\frac{1}{2} - \frac{2}{S} \right) + \frac{2}{S} I_2 = 0$$

$$= \frac{I_2}{2} + \frac{I_2}{S} + \frac{2}{S} I_2 = 1$$

$$\Rightarrow 1 + \left( S I_2 + I_2 \right) \left( -\frac{1}{2} - \frac{2}{S} \right) + \frac{2}{S} I_2 = 0$$

$$\frac{I_2}{S} \left( 2 + 2 \right) = 1$$

$$\Rightarrow \frac{1 + S I_2}{4} - \frac{I_2}{2} - \frac{I_2}{S} - \frac{I_2}{S} + \frac{2}{S} I_2 = 0$$

$$I_2 = \frac{S}{4}$$

$$\Rightarrow 1 - I_2 \left( \frac{S}{4} + \frac{1}{2} + \frac{1}{S} + \frac{2}{S} \right) = 0$$

$$\Rightarrow I_2 + I_2 \left[ \frac{1}{S} + \frac{2}{S} \right] = 1$$

$$\Rightarrow 1 - I_2 \left( \frac{S}{4} + \frac{3}{2} + \frac{3}{S} \right) = 0$$

$$\Rightarrow I_2 + \frac{3}{2} I_2 = 1$$

$$I_2 = \frac{1}{\left( \frac{S}{4} + \frac{3}{2} + \frac{3}{S} \right)}$$

$$\frac{(S+6+12)}{1S}$$

$$\frac{4S}{S+18}$$


$$= I_2 \left[ \frac{1}{2} + \frac{3}{S} \right] = 1$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{(S+4)}{(S+6)} \quad Y_{12} = \frac{I_2}{V_1} = \frac{-4}{(S+6)}$$

$$I_2 = \frac{S+6}{2S} = 1$$

$$I_2 > \frac{2S}{S+6}$$

$$\frac{1}{2} I_1 V_2 \quad Y_2 \quad I_2$$

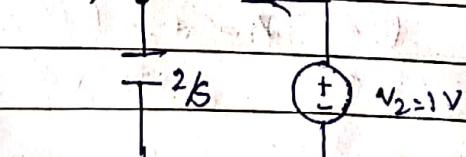
KCL at node  $V_2$ 

$$\Rightarrow \frac{V_2 - 1}{2} + V_2 = \frac{1}{2}$$

DATE

$$\frac{I_1 + 2}{s} (I_1 + I_2) = 0 \rightarrow ① \quad I_1 = \frac{s+4}{s+6} \quad I_2 = \frac{s+4}{s+6}$$
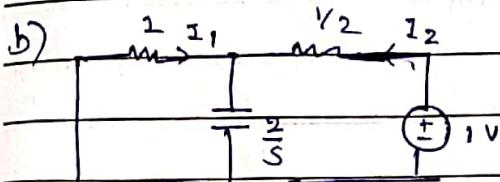
$$\frac{I_1 + I_2}{2} = 1 \rightarrow ②$$



$$\Rightarrow I = \frac{1}{2} I_2 + \frac{2}{s} (I_1 + I_2)$$

$$\Rightarrow I = \frac{I_2}{2} + \frac{2}{s} I_1 + \frac{2}{s} I_2$$

$$Y_{11} = \left[ \frac{I_1}{V_2} \right] = -\frac{4}{s+6} \quad I_1 = -\frac{4}{s+6} \quad I_2 = \frac{2(s+2)}{s+6}$$

$$Y_{22} = \frac{2(s+2)}{s+6}$$

$$Y = \begin{bmatrix} \frac{s+4}{s+6} & -\frac{4}{s+6} \\ -\frac{4}{s+6} & \frac{2(s+2)}{s+6} \end{bmatrix} \Rightarrow \begin{bmatrix} \frac{8}{2} + \frac{(s+4)}{s+6} & -\frac{3}{2} - \frac{4}{s+6} \\ -\frac{5}{2} - \left( \frac{4}{s+6} \right) & \frac{3}{2} + \frac{2(s+2)}{s+6} \end{bmatrix}$$



$$\frac{s}{2} + \frac{s+4}{s+6} \Rightarrow \frac{s^2 + 6s + 2s + 8}{2s + 12} \Rightarrow \frac{s^2 + 8s + 8}{2s + 12}$$

$$-\frac{5}{2} - \frac{4}{s+6} \Rightarrow \frac{-s^2 - 6s - 8}{2(s+6)} \Rightarrow \frac{-s^2 - 6s - 8}{2s + 12}$$

$$-\frac{5}{2} - \frac{4}{s+6} \Rightarrow \frac{-s^2 - 6s - 8}{2s + 12}$$

$$\frac{s}{2} + \frac{2s+4}{s+6} \Rightarrow \frac{s^2 + 6s + 4s + 8}{2s + 12} = \frac{s^2 + 10s + 8}{2s + 12}$$

Q: Find Y parameters of the network

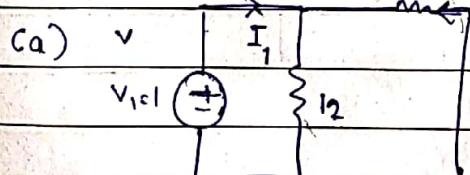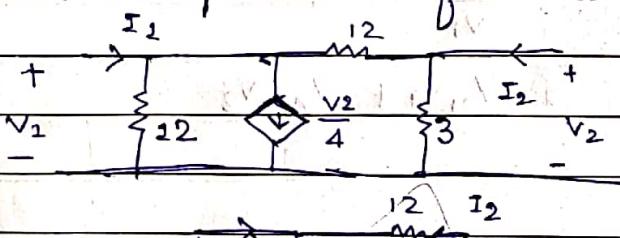

$$I_1 - 12(I_1 + I_2) = 0$$

$$I_1 = 12(I_1 + I_2) \rightarrow ①$$

$$I = -I_2 (-11I_2)$$

$$+ 12I_2 + 12(I_2 + I_1) = 0$$

$$\frac{-1}{12} = I_2$$

$$I_1 = -12I_2$$

$$24I_2 + 12I_1 = 0$$

DATE

$$\begin{aligned} 2I_2 + I_1 &= 0 \\ I_1 &= -2I_2 \end{aligned}$$


$$\begin{aligned} I &= 12(I_1 + I_2) \\ &= 12(-2I_2 + I_2) \\ I &= 12(-I_2) \end{aligned}$$

$$I_1 = -2 \left( \frac{-1}{6} I_2 \right)$$

$$I_2 = \frac{-1}{12} A$$

$$= \frac{1}{6} A$$

b)

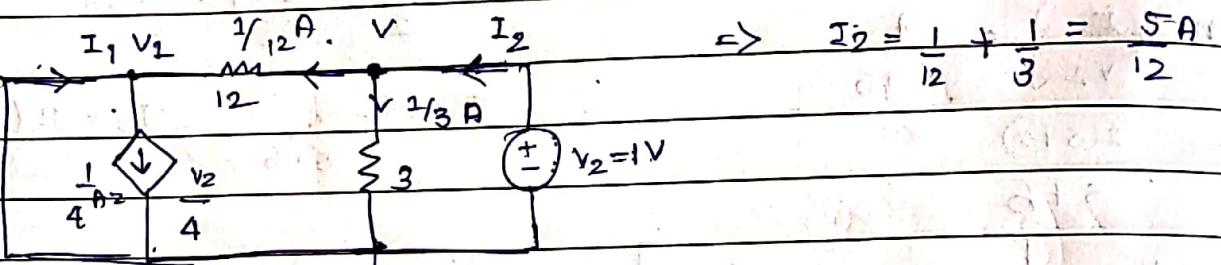


$$I_1 = \frac{V_2}{4} + \frac{V_1 - V_2}{12}$$

$$I_1 = \frac{V_2 - V_2 + V_1}{4} = \frac{V_1}{4}$$

$$I_1 = \frac{V_2 + V_1}{6}$$

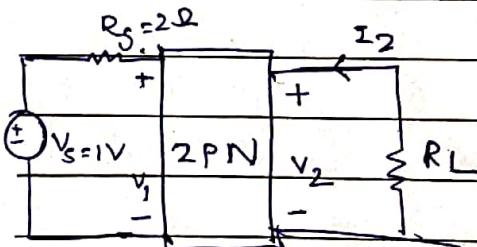Q: Given  $V_s = 1V$  &  $R_s = 2\Omega$  &  $\gamma = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix}$  for what value of  $R_L$  power transferred is max.




$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$I_1 = 2V_1 + (-1)V_2 \rightarrow ①$$

$$I_2 = (-1)V_1 + 2V_2 \rightarrow ②$$

(a) To find  $V_{AB}$

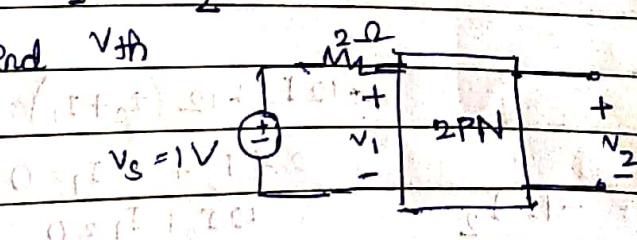

DATE

from ②  $v_1 = 2v_2 \rightarrow ③$

KVL for 1st loop  $v_s - 2I_1 - v_1 = 0$

$$1 - 2I_1 - v_1 = 0$$

$$v_1 = 1 - 2I_1 \rightarrow ④$$

$$I_1 = 2v_1 - v_2$$

$$I_1 = 2(2v_2) - v_2 = 4v_2 - v_2 = 3v_2$$

$$v_1 = 1 - 2(3v_2)$$

$$v_1 = 1 - 6v_2$$


$$2v_2 + 6v_2 = 1$$

$$8v_2 = 1$$

$$v_2 = \frac{1}{8}$$

$$R_{th} =$$

$$I_2 = 0 \quad -2I_1 - v_1 = 0$$

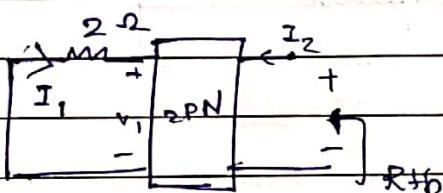

$$v_1 = -2I_1 \rightarrow ①$$

$$I_2 = 2v_1 - v_2$$

$$= 2(-2I_1) - v_2$$

$$v_1 = 2v_2$$

$$I_1 =$$

$$I_1 + 4I_1 = -v_2$$

$$-2I_1 = 2v_2$$

$$5I_1 = -v_2$$

$$0 = 2I_1 + 2v_2 = 0$$

$$I_1 = -\frac{v_2}{2}$$

$$-2I_1 = 2v_2 = 0$$


$$-2I_1 = v_2$$

2

X

$$v_2 = -I_1$$

$$R_{th} =$$

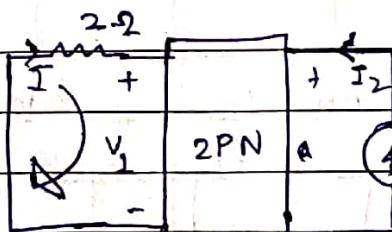

$$I_2 = 1A$$

30th Oct' 19

$$\text{from } ③ \quad 1 = -2I_1 + 2v_2$$

$$\text{from } ② \quad I_1 = 2(-2I_1) - v_2$$

$$-I_1 + 4I_1 = -v_2$$

$$v_1 = -2I_1 \rightarrow ①$$

$$5I_1 = -v_2$$

$$I_1 = 2v_1 - v_2 \rightarrow ②$$

$$I_1 = -\frac{v_2}{5}$$

$$I_2 = -v_1 + 2v_2 \rightarrow ③$$

$$\frac{1}{12 \times 8} = -\frac{1}{12} + \frac{1}{8}$$

PES  
UNIVERSITY

DATE


$$I = -2 \left( \frac{-V_2}{5} \right) + 2V_2 \Rightarrow I = \frac{2V_2 + 2V_2}{5}$$

$$\Rightarrow I = \frac{12V_2}{5}$$

$$\Rightarrow V_2 = \frac{5}{12} I \quad \text{X} \quad \frac{5}{12} //$$


 $\frac{5}{12}$ 
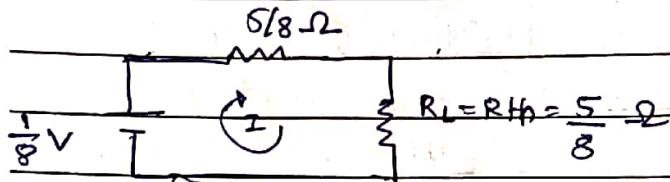
$$R_{Th} = \frac{V_2}{I_2} = \frac{5}{8} \Omega$$




$$P = 0.25 \times 10^{-3} = \left( \frac{1}{10} \right)^2 \times \frac{5}{8}$$

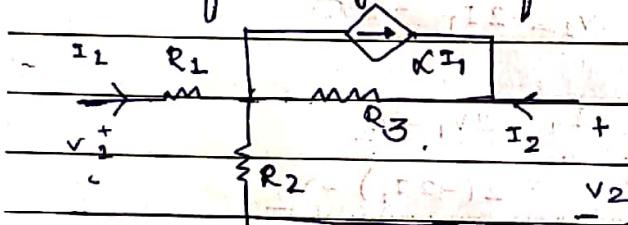Q: For the following vckt find h - parameters.



by Source transformation

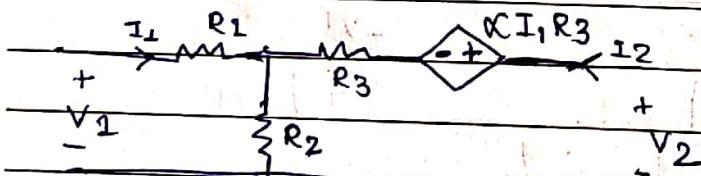


$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = V_1$$

$$h_{21} = \frac{I_2}{V_1}$$

$$V_2 = 0$$

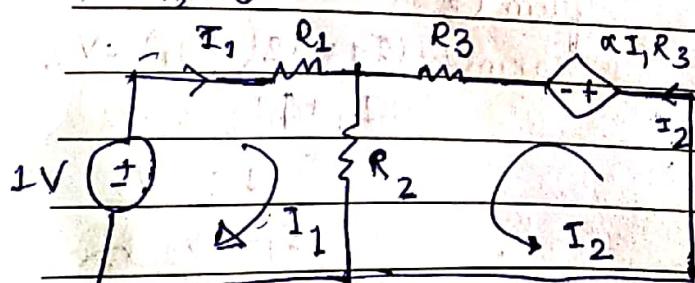

DATE

KVL for Loop 1 :

$$1 - R_1 I_1 - R_2 (I_1 + I_2) = 0$$

$$1 - R_1 I_1 - R_2 I_1 - R_2 I_2 = 0$$

$$1 = R_1 I_1 + R_2 I_1 + R_2 I_2 = 0$$

$$1 = I_1 (R_1 + R_2) + I_2 R_2 = 0$$

KVL for 2 :

$$+ \alpha I_1 R_3 + I_2 R_3 + R_2 (I_2 + I_1) = 0$$

$$+ \alpha I_1 R_3 + I_2 R_3 + R_2 I_2 + R_2 I_1$$

$$I_1 (\alpha R_3 + R_2) + I_2 (R_3 + R_2) = 0$$

$$I_1 (\alpha R_3 + R_2) = - I_2 (R_3 + R_2)$$

$$\frac{I_2}{I_1} = - \frac{(\alpha R_3 + R_2)}{(R_3 + R_2)}$$

$$1 = I_2 (R_1 + R_2) + I_2 \left( - \frac{(\alpha R_3 + R_2)}{(R_3 + R_2)} \right)$$

$$1 = I_2 (R_1 + R_2) - \left[ I_2 \left( \frac{(\alpha R_3 + R_2)}{(R_3 + R_2)} \right) R_2 \right]$$

$$1 = I_2 (R_1 + R_2) - I_2 R_2 \frac{(\alpha R_3 + R_2)}{(R_3 + R_2)}$$

$$1 = I_2 \left[ \frac{(R_1 + R_2) - (\alpha R_3 + R_2)}{R_3 + R_2} \right]$$

$$1 = I_2 \left[ \frac{R_1 R_3 + R_2 R_3 + R_1 R_2 + R_2^2 - R_2 \alpha R_3 - R_2^2}{R_3 + R_2} \right]$$


$$1 = I_2 \left[ \frac{R_1 R_3 + R_2 R_3 + R_1 R_2 - R_2 \alpha R_3}{R_3 + R_2} \right]$$

$$I_1 = \frac{R_3 + R_2}{R_1 R_3 + R_2 R_3 + R_1 R_2 - R_2 \alpha R_3} = \frac{R_3 + R_2}{R_1 (R_3 + R_2) + R_2 (R_3 - \alpha R_3)}$$

$$h_{11} = \frac{R_1 (R_3 + R_2) + R_2 (R_3 - \alpha R_3)}{R_3 + R_2} = \frac{R_1 + R_2 (R_3 - \alpha R_3)}{R_3 + R_2}$$

DATE

b)  $I_1 = 0$

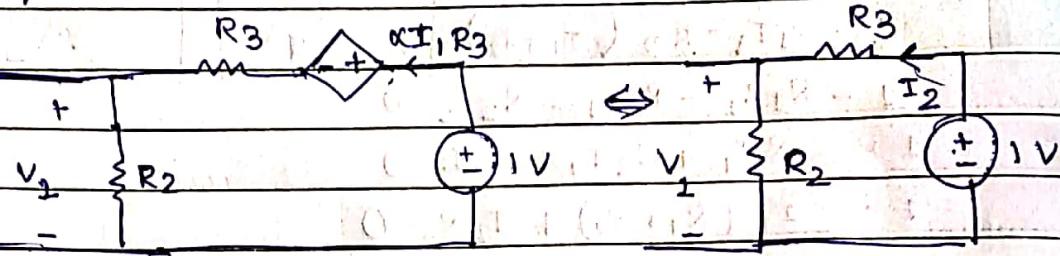

$$1 - I_2 R_3 - I_2 R_2 = 0 \quad h_{12} = V_1 \quad |$$

$$1 - k I_2 (R_3 + R_2) = 0 \quad V_2 \quad |$$

$$1 = I_2 (R_3 + R_2) \quad h_{22} = I_2 \quad |$$


$$I_2 = \frac{1}{R_3 + R_2} \quad |$$

$$V_1 = \left( R_2 \right) \left( \frac{1}{R_3 + R_2} \right) = \frac{R_2}{R_3 + R_2}$$

$$h_{12} = \frac{R_2}{R_3 + R_2} \quad h_{22} = 1$$

$$R_3 + R_2 - (R_3 + R_2)$$

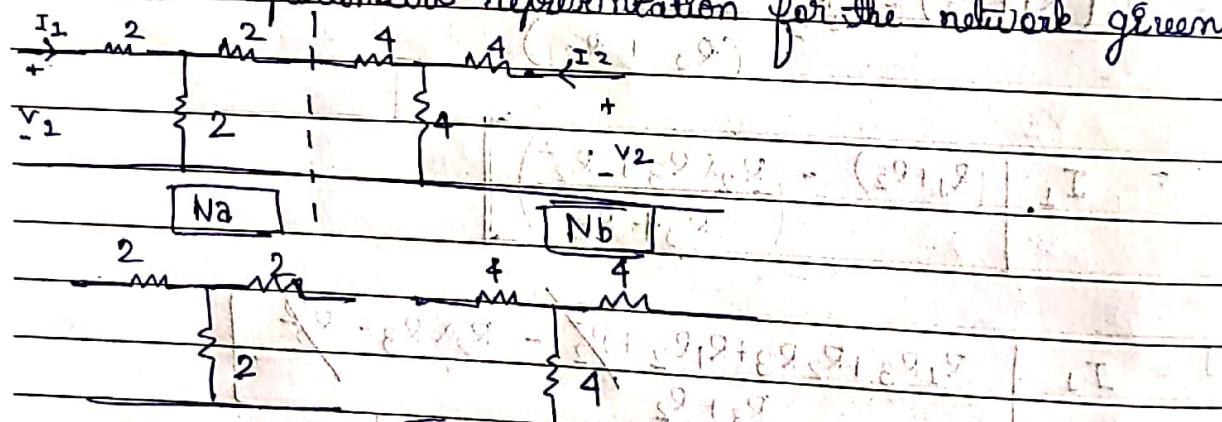Find suitable parametric representation for the network given.



T parameter


$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \frac{V_1}{V_2}$$

$$C = \frac{I_1}{V_2}$$

$$\therefore I_2 = 0$$

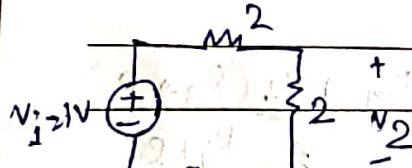


$$T_1 = \frac{1}{4} A$$

$$V_2 = \frac{1}{2} \left( \frac{1}{4} \right) = \frac{1}{2} V$$

DATE

$$A = \frac{1 \times 2}{1} = 2 \quad C = \frac{1}{4} \times \frac{2}{1} = \frac{1}{2}$$

b)  $V_2 = 0$

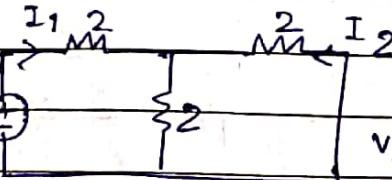

$$1 = +2I_1 + 2(I_1 + I_2)$$

$$R_{eq} = (2||2) + 2$$

$$\therefore = 3\Omega$$


$$I_1 = \frac{1}{3} A$$

$$I_2 = -\frac{1}{3} \times \frac{2}{4} = -\frac{2}{12}$$

$$B = -\frac{V_1}{I_2} = -\frac{-1 \times 12}{-2} = 6 \quad D = -\frac{I_1}{I_2} = -\frac{1}{\frac{2}{12}} = 2$$

$$\begin{bmatrix} 2 & 6 \\ \frac{1}{2} & 2 \end{bmatrix}$$

b)  $I_2 = 0$

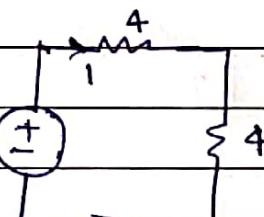


$$I_1 = \frac{1}{8} \quad V_2 = 4 \left( \frac{1}{8} \right) = \frac{1}{2}$$

$$A_b = \frac{V_1}{V_2} = \frac{1 \times 2}{1} = 2$$

$$C_b = \frac{I_1}{V_2} = \frac{1}{8} \times \frac{2}{1} = \frac{1}{4}$$

$$V_2 = 0$$

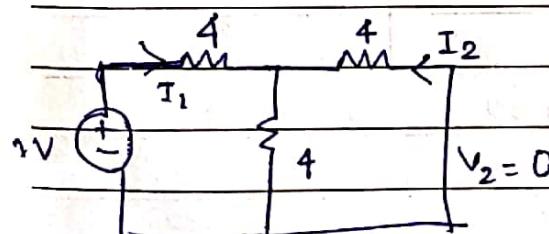

$$R_{eq} = (4||4) + 4 \\ = 2 + 4 \\ = 6$$

$$I_1 = \frac{1}{6} A$$

$$I_2 = -\frac{1}{6} \times \frac{4}{8} = -\frac{1}{12} A$$

$$B_b = -\frac{V_1}{I_2} = -\frac{-1 \times 12}{-1} = 12$$

$$D_b = -\frac{I_1}{I_2} = -\frac{\frac{1}{6} \times 12}{-1} = 2$$

DATE

$$\begin{bmatrix} 2 & 6 \\ \frac{1}{2} & 2 \end{bmatrix} = \begin{bmatrix} 2 & 12 \\ \frac{1}{4} & 2 \end{bmatrix} = \begin{bmatrix} 4 + \frac{6}{2} & 24 + 12 \\ \frac{1}{8} + \frac{1}{2} & 6 + 4 \end{bmatrix}$$

Q: 2)

$$\text{parallel } - Y$$

$$\begin{bmatrix} 2 & 2 \\ 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix}$$

$$Q: 3) Z = \begin{bmatrix} 50 & 25 \\ 25 & 100 \end{bmatrix} \quad z_{12} = z_{21} \text{ reciprocal}$$

$$(z_{11} - z_{12}) \quad z_b \quad z_{22} - z_{12} = 75$$

$$z_a = 25 \quad z_c (z_{12}) = 25$$

$$= 25$$

$$= 25$$

$$+ 100 = 125$$

$$+ 100 = 100$$

$$+ 100 = 100$$

$$+ 100 = 100$$

$$+ 100 = 100$$

$$+ 100 = 100$$

$$+ 100 = 100$$

$$+ 100 = 100$$

$$+ 100 = 100$$