

## DIGITAL DESIGN USING HDL LABORATORY (UE18EC206)


### EXPERIMENT-11

#### **SIMULATION OF MEALY AND MOORE MODELS USING XILINX VIVADO TOOL**

**Aim:** Write a verilog code to simulate Mealy and Moore machine Sequence detector for the given sequence

#### **Sequence detector (1011)**

❖ Mealy model

 

```
module mealy_1011( input clk, reset, inp, output outp);
```

```
    reg outp;
```

```
    reg [1:0] state;
```

```
    reg [1:0] next_state;
```

```
always @(posedge clk)
```

```
begin
```

```
    if (reset)
```

```
state <= 2'b00;
```

else

state <= next\_state;

end

**always @(state, inp)**

case( state )

2'b00: begin

if( inp )

begin

next\_state <= 2'b01;

outp <= 0;

end

else

begin

next\_state <= 2'b00;

outp <= 0;

end

end

2'b01: begin

if( inp )

begin

next\_state <= 2'b01;

outp <= 0;

end

```

    else

        begin

            next_state <= 2'b10;

            outp <= 0;

        end

    end

2'b10: begin

    if( inp )

        begin

            next_state <= 2'b11;

            outp <= 0;

        end

    else

        begin

            next_state <= 2'b00;

            outp <= 0;

        end

    end

2'b11: begin

    if( inp )

        begin

            next_state <= 2'b01;

            outp <= 1;

```

```

        end

    else

        begin

            next_state <= 2'b10;

            outp <= 0;

        end

    end


end

endmodule

```

### Moore:

Moore model

 

```

module moore_1011( input clk, reset, inp, output outp);

```

```

    reg outp;

```

```

    reg [2:0] state;

```

```
reg [2:0] next_state;
```

```
always @(posedge clk)
```

```
begin
```

```
    if (reset)
```

```
        state <= 3b000;
```

```
    else
```

```
        state = next_state;
```

```
end
```

```
always @(state, inp)
```

```
case( state )
```

```
    3'b000: begin
```

```
        if( inp )
```

```
            next_state <= 3'b001;
```

```
        else
```

```
            next_state <= 3'b000;
```

```
        end
```

```
    3'b001: begin
```

```
        if( inp )
```

```
            next_state <= 3'b001;
```

```
        else
```

```
            next_state <= 3'b010;
```

```
        end
```

```
    3'b010: begin
```

```

        if( inp )

            next_state <= 3'b011;

        else

            next_state <= 3'b000;

        end

3'b011: begin

    if( inp )

        next_state <= 3'b100;

    else

        next_state <= 3'b010;

    end

3'b100: begin

    if( inp )

        next_state <= 3'b001;

    else

        next_state <= 3'b010;

    end

endcase

always @ (state or reset)

begin

    if (reset)

        outp = 0;

    else

```

```

        case(state)

            3'b000: outp = 0;

            3'b001: outp = 0;

            3'b010: outp = 0;

            3'b011: outp = 0;

            3'b100: outp = 1;

        endcase

    end

endmodule

```

### **Testbench:**

```

module mealy_1011_tb();

    reg clk,reset,inp;

    wire outp;

    mealy_1011 uut(clk,reset,inp,outp);

    initial

        begin

            clk=0; reset=0; inp=0;

            #10 reset=1;

            #15 reset=0;

            #15 inp=1;

            #15 inp=0;

            #10 inp=1;

            #10 inp=1;

            #15 inp=1;

            #15 inp=0;

            #10 inp=1;

        end

endmodule

```

```
#10 inp=1;
```

```
#10 inp=0;
```

```
end
```

```
always #5 clk=~clk;
```

```
endmodule
```