

Network Analysis & Systems

Koshy George



Dept. of Elect. & Comm. Engineering,
PES University;
PES Centre for Intelligent Systems

UE18EC201: Network Analysis & Systems



Disclaimer (1)

- **Errors and Omissions:** The author assumes no responsibility or liability for any errors or omissions in the contents of this file. The information is provided on an “as is” basis with no guarantees of completeness, accuracy, usefulness or timeliness and without any warranties of any kind whatsoever, express or implied.
- **Breach of Confidentiality:** The information in this file are confidential and intended solely for the non-commercial use of the individual or entity to whom this file has been given, who accepts full responsibility for its use. You are not permitted to disseminate, distribute, or copy this file. If you are not the intended recipient you are notified that disclosing, copying, distributing or taking any action in reliance on the contents of this information is strictly prohibited.



Disclaimer (2)

- **Fair Use:** This file contains copyrighted material the use of which has not always been specifically authorised by the copyright owner.
- **Copyright:** No part of this file may be reproduced, stored in a retrieval system or transmitted in any form or by any means, mechanical, electronic, photocopying, recording or otherwise without the written permission of the author. Copyright ©2019 K. George. All rights reserved.



Network Analysis and Synthesis

Part V: Network Synthesis




RC Impedance Functions (1)

Recall: The PFE of an *LC*-immittance function

$$\begin{aligned}
 H(s) &= \frac{K(s^2 + \omega_1^2)(s^2 + \omega_3^2) \cdots (s^2 + \omega_i^2) \cdots}{s(s^2 + \omega_2^2)(s^2 + \omega_4^2) \cdots (s^2 + \omega_j^2) \cdots} \\
 &= \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s
 \end{aligned}$$

Foster Form I realisation:

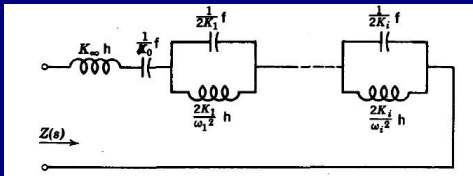


RC Impedance Functions (1)

Recall: The PFE of an *LC*-immittance function

$$\begin{aligned}
 H(s) &= \frac{K(s^2 + \omega_1^2)(s^2 + \omega_3^2) \cdots (s^2 + \omega_i^2) \cdots}{s(s^2 + \omega_2^2)(s^2 + \omega_4^2) \cdots (s^2 + \omega_j^2) \cdots} \\
 &= \frac{k_0}{s} + \frac{2k_2s}{s^2 + \omega_2^2} + \frac{2k_4s}{s^2 + \omega_4^2} + \cdots + k_\infty s
 \end{aligned}$$


Foster Form I realisation:

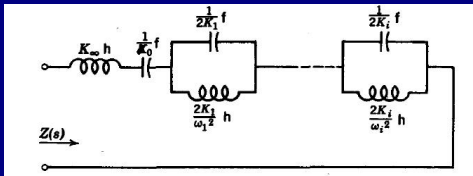

- Replace all inductances by resistances



RC Impedance Functions (2)

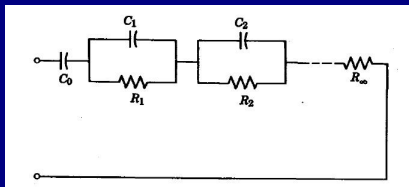


Therefore,

$$Z(s) =$$



RC Impedance Functions (2)

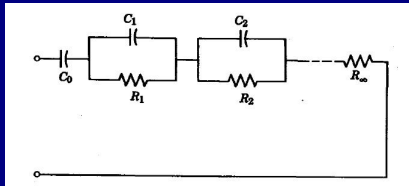


Therefore,

$$Z(s) = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

where $C_0 = 1/K_0$, $R_\infty = K_\infty$, $C_1 = 1/K_1$, $R_1 = K_1/\sigma_1$, and so on.



RC Impedance Functions (2)

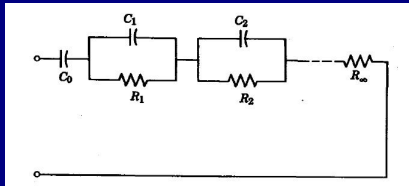

Therefore,

$$Z(s) = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

where $C_0 = 1/K_0$, $R_\infty = K_\infty$, $C_1 = 1/K_1$, $R_1 = K_1/\sigma_1$, and so on.

- Clearly, the poles of an *RC*-impedance are on the negative real axis.
- The residues are real and positive.



RC Impedance Functions (3)

- From the Foster II Form for an RC -admittance function, it follows that the poles are also on the negative real axis.
- Therefore, the poles and zeros of an RC -immittance function are on the negative real-axis.



RC Impedance Functions (3)

- From the Foster II Form for an RC -admittance function, it follows that the poles are also on the negative real axis.
- Therefore, the poles and zeros of an RC -immittance function are on the negative real-axis.
- Moreover,

$$\frac{dZ(\sigma)}{d\sigma} =$$



RC Impedance Functions (3)

- From the Foster II Form for an RC -admittance function, it follows that the poles are also on the negative real axis.
- Therefore, the poles and zeros of an RC -immittance function are on the negative real-axis.
- Moreover,

$$\frac{dZ(\sigma)}{d\sigma} = -\frac{K_0}{\sigma^2} - \frac{K_1}{(\sigma + \sigma_1)^2} - \frac{K_1}{(\sigma + \sigma_2)^2} - \dots \leq 0$$



RC Impedance Functions (3)

- From the Foster II Form for an RC -admittance function, it follows that the poles are also on the negative real axis.
- Therefore, the poles and zeros of an RC -immittance function are on the negative real-axis.
- Moreover,

$$\frac{dZ(\sigma)}{d\sigma} = -\frac{K_0}{\sigma^2} - \frac{K_1}{(\sigma + \sigma_1)^2} - \frac{K_1}{(\sigma + \sigma_2)^2} - \dots \leq 0$$

- At $\sigma = 0$, the capacitor C_0 , if it exists, is a o.c. Therefore, $Z(s)$ has a pole at $\sigma = 0$. If C_0 does not exist, then

$$Z(0) = R_1 + R_2 + \dots + R_\infty$$



RC Impedance Functions (4)

- At $\sigma = \infty$, all capacitors are s.c. If R_∞ exists, then $Z(\infty) = R_\infty$; otherwise, $Z(\infty) = 0$.
- To summarise,

$$Z(0) = \begin{cases} \infty, & C_0 \text{ present} \\ \sum R_i, & C_0 \text{ missing} \end{cases}$$

$$Z(\infty) = \begin{cases} 0, & R_\infty \text{ missing} \\ R_\infty, & R_\infty \text{ present} \end{cases}$$

Therefore, $Z(0) \geq Z(\infty)$.



RC Impedance Functions (5)

$$Z(s) = \frac{(s + \sigma_2)(s + \sigma_4)}{(s + \sigma_1)(s + \sigma_3)}$$



RC Impedance Functions (5)

$$Z(s) = \frac{(s + \sigma_2)(s + \sigma_4)}{(s + \sigma_1)(s + \sigma_3)}$$


- Clearly $Z(0) = \frac{\sigma_2\sigma_4}{\sigma_1\sigma_3}$.
- Also, the poles and zeros interlace on the negative real axis.



RC Impedance Functions (5)

$$Z(s) = \frac{(s + \sigma_2)(s + \sigma_4)}{(s + \sigma_1)(s + \sigma_3)}$$

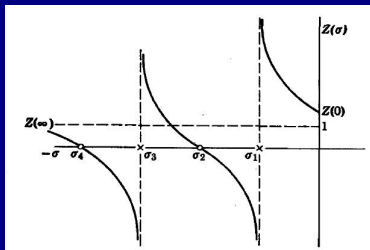- Clearly $Z(0) = \frac{\sigma_2\sigma_4}{\sigma_1\sigma_3}$.
- Also, the poles and zeros interlace on the negative real axis.



RC Impedance Functions (6)

To summarise:

- The poles and zeros lie on the negative real axis.
- The poles and zeros interlace.
- The singularity nearest to, or at, the origin must be a pole.
- The singularity nearest to, or at, $-\infty$ must be a zero.
- The residues of the poles must be real and positive.



RC Impedance Functions (6)

■

$$Z(s) = \frac{(s+1)(s+8)}{(s+2)(s+4)}$$



RC Impedance Functions (6)

■

$$Z(s) = \frac{(s+1)(s+8)}{(s+2)(s+4)}$$

■

$$Z(s) = \frac{(s+2)(s+4)}{(s+1)}$$



RC Impedance Functions (6)

■

$$Z(s) = \frac{(s+1)(s+8)}{(s+2)(s+4)}$$

■

$$Z(s) = \frac{(s+2)(s+4)}{(s+1)}$$

■

$$Z(s) = \frac{(s+1)(s+2)}{s(s+3)}$$



RC Impedance Functions (7)

Consider the network function

$$H(s) =$$



RC Impedance Functions (7)

Consider the network function

$$H(s) = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

If $H(s)$ is an admittance, then




RC Impedance Functions (7)

Consider the network function

$$H(s) = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

If $H(s)$ is an admittance, then

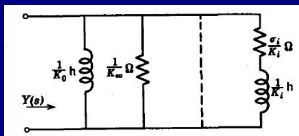

- Thus, an RC -impedance $Z_{RC}(s)$ can also be realised as an RL -admittance $Y_{RL}(s)$.
- Clearly, all the properties of RL -admittances are the same as that of RC -impedances



RC Impedance or *RL* Admittance Functions (1)

- Foster one-ports are synthesised by PFE.
- The first step is to remove $\min \operatorname{Re} Z(j\omega) = Z(\infty)$.
- For a strictly proper network function, $Z(\infty) = 0$.
- If the degree of the numerator is equal to the degree of the denominator, $Z(\infty)$ is obtained by dividing the denominator into the numerator. The quotient is $Z(\infty)$.



RC Impedance or RL Admittance Functions (1)

- Foster one-ports are synthesised by PFE.
- The first step is to remove $\min \operatorname{Re} Z(j\omega) = Z(\infty)$.
- For a strictly proper network function, $Z(\infty) = 0$.
- If the degree of the numerator is equal to the degree of the denominator, $Z(\infty)$ is obtained by dividing the denominator into the numerator. The quotient is $Z(\infty)$.
- The same remarks hold for RL admittance functions $Y(j\omega)$.



RC Impedance or *RL* Admittance Functions (2)


$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)} =$$



RC Impedance or RL Admittance Functions (2)

$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)} = \frac{8}{s} + \frac{1}{s+3} + 3$$


As an RC impedance (Foster Form I):

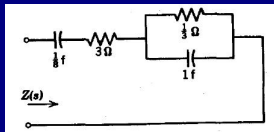


RC Impedance or RL Admittance Functions (2)

$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)} = \frac{8}{s} + \frac{1}{s+3} + 3$$

As an *RC* impedance (Foster Form I):

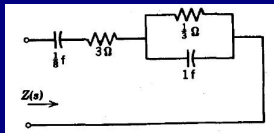

As an *RL* admittance (Foster Form II):

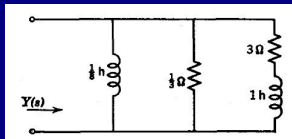

RC Impedance or *RL* Admittance Functions (3)

- Alternatively, once $\min \operatorname{Re} Z(j\omega) = Z(\infty)$ is removed, a zero at $s = \infty$ is created for the remainder. Upon inversion, it has a pole at $s = \infty$, which can be removed. This process can be repeated.
- This is merely CFE.
- The quotients represent the elements of a ladder network: Cauer Form I



RC Impedance or *RL* Admittance Functions (4)

$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$



RC Impedance or RL Admittance Functions (4)

$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

$$\begin{array}{r}
 s^2 + 3s \overline{) 3s^2 + 18s + 24} \quad (3) \\
 \underline{3s^2 + 9s} \\
 9s + 24 \quad (s^2 + 3s \overline{) \frac{1}{9}s}) \\
 \underline{\frac{1}{9}s^2 + \frac{8}{9}s} \\
 \frac{1}{9}s \quad (9s + 24 \overline{) \frac{1}{9}s}) \\
 \underline{\frac{1}{9}s} \\
 24 \quad (\frac{1}{9}s \overline{) 24}) \\
 \underline{\frac{1}{9}s} \\
 \hline
 \frac{1}{9}s
 \end{array}$$



RC Impedance or *RL* Admittance Functions (5)

$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$


$H(s)$ as an impedance (Cauer Form I):



RC Impedance or RL Admittance Functions (5)

$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

$H(s)$ as an impedance (Cauer Form I):

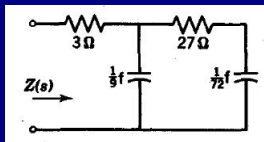


$H(s)$ as an admittance (Cauer Form I):




RC Impedance or RL Admittance Functions (5)

$$H(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

$H(s)$ as an impedance (Cauer Form I):

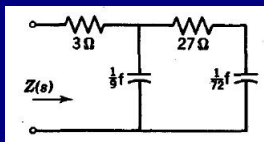

$H(s)$ as an admittance (Cauer Form I):

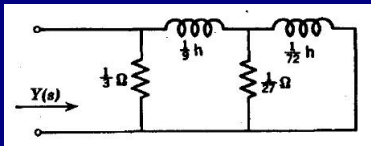

RC Admittance and *RL* Impedance Functions (1)

Consider the network function

$$H(s) = \frac{K_0}{s} + K_\infty + \frac{K_1 s}{s + \sigma_1} + \frac{K_1 s}{s + \sigma_2} + \dots$$

- Observe that the terms (third term onwards) is multiplied by a factor s . Otherwise, they cannot be realised as *RL*-impedance or *RC*-admittance.



RC Admittance and *RL* Impedance Functions (1)

Consider the network function

$$H(s) = \frac{K_0}{s} + K_\infty + \frac{K_1 s}{s + \sigma_1} + \frac{K_1 s}{s + \sigma_2} + \dots$$

- Observe that the terms (third term onwards) is multiplied by a factor s . Otherwise, they cannot be realised as *RL*-impedance or *RC*-admittance.

The properties of *RC* Admittance and *RL* Impedance Functions are:

- The poles and zeros lie on the negative real axis.
- The poles and zeros interlace.
- The singularity nearest to, or at, the origin must be a zero.
- The singularity nearest to, or at, $-\infty$ must be a pole.
- The residues of the poles must be real and negative.



RC Admittance and RL Impedance Functions (2)

Since the residue is negative, the following artifice is used:

$$\frac{H(s)}{s} = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

where $K_0, K_\infty, K_1, \dots, \geq 0$.

- That is, the properties of $Z_{RL}(s)/s$ are the same as that of an RC impedance.



RC Admittance and RL Impedance Functions (2)

Since the residue is negative, the following artifice is used:

$$\frac{H(s)}{s} = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

where $K_0, K_\infty, K_1, \dots, \geq 0$.

- That is, the properties of $Z_{RL}(s)/s$ are the same as that of an RC impedance.

A PFE of

$$H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)} =$$



RC Admittance and RL Impedance Functions (2)

Since the residue is negative, the following artifice is used:

$$\frac{H(s)}{s} = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

where $K_0, K_\infty, K_1, \dots, \geq 0$.

- That is, the properties of $Z_{RL}(s)/s$ are the same as that of an RC impedance.

A PFE of

$$H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)} = 2 - \frac{1/2}{s+2} - \frac{15/2}{s+6}$$

In contrast, a PFE of

$$\frac{H(s)}{s} =$$



RC Admittance and RL Impedance Functions (2)

Since the residue is negative, the following artifice is used:

$$\frac{H(s)}{s} = \frac{K_0}{s} + K_\infty + \frac{K_1}{s + \sigma_1} + \frac{K_1}{s + \sigma_2} + \dots$$

where $K_0, K_\infty, K_1, \dots, \geq 0$.

- That is, the properties of $Z_{RL}(s)/s$ are the same as that of an RC impedance.

A PFE of

$$H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)} = 2 - \frac{1/2}{s+2} - \frac{15/2}{s+6}$$

In contrast, a PFE of

$$\frac{H(s)}{s} = \frac{1/2}{s} + \frac{1/4}{s+2} + \frac{5/4}{s+6}$$



RC Admittance and *RL* Impedance Functions (3)

Therefore, $H(s) = \frac{1}{2} + \frac{s/4}{s+2} + \frac{5s/4}{s+6}$.


$H(s)$ as an admittance (Foster Form I):



RC Admittance and RL Impedance Functions (3)

Therefore, $H(s) = \frac{1}{2} + \frac{s/4}{s+2} + \frac{5s/4}{s+6}$.

$H(s)$ as an admittance (Foster Form I):

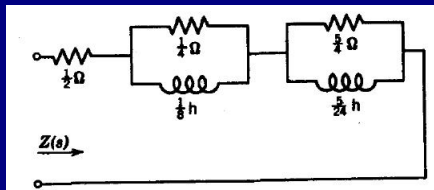


$H(s)$ as an impedance (Foster Form II):




RC Admittance and RL Impedance Functions (3)

Therefore, $H(s) = \frac{1}{2} + \frac{s/4}{s+2} + \frac{5s/4}{s+6}$.

$H(s)$ as an admittance (Foster Form I):

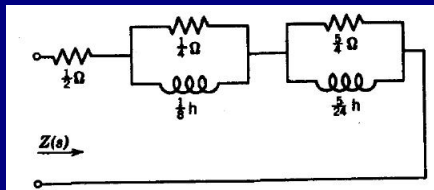

$H(s)$ as an impedance (Foster Form II):

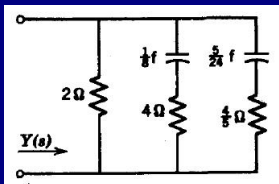

RC Admittance and *RL* Impedance Functions (4)

- To synthesise a Cauer one-port, one must remove $Z(0) = \min \operatorname{Re} Z(j\omega)$. The remainder has a zero at $s = 0$.
- Therefore, the inverse has a pole at $s = 0$, which is then removed.
- The process is repeated.



RC Admittance and RL Impedance Functions (4)

- To synthesise a Cauer one-port, one must remove $Z(0) = \min \operatorname{Re} Z(j\omega)$. The remainder has a zero at $s = 0$.
- Therefore, the inverse has a pole at $s = 0$, which is then removed.
- The process is repeated.
- This is a CFE with the polynomials arranged in ascending order.



RC Admittance and *RL* Impedance Functions (5)

$$H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$



RC Admittance and *RL* Impedance Functions (6)

$$H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$


$H(s)$ as an impedance (Cauer Form II):



RC Admittance and RL Impedance Functions (6)

$$H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

$H(s)$ as an impedance (Cauer Form II):

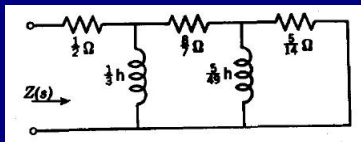


$H(s)$ as an admittance (Cauer Form II):




RC Admittance and RL Impedance Functions (6)

$$H(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

$H(s)$ as an impedance (Cauer Form II):

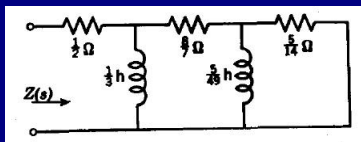

$H(s)$ as an admittance (Cauer Form II):

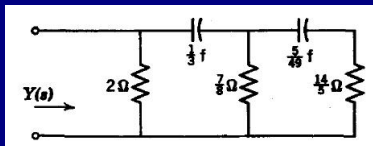

Special *RLC* Functions (1)

Consider

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

- This function is neither *LC*, *RC* nor *RL*.



Special *RLC* Functions (1)

Consider

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

- This function is neither *LC*, *RC* nor *RL*.
- Nonetheless, the CFE is



Special *RLC* Functions (1)

Consider

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

- This function is neither *LC*, *RC* nor *RL*.
- Nonetheless, the CFE is

$$\begin{array}{r} s^2 + s + 1 \overline{) s^2 + 2s + 2} \quad (1 \leftarrow Z \\ \underline{s^2 + + 1} \\ s + 1 \overline{) s^2 + s + 1} \quad (s \leftarrow Y \\ \underline{s^2 + s} \\ 1 \overline{) s + 1} \quad (s + 1 \leftarrow Z \\ \underline{s + 1} \\ \hline \end{array}$$




Special RLC Functions (2)

Thus, a realisation of

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

is

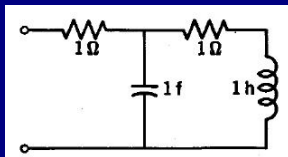


Special RLC Functions (2)

Thus, a realisation of

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

is

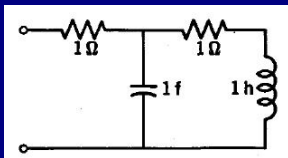

Consider

$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)}$$

- The poles and zeros do not interlace.



Special *RLC* Functions (3)

$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)}$$

■ The PFE

$$Y(s) =$$



Special *RLC* Functions (3)

$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)}$$

■ The PFE

$$Y(s) = 1 + \frac{2/3}{s+1} + \frac{-2/3}{s+4}$$

cannot be used. However,

$$\frac{Y(s)}{s} =$$



Special *RLC* Functions (3)

$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)}$$

■ The PFE

$$Y(s) = 1 + \frac{2/3}{s+1} + \frac{-2/3}{s+4}$$

cannot be used. However,

$$\frac{Y(s)}{s} = \frac{3}{2} - \frac{2/3}{s+1} + \frac{1/6}{s+4}$$

$$\Rightarrow Y(s) =$$



Special *RLC* Functions (3)

$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)}$$

■ The PFE

$$Y(s) = 1 + \frac{2/3}{s+1} + \frac{-2/3}{s+4}$$

cannot be used. However,

$$\begin{aligned} \frac{Y(s)}{s} &= \frac{3}{2} - \frac{2/3}{s+1} + \frac{1/6}{s+4} \\ \Rightarrow Y(s) &= \frac{3}{2} - \frac{2s/3}{s+1} + \frac{s/6}{s+4} \end{aligned}$$



Special *RLC* Functions (3)

$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)}$$

■ The PFE

$$Y(s) = 1 + \frac{2/3}{s+1} + \frac{-2/3}{s+4}$$


cannot be used. However,

$$\begin{aligned} \frac{Y(s)}{s} &= \frac{3}{2} - \frac{2/3}{s+1} + \frac{1/6}{s+4} \\ \Rightarrow Y(s) &= \frac{3}{2} - \frac{2s/3}{s+1} + \frac{s/6}{s+4} \\ &= \frac{3}{2} - \left(\frac{2}{3} - \frac{2/3}{s+1} \right) + \frac{s/6}{s+4} \\ &= \frac{5}{6} + \frac{2/3}{s+1} + \frac{s/6}{s+4} \end{aligned}$$



Special *RLC* Functions (3)
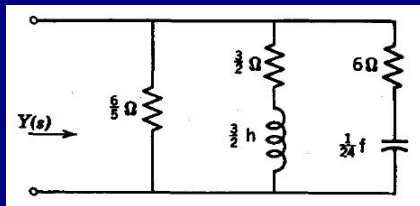
$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)} = \frac{5}{6} + \frac{2/3}{s+1} + \frac{s/6}{s+4}$$



Special *RLC* Functions (4)

$$Y(s) = \frac{(s+2)(s+3)}{(s+1)(s+4)}$$


- Sometimes, a mixed CFE can help:

$$\begin{array}{r}
 6 + 5s + s^2 \overline{) 4 + 5s + s^2 \left(\frac{1}{3} \right)} \\
 \underline{4 + \frac{10}{3}s + \frac{8}{3}s^2} \\
 \frac{1}{3}s + \frac{1}{3}s^2 \overline{) 6 + 5s + s^2 \left(\frac{18}{5}s \right)} \\
 \underline{6 + \frac{8}{3}s} \\
 \frac{10}{3}s + s^2 \overline{) \frac{1}{3}s^2 + \frac{8}{3}s \left(\frac{1}{3} \right)} \\
 \underline{\frac{1}{3}s^2 + \frac{10}{9}s} \\
 \frac{8}{15}s \overline{) \frac{8}{15}s + s^2 \left(\frac{12}{15} \right)} \\
 \underline{\frac{8}{15}s} \\
 s^2 \overline{) \frac{8}{15}s \left(\frac{6}{15}s \right)} \\
 \underline{\frac{8}{15}s} \\
 \underline{\underline{\frac{8}{15}s}}
 \end{array}$$




Special RLC Functions (5)

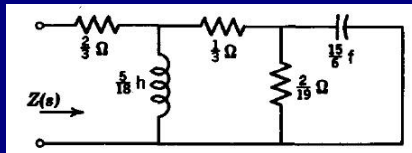- Observe a reversal of the order of polynomials involved.
- Realisation:



Special *RLC* Functions (5)

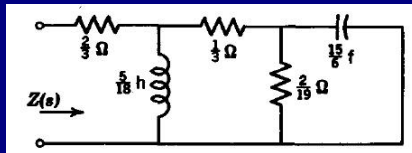- Observe a reversal of the order of polynomials involved.
- Realisation:



- Moral: For a PR function, if it is not synthesisable using only two kinds of elements, still try a PFE or a CFE. It may still work out with three kinds of elements.
- Appears (with the current level of knowledge that has been gathered) to be more of an art than science.

