

DATE

## Experiment No - 10

### Design of Counters using Xilinx Vivado Tool

#### (i) Asynchronous Counter.


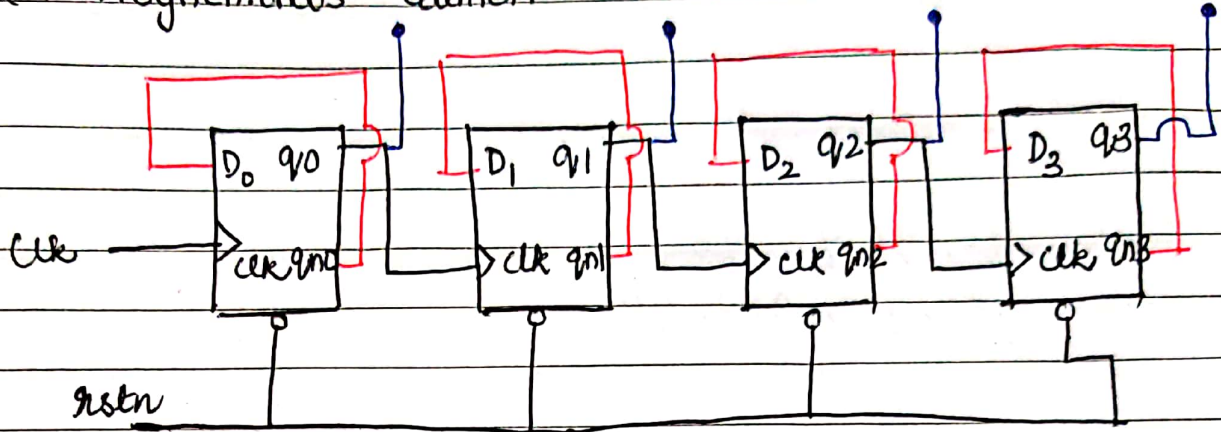


Fig: Asynchronous Down Counter
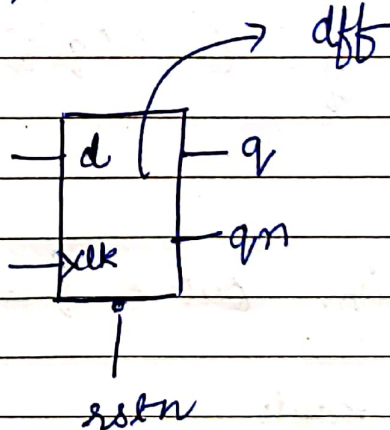
#### Verilog Code (Structural Style)

```
module dff (d, clk, rstn, q, qn);
    input d, clk, rstn;
    output q, qn;
    reg q, qn;
    always @ (posedge clk or negedge rstn)
    begin
        if (!rstn)
            q <= 0;
        else
            q <= d;
        end
        assign qn = ~q;
    endmodule
```



Verilog code for asynchronous Counter

```
module asynchronous (clk, rstn, out);  
input clk, rstn;  
output [3:0] out;
```

```
wire q0, q1, q2, q3;
```

```
wire qn0, qn1, qn2, qn3;
```

```
dff ffo (.d(qn0), .clk(clk), .rstn(rstn), .q(q0),  
        .qn(qn0));
```

```
dff ff1 (.d(qn1), .clk(q0), .rstn(rstn), .q(q1),  
        .qn(qn1));
```

```
dff ff2 (.d(qn2), .clk(q1), .rstn(rstn), .q(q2),  
        .qn(qn2));
```

```
dff ff3 (.d(qn3), .clk(q2), .rstn(rstn), .q(q3),  
        .qn(qn3));
```

```
assign out = { q3, q2, q1, q0 };
```

```
endmodule
```

Test Bench

```
module asynchronous_tb,  
    reg clk, rstn;  
    wire [3:0] out;
```

```
    asynchronous_dut (clk, rstn, out);
```

```
    initial
```

```
    begin
```

```
        rstn = 0;
```

```
        clk = 0;
```


```
        #20 rstn = 1;
```

```
    end
```

```
    always
```

```
        #5 clk = ~clk;
```

```
endmodule.
```

 




## (ii) Synchronous Counters

→ [up down counter]

→ Behavioural style

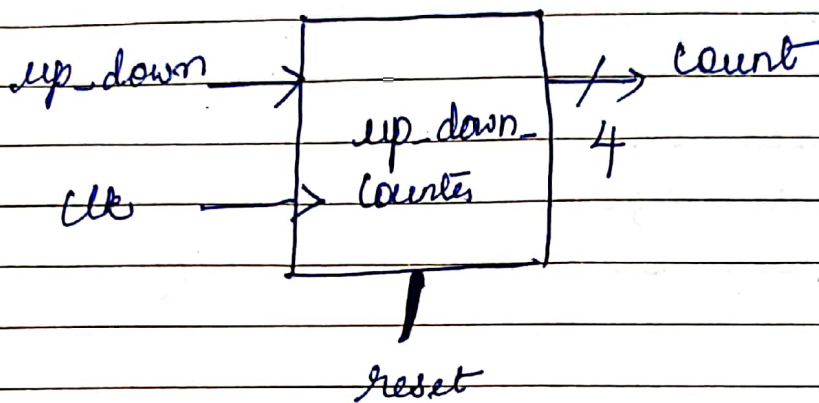Verilog Code for Synchronous up-down counter

```

module up-down-counter (up-down, clk, reset,
                        count);

```

```

    input up-down, clk, reset;

```

```

    output [3:0] count;

```

```

    reg [3:0] count-up-down;

```

*Am registering a temporary variable*

```

    always@ (posedge clk or posedge reset)
    begin

```

```

        if (reset)

```

```

            count-up-down <= 4'h0;

```

DATE

else if (up-down)

count-up-down  $\leq$  count-up-down + 4'd1;

else

count-up-down  $\leq$  count-up-down - 4'd1;

end

assign count = count-up-down;

endmodule

### Test Bench code

```
module up-down-counter_tb;  
  reg clk, reset, up-down;  
  wire [3:0] count;
```

```
  up-down-counter dut(up-down, clk, reset,  
                      count);
```

initial

begin

clk = 0;

forever #5 clk = ~clk;

end

initial

begin

reset = 1;

up\_down = 0;

#20 reset = 0;

#200 up\_down = 1;


end

endmodule

### 3 Any Sequence Counter

→ To count the sequence 0, 2, 4, 6.

#### 1 State diagram

 

I will choose D-fl for the design of any sequence counter.



## State table

Present state  
 $q_2 q_1 q_0$ Next state  
 $q_2 q_1 q_0$ flip flop input  
equations  
 $d_0 d_1 d_2$ 

0 0 0

0 1 0

0 1 0

0 0 1

0 1 0

1 0 0

1 0 0

0 1 1

1 0 0

1 1 0

1 1 0

1 0 1

1 1 0

0 0 0

0 0 0

1 1 1

~~$d_0$~~

		$q_1 q_0$	00	01	11	10
$q_2$	0		0	x	x	1
	1		1	x	x	0

$\rightarrow \bar{q}_2 q_1$

$q_2 \bar{q}_1 = \bar{q}_2 q_1 + q_2 \bar{q}_1 = q_2 \oplus q_1$

$$d_0 = q_2 \oplus q_1 \rightarrow \text{equ (1)}$$

~~$d_1$~~

		$q_1 q_0$	00	01	11	10
$q_2$	0		1	x	x	0
	1		1	x	x	0

$\rightarrow \bar{q}_1 \bar{q}_0$

$$d_1 = \bar{q}_1 \bar{q}_0 \rightarrow \text{equ (2)}$$

 $q_1$ 

$$d_1 = \bar{q}_1 \rightarrow \text{equ (2)}$$

~~$d_2$~~

		$q_1 q_2$	00	01	11	10
$q_0$	0		0	x	x	0
	1		0	x	x	0

$$d_2 = 0 \rightarrow \text{equ (3)}$$

Verilog code for anysequence counter

```
module anysequencecounter ( q, rst, clk );
```

```
input clk, rst;
```

```
output [2:0] q;
```

```
reg q;
```

```
wire [2:0] d;
```

```
assign d[0] = q[2] ^ q[1];
```

```
assign d[1] = ~(q[1] & q[2]) ^ q[1];
```

```
assign d[2] = 1'b0;
```

```
always @ (posedge clk or negedge rst)
```

```
begin
```

```
if (!rst)
```

```
q <= 1'b0;
```

```
else
```

```
q <= d;
```

```
end
```

```
endmodule
```