

Chapter 6: Frequency Response of Amplifiers

6.1 Basic Current Mirrors

6.2 Common-Source Stage

6.3 Source Followers


6.4 Common-Gate Stage

6.5 Cascode Stage

6.6 Differential Pair


6.7 Gain-Bandwidth Trade-Offs

General Considerations

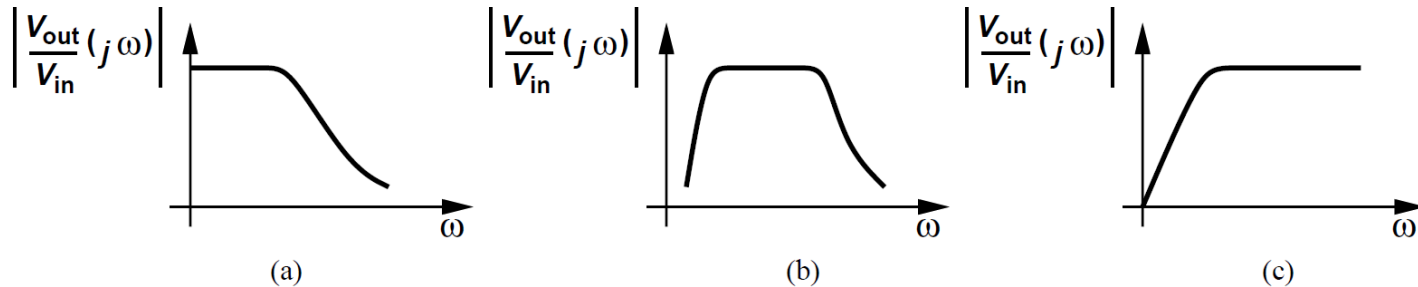


- In this chapter, we are primarily interested in the magnitude of the transfer function.
- The magnitude of a complex number $a + jb$ is given by $\sqrt{a^2 + b^2}$
- Zeros and poles are respectively defined as the roots of the numerator and denominator of the transfer function.

Miller effect

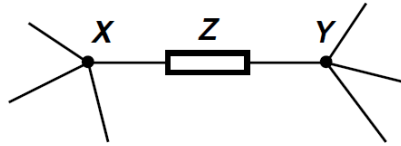

(a)

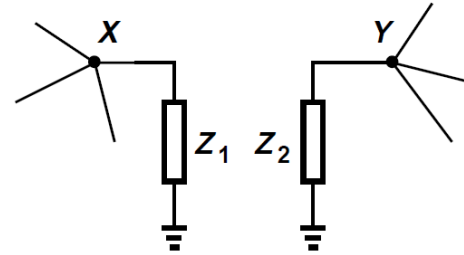

(b)


- If the circuit of Fig (a) can be converted to that of Fig (b), then

$$Z_1 = Z / (1 - A_v)$$


$$Z_2 = Z / (1 - A_v^{-1})$$

$$A_v = V_Y / V_X$$

Example

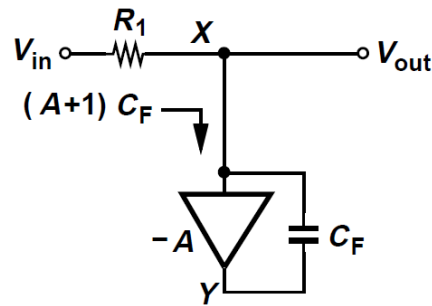


(a)

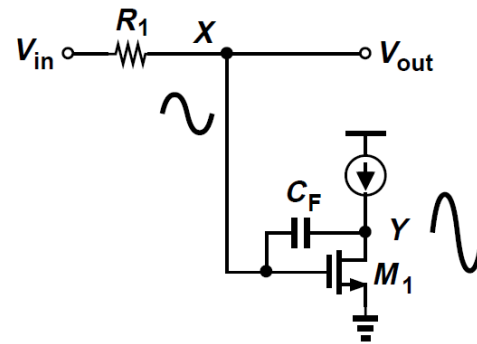


(b)

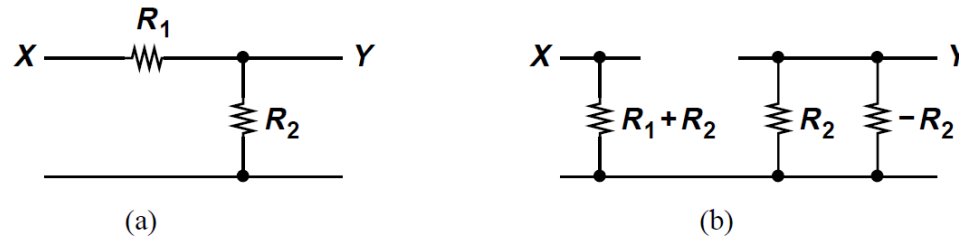- A student needs a large Capacitor and decides to utilize the Miller multiplication
- What is the issues in this approach?



Improper application of Miller's theorem

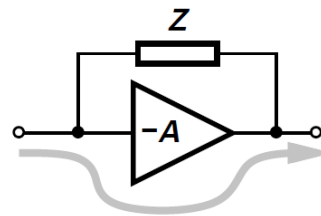


Main Signal Path


Typical case for valid application of Miller's theorem.

- **Miller's theorem does not stipulate the conditions under which this conversion is valid.**
- **If the impedance Z forms the only signal path between X and Y , then the conversion is often invalid.**

Example

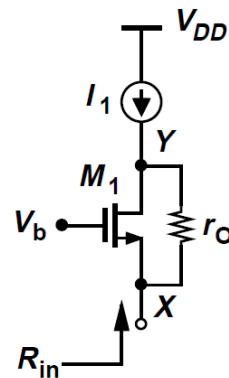

(a)

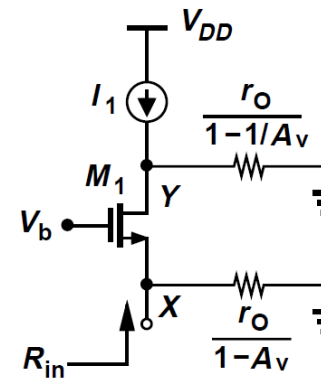


(b)

- Calculate the input resistance of the circuit shown.
- Since A_v is usually greater than unity, $r_O/(1 - A_v)$ is a negative resistance.
- $A_v = 1 + (g_m + g_{mb})r_O$


$$\begin{aligned}
 R_{in} &= \frac{r_O}{1 - [1 + (g_m + g_{mb})r_O]} \parallel \frac{1}{g_m + g_{mb}} \\
 &= \frac{-1}{g_m + g_{mb}} \parallel \frac{1}{g_m + g_{mb}} \\
 &= \infty.
 \end{aligned}$$

Example

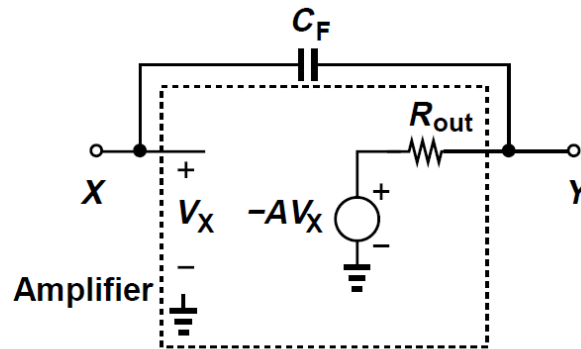

- The value of $A_v = V_Y / V_X$ must be calculated at the frequency of interest.
- In the figure, the equivalent circuit $V_Y \neq -AV_X$ that at high frequencies.
- In many cases we use the low-frequency value of V_Y / V_X to gain insight.
- We call this approach “Miller’s approximation.”

Example

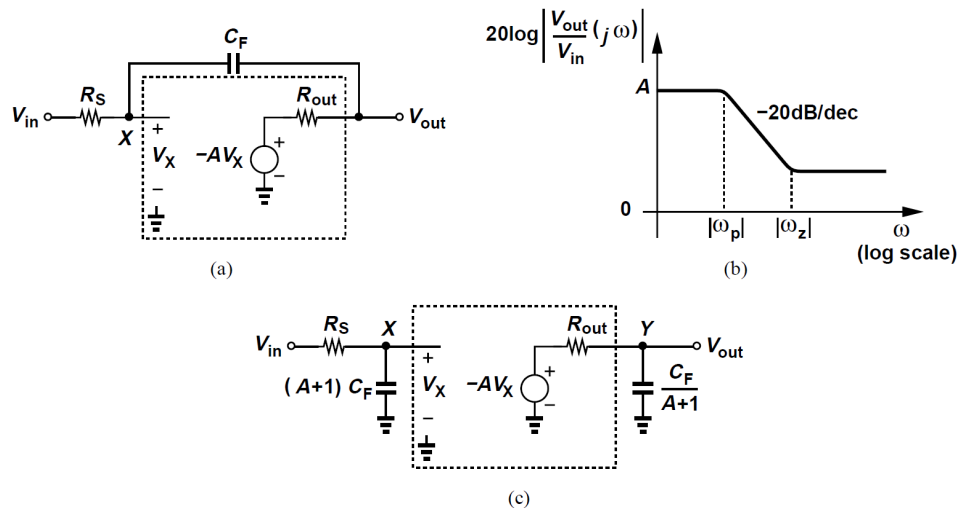

- **Direct Calculation:**


$$\frac{V_{out}}{V_{in}}(s) = \frac{R_{out}C_F s - A}{[(A+1)R_S + R_{out}]C_F s + 1}$$

- **Miller Approximation:**


$$\frac{V_{out}}{V_{in}}(s) = \frac{-A}{[(1+A)R_S C_F s + 1] \left(\frac{1}{1+A^{-1}} C_F R_{out} s + 1 \right)}$$

- **Miller's approximation has eliminated the zero and predicted two poles for the circuit!**

Example

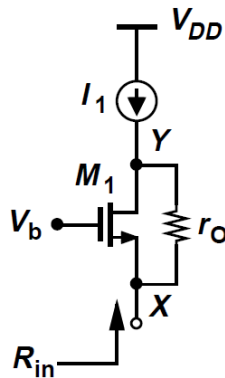

(a)

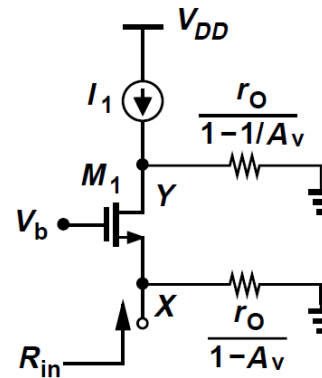


(b)

$$\begin{aligned}
 R_{out} &= \frac{r_O}{1 - 1/A_v} \\
 &= \frac{r_O}{1 - [1 + (g_m + g_{mb})r_O]^{-1}} \\
 &= \frac{1}{g_m + g_{mb}} + r_O,
 \end{aligned}$$

- Actual Rout = r0
- Miller's approximation:
- (1) it may eliminate zeros
- (2) it may predict additional poles
- (3) it does not correctly compute the "output" impedance.


Association of Poles with Nodes

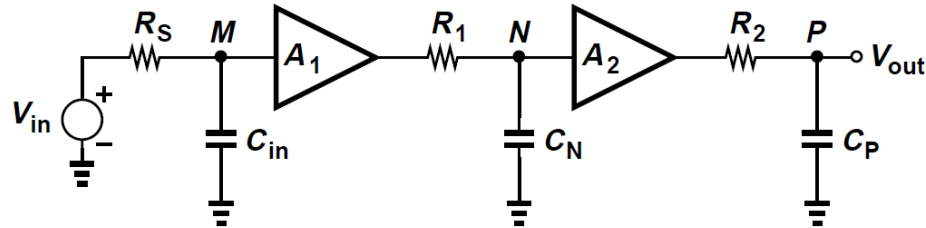


- The overall transfer function can be written as

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + R_S C_{in} s} \cdot \frac{A_2}{1 + R_1 C_N s} \cdot \frac{1}{1 + R_2 C_P s}$$

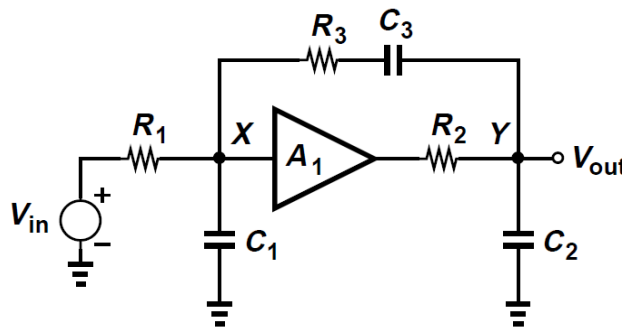- Each node in the circuit contributes one pole to the transfer function.
- Not valid in general. Example:



Example

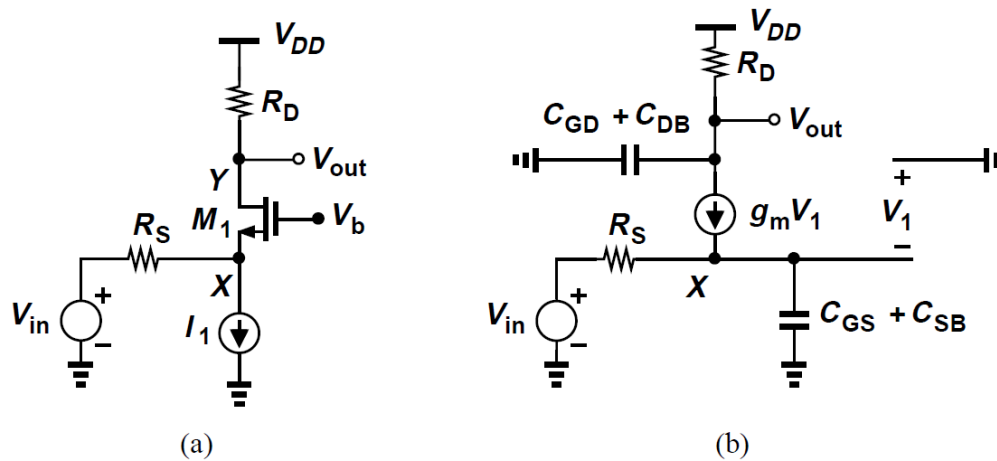

- At node X:

$$\omega_{in} = \left[(C_{GS} + C_{SB}) \left(R_S \parallel \frac{1}{g_m + g_{mb}} \right) \right]^{-1}$$


- At node Y:

$$\omega_{out} = [(C_{DG} + C_{DB})R_D]^{-1}$$


- The overall transfer function:

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \cdot \frac{1}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$

Common-Source Stage

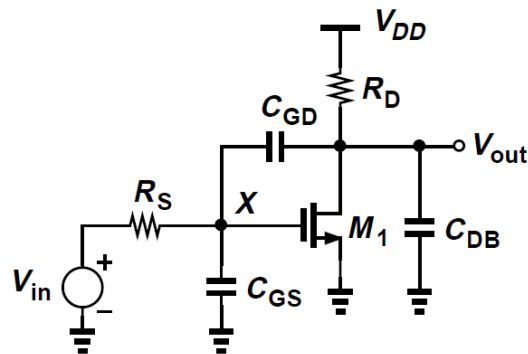

(a)

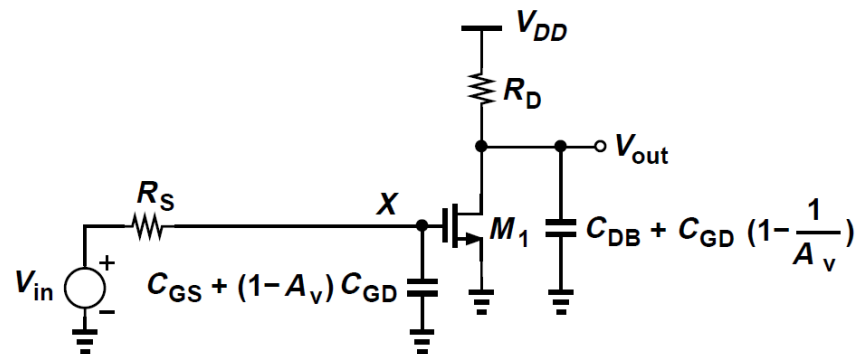

(b)

- The magnitude of the “input” pole


$$\omega_{in} = \frac{1}{R_S [C_{GS} + (1 + g_m R_D) C_{GD}]}$$

- At the output node

$$\omega_{out} = \frac{1}{R_D (C_{DB} + C_{GD})}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$

Direct Analysis

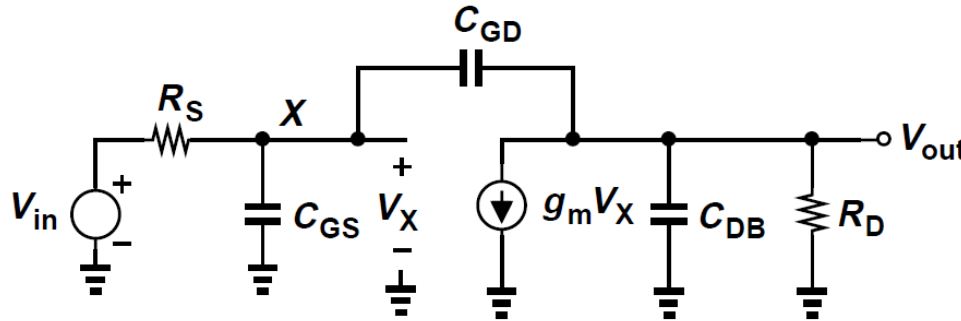


$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{R_S R_D s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

- While the denominator appears rather complicated, it can yield intuitive expressions for the two poles. $|\omega_{p1}| \ll |\omega_{p2}|$
- “Dominant pole” approximation.


$$\omega_{p1} = \frac{1}{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}$$

- The intuitive approach provides a rough estimate with much less effort.

Example

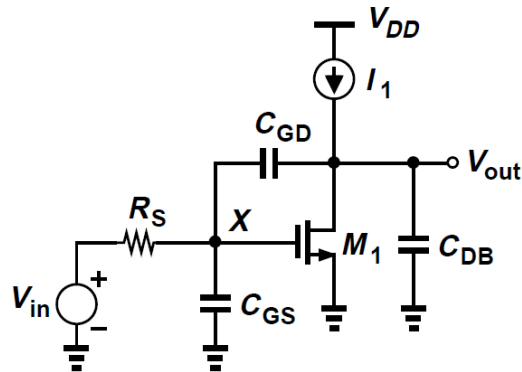

(a)

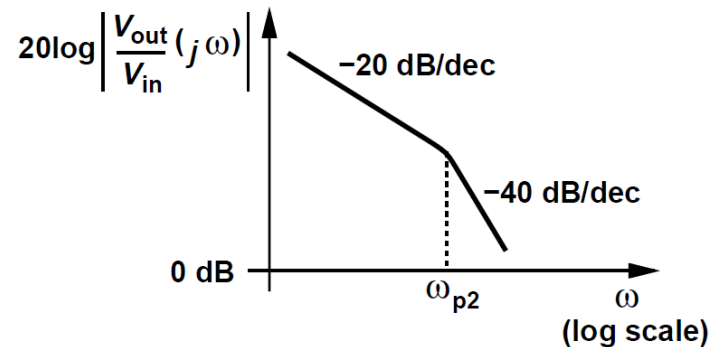

(b)



$$\begin{aligned} \frac{V_{out}}{V_{in}}(s) &= \frac{C_{GD}s - g_m}{R_S \xi s^2 + [g_m R_S C_{GD} + (C_{GD} + C_{DB})]s} \\ &= \frac{C_{GD}s - g_m}{s[R_S(C_{GS}C_{GD} + C_{GS}C_{DB} + C_{GD}C_{DB})s + (g_m R_S + 1)C_{GD} + C_{DB}]} \end{aligned}$$

- One pole is at the origin because the dc gain is infinity.
- For a large CDB or load capacitance

$$\omega_{p2} \approx \frac{1}{R_S(C_{GS} + C_{GD})}$$

- No miller multiplication. Why?

Zero in Transfer Function

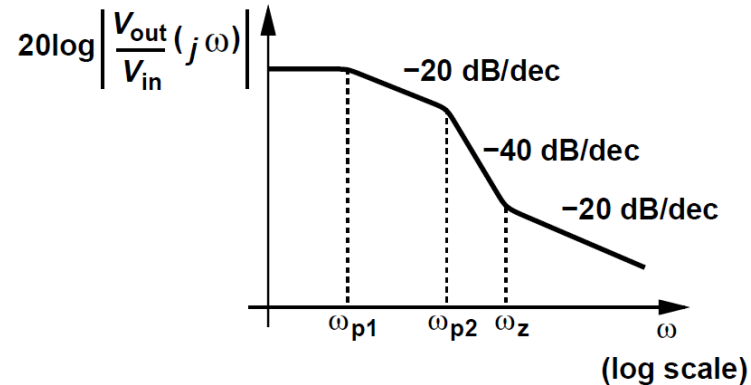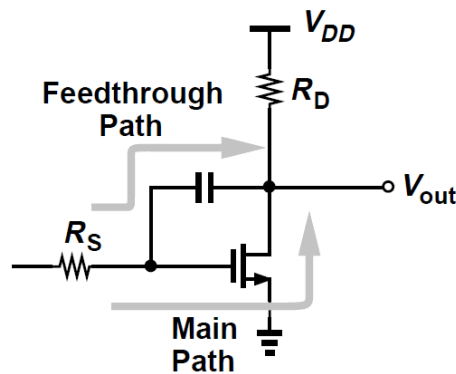


$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{GD}s - g_m)R_D}{R_S R_D s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

- The transfer function of exhibits a zero given by

$$\omega_z = +g_m / C_{GD}$$

- C_{GD} provides a feedthrough path that conducts the input signal to the output at very high frequencies.

Calculating zero in a CS stage

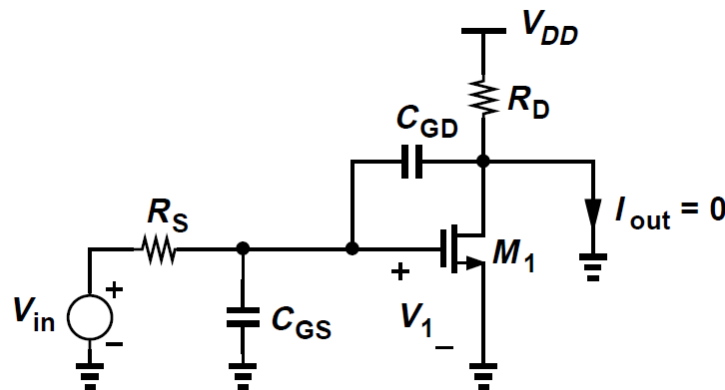


- The transfer function $V_{out}(s) = V_{in}(s)$ must drop to zero for $s = s_z$.
- Therefore, the currents through C_{GD} and M_1 are equal and opposite:

$$V_1 C_{GD} s_z = g_m V_1$$

- That is $s_z = +g_m / C_{GD}$

Example

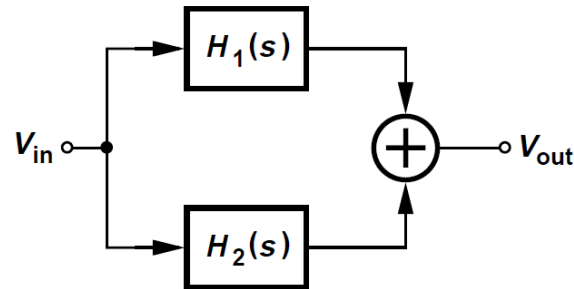


- Can this (the zero) occur if $H_1(s)$ and $H_2(s)$ are first-order low-pass circuits?
- $H_1 = A_1 / (1 + s/\omega_{p1})$ and $H_2 = A_2 / (1 + s/\omega_{p2})$

$$\frac{V_{out}}{V_{in}}(s) = \frac{\left(\frac{A_1}{\omega_{p2}} + \frac{A_2}{\omega_{p1}}\right)s + A_1 + A_2}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$


- The overall transfer function contains a zero.

Example

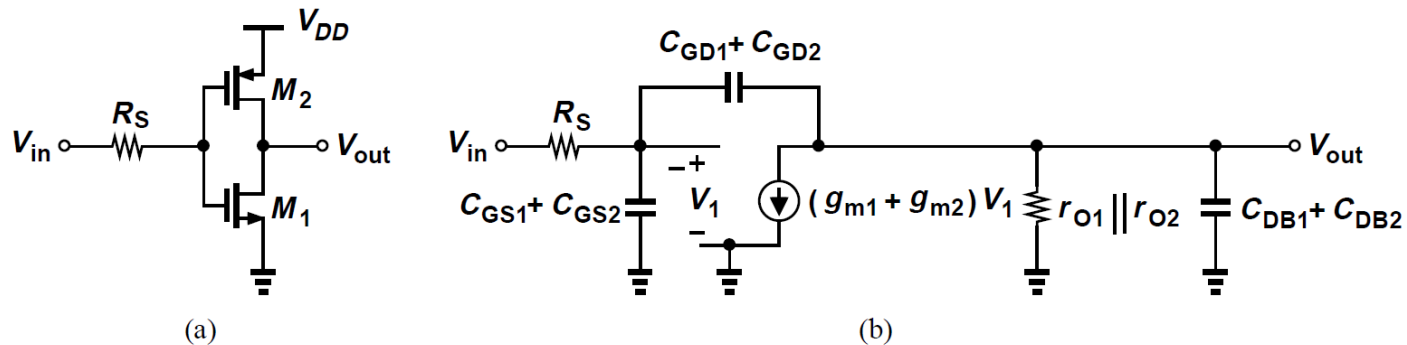

- Since the corresponding terminals of M_1 and M_2 are shorted to one another in the small-signal model, we merge the two transistors.
- The circuit thus has the same transfer function as the simple CS stage.

Miller's Approximation

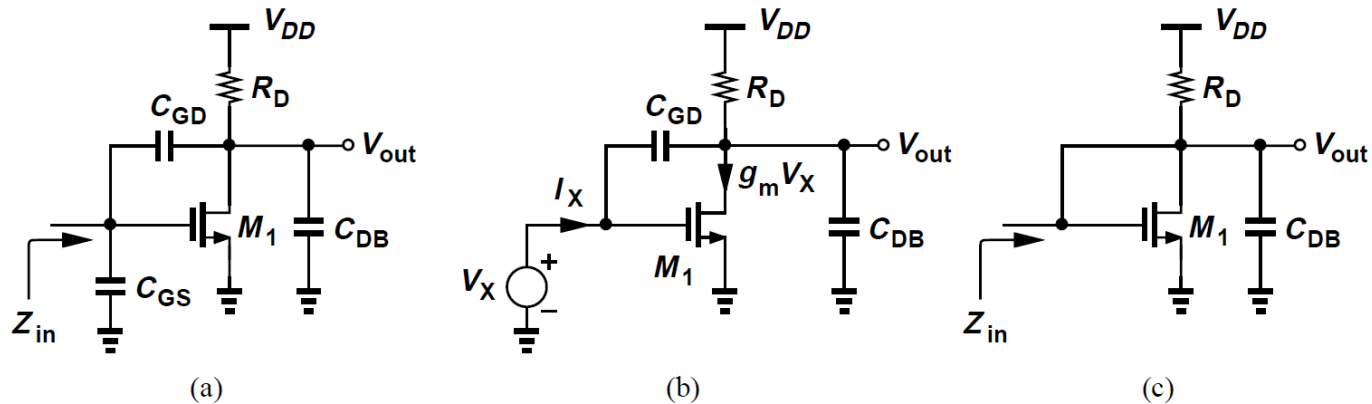

- With the aid of Miller's approximation,


$$Z_{in} = \frac{1}{[C_{GS} + (1 + g_m R_D)C_{GD}]s}$$

- But at high frequencies, the effect of the output node capacitance must be taken into account.
- Ignore C_{GS}


$$\frac{V_X}{I_X} = \frac{1 + R_D(C_{GD} + C_{DB})s}{C_{GD}s(1 + g_m R_D + R_D C_{DB}s)}$$

- if C_{GD} is large, it provides a low impedance path between the gate and drain of M_1 .

Source Followers

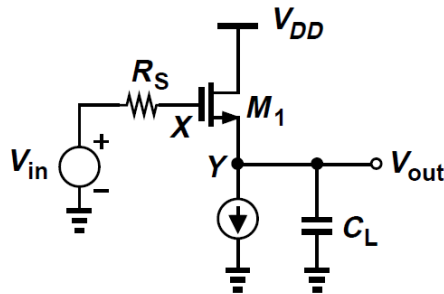

(a)

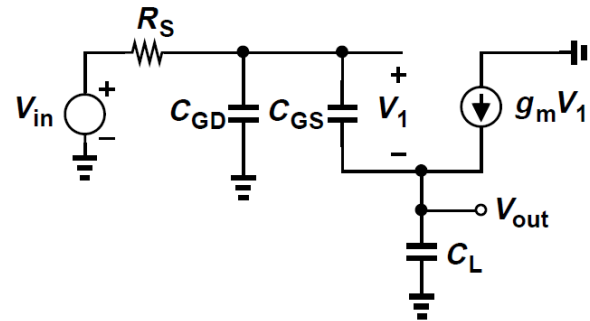


(b)

- The strong interaction between nodes X and Y through C_{GS} makes it difficult to associate a pole with each node.


$$\frac{V_{out}}{V_{in}}(s) = \frac{g_m + C_{GS}s}{R_S(C_{GS}C_L + C_{GS}C_{GD} + C_{GD}C_L)s^2 + (g_m R_S C_{GD} + C_L + C_{GS})s + g_m}$$

- Contains a zero in the left half plane. Why?

Example

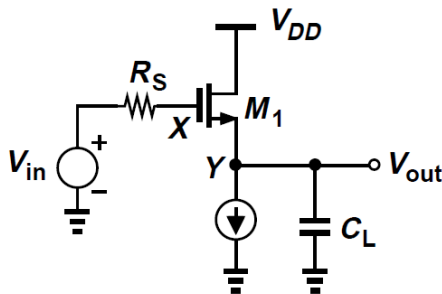

(a)

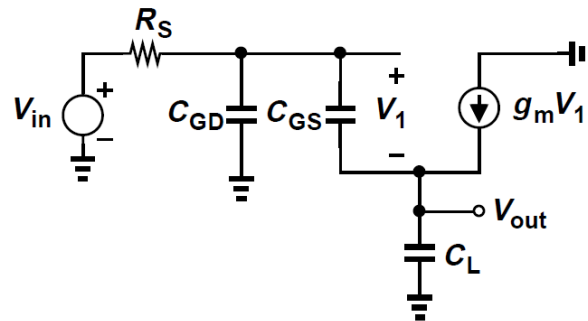


(b)

- Transfer function if $C_L = 0$?

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{g_m + C_{GS}s}{R_S C_{GS} C_{GD} s^2 + (g_m R_S C_{GD} + C_{GS})s + g_m} \\ &= \frac{g_m + C_{GS}s}{(1 + R_S C_{GD}s)(g_m + C_{GS}s)} \\ &= \frac{1}{1 + R_S C_{GD}s}. \end{aligned}$$

- C_{GS} disappear
- In the absence of channel-length modulation and body effect, the voltage gain from the gate to the source is equal to unity.

Input impedance

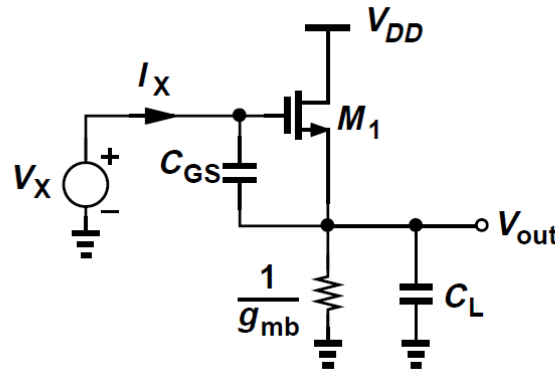


- C_{GD} simply shunts the input and can be ignored initially.

$$Z_{in} = \frac{1}{C_{GS}s} + \left(1 + \frac{g_m}{C_{GS}s}\right) \frac{1}{g_{mb} + C_L s}$$

- If $g_{mb} = 0$ and $C_L = 0$, then $Z_{in} = \infty$
- C_{GS} is entirely bootstrapped by the source follower and draws no current from the input.
- At Low frequency the overall input capacitance is equal to C_{GD} plus a fraction of C_{GS} .

$$Z_{in} \approx \frac{1}{C_{GS}s} \left(1 + \frac{g_m}{g_{mb}}\right) + \frac{1}{g_{mb}}$$

Input Impedance



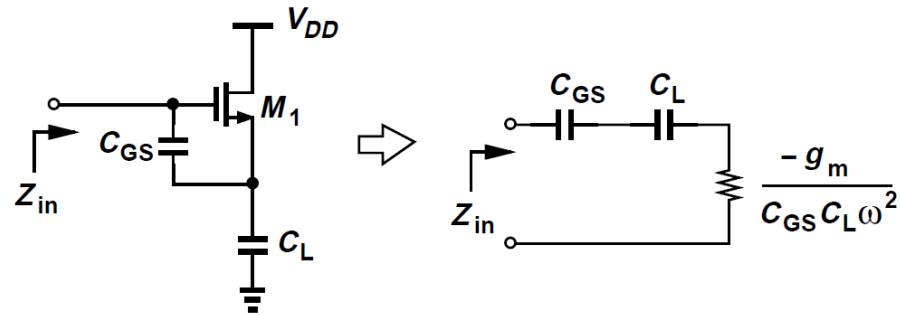


- At high frequencies, $g_{mb} \ll |C_L s|$

$$Z_{in} \approx \frac{1}{C_{GS}s} + \frac{1}{C_L s} + \frac{g_m}{C_{GS}C_L s^2}$$

- A source follower driving a load capacitance exhibits a negative input resistance, possibly causing instability.

Output Impedance

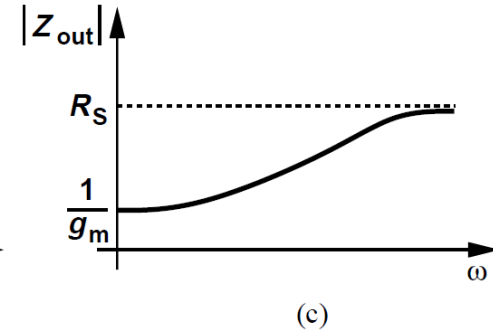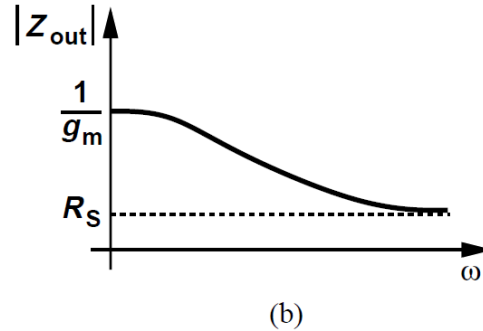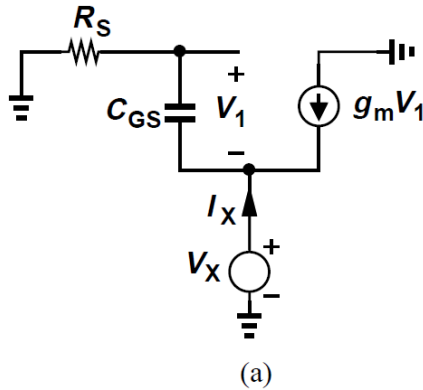


$$Z_{out} = \frac{V_X}{I_X}$$

$$= \frac{R_S C_{GS} s + 1}{g_m + C_{GS} s}$$

- **At low frequency:** $Z_{out} \approx 1/g_m$
- **At very high frequencies,** $Z_{out} \approx R_S$
- **Because C_{GS} shorts the gate and the source.**
- **Which one of these variations is more realistic?**

Output Impedance

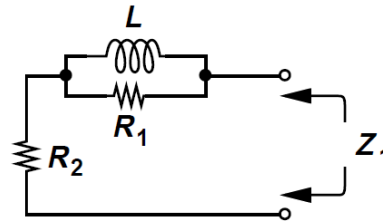

1. Equivalent output impedance of a source follower


- Since the output impedance increases with frequency, we postulate that it contains an inductive component.

$$Z_{out} - \frac{1}{g_m} = \frac{C_{GS}s \left(R_S - \frac{1}{g_m} \right)}{g_m + C_{GS}s}$$


$$\frac{1}{Z_{out} - \frac{1}{g_m}} = \frac{1}{R_S - \frac{1}{g_m}} + \frac{1}{\frac{C_{GS}s}{g_m} \left(R_S - \frac{1}{g_m} \right)}$$

$$L = \frac{C_{GS}}{g_m} \left(R_S - \frac{1}{g_m} \right)$$

Example

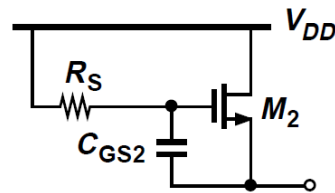


(a)

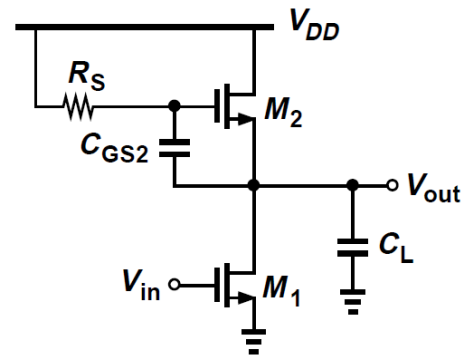

(b)

- Can we construct a (two-terminal) inductor from a source follower?
- Yes, but non-ideal.
- It also incurs a parallel resistance and a series resistance.
- The inductance can partially cancel the load capacitance, C_L , at high frequencies, thus extending the bandwidth.

Common-Gate Stage

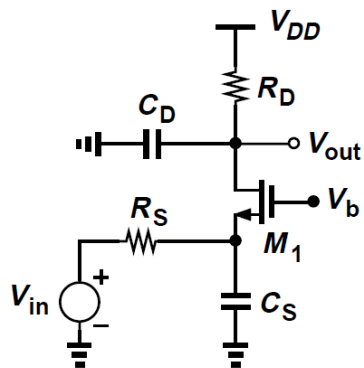


Common-gate stage at high frequencies

- **A transfer function**

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{mb})R_D}{1 + (g_m + g_{mb})R_S} \frac{1}{\left(1 + \frac{C_S}{g_m + g_{mb} + R_S^{-1}}s\right)(1 + R_D C_D s)}$$

- **No Miller multiplication of capacitances.**
- **R_D is typically maximized, so the dc level of the input signal must be quite low.**
- **As an amplifier in cases where a low input impedance is required**
- **In cascode stages.**

Example

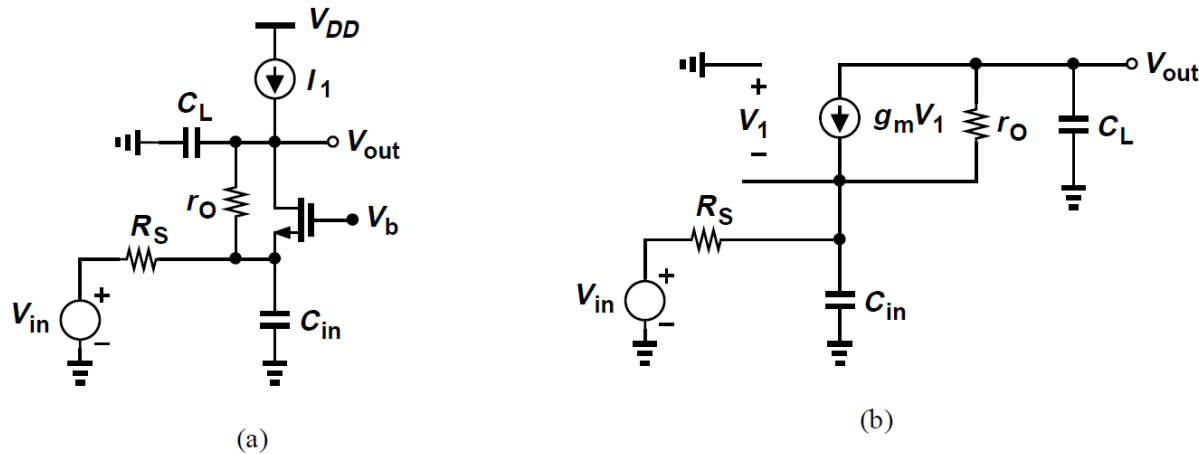


- Why Z_{in} becomes independent of C_L as this capacitance increases?

$$Z_{in} = \frac{1}{g_m + g_{mb}} + \frac{1}{C_L s} \cdot \frac{1}{(g_m + g_{mb})r_O}$$

- As C_L or s increases, Z_{in} approaches $1/(g_m + g_{mb})$
- C_L lowers the voltage gain of the circuit, thereby suppressing the effect of the negative resistance introduced by Miller effect through r_O .

CG Stage

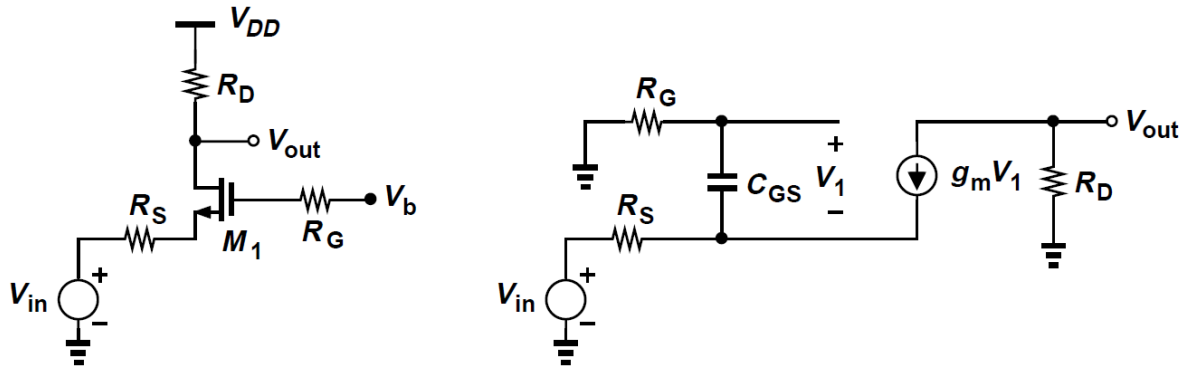


- The bias network providing the gate voltage exhibits a finite impedance.
- Consider only C_{GS} here.

$$\frac{V_{out}}{V_{in}} = \frac{g_m R_D}{(R_G + R_S)C_{GS}s + 1 + g_m R_S},$$

$$\omega_p = \frac{1 + g_m R_S}{(R_G + R_S)C_{GS}}.$$

- Lowering the pole magnitude.
- Output impedance of the circuit drops at high frequencies.

Cascode Stage

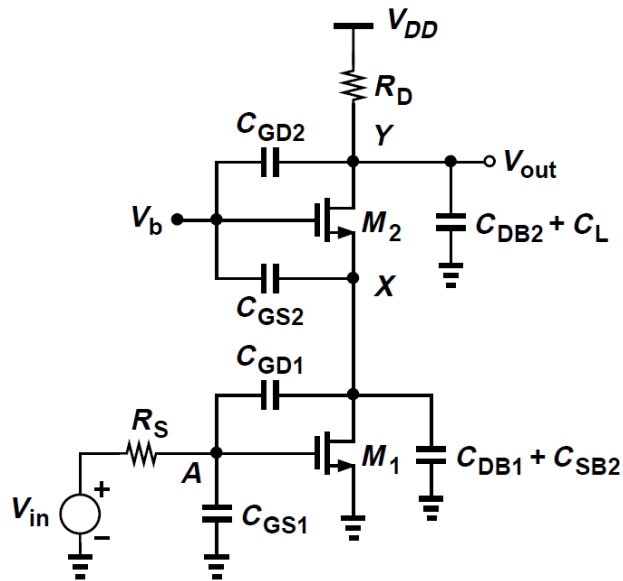

$$\omega_{p,A} = \frac{1}{R_S \left[C_{GS1} + \left(1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{GD1} \right]}$$


$$\omega_{p,X} = \frac{g_{m2} + g_{mb2}}{2C_{GD1} + C_{DB1} + C_{SB2} + C_{GS2}}$$

$$\omega_{p,Y} = \frac{1}{R_D(C_{DB2} + C_L + C_{GD2})}$$


High-frequency model of a cascode stage.

- **Miller effect is less significant in cascode amplifiers than in common-source stages.**
- **But $\omega_{p,X}$ is typically quite higher than the other two.**
- **What if R_D is replaced by a current source?**
- **Pole at node X may be quite lower, but transfer function will not affect much by this. See example.**

Example

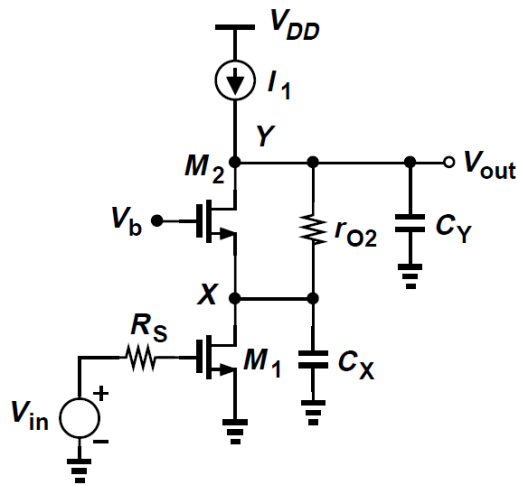

(a)

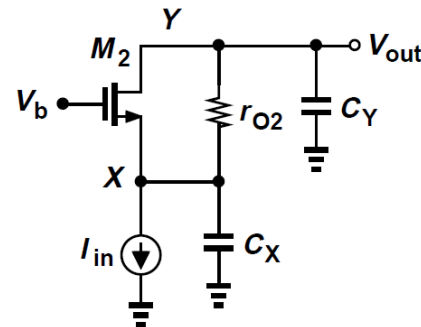

(b)

- Compute the transfer function.


$$\frac{V_{out}}{I_{in}} = -\frac{g_{m2}r_{O2} + 1}{C_X s} \cdot \frac{1}{1 + (1 + g_{m2}r_{O2})\frac{C_Y}{C_X} + C_Y r_{O2} s}$$

- For $g_{m2}r_{O2} \gg 1$

$$\frac{V_{out}}{V_{in}} = -\frac{g_{m1}g_{m2}}{C_Y C_X s} \frac{1}{g_{m2}/C_X + s}$$

- The magnitude of the pole at node X is still given by g_{m2}/C_X . Why?

Differential Pair


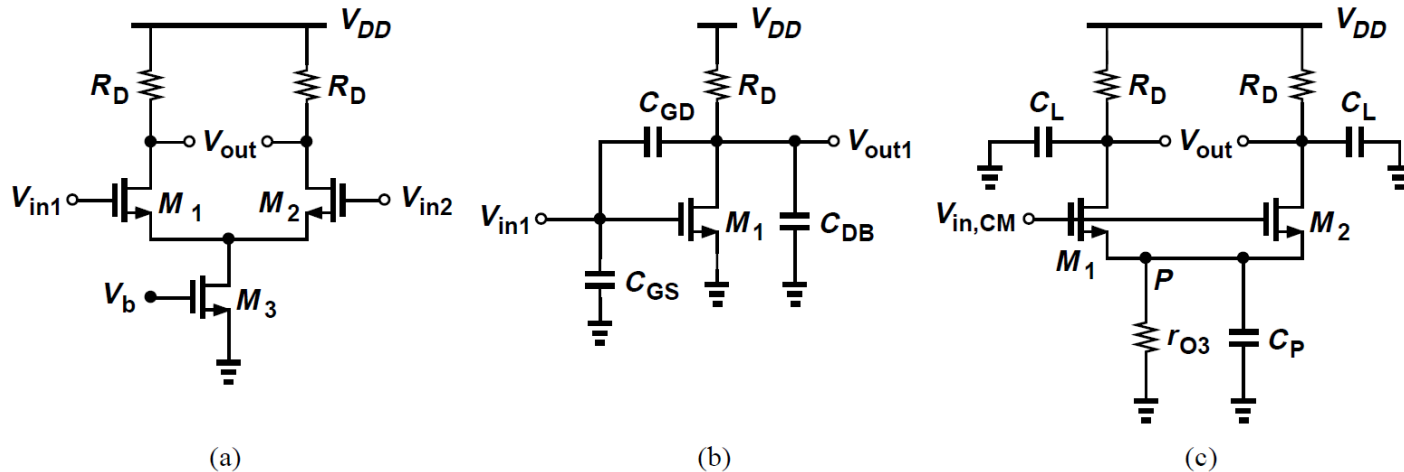


- For differential signals, the response is identical to that of a common-source stage.
- the common-mode rejection of the circuit degrades considerably at high frequencies.

$$A_{v,CM} = - \frac{\Delta g_m \left[R_D \parallel \left(\frac{1}{C_L s} \right) \right]}{(g_{m1} + g_{m2}) \left[r_{O3} \parallel \left(\frac{1}{C_P s} \right) \right] + 1}$$

- Channel-length modulation, body effect, and other capacitances are neglected.


Differential Pair

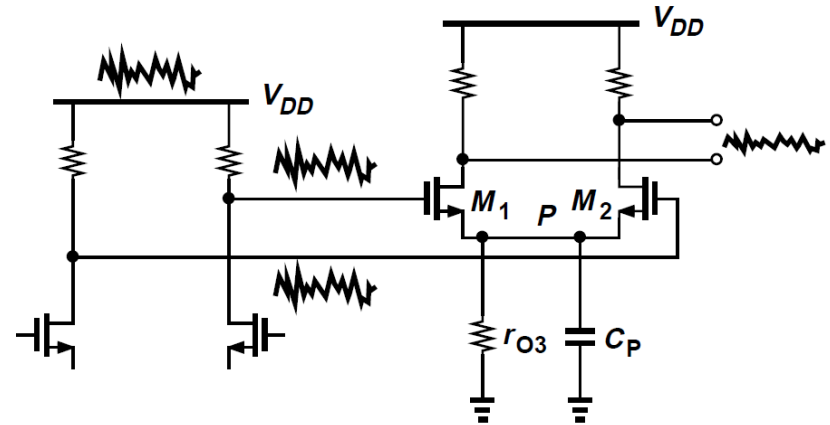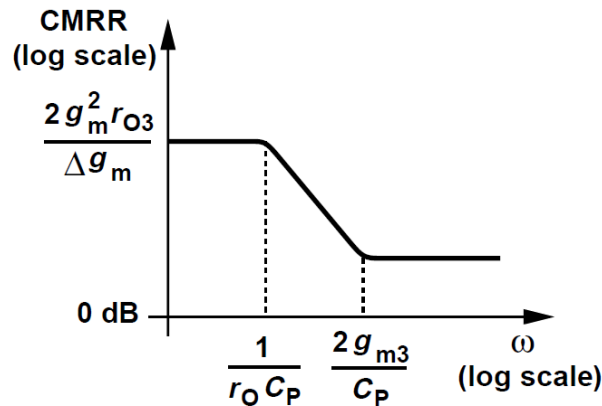

$$\text{CMRR} \approx \frac{g_m}{\Delta g_m} \frac{r_{O3} C_P s + 1 + 2g_m r_{O3}}{r_{O3} C_P s + 1}$$


- This transfer function contains a zero and a pole.
- The magnitude of the zero is much greater than the pole.
- Common-mode disturbance at node P translates to a differential noise component at the output, if the supply voltage contains high-frequency noise and the circuit exhibits mismatches.
- Trade-off between voltage headroom and CMRR.

Diff Pair

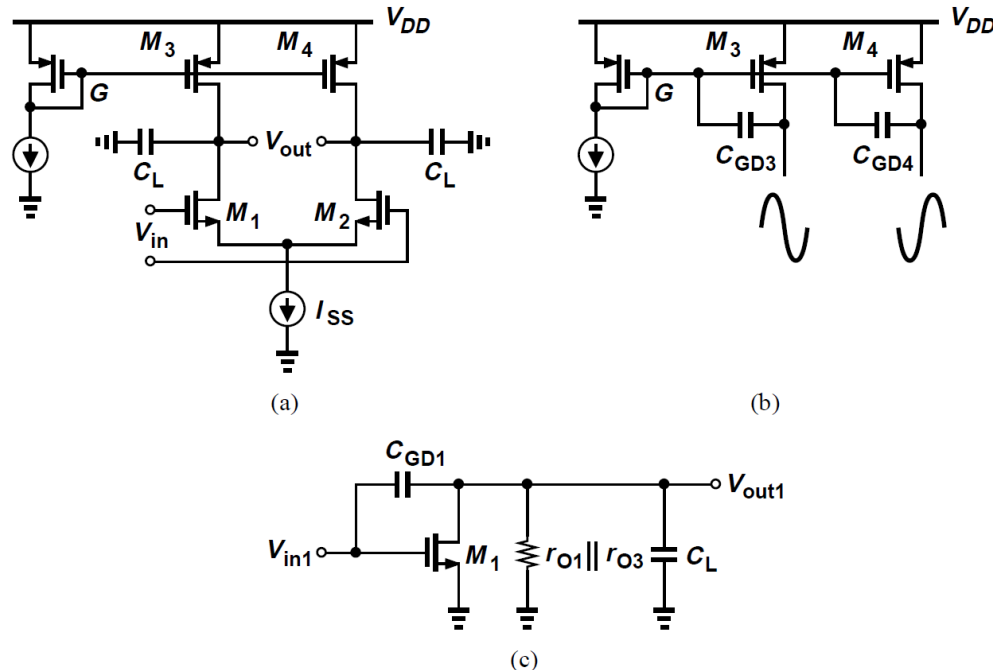



- Frequency response of differential pairs with high-impedance loads.
- Fig (b) C_{GD3} and C_{GD4} conduct equal and opposite currents to node G , making this node an ac ground.
- The differential half circuit is depicted in Fig. (c).
- More on chapter 10

Differential Pair with Active Load

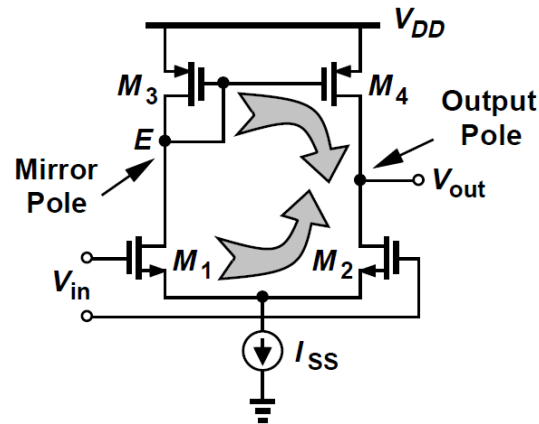

- How many poles does this circuit have?
- The severe trade-off between g_m and CGS of PMOS devices results in a pole that impacts the performance of the circuit.
- The pole associated with node E is called a “mirror pole.”

Active Load

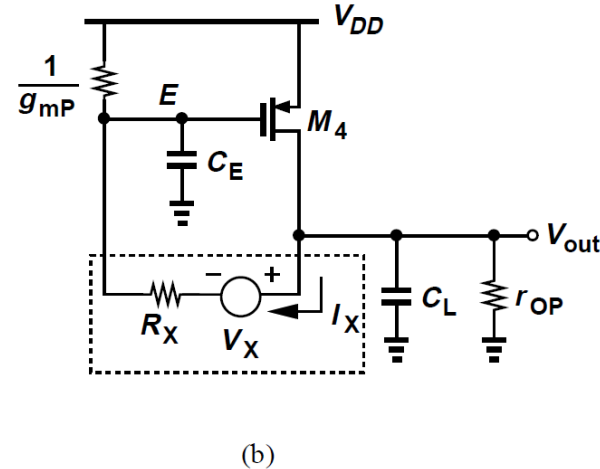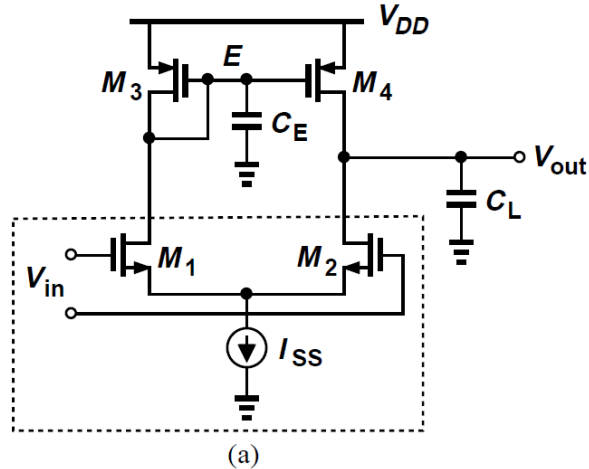

- Replacing V_{in} , M_1 , and M_2 by a Thevenin equivalent.

$$V_X = g_{mN} r_{ON} V_{in}$$

$$R_X = 2r_{ON}$$


$$\frac{V_{out}}{V_{in}}$$

$$= \frac{g_{mN} r_{ON} (2g_{mP} + C_E s) r_{OP}}{2r_{OP} r_{ON} C_E C_L s^2 + [(2r_{ON} + r_{OP}) C_E + r_{OP} (1 + 2g_{mP} r_{ON}) C_L] s + 2g_{mP} (r_{ON} + r_{OP})}$$

$$\omega_{p1} \approx \frac{1}{(r_{ON} \parallel r_{OP}) C_L}$$

$$\omega_{p2} \approx \frac{g_{mP}}{C_E}$$

Active Load

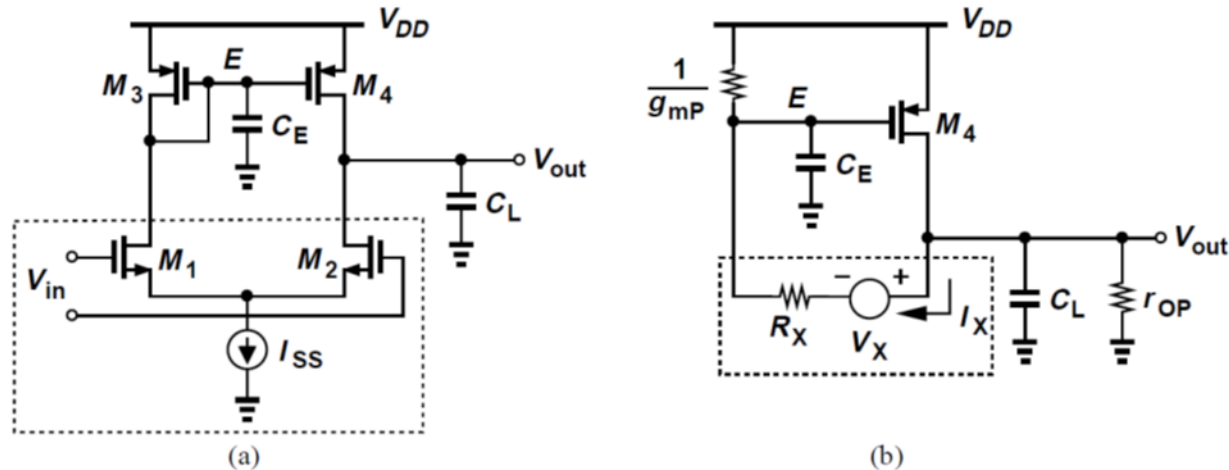


- A zero with a magnitude of $2g_{mP}/C_E$ in the left half plane.
- The appearance of such a zero can be understood by noting that the circuit consists of a “slow path” (M_1, M_3 and M_4) in parallel with a “fast path” (M_1 and M_2) by $A_0/[(1 + s/\omega_{p1})(1 + s/\omega_{p2})]$ and $A_0/(1 + s/\omega_{p1})$

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + s/\omega_{p1}} \left(\frac{1}{1 + s/\omega_{p2}} + 1 \right)$$


$$= \frac{A_0(2 + s/\omega_{p2})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

Example

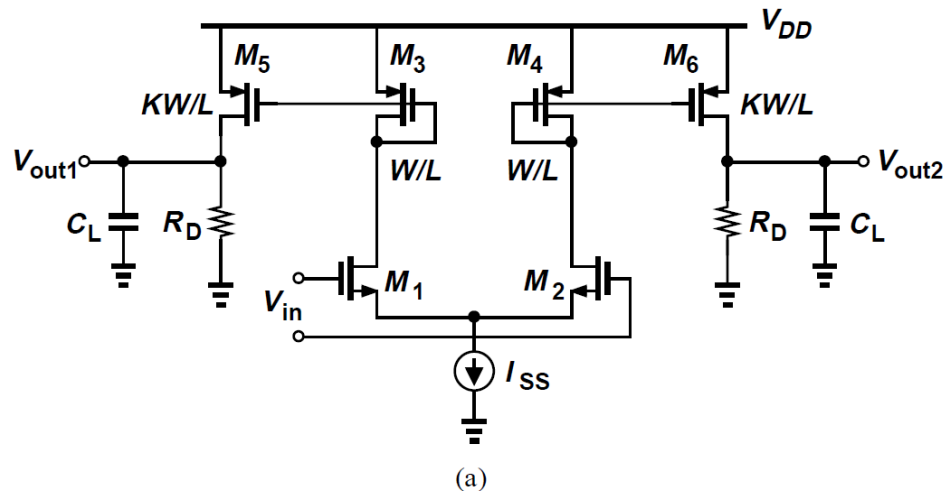


- Not all fully differential circuits are free from mirror poles.
- Estimate the low-frequency gain and the transfer function of this circuit.


Example

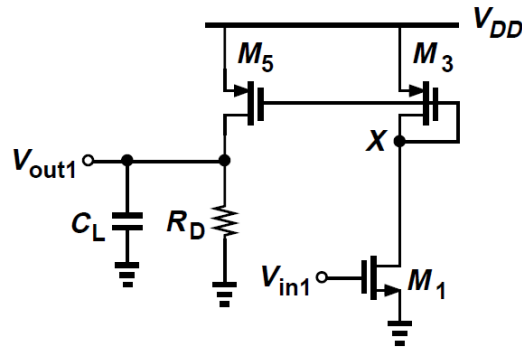

(b)

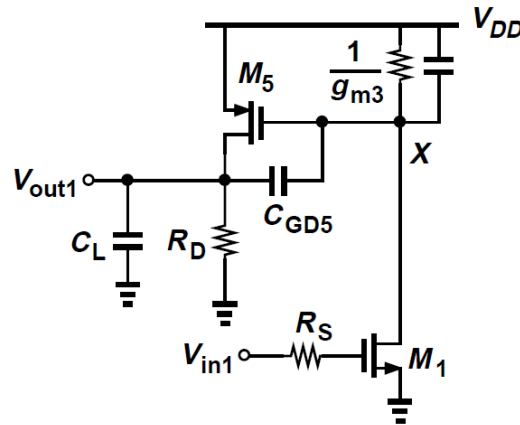

(c)

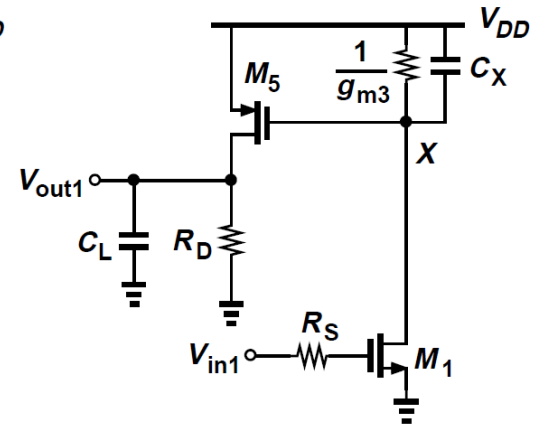

(d)

- M5 multiplies the drain current of M3 by K.

$$A_v = g_{m1} K R_D$$


- Assume $R_D C_L$ is relatively small so that the Miller multiplication of C_{GD5} can be approximated as

$$C_{GD5}(1 + g_{m5} R_D)$$

$$\frac{V_{out1}}{V_X}(s) = -g_{m5} R_D \frac{1}{1 + R_D C_L s}$$


- The overall transfer function is then equal to V_X/V_{in1} multiplied by V_{out1}/V_X .

Gain-Bandwidth Trade-Offs

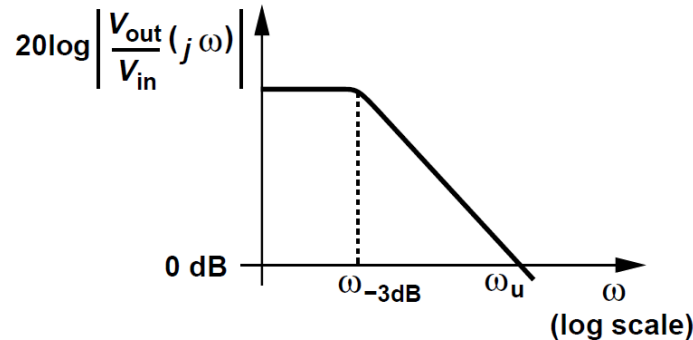

- We wish to maximize both the gain and the bandwidth of amplifiers.
- we are interested in both the 3-dB bandwidth, $\omega_{-3\text{dB}}$ and the “unity-gain” bandwidth, ω_u .


One pole circuit

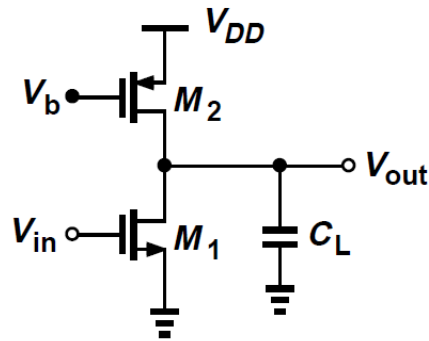

$$\begin{aligned}GBW &= A_0\omega_p \\&= g_{m1}(r_{O1}||r_{O2})\frac{1}{2\pi(r_{O1}||r_{O2})C_L} \\&= \frac{g_{m1}}{2\pi C_L}.\end{aligned}$$

$$\begin{aligned}\omega_u &= \sqrt{A_0^2 - 1}\omega_p \\&\approx A_0\omega_p\end{aligned}$$

Multi-Pole Circuits

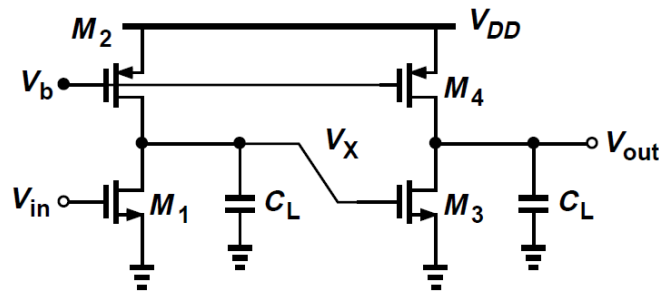

- It is possible to increase the GBW product by cascading two or more gain stages.
- Assume the two stages are identical and neglect other capacitances.


$$\frac{V_{out}}{V_{in}} = \frac{A_0^2}{\left(1 + \frac{s}{\omega_p}\right)^2}$$

$$\begin{aligned}\omega_{-3-dB} &= \sqrt{\sqrt{2} - 1} \omega_p \\ &\approx 0.64 \omega_p.\end{aligned}$$

$$GBW = \sqrt{\sqrt{2} - 1} A_0^2 \omega_p$$

- While raising the GBW product, cascading reduces the bandwidth.

Appendix A: Extra Element Theorem

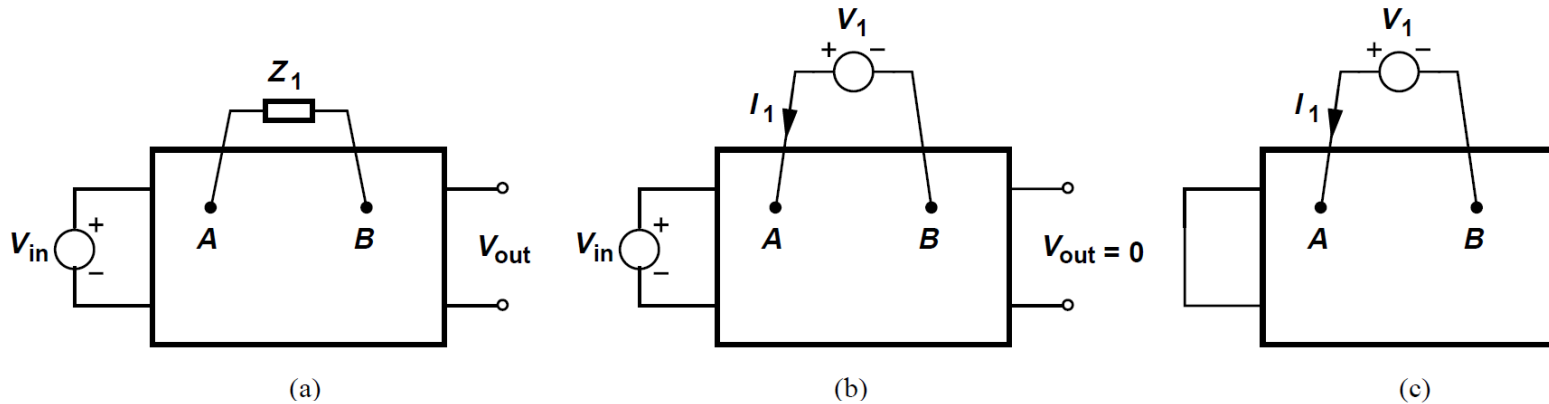


- Suppose the transfer function of a circuit is known and denoted by $H(s)$. Add an extra impedance Z_1 between two nodes of the circuit.
- New transfer function:

$$G(s) = H(s) \frac{1 + \frac{Z_{out,0}}{Z_1}}{1 + \frac{Z_{in,0}}{Z_1}}$$

- Particularly useful for frequency response analysis.

Example 1

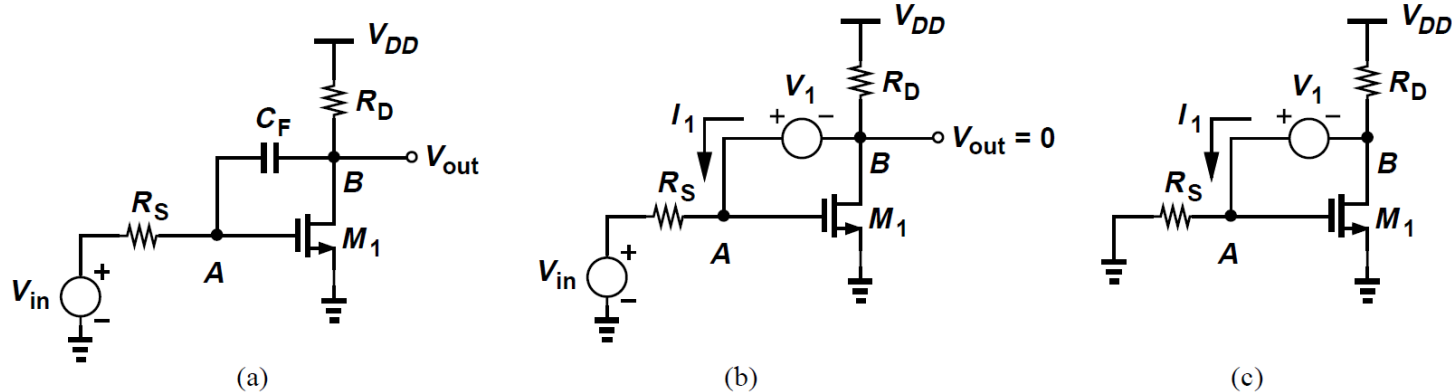

- Find the transfer function.

$$H(s) = -g_m(R_D || r_O)$$


$$Z_{out,0} = -1/g_m$$

- The negative sign of $Z_{out,0}$ does not imply a negative impedance between A and B, since $V_{in} \neq 0$

$$Z_{in,0} = (1 + g_m R_S)R_D + R_S = (1 + g_m R_D)R_S + R_D$$

$$G(s) = -g_m(R_D || r_O) \frac{1 - \frac{1}{g_m} C_F s}{1 + [(1 + g_m R_D)R_S + R_D] C_F s}$$

Example 2

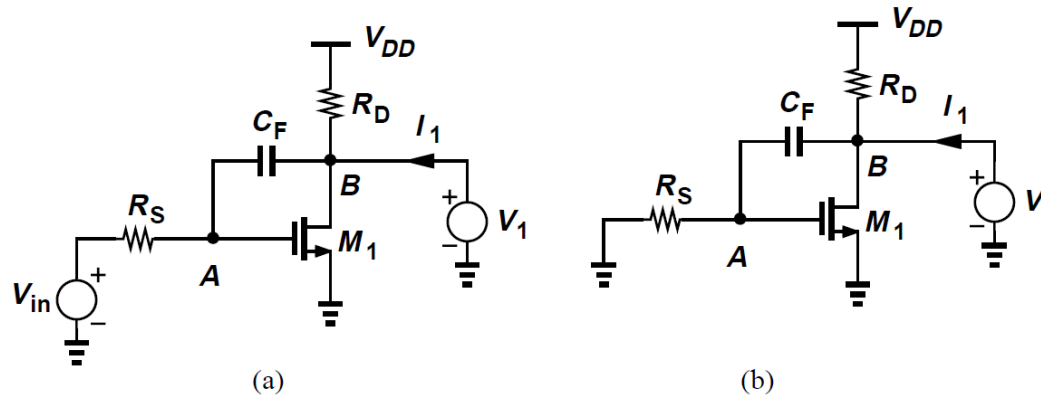


- Include CB, from node B to ground.

$$Z_{out,0} = 0$$

$$Z_{in,0} = \frac{R_D(R_S C_F s + 1)}{R_S(1 + g_m R_D) + R_D]C_F s + 1}$$


$$G(s) = -g_m(R_D || r_O) \frac{1 - \frac{C_F}{g_m} s}{1 + [(1 + g_m R_D)R_S + R_D]C_F s} \frac{1}{1 + \frac{R_D(R_S C_F s + 1)C_B s}{[R_S(1 + g_m R_D) + R_D]C_F s + 1}}$$

Appendix B: Zero-Value Time Constant

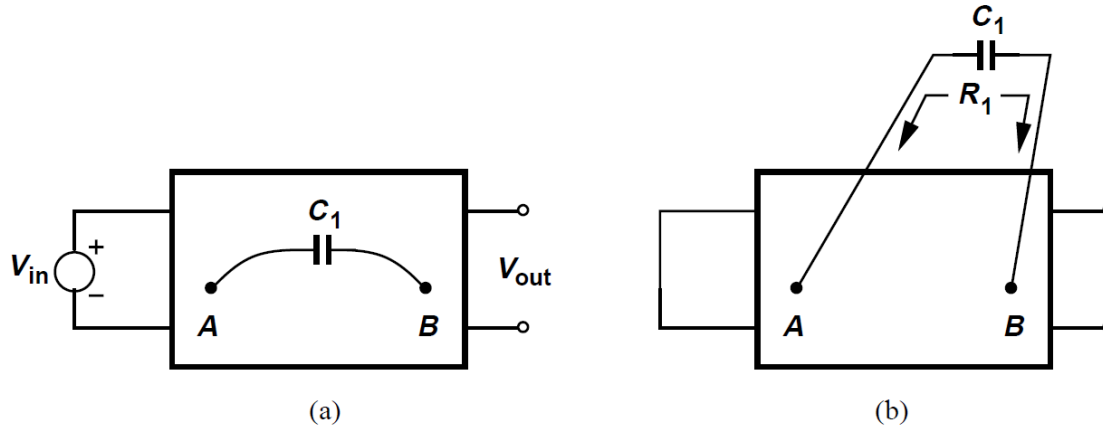

- Suppose a circuit contains one capacitor and no other storage elements.
- Wish to determine the pole of the system.
- Set the input to zero, compute the resistance, R_1 , seen by C_1 , and express the pole as $1/(R_1C_1)$.

Example

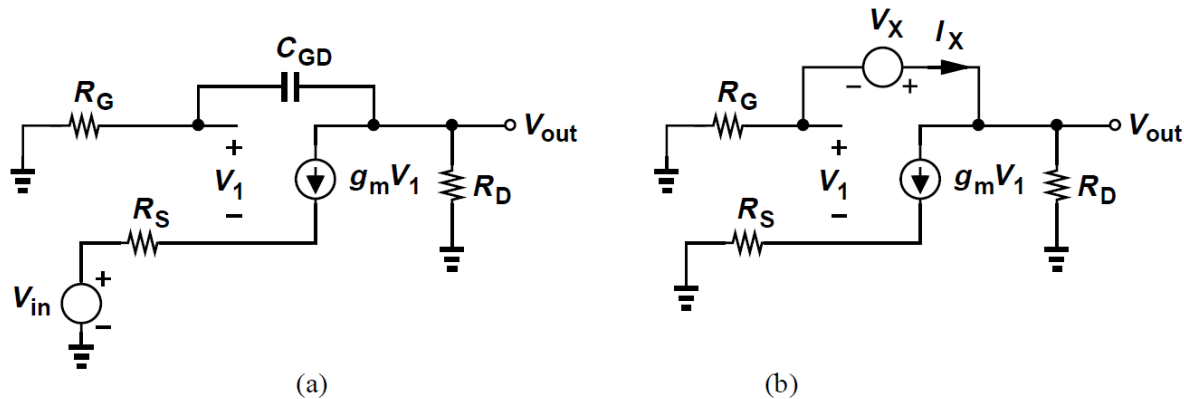


- If only C_{GD} is considered, determine the pole frequency.

$$g_m V_1 R_S + V_1 = -I_X R_G$$

$$\frac{V_X}{I_X} = R_D + \left(\frac{g_m R_D}{1 + g_m R_S} + 1 \right) R_G = R_{eq}$$

- The pole is given by $1/(R_{eq} C_{GD})$

Example

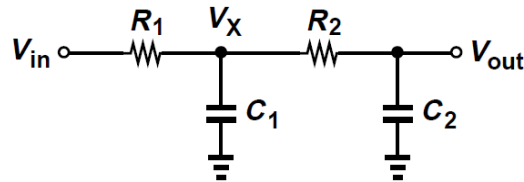

- Writing a KVL around V_{in} , R_1 , R_2 , and V_{out} gives


$$\frac{V_{out}}{V_{in}}(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + [R_1 C_1 + (R_1 + R_2) C_2] s + 1}$$

- The dominant pole is indeed equal to the inverse of the sum of the zero-value time constants.
(need to prove)

$$B_s = \omega_{p1}^{-1} + \omega_{p2}^{-1} + \cdots + \omega_{pn}^{-1} = R_1 C_1 + R_2 C_2 + \cdots + R_n C_n$$


- The ZVTC method proves useful if we wish to estimate the 3-dB bandwidth of a circuit.

Example

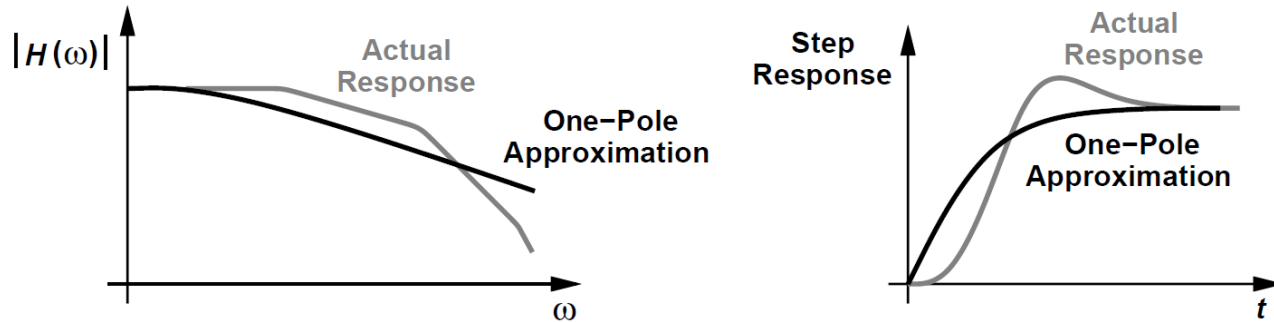

- Approximation of the frequency and time responses by one-pole counterparts.

Example 1

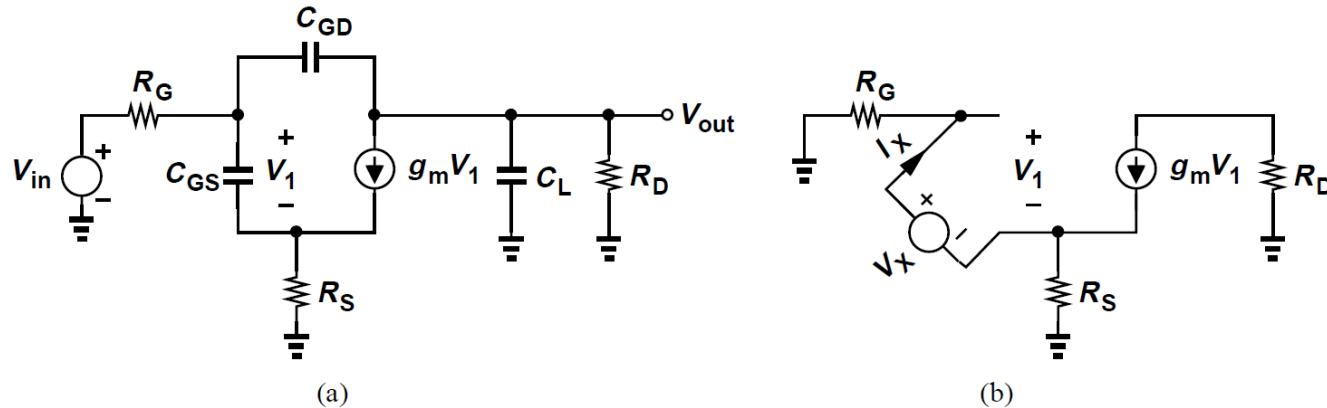

- Estimate the 3-dB bandwidth.
- Begin with the time constant associated with C_{GS} and set C_{GD} and C_L to zero.


$$R_{CGS} = \frac{R_G + R_S}{1 + g_m R_S}$$

$$R_{CGD} = R_D + \left(\frac{g_m R_D}{1 + g_m R_S} + 1 \right) R_G$$

- The resistance seen by C_L is simply equal to R_D .

$$\omega_{-3dB}^{-1} = \frac{R_G + R_S}{1 + g_m R_S} C_{GS} + \left[R_D + \left(\frac{g_m R_D}{1 + g_m R_S} + 1 \right) R_G \right] C_{GD} + R_D C_L$$

Example2

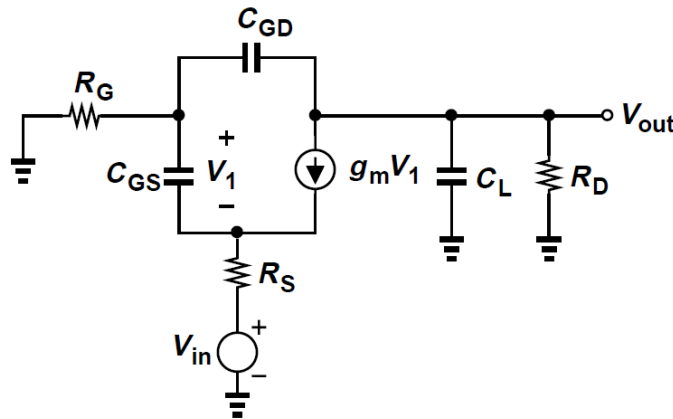

- Find 3-dB band width of a common-gate stage containing a gate resistance of R_G and a source resistance of R_S .
- The resulting equivalent circuits are identical for CS and CG stages, yielding the same time constants and hence the same bandwidth.
- Does this result contradict our earlier assertion that the CG stage is free from the Miller effect?
- No. Why?