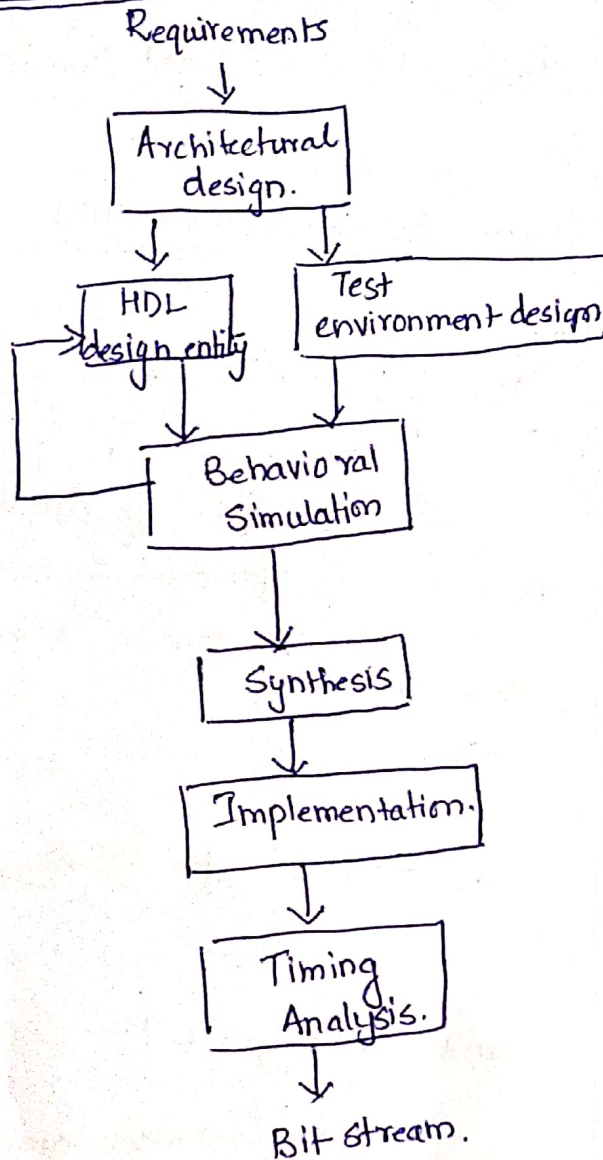


# FPGA DESIGN FLOW




## 4. Timing Verification

↳ Confirming that the fabricated, integrated circuit will operate at a specified speed.
 
## 5. Fault Simulation

↳ Comparing the behavior of an ideal circuit with the behavior of the circuit that contains a process-induced flaw.




## Verilog Code Syntax

VHDL

↳ VHSIC HDL

Verilog

## Verilog Syntax

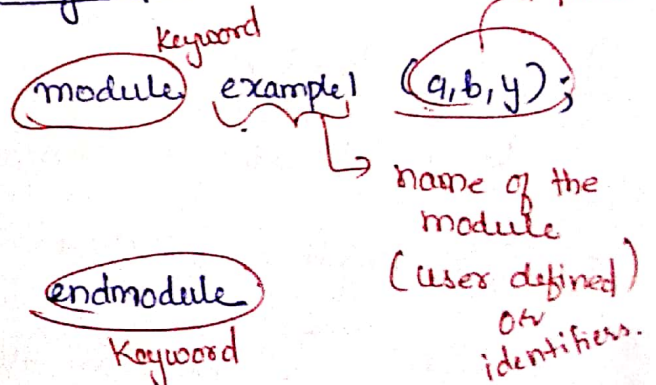

Ⓐ Module declaration.

## Few Terminologies

### 1. Design entity

↳ HDL

### 2. Logic Simulation

↳ functional Verification of the design.

↳ We use the design file and the test bench file

### 3. Logic Synthesis

↳ Generation of netlist

## (b) Verilog Ports.

1. Input port
  2. Output port
  3. inout port
- } unidirectional  
→ Bidirectional.

## Port declaration

```
module example (a,b,y);  
  input a,b; } → Port declaration.  
  output y;  
  :  
  :  
endmodule
```

## (c) Types of Verilog Styles.

1. Data Flow Style
2. Behavioral Style
3. Structural Style
4. Mixed Style

Note: Verilog Code is case Sensitive.

## (d) Verilog Primitives.

Verilog Provides a standard

Set of Primitives, such as

- \* and
- \* nand
- \* or
- \* nor
- \* not

} These are also  
called as built-in  
Primitives. Or  
System Primitives

## Note

Verilog provides the ability to  
define User-Defined Primitives (UDP)

## Circuit to demonstrate HDL

## Note

and (y, a, b);


→ always output port  
should be put first  
followed by the  
respective inputs.

equal to




and G1 (y, a, b);

→ instance name.

 

and G2 (y, a, b, c);

 



## Gate Delays


timescale 1ns/100ps  
↓  
Compiler directive.

When a HDL model is simulated, It is sometime necessary to specify the amount of delay from the input to the output of its gates.

In Verilog propagation delay of a gate is specified in terms of time units and by the symbol #.

The number associated with the time delays in Verilog are dimensionless. The association of a time unit with physical time is made with the timescale Compiler directive.

Simple\_Circuit

 

// Verilog model for Simple\_Circuit

```
module Simple_Circuit (A,B,C,D,E);
```

```
  input A,B,C;
  output D,E;
  wire W1;
```

→ Port declaration

```
  and G1 (W1,A,B);
  not G2 (E,C);
  or G3 (D,W1,E);
```

→ Functionality in Structural style using Primitives

```
endmodule
```

### Note:

Please be clear with the terms instantiation and declaration.

## Gate-level model with propagation delay.

'timescale ms/loops.

Module Simple\_Circuit (A,B,C,D,E)

Input A,B,C;

Output D,E;

Wire W1

and #30 G1 (W1,A,B);

not #10 G2 (E,C);

or #20 G3 (D,W1,E);

endmodule.

begin

A = 1'b0; B = 1'b0; C = 1'b0;

#10 A = 1'b0; B = 1'b0; C = 1'b1;

#10 A = 1'b0; B = 1'b1; C = 1'b0;

delay

end

endmodule

Note: 1

\* Initial block is a non-synthesizable block

\* Initial block executes only once

\* The initial block starts the execution at time zero.

\* Initial blocks are sequential.

Note: 2

\* If I have multiple statements, I should enclose them between a "begin" and "end" statements.

## Test Bench code:

module SimpleCircuit\_tb;

reg A,B,C;

wire D,E;

Simple\_Circuit T1 (A,B,C,D,E);

initial → Initial block.

} Design under Verification



## User Defined Primitives (UDP)

The user can create additional Primitives by defining them in tabular form. These type of Circuits are referred as user defined Primitives.

### General Rules :

1. It is declared with the keyword `primitive` followed by the name and portlist.
2. There can be only one output, and it must be listed first in the port list and declared with the keyword `output`.
3. There can be any number of inputs. The order in which they are listed in the input declaration must confirm to the order in which they are given values in the table that follows.
4. The truth table is enclosed within the keywords `table` and `endtable`.

5. The values of the inputs are listed in order, ending with a colon (':').

The output is always the last entry in a row and is followed by a semicolon (';').

6. The declaration of a UDP ends with the keyword `endprimitive`.

### Example

Write an UDP for the function.

$$f(A, B, C) = \sum (0, 2, 4, 6, 7);$$

// Verilog code for UDP example

```
Primitive UDP_02467 (D, A, B, C);
```

```
output D;
```

```
input A, B, C;
```

```
table
```

```
000 : 1;
```

```
001 : 0;
```

```
010 : 1;
```

```
011 : 0;
```

```
100 : 1;
```

```
101 : 0;
```


```
110 : 1;
```

```
111 : 1;
```

```
endtable
```

```
endprimitive
```

 Eg: Write the Verilog code for the circuit given below.



Solution

```
module design1 (A, B, C, D, E, F);
    input A, B, C, D;
    output E, F;
    UDP_02467 U1(E, A, B, C);
    and U2(F, E, D);
endmodule
```

Structural  
Style or  
gate level  
style

## Verilog Operators

Logical operators.

! (logical negation)

& (logical and)

|| (logical or)

Bit-wise operators

~ (negation)

& (and)

| (or)

^ (xor)

~^ or ~^~ (xnor)

Eg: Write a verilog code for the given boolean expression

$$D = AB + \bar{C}$$

$$E = \bar{C}$$

## Dataflow Style Verilog Coding

```
module sample (A, B, C, D, E);
    input A, B, C;
    output D, E;
    assign D = (A & B) || (!C);
    assign E = !C;
endmodule
```