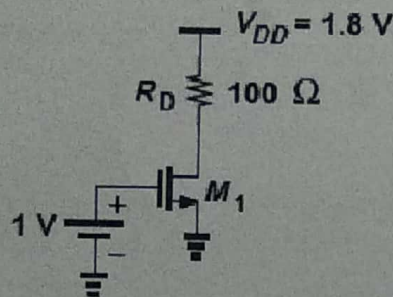


# CMOS Analog Circuit Design


## Assignment – 1 (PART -1)

Q.1 In the circuit shown below Determine ,  $V_{DS}$ ,  $g_m$  and  $r_o$  . Assume  $V_{TH} = 0.4$  V and  $\mu_n C_{ox} = \frac{200 \mu A}{V^2}$ ,  $\lambda = 0.1 V^{-1}$ ,  $W/L = 20/0.18$  .







Q.2 Determine how the transconductance of a MOSFET (operating in saturation) changes if, (a)  $W/L$  is doubled but  $I_D$  remains constant. (b)  $V_{GS} - V_{TH}$  is doubled but  $I_D$  remains constant. (c)  $I_D$  is doubled but  $W/L$  remains constant. (d)  $I_D$  is doubled but  $V_{GS} - V_{TH}$  remains constant.

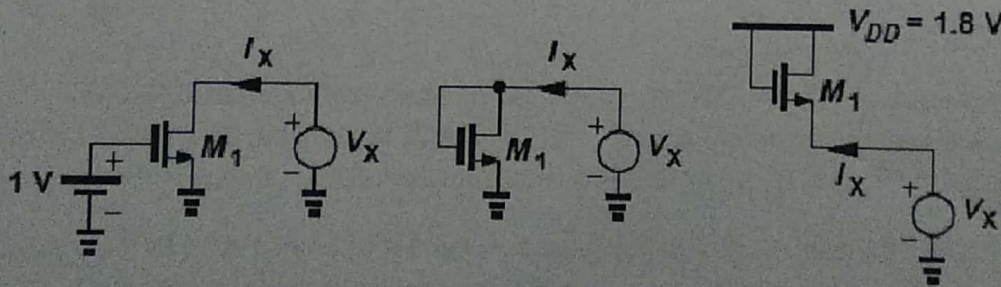Q.3 Sketch  $I_X$  as a function of  $V_X$  for the circuits shown below. Assume  $V_X$  goes from 0 to  $V_{DD} = 1.8$  V. Also,  $\lambda = 0$ . Determine at what value of  $V_X$  the device changes its region of operation.






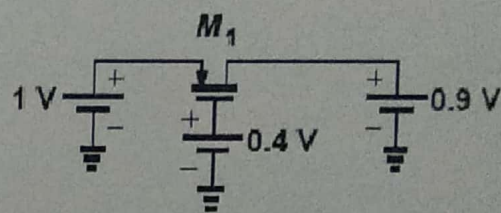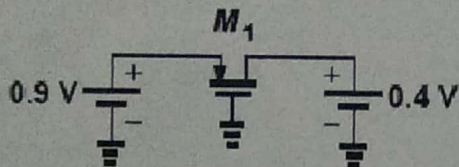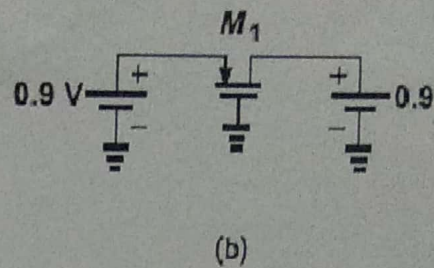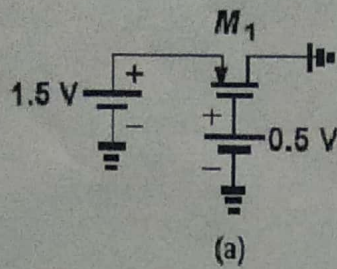Q.4 Determine the region of operation of  $M_1$  in each circuit shown below,




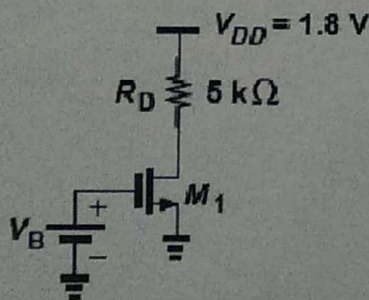Q.5 Calculate the bias current of  $M_1$  in Fig. 6.23. Assume  $\mu nC_{ox} = 100 \mu A/V^2$  and  $V_{TH} = 0.4 V$ ,  $V_B = 1V$  and  $W/L = 20/0.18$ . If the gate voltage increases by 10 mV, what is the change in the drain voltage?



Q.6 A MOSFET carries a drain current of 1 mA with  $V_{DS} = 0.5 V$  in saturation. Determine the change in  $I_D$  if  $V_{DS}$  rises to 1 V and  $\lambda = 0.1V^{-1}$ . What is the device output resistance? Assuming  $\lambda$  is inversely proportional to  $L$ , calculate change in  $I_D$  and  $r_o$ , if both  $W$  and  $L$  are doubled.

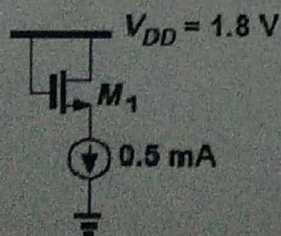Q.7 If a MOSFET is biased at a drain current of 0.5 mA. If  $\mu nC_{ox} = 100 \mu A/V^2$ ,  $W/L = 10$  and  $\lambda = 0.1V^{-1}$ . Calculate its small signal parameters.




Q.8 If  $\lambda = 0.1V^{-1}$  and  $W/L = 20/0.18$ , construct the small-signal model of the circuit shown below and determine all the small signal parameters.



Q.9 An NMOS device with  $\lambda = 0.2 \text{ V}^{-1}$  must provide a  $g_m r_o$  of 20 with  $V_{DS} = 1.5 \text{ V}$ . Determine the required value of  $W/L$  if  $I_D = 0.5 \text{ mA}$ .

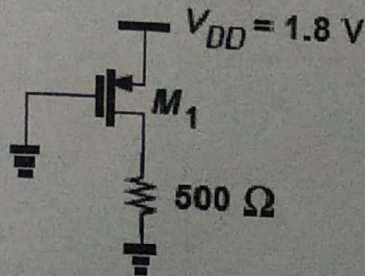Q.10 If  $W/L = 10/0.18$  and  $\lambda = 0$ , determine the  $V_{SD}$  and  $I_D$  of  $M_1$  in circuit shown below. Assume  $\mu_p C_{ox} = 100 \mu\text{A/V}^2$ ,  $V_{TH} = -0.4 \text{ V}$



Note: If required / Not specified in problem, Assume  $\mu_n C_{ox} = \frac{200 \mu\text{A}}{\text{V}^2}$  (for NMOS),

$\mu_p C_{ox} = \frac{100 \mu\text{A}}{\text{V}^2}$  (for PMOS) and  $V_{TH} = 0.4 \text{ V}$  for NMOS devices and  $-0.4 \text{ V}$  for PMOS devices.