

DATE Transient Characteristics

- * Analysis purely resistive circuit have shown that by applying KVL, KCL produces algebraic eq's.
- * Analysis of Circuits having R, L and C elements will lead to differential eq's of order 2/1.
 - RL, RC - 1st order differential eq's.
 - RLC - 2nd " "

Analysis of such differential eq's are quite difficult compared to algebraic eq's.

- * The solution of these differential eq's will give equations that govern the behaviour of the current / voltage.

- * Analysis of these differential eq's are done in two ways.

a) Source free - By using the initial energy stored in storage elements like C/L . Such responses are due to initial conditions / zero input response.

In this,

i) No external excitations used (No external excitation like voltage / current source used)

ii) The stored energy causes the current flow in a closed path & this energy gets dissipated in the form of heat as current passes through resistor gradually. Over a time period stored energy becomes zero.

The responses obtained by such initial conditions are called as zero input response / natural response.

"The Response which is obtained due to initial energy stored due to physical characteristic of circuit elements but not due to external independent sources are called Natural response".

b) Using External independent source - In this, an external excitation used along with initial conditions. The initial conditions may be is

i) Zero state - No energy stored initially ~~is~~ is L/C .

ii) Non-zero state where energy storing elements in the sys are holding ~~is~~ energy because of initial condition is history.

Due to these different ~~some~~ conditions of the ckt we get different types of responses.

Case (i) : If the initial state is zero state when external excitation is applied. The response obtained is called response due to forcing function i.e forced response.

Case (ii) : If the initial state is non-zero (L/C holding energy) Then, the response obtained will have two - components

- a) Natural response b) forced response

∴ The response is called complete response

$$\boxed{\text{Complete Response} = \text{Natural Response} + \text{forced response}} \\ (\text{zero input resp})$$

- When forced response is ~~done~~ being done with a external excitation over a time interval, the response reaches steady state (branch voltage and ~~current~~ node voltages are not changing with respect to time). The response ^{obtained} before the response reaches steady state is called transient response.

- The transient response is temporary, it decays to zero as time approaches infinity i.e It dies out with time.
- Steady state is one which remains after the transient response has died out.

∴ The total response can be rearranged into two parts as transient response & steady state response

$$\boxed{\text{Complete Response} = \text{transient Response} + \text{steady state response}}$$

DATE Transient Response

- We have seen that applying Kirchoff's laws to purely resistive circuits results in algebraic eq² which can be solved easily.
- Applying Kirchoff's laws to RL, RC, RLC (Serial & parallel) circuit leads to differential eq² which are more difficult to solve.

* Resistor (R)

- It is linear, time invariant bilateral element which obeys Ohm's law.


$$\boxed{V = iR \quad i = V/R = GV \text{ where } G = 1/R}$$

- It is a memory less elements as it cannot hold energy. In fact - it dissipates energy in the form heat.

- The current (i) through Resistor (R) changes instantaneously if voltage ' V ' changes.

* Inductor (L) : ~~at x~~

- It is linear, time invariant bilateral element when it is in relaxed state.

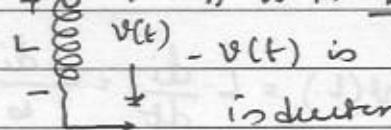 - $v(t)$ is voltage across inductor, $i(t)$ is current through inductor

- $\omega \cdot L \cdot t$

$$v(t) = L \cdot \frac{di}{dt} \quad \text{--- (1)}$$

$$di = \frac{1}{L} v(t) \cdot dt \quad \text{--- (2)}$$

Integrating eq² (2) on both sides by ^{lim} _{$t \rightarrow -\infty$} to t we get $i(t)$ at t .

$$\therefore i(t) = \frac{1}{L} \int_{-\infty}^t v(\tau) \cdot d\tau = \frac{1}{L} \left[\underbrace{\frac{1}{L} \int_{-\infty}^{0^-} v(\tau) \cdot d\tau}_{\text{term 1 indicates current } t < 0} + \underbrace{\frac{1}{L} \int_0^t v(\tau) \cdot d\tau}_{\text{term 2 indicates current } t \geq 0} \right]$$

$i(t)$ brings inductor in history (history) $t < 0$ (present) $t \geq 0$

$$\boxed{i(t) = i(0^-) + \frac{1}{L} \int_{0^-}^{t_0} v(\tau) \cdot d\tau} \quad \text{--- (3)}$$

DATE


Now at $t = 0^+$ [instant after switch k is closed]

$$i(0^+) = i(0^-) + \frac{1}{L} \int_{0^-}^{0^+} v(\tau) \cdot d\tau$$

$$\boxed{i(0^+) = i(0^-)}$$

As inductor

As current through

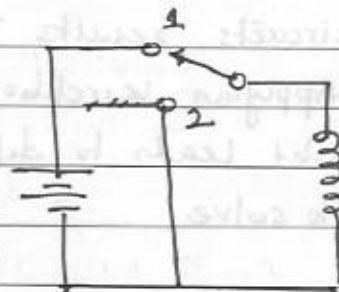


inductor does not change instantaneously

Case(i) : Assume L is relaxed state initially ie $i(0^-) = 0$.

Case (a) : At the time of switching ie $t = 0^+$

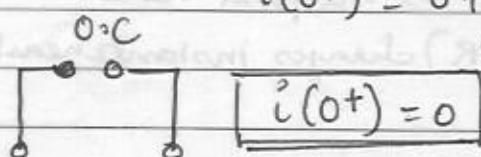
$$i(0^+) = 0 + \int_{0^-}^{0^+} v(\tau) \cdot d\tau \quad \text{As inductance can not energise instantaneously}$$



It means inductor acts as open circuit (O.C)

Case (b) : At steady state ($t = \infty$)
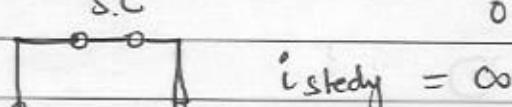
$$i(\infty) = 0 + \int_{0^-}^{\infty} v(\tau) \cdot d\tau \quad \text{if } v(L) = L \cdot \frac{di}{dt} = L \cdot \frac{di}{0} = 0V$$



It means inductor acts as short cut (SC) in steady state.

Case (ii) : Assuming inductor L carries some ^{already} energised state carrying some current I_0 .

(a) At $t = 0^+$

$$i(0^+) = i(0^-) + \int_{0^-}^{0^+} v(\tau) \cdot d\tau$$


$$\boxed{i(0^+) = I_0 = i(0^-)}$$

It means inductor acts as a current source


DATE

(b) At steady state $t = \infty$

$$i(\omega) = I_0 + \int_0^\infty v(\tau) \cdot d\tau. \quad v(t) = L \cdot \frac{di}{dt} = L \cdot \frac{di}{\infty} = 0$$

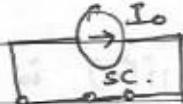 $= I_0 + \text{short circuit}$ ∴ A current source I_0 is in parallel with short circuit

*Capacitor : We know that

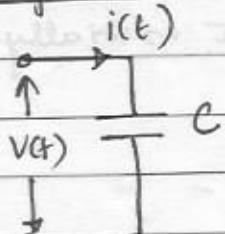

$$i(t) = C \cdot \frac{dv(t)}{dt}$$

$$\left[dv(t) = \frac{1}{C} i(t) \cdot dt \right] -①$$

Integrating on both sides from $[-\infty \text{ to } t]$, $v(t)$ is obtained

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) \cdot d\tau.$$

$$\left[v(t) = \frac{1}{C} \int_{-\infty}^{0^-} i(\tau) \cdot d\tau + \frac{1}{C} \int_{0^-}^t i(\tau) \cdot d\tau \right] -②$$

Potential ^{due to} Change stored in history

$$\left[v(t) = v(0^-) + \frac{1}{C} \int_{0^-}^t i(\tau) \cdot d\tau \right] -③$$


Case (i) : Capacitor initially is relaxed state.

$$\therefore v(t) = \frac{1}{C} \int_0^t i(\tau) \cdot d\tau. -④$$

(a) : At $t = 0^+$ or

$$v(0^+) = \frac{1}{C} \int_0^0 i(\tau) \cdot d\tau$$

Capacitor can't charge instantaneously

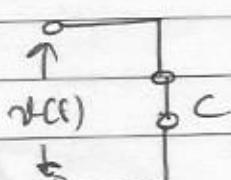

$$\therefore [v(0^+) = 0] -⑤$$

It means, Capacitor 'C' at $t = 0^+$ with initial relaxed state acts as short circuit.

b) At steady state $t = \infty$

$$v(\infty) = \frac{1}{C} \int_{0^-}^{\infty} i(c) \cdot dc \underset{i(t) = 0}{=} 0 \quad i(t) = C \cdot \frac{dv(t)}{dt} = C \cdot \frac{d v(\infty)}{\infty} = 0 \quad (6)$$


As $i(t)$ is zero at $t = \infty$ it means Capacitor can't be charged further ie Capacitor is charged to max & holding max energy. Acts as Open circuit

Case (ii) Assume capacitor is not in relaxed state initially

$$\therefore v(0^-) = V_0 \text{ then}$$

$$v(t) = V_0 + \int_{0^-}^t i(c) \cdot dc \quad (7)$$

a) At $t = 0^+$

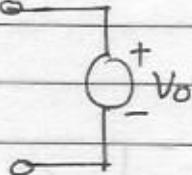


$$v(0^+) = V_0 + \int_{0^-}^{0^+} i(c) \cdot dc \quad \text{can't charge instantaneously}$$

$\therefore v(0^+) = V_0$
It means acts as voltage source.









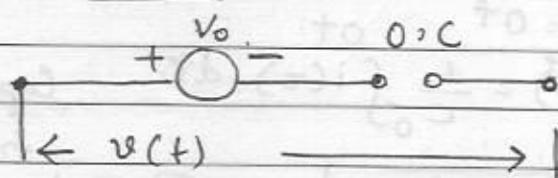
b) At steady state ($t = \infty$)

$$v(\infty) = V_0 + \int_{0^-}^{\infty} i(c) \cdot dc \quad i(t) = C \cdot \frac{dv(t)}{dt} = 0$$

$i(t)$ through capacitor becomes 0. It means capacitor can't be charged further. Hence Capacitor acts as voltage source in series with O.C




Summary

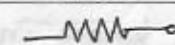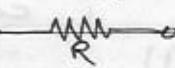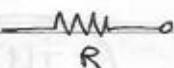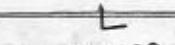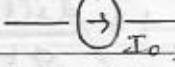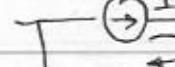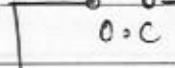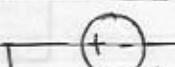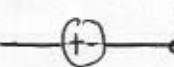Element	Inital $t = 0^-$	$t = 0^+$ (After switch)	$t = \infty$ (Stady state)
R		$v(t) = R \cdot i(t)$ $i(t) = \frac{v(t)}{R}$	$v(t) = R \cdot i(t)$
(1) 	$v(t) = R \cdot i(t)$ $i(t) = \frac{v(t)}{R}$		
(2) 	$v(0^+) = 0$, $v(t) = L \cdot \frac{di}{dt}$ $i(t) = \int_{-\infty}^t v(z) dz$ $= i(0^-) + \frac{1}{L} \int_{0^-}^t v(z) dz$	$i(t) = i(0^-) + \frac{1}{L} \int_0^t v(z) dz$ $\therefore v(t) = L \cdot \frac{di}{dt} = 0$ $i(t) = 0 + \frac{1}{L} \int_0^\infty v(z) dz$ Hence $i(t) = 0$	$i(t) = 0 + \frac{1}{L} \int_0^\infty v(z) dz$ $v(t) = L \cdot \frac{di}{dt} = 0$ Hence, $i(t) = 0$
(3) Capacitor (C)	$i(0^-) = I_0$	$i(t) = I_0 + 0$.  current source	$i(t) = I_0 + 0$  SC
	$v(0^-) = 0$	$v(t) = 0 + \frac{1}{C} \int_{0^-}^t i(z) dz$ $= 0 + \int_{0^-}^{0^+} i(z) dz$ $v(t) = 0$	$v(t) = 0 + \frac{1}{C} \int_0^\infty i(z) dz$ $i(t) = C \cdot \frac{dv(t)}{dt} = 0$ $v(t) = 0 + 0 \text{ (max)}$
	$i(t) = C \cdot \frac{dv(t)}{dt}$ $v(t) = \frac{1}{C} \int_{0^-}^t i(z) dz +$ $= V(0^-) + \frac{1}{C} \int_{0^-}^t i(z) dz$	 Capacitor acts as SC	 Cap acts 0:C
	$v(0^-) = V_0$	$v(t) = V_0 + \frac{1}{C} \int_{0^-}^t i(z) dz$ $\boxed{v(t) = V_0}$	$v(t) = V_0 + \frac{1}{C} \int_{0^-}^\infty i(z) dz$ $= V_0 + 0$
		 acts as voltage source	 0:C

* Transient Response of Driven Series RL circuit

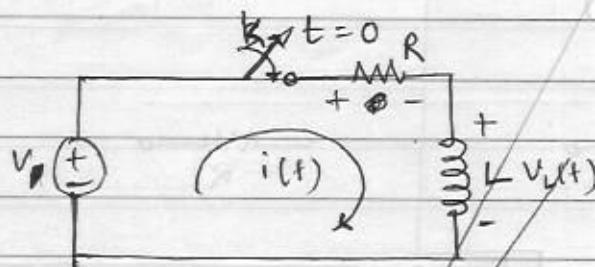Transient response of driven series RL ckt is used to find expression of current through inductor (L) for $t > 0$



- It is important to know initial condition of current through inductor L .

Let us consider that, Initial current through inductor is I_0 at $t = 0^-$ (switch K is open).

$$i(0^-) = I_0$$

At $t = 0^+$ /c At the time of switching

$$i(0^+) = i(0^-) + \frac{1}{L} \int_{0^-}^{0^+} v(t) dt$$

$i(0^+) = i(0^-)$ \rightarrow Current through inductor cannot change instantaneously

Now at $t = 0^+$ switch K is closed.

Using KVL

$$-Ri(t) - L \frac{di(t)}{dt} + V = 0$$

$$V = R i(t) + L \frac{di(t)}{dt} \quad t > 0 \quad \text{--- (1)}$$

By dividing both sides by R & rearranging

$$\frac{V}{R} = i(t) = \frac{L}{R} \frac{di(t)}{dt}$$

$$\frac{L}{R} \frac{di(t)}{dt} = \left(\frac{V}{R} - i(t) \right)$$

$$\frac{di(t)}{\left(\frac{V}{R} - i(t) \right)} = \frac{R}{L} dt \quad \text{separating variables}$$

$$V - R i(t) = L \frac{di(t)}{dt}$$


$$V - R i(t) \therefore \left[dt = \frac{L di(t)}{V - R i(t)} \right] \quad \text{--- (2)}$$

DATE

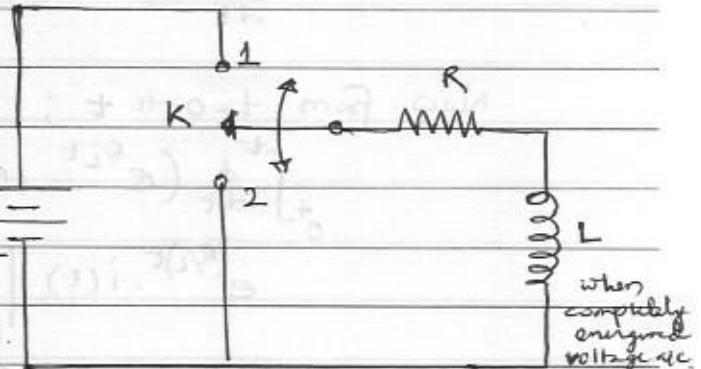a) A source free RL Circuit :

- Assume that, the switch K is position 1 for a long duration of time. It

means there is a equilibrium before switching. Under such equilibrium state the inductor acts as a short ckt (sc) ie Voltage across Inductor is zero \therefore back emf = V.



- Let $t=0$, be the reference instant of time when transition of switch takes place.

- Objective of Analysis - Obtain the equation that governs the behaviour of the current from the moment that equilibrium is altered.


- At $t=0^-$ \rightarrow time immediately before transition of switch Since there is a equilibrium at $t=0^-$, the current is the circuit is constant ie before transition, for all time $t \in (-\infty, 0^-)$ where $\infty > 0$.

$$\begin{aligned} i(t) &= \frac{V}{R} \triangleq I_0. \\ \therefore i(0^-) &= I_0. \end{aligned} \quad \left. \right\} - (1)$$

- After the transition of switch from position 1 to 2

Using KVL

$$L \frac{di}{dt} + Ri = 0 \quad - (2)$$

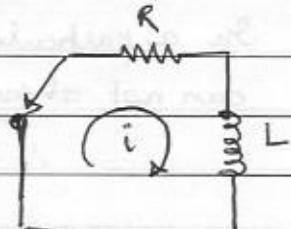

It is homogeneous first order ordinary differential eq² with constant coefficients.

The sol^e for eq² ② can be obtained by solving eq² ②

$$\frac{di}{dt} + \frac{R}{L} \cdot i = 0$$

Multiply throughout by integrating factor $e^{\left(\frac{R}{L}\right)t}$

$$e^{\left(\frac{R}{L}\right)t} \cdot \frac{di}{dt} + e^{\left(\frac{R}{L}\right)t} \left(\frac{R}{L}\right) i = 0 \quad - (3)$$

Clearly eq 2 is of the form $\frac{d}{dt}(uv) = u \cdot \frac{dv}{dt} + v \cdot \frac{du}{dt}$

$$\therefore \frac{d}{dt}(e^{\frac{R}{L}t} \cdot i(t)) = 0$$

Now from $t=0$ to t ;

$$\int_{0^+}^t \frac{d}{dt}(e^{\frac{R}{L}t} \cdot i(t)) dt = 0.$$

$$e^{(R/L)t} \cdot i(t) \Big|_{0^+}^t = 0.$$

$$e^{\frac{R}{L}t} i(t) - e^0 \cdot i(0^+) = 0.$$

$$e^{\frac{R}{L}t} i(t) = i(0^+)$$

$$V(t) = L \cdot \frac{di}{dt}$$

$$= L \cdot \frac{d}{dt}(i(0^+) \cdot e^{\frac{R}{L}t})$$

$$= L \cdot V \cdot \frac{R}{L} e^{-\frac{R}{L}t}$$

$$V(t) = -V_0 \cdot e^{-\frac{R}{L}t}$$

(or) By separating variables in eq 2

$$di = -\frac{R}{L} dt$$

$$\int_{0^+}^t \frac{di}{i} = -\frac{R}{L} \int_{0^+}^t dt$$

$$\ln i \Big|_{0^+}^t = -\frac{R}{L} t$$

$$\ln(i(t)) - \ln(i(0^+)) = -\frac{R}{L} t$$

$$\ln \left(\frac{i(t)}{i(0^+)} \right) = -\frac{R}{L} t$$

xplain by exponential on both sides

$$\frac{i(t)}{i(0^+)} = e^{-\frac{R}{L}t}$$

$$i(t) = i(0^+) \cdot e^{-\frac{R}{L}t}$$

In general, If the eq obtained is a 1st order homogeneous differential eq of the form

$$\frac{dy}{dt} + \frac{a_1}{a_0} y = 0.$$

Sol to any homogeneous ODE is of the form

then $y(t) = y(0^+) e^{-\left(\frac{a_1}{a_0}\right)t}$

where $T = \frac{a_0}{a_1}$

- (5) where $y(0^+)$ & $\frac{a_1}{a_0}$ varies.

In a particular ckt, we know that current in the inductor can not change instantaneously

$$\therefore i(0^+) = i(0^-) = \frac{V}{R} = I_0.$$

Hence eq 4 can be written as


$$i(t) = \frac{V}{R} \cdot e^{-\frac{R}{L}t} \quad \text{if } t \geq 0^+. \quad - (6)$$

Now, eq 2 (6) can be written as


$$i(t) = \frac{V}{R} \cdot e^{-t/T} \quad \text{if } t \geq 0^+ \\ \text{where } T = \frac{L}{R} \quad \text{---(2)}$$

$$T = \frac{L}{R} \quad \text{---(3)}$$

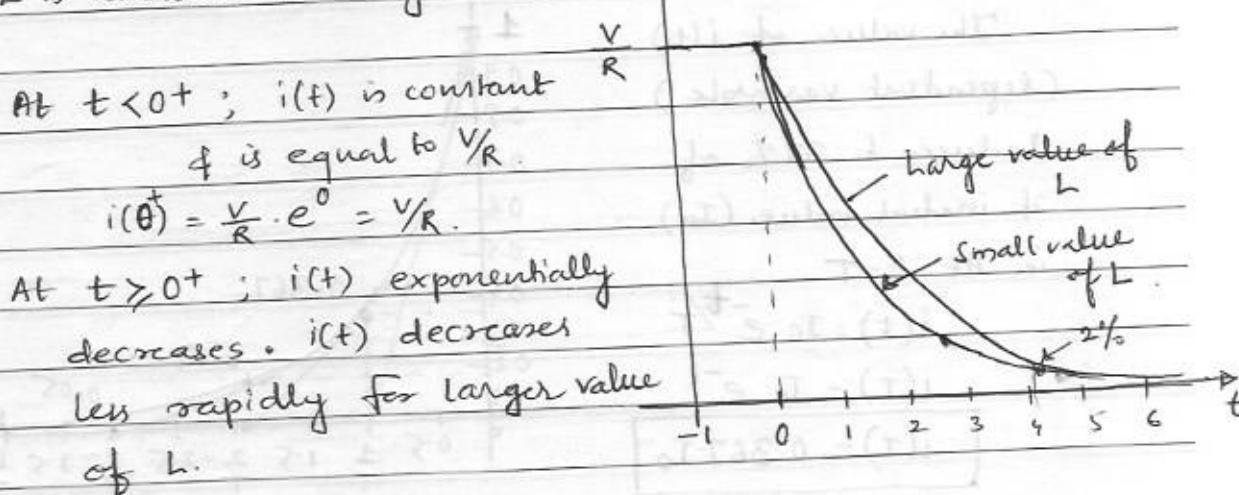- a) Response curve of $i(t)$ where V and R are held constant & L is allowed to vary



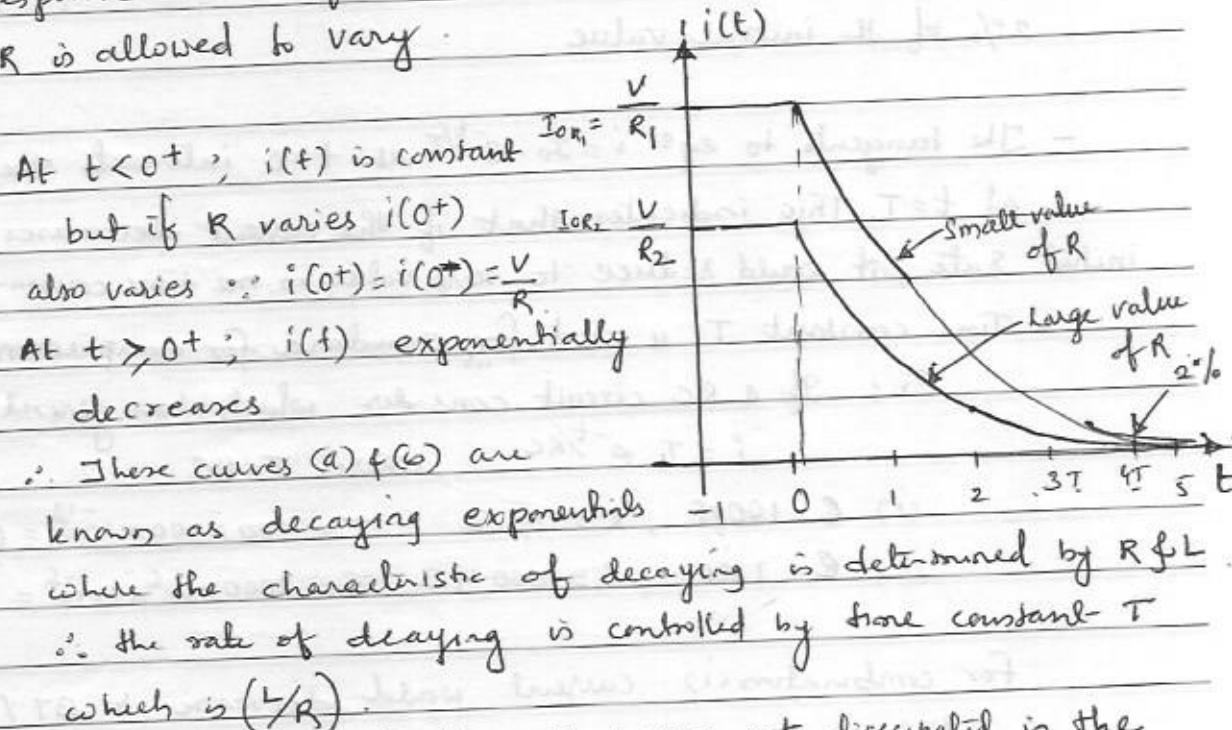- b) Response curve of $i(t)$ where V & L are held constant and R is allowed to vary.



At $t \geq 0^+$; Eventually all energy gets dissipated in the form of heat through resistor R and current $i(t)$ becomes zero.

t_0	t/T	$i(t) = V/R \cdot e^{-t/T}$	$i(t)/V_R$
0	0	V/R	1
T	1	$V_R \cdot e^{-1} = 0.367 \frac{V}{R}$	0.367
2T	2	$0.14(V_R)$	0.14
3T	3	$0.05 V_R$	0.05
4T	4	$0.018 V_R$	0.018
5T	5	$0.0067 V_R$	0.0067

The value of $i(t)$
(dependent variable)


reduces to 37% of
its initial value (I_0)

i.e. At $t=T$.

$$i(t) = I_0 \cdot e^{-t/T}$$

$$i(T) = I_0 \cdot e^{-1}$$

$$\boxed{i(T) = 0.367 I_0}$$

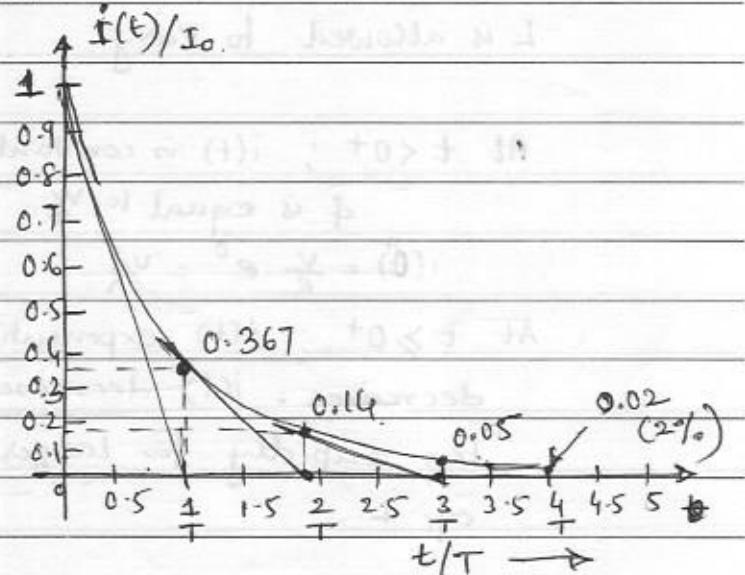

By similar computations at $t=4T$, current decreases approximately 2% of the initial value.

- The tangent to eq² $i = I_0 \cdot e^{-t/T}$ at $t=0$ intersects the $i=0$ line at $t=T$. This indicates that if the current decreases at the initial rate, it would reduce to zero value in one time constant.

- Time constant T is used as standard for comparison.

Ex: If a RC circuit consider which has general soln as

$$i = I_0 e^{-t/RC} \quad \text{where } T = RC$$

$$(i) C = 100 \mu F, R = 100 \Omega \quad T = 100 \times 100 \times 10^{-12} = 0.1 \text{ msec}$$

$$(ii) C = 1 \mu F, R = 1000 M\Omega \quad T = 1000 \times 10^6 \times 1 \times 10^{-6} = 1000 \text{ sec}$$

(or) 17 Sec

for combination (i) current would decrease to 37% of its initial value in small time interval 0.1 msec where as case (ii) it takes 17 sec to decrease to 37% of initial value.

Note: Approximately @ 4T constants transient approximately disappears

DATE

b) A Source Driven RL Circuit

Consider an RL ckt with
constant applied voltage
at $t=0$.

By KVL,

$$L \cdot \frac{di}{dt} + R i = V \quad \text{--- (1)}$$

$$\frac{di}{dt} + \frac{R}{L} \cdot i = \frac{V}{L} \quad \text{--- (2)}$$

It is Non homogeneous first order differential eq of the form

$$\frac{dy}{dt} + \frac{\alpha_1}{\alpha_0} y = \frac{E}{B} \quad \text{--- (3)}$$

Now multiplying both sides by integrating factor $e^{t(\frac{\alpha_1}{\alpha_0})}$

$$e^{\frac{\alpha_1}{\alpha_0} t} \cdot \frac{dy}{dt} + e^{\frac{\alpha_1}{\alpha_0} t} \left(\frac{\alpha_1}{\alpha_0} \right) y = E \cdot e^{\frac{\alpha_1}{\alpha_0} t}$$

$$\frac{d}{dt} \left(e^{\frac{\alpha_1}{\alpha_0} t} \cdot y \right) = E \cdot e^{\frac{\alpha_1}{\alpha_0} t} \quad \int e^{zx} dt = \frac{e^{zx}}{z}$$

Integrating from 0 to t

$$e^{\frac{\alpha_1}{\alpha_0} t} y(t) \Big|_0^t = E \left(\frac{\alpha_0}{\alpha_1} \right) e^{\frac{\alpha_1}{\alpha_0} t} \Big|_0^t$$

$$e^{\frac{\alpha_1}{\alpha_0} t} y(t) - e^0 y(0) = E \frac{\alpha_0}{\alpha_1} e^{\frac{(\alpha_1 \alpha_0)}{\alpha_0} t} - E \frac{\alpha_0}{\alpha_1} e^0 E \left(\frac{\alpha_0}{\alpha_1} \right) \cdot e^0$$

$$e^{\frac{\alpha_1}{\alpha_0} t} y(t) - y(0) = E \left(\frac{\alpha_0}{\alpha_1} \right) \left[e^{\frac{\alpha_1}{\alpha_0} t} - 1 \right]$$

$$y(t) = y(0) + E \left(\frac{\alpha_0}{\alpha_1} \right) \left[e^{\frac{\alpha_1}{\alpha_0} t} - 1 \right]$$

$$y(t) = y(0) \cdot e^{-\frac{\alpha_1 t}{\alpha_0}} + E \left(\frac{\alpha_0}{\alpha_1} \right) \left[1 - e^{-\frac{\alpha_1 t}{\alpha_0}} \right]$$

$$\text{if } T = \frac{\alpha_0}{\alpha_1}, \quad \boxed{y(t) = y(0) e^{-t/T} + ET (1 - e^{-t/T})} \quad \text{--- (4)}$$

from (2)

$$E = \frac{V}{L}, \quad T = \frac{L}{R} \quad y(0) = I(0) \quad y(t) = i(t)$$

Substituting above in eq² (4)

$$\therefore i(t) = i(0) \cdot e^{-t/T} + \frac{V}{L} \times \frac{L}{R} (1 - e^{-t/T}), \quad t \geq 0^+$$

$$\boxed{i(t) = i(0) \cdot e^{-t/T} + \underbrace{\frac{V}{R} (1 - e^{-t/T})}_{B}} \quad - (5) \quad \forall t \geq 0^+$$

A

By rearranging

$$i(t) = i(0) e^{-t/T} + \frac{V}{R} - \frac{V}{R} e^{-t/T}$$

$$\boxed{i(t) = \underbrace{\left(i(0) - \frac{V}{R} \right)}_{C} e^{-t/T} + \underbrace{\frac{V}{R}}_{D}} \quad - (6)$$

$$(6) = \boxed{\frac{V}{R} - \left(\frac{V}{R} - i(0) \right) e^{-t/T}} = \boxed{i(\infty) - (i(\infty) - i(0)) e^{-t/T}}$$

A \rightarrow zero input response (source free) - NaturalB \rightarrow forced response (due to forcing function)C \rightarrow transient responseD \rightarrow steady state response : $\lim_{t \rightarrow \infty} i(t)$

In general,

$$y(t) = \underbrace{y(0) \cdot e^{-t/T}}_A + \underbrace{ET (1 - e^{-t/T})}_B \quad \text{where } T = \frac{\alpha_0}{\alpha_1}$$

By rearranging

$$y(t) = \underbrace{(y(0) - ET)}_C e^{-t/T} + \underbrace{ET}_D \quad - (7)$$

transient part must adjust itself such that so that the it does not
then the response will be in \Rightarrow steady state.

DATE _____

forced Response (B)

- After a long time, the switch K transition from 2 to 1

- then,

$$i(0^-) = 0,$$

By KVL

$$L \cdot \frac{di}{dt} + Ri = V$$

$$i(t) = i(0^+) \cdot e^{-t/\tau} + \frac{V}{R} (1 - e^{-t/\tau})$$

$$\text{As } i(0^-) = 0 \quad \therefore i(0^+) = 0.$$

Therefore,

$$\boxed{i(t) = \frac{V}{R} (1 - e^{-t/\tau})} \quad t > 0 \quad \text{--- (7)}$$

The steady state part is $i(\infty) = V/R$.

$$t = T$$

$$i(T) = \frac{V}{R} (1 - e^{-1}) = (1 - 0.37) I_0 = 0.63 I_0.$$

$$t = 0$$

$$i(0) = \frac{V}{R} (1 - e^0) = 0.$$

It's clear that at $t = T$ $\frac{i(0)}{I_0}$ the current reaches 63% $\frac{V}{R}$ of its final value. ie



In one time constant.

If the current increases to 0.63

approximately 98% of

the final value is

4T constants.

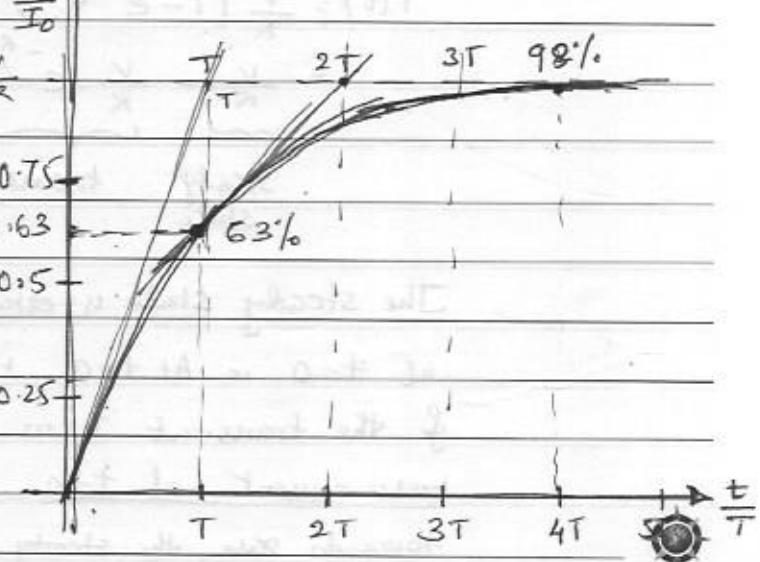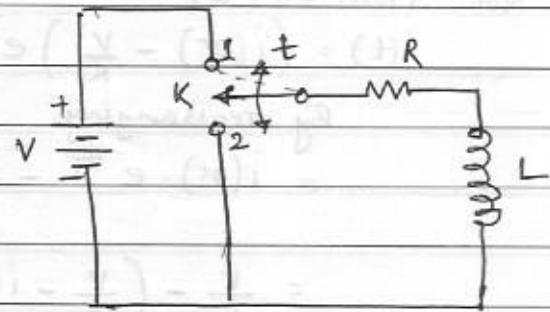A tangent drawn at $t = 0$,which intersects $i = I_0 = \frac{V}{R}$ at $t = T$ which means If the current i increases at initial rate, it reaches steady state at $t = T$ 

Now from eq (6)

$$i(t) = \left(i(0^+) - \frac{V}{R} \right) e^{-\frac{t}{T}} + \frac{V}{R}$$

By rearranging

$$= i(0^+) \cdot e^{-\frac{t}{T}} - \frac{V}{R} \cdot e^{-\frac{t}{T}} + \frac{V}{R}$$

$$= \frac{V}{R} - \left(\frac{V}{R} - i(0^+) \right) e^{-\frac{t}{T}}$$

$$\boxed{i(t) = i(\infty) - \underbrace{(i(\infty) - i(0^+))}_{\substack{\text{steady} \\ \text{state}}} e^{-\frac{t}{T}} - \underbrace{(i(0^+) - \frac{V}{R})}_{\text{transient}}}_{\substack{\text{portion}}} \quad (8)$$

It means, the response is made up of two parts of solz


- i) particular transient portion (complementary function)
- ii) steady state value

The steady state value is regarded as having been established at $t=0$, and the transient must adjust itself, mathematically, to account for the response at $t=0$ and all other time.

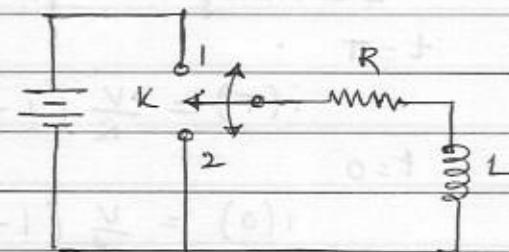Example (1)

$$i = i_{ss} + i_t$$


Switch moved from position
2 to 1 at $t=0$. By KVL



$$i(t) = \frac{V}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$

$$= \frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L}t}$$

steady state transient

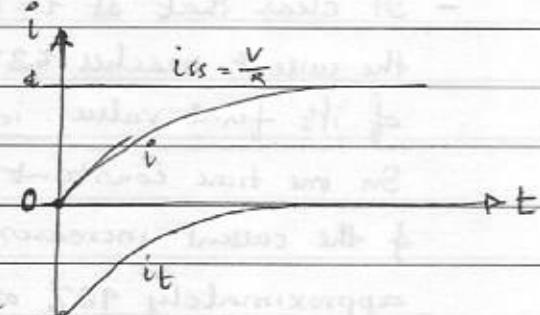

The steady state is established
at $t=0$ ie At $t=0$; $i = i_{ss} = \frac{V}{R}$

& the transient term is adjusted such that there is
zero current at $t=0$. As transient part starts adjusting
towards zero, the steady current i starts moving towards
steady state i_{ss} .

DATE

9/16

Example(2)

Case(i) : We close the switch

at $t=0$. This means $V = \frac{V}{R_1 + R_2}$

switch was open for

a long time.

$$\therefore i(0^-) = \frac{V}{R_1 + R_2} \quad \text{and} \quad i(\infty) = \frac{V}{R_1} \quad T = \frac{L}{R_1}$$

$$\text{Now } i(t) = i(\infty) - (i(\infty) - i(0^+)) e^{-\frac{t}{T}} =$$

$$i = \frac{V}{R_1} - \left(\frac{V}{R_1} - \frac{V}{R_1 + R_2} \right) e^{-\frac{R_1 t}{L}}$$

$$i(\infty) = \frac{V}{R_1} - \left(\frac{V(R_1 + R_2) - VR_1}{R_1(R_1 + R_2)} \right) e^{-\frac{R_1 t}{L}}$$

$$i(0) = \frac{V}{R_1} - \left(\frac{VR_2}{R_1(R_1 + R_2)} \right) e^{-\frac{R_1 t}{L}}$$

$$i = \frac{V}{R_1} - \frac{V}{R_1} \left(\frac{R_2}{R_1 + R_2} \right) e^{-\frac{R_1 t}{L}}$$


$$i = \frac{V}{R_1} \left(1 - \frac{R_2}{R_1 + R_2} \cdot e^{-\frac{R_1 t}{L}} \right)$$

Case(ii) : After the steady state is reached. (switch was closed for

Now, if switch is opened.

Long time)
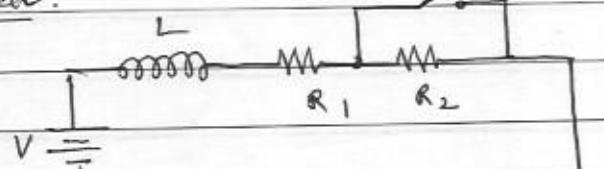
$$\text{At } t=0^-; i(0^-) = \frac{V}{R_1}$$



$$i(\infty) = \left(\frac{V}{R_1 + R_2} \right) \quad T = \frac{L}{R_1 + R_2}$$

$$\text{if } T = \frac{L}{R_1 + R_2} \quad \text{By substituting there is eq 2(8)}$$

$$i = \left(\frac{V}{R_1 + R_2} \right) - \left(\frac{V}{R_1 + R_2} - \frac{V}{R_1} \right) e^{-t \left(\frac{R_1 + R_2}{L} \right)}$$

$$= \left(\frac{V}{R_1 + R_2} \right) - \left(\frac{VR_1 - V(R_1 + R_2)}{R_1(R_1 + R_2)} \right) e^{-t \left(\frac{R_1 + R_2}{L} \right)}$$


$$i = \frac{V}{R_1 + R_2} - \left(\frac{-VR_2}{R_1(R_1 + R_2)} \right) e^{-\left(\frac{R_1 + R_2}{L}\right)t}$$

$$= \frac{V}{R_1 + R_2} \left(1 + \frac{R_2}{R_1} e^{-\left(\frac{R_1 + R_2}{L}\right)t} \right)$$

$$\boxed{i = \frac{V}{R_1 + R_2} \left(1 + \frac{R_2}{R_1} e^{-\left(\frac{R_1 + R_2}{L}\right)t} \right)}$$

$$\frac{V}{R_1} \quad i(0)$$

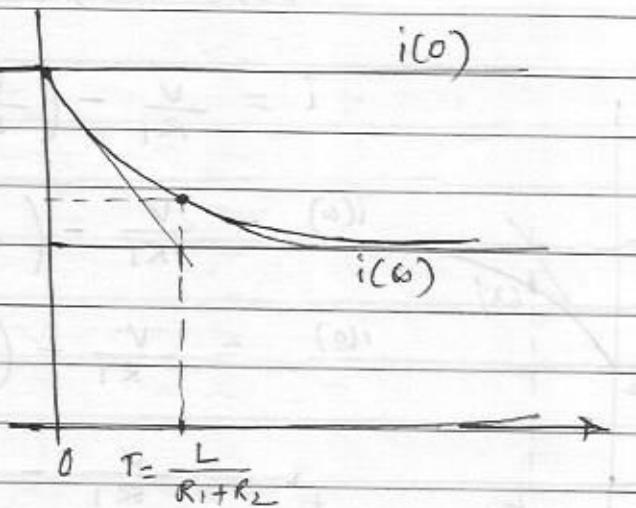Here in case (i) f(ii)
we observe that the
time constant are
different.



DATE

* zero input / source free RC nw.

Switch K is at position 1

for long time. \therefore

Voltage is completely

charged $V_C = V$ ie

acting as open ckt (O.C)

Now, at $t=0^+$

$$V_C(0^-) = V = V_0. \quad -(1)$$


At $t=0^+$

$V_C(0^+) = V_C(0^-) = V = V_0$ as charge of capacitor
cannot change instantaneously

By KVL,

$$C \frac{dV}{dt} + \frac{V}{R} = 0.$$
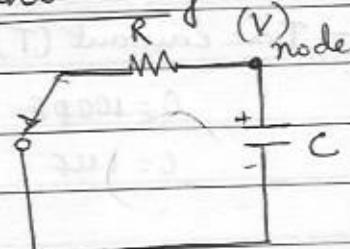
$$\left[\frac{dV}{dt} + \frac{V}{RC} = 0 \right] \quad -(2)$$



Eq² (2) is homogeneous 1st order differential eq²
W.K.T is general for homogeneous 1st order diff
eq² of this form as response

$$y(t) = y(0) \cdot e^{-\frac{t}{RC}}$$

\therefore Now solve for eq² (2) \Rightarrow

$$\underline{V(t)}$$

$$\left[V(t) = V(0^+) \cdot e^{-\frac{t}{RC}} \right] \quad -(3).$$

As at $t=0$; $V(0^+) = V(0^-) = V_0$.

$$\left[V(t) = V_0 \cdot e^{-\frac{t}{RC}} \right] \quad -(4)$$

Time constant $T = RC$

$$\boxed{V(t) = V_0 \cdot e^{-\frac{t}{T}}} \quad -(5)$$


$$V(t) = V \cdot e^{-\frac{t}{RC}}$$

$$i(t) = C \cdot \frac{dV}{dt} \\ = C \cdot \frac{d}{dt} (V_0 \cdot e^{-\frac{t}{RC}})$$

$$= C \cdot V_0 \left(-\frac{1}{RC} \right) e^{-\frac{t}{RC}} \\ = -\frac{V_0}{R} \cdot e^{-\frac{t}{RC}}$$

$$\boxed{i(t) = -\frac{V}{R} \cdot e^{-\frac{t}{RC}}}$$

DATE

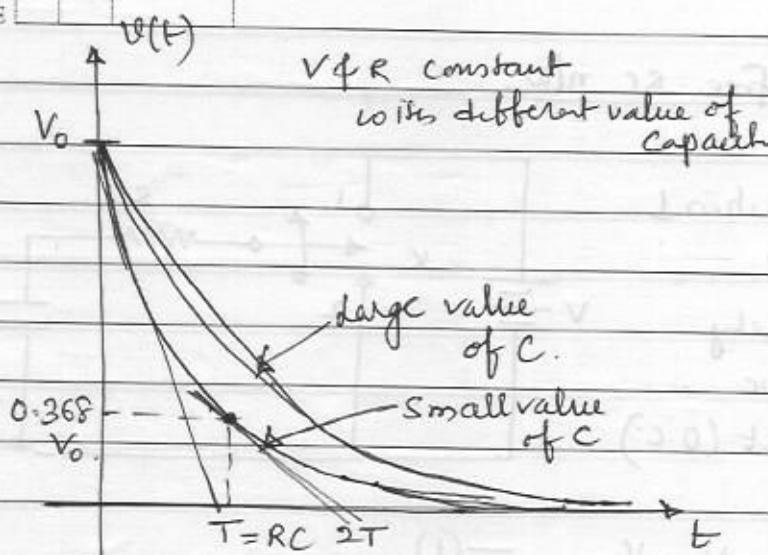

It means voltage a/c the capacitor decays by 37% of initial value in one time constant T .

If a tangent is taken at $t=0$, it indicates that the Voltage a/c capacitor can completely discharge

If is the T state if it decays with initial rate.

- Time constant (T) is used as standard for comparison.

$$C = 100 \text{ pF} \quad R = 100 \Omega \quad RC = 0.1 \text{ msec}$$

$$C = 1 \mu\text{F} \quad R = 1000 \text{ M}\Omega \quad RC = 1000 \text{ sec} \stackrel{?}{=} 17 \text{ sec}$$

Q- The energy stored in capacitor is $C V^2 / 2$, charge flows through the resistor from one plate of cap to the other & energy dissipated in the resistor at the rate $R i^2$. The reduction in energy stored energy due to dissipation reduces the voltage of capacitor to zero. Eventually current

* Current $i_C(t)$..

$$\begin{aligned} i_C(t) &= \frac{dq}{dt} = \frac{d(CV)}{dt} = \frac{d(CV)}{dt} \\ &= C \cdot \frac{d}{dt}(V_0 \cdot e^{-\frac{t}{RC}}) \end{aligned}$$

$$= C V_0 \left(-\frac{1}{RC} \right) e^{-\frac{t}{RC}}$$

$$= -\left(\frac{V_0}{R}\right) \cdot e^{-\frac{t}{RC}}$$

$i_C(t) = -\frac{V_0}{R} \cdot e^{-\frac{t}{RC}}$

-(6)

DATE * Source free RC circuit

Switch is there in position 1 for long time. \therefore Capacitor is charged to applied voltage 'V' and acting as O.C.


$$\therefore \text{At } t < 0; V(0^-) = V \quad \text{--- (1)}$$

Now at $t > 0$, switch position is changed from 1 to 2.

By KCL

$$C \cdot \frac{dv}{dt} + \frac{v}{R} = 0$$
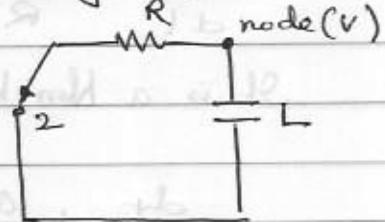
$$\frac{dv}{dt} + \frac{v}{RC} = 0 \quad \text{--- (2)}$$



1st order

W.K.T Above eq² is a homogeneous differential eq²

of form $\frac{dy}{dt} + \frac{a_1}{a_0} \cdot y = 0$.

\therefore Response of such homogeneous differ eq² is

$$y(t) = y(0) \cdot e^{-\frac{a_1}{a_0} \cdot t}$$


$$\frac{a_1}{a_0} = \frac{1}{RC}$$

Hence

$$v(t) = v(0^+) \cdot e^{-\frac{t}{RC}} \quad \text{--- (3)}$$

$$\therefore v(t) = V \cdot e^{-\frac{t}{RC}}$$

from (3) i(t) can be derived as

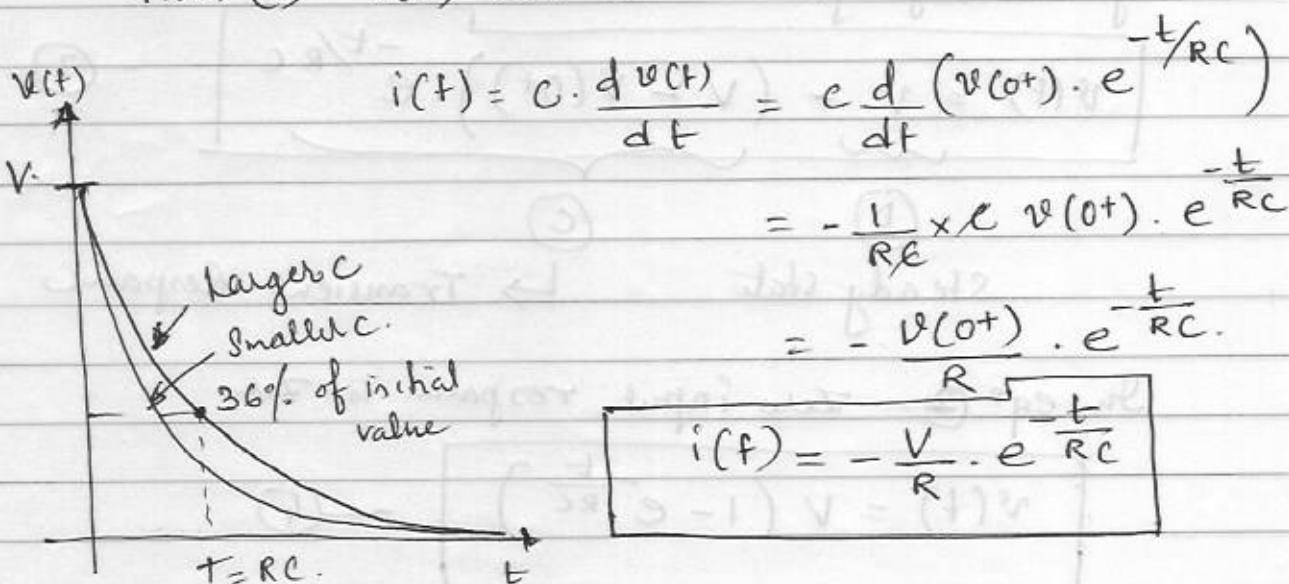

$$i(t) = -\frac{V}{R} \cdot e^{-\frac{t}{RC}}$$


DATE

By KCL

$$C \cdot \frac{dV(t)}{dt} + \frac{V(t) - V_0}{R} = 0$$

$$\frac{dV(t)}{dt} + \frac{V(t)}{RC} - \frac{V_0}{RC} = 0$$
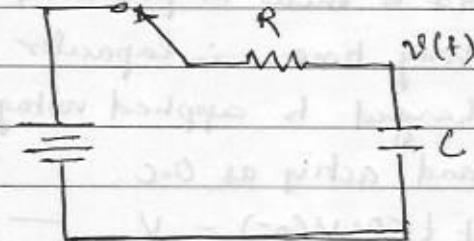
$$\frac{dV(t)}{dt} + \frac{V(t)}{RC} = \frac{V_0}{RC} \quad \text{--- (1)}$$



It is a Non homogeneous differential eq of the form

$$\frac{dy}{dt} + \frac{a_1}{a_0} y = E$$

The response of above eq is

$$y(t) = y(0) \cdot e^{-\frac{a_1 t}{a_0}} + E \left(\frac{a_0}{a_1} \right) \left(1 - e^{-\frac{a_1 t}{a_0}} \right)$$

$$V(t) = V(0^+) \cdot e^{-\frac{t}{RC}} + \frac{V}{RC} \left(1 - e^{-\frac{t}{T}} \right)$$

$$\boxed{V(t) = V(0^+) \cdot e^{-\frac{t}{RC}} + V \left(1 - e^{-\frac{t}{T}} \right)} \quad \text{--- (2)}$$

Zero i/p Resp (A)

(B) forced Response

By rearranging

$$\boxed{V(t) = V - (V - V(0^+)) \cdot e^{-\frac{t}{RC}}} \quad \text{--- (3)}$$

(D)

(C)

Steady state

Transient Response

In eq (3) zero input response is zero.

$$\boxed{V(t) = V \left(1 - e^{-\frac{t}{RC}} \right)} \quad \text{--- (4)}$$


Forced Response

DATE

* Laplace transform

A source free RL ckt
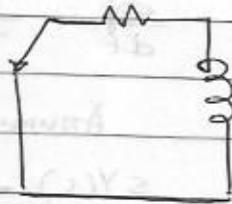
$$L \frac{di}{dt} + Ri = 0 \quad \text{--- (1)}$$



By applying Laplace transform

$$L s \left(\frac{di}{dt} \right) + R i(s) = 0$$

$$L \cdot \left[s I(s) - i(0^-) \right] + R I(s) = 0 \quad \alpha \left(\frac{d(f(t))}{dt} \right) = L$$

$$L s I(s) - L i(0^-) + R I(s) = 0.$$

$$I(s) (Ls + R) = L i(0^+)$$

$$I(s) \left(Ls + R \right) = L \cdot \frac{V}{R}$$

$$I(s) = \frac{L \cdot V}{R (Ls + R)}$$

$$= \frac{V}{R} \times \frac{1}{s + \frac{R}{L}}$$

$$I(s) = \frac{V}{R} \left(\frac{1}{s + R/L} \right)$$

Taking Inverse Laplace transform

$$i(t) = \frac{V}{R} e^{-\frac{R}{L}t}$$

- for a Source driven RL ckt

$$L \frac{di}{dt} + Ri = V \quad \text{--- (1)}$$

taking Laplace transform

$$L \left[s I(s) - I(0^-) \right] + R I(s) = \frac{V}{s}$$

$$L s I(s) - L I(0^-) + R I(s) = \frac{V}{s}$$

$$I(s) [Ls + R] - L \frac{I(0^-)}{s} = \frac{V}{s}$$

$$I(s) [Ls + R] = \frac{V}{s}$$

$$\frac{dy}{dt} + \frac{1}{T} y = E \quad \text{---(1)}$$

Assuming all signals are Laplace transformable

$$sY(s) - y(0^-) + \frac{1}{T} Y(s) = E(s)$$

$$Y(s) (s + \frac{1}{T}) = E(s) + y(0^-)$$

$$Y(s) = \frac{y(0^-)}{(s + \frac{1}{T})} + \frac{E(s)}{(s + \frac{1}{T})}$$

E is constant

$$Y(s) = \frac{y(0^-)}{s + \frac{1}{T}} + \frac{E}{s(s + \frac{1}{T})}$$

combined analysis method

$$\frac{1}{s + \frac{1}{T}} = \frac{1}{s} - \frac{\frac{1}{T}}{s + \frac{1}{T}}$$

General Non-homogeneous 1st order differential eq 2

$$\frac{dy}{dt} + \frac{1}{T} y = E$$

Assuming all signals are Laplace transform

$$sY(s) - y(0^-) + \frac{1}{T} Y(s) = E(s)$$

i.e

$$Y(s) (s + \frac{1}{T}) - y(0^-) = E(s)$$

$$Y(s) = \frac{y(0^-)}{(s + \frac{1}{T})} + \frac{E(s)}{s(s + \frac{1}{T})}$$

E is a constant

$$Y(s) = \frac{y(0^-)}{(s + \frac{1}{T})} + \frac{E}{s(s + \frac{1}{T})}$$

finding roots

$$\frac{E}{s(s + \frac{1}{T})} = \frac{A}{s} + \frac{B}{(s + \frac{1}{T})}$$

$$\frac{E}{s} = A(s + \frac{1}{T}) + BS$$

$$s=0 ; \quad E = \frac{A}{T} \quad A = E/T ET$$

$$s = -\frac{1}{T} ; \quad E = B(-\frac{1}{T}) \therefore B = -ET$$

$$Y(s) = \frac{y(0^-)}{(s + \frac{1}{T})} + \left(\frac{ET}{s} - \frac{ET}{(s + \frac{1}{T})} \right)$$

$$= \frac{y(0^-)}{(s + \frac{1}{T})} + ET \left(\frac{1}{s} - \frac{1}{(s + \frac{1}{T})} \right)$$

$$\boxed{y(t) = y(0^-) e^{\frac{t}{T}} + ET \left(1 - e^{-\frac{t}{T}} \right)} \quad t \geq 0$$

$$i(t) = i(0^-) e^{-\frac{t}{T}} + \frac{V_x K}{R} (1 - e^{-\frac{t}{T}})$$

$$= i(0^-) e^{\frac{t}{T}} + \frac{V_R}{R} (1 - e^{-\frac{t}{T}})$$

- * First order differential eqns have only one time constant
- * These eqns result from network with single inductor (or) capacitor in combination with any number of resistor (or).
- * If more complex nw can be reduced to a single equivalent resistor and single equivalent inductor (or) capacitor

* 4.22) Consider RL drives by voltage source

$$Ri(t) + L \cdot \frac{di}{dt} = V \quad \rightarrow (1)$$

Laplace on both sides

$$R I(s) + L [s I(s) - I(0^-)] = V/s$$

$$I(s) [R + sL] - L \cdot I(0^-) = V/s$$

$$L \frac{d}{dt} f(t)$$

$$= s F(s) - f(0^-)$$

Case(i) Assuming inductor is in closed state initially

$$I(s) [R + sL] = V/s$$

$$I(s) = \frac{V}{s(R + sL)} \quad \text{--- (1)}$$

$$I(s) = \frac{V}{Ls(\frac{R}{L} + s)} \quad \text{--- (2)}$$

$$\frac{V}{Ls(s + \frac{R}{L})} = \frac{A}{s} + \frac{B}{(s + R/L)}$$

$$\frac{V}{L} = A(s + R/L) + BS.$$

$$s = 0$$

$$s = -R/L$$

$$\frac{V}{L} = A(R/L)$$

$$\frac{V}{L} = B(-R/L)$$

$$\boxed{A = \frac{V}{L} \times \frac{L}{R} = \frac{V}{R}}$$

$$\frac{V}{L} \times \frac{R}{R} = -B$$

$$\boxed{B = -V/R}$$

$$\therefore \frac{V}{Ls(s + R/L)} = \frac{V}{Rs} - \frac{V}{R(s + R/L)} = 0$$

$$\text{from (1)} \quad I(s) = \frac{V}{Rs} - \frac{V}{R(s + R/L)}$$

Inverse Laplace transform

$$i(t) = \frac{V}{R} - \frac{V}{R} \cdot e^{-\frac{Rt}{L}}$$

$$\boxed{i(t) = \frac{V}{R} (1 - e^{-R/L t})}$$

Case (ii) : Inductor L ~~not~~ is relaxed state

$$I(s) [R + sL] - L \cdot I(0^-) = \frac{V}{s}$$

$$I(s) = \frac{\frac{V}{s} + L \cdot I(0^-)}{(R + sL)}$$

$$= \frac{V}{s(R + sL)} + \frac{L \cdot I(0^-)}{(R + sL)}$$

$$= \frac{V}{s\left(\frac{R}{L} + s\right)} + \frac{L \cdot I(0^-)}{L\left(\frac{R}{L} + s\right)}$$

$$= \frac{I(0^-)}{\left(s + \frac{R}{L}\right)} + \frac{V}{Ls\left(\frac{R}{L} + s\right)}$$

$$I(s) = \frac{I(0^-)}{\left(s + \frac{R}{L}\right)} + \left(-\frac{V}{Rs} - \frac{V}{R\left(s + \frac{R}{L}\right)} \right)$$

By ILT \Rightarrow

$$\boxed{i(t) = I(0^-) \cdot e^{-\frac{R}{L}t} + \frac{V}{R} \left(1 - e^{-\frac{R}{L}t} \right)}$$


DATE

- 1) Determine the current i_R through resistor at $t = 1\text{ nsec}$.
- $i_R(0) = 6\text{ A}$

$$\text{So: } i(t) = i(0) \cdot e^{-\frac{R}{L}t}$$

$$= 6 \times e^{-\frac{1 \times 10^9}{500 \times 10^{-9}}t}$$



$$i(t) = 6 \times e^{-2 \times 10^9 t}$$

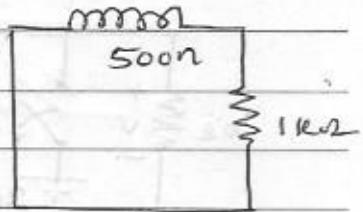At $t = 1\text{ nsec}$

$$i(1\text{ nsec}) = 6 \times e^{-2 \times 10^9 \times 10^{-9}}$$

$$= .812\text{ A} = 812\text{ mA}$$

- 2) Determine the inductor voltage v in the circuit for $t > 0$

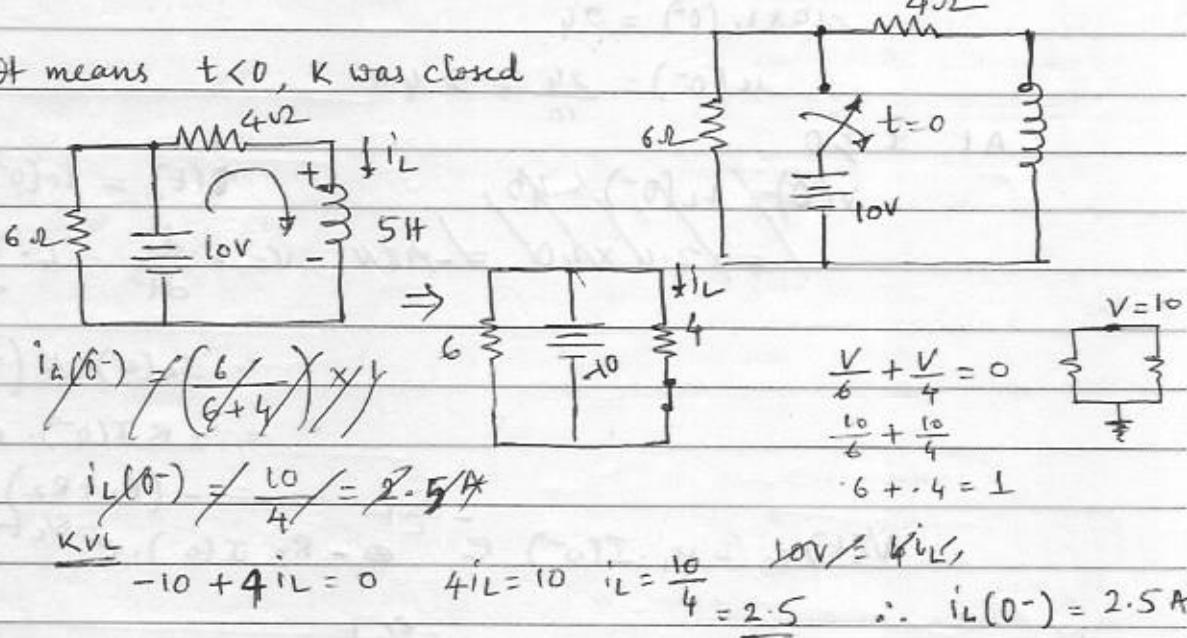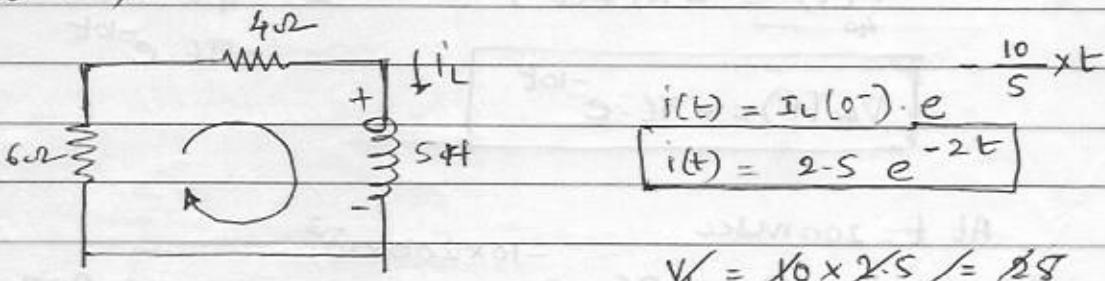It means $t < 0$, K was closedAt $t > 0$ 

$$\rightarrow V_L = L \cdot \frac{di}{dt} = 5 \times \frac{d}{dt}(2.5)$$

$$= L \cdot \frac{d}{dt}(i(0) \cdot e^{-\frac{R}{L}t})$$




$$= 5 \times \left(-\frac{R}{L}\right) i(0+) \cdot e^{-\frac{R}{L}t}$$

$$= -R \cdot i(0+) \cdot e^{-\frac{R}{L}t}$$

$$= -10 \times 2.5 \times e^{-\frac{10}{5}t}$$

$$V_L = -25 e^{-2t}$$

DATE

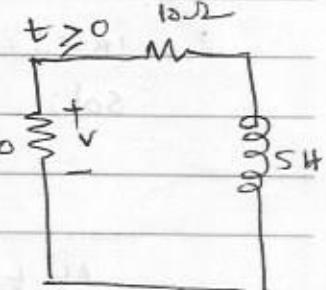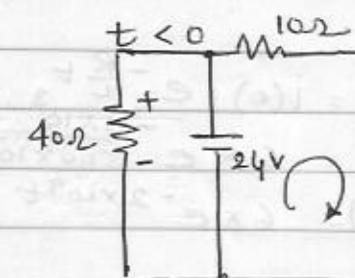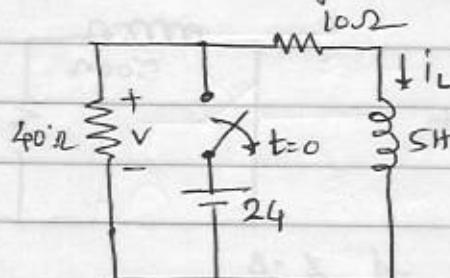(3) find the voltage labeled v at $t = 200 \text{ ms}$ At $t < 0$ for long time, L is sc.

KVL to loop 2

$$10 \times i_L(0^-) = 24$$

$$i_L(0^-) = \frac{24}{10} = 2.4 \text{ A.}$$

At $t > 0$

$$v(t) = i_L(0^-) \times 4\Omega,$$

$$= -2.4 \times 4\Omega = -9.6 \text{ V}$$

$$i(t) = I_0(0^-) \cdot e^{-\frac{R}{L}t}$$

$$= I_0(0^-) \cdot e^{-\frac{R}{L}t}$$

$$= -R I(0^-) \cdot e^{-\frac{R}{L}t}$$

$$= -(R_1 + R_2) I(0^-) \cdot e^{-\frac{R}{L}t}$$

$$v(t) = -R_1 \cdot I(0^-) \cdot e^{-\frac{R}{L}t} - R_2 \cdot I(0^-) \cdot e^{-\frac{R}{L}t}$$

$$v(t) = -R_2 I(0^-) \cdot e^{-\frac{R}{L}t} = -40 \times 2.4 \times e^{-\frac{50}{5}t}$$


$$= -96 \cdot e^{-10t}$$

$$\boxed{v_{40}(t) = -96 \cdot e^{-10t}}$$



At $t = 200 \text{ ms}$

$$v_{40}(t) = -96 \times e^{-10 \times 200 \times 10^{-3}} = -12.992 \text{ V}$$

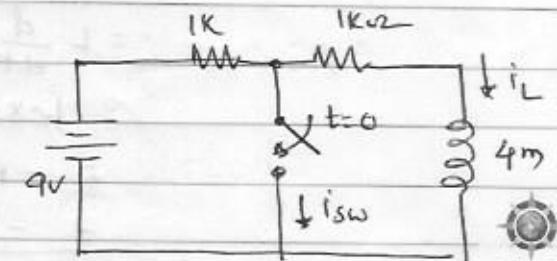* (4) After being in the configuration shown for hours, the switch in the circuit is closed at $t = 0$. At $t = 5 \text{ sec}$
Calculate a) i_L b) i_{sw}



DATE

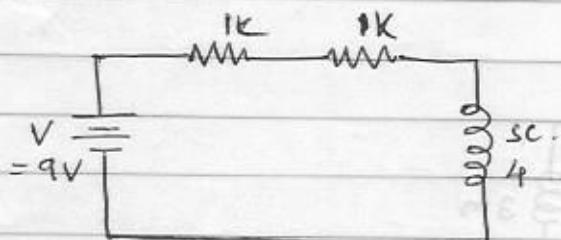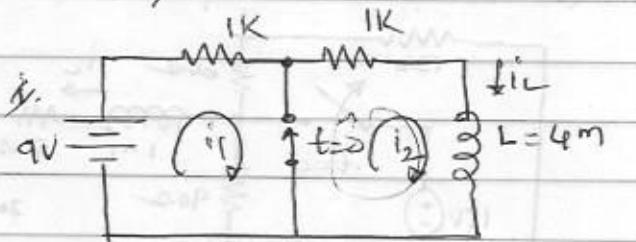At $t < 0$  $t > 0$ 

$$i_L(0^-) = \frac{V}{R} = \frac{9V}{2k} = 4.5mA$$

$$i_L(t) = i(0^+) \cdot e^{-\frac{R}{L} \cdot t}$$

$$= 4.5 \times 10^{-3} e^{-\frac{1k}{4m}}$$

$$i_L(t) = 4.5 \times 10^{-3} e^{-0.25 \times 10^6 t}$$

$$\text{At } t = 500\mu\text{s} \quad i(500\mu\text{s}) = 4.5 \times 10^{-3} e^{-0.25 \times 10^6 \times 500 \times 10^{-6}} = 1.289mA$$


$$i_{sw} = i_1 - i_L = \frac{9V}{1 \times 10^3} - 1.289mA$$

$$= 9mA - 1.289mA$$

$$i_{sw} = 7.71mA$$


* (5) Assuming the switch has been in position drawn in fig for long time, Determine the value of $v + i_L$

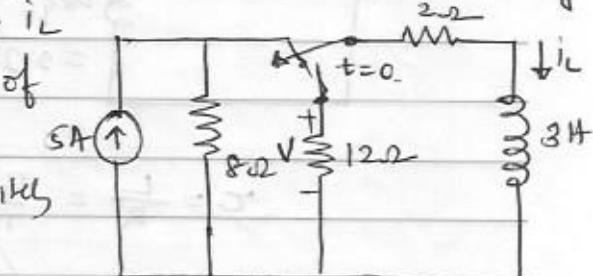a) the instant just before prior of changing position of switch




b) the instant just after the switch changes position

Ans:

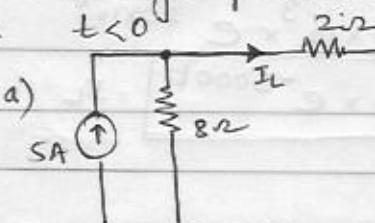

$$i_L = \left(\frac{8}{8+2}\right) \times 5 = 4A$$

$$i_L(0^-) = 4A \quad v = 0V$$

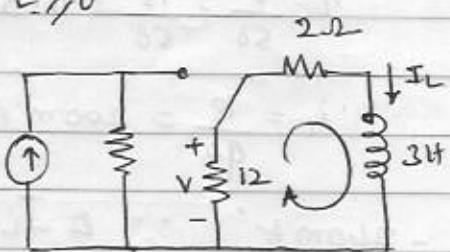
b) $t > 0$ 

$$i_L(0^+) = i_L(0^-) = 4A$$

$$v = -i_L(0^+) \times 12$$

$$= -4 \times 12 = -48V$$


DATE

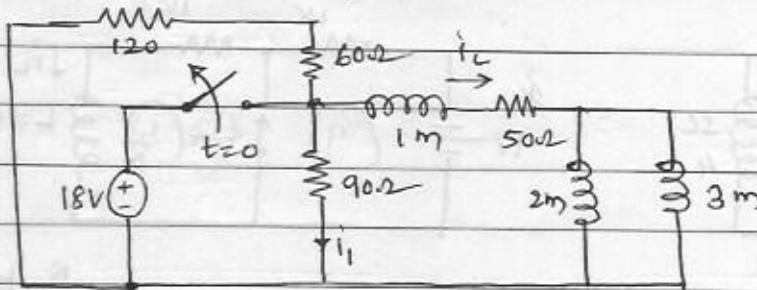(6) Determine both i_1 and i_L in the cktAt $t < 0$

$$R_{eq} = \left(\frac{2m \times 3m}{2m + 3m} + 1 \right)$$


$$= 2.2 \text{ mH}$$

$$R_{eq} = \left(\frac{90 \times 180}{90 + 180} \right) + 50 = 110 \text{ } \cancel{\Omega}$$

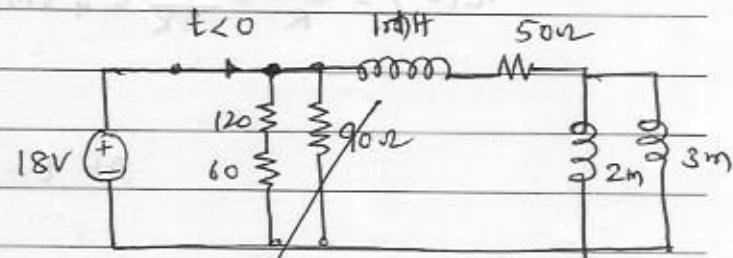At $t = 0$; switch is disconnected

$$R_{eq} = 110 \Omega$$


$$= 2.2 \text{ mH}$$

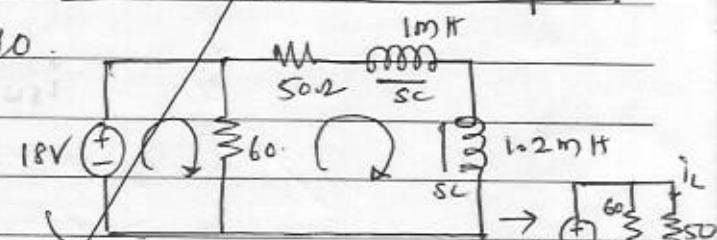

$$\tau = \frac{L}{R} = \frac{2.2 \text{ m}}{110} = 20 \mu \text{sec}$$


$$i(t) = I(0^+) \cdot e^{\frac{-t}{20\mu\text{s}}} = 360 \times 10^{-3} \times e^{-\frac{t}{20 \times 10^{-6}}}.$$

$$i_L(t) = 360 \times e^{-5000t} = i_L$$

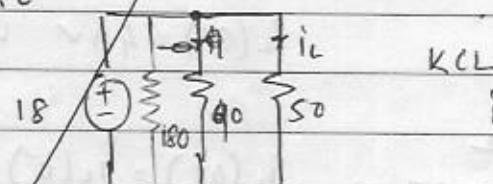At $t < 0$ 

KCL

$$i_L = \frac{V}{50} = \frac{18}{50} = 0.36 \text{ A} = 360 \text{ mA}$$

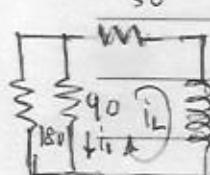
At $t > 0$ 

Current Divider

$$i_1(0^+) = \frac{(i_L(0^-) \times 180)}{180 + 90} = -240 \text{ mA} \quad \because i_L \text{ opposite to } i_1$$

$$i_1(t) = -240 e^{-5000t}$$

DATE

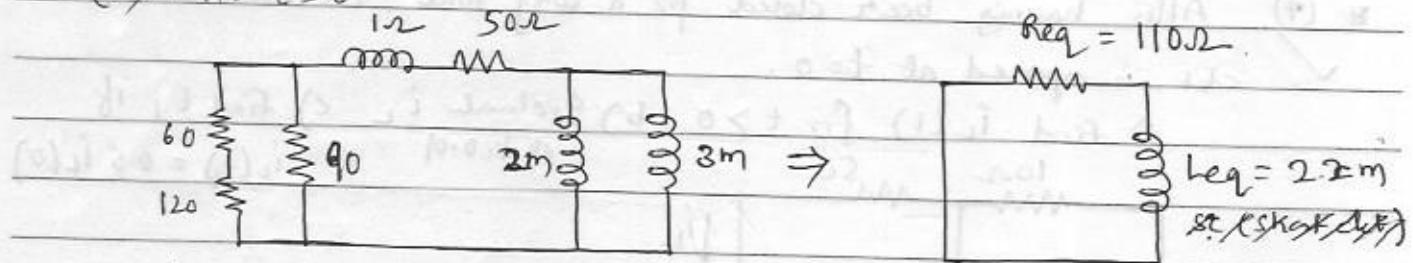(b) At $t=0$ At $t > 0$


$$Req = \left(\frac{90 \times 180}{90+180} \right) + 50 = 110\Omega$$

$L_{eq} = 2.2mH$

$$L_{eq} = \frac{3m \times 2m}{(3+2)m} H = 2.2mH$$

$$T = \frac{L}{R} = \frac{2.2m}{110} = 20ms$$

$$i_L(t) = i_L(0^+) \cdot e^{-\frac{t}{T}} = \frac{i_L(0^+)}{360} \cdot e^{-\frac{t}{20ms}} \text{ mA} = I(0^+) \cdot e^{-\frac{5000t}{1}} \text{ mA}$$

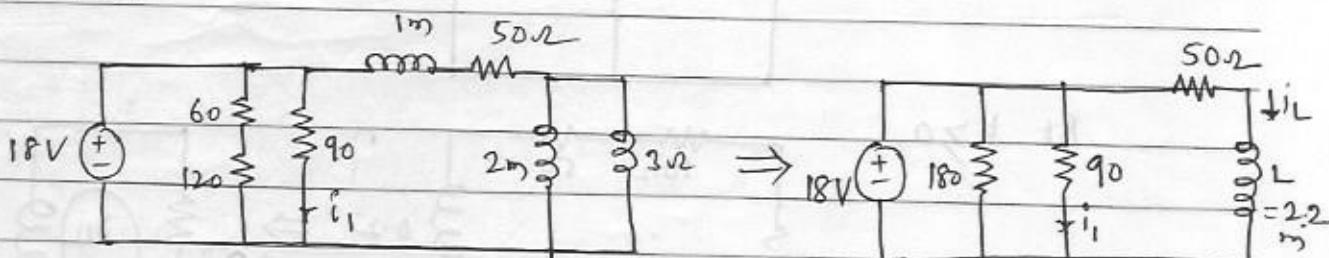At $t < 0$ 

By KCL


$$I_L = i_L(0^-) = \frac{18}{50} \text{ mA}$$

$$\frac{i_L(0^-) V}{90} = \frac{18}{90} = 200mA$$

$$\therefore i_L(0^+) = i_L(0^-) = 360mA$$

Hence @ $t > 0$

$$i_L(t) = 360 e^{-\frac{5000t}{1}} \text{ mA}$$

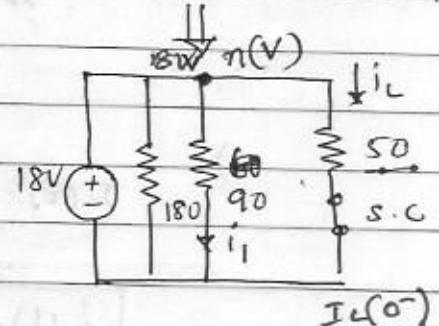At $t > 0$; Using current divider

$$i_L(0^+) = I_L(0^+)$$

$$i_L(0^+) =$$

$$\text{There is No restriction on } i_1 \quad i_1(0^+) = -\left(\frac{180}{90+180}\right) i_L(0^+)$$


changing instantaneously

at $t=0$ as it

current through Return.

$$\text{So if value @ } t=0^- \text{ is } i_1(0^-) = 200mA$$

$$\text{& } i_1(0^+) = -240mA$$

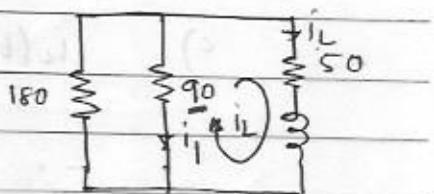

$$= -\left(\frac{180}{270} \times 360 \text{ mA}\right)$$

$$i_1 = -\left(\frac{180}{180+90}\right) \cdot 26$$

$$i_1(t) = -240 e^{-\frac{5000t}{1}} \text{ mA}$$


DATE

- * (4) After having been closed for a long time, the switch in the circuit is opened at $t=0$.


a) find $i_L(t)$ for $t > 0$ b) Evaluate i_L c) find t_1 if

≈ 0.01

$$i_L(t_1) = 0.5 i_L(0)$$

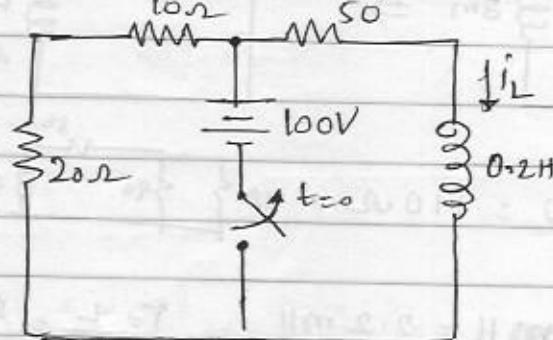


At $t < 0$

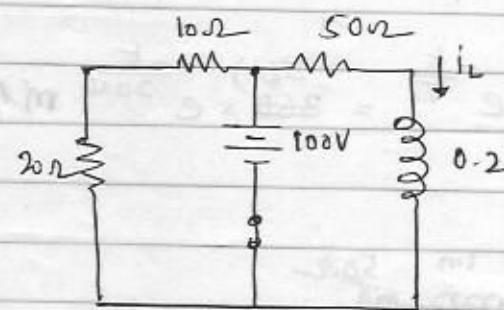

$$i_L(0^-) = \frac{V}{R} = \frac{100}{50} = 2A$$

At $t > 0$

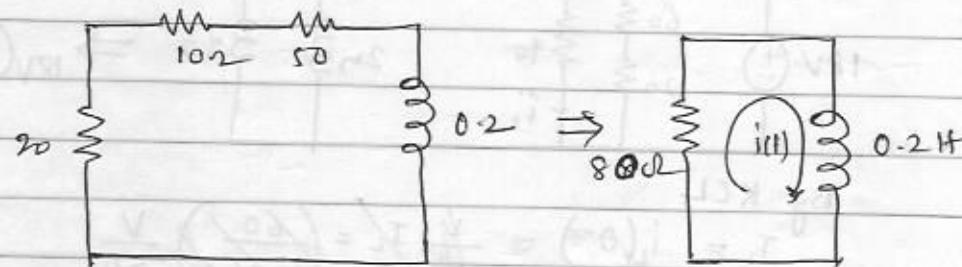

a)

$$i_L(t) = i(0^+) \cdot e^{-\frac{t}{T}}$$

$$= 2 \cdot e^{-\frac{t}{2.5 \times 10^{-3}}}$$

$$i_L(t) = 2 \cdot e^{-400t} \text{ A}$$

$$T = \frac{L}{R} = \frac{0.2H}{8\Omega} = 2.5 \times 10^{-3} \text{ sec}$$

$$= 2.5 \text{ msec}$$

b) $i_L(0.01) = 2e^{-400 \times 0.01} = 0.0366 \text{ A} = 36.6 \text{ mA}$

c)

$$i_L(t_1) = 0.5 i_L(0^+)$$

$$= 0.5 \times 2 = 1$$

$$\therefore 1 = 2 \cdot e^{-400t_1}$$

$$\frac{1}{2} = e^{-400t_1}$$

$$400t_1 = \ln(2)$$

$$400t_1 = 0.6931 \quad \therefore t_1 = 1.7328 \text{ sec}$$

$$i_L(t_1) = 2 \cdot e^{-400t_1}$$

$$0.5 i_L(0^+) = 2 \cdot e^{-400t_1}$$

$$0.5(2) = 2 e^{-400t_1}$$


$$\frac{1}{2} = e^{-400t_1}$$

$$e^{400t_1} = 2$$


DATE

* (8) a) find $V_C(t)$ for all time in the circuit

b) At what time is $V_C = 0.1 V_C(0)$

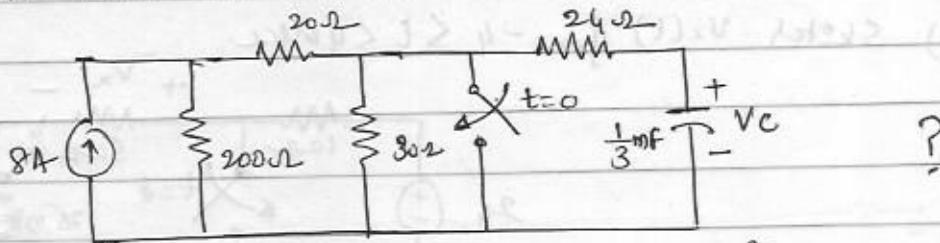


At $t \leq 0^-$ $V_C(0^-)$

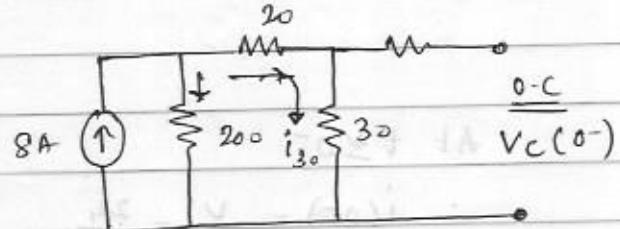

a).

$$i_{30} = \left(\frac{200}{200+30} \right) 8 = 6.4 \text{ A}$$
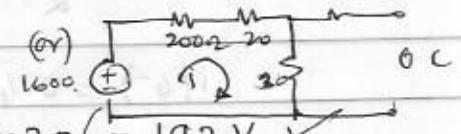
$$V_C(0^-) = i_{30} \times 30 = 6.4 \times 30$$



$$i = \frac{1600}{200+20+30} = 6.4 \text{ A}$$

$$V_C(0^-) = 6.4 \times 30 = 192 \text{ V.}$$

$$T = RC = 24 \times \frac{1}{3} \times 10^{-3} = 8 \times 10^{-3}.$$

At $t \geq 0^+$

$$V_C(t) = V_C(0^+) \cdot e^{-\frac{t}{RC}}$$

$$= 192 \cdot e^{-\frac{t}{8 \times 10^{-3}}}$$

$$V_C(t) = 192 e^{-125t}$$

$$b) V_C(t) = 192 \cdot e^{-125t}$$

$$0.1 V_C(0) = 192 \cdot e^{-125t}$$

$$0.1 \times 192 = 192 \cdot e^{-125t}$$


$$e^{-125t} = 0.1 \quad e^{125t} = 10.$$

$$125t = \ln(10)$$

$$t = \frac{2.30}{125} = 0.018 \text{ sec}$$

$$= 18.4 \text{ msec}$$
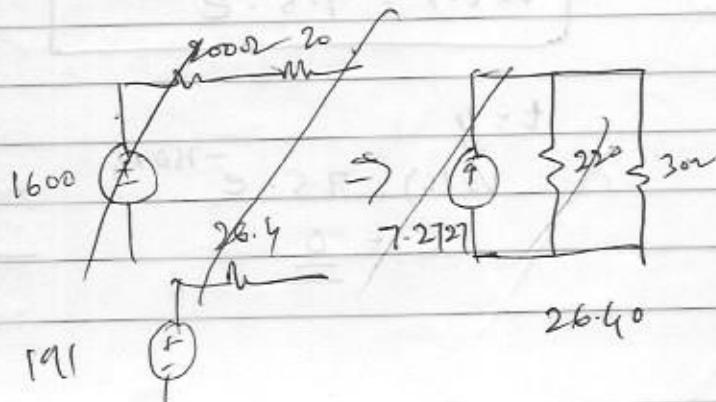
$$\underline{\underline{t = 18.4 \text{ msec}}}$$




$$I_C(t) = 0.5 jy(0) \\ - 0.5x.$$

* (9) Switch has been open for long time before it closes at $t=0$.

✓ a) Find $i_L(t)$ for $t > 0$.


b) Sketch $v_x(t)$ for $-4 < t < 4$ msec

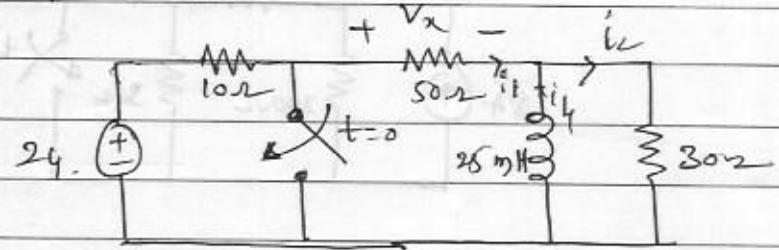

At $t \leq 0^-$

$$\therefore i(0^-) = \frac{V}{R} = \frac{24}{60} = 0.4 \text{ A}$$

$$i(0^-) = 0.4 \text{ A}$$

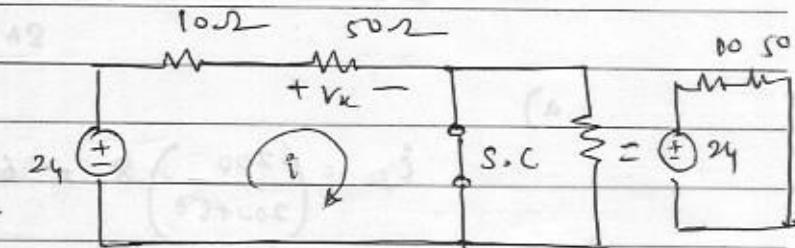

$$v_x(0^-) = 0.4 \times 50 = 20 \text{ V}$$

At $t \geq 0^+$

$$i(0^+) = i(0^-)$$

$$i_L(t) = i(0^+) \cdot e^{-\frac{t}{T}}$$

$$= 0.4 \cdot e^{-\frac{t}{1.333 \text{ msec}}}$$

$$i_L(t) = 0.4 e^{-750t}$$

$$R_m = \frac{50 \times 30}{50 + 30} = 18.75 \Omega$$

$$T = \frac{L}{R} = \frac{25 \times 10^{-3}}{18.75} = 1.333 \text{ msec}$$

Current through resistor $i_1 = \left(\frac{30}{30+50}\right) \times i_L(0^+) = \frac{30}{80} \times 0.4 = 0.15 \text{ A}$


Instantaneously $v_x(0^+) = 0.15 \times 50 = 7.5 \text{ V}$

$$v_x(t) = 7.5 \cdot e^{-750t}$$

$$t = 4$$


$$v_x(4) = 7.5 \cdot e^{-750 \times 4}$$

$$= 0$$

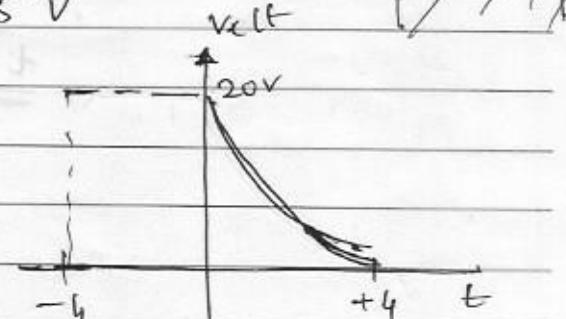

$$\frac{V - 24}{R} + \frac{1}{L} \int i dt + \frac{V}{Z_0} = 0$$

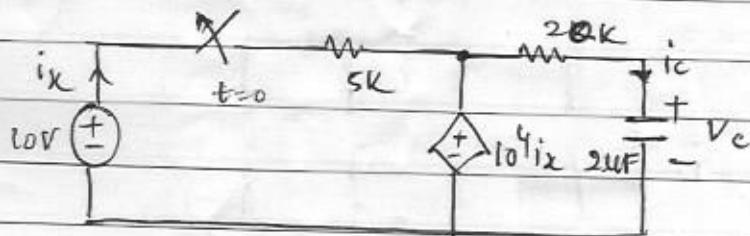(5) Determine $V_c(t)$ and $i_c(t)$ for the ckt and sketch the curves



KVL @ loop 1

$$-10 + 5000 ix + 10^4 ix = 0.$$

$$(5000 + 10^4) ix = 10$$

$$ix = 10 / (5000 + 10^4) = 0.666 \text{ mA}$$


$$\therefore V_c(0-) = 10^4 ix = 10^4 \times 0.666 \text{ mA} = 6.667 \text{ V} = V_c(0+)$$

At $t=0+$

$$\begin{aligned} V_c(t) &= V_c(0+) \cdot e^{-\frac{1}{RC} t} \\ &= 6.667 e^{-\frac{1}{20 \times 10^3 \times 2 \times 10^{-6}} t} \\ &= 6.667 e^{-\frac{1}{0.04} t} \\ \boxed{V_c(t) &= 6.667 e^{-25t}.} \end{aligned}$$

$$i_c(t) = C \cdot \frac{dV_c(t)}{dt} = 2 \times 10^{-6} \frac{d}{dt} (6.667 e^{-25t})$$
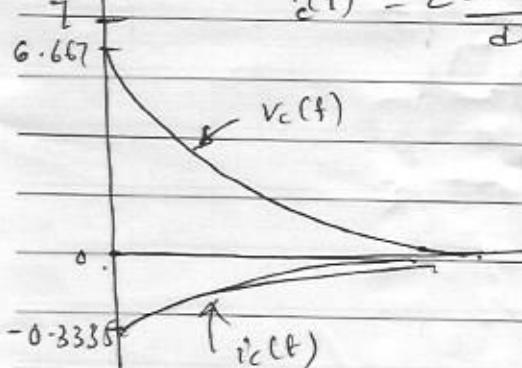
$$\begin{aligned} &= 2 \times 10^{-6} \times 6.667 \times (-25) \cdot e^{-25t} \\ &= -0.3335 \times 10^{-3} e^{-25t} \end{aligned}$$




DATE

DATE

(10) $V(t) = 56 e^{-200t}$ & $i(t) = 8 \cdot e^{-200t}$ for $t > 0$.

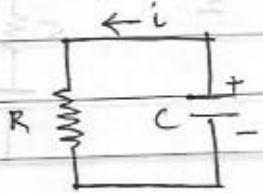- a) find the value of $R + C$. b) calculate τ c) determine time required for the voltage to decay half its initial value at $t = 0$.



a) $R = \frac{V(t)}{i(t)} = \frac{56 e^{-200t}}{8 e^{-200t}} = 7 \text{ k}\Omega$

$\frac{1}{RC} = 200 \quad \therefore C = \frac{1}{R \cdot 200} = \frac{1}{7 \text{ k} \times 200} = 0.714 \text{ nF}$


b) $\frac{1}{RC} = 200 \quad \therefore \tau = RC = \frac{1}{200} = 5 \text{ msec}$

c) $V(t) = 56 e^{-200t} \quad 28 = 56 e^{-200t} \quad \frac{1}{2} = e^{-200t}$


$\ln(0.5) = -200t$

$t = 3.4657 \text{ msec}$


- (11)(2) Find time constant for RC ckt

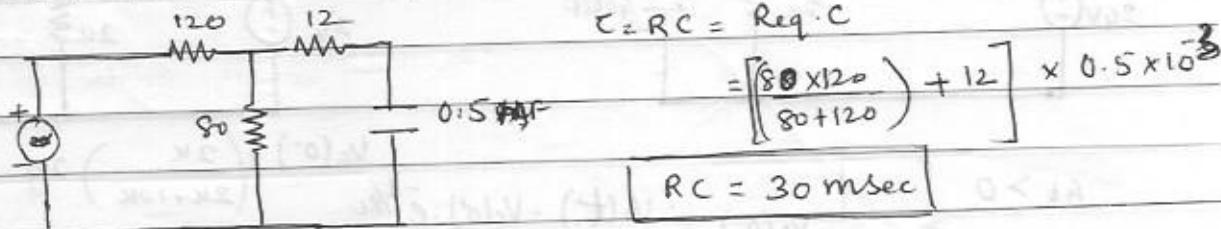

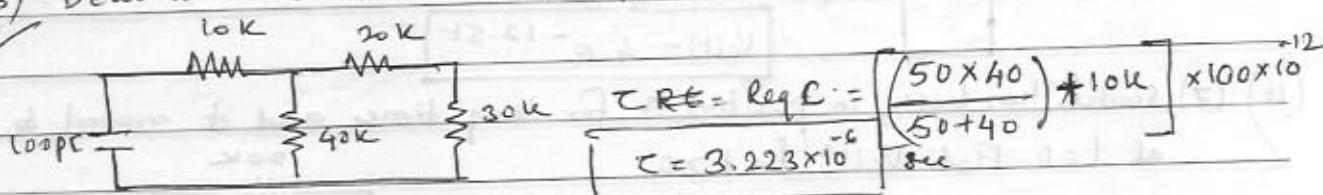
- (12)(3) Determine the time constant for the ckt



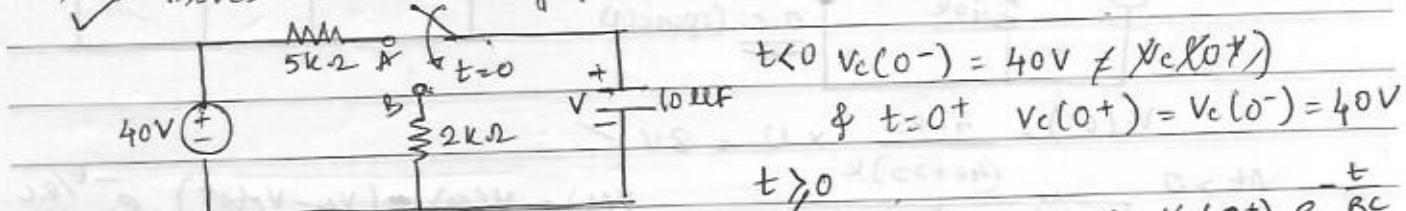- (13)(4) The switch has been in position A for long time. Assume the switch moves instantaneously from A to B at $t = 0$. find V for $t > 0$.



$$\begin{aligned} V_c(t) &= V_0(e^{At}) \cdot e^{-\frac{t}{RC}} \\ &= 40 e^{-\frac{t}{2 \times 10 \times 10 \times 10^{-9}}} \\ &= 40 e^{-\frac{t}{0.2}} \\ V_c(t) &= 40 e^{-50t} \end{aligned}$$

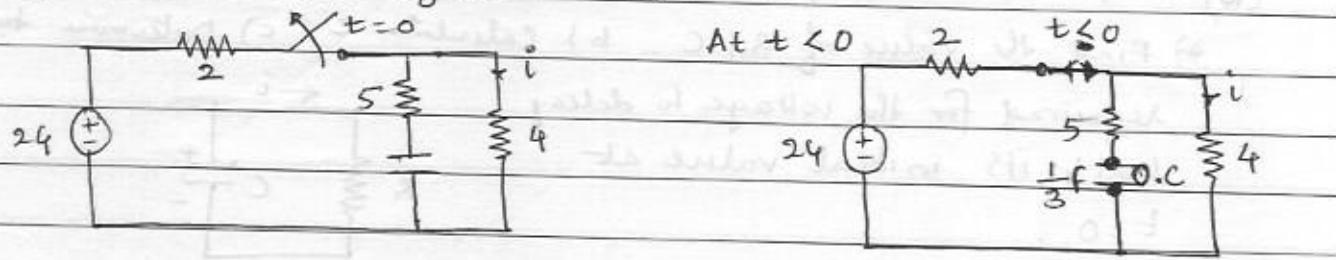(14) (5) Circuit shown in fig. find $i(t)$, $t > 0$.

C u O.C.

At $t > 0$

$$i = 24 / (2 + 4) = 4 \text{ A}$$

$$V_c(t) = V_c(0^+) \cdot e^{-\frac{t}{RC}}$$


$$i(0^-) = 4 \text{ A} = i(0^+)$$

$$= 16 \cdot e^{-t/4 \times \frac{1}{3}} \therefore V_c(0^-) \text{ is } .$$

$$V_c(t) = 16 \cdot e^{-t/3}$$

$$-24 + 2 \times 4 + V_c(0^-) = 0$$

$$V_c(0^-) = 24 - 8 = 16 \text{ V ?}$$

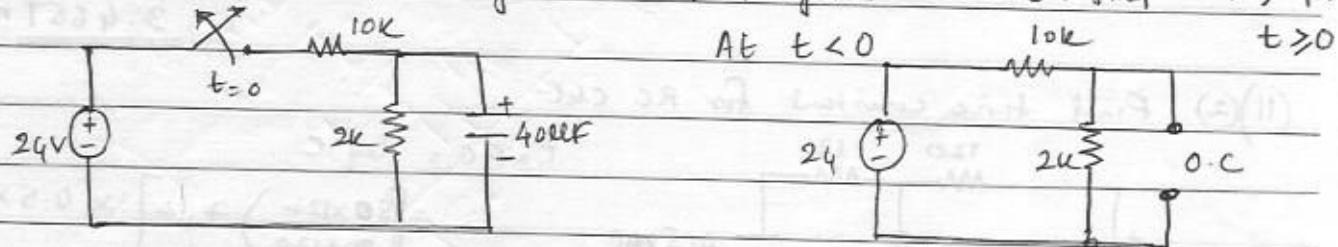(15) (6) Switch is closed for long time and it opens at $t=0$. Find $V_c(t)$ for

$$V_c(0^-) = \left(\frac{2k}{2k + 10k} \right) 24 = 4 \text{ V}$$


At $t > 0$

$$\frac{2k}{2k + 10k} V_c(0^+) = 4 \text{ V}$$

$$V_c(t) = V_c(0^+) \cdot e^{-t/RC}$$

$$= 4 \cdot e^{-t/2k \times 400 \times 10^{-9}} \therefore V_c(0^+) = V_c(0^-) = 4 \text{ V}$$

$$V_c(t) = 4 \cdot e^{-12.5t}$$

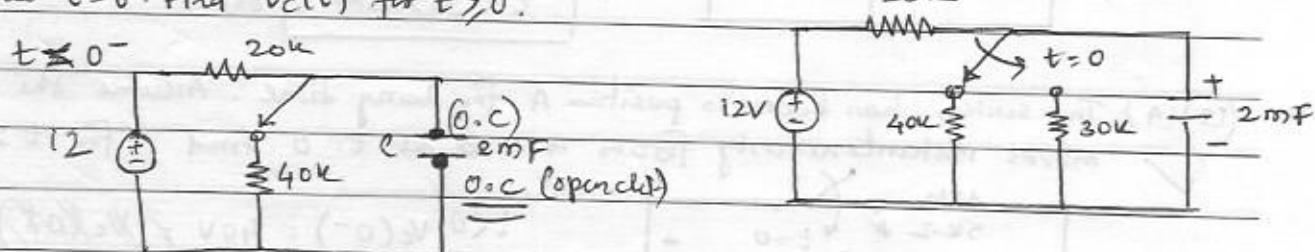(16) (7) Switch has been in position A for long time and it moved to position B at $t=0$. Find $V_c(t)$ for $t > 0$.

$$V_c(0^-) = \frac{40k}{40k + 20k} \times 12 = 8 \text{ V }$$

At $t > 0$

$$\frac{20k}{(40+20)k} \times 12 = 7.2 \text{ V}$$

$$V(t) = V(\infty) + (V_{0^-} - V_c(0^+)) \cdot e^{-t/RC}$$

$$= 7.2 + (7.2 - 8) e^{-t/RC}$$

$$= 7.2 + 0.8 e^{-t/RC}$$

$$(or) V(t) = V_c(0^+) e^{-t/RC} + V_0 (1 - e^{-t/RC})$$


$$= 8e^{-t/RC} + 7.2 (1 - e^{-t/RC})$$

$$= 8e^{-t/RC} + 7.2 - 7.2 e^{-t/RC}$$

$$= 7.2 + 10 e^{-t/RC}$$

DATE

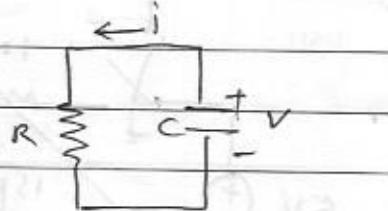(17)(8) $V = 10 \cdot e^{-4t}$ $i = 0.2 e^{-4t} A$ $t > 0$.



a) find R and C b) time constant τ

c) Calculate initial energy

d) Time it takes to discharge 50% of initial energy

a) $R = \frac{V}{i} = \frac{10}{0.2} = 50 \Omega$ $\therefore RC = 4$ $C = \frac{4}{50} = 5 \text{ mF}$


b) $\tau = RC = \frac{1}{RC} = 4 \quad \therefore RC = \frac{1}{\tau} = 0.25 \text{ msec}$

c) Initial energy

$$W_C(0) = \frac{1}{2} CV^2 = \frac{1}{2} \times 5 \times 10^{-3} \times (10)^2 = 0.25$$

d) ?

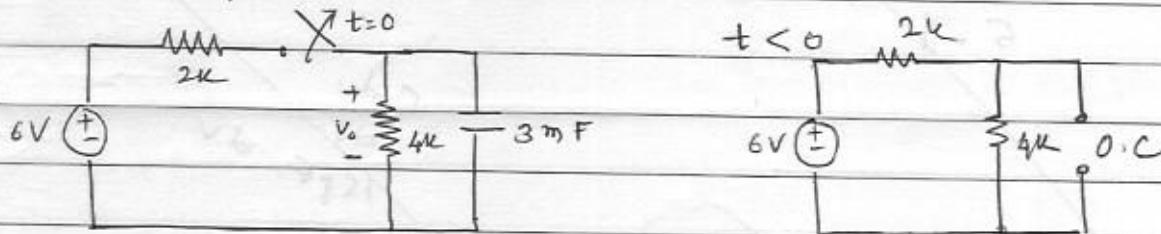(18)(9) Switch is open at $t=0$. find V_o for $t > 0$





$$V_C(0-) = \left(\frac{4k}{4k+2k} \right) \times 6 = 4V$$

At $t > 0$

$$\begin{aligned} V_C(t) &= V_C(0+) \cdot e^{-t/RC} \\ &= 4 \cdot e^{-t/(4k \times 3m)} \\ &= 4 \cdot e^{-t/12} = 4 \cdot e^{-0.0833t}. \end{aligned}$$

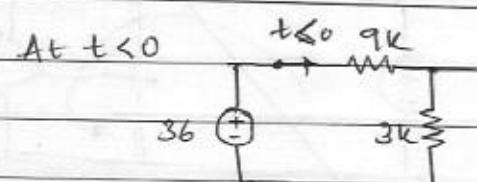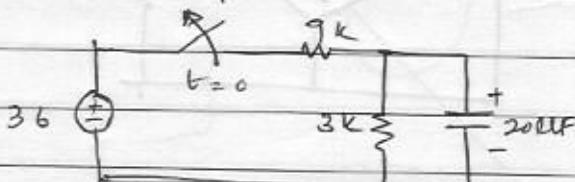(19)(10) Find $V_C(t)$ for $t > 0$ & find the time necessary for cap voltage to decay to $\frac{1}{3}$ rd of the value at $t=0$



$$V_C(0-) = \left(\frac{3k}{3k+9k} \right) \times 36 = 9V$$

At $t > 0$


$$V_C(t) = V_C(0+) \cdot e^{-t/RC}$$

$$= 9 \cdot e^{-t/(3 \times 20 \times 10^{-6})} = 9 \cdot e^{-\frac{t}{60m}}$$

$$\frac{1}{3} \times 9 = 9 \cdot e^{-\frac{t}{60m}}$$

$$3 = 9 \cdot e^{-16.67t} \Rightarrow \frac{3}{9} = e^{-16.67t} \therefore [t = 65.89 \text{ msec}]$$

DATE

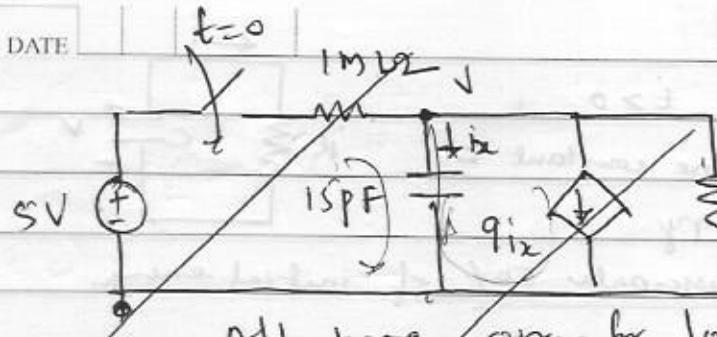


After being open for long time, the switch closes at $t=0$. Find $V_1(t)$ for $t>0$

$$i(0^-) = 0^- ; i(0^+)$$

if $t=0^-$:

$$i_L(0^-) = 0$$

$t=0^-$

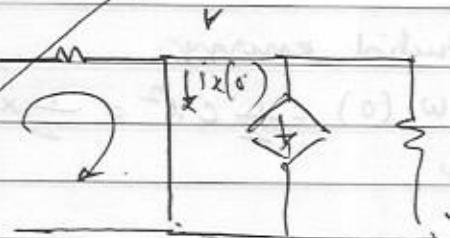

$5 - i$


$$C \frac{dv}{dt} + i_L$$

$$\frac{v - 5}{i} + C \frac{dv}{dt} + q_{ix} + \frac{v}{2m} = 0$$

$$v - 5 + i_L + q_{ix} + \frac{v}{2 \times 10^3} = 0$$

$$C \frac{dv}{dt}$$

$$V_1(t) =$$

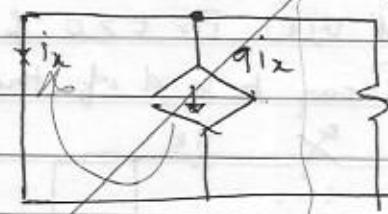

DATE

4.21) The circuit shown in fig consists of a resistor and a relay with inductance L. The relay is adjusted so that it is activated when current through the coil is 0.008 Amps. The switch K is closed at $t=0$, and observed that the relay is activated when $t=0.1$ sec.


Find a) Inductance L of coil b) the equation $i(t)$

$$\text{Sol: } i(t) = 0.008 \text{ A}$$

$$t = 0.1 \text{ sec.}$$

$$\begin{aligned} 4T &= 0.1 \\ \frac{4L}{R} &= 0.1 \\ L &= 0.1 \times R \end{aligned}$$

With other all terms evaluated

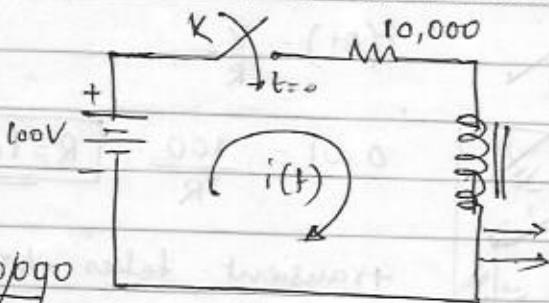

$$i(0^-) = 0 \text{ as } K \text{ is open.}$$

At $t > 0$

$$i(\infty) = \frac{V}{R} = \frac{10,000}{10,000} = 0.01 \text{ Amps.}$$

$$i(t) = i(\infty) - (i(\infty) - i(0^+)) \cdot e^{-\frac{R}{L}t}$$

$$= 0.01 - (0.01 - 0) \cdot e^{-\frac{10000}{L}t}$$

$$i(t) = 0.01 - 0.01 \cdot e^{-\frac{10000}{L}t}$$

$$\text{At } t = 0.1 \text{ sec, } i(0.1) = 0.0008 \text{ A}$$

$$0.0008 = 0.01 - 0.01 \cdot e^{-\frac{10000 \times 0.1}{L}}$$

$$f 0.2 = f 0.01 e^{-\frac{1000}{L}} = e^{-\frac{1000}{L}}$$

$$\cdot \ln(0.2) = -1000/L$$

$$f 1.6094 = f 1000/L$$

$$i(t) = 0.01 (1 - e^{-\frac{16.094}{L}t})$$

$$L = \frac{1000}{1.6094} = 621.349 \text{ H}$$

$$b) i(t) = \frac{V}{R} - \left(\frac{V}{R} - i(0^+) \right) e^{-\frac{R}{L}t}$$

$$= \frac{100}{10,000} - \left(\frac{100}{10,000} - 0 \right) e^{-\frac{10000}{621.349}t}$$

$$i(t) = 0.01 - 0.01 \times e^{-16.094t}$$

DATE

4.20) In the circuit shown, switch K is closed at $t=0$. The current waveform is observed with CRO. The initial value of current is measured to be 0.01 Amps. The transient appears to disappear in 0.1 sec. find


a) the value of R b) the eq² of $i(t)$

so:

$$\text{At } t=0; i(0^+) = 0.01 \text{ Amps.}$$

$$i(0^+) = \frac{V}{R}$$
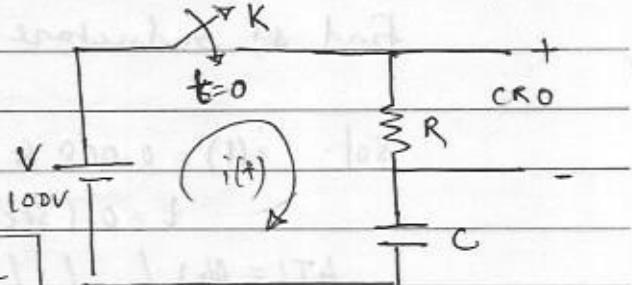
$$0.01 = \frac{100}{R} \quad \boxed{R = 10k\Omega}$$



transient takes $4T$ approximately to disappear

$$4T = 0.1 \text{ sec}$$

$$4RC = 0.1$$

$$4 \times 10 \times 10^3 C = 0.1$$

$$C = \frac{0.1}{4 \times 10 \times 10^3} = 2.5 \mu\text{F}$$

$$i(t) = \frac{V_0}{R} e^{-t/RC} + \frac{V}{R} e^{t/RC}$$

$$= \frac{100}{10000} \cdot e^{-t/0.25}$$

$$i(t) = 0.01 \cdot e^{-t/0.25} + \frac{100}{10 \times 10^3} (1 - e^{-t/0.25})$$

$$v(t) = V - (V - v(0^+)) e^{-t/RC}$$

$$= 100 - (100 - v(0^+)) e^{-t/0.25}$$

$$v(t) = 100 - (100 - v(0^+)) e^{-4t}$$

$$c \cdot \frac{dv}{dt} = (c \cdot 100 \times -4) - v(0^+)(-4) e^{-4t}$$

$$= -400c + 4v(0^+) e^{-4t}$$

$$v(t) = v(0^+) e^{-t/RC} + V(1 - e^{-t/RC})$$

$$i(t) = \frac{d}{dt} v(t)$$

$$= c \cdot v(0^+) \left(-\frac{1}{RC} \right) e^{-t/RC}$$

$$+ c \cdot V \left(-\frac{1}{RC} \right) e^{-t/RC}$$

$$i(t) = \frac{V}{R} e^{-t/RC}$$

$$= -\frac{100}{10 \times 10^3 \times 2.5 \times 10^{-6}} e^{-t/0.025}$$

$$= +0.01 \cdot e^{-t/0.025}$$

$$\boxed{i(t) = +0.01 \cdot e^{-40t}}$$

$$= -\frac{1}{R} (V(0^+) + V) e^{-t/RC}$$

$$= -\frac{V_0 + V}{R} e^{-t/RC} - \frac{V}{R} e^{-t/RC}$$

DATE

- 423) Consider the exponentially decreasing function $i = K \cdot e^{-t/T}$ where T is time constant. Let the tangent drawn from the curve at $t=t_1$ intersect the line $i=0$ at t_2 . Show that for any such point, $i(t_1)$, $t_2 - t_1 = T$.

$$i = K \cdot e^{-t/T}$$

slope of i can be found by taking derivative of i

$$\therefore \frac{di}{dt} = \frac{d(K \cdot e^{-t/T})}{dt}$$

$$\left[\frac{di}{dt} = -\frac{K}{T} \cdot e^{-t/T} \right] \quad -(1)$$

eq(1) is slope at any time t :

\therefore Slope at time t_1 .

$$\left[\frac{di}{dt} = -\frac{K}{T} e^{-t_1/T} \right] \quad -(2) \quad \& \quad i(t_1) = K \cdot e^{-t_1/T}$$

$$\left[\tan \theta = \frac{i(t_1)}{\tan(180-\theta)(t_2-t_1)} = \frac{K \cdot e^{-t_1/T}}{(t_2-t_1)} \right] \quad -(3) \quad \therefore -\tan \theta = \frac{K \cdot e^{-t_1/T}}{(t_2-t_1)}$$

equating (2) & (3)


$$\frac{t_1}{T} = \frac{-t_1}{t_2 - t_1}$$

$$\therefore T = t_2 - t_1$$

(\rightarrow) sign indicates that the curve is decreasing.

t_2 - time at which the tangent taken on curve at t_1 intersects the $i=0$ line.

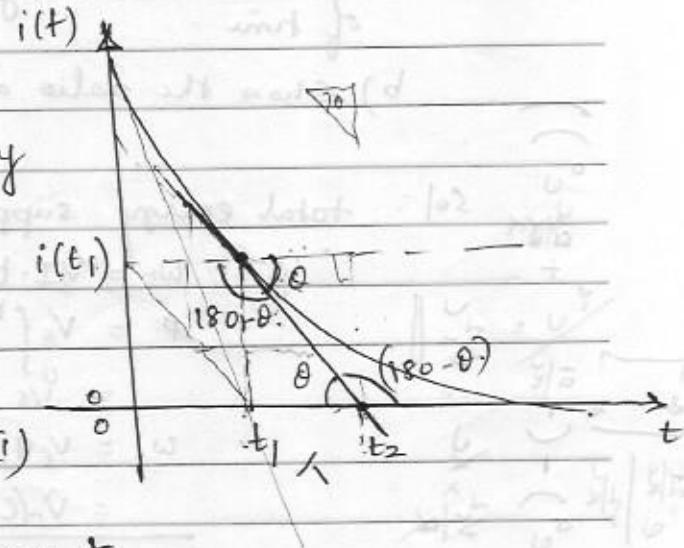t_1 - time at which tangent of curve $i(t)$ is taken.



DATE

- 4.22) A switch is closed at $t=0$, connecting battery of voltage V_s with series RC circuit.

a) Determine the ratio of energy delivered to the capacitor to the total energy supplied by source as a function of time.

b) Show the ratio approaches 0.50 at $t \rightarrow \infty$.

Sol: total energy supplied by source

$$W_s = V_s I \cdot t$$

$$I = V_s \int_0^t I \cdot dt \quad \text{from } (0-t) \text{ ie after } k \text{ is closed}$$

$$= V_s \int_0^t \frac{dq}{dt} dt \quad \text{at } t=0$$

$$W_s = V_s q \quad \therefore q = \int_0^t I \cdot dt \quad i = \frac{dq}{dt}$$

$$= V_s (CV) \quad q = C \cdot v \quad idt = dq$$

$$[W_s = CV_s^2] \quad q = \int_0^t idt$$

Voltage across the Capacitor

$$V_c(t) = V_s (1 - e^{-t/RC})$$

Power absorbed by Capacitor

$$P = V_c(t) \times i_c(t)$$

$$= V_s (1 - e^{-t/RC}) \times C \frac{d}{dt} (V_s (1 - e^{-t/RC}))$$

$$= V_s (1 - e^{-t/RC}) \times C \times \left(\frac{1}{RC}\right) V_s \cdot e^{-t/RC}$$

$$= V_s (1 - e^{-t/RC}) \times \frac{C V_s}{R} \cdot e^{-t/RC}$$

b) Ratio = Energy stored in cap

$$\text{Energy supplied by source} = \left(\frac{V_s^2}{R} - \frac{V_s^2}{R} e^{-t/RC} \right)$$

$$= \frac{1}{2} C V_s^2 = \frac{V_s^2}{R} e^{-t/RC} - \frac{V_s^2}{R} e^{-2t/RC}$$

$$= \frac{1}{2} = 0.5 \quad P = \frac{V_s^2}{R} [e^{-t/RC} - e^{-2t/RC}]$$

Energy stored in capacitor

$$\frac{V_s^2}{2} \left[\frac{e^{-t/RC}}{-\frac{1}{RC}} \Big|_0^\infty \right] = \frac{V_s^2}{2} \left[\frac{e^{-2t/RC}}{-\frac{2}{RC}} \Big|_0^\infty \right] = \frac{V_s^2}{R} \int_0^\infty e^{-t/RC} \cdot dt - \frac{V_s^2}{2} \int_0^\infty e^{-2t/RC} \cdot dt$$


$$E = \frac{V_s^2}{R} \left[\frac{RC}{2} - \frac{RC}{2} \right] = \frac{V_s^2 + RC}{R} \cdot \frac{RC}{2} = \left(\frac{1}{2} C V_s^2 \right) \textcircled{2}$$

DATE

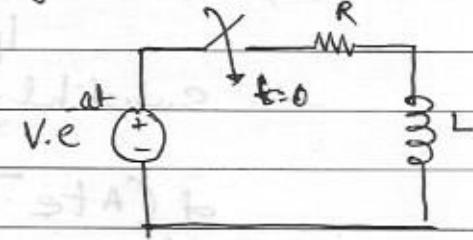(i) A RL circuit with driving force voltage $v(t) = V \cdot e^{-at}$

By KVL

$$\left[L \frac{di}{dt} + Ri = V \cdot e^{-at} \right]$$



$$\left[\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L} \cdot e^{-at} \right] \quad -(1)$$

for this, complete response $i(t) = i_c(t) + i_p(t)$.Case(i) : complementary sol is obtained for zero i/p.

$$\therefore \frac{di}{dt} + (R/L)i = 0 \text{ which has charactr eq of the form } (s + \frac{R}{L})$$

The sol² of such characteristic eq² is given by

$$i_c(t) = K \cdot e^{+st} = -(2)$$

for given differential eq² $s = -R/L$.

$$\therefore [i_c(t) = K \cdot e^{-\frac{R}{L}t}] \quad -(3)$$

Case(ii) : Particular sol²a) If $a \neq R/L$; then particular sol² can't be

$$[i_p(t) = A \cdot e^{-at}] \quad -(4) \quad \because \text{for a LTI system}$$

the particular sol² will be in the same form as that of input.

Substitute (4) in (1) and differentiate

$$\frac{d}{dt} (A \cdot e^{-at}) + \frac{R}{L} (A \cdot e^{-at}) = \frac{V}{L} \cdot e^{-at}$$

$$-AA \cdot e^{-at} + \frac{R}{L} \cdot A \cdot e^{-at} = \frac{V}{L} \cdot e^{-at}$$

$$\begin{cases} i(t) = i_c(t) + i_p(t) \\ = Ke^{-\frac{R}{L}t} + \left(\frac{V}{R-La} \right) \cdot e^{-at} \end{cases}$$

$$-AA + R/L A = \frac{V}{L} \quad \therefore A(R/L - a) = \frac{V}{L}$$

$$A = \frac{V}{R - La} - \frac{V}{(R - La)}$$

$$\therefore [i_p(t) = A \cdot e^{-at} = \frac{V}{(R - La)} \cdot e^{-at}] \quad -(5)$$

Ex. b) If $\alpha = R/L$, then particular sol. be
 $i_p(t) = A \cdot t \cdot e^{-\alpha t}$

Substituting in differential eqⁿ and solving

$$\frac{d(Ate^{-\alpha t})}{dt} + \frac{R}{L}(A \cdot t \cdot e^{-\alpha t}) = \frac{V}{L}e^{-\alpha t}$$

$$A \left[t(-\alpha) \cdot e^{-\alpha t} + e^{-\alpha t} \times 1 \right] + \frac{R}{L} A t e^{-\alpha t} = \frac{V}{L} e^{-\alpha t}$$

$$-a A t e^{-\alpha t} + A \cdot e^{-\alpha t} + \frac{R}{L} A t e^{-\alpha t} = \frac{V}{L} e^{-\alpha t}$$

$$\therefore A(-\alpha t + 1 + \frac{R}{L} t) = \frac{V}{L}$$

$$\text{As } \alpha = \frac{R}{L}$$

$$A \left(-\frac{R}{L}t + 1 + \frac{R}{L}t \right) = \frac{V}{L}$$

$$A = \frac{V}{L}$$

Hence $i_p(t) = A t e^{-\alpha t}$

$$i_p(t) = \left(\frac{V}{L} \right) t \cdot e^{-\alpha t} \quad (7)$$

$$\therefore i(t) = i_c(t) + i_p(t)$$

$$i(t) = k \cdot e^{\frac{-Rt}{L}} + \left(\frac{V}{L} \right) t \cdot e^{-\alpha t} \quad (8)$$

Arbitrary constant k is then determined by the initial condition in each case.

by substituting $i(0^+)$ at $t=0$ is eqⁿ
 (6) & (8).

Ex. In (8)

$$i(t) = k \cdot e^{\frac{-Rt}{L}} + \frac{V}{L} t \cdot e^{-\alpha t}$$

$$i(0^+) = k \cdot e^0 + \frac{V}{L} (0) \cdot e^0$$

$$k = i(0^+) = 0$$

in (6)

$$i(0^+) = k \cdot e^0$$

$$+ \frac{V}{(R-La)} e^0$$

$$0 = k + \left(\frac{V}{R-La} \right)$$


$$(k = -\frac{V}{R-La})$$

DATE _____

* Consider an RC network with the excitation $V \sin(\omega t)$

By KVL
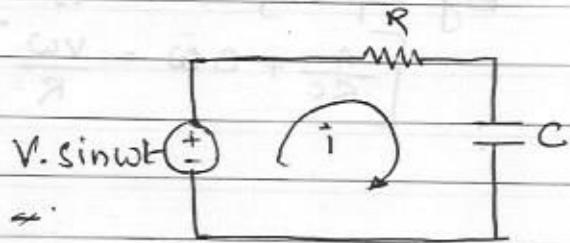
$$Ri + \frac{1}{C} \int_{-\infty}^t i(c) \cdot dc = V \sin \omega t$$



By differentiating and rearranging

$$R \cdot \frac{di}{dt} + \frac{1}{C} i = V \cdot \omega \cdot \cos \omega t$$

$$\left[\frac{di}{dt} + \frac{1}{RC} i = \frac{V \cdot \omega \cdot \cos \omega t}{R} \right] \quad (1)$$

Case (i) : Complementary sol is obtained for zero input cond-

$$\frac{di}{dt} + \frac{1}{RC} i = 0$$

Auxiliary eq

$$\left[si + \frac{1}{RC} i = 0 \right] \text{ which is } (2)$$

The characteristic eq is of the form $s + \frac{1}{RC} = 0$

For the sol for Auxiliary eq of form given in (2)

$$\left[i_c(t) = k \cdot e^{st} \right] \quad (3)$$

$$\therefore i_c(t) = k \cdot e^{-\frac{s}{RC} t} \quad \therefore s = -\frac{1}{RC}$$

Case (ii) : Particular sol for eq (1) will be of the form

$$i_p(t) = A \cos \omega t + B \sin \omega t \quad (4)$$

∴ for any LTI system, the particular sol will be in the same form as that of input

By substituting (4) in (1) and differentiating.

$$\frac{d(A \cos \omega t + B \sin \omega t)}{dt} + \frac{1}{RC} (A \cos \omega t + B \sin \omega t) = \frac{V \omega \cos \omega t}{R}$$

$$\left\{ -\omega A \sin \omega t + \omega B \cos \omega t + \frac{A}{RC} \cos \omega t + \frac{B}{RC} \sin \omega t \right. \\ \left. = \frac{V}{R} \omega \sin \omega t \right.$$

By rearranging

$$\left[\left(B \omega + \frac{A}{RC} \right) \cos \omega t + \left(\frac{B}{RC} - \omega A \right) \sin \omega t = \frac{V}{R} \omega \cos \omega t \right. \\ \left. + 0 \cdot \sin \omega t \right]$$

By equating the coefficient on LHS with RHS.

$$\left[\frac{A}{RC} + B\omega = \frac{V\omega}{R} \right] \quad (5)$$

$$\left[\frac{B}{RC} - A\omega = 0 \right] \quad (6)$$

$$\frac{B}{RC} = A\omega$$

$$\therefore [B = A\omega RC] \quad (7)$$

(7) in (5)

$$\frac{A}{RC} + (A\omega RC) \cdot \omega = \frac{V\omega}{R}$$

$$A \left(\frac{1}{RC} + \omega^2 RC \right) = \frac{V\omega}{R}$$

$$A \left(\frac{1 + \omega^2 R^2 C^2}{RC} \right) = \frac{V\omega}{R}$$

$$\left[A = \frac{V\omega}{R} \times \frac{RC}{(1 + \omega^2 R^2 C^2)} = \frac{V\omega C}{(1 + \omega^2 R^2 C^2)} \right] \quad (8)$$

$$\therefore [B = A\omega RC = \left(\frac{V\omega C \times \omega RC}{1 + \omega^2 R^2 C^2} \right) = \frac{\omega^2 R C^2 V}{1 + \omega^2 R^2 C^2}] \quad (9)$$

Now substituting (8) & (9) in eq 2 (4)

$$i_p(t) = A \cdot \cos \omega t + B \cdot \sin \omega t$$

$$= \frac{V\omega C}{(1 + \omega^2 R^2 C^2)} \cdot \cos \omega t + \frac{\omega^2 R C^2 V}{(1 + \omega^2 R^2 C^2)} \cdot \sin \omega t$$

$$= \frac{V}{(1 + \omega^2 R^2 C^2)} \left[\omega C \cdot \cos \omega t + \omega^2 R C^2 \cdot \sin \omega t \right]$$

$$= \frac{V}{\left(\frac{1}{\omega^2 C^2} + R^2 \right)} \left[\frac{\omega C \cdot \cos \omega t}{\omega^2 C^2} + \frac{\omega^2 R \cdot \sin \omega t}{\omega^2 C^2} \right]$$

$$i_p(t) = \frac{V}{\left(R^2 + \frac{1}{\omega^2 C^2} \right)} \left[\frac{\cos \omega t}{\omega C} + \frac{R \cdot \sin \omega t}{\omega^2 C^2} \right] \quad (10)$$

DATE

In eq² (10) Substitute $\frac{1}{\omega C} = k \cdot \cos \theta$ and $R = k \cdot \sin \theta$

$$i_p(t) = \left(\frac{V}{R^2 + \frac{1}{\omega^2 C^2}} \right) [k \cdot \cos \theta \cdot \cos \omega t + k \sin \theta \cdot \sin \omega t]$$

$$\left[i_p(t) = \left(\frac{KV}{R^2 + \frac{1}{\omega^2 C^2}} \right) [\cos(\omega t - \theta)] \right] \quad \text{--- (11)}$$

Now,

$$\frac{k \cdot \sin \theta}{k \cos \theta} = \frac{R}{\omega C} = R \omega C$$

$$\therefore \tan \theta = R \omega C \quad [\theta = \tan^{-1}(R \omega C)] \quad \text{--- (a)}$$

$$k^2 \sin^2 \theta + k^2 \cos^2 \theta = R^2 + \frac{1}{\omega^2 C^2}$$

$$k^2 = R^2 + \frac{1}{\omega^2 C^2}$$

$$k = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} \quad \text{--- (b)}$$

Substituting k and θ from (a), (b) to eq² (11)

$$i_p(t) = \left[\frac{KV \left(\sqrt{R^2 + \frac{1}{\omega^2 C^2}} \right)}{\left(R^2 + \frac{1}{\omega^2 C^2} \right)} \right] (\cos(\omega t - \tan^{-1}(R \omega C)))$$

$$\boxed{i_p(t) = \frac{V}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t - \tan^{-1}(R \omega C))} \quad \text{--- (12)}$$

$$i(t) = i_c(t) + i_p(t) \quad \text{--- (13)}$$

& k in $i_c(t)$ is found by using initial conditions applied to eq² (12) at $t=0$; $i(0+) = 0$.

$$i(t) = k \cdot e^{-\frac{t}{RC}} + \frac{v}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(\omega t - \tan^{-1} \omega RC)$$

At $t=0$, $i(0^+) = 0$.



$$0 = k \cdot e^0 + \frac{v}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \cos(0 - \tan^{-1} \omega RC)$$

$$k = + \left(\frac{v}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \right) \cos(\tan^{-1} \omega RC)$$

DATE

Step 1 - Draw the equivalent ckt for $t=0^+$, based on equivalent element representations for L, C based on initial cond'n

Element	$i(0^-)$	$i(0^+)$ [Initial]	$i(\infty)$ [final]
---------	----------	--------------------	---------------------

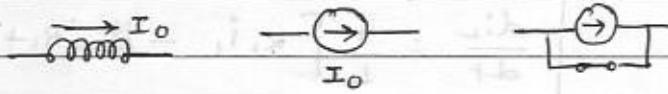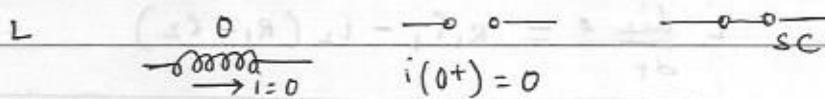

C	$i(0^-)$	$i(0^+)$	$i(\infty)$
---	----------	----------	-------------

\rightarrow (relaxed) \rightarrow S.C. \rightarrow O.C.


Capacitor is charged to C.V.

\rightarrow $\frac{d}{dt} V_0$ \rightarrow $\frac{+}{-}$ \rightarrow $\frac{+}{-}$ V_0 O.C.

2) For each ~~resistor~~ element in the n/w, we must determine just what will happen when switching action ~~is~~ takes place. From this analysis, a new schematic of an equivalent n/w for $t=0^+$ may be constructed according to these rules.

- Replace all inductor with open circuit (∞) with current generator having the value of current flowing at $t=0^+$.
 - Replace all capacitor with s.c. (∞) with voltage $s.C.$ of voltage $V_0 = Q_0/C$ if there is an initial charge.
 - Resistor as it is - Left w/o change
- 3) Using KVL/KCL get the derivatives. Integro-differential eq's are written based on ckt obtained in step 2

Example:

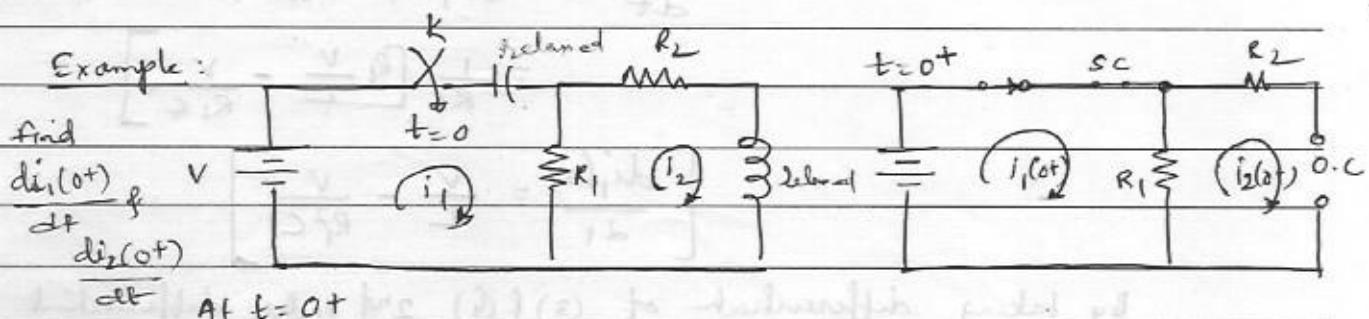

From the equivalent ckt is clear that

$$i_1(0^+) = \frac{V}{R_1} \quad \text{and} \quad i_2(0^+) = 0$$

Apply KVL to both the loops

$$\frac{1}{C} \int_{-\infty}^t i_1(z) dz + R_1(i_1 - i_2) = V \quad \text{--- (1)} \quad \left. \begin{array}{l} \text{these} \\ \text{eq's hold} \end{array} \right\}$$

$$R_1(i_2 - i_1) + R_2 i_2 + L \cdot \frac{di_2}{dt} = 0 \quad \text{--- (2)} \quad \left. \begin{array}{l} \text{good for all } t. \end{array} \right\}$$

Eq (2) can be written as

$$\begin{aligned} \frac{di_2}{dt} &= -R_1(i_2 - i_1) - R_2 i_2 \\ &= -R_1 i_2 + R_1 i_1 - R_2 i_2 \end{aligned}$$

$$L \cdot \frac{di_2}{dt} = R_1 i_1 - i_2 (R_1 + R_2)$$

$$\boxed{\frac{di_2}{dt} = \frac{1}{L} [R_1 i_1 - \frac{1}{2} (R_1 + R_2) i_2]} \quad \text{-(general)} \quad \text{-(3)}$$

At $t=0^+$

$$\frac{di_2}{dt}(0^+) = \frac{1}{L} [R_1 i_1(0^+) - (R_1 + R_2) i_2(0^+)] \quad t=0^+$$

$$\frac{di_2}{dt}(0^+) = \frac{1}{L} [R_1 \times \frac{V}{R_1} - (R_1 + R_2) \cdot 0]$$

$$\boxed{\frac{di_2}{dt}(0^+) = \frac{V}{L}}$$

For (1), take differentiation

$$\boxed{\frac{i_1}{C} + R_1 \frac{di_1}{dt} - R_1 \frac{di_2}{dt} = 0} \quad \text{-(general)} \quad \text{-(4)}$$

At $t=0^+$

$$\frac{i_1(0^+)}{C} + R_1 \frac{di_1}{dt} = R_1 \frac{di_2}{dt} - \frac{i_1(0^+)}{C} \Rightarrow$$

$$\frac{di_1(0^+)}{dt} = \frac{1}{R_1} \left[R_1 \frac{di_2(0^+)}{dt} - \frac{i_1(0^+)}{C} \right]$$

$$\frac{di_1(0^+)}{dt} = \frac{1}{R_1} \left(\frac{V}{L} - \frac{i_1(0^+)}{C} \right)$$

$$= \frac{1}{R_1} \left[R_1 \frac{V}{L} - \frac{V}{R_1 C} \right]$$

$$\boxed{\frac{di_1(0^+)}{dt} = \frac{V}{L} - \frac{V}{R_1 C}}$$

By taking differentiation of (3) & (4) 2nd order differential eq's can be obtained.

* Second order System

Consider

$$a_0 \frac{d^2 i}{dt^2} + a_1 \frac{di}{dt} + a_2 i = 0 \quad \dots (1)$$

$$\text{if } i(t) = k \cdot e^{st}$$

then,

$$a_0 \frac{d^2(k \cdot e^{st})}{dt^2} + a_1 \frac{d(k \cdot e^{st})}{dt} + a_2(k \cdot e^{st}) = 0$$

$$a_0 s^2 k \cdot e^{st} + a_1 s \cdot k \cdot e^{st} + a_2 k \cdot e^{st} = 0$$

$$(a_0 s^2 + a_1 s + a_2) k \cdot e^{st} = 0 \quad \dots (2)$$

On this,

$a_0 s^2 + a_1 s + a_2$, is the characteristic or auxillary polynomial

Endently, the roots are

$$s_1, s_2 = -\frac{a_1}{2a_0} \pm \sqrt{\frac{a_1^2 - 4a_0 a_2}{4a_0}}$$

∴ with roots s_1, s_2 , the characteristic eqⁿ (2) can be written

$$i_1(t) = k_1 e^{s_1 t} \quad \& \quad i_2(t) = k_2 e^{s_2 t}$$

result is

$$(a_0 s_i^2 + a_1 s_i + a_2) k \cdot e^{s_i t} = 0 \quad \dots (3)$$

and hence are solⁿ of the second order differential eq^s.

i_1 & i_2 are solutions, then so is any linear combination $\alpha i_1 + \beta i_2$ for all $\alpha, \beta \in \mathbb{R}$

∴ The general solⁿ

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} \quad \dots (4)$$

the roots s_1, s_2 may be


(i) Real and different

(ii) Real and equal or

(iii) Complex conjugate pair.

Let us consider a series RLC nw

By applying KVL

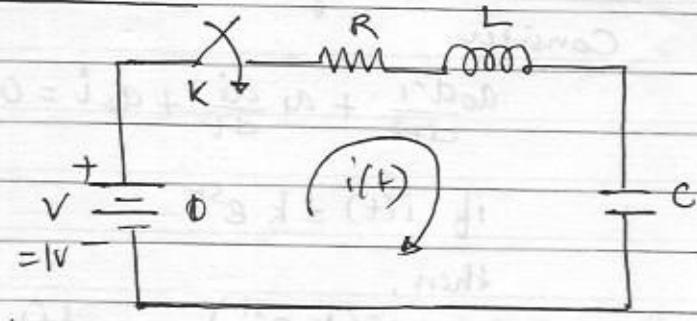

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = V \quad \text{--- (1)}$$

Differentiating

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0 \quad \text{--- (2)}$$

Thus auxillary equation is

$$(Ls^2 + Rs + \frac{1}{C}) k e^{st} = 0$$

where $Ls^2 + Rs + \frac{1}{C}$ is auxillary eqe

\therefore By L to characteristic (auxillary eq²)

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Clearly

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4\frac{1}{LC}}$$

$$\therefore i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$= -\frac{R}{2L} \pm \sqrt{\frac{1}{4}\left(\frac{R}{L}\right)^2 - \frac{4}{4}\left(\frac{1}{LC}\right)}$$

$$\text{Xplgn by 2} = -\frac{R}{2L} \times 2 \pm \sqrt{\frac{4}{4}\left(\frac{R}{L}\right)^2 - 4\left(\frac{1}{LC}\right)}$$

$$\boxed{s_1, s_2 = -\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4\frac{1}{LC}}} \quad \text{--- (3)}$$

Example : if $R = 3\Omega$, $L = 1H$ and $C = \frac{1}{2}F$ in the ckt

$$1s^2 + 3s + \frac{1}{\left(\frac{1}{2}\right)} = 0 \quad s^2 + 3s + 2 = 0.$$

Roots are

$$s^2 + 3s + 2 = (s+1)(s+2) = 0$$


$$\therefore s_1 = -1, s_2 = -2$$

DATE

* Series RLC Circuit driven by D.C Excitation

$$t=0^-;$$

$$i(0^-) = 0 = i(0^+)$$

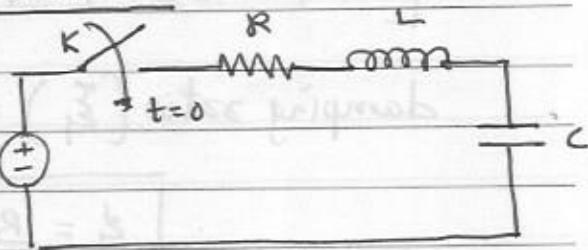

$t \rightarrow 0$; R is closed at $t=0$

$\therefore i(0^+) = i(0^-)$ as current through inductor cannot change instantaneously

By KVL,

$$L \cdot \frac{di}{dt} + Ri + \frac{1}{C} \int_{-\infty}^t i \cdot d\tau = V \quad (1)$$

$$L \cdot \frac{di}{dt} + Ri + \frac{1}{C} \int_0^0 i \cdot d\tau + \frac{1}{C} \int_0^t i \cdot d\tau = 0$$

By differentiating

$$\left[L \frac{d^2i}{dt^2} + R \cdot \frac{di}{dt} + \frac{1}{C} i = 0 \right] \quad (2) \quad \begin{matrix} \text{Homogeneous} \\ \text{2nd order diff} \end{matrix}$$

The characteristic eq: can be written as

$$L \cdot s^2 i + \left(\frac{R}{L} s + \frac{1}{LC} \right) i = 0$$

$$\left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) i = 0 \quad \text{where } i = k \cdot e^{st} \quad \begin{matrix} \text{as it is general} \\ \text{sol: for homogeneous diff} \\ \text{eqn} \end{matrix}$$

The roots of $\left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0$ are

$$s_1, s_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-\left(\frac{R}{L}\right) \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4 \times \frac{1}{LC}}}{2}$$

$$s_1, s_2 = \left[-\left(\frac{R}{2L}\right) \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2} \right] \quad (3)$$

where $\alpha = \text{damping factor} = \frac{R}{2L}$

$$\omega_n = \text{Natural freq} = \frac{1}{\sqrt{LC}}$$

$$\therefore s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_n^2} \quad (4)$$

$$\text{when char. eqn} \left(s^2 + \frac{2(R)}{2L} s + \left(\frac{1}{\sqrt{LC}}\right)^2 \right) i = 0$$

$$[s^2 + 2\alpha s + \omega_s^2 = 0] - (4)$$

damping ratio (ξ) = $\frac{\alpha}{\omega_s} = \frac{R/2L}{1/\sqrt{LC}} = \frac{R}{2L} \times \sqrt{L/C} = \frac{R}{2\sqrt{LC}}$

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

Eq² (4) can be written as.

$$[s^2 + 2\xi\omega_s s + \omega_s^2 = 0] - (5)$$

and

and s_1, s_2 can be written as

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_s^2}$$

$$= -(\xi\omega_s) \pm \sqrt{(\xi\omega_s)^2 - \omega_s^2}$$

$$s_1, s_2 = -\xi\omega_s \pm \omega_s \sqrt{\xi^2 - 1} \quad - (6)$$

The roots s_1, s_2

- i) Real, Negative and Unequal.
- ii) Real, Negative and Equal
- iii) Complex conjugate with negative real part.
- iv) Imaginary conjugate.

$\alpha > \omega_s$, $\xi > 1$
$\alpha = \omega_s$, $\xi = 1$
$\alpha < \omega_s$, $0 < \xi < 1$
$\alpha = 0$, $\xi = 0$.

(i) s_1, s_2 are real, Negative and Unequal.

∴ General sol² of i(t) w.r.t s_1, s_2 is

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} \quad - (7)$$

where k_1 & k_2 are found based on initial conditions.



DATE


(Case i) : $s_1, s_2 \rightarrow$ Real, Negative and Unequal.

These roots are obtained when

$$\alpha > \omega_s \text{ ie } \frac{R}{2L} > \frac{1}{\sqrt{LC}} \therefore \frac{\alpha}{\omega_s} > 1$$

$$\therefore i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} \quad R > \frac{2L}{\sqrt{LC}}$$
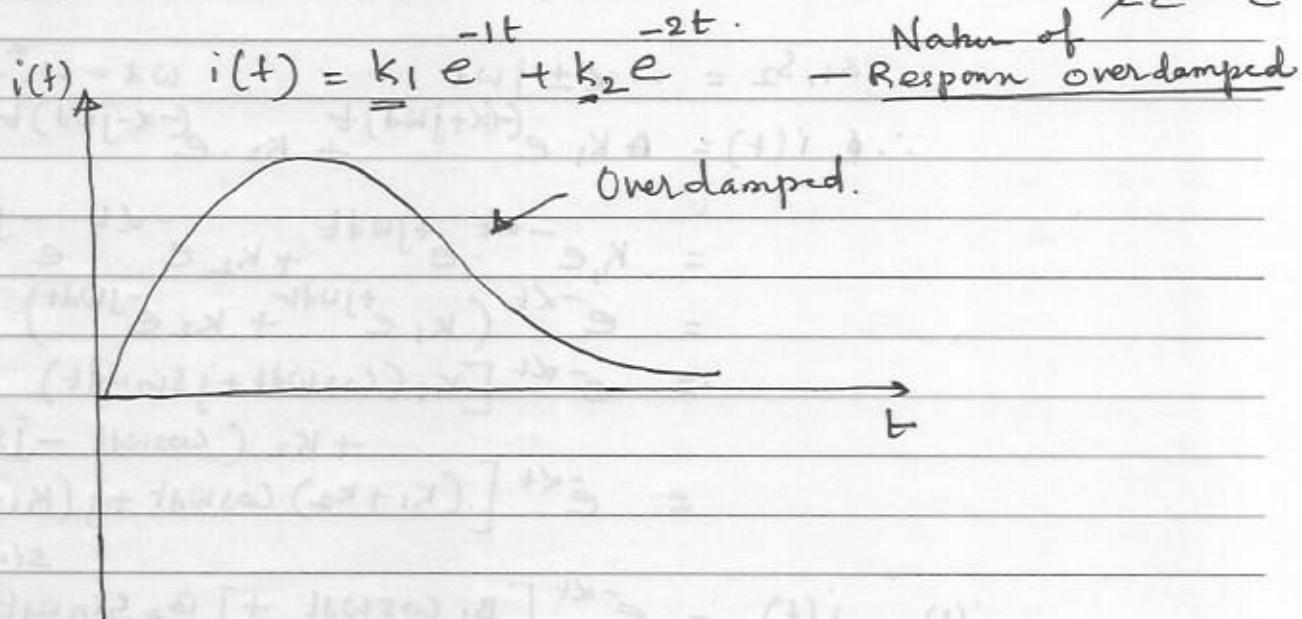
$$\underline{\text{Ex:}} \quad s_1 = -1 \quad \& \quad s_2 = -2, \text{ then} \quad R^2 > \frac{4L^2}{\omega_s^2} > \frac{4L}{C}$$



(Case ii) : s_1, s_2 are real, negative and equal

These roots ~~can~~ are obtained when

$$\alpha = \omega_s ; \quad \frac{R}{2L} = \frac{1}{\sqrt{LC}} \quad \frac{\alpha}{\omega_s} = \frac{R}{\omega_s} = 1.$$

$$\left[R = \frac{2L}{\sqrt{LC}} = 2\sqrt{\frac{L}{C}} = R_{cr.} \right]$$

Now,

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_s^2} \\ = -\alpha \pm \sqrt{\omega_s^2 - \omega_s^2} \quad \alpha = \omega_s.$$

$$s_1, s_2 = -\alpha$$

$$\therefore i(t) = k_1 e^{-\alpha t} + k_2 e^{-\alpha t}$$

$$\boxed{i(t) = e^{-\alpha t} (k_1 + k_2)}$$

Case (iii) : Roots (s_1, s_2) are complex conjugate

- When $\alpha < \omega_s$,

$$\frac{R}{2L} < \frac{1}{\sqrt{LC}}$$

$$R < \frac{2L}{\sqrt{LC}}$$

$$R < 2\sqrt{\frac{L}{C}} = R_{cr}$$

$$\rightarrow s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_s^2}$$

$$= -\alpha \pm \sqrt{-(\omega_s^2 - \alpha^2)}$$

$$= -\alpha \pm j\sqrt{\omega_s^2 - \alpha^2}$$

$$s_1, s_2 = -\alpha \pm j\omega_d \quad \omega_d = \omega_s - \alpha$$

$$\therefore i(t) = K_1 e^{(-\alpha + j\omega_d)t} + K_2 e^{(-\alpha - j\omega_d)t}$$

$$= K_1 e^{-\alpha t} \cdot e^{j\omega_d t} + K_2 e^{-\alpha t} \cdot e^{-j\omega_d t}$$

$$= e^{-\alpha t} (K_1 e^{j\omega_d t} + K_2 e^{-j\omega_d t})$$


$$= e^{-\alpha t} [K_1 (\cos \omega_d t + j \sin \omega_d t)]$$

$$+ K_2 (\cos \omega_d t - j \sin \omega_d t)]$$

$$= e^{-\alpha t} [(K_1 + K_2) \cos \omega_d t + j(K_1 - K_2) \sin \omega_d t]$$

$$i(t) = e^{-\alpha t} [B_1 \cos \omega_d t + j B_2 \sin \omega_d t]$$
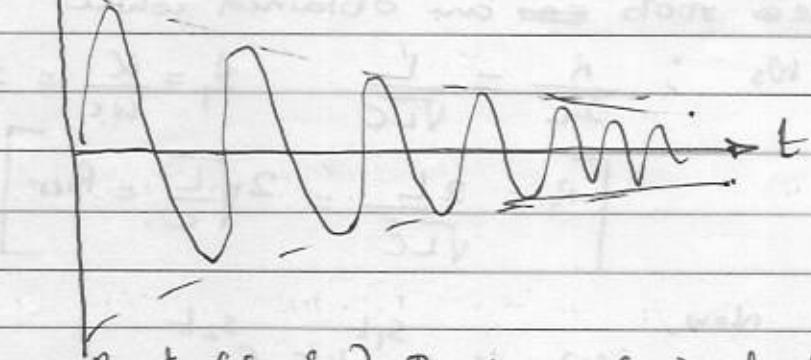
$$\text{where } \omega_d = \omega_s - \alpha.$$



Case (iv): Roots (s_1, s_2) Imaginary Conjugate ($\pm j\omega_s$)

When $\alpha = 0$

$$s_1, s_2 = -0 \pm \sqrt{0^2 - \omega_s^2}$$

$$= \pm j\sqrt{\omega_s^2} = \pm j\omega_s.$$


$$\therefore i(t) = K_1 e^{+j\omega_s t} + K_2 e^{-j\omega_s t}$$

$$= K_1 (\cos \omega_s t + j \sin \omega_s t)$$

$$+ K_2 (\cos \omega_s t - j \sin \omega_s t)$$

$$i(t) = (K_1 + K_2) \cos \omega_s t + j(K_1 - K_2) \sin \omega_s t$$
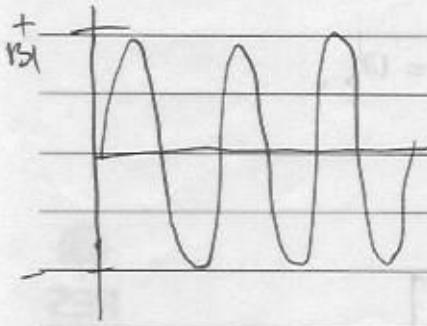
$$= B_1 \cos \omega_s t + j B_2 \sin \omega_s t.$$



DATE

Transient Response of Series RLC with DC ExcitationAt $t=0^-$

$$i(0^-) = 0$$

At $t=0^+$

$$i(0^+) = i(0^-) = 0, V_C(0^+) = 0$$

By KVL,

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int_{-\infty}^t i \cdot dt = V \quad \boxed{1}$$

$$\frac{di(0^+)}{dt} = V - Ri - \frac{1}{C} \int_{-\infty}^0 i \cdot dt \quad \boxed{2}$$

$$\frac{di(0^+)}{dt} = \frac{V}{L} \quad \boxed{3}$$

Differentiating

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad \boxed{4}$$

If eq² is a Homogeneous 2nd order differential eq² where
 $i(t) = k \cdot e^{st}$ form.

Auxiliary eq² / characteristic eq² can be written as

$$s^2 i + \left(\frac{R}{L}\right) s i + \frac{1}{LC} i = 0$$

$$(s^2 + \left(\frac{R}{L}\right)s + \left(\frac{1}{LC}\right))i = 0 \quad (s^2 + \frac{R}{L}s + \frac{1}{LC})k e^{st} = 0$$

Now roots of $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$ given by $\boxed{5}$

$$s_1, s_2 = -\frac{b}{2a} \pm \sqrt{\frac{b^2 - 4ac}{4a^2}} = -\left(\frac{R}{2L}\right) \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)^2} \quad \boxed{6}$$

Damping

Ratio

where $\frac{1}{\sqrt{LC}} = \omega_s$ = Natural Frequency

$$\xi_s = \frac{\alpha}{\omega_s} = \frac{R \times \sqrt{LC}}{1/\sqrt{LC}} = \frac{R \sqrt{L}}{2\sqrt{C}} \quad \frac{R}{2L} = \alpha = \text{Damping factor.} \quad \boxed{7}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_s^2} \quad \boxed{8}$$

$$s^2 + 2\left(\frac{R}{2L}\right)s + \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)^2} = 0$$

$$\left[s^2 + 2\alpha s + \omega_s^2 = 0 \right] \quad \boxed{9}$$

$$\alpha = \xi_s \omega_s \text{ then } \left[s^2 + 2\xi_s \omega_s s + \omega_s^2 = 0 \right] \quad \boxed{10}$$

then

$$s_1, s_2 = -\xi_s \omega_s \pm \sqrt{(\xi_s \omega_s)^2 - \omega_s^2}$$

$$\left[s_1, s_2 = -\xi_s \omega_s \pm \omega_s \sqrt{(\xi_s)^2 - 1} \right] \quad \boxed{11}$$

Roots s_1, s_2 may be will lead to two components of i w.r.t s_1 and s_2

$$\therefore [i(t) = i_1(t) + i_2(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}] \quad (1)$$

while s_1, s_2 may

a) Real, Negative and Unequal

b) Real, Negative and Equal

$$-\alpha \pm \sqrt{\alpha^2 - \omega_s^2}$$

c) Complex conjugate with Negative α .

d) Complex Conjugate with $\alpha=0$; ie Imaginary Conjugate

Damping Ratio	Nature of Roots	$i(t)$	Nature of Response
$\alpha = \omega_s$	$\xi = 1$ Real, Negative <u>Equal</u>	$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$	- Critically damped
$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$	$\omega - \alpha \pm \sqrt{\omega_s^2 - \omega^2}$ $\therefore s_1, s_2 = -\alpha$	$i(t) = k_1 e^{-\alpha t} + k_2 e^{-\alpha t}$ $= \bar{e}^{-\alpha t} (k_1 + k_2)$	
$\alpha > \omega_s$ $\frac{R}{2L} > \frac{1}{\sqrt{LC}}$	Real, Negative <u>Not equal</u> s_1, s_2 where $s_1 \neq s_2$ Ex: $s_1 = -1$ & $s_2 = -2$	$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$ $i(t) = k_1 e^{-s_1 t} + k_2 e^{-s_2 t}$ $\therefore i(t) = k_1 e^{-1t} + k_2 e^{-2t}$	Overdamped

$\alpha < \omega_s$ $\frac{R}{2L} < \frac{1}{\sqrt{LC}}$	$\xi < 1$ $s_1, s_2 = -\alpha \pm j\omega_d$ $\omega_d = \sqrt{\omega_s^2 - \alpha^2}$ Complex conjugate	$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$ $= k_1 e^{(\alpha+j\omega_d)t} + k_2 e^{(\alpha-j\omega_d)t}$ $= k_1 e^{-\alpha t} \cdot e^{j\omega_d t} + k_2 e^{-\alpha t} \cdot e^{-j\omega_d t}$ $= e^{-\alpha t} (k_1 e^{j\omega_d t} + k_2 e^{-j\omega_d t})$ $= e^{-\alpha t} (k_1 (\cos \omega_d t + j \sin \omega_d t) + k_2 (\cos \omega_d t - j \sin \omega_d t))$ $i(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$	Underdamped
---	---	--	-------------


$\alpha = 0$	$\xi = 0$ $s_1, s_2 = \pm j\omega_s$ $= \pm j\sqrt{\omega_s^2}$ $= \pm j\omega_s$	$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$ $= k_1 e^{j\omega_s t} + k_2 e^{-j\omega_s t}$ $= k_1 (\cos \omega_s t + j \sin \omega_s t) + k_2 (\cos \omega_s t - j \sin \omega_s t)$ $= (k_1 + k_2) \cos \omega_s t + j(k_1 - k_2) \sin \omega_s t$	Both the terms Oscillating
--------------	--	---	----------------------------

DATE

$$\boxed{\text{Ex (1)}}: i(0^-) = 0$$

$$\text{At } t=0^+; i(0^+) = i(0^-)$$
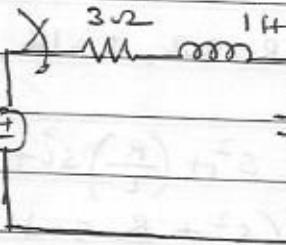
$$\frac{di}{dt}(0^+) = \frac{V}{L} = \frac{1}{1} = 1 \text{ Amp/s}$$



$$V = 1V$$

$$RVL \left(\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \right) - (1)$$

$$s^2 i + \left(\frac{R}{L} \right) s i + \frac{1}{LC} i = 0 \quad \left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) i = 0.$$

Chara eqz will be

$$\left[s^2 + \left(\frac{3}{1} \right) s + \left(\frac{1}{1 \times \frac{1}{2}} \right) \right] i = 0. \quad \alpha = \frac{R}{2L} = \frac{3}{2 \times 1} = 1.5$$

$$(s^2 + 3s + 2) k \cdot e^{st} = 0. \quad \omega_s = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 0.5}} = \sqrt{2}$$

Roots of $s^2 + 3s + 2$

$$\omega_s = 1.414$$

$$\therefore [i(t) = k_1 e^{-t} + k_2 e^{-2t}] - (2) \quad \alpha > \omega_s. \quad \therefore \text{Overdamped}$$

Using initial cond² k_1 & k_2 can be determined.

$$i(0^+) = k_1 e^{1(0)} + k_2 e^{-2(0)}$$

$$\frac{di(0^+)}{dt} = k_1(-1)e^{-t} + k_2(-2)e^{-2t}$$

$$i(0^+) = k_1 + k_2$$

$$= -k_1 e^{-t} - 2k_2 e^{-2t}$$

$$\therefore [k_1 + k_2 = 0] \quad \therefore i(0^+) = 0.$$

$$= -k_1 e^0 - 2k_2 e^0.$$

L @

$$\frac{di(0^+)}{dt} = -k_1 - 2k_2$$

$$\therefore V = -k_1 - 2k_2$$

$$[-k_1 - 2k_2 = 1] - (b)$$

Solving @ and (b)


$$k_1 = 1 \text{ and } k_2 = -1$$

$$\therefore i(t) = k_1 e^{-t} + k_2 e^{-2t}$$

$$= 1 e^{-t} - 1 e^{-2t}$$

$$\boxed{i(t) = e^{-t} - e^{-2t}}$$

\therefore no response is Overdamping

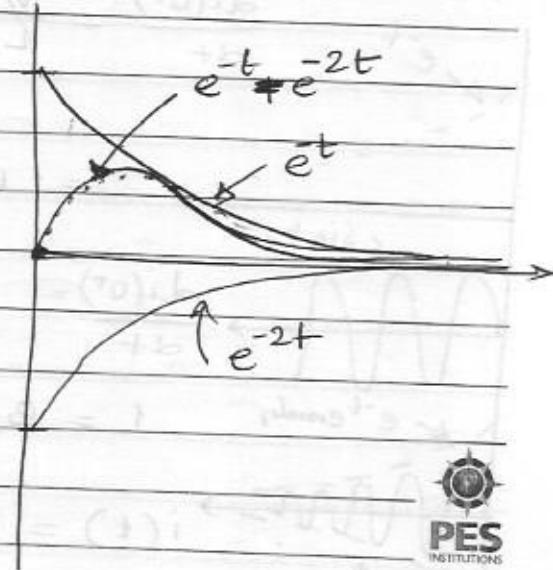

Ex(2) : $R = 2\Omega$, $L = 1H$, $C = \frac{1}{2}F$, $V = 1V$

$$s^2 + \left(\frac{R}{L}\right)s + \frac{1}{LC} i = 0.$$

$$\left(s^2 + \frac{R}{L}s + \frac{1}{LC}\right)ke^{st} = 0$$

$$s^2 + 2s + 2 = 0$$

Roots will be $s_1 = -1+j$ & $s_2 = -1-j$

st indicated that nature is Undamped resp. - Undamped

$$i(t) = e^{st} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

$$= e^{-t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

$$\omega_d = \sqrt{\omega_s^2 - \alpha^2}$$

$$= \sqrt{(1.4142)^2 - (1)^2}$$

$$= 0.9999 = 1$$

$$i(t) = \cancel{K_1 e^{(-1+j)t}} + \cancel{K_2 e^{(-1-j)t}}$$

$$= K_1 (e^{-t} \cdot e^{jt}) + K_2 (e^{-t} \cdot e^{-jt})$$

$$= e^{-t} [K_1 e^{jt} + K_2 e^{-jt}]$$

$$= e^{-t} [K_1 (\cos$$

$$i(t) = e^{-t} (B_1 \cos(1)t + B_2 \sin(1)t)$$

$$i(t) = e^{-t} (B_1 \cos t + jB_2 \sin t)$$

$$t=0^+$$

$$i(0^+) = e^0 (B_1 \cos(0) + jB_2 \sin(0))$$


$$i(0^+) = 0 \cdot B_1 + 0 \quad \therefore B_1 = 0$$

$$\frac{di(0^+)}{dt} = \cancel{\frac{V}{L}} / \cancel{1} = B_2 [e^{-t} \cdot (-\sin t) + \cos t \cdot (-1) \cdot e^{-t}]$$

$$B_2 [e^{-t} \cos t + j \sin t \cdot (-1) \cdot e^{-t}]$$


$$= B_2 [e^0 (0) + -j0 \cdot e^0]$$

$$+ B_2 [1 + 0]$$

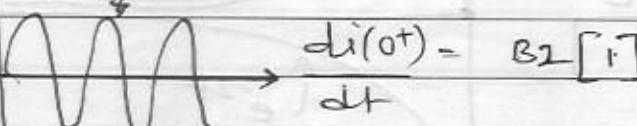

$$\frac{di(0^+)}{dt} = B_2 [1]$$

$$1 = B_2 \quad \therefore B_2 = 1$$

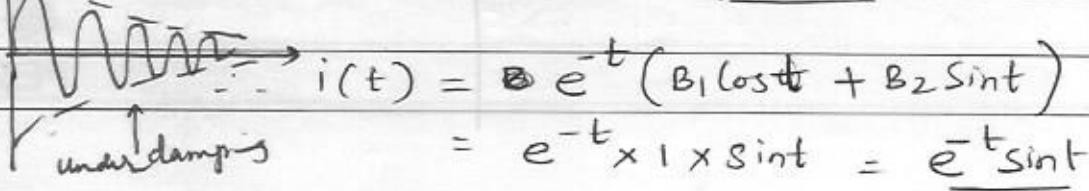

$$i(t) = e^{-t} (B_1 \cos t + B_2 \sin t)$$

$$= e^{-t} \times 1 \times \sin t = e^{-t} \underline{\sin t}$$

DATE Ex (3) ✓

* Parallel R-L-C

At $t=0^-$, switch K

is closed.

$$[V(0^-) = 0] @, I_L(0^-) = 0$$

At $t=0^+$, K is open

By KCL

$$[V_C(0^+) = V_C(0) = 0.] - (a)$$

$$C \cdot \frac{dv}{dt} + \frac{V}{R} + \frac{1}{L} \int_{-\infty}^t V \cdot dz = I \quad -(1)$$

$$C \frac{dv(0^+)}{dt} + \frac{V(0^+)}{R} + \frac{1}{L} \int_{-\infty}^{0^+} V(0^+) \cdot dz = I$$

$I_L(0^-) = 0$

$$C \cdot \frac{dv(0^+)}{dt} = I.$$

$$\boxed{\frac{dv(0^+)}{dt} = \frac{I}{C} = \frac{1}{2} = 0.5} \quad -(b)$$

(a) and (b) are initial conditions.

Differentially eq = (1)

$$C \frac{d^2V}{dt^2} + \frac{1}{R} \cdot \frac{dv}{dt} + \frac{1}{L} V = I.$$

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \cdot \frac{dv}{dt} + \frac{1}{LC} V = I$$

$$\left(s^2 + \frac{1}{RC} s + \frac{1}{LC} \right) V = I \quad \text{when } V = K \cdot e^{st}.$$

for homogeneous differential eq

Roots :

$$s_1, s_2 = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{1}{LC}}}{2 \times 1}$$

$$s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$$

$$\alpha = \frac{1}{2RC} \quad \& \quad \omega_s = \frac{1}{\sqrt{LC}}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_s^2}$$



According gives R, L, C values

$$s^2 + \frac{1}{\frac{1}{8} \times 2} s + \frac{1}{\frac{1}{8} \times 2} = 0$$

$$s^2 + 4s + 4 = 0$$

$$\therefore s_1, s_2 = -2 \quad -\text{Real and equal roots.}$$

W.K.T

General solⁿ of 2nd order differential eqn will have two elements.

$$y(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$v(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$\text{As root } s_1, s_2 = s = -2$$

$$v(0^+) = k \cdot e^0$$

$$v(0^+) = k$$

$$\therefore k = 0$$

$$\therefore \frac{dv(0^+)}{dt} = -2k \cdot e^{-2t}$$

$$\therefore v(0^+) = 0$$

$$k = 2$$

$$\frac{dv(0^+)}{dt} = k e^{-2t}$$

$$= -2k \cdot e^{-2t}$$

$= -2 \times 2 \cdot e^{-2t}$ So, for repeated roots, the general solⁿ will be of the

$\boxed{1 \neq -4}$ form

$$[y(t) = k_1 e^{s_1 t} + k_2 \cdot t \cdot e^{s_1 t}]$$

$$\text{Now, } [v(t) = k_1 e^{-2t} + k_2 t e^{-2t}] - (3)$$

Using initial condⁿ. $t = 0^+$

$$v(0^+) = k_1 e^{-2t} + k_2 t e^{-2t}$$

$$= k_1 e^0 + k_2 \cdot 0 \cdot e^0$$

$$v(0^+) = k_1$$

$$\therefore \boxed{k_1 = 0} \text{ as } v(0^+) = 0$$

$$\frac{dv}{dt} = k_1 (-2) \cdot e^{-2t}$$

$$+ k_2 [t \cdot (-2) e^{-2t} + e^{-2t} (1)]$$

$$\frac{dv(0^+)}{dt} = 0 \times (-2) e^0$$

$$+ k_2 [0 \times (-2) e^{-2t} + e^0]$$

$$\frac{dv(0^+)}{dt} = k_2$$

$$\therefore k_2 = \underline{\underline{0.5}}$$

$$\frac{d^2 v}{dt^2} = 0 \quad \boxed{*}$$

1st integral


$$\frac{dv}{dt} = k_2$$

2nd integral

$$v(t) = k_1 + k_2 t$$

Using $k_1 + k_2$

$$v(t) = 0.5 t e^{-2t}$$

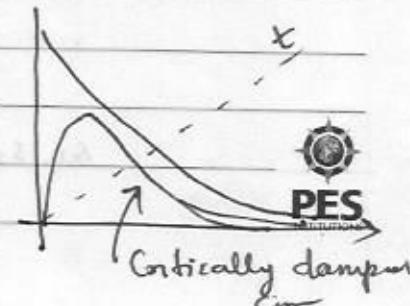


DATE _____

Example (1) : In the ckt shown, $V = 10V$, $R = 10\Omega$, $L = 1H$, $C = 100\mu F$ and $v_C(0) = 0$. Let's find $i(0^+)$, $\frac{di}{dt}(0^+)$, and $\frac{d^2i(0^+)}{dt^2}$

At $t = 0$; switch is closed

By KVL
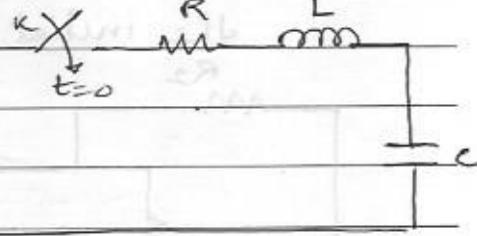
$$\left[L \cdot \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = V \right] \quad (1)$$



(i) At $t = 0^+$, L is o.c & C is sc.

$$\therefore i(0^+) = \frac{V}{R}$$



(ii) From eq² (1), By rearranging

we get

$$L \cdot \frac{di}{dt} = V - Ri - \frac{1}{C} \int i dt$$

L acts as o.c as ~~it's a current source~~

$$\frac{di}{dt} = \frac{V}{L} - \frac{R}{L} i - \frac{1}{RC} \int i dt$$

$$v_C(0^+) = 0$$

At $t = 0^+$

$$\frac{di(0^+)}{dt} = \frac{V}{L} - \frac{R}{L} i(0^+) - \frac{1}{RC} \int_{0^+}^{0^+} i(0^+) dt$$

$$\left[\frac{di(0^+)}{dt} = \frac{V}{L} \right] \quad (2) \quad \therefore \frac{di(0^+)}{dt} = \frac{10}{1} = 10 \text{ Amp/sec}$$

(iii) By taking derivative on both sides of eq² (1)

$$L \cdot \frac{d^2i}{dt^2} + R \cdot \frac{di}{dt} + \frac{i}{C} = 0$$

$$\text{At } t = 0^+ \quad \frac{d^2i(0^+)}{dt^2} = - \frac{R}{L} \cdot \frac{di(0^+)}{dt} - \frac{i(0^+)}{C}$$


$$= - \frac{R}{L} \times \frac{V}{L} - \frac{0}{C}$$

$$\frac{d^2i(0^+)}{dt^2} = - \frac{10}{1} \times 10 = -100 \text{ Amp/sec}^2$$

$$\therefore i(0^+) = 0 \quad \frac{di(0^+)}{dt} = \frac{V}{L} = 10 \text{ Amp/sec} \quad \frac{d^2i(0^+)}{dt^2} = - \frac{R}{L} \cdot \frac{di(0^+)}{dt} - \frac{i(0^+)}{C}$$

$$= - \frac{10 \times 10}{1} = -100 \text{ Amp/sec}^2$$

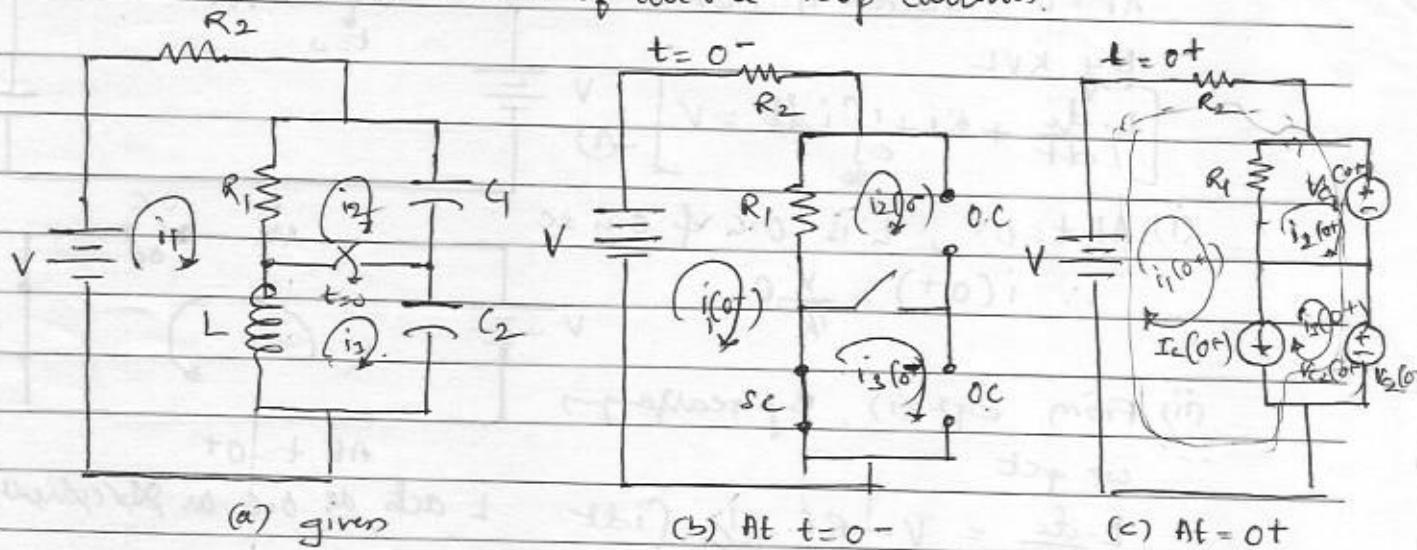Example (2): In the net shown, steady state is reached with the switch K open and at $t=0$, the switch is closed. Find the initial values of all the loop currents.



(i) At $t=0^-$

$$i_1(0^-) = \left(\frac{V}{R_1 + R_2} \right) = i_{R_1}(0^-) = i_L(0^-) \quad \& \quad i_2(0^-) = 0, i_3(0^-) = 0$$

$$V_{C_1}(0^-) + V_{C_2}(0^-) = \left(\frac{R_1}{R_1 + R_2} \right) V \quad - (1)$$

$$\frac{R_1}{R_1 + R_2} V$$

Charges on the capacitors will be same as they are in series.

$$q_1(0^-) = q_2(0^-)$$

$$C_1 V_{C_1}(0^-) = C_2 V_{C_2}(0^-)$$

$$\frac{V_{C_1}(0^-)}{V_{C_2}(0^-)} = \frac{C_2}{C_1} \quad - (2)$$

(2) / $i_2(0^-) \div$ eq(1) both side by $V_{C_2}(0^-)$

$$\frac{V_{C_1}(0^-)}{V_{C_2}(0^-)} + 1 = \left(\frac{R_1}{R_1 + R_2} \right) V \quad - (3)$$

Substitute (2) in (3)

$$\frac{C_2}{C_1} + 1 = \frac{(R_1/R_1 + R_2)V}{V_{C_2}(0^-)}$$

$$\frac{V_{C_2}(0^-)}{\left(\frac{C_2 + C_1}{C_1} \right)} = \left(\frac{R_1}{R_1 + R_2} \right) V = \left[\left(\frac{C_1}{C_1 + C_2} \right) \left(\frac{R_1}{R_1 + R_2} \right) V \right]$$

Now

$$V_{C_1}(0^-) = \left(\frac{C_2}{C_1 + C_2} \right) \cdot \left(\frac{R_1}{R_1 + R_2} \right) V$$

DATE

At $t=0^+$

KVL @ outer Loop (peripheral)

$$V = i_1(0^+) R_2 + V_{C_1}(0^+) + V_{C_2}(0^+) = V.$$

$$\left(\frac{V}{R_1+R_2} \right) R_2 + \left(\frac{C_2}{C_1+C_2} \right) \left(\frac{R_1}{R_1+R_2} \right) V + \left(\frac{C_1}{C_1+C_2} \right) \left(\frac{R_1}{R_1+R_2} \right) V = V$$

$$i_1(0^+) R_2 - V \left(\frac{R_1}{R_1+R_2} \right) + \frac{R_1}{R_1+R_2} V \left(\frac{C_2}{C_1+C_2} + \frac{C_1}{C_1+C_2} \right) = V$$

$$i_1(0^+) R_2 = V - V_{C_1}(0^+) - V_{C_2}(0^+)$$

$$= V - \left[\left(\frac{C_2}{C_1+C_2} \right) \left(\frac{R_1}{R_1+R_2} \right) V \right] - \left[\left(\frac{C_1}{C_1+C_2} \right) \left(\frac{R_1}{R_1+R_2} \right) V \right]$$

$$= V \left[1 - \frac{C_2 R_1 + C_1 R_1}{(C_1+C_2)(R_1+R_2)} \right]$$

$$= V \left[1 - \frac{R_1(C_1+C_2)}{(C_1+C_2)(R_1+R_2)} \right]$$

$$= V \left[1 - \frac{R_1}{R_1+R_2} \right]$$

$$i_1(0^+) R_2 = V \left[\frac{R_1+R_2 - R_1}{R_1+R_2} \right]$$

$$i_1(0^+) = \frac{V}{R_2} \left(\frac{R_2}{R_1+R_2} \right) = \frac{V}{R_1+R_2} = i(0^-) = I_L(0^+)$$

Loop 3:

$$(i_3(0^+) - i_1(0^+))$$

Current through inductor is $(i_1(0^+) - i_3(0^+)) = I_L(0^+)$

As we known current through inductor can't change -

$$\text{instantaneously } i_1(0^+) - i_3(0^+) = \frac{V}{R_1+R_2} \quad : \quad i_1(0^+) = i_1(0^-)$$

$$= \frac{V}{R_1+R_2}$$

Hence $i_3(0^+) = 0$.

Loop 2: KVL @ loop 2.

$$(i_2(0^+) - i_1(0^+)) R_1 + V_{C_1}(0^+) = 0$$

Voltage a/c induct capacitor can't change instantaneously

$$i_2(0^+) R_1 - i_1(0^+) R_1 = -V_{C_1}(0^+)$$

$$= - \left[\left(\frac{C_2}{C_1+C_2} \right) \left(\frac{R_1}{R_1+R_2} \right) V \right]$$

$$i_2(0^+) R_1 = i_1(0^+) R_1 - \left(\frac{C_2}{C_1+C_2} \right) \left(\frac{R_1}{R_1+R_2} \right) V$$

$$i_2(0+) R_f = \left(\frac{V}{R_f + R_L} \right) R_f - \left(\frac{C_2}{C_1 + C_2} \right) \left(\frac{R_f}{R_f + R_L} \right) V$$

$$= \frac{V R_f}{R_f + R_L} \left[1 - \frac{C_2}{C_1 + C_2} \right]$$

$$i_2(0+) R_f = \frac{V R_f}{R_f + R_L} \left[\frac{C_1 + C_2 - R_f}{C_1 + C_2} \right]$$



$$\boxed{i_2(0+) = \left(\frac{V}{R_f + R_L} \right) \left(\frac{C_1}{C_1 + C_2} \right)} \quad \checkmark$$

DATE

- 5.25) Switch k is opened at $t=0$ after the network has attained a steady state with switch closed.

a) find an expression for the voltage acr switch K at $t=0^+$

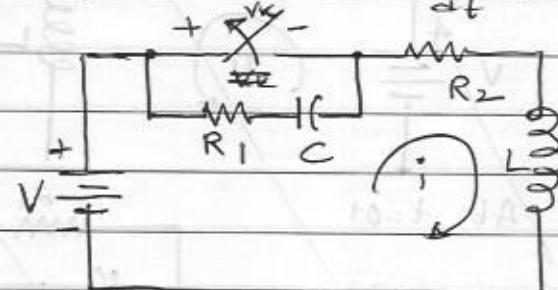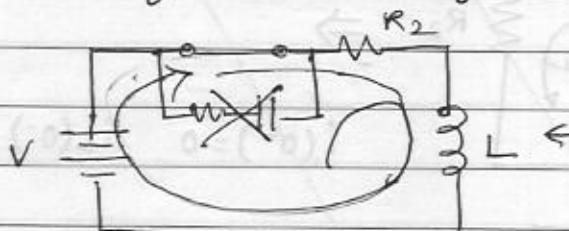b) If the parameters are adjusted such that $i(0^+) = 1$ and $\frac{di}{dt}(0^+) = -1$. What is the value of derivative of voltage acr the switch $\frac{dV_x}{dt}(0^+)$?



$$V_c(0^-) = 0; \quad i_L(0^-) = \frac{V}{R_2} = ;$$


At $t=0^+$; As ckt has reached steady state

$$i_L(0^+) = i_L(0^-) = \frac{V}{R_2} \quad V_c(0^+) = V_c(0^-) = 0.$$

$$V_c(0^-) = 0$$

& Switch K is open

By KVL

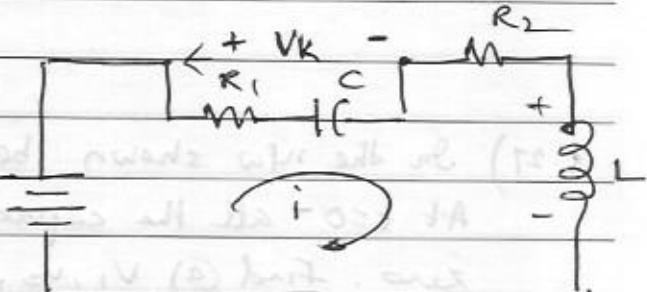

$$iR_1 + Vx + iR_2 + L \frac{di}{dt} = V$$

Voltage acr switch K.

$$Vx = R_1 i(0^+) + \frac{1}{C} \int_{-\infty}^{0^+} i dt \quad (i)$$

$$i(0^-) = \frac{V}{R_2}$$

& $V_c(0^-) = 0$.

$$Vx(0^+) = R_1 i(0^+) + \frac{1}{C} \int_{0^+}^{\infty} i(0^+) dt \quad (\because V_c(0^-) = 0)$$

$$= R_1 i(0^+) + V_c(0^+)$$

$$\boxed{Vx(0^+) = R_1 \frac{V}{R_2}}$$

b) derivation of eq2 (1)

$$\frac{dVx}{dt} = R_1 \cdot \frac{di(t)}{dt} + \frac{i}{C} = 0$$

$$\frac{di}{dt}(0^+) = 1$$

$$i(0^+) = 1$$

$$\frac{dVx(0^+)}{dt} = R_1 \frac{d}{dt} i(0^+) + \frac{i(0^+)}{C} = 0$$


$$= R_1 (\pm 1) + \frac{(1)}{C} = \frac{1}{C} - R_1$$

$$\boxed{\frac{dVx(0^+)}{dt} = \frac{1}{C} - R_1}$$


5.26) K is closed at $t=0$ connecting battery with unenergized systems

a) find voltage V_a at $t=0^+$.

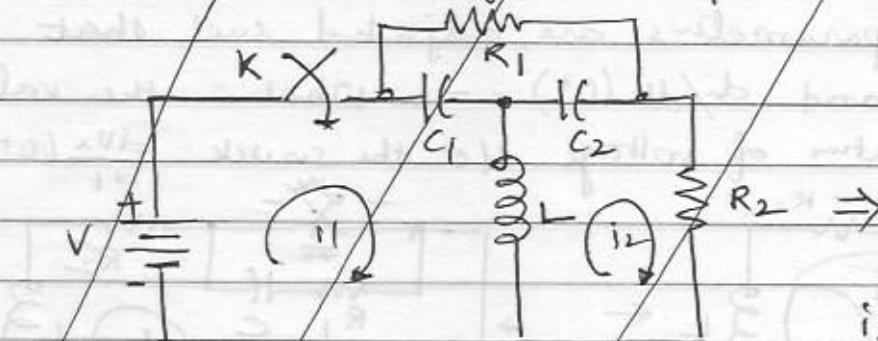b) find voltage across capacitor C_1 at $t=\infty$




$$i_1(0^-) = 0 \quad i_2(0^-) = 0$$

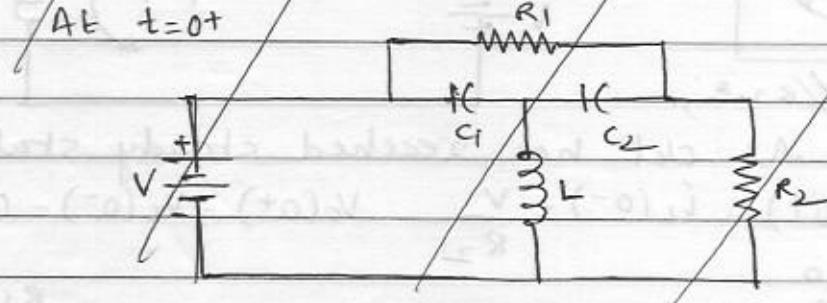

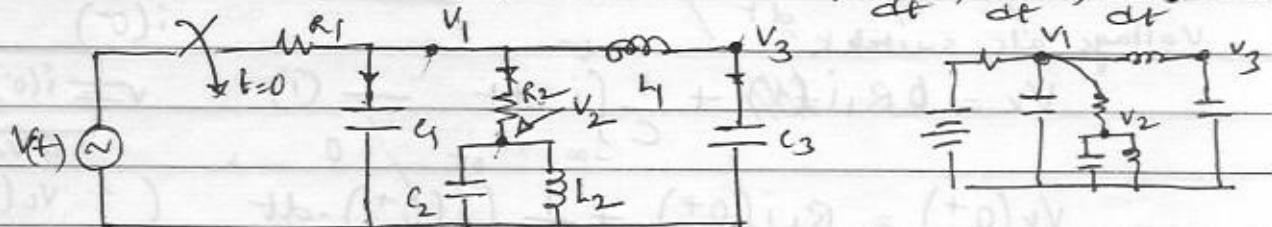5.27) In the nfw shown below, the switch K is closed at $t=0$.

At $t=0^-$ all the capacitor voltages and inductor currents are zero. Find (a) V_1, V_2, V_3 at $t=0^+$ b) $\frac{dv_1}{dt}, \frac{dv_2}{dt}, \frac{dv_3}{dt}$ at $t=0^+$



$$\text{i) } i_{L1}(0^-) = i_{L2}(0^-) = 0 \quad \& \quad V_{C1}(0^-) = V_{C2}(0^-) = V_{C3}(0^-) = 0$$

ii) At node V_1

$$\rightarrow \frac{V_1 - V(t)}{R_1} + C_1 \cdot \frac{dv_1}{dt} + \frac{V_1 - V_2}{R_2} + \frac{1}{L_1} \int_{-\infty}^t (V_1 - V_2 - V_3) \cdot dt$$

At $t=0^+$

$$\frac{V_1(0^+) - V(t)}{R_1} + C_1 \frac{dV_1(0^+)}{dt} + \frac{V_1(0^+) - V_2(0^+)}{R_2} + \frac{1}{L_1} \int_{-\infty}^0 (V_1(0^+) - V_3(0^+)) dt$$

$$\bullet \frac{V(t)}{R_1} = C_1 \frac{dV_1(0^+)}{dt} + 0 + 0$$

$$\therefore \frac{dV_1(0^+)}{dt} = \frac{1}{C_1} \cdot \frac{V(t)}{R_1}$$

DATE

ii) At node V_2 (KCL)

$$\frac{V_2 - V_1}{R_2} + C_2 \cdot \frac{dV_2}{dt} + \frac{1}{L_2} \int_{-\infty}^t V_2 \cdot dt = 0.$$

At $t=0^+$

$$\frac{V_2(0^+) - V_1(0^+)}{R_2} + C_2 \cdot \frac{dV_2(0^+)}{dt} + \frac{1}{L_2} \int_{-\infty}^0 V_2(0^+) \cdot dt = 0$$

$$\frac{0}{R_2} + C_2 \cdot \frac{dV_2(0^+)}{dt} + 0 = 0. \quad I_{L_2}(0^+)$$

$$\therefore \boxed{\frac{dV_2(0^+)}{dt} = 0} \quad \checkmark$$

iii) $V_3 - V_1$ & At node 3 (KCL)

$$\frac{1}{L_1} \int_{-\infty}^t (V_3 - V_1) dt + C_3 \cdot \frac{dV_3}{dt} + V_3 - V_2 = 0$$

$$I_{L_1}(0^+) = 0$$


At $t=0^+$

$$\frac{1}{L_1} \int_{-\infty}^0 V_3(0^+) - V_1(0^+) \cdot dt + C_3 \cdot \frac{dV_3(0^+)}{dt} = 0$$

$$C_3 \cdot \frac{dV_3(0^+)}{dt} = 0$$

$$\boxed{\frac{dV_3(0^+)}{dt} = 0} \quad \checkmark$$


- S.28) In the n/w shown steady state is reaches and at $t=0$, switch K is opened a) find the voltage acf switch, V_K at $t=0^+$
 b) find $\frac{dV_K}{dt}$ at $t=0^+$

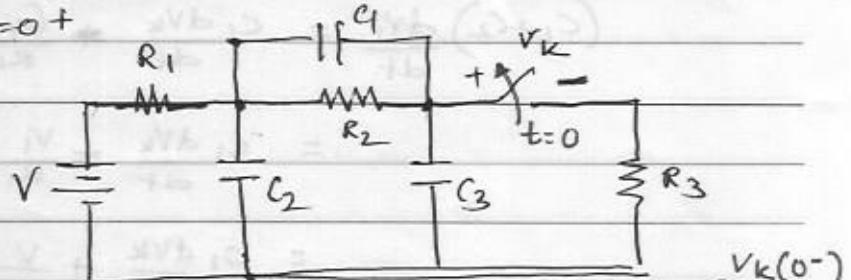At $t=0^+$

$$i(0^-) = \frac{V}{R_1 + R_2 + R_3}$$

$$V_K(0^-) = 0.$$
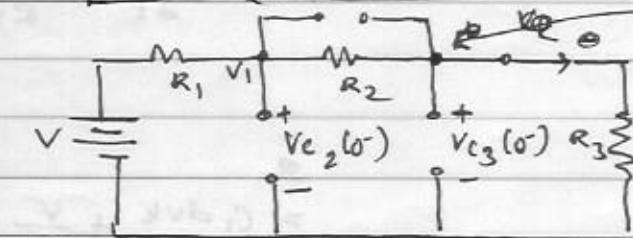
$$\therefore \text{At } t=0^+ \quad i(0^+) = \frac{V}{R_1 + R_2 + R_3}$$



$$\text{Loop 1: } V_{C_2(0^-)} + R_1 i - V = 0$$

$$\therefore [V_{C_2(0^-)} = V - R_1 i]$$

$$= V - R_1 \left(\frac{V}{R_1 + R_2 + R_3} \right)$$


$$\boxed{V_{C_2(0^-)} = V - \frac{VR_1}{R_1 + R_2 + R_3}} \quad -(2)$$

$$= \frac{V(R_1 + R_2 + R_3) - VR_1}{R_1 + R_2 + R_3}$$

$$\boxed{V_{C_2(0^-)} = \frac{V(R_2 + R_3)}{R_1 + R_2 + R_3} = V_{C_2(0^+)} = V_1(0^-) \equiv} \quad -(2)$$

$$\boxed{V_{C_3(0^-)} = V_k(0^-) = V_X(0^+) = i(0^-) \times R_3} \\ = \frac{V \times R_3}{R_1 + R_2 + R_3} \quad -(3)$$

At $t=0^+$

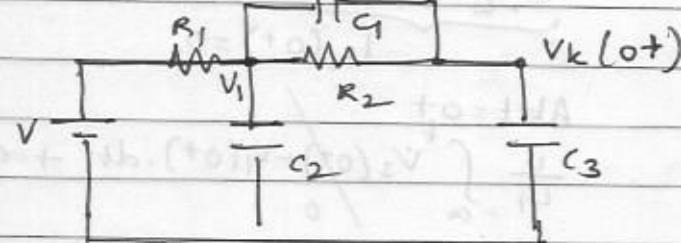

Applying KCL at node V_1

$$\frac{V_1 - V}{R_1} + C_2 \cdot \frac{dV_1}{dt} + C_1 \frac{d(V_1 - V_k)}{dt} + \frac{V_1 - V_k}{R_2} = 0$$

$$\frac{V_1 - V}{R_1} + C_2 \cdot \frac{dV_1}{dt} + \frac{C_1 dV_1}{dt} - C_1 \frac{dV_k}{dt} + \frac{V_1 - V_k}{R_2} = 0$$

$$(C_1 + C_2) \frac{dV_1}{dt} + \frac{V_1 - V}{R_1} - C_1 \frac{dV_k}{dt} + \frac{V_1 - V_k}{R_2} = 0$$

$$(C_1 + C_2) \frac{dV_1}{dt} = C_1 \frac{dV_k}{dt} \Rightarrow \frac{(V_1 - V)}{R_1} \neq \frac{C_1 \frac{dV_k}{dt}}{R_2} - \frac{(V_1 - V_k)}{R_2}$$

$$= C_1 \frac{dV_k}{dt} - \frac{V_1 - V}{R_1} + \frac{V}{R_1} + \frac{C_1 \frac{dV_k}{dt}}{R_2} - \frac{V_1}{R_2} + \frac{V_k}{R_2}$$

$$= C_1 \frac{dV_k}{dt} + \frac{V}{R_1} - \frac{V(R_2 + R_3)}{R_1(R_1 + R_2 + R_3)} - \frac{V(R_2 + R_3)}{R_2(R_1 + R_2 + R_3)} \\ + \frac{V(R_3)}{R_2(R_1 + R_2 + R_3)}$$

$$= C_1 \frac{dV_k}{dt} + \frac{V}{R_1} - \frac{V(R_2 + R_3)}{R_1(R_1 + R_2 + R_3)} - \frac{VR_2}{R_2(R_1 + R_2 + R_3)}$$

DATE

$$= C_1 \frac{dV_k}{dt} + \frac{1}{R_1} \left[V - V(R_2 + R_3) \right] - \frac{V}{R_1 + R_2 + R_3}$$

$$= \dots + \frac{1}{R_1} \left[\frac{V(R_1 + R_2 + R_3) - V(R_2 + R_3)}{(R_1 + R_2 + R_3)} \right] - \frac{V}{R_1 + R_2 + R_3}$$

$$= C_1 \frac{dV_k}{dt} + \frac{1}{R_1} \left[\frac{VR_1}{(R_1 + R_2 + R_3)} \right] - \frac{V}{R_1 + R_2 + R_3}$$

$$\boxed{\left(C_1 + C_2 \right) \frac{dV_1}{dt} = C_1 \frac{dV_k}{dt}} \quad + \textcircled{1} \quad \frac{dV_k}{dt} = \left(\frac{C_1 + C_2}{C_1} \right) \cdot \frac{dV_1}{dt}$$

$$\boxed{\frac{dV_1}{dt} = \left(\frac{C_1}{C_1 + C_2} \right) \frac{dV_k}{dt}} - \textcircled{4}$$

KCL at V_k

$$C_1 \frac{d(V_k - V_1)}{dt} + \frac{V_k - V_1}{R_2} + C_3 \cdot \frac{dV_k}{dt} = 0$$

$$C_1 \frac{dV_k}{dt} - C_1 \frac{dV_1}{dt} + \frac{V_k}{R_2} - \frac{V_1}{R_2} + C_3 \frac{dV_k}{dt} = 0$$

$$(C_1 + C_3) \frac{dV_k}{dt} = C_1 \frac{dV_1}{dt} + \frac{V_1}{R_2} - \frac{V_k}{R_2}$$

$$= C_1 \frac{dV_1}{dt} + \frac{1}{R_2} [V_1 - V_k]$$

$$= C_1 \frac{dV_1}{dt} + \frac{1}{R_2} \left[\frac{V(R_2 + R_3)}{R_1 + R_2 + R_3} - \frac{VR_3}{R_1 + R_2 + R_3} \right]$$

$$= C_1 \frac{dV_1}{dt} + \frac{1}{R_2} \left[\frac{VR_2}{R_1 + R_2 + R_3} \right]$$

$$(C_1 + C_3) \frac{dV_k}{dt} = C_1 \frac{dV_1}{dt} + \frac{V}{R_1 + R_2 + R_3} - \textcircled{5}$$

(4) is (5)

$$= \left(\frac{C_1^2}{C_1 + C_2} \right) \frac{dV_k}{dt} + \frac{V}{R_1 + R_2 + R_3}$$

$$(C_1 + C_3) \frac{dV_k}{dt} - \frac{C_1^2}{C_1 + C_2} \frac{dV_k}{dt} = \frac{V}{R_1 + R_2 + R_3}$$

$$\frac{dV_k}{dt} \left[(C_1 + C_3) - \frac{C_1^2}{C_1 + C_2} \right] = \frac{V}{R_1 + R_2 + R_3}$$

$$\frac{dV_k}{dt} \left[\frac{C_1^2 + C_1 C_2 + C_1 C_3 + C_2 C_3 - C_1^2}{C_1 + C_2} \right] = \frac{V}{R_1 + R_2 + R_3}$$

$$\boxed{\frac{dV_k}{dt} = \frac{V(C_1 + C_2)}{(C_1 C_2 + C_1 C_3 + C_2 C_3)(R_1 + R_2 + R_3)}}$$

DATE

$$\frac{[(C_1 + C_2)V - V]}{C_1 + C_2} + \frac{V}{R_2} =$$

$$\frac{[(C_1 + C_2)V - (C_1 + C_2 + R_1)V]}{C_1 + C_2 + R_1} + \frac{V}{R_2} =$$

$$\frac{V}{C_1 + C_2 + R_1} + \frac{V}{R_2} =$$

$$\frac{V}{C_1 + C_2 + R_1} + \frac{V}{R_2} = \frac{V}{R_2} = \frac{V}{R_2}$$

$$\textcircled{1} - \left[\frac{V}{R_2} \left(\frac{-R_1}{C_1 + C_2 + R_1} \right) \right] =$$

AV to -12V

$$0 = \frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} + \frac{V - 12V}{R_2} = \frac{(V - 12V)}{R_2}$$

$$0 = \frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} + \frac{-11V}{R_2} = \frac{-11V}{R_2}$$

$$\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} = \frac{-11V}{R_2} = \frac{-11V}{R_2}$$

$$\left[\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \right] \frac{1}{R_2} = \frac{-11V}{R_2^2}$$

$$\left[\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \right] \frac{1}{R_2} + \frac{V}{R_2} = 0$$

$$\left[\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \right] \frac{1}{R_2} + \frac{V}{R_2} = \frac{V}{R_2}$$

$$\textcircled{2} - \left[\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \right] \frac{1}{R_2} + \frac{V}{R_2} = \frac{V}{R_2}$$

$$\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \cdot \frac{1}{R_2} + \frac{V}{R_2} = \frac{V}{R_2}$$

$$\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \cdot \frac{1}{R_2} + \frac{V}{R_2} = \frac{V}{R_2}$$

$$\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \cdot \frac{1}{R_2} + \frac{V}{R_2} = \frac{V}{R_2}$$

$$\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \cdot \frac{1}{R_2} + \frac{V}{R_2} = \frac{V}{R_2}$$

$$\frac{V}{R_2} \cdot \frac{-R_1}{C_1 + C_2 + R_1} \cdot \frac{1}{R_2} + \frac{V}{R_2} = \frac{V}{R_2}$$


DATE _____

6.29) Consider a RLC ckt, which is excited by a voltage source

- Determine the characteristic eq₂ corresponds to differential eq₂ for $i(t)$
- Suppose L & C are fixed in value but R varies from 0 to ∞ . What will be locus of the roots of the characteristic eq₂?
- Plot the roots of characteristic eq₂ in s-plane if L=1H, C=1mF & R has the values (i) 500Ω (ii) 1kΩ (iii) 3kΩ (iv) 5kΩ

Sol:
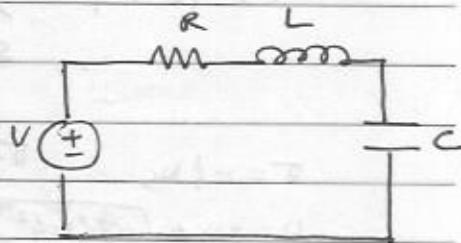
$$a) L \cdot \frac{di}{dt} + Ri + \frac{1}{C} \int_{-\infty}^t i \cdot dt = V$$



By differentiating

$$L \cdot \frac{d^2i}{dt^2} + R \cdot \frac{di}{dt} + \frac{1}{C} i = 0$$

$$\left(\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i \right) = 0$$

$$\left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) i = 0 \quad \text{where } i = k \cdot e^{st} \text{ form for homogen}$$

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$$

$$s_1, s_2 = -\alpha \pm \sqrt{(\alpha)^2 - \omega_s^2} \quad - \text{ Roots may be}$$

$$\therefore i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

- i) Real, Not equal
- ii) Real & equal
- iii) Complex (conjugate)

$$\alpha = \frac{R}{2L} \quad \omega_s = \frac{1}{\sqrt{LC}} \quad \xi = \frac{R}{L} \sqrt{\frac{C}{L}}$$

$$\xi = \frac{\alpha}{\omega_s} \quad \alpha = \xi \cdot \omega_s$$

$$\therefore s_1, s_2 = -\xi \omega_s \pm \sqrt{\left(\xi \omega_s\right)^2 - \omega_s^2}$$

$$\boxed{s_1, s_2 = -\xi \omega_s \pm \omega_s \sqrt{\xi^2 - 1}}$$

$$\xi = \frac{R}{L} \sqrt{\frac{C}{L}} \quad \text{if } R \text{ varies from } 0 \text{ to } \infty$$

ξ varies from 0 to ∞ .



PES

INSTITUTIONS

Case(i) ; when $R=0, \xi=0$

$$\therefore s_1, s_2 = -\xi \omega_s \pm \omega_s \sqrt{\xi^2 - 1}$$

$$= 0 + \omega_s \sqrt{-1}$$

$$[s_1, s_2 = \pm j \omega_s] \quad -(i)$$

Roots are complex conjugate & purely imaginary,
& Response is oscillatory if Roots lies on imaginary axis

case(2) ($0 < \xi < 1$)

$$s_1, s_2 = -\xi \omega_s \pm \omega_s \sqrt{\xi^2 - 1} = \underline{0 \pm j \omega_s}$$

$$= -\xi \omega_s \pm \omega_s \sqrt{-(1 - \xi^2)} = -\xi \omega_s \pm j \sqrt{1 - \xi^2}$$

$$\tau = -\xi \omega_s \quad \tau^2 + \omega^2 = \xi^2 \omega_s^2 \pm \omega_s^2 (\xi^2 - 1) = \underline{\tau \pm j \omega}$$

$$\omega = j \omega_s \sqrt{1 - (1 - \xi^2)} = \frac{1}{\xi} \omega_s^2 \pm \omega_s^2 \xi^2 - \omega_s^2$$

$$\tau^2 = \xi^2 \omega_s^2 \quad \tau^2 + \omega^2 = \xi^2 \omega_s^2 \pm j \omega (1 - \xi^2)$$

$$\omega^2 = \omega_s^2 (1 - \xi^2) \quad = \xi^2 \omega_s^2 \pm \omega_s^2 - \omega_s^2 \xi^2$$


$$\boxed{\tau^2 + \omega^2 = \omega_s^2}$$

Roots move on a circle, described by a circle of radius ω_s .

Case iii) $\xi > 1$; $s_1, s_2 = -\xi \omega_s \pm \omega_s \sqrt{\xi^2 - 1} \quad \xi > 1, \xi^2 > 1$
 $= -\xi \omega_s \pm \omega_s \sqrt{\xi^2 - 1} \quad \therefore 1 is neglected.$

 $s_1, s_2 = -\xi \omega_s \pm \omega_s \xi$
 $s_1 = -\xi \omega_s + \omega_s \xi \quad s_2 = -\xi \omega_s - \omega_s \xi$
 $= \underline{0} \quad = -2 \xi \omega_s$

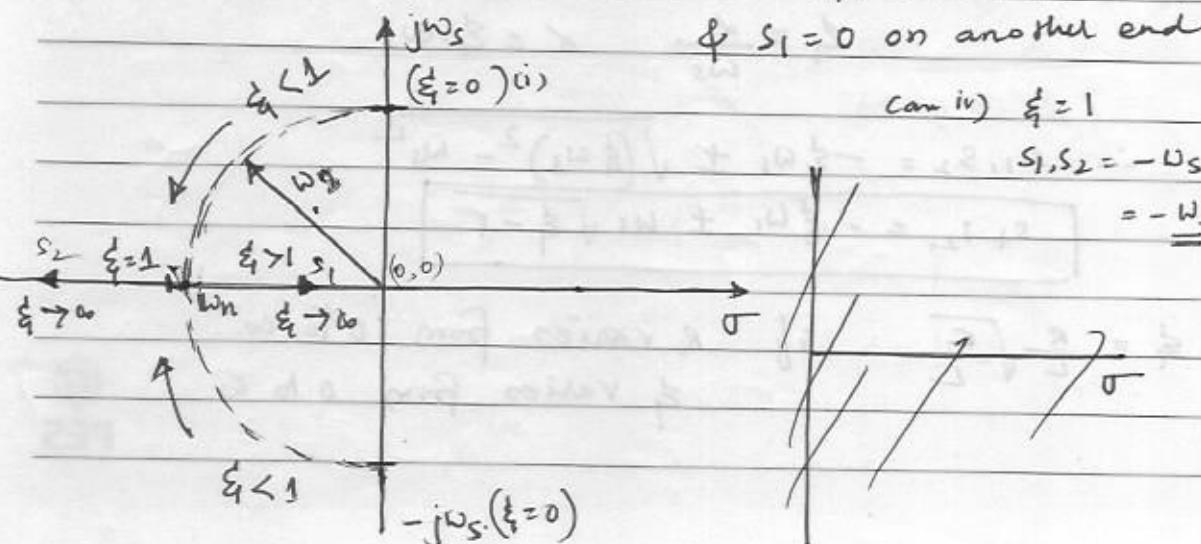As $\xi \rightarrow \infty, s_2 \rightarrow -\infty$ at one end.





case iv) $\xi = 1$

$$s_1, s_2 = -\omega_s \pm \omega_s \sqrt{1 - 1}$$

$$= -\underline{\omega_s}$$

DATE

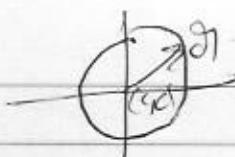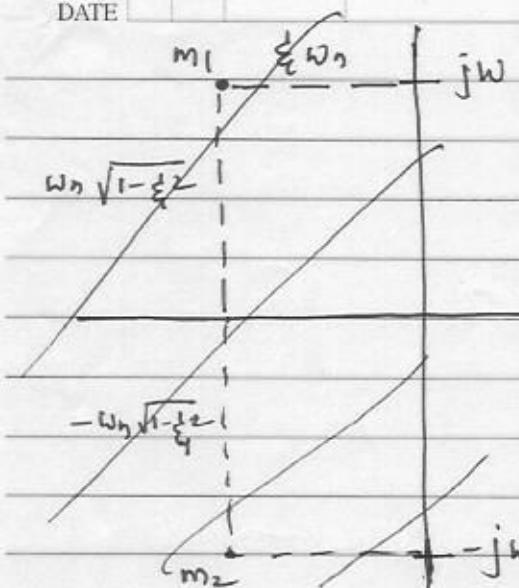

$$\begin{aligned} x^2 + y^2 &= 1 \\ (x-jy)^2 + (y-jx) &= 1 \\ S_1, S_2 = -\frac{j}{\xi} w_n \pm \sqrt{1-\xi^2} \end{aligned}$$

$$0 < \xi < 1$$

(a) Location of Roots

1) $R = 500\Omega, L = 1H, C = 10\mu F$

$$w_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10 \times 10^{-6}}} = 1000 \text{ Hz}$$

$$\xi = \frac{R}{2\sqrt{\frac{C}{L}}} = \frac{500}{2\sqrt{\frac{1 \times 10^{-6}}{1}}} =$$

$$\xi = 0.25. \quad \therefore \xi < 1$$

(1) $S_1 = (-250 + j968.24)$

$$S_1, S_2 = -\frac{j}{\xi} w_n \pm j w_n \sqrt{1-\xi^2}$$

$$= -0.25 \times 1000 \pm j 1000 \sqrt{1-0.25^2}$$

$$= -250 \pm j 968.245$$

-250

2) $R = 1000\Omega$

$$w_n = 1000 \text{ Hz}$$

$$\xi = \frac{1000}{2} \sqrt{\frac{1 \times 10^{-6}}{1}} =$$

$$= 500 \times 1 \times 10^{-3}$$

$$\xi = 0.5 \quad \boxed{\xi < 1}$$

$$= (-250 - j968.24)$$

(2) $-500 + j966.025$

$$S_1, S_2 = -0.5 \times 1000 \pm j 1000 \sqrt{1-0.5^2}$$

$$\boxed{S_1, S_2 = -500 \pm j 866.025}$$

-500

3) $R = 3000$.

$$\xi = \frac{3000}{2} \sqrt{\frac{1 \times 10^{-6}}{1}} = 1500 \times 1 \times 10^{-3} = 1.5$$

$$\boxed{\xi > 1}$$

(3)

$$\begin{aligned} S_1, S_2 &= -\frac{j}{\xi} w_n \pm w_n \sqrt{\xi^2 - 1} \\ &= -1.5 \times 1000 \pm 1000 \sqrt{1.5^2 - 1} \end{aligned}$$

$$S_1, S_2 = -1500 \pm j 1118$$

$$S_1, S_2 = -1500 - j 1118, -2618$$

4) $R = 5000$

$$\xi = 2.5 \quad \xi > 1$$

$$S_1, S_2 = -2500 \pm 2291.28 = -208.72, -4791.25$$

$$\begin{matrix} S_2 \\ \rightarrow \infty \end{matrix}$$

$$\begin{matrix} S_1 \\ \rightarrow 0 \end{matrix}$$

DATE

1 > } > 2

Welding resistance is

proportional to current (I)

proportional to electrode length (L)

$$\text{Current} = \frac{k}{L} I^2$$

$$1 > 2 \rightarrow 2.00 = 3$$

$$k = 1 \rightarrow k = 2.00 \rightarrow 2.00 \text{ PARAP} \quad (W[100] = 12) \quad (1)$$

$$2.00 = 0.00$$

$$= 0.00 \rightarrow 0.00$$

$$= 0.00$$

$$2.00 \times 2.00 = 4$$

$$= 0.00$$

$$2.00 \times 0.00 =$$

$$(0.00)(-0.00) =$$

$$1 > 2 \rightarrow 2.00 = 3$$

$$2.00 = 3$$

$$2.00 = 0.00 \times 2.00 = 2.00$$

$$[2.00 \times 2.00] + 0.00 = 2.00$$

$$0.00 = 0.00 \quad (6)$$

$$0.00 \times 0.00 = 0.00$$

$$2.00 = 3$$

$$[1 < 2]$$

$$2.00 = 0.00 \rightarrow 2.00$$

$$R1000 \times 0.00 = -0.00$$

$$2.00 = -0.00 = 0.00 = 2.00$$

$$0.00 = 0$$

$$1 < 2 \rightarrow 2.00 = 3$$

$$2.00 \times 0.00 = 0.00 \rightarrow 2.00 = 2.00$$


DATE

discharge of lightning

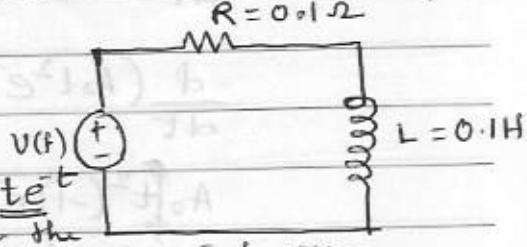- 6.23 (1) A bolt $\frac{di}{dt}$ of lightening having a waveform which approximates as $V(t) = t \cdot e^{-t}$ strikes a transmission line having resistance of $R = 0.1\Omega$ and inductance $L = 0.1H$ (the line to line capacitance negligible)

What is the form of the current as a function of time?

(This current will be Amp/Unit volt $= \frac{t}{L} e^{-t}$ of lightning, where the time base is linear
solt:




solt:

$$KVL \quad L \cdot \frac{di}{dt} + Ri = t \cdot e^{-t} \quad (1)$$

$$\frac{di}{dt} + \left(\frac{R}{L}\right)i = \frac{t}{L} e^{-t}$$
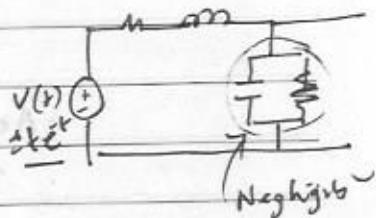
$$\frac{di}{dt} + \left(\frac{0.1}{0.1}\right)i = \frac{t}{0.1} e^{-t}$$



$$\boxed{\frac{di}{dt} + i = 10t \cdot e^{-t}} \quad (2)$$

Characteristic eq2 can be written as

$$si + i = 10t \cdot e^{-t}$$

$$\boxed{(s+1)i = 10t \cdot e^{-t}} \quad (3)$$

The response of the n/w.

$$\boxed{i(t) = i_c(t) + i_p(t)}$$

(i) Complementary sol² $i_c(t)$ of the form $K \cdot e^{st}$

$$(s+1)i = 0$$

$$\therefore s = -1 \quad \text{and} \quad i_c(t) = K \cdot e^{st} \\ = K \cdot e^{-t}$$

$$\boxed{i_c(t) = K \cdot e^{-t}} \quad (4)$$

(ii) Particular sol² $i_p(t)$

In this, forcing factor is $(10t)e^{-t}$ ie $(At^n)e^{-t}$ form

$$\therefore i_p(t) = (A_0 t + A_1) e^{-t}$$

$$\boxed{i_p(t) = A_0 t e^{-t} + A_1 e^{-t}} \quad (5)$$

\hookrightarrow It is of $i_c(t)$ form.

\therefore change the form by multiplying by a linear factor to eq2 (5)

$$i_p(t) = (A_0 t e^{-t} + A_1 e^{-t}) \times t = \boxed{A_0 t^2 e^{-t} + A_1 t \cdot e^{-t}} \quad (6)$$

Substituting $i_p(t) - eq^2(6)$ in $eq^2(2)$

$$\frac{d(i_p(t))}{dt} + i_p(t) = 10t e^{-t}$$

$$\frac{d(A_0 t^2 e^{-t} + A_1 t e^{-t})}{dt} = 10t e^{-t}$$

$$A_0 \cancel{t^2(-1)e^{-t}} + A_0 \cancel{e^{-t} 2(t)} + A_1 \cancel{t(-1)e^{-t}} + A_1 \cancel{e^{-t}(1)} = 10t e^{-t}$$

$$-A_0 t^2 e^{-t} + A_0 2t e^{-t} \cancel{+ A_1 t e^{-t} + A_1 e^{-t}} = 10t e^{-t}$$

$$-A_0 t^2 e^{-t} + A_0 2t e^{-t} + A_1 t e^{-t} = 10t e^{-t}$$

$$-A_0 t^2 e^{-t} + \cancel{A_0 2t e^{-t}} - A_1 t e^{-t} + A_1 e^{-t} \\ + A_0 t^2 e^{-t} + A_1 t e^{-t} = \underline{10t e^{-t}} + 0 e^{-t}$$

Equaling coefficients

$$2A_0 = 10$$

$$A_1 = 0$$

$$\boxed{A_0 = 5}$$

$$\therefore i_p(t) = A_0 t^2 e^{-t} + A_1 t e^{-t} \\ = \underline{s t^2 e^{-t}} + 0 t e^{-t} = s t^2 e^{-t}$$

$$\boxed{i(t) = \cancel{K e^{-t}} + s t^2 e^{-t}} \quad -(7) \quad \boxed{i(t) = s t^2 e^{-t}}$$

Using initial condition. i.e $i(0^-) = 0 = i(0^+)$, K is found
 $t=0^+$ in $eq^2(7)$ $i(0^+) = K e^0 + 50$

$$i(0^+) = K$$

$$\boxed{K = 0}$$

$$\therefore i(t) = 0 \times e^{-t} + s t^2 e^{-t}$$

$$\boxed{i(t) = s t^2 e^{-t}} \quad -(8)$$

This indicates that there is No complementary sol²; $i(t)$ has only particular sol².

DATE

$$\text{method 2: } \frac{di}{dt} + i = 10te^{-t} \quad (1)$$

$$\frac{di}{dt} + i = 0$$

$$\text{LT } sI(s) - i(0^-) + I(s) = \frac{10}{(s+1)^2}$$

$$sI(s) - i(0^-) + I(s) = 0$$

$$(s+1)I(s) = i(0^-)$$

$$sI(s) + I(s) = \frac{10}{(s+1)^2}$$

$$\frac{I(s)}{s+1} = 0$$

$$I(s)(s+1) = \frac{10}{(s+1)^2}$$

$$\text{ILT } i_c(t) = 0$$


$$I(s) = \frac{10}{(s+1)^3} \quad (2)$$

$$\frac{10}{10 \times t^2 e^{-t}} \times t^2 e^{-t}$$

Using ILT

$$i_p(t) = \frac{10}{2!} t^2 e^{-t} = 5t^2 e^{-t}$$

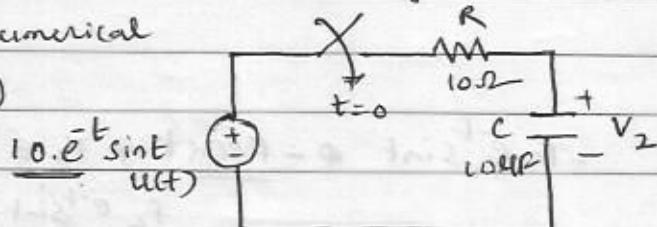- 6.24) In the n/w switch K is closed at $t=0$ with capacitor initially uncharged. For the numerical values given find $i(t)$



sol: KVL to the loop.

$$Ri + \frac{1}{C} \int_{-\infty}^t i \cdot d\tau = 10e^{-t} \sin t \quad (1)$$

$$R \frac{di}{dt} + \frac{1}{C} i = 10 \left[e^{-t} \cos t + \sin(-1) e^{-t} \right]$$

$$\left[\frac{di}{dt} + \frac{1}{RC} i = \frac{10}{R} [e^{-t} \cos t - \sin(-1) e^{-t}] \right] \quad (2)$$

Substitute $R \otimes C$

$$\text{Backward then, } \frac{di}{dt} + 10^4 i = (e^{-t} \cos t - e^{-t} \sin t) \quad (2)$$

$$(1) \text{ Complementary sol: } i_c(t) = K \cdot e^{st} \quad \rightarrow \text{RHS.}$$

$$\frac{di}{dt} + \frac{1}{RC} i = 0 \quad si + \left(\frac{1}{RC} \right) i = 0 \quad \text{general}$$

$$\left(s + \frac{1}{RC} \right) = 0$$

$$\therefore i_c(t) = K \cdot e^{-10^4 t}$$

$$s = -\frac{1}{RC} = -\frac{1}{10 \times 10 \times 10^{-6}}$$

$$s = -10^4$$

(ii) Particular sol: $i_p(t) = \text{w.r.t to forcing function}$

$$10 \cdot e^{-t} \cdot \sin t \quad \boxed{10e^{-t} \cos t - 10e^{-t} \cdot \sin t}$$

$$10t^0 e^{-t} \cdot \sin t$$

$$i_p(t) = e^{-t} (A_1 \cos \omega t + B_1 \sin \omega t) - e^{-t} (A_2 \cos \omega t + B_2 \sin \omega t)$$

$$= e^{-t} \left(\frac{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} \right) \cos(\omega t - \tan^{-1}(RC))$$

$$- e^{-t} (A_2 \cos \omega t +$$

$$\boxed{i_p(t) = F_1 e^{-t} \cos \omega t + F_2 e^{-t} \sin \omega t} \quad -(4)$$

(4) in (2)

$$\frac{d}{dt} (F_1 e^{-t} \cos \omega t + F_2 e^{-t} \sin \omega t) + \frac{1}{RC} (F_1 e^{-t} \cos \omega t + F_2 e^{-t} \sin \omega t)$$

$$= 10e^{-t} \cos t - 10e^{-t} \sin t$$

$$F_1 e^{-t} \cdot (-\sin t) + F_1 \cos t \cdot (-1) e^{-t} + F_2 e^{-t} \cos t + F_2 e^{-t} \sin t (-1) \cdot e^{-t}$$

$$+ \frac{1}{RC} (F_1 e^{-t} \cos t + F_2 e^{-t} \sin t)$$

$$= 10e^{-t} \cos t - 10e^{-t} \sin t$$

$$-F_1 e^{-t} \sin t - F_1 e^{-t} \cos t + F_2 e^{-t} \cos t - F_2 e^{-t} \sin t + 10^4 (F_1 e^{-t} \cos t + F_2 e^{-t} \sin t) = 10e^{-t} \cos t - 10e^{-t} \sin t$$

$$-F_1 e^{-t} \sin t + 9999 F_1 e^{-t} \cos t + F_2 e^{-t} \cos t + 9999 F_2 e^{-t} \sin t = 10e^{-t} \cos t - 10e^{-t} \sin t$$

$$e^{-t} \sin t (9999 F_2 - F_1) + e^{-t} \cos t (9999 F_1 + F_2) = 10e^{-t} \cos t - 10e^{-t} \sin t$$

$$9999 F_2 - F_1 = 10^4 - 1$$

$$9999 F_1 + F_2 = 10^4 - 1$$

$$\begin{aligned} -F_1 + 9999 F_2 &= -1 \\ 9999 F_1 + F_2 &= 1 \end{aligned} \quad \left. \right\} \quad -(5)$$

$$F_1 = 1 \times 10^{-4}$$

$$F_2 = -9.999 \times 10^{-5}$$

$$\therefore \boxed{i_p(t) = 10^4 e^{-t} \cos t - 10^4 e^{-t} \sin t} \quad = -10^{-4}$$

$$i(t) = i_c(t) + i_p(t)$$

DATE

$$i(t) = K \cdot e^{-10^4 t} + 10^4 e^{-t} \cos t - 10^4 e^{-t} \sin t$$

$t=0$ By substituting initial cond: K is found.

$$i(0+) = K e^0 + 10^4 e^0 \cos(0) - 10^4 e^0 \sin(0)$$

$$= K + 10^4 - 10^4(0)$$

$$0 = K + 10^4$$

Final response: $K = -10^4$.

$$\therefore i(t) = -10^4 e^{-10^4 t} + 10^4 e^{-t} \cos t - 10^4 e^{-t} \sin t$$

6.33) A switch is closed at $t=0$, connecting a battery of voltage V with series RL ckt.

a) Show that, energy in the resistor as function of time is

$$w_R = \frac{V^2}{R} \left(t + \frac{2L}{R} e^{-t\frac{R}{L}} - \frac{L}{2R} e^{-2\frac{R}{L}t} - \frac{3L}{2R} \right) \text{Jah}$$


b) find an expression for energy in magnetic field as a function of time

c) sketch w_R and w_L as functions of time. Show the steady state asymptotes, that is, the values that w_R, w_L approach as $t \rightarrow \infty$

d) find the total energy supplied by the voltage source is steady state as function of time.

a) $i(0-) = 0 = i(0+)$

$$i(\infty) = \frac{V}{R}$$

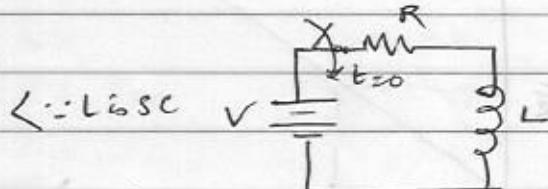

$$w_R = \frac{1}{2} \int_0^t i^2(z) \cdot R \cdot dt = \frac{1}{2} \int_0^t \left(\frac{V}{R}\right)^2 \cdot R \cdot dt.$$

$$\left[i(t) = \frac{V}{R} \left(1 - e^{-t\frac{R}{L}} \right) \right] \quad \text{--- (1)}$$

$$w_R = \int_0^t i^2(z) \cdot R \cdot dt = \int_0^t \left(\frac{V}{R}\right)^2 \left(1 - e^{-t\frac{R}{L}}\right)^2 \cdot R \cdot dt$$

$$= \frac{V^2}{R^2} \cdot R \int_0^t \left(1 - e^{-\frac{R}{L}t}\right)^2 \cdot dt$$

DATE

$$\omega_R = \frac{V^2}{R} \int_0^t (1 + e^{-2t\frac{R}{L}} - 2 \times 1 \times e^{-t\frac{R}{L}}) dt$$

$$= \frac{V^2}{R} \left[t \left| -\frac{e^{-2t\frac{R}{L}}}{2\left(\frac{R}{L}\right)} \right|_0^t + \frac{2}{R} \left| e^{-t\frac{R}{L}} \right|_0^t \right]$$

$$= \frac{V^2}{R} \left[t - \left(\frac{L}{2R} e^{-2t\frac{R}{L}} - \frac{L}{2R} e^0 \right) + \left(\frac{2L}{R} \left(e^{-t\frac{R}{L}} - e^0 \right) \right) \right]$$

$$= \frac{V^2}{2} \left[t - \frac{L}{2R} e^{-2t\frac{R}{L}} + \frac{L}{2R} + \frac{2L}{R} e^{-t\frac{R}{L}} - \frac{2L}{R} \right]$$



$$= \frac{V^2}{2} \left[t + \frac{2L}{R} e^{-t\frac{R}{L}} - \frac{L}{2R} e^{-2t\frac{R}{L}} + \frac{L}{2R} - \frac{2L}{R} \right]$$

$$\omega_R = \frac{V^2}{2} \left[t + \frac{2L}{R} e^{-t\frac{R}{L}} - \frac{L}{2R} e^{-2t\frac{R}{L}} - \frac{3L}{2R} \right] \text{ Joules}$$

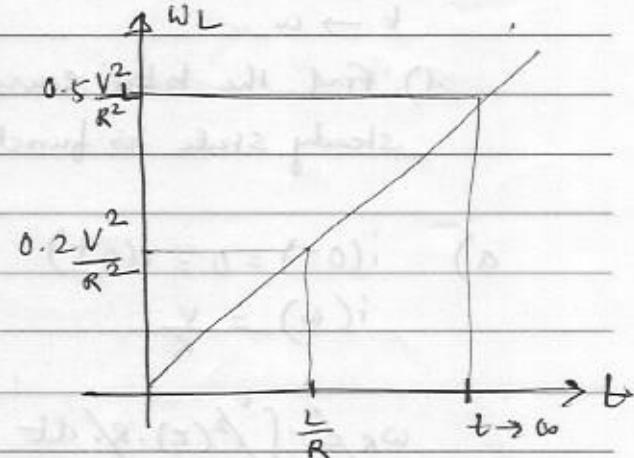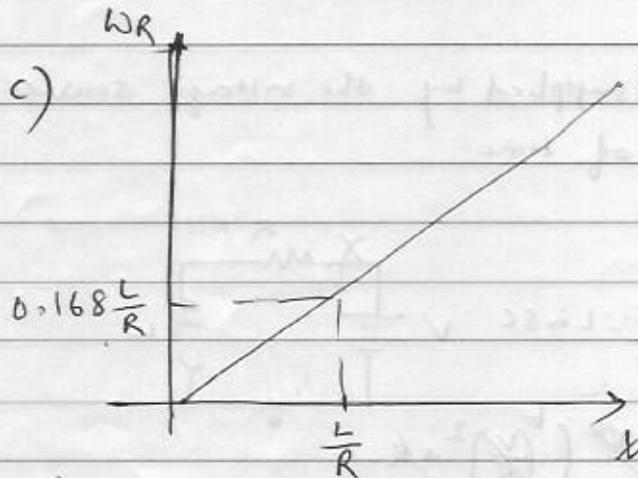b) Energy is magnetic f

$$W_L = \frac{1}{2} L i^2(t)$$

$$= \frac{1}{2} \times L \times \frac{V^2}{R^2} \left(1 - e^{-\frac{R}{L}t} \right)^2$$



d)



DATE

* Special cases [Capacitor voltage & Inductor current changes instantaneously]

- Capacitors are not initially charged and switch K is closed at $t=0$

- w.r.t capacitor acts like a short circuit

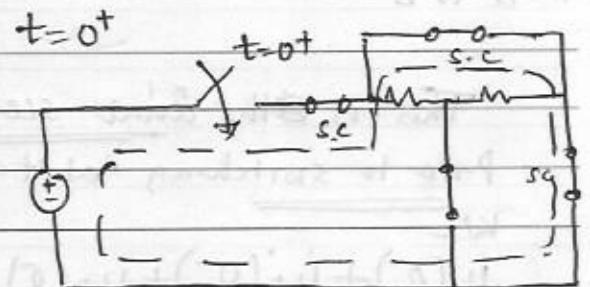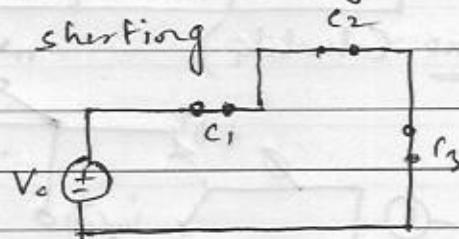\therefore It results into voltage source shorting



\therefore the voltage source produces an infinite current over an infinitesimally short interval of time.

- The charge transferred,

$q = \int_{0^-}^{0^+} i(t) dt$ is however finite and is such that

$$V_o = V_{C_1}(0^+) + V_{C_2}(0^+) + V_{C_3}(0^+)$$

$$V_o = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3}$$

(All initially loop with series $\therefore q$ is same)

[Thus infinite current in the interval $[0^-, 0^+]$ deposits sufficient charges on the cap that KVL satisfied]

The infinite current in the interval $[0^-, 0^+]$ is mathematically modelled using Dirac Delta impulse.

Under this condition; the voltage across a cap changes instantaneously.


A similar analysis holds even if the cap is charged prior to switching

Note: Ideal model of cap is assumed, In practice there is always some shag resistance which prevents infinite current flowing

Cox (ii) : Duality case

- There is No current flowing through inductors initially & switch close at $t=0$;

i.e changes position from a to b

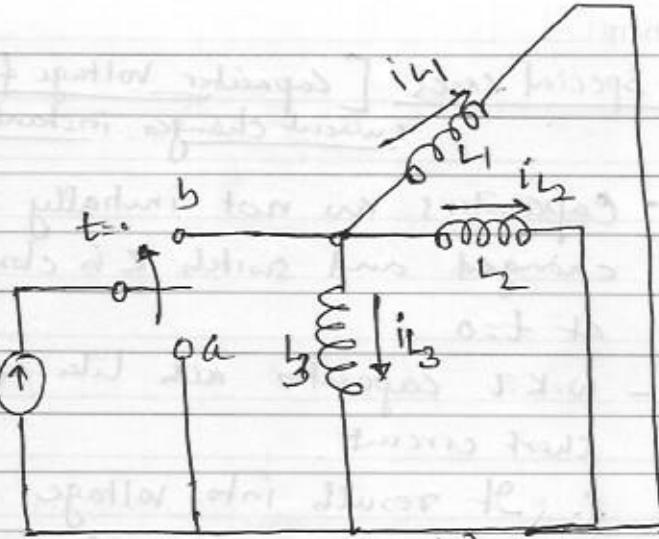

This is the dual scenario (duality)

- Prior to switching at $t=0^-$

KCL


$$i_{L1}(0^-) + i_{L2}(0^-) + i_{L3}(0^-) = 0 \quad (1)$$

- Immediately after switch $t=0^+$, KCL

$$i_{L1}(0^+) + i_{L2}(0^+) + i_{L3}(0^+) = I_0 \quad (2)$$

From (2), it is clear that $i_{L1}(0^+), i_{L2}(0^+), i_{L3}(0^+)$ cannot be zero

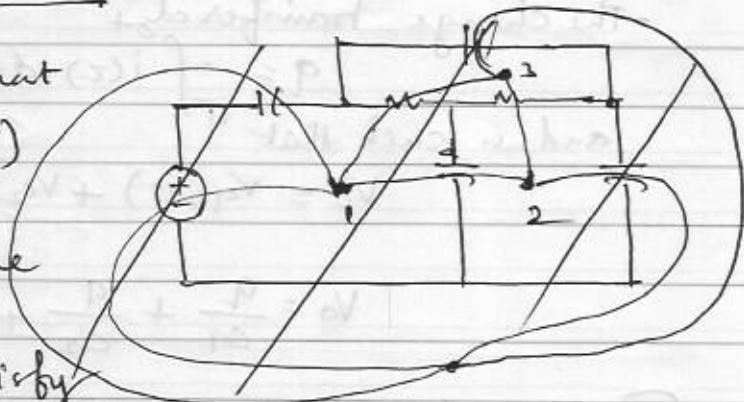∴ Current through the inductor must change instantaneously to satisfy both the eq²



- In this case, An infinite voltage is generated due to switching action that produces sufficient ~~flux~~ finite flux for the above to satisfy

$$\phi = \int_{0^-}^{0^+} v(t) \cdot dt \Rightarrow \frac{\phi}{L_1} + \frac{\phi}{L_2} + \frac{\phi}{L_3} = I_0$$

DATE _____

- The infinite voltage in the interval $[0^-, 0^+]$ is mathematically modelled using the Dirac Delta impulse.
- Under this case, the current through an inductor changes instantaneously.
- A similar analysis holds even if the inductors are carrying prior to switching.
- Note, ideal model of inductor is assumed. In practice, there is always some stray resistance which prevents infinite voltage to be generated.

* Note : Relationship between quantity $\Omega = \frac{1}{2\xi}$

Overdamped : $\xi > 1$ or $\alpha < 0.5$ ($\Rightarrow R > R_{cr}$)

Critically damped : $\xi = 1$. or $\alpha = 0.5$ ($R = R_{cr}$)

Underdamped : $\xi < 1$, $\alpha > 0.5$ ($\Rightarrow R < R_{cr}$)

* RL Ckt driven by $V \sin(\omega t + \theta)$.

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L} \sin(\omega t + \theta)$$

Using the procedure

$$i_p(t) = \frac{V}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\omega t + \theta - \tan^{-1} \frac{\omega L}{R}\right)$$

$$\therefore i(t) = \frac{V}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\omega t + \theta - \tan^{-1} \frac{\omega L}{R}\right) + k e^{-\frac{Rt}{L}}$$

If switch is closed at $t=0$, $i(0^+) = 0$.

$$\therefore k = -\frac{V}{\sqrt{R^2 + \omega^2 L^2}} \sin\left(\theta - \tan^{-1} \frac{\omega L}{R}\right)$$

$$k = -\frac{v}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\theta - \tan^{-1} \left(\frac{\omega L}{R} \right) \right)$$

If θ is chosen s.t

$$\theta = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

then $k=0$

- There is no transient response
- A similar phenomenon can be shown to exist for RC

nfu
factor in $v(t)^2$

Necessary choice for particular integral

V

$a_1 t^n$

$a_2 e^{rt}$

$a_3 \cos \omega t$

$a_4 \sin \omega t$

A

$B_0 t^n + B_1 t^{n-1} + \dots + B_{n-1} t + B_n$,

$C e^{rt}$

$\} D \cos \omega t + E \sin \omega t$

$a_5 t^n e^{rt} \cos \omega t$

$a_6 t^n e^{rt} \sin \omega t$

$(F_1 t^n + \dots + F_{n-1} t + F_n) e^{rt} \cos \omega t$


$+ (G_1 t^n + \dots + G_n) e^{rt} \sin \omega t$.

DATE

* Waveform Synthesis (


A unit step function

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

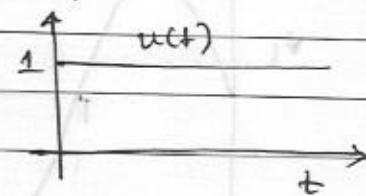A function which changed abruptly from zero to unit value at $t=0$

(i) A pulse function in terms of step functions.


$$u(t-a)$$

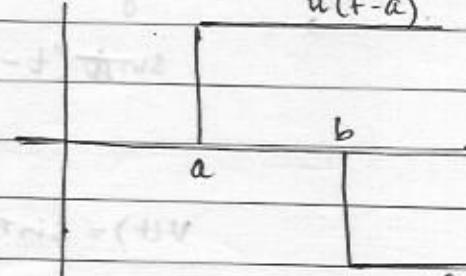

$$v(t) = u(t-a) + (-u(t-b))$$

$$v(t) = u(t-a) - u(t-b)$$

$$u(b-t)$$

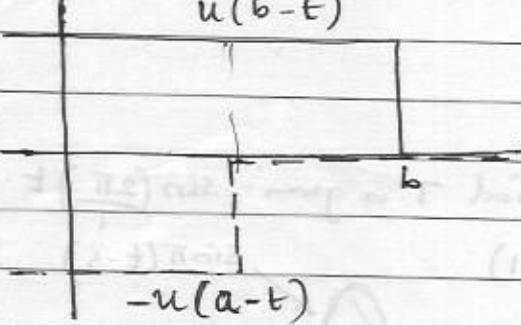


$$u(b-t) + (-u(a-t))$$

$$u(t-a)$$


$$v(t) = u(b-t) - u(a-b)$$

$$u(b-t)$$

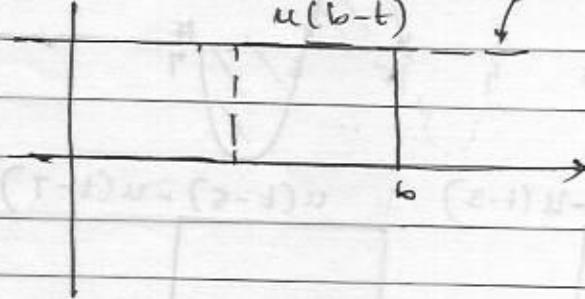


$$v(t) = u(t-a) \times u(b-t)$$


(ii) A half cycle of sinewave

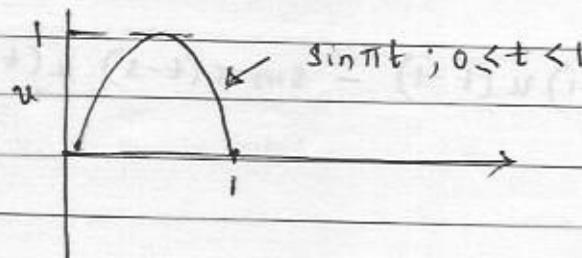


DATE

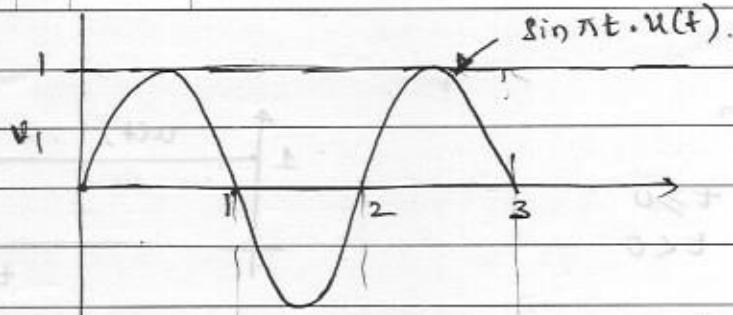

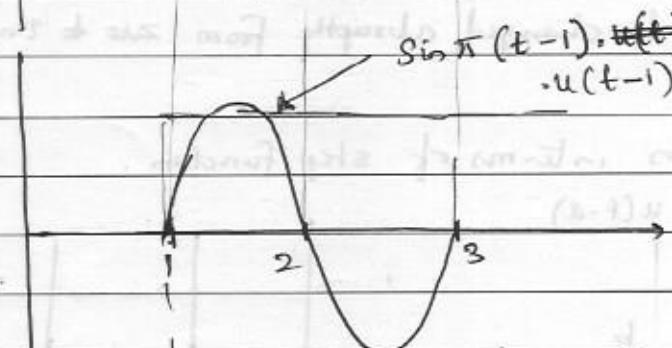- Sinewave defined for positive time, and zero for all \leftarrow negative time.
 $\sin\pi t \cdot u(t)$.




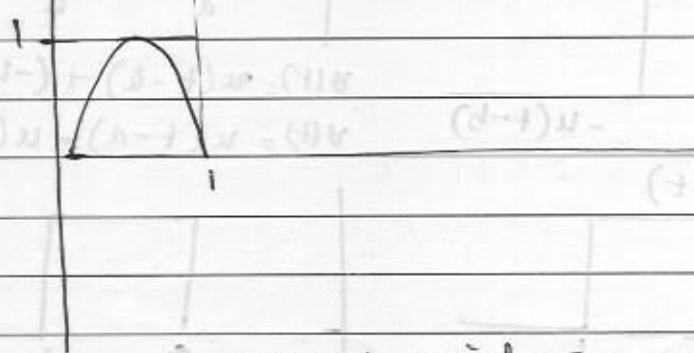- Sinewave is shifted version of $\sin\pi t \cdot u(t)$ by 1 unit times
 $\sin\pi(t-1) \cdot u(t-1)$




$$v(t) = \sin\pi t \cdot u(t) + \sin\pi(t-1) \cdot u(t-1).$$

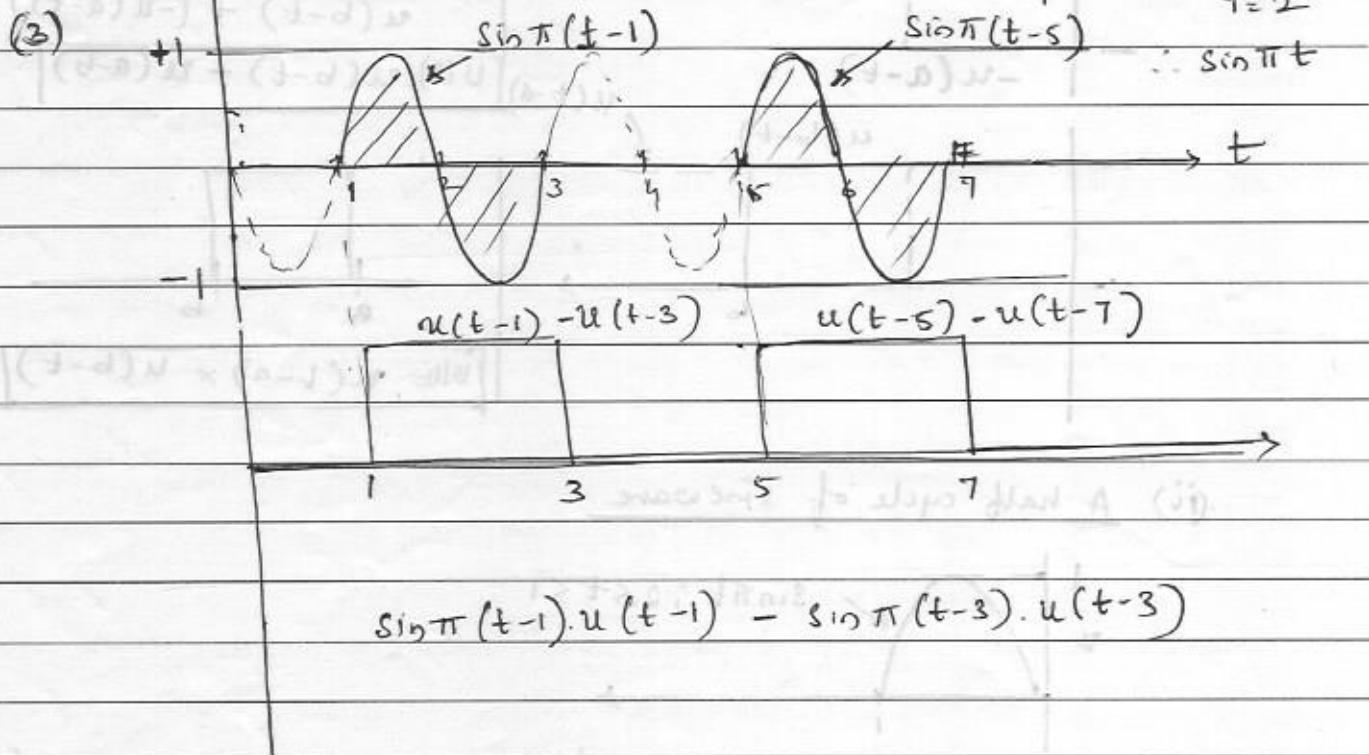Sinewave with period T is given $\sin\left(\frac{2\pi}{T}\right)t$. In this



$$\sin\pi(t-1) \cdot u(t-1) - \sin\pi(t-3) \cdot u(t-3)$$


DATE

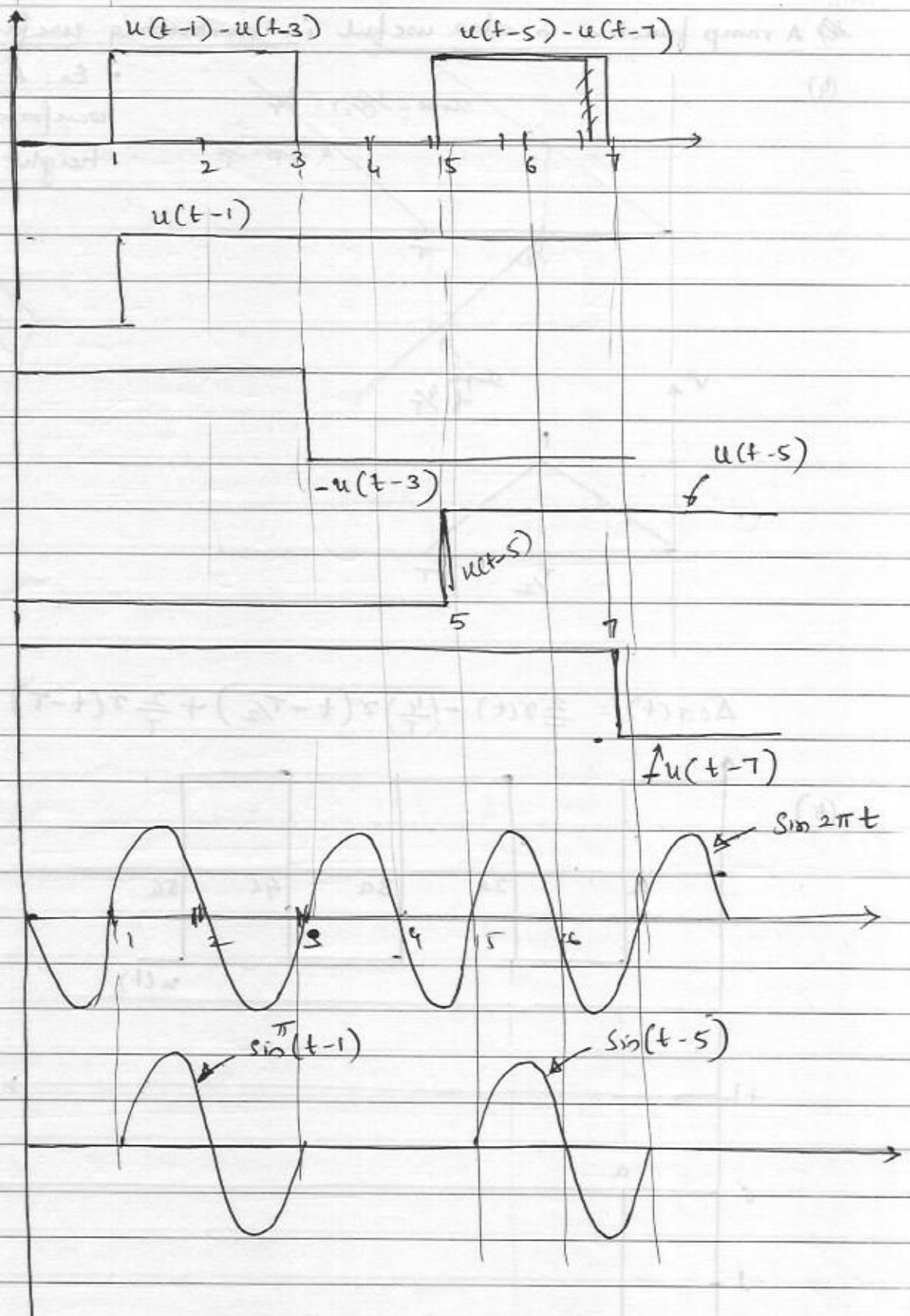

$$u(t) = [\sin \pi(t-1) \cdot u(t-1)] - [\sin \pi(t-3) \cdot u(t-3)] + [\sin \pi(t-5) \cdot u(t-5)] - [\sin \pi(t-7) \cdot u(t-7)] \quad (1)$$

(4) A ramp function is also useful in constructing useful waveform


(4)

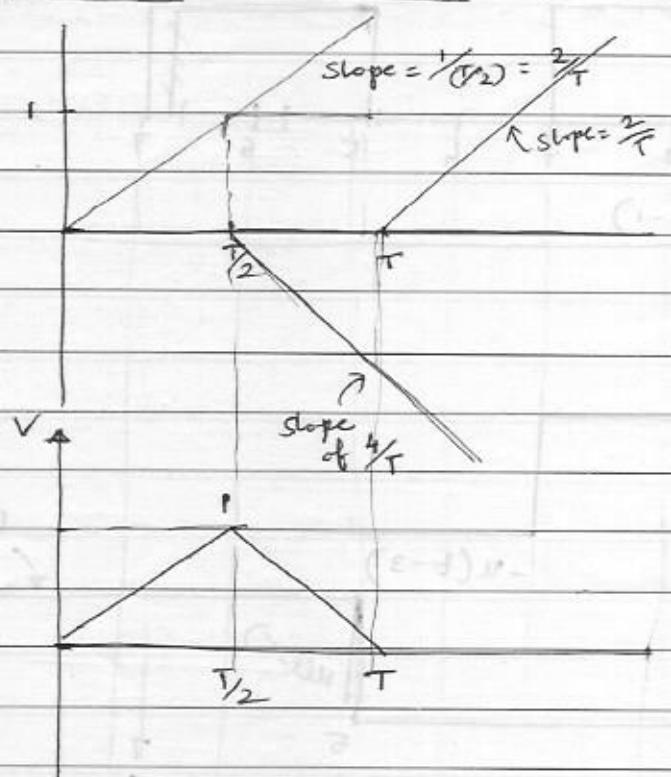


- Ex: A triangular waveform with unit height and T duration

$$\Delta_{0,T}(t) = \frac{2}{T} \gamma(t) - \left(\frac{4}{T}\right) \gamma(t - T/2) + \frac{2}{T} \gamma(t - T)$$

(5)

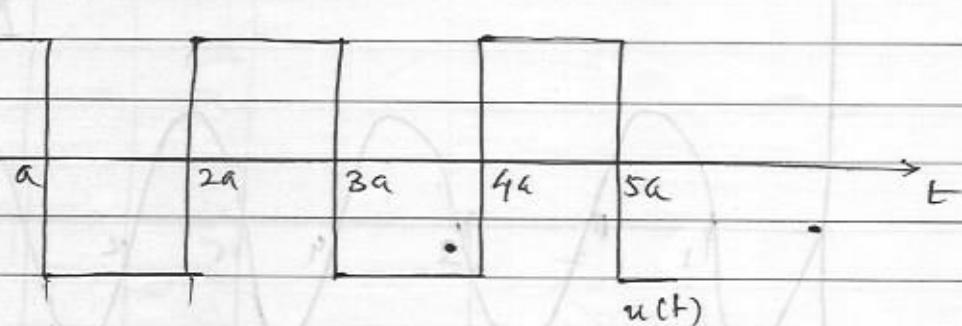


$$-2u(t-a)$$

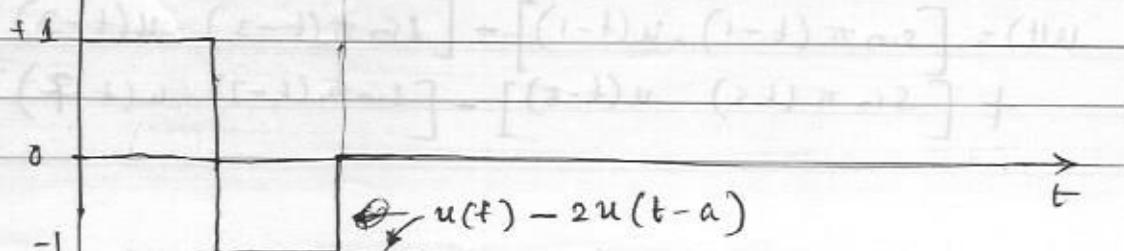

$$v(t) = u(t) - 2u(t-a) + 2u(t-2a) - 2u(t-3a) + 2u(t+3a)$$

48

DATE

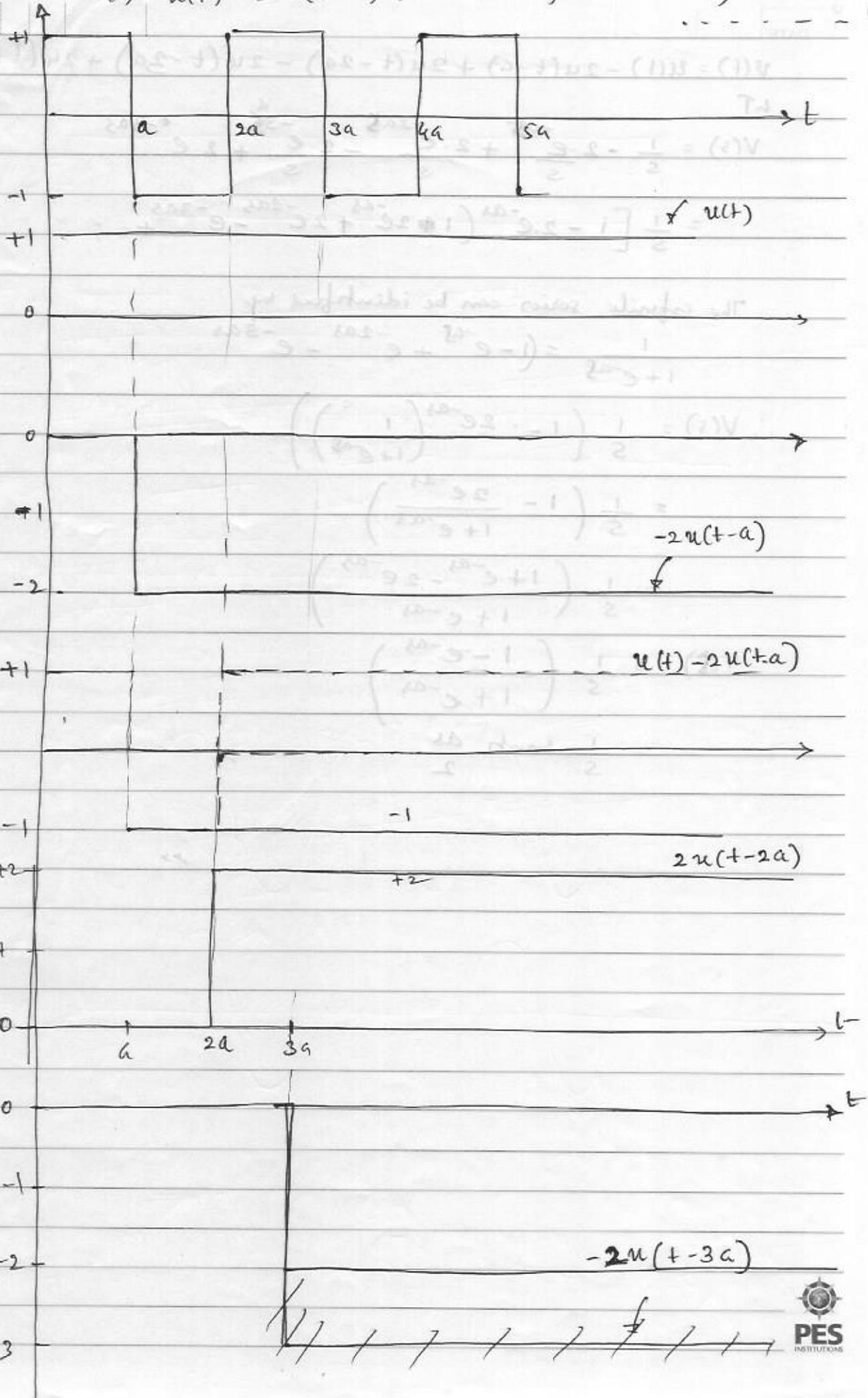

DATE

$$v(t) = u(t) - 2u(t-a) + 2u(t-2a) - 2u(t-3a) + 2u(t)$$

WT

$$V(s) = \frac{1}{s} - 2 \cdot \frac{e^{-as}}{s} + 2 \cdot \frac{e^{-2as}}{s} - 2 \cdot \frac{e^{-3as}}{s} + 2 \cdot e^{-3as}$$

$$= \frac{1}{s} \left[1 - 2e^{-as} (1 - 2e^{-as} + 2e^{-2as} - e^{-3as} + \dots) \right]$$

The infinite series can be identified by

$$\frac{1}{1+e^{-as}} = (1 - e^{-as} + e^{-2as} - e^{-3as} \dots)$$

$$\therefore V(s) = \frac{1}{s} \left(1 - 2e^{-as} \left(\frac{1}{1+e^{-as}} \right) \right)$$

$$= \frac{1}{s} \left(1 - \frac{2e^{-as}}{1+e^{-as}} \right)$$

$$= \frac{1}{s} \left(\frac{1+e^{-as}-2e^{-as}}{1+e^{-as}} \right)$$

$$V(s) = \frac{1}{s} \left(\frac{1-e^{-as}}{1+e^{-as}} \right)$$

$$= \frac{1}{s} \tanh \frac{as}{2}$$

(as-t) use