
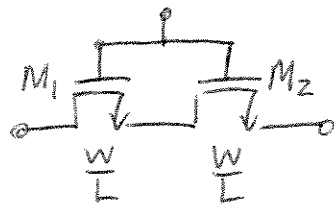



1.

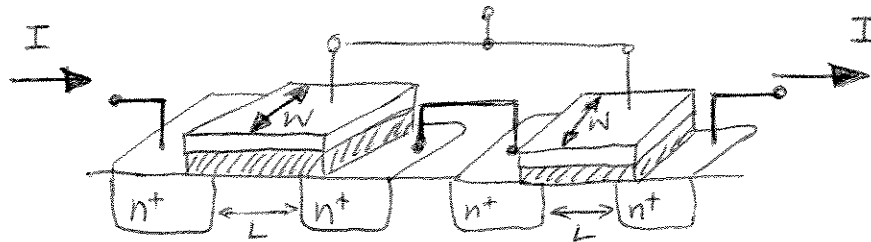

Intuitively, this is similar to having twice of the original channel length:



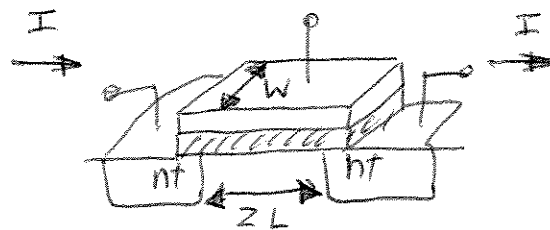
Since current flowing into either non-gate terminals must come out at the other terminal (KCL) and the intermediate node is equipotential, this is as if we have a  $M_{eq}$  with width  $W$  & length  $2L$ :



This approximation can simplify a lot of calculations.

2. A key point to remember: the charge density APPROACHES zero (not EQUALS) at pinch-off. In other words,  $Q$  is never exactly equal to zero (albeit very close.) Another way to view this phenomenon is by observing  $I = Q \cdot v$ : recognize that  $v$  is finite. Since we get some finite value of  $I$  at pinch-off, we expect  $Q \neq 0$ .

Consider the following:

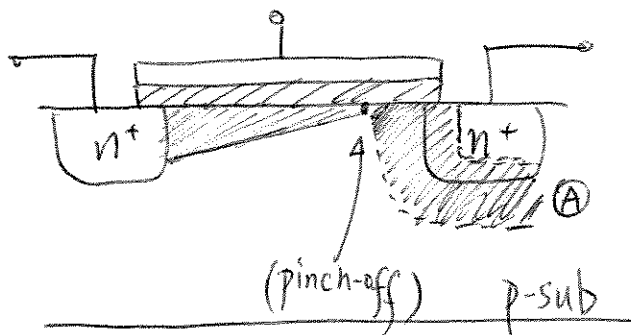

The shaded region, (A), represents a reverse-biased pn junction. Just as a diode, there exist minority

profiles on p & n sides, which  $\neq 0$ .

Pinch-off implies that the depletion region created no longer has free carriers. The depletion still sweeps all electrons from inversion channel to drain.

3. Given :  $C_{ox} = 10 \text{ fF}/\mu\text{m}^2$      $W = 5 \mu\text{m}$      $L = 0.1 \mu\text{m}$   
 $V_{GS} - V_{TH} = 1 \text{ V}$      $V_{DS} = 0$


Find : total charge stored in channel,  $Q_{tot}$

$$Q_{tot} = W C_{ox} (V_{GS} - V_{TH}) L$$

$$= (5 \mu\text{m})(10 \text{ fF}/\mu\text{m}^2)(1 \text{ V})(0.1 \mu\text{m}) = 5 \text{ fC}$$

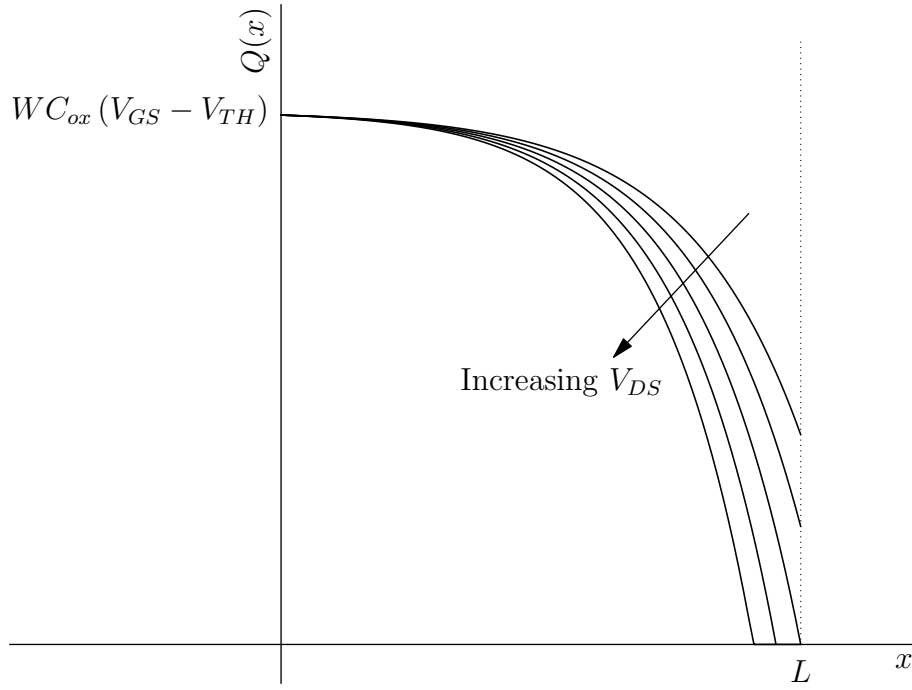6.4 (a)


$$\begin{aligned} Q(x) &= WC_{ox} (V_{GS} - V(x) - V_{TH}) \\ &= WC_{ox} (V_{GS} - V_{TH}) - WC_{ox} V(x) \end{aligned}$$



The curve that intersects the axis at  $x = L$  (i.e., the curve for which the channel begins to pinch off) corresponds to  $V_{DS} = V_{GS} - V_{TH}$ .

(b)
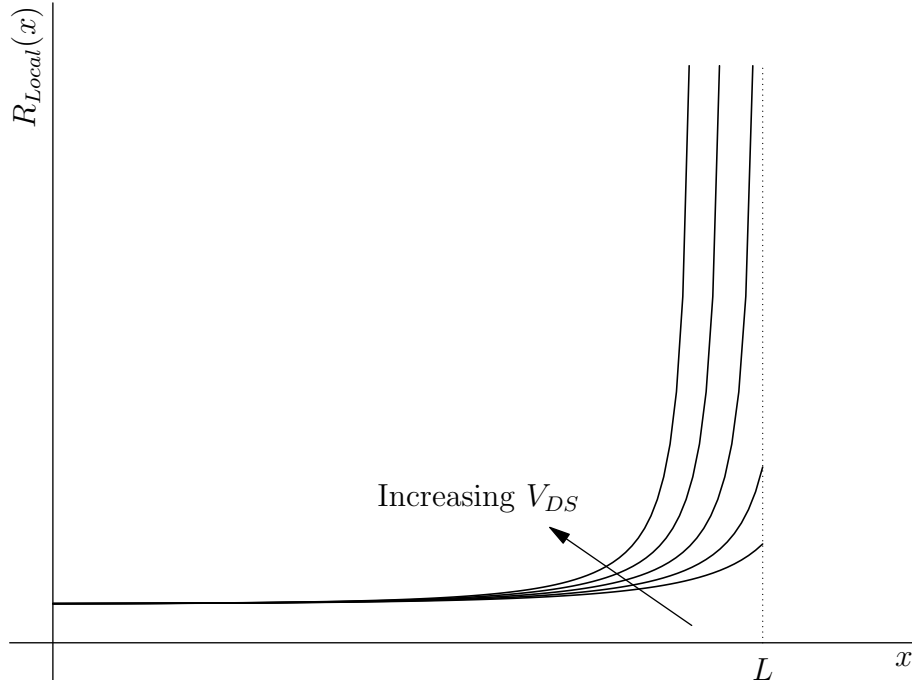
$$R_{Local}(x) \propto \frac{1}{\mu Q(x)}$$



Note that  $R_{Local}$  diverges at  $x = L$  when  $V_{DS} = V_{GS} - V_{TH}$ .

$$5. \quad I_D = W C_{ox} [V_{GS} - V(x) - V_{TH}] \mu_n \frac{dV(x)}{dx}$$

$$\text{Define : } A = \frac{I_D}{W C_{ox} \mu_n}, \quad B = V_{GS} - V_{TH}$$

$$\Rightarrow A = (B - V) \frac{dV}{dx} = \frac{d}{dx} \left( BV - \frac{V^2}{2} \right)$$

Integrating  $A = \frac{d}{dx} (BV - V^2/2)$  gives:

$$Ax = BV - V^2/2 \Rightarrow V^2 - 2BV + 2Ax = 0$$


Using quadratic formula:

$$\begin{aligned} V_{+,-} &= \frac{2B \pm \sqrt{4B^2 - 4 \cdot 2A}}{2} = B \pm \sqrt{B^2 - 2Ax} \\ &= B \left( 1 \pm \sqrt{1 - 2 \left( \frac{A}{B^2} \right) x} \right) \end{aligned}$$

$$= (V_{GS} - V_{TH}) \left\{ 1 \pm \sqrt{1 - \left[ 2 \cdot \frac{I_D}{W C_{ox} \mu_n (V_{GS} - V_{TH})^2} \right] x} \right\}$$


We know that  $0 \leq V(x) \leq V_{GS} - V_{TH}$  (pinch-off),  
and the term inside the square root is  $> 0$ .  
Therefore, we take  $V_-$  as the solution.

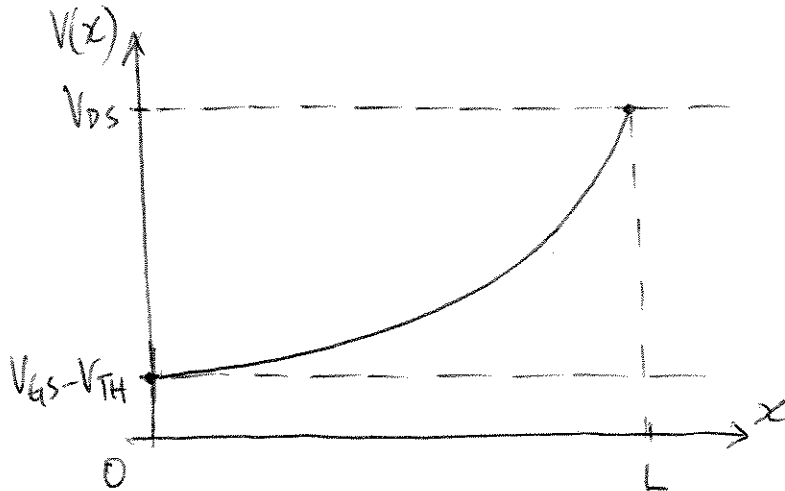i.e.  $V(x) = (V_{GS} - V_{TH}) \left\{ 1 - \sqrt{1 - \left[ \frac{2I_D}{WCox\mu_n(V_{GS} - V_{TH})^2} \right] x} \right\}$



$\because I_D \propto W$   
 $\Rightarrow V(x)$  is  
 independent  
 of  $W$ .
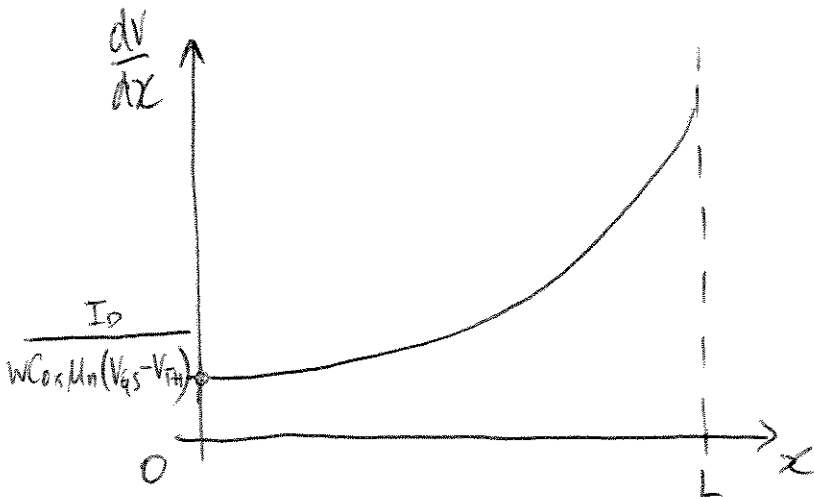
$$\frac{dV}{dx} = \frac{I_D}{WCox\mu_n(V_{GS} - V_{TH})} \cdot \left[ 1 - \frac{2I_D \cdot x}{WCox\mu_n(V_{GS} - V_{TH})^2} \right]^{-\frac{1}{2}}$$



6. No.

By varying  $V_{GS} - V_{TH}$  &  $V_{DS}$ , we can only obtain  $\mu_{nCox} \frac{W}{L}$ , but not  $\mu_{nCox}$  &  $\frac{W}{L}$

individually.



7. Given : NMOS  $I_D = 1 \text{ mA}$   $V_{GS} - V_{TH} = 0.6 \text{ V}$   
 $I_D = 1.6 \text{ mA}$   $V_{GS} - V_{TH} = 0.8 \text{ V}$   
(triode region)  $\mu_n C_{ox} = 200 \frac{\mu\text{A}}{\text{V}^2}$

Find  $V_{DS}$  &  $W/L$ .

$$1 \text{ mA} = \mu_n C_{ox} \frac{W}{L} \left[ (0.6) V_{DS} - V_{DS}^2/2 \right] \quad \text{--- ①}$$

$$1.6 \text{ mA} = \mu_n C_{ox} \frac{W}{L} \left[ (0.8) V_{DS} - V_{DS}^2/2 \right] \quad \text{--- ②}$$

$$\text{②} \div \text{①} : 1.6 = \frac{0.8 V_{DS} - V_{DS}^2/2}{0.6 V_{DS} - V_{DS}^2/2} = \frac{1.6 - V_{DS}}{1.2 - V_{DS}}$$

$$\Rightarrow V_{DS} = \frac{1.6(0.2)}{0.6} \approx 0.533 \text{ V}$$

$$\begin{aligned} \Rightarrow \frac{W}{L} &= \frac{I_D}{\mu_n C_{ox} [(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2/2]} \\ &= \frac{1 \text{ mA}}{200 \frac{\mu\text{A}}{\text{V}^2} [(0.6 \text{ V})(0.533 \text{ V}) - (0.533 \text{ V})^2/2]} \\ &\approx 28. \end{aligned}$$

$$8. \quad I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2]$$

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = \frac{1}{2} \mu C_{ox} \frac{W}{L} \cdot 2 V_{DS} = \mu C_{ox} \frac{W}{L} V_{DS}$$

$$g_m|_{V_{DS}=0} = 0.$$

Intuitively, when  $V_{GS} > V_{TH}$ , mobile charges (channel) become available. This determines the on-resistance. But since there is no  $I_D$  ( $\because V_{DS}=0$ ), it does not matter if there is an incremental change in  $V_{GS}$  (i.e.  $\partial V_{GS}$ ). Since varying  $V_{GS}$  gives no change in  $I_D$ ,  $g_m|_{V_{DS}=0} = 0$ .

9. Given:  $V_{DD} = 1.8 \text{ V}$        $\frac{W}{L} = 20$        $\mu_n C_{ox} = 200 \frac{\mu A}{V^2}$   
 $V_{TH} = 0.4 \text{ V}$

Find minimum-on resistance.

$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})}$$
$$= \frac{1}{\left(200 \frac{\mu A}{V^2}\right)(20)(1.8 - 0.4)V} = 179. \Omega$$

$$10. \quad 500 = \frac{1}{\mu_n C_{ox} \frac{W}{L} (1 - V_{TH})}$$

$$400 = \frac{1}{\mu_n C_{ox} \frac{W}{L} (1.5 - V_{TH})}$$

For the same NMOS,  $\mu_n C_{ox}$  &  $\frac{W}{L}$  are fixed

$$\Rightarrow 500(1 - V_{TH}) \stackrel{?}{=} 400(1.5 - V_{TH})$$

$$500(0.6) \neq 400(1.1)$$

$\therefore$  This is not possible.

$$11. \quad I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$r_{DS, tri} \triangleq \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \left[ \frac{\partial}{\partial V_{DS}} \left\{ \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] \right\} \right]^{-1}$$

$$= \left[ \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) - \mu C_{ox} \frac{W}{L} V_{DS} \right]^{-1}$$

$$= \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH} - V_{DS})}$$

12. When MOS operates as a resistor,


$$R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$

$$\Rightarrow \tau = R_{on} C_{GS} = \frac{WL C_{ox}}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})} = \frac{L^2}{\mu (V_{GS} - V_{TH})}$$

To minimize the time constant,

- 1) use minimum channel length, and
- 2) maximize overdrive voltage.


13.

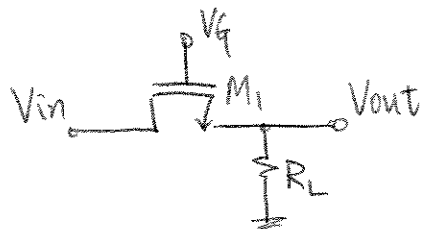

Given  $V_{in} \approx 0$   
 $V_G = 1.8 \text{ V}$   
 $R_L = 100 \Omega$

Find  $\frac{W}{L}$  such that signal output attenuates by only 5%.

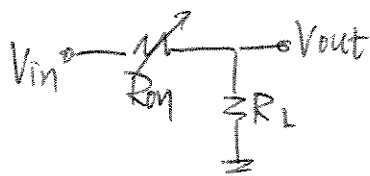
$V_{in} \approx 0$  implies that we can approximate  $M_1$  as a linear resistance controlled by  $V_G$ . Therefore, the equivalent circuit becomes a resistive divider:



$$\begin{aligned} V_{out} &= 0.95 V_{in} \\ &= \frac{R_L}{R_{on} + R_L} V_{in} \\ \Rightarrow R_{on} &\approx 5.3 \Omega \end{aligned}$$

$$\begin{aligned} \therefore \frac{W}{L} &= \frac{1}{\mu C_{ox} (V_{GS} - V_{TH}) R_{on}} \approx \frac{1}{\frac{200 \mu A}{V^2} (1.8 - 0.4)(5.352)} \\ &= 674. \end{aligned}$$

14.

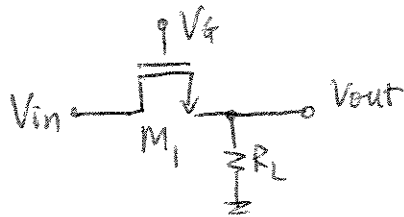

$V_0 \sim \text{few mV.}$

$$(a) \quad V_{in} = V_0 \cos \omega t \quad V_{out} = 0.95 (V_0 \cos \omega t)$$

$$V_{out} = \frac{R_L}{R_{on} + R_L} V_{in} \Rightarrow \frac{R_L}{R_{on} + R_L} = 0.95 V_0$$

$$R_{on} = \frac{R_L}{\left( \frac{0.95 V_0}{1 - 0.95 V_0} \right)} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_g - V_{TH})}$$

$$\therefore \frac{W}{L} = \frac{0.95 V_0 / (1 - 0.95 V_0)}{\mu_n C_{ox} R_L (V_g - V_{TH})}$$


$$(b) \quad V_{out} = 0.95 V_{in} = 0.95 (V_0 \cos \omega t + 0.5) \\ \approx 0.95 \times 0.5 = 0.475 \\ (\because V_0 \text{ is relatively small})$$

$$\therefore R_{on} = \frac{R_L}{0.9} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_g - V_{TH})}$$

$$\Rightarrow \frac{W}{L} = \frac{0.9}{\mu_n C_{ox} R_L (V_g - V_{TH})}$$



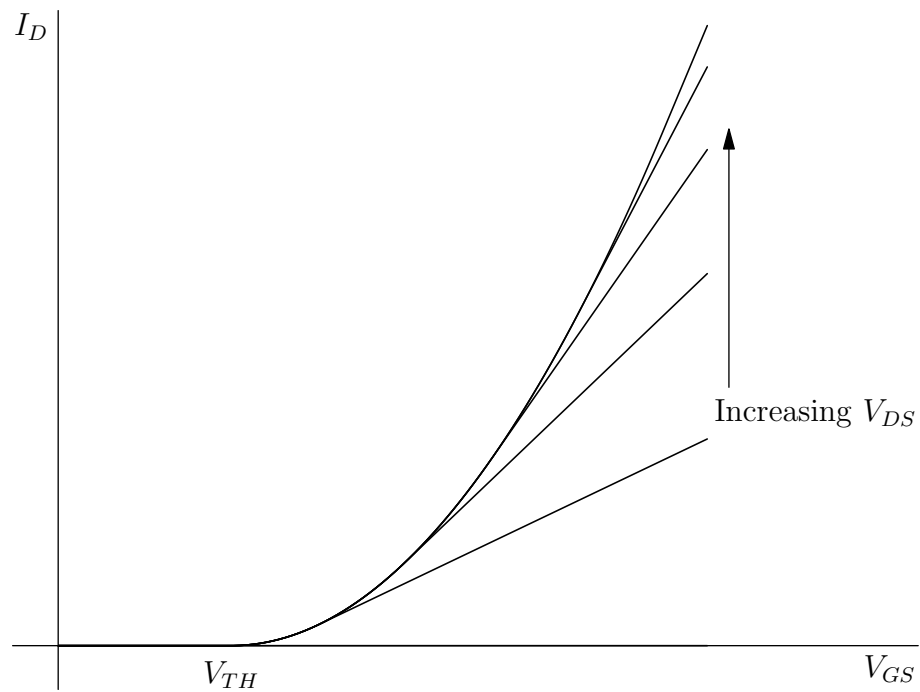Results show that if there is no DC voltage as input, the  $R_{on}$  varies with changing sinewave. With a DC bias voltage,  $R_{on}$  becomes more stable (independent of  $V_o$ ).



Initially, when  $V_{GS}$  is small, the transistor is in cutoff and no current flows. Once  $V_{GS}$  increases beyond  $V_{TH}$ , the curves start following the square-law characteristic as the transistor enters saturation. However, once  $V_{GS}$  increases past  $V_{DS} + V_{TH}$  (i.e., when  $V_{DS} < V_{GS} - V_{TH}$ ), the transistor goes into triode and the curves become linear. As we increase  $V_{DS}$ , the transistor stays in saturation up to larger values of  $V_{GS}$ , as expected.

16. The peak of the parabola signifies pinch-off (i.e.  $V_{DS} = V_{GS} - V_{TH}$ ). This means that (with  $\lambda = 0$ )  $I_D$  cannot be increased further by increasing  $V_{DS}$ . Since this curve must be continuous, the peak  $I_D$  must originate from the peak of the parabola.

6.17

$$\begin{aligned}
 I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^\alpha, \quad \alpha < 2 \\
 g_m &\triangleq \frac{\partial I_D}{\partial V_{GS}} \\
 &= \frac{\alpha}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^{\alpha-1} \\
 &= \boxed{\frac{\alpha I_D}{V_{GS} - V_{TH}}}
 \end{aligned}$$

$$18. \quad I_D = W C_{ox} (V_{GS} - V_{TH}) V_{SAT}$$

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = W C_{ox} V_{SAT}$$

19. (a) OFF  $\because V_{GS} = 0$

(b) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH}$  &  
 $V_{DS} \ll 2(V_{GS} - V_{TH})$

(d) TRIODE  $\because V_{GS} > V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$   
(REMEMBER: MOSFET is symmetric)

(e) TRIODE  $\because V_{GS} > V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$

(f) OFF  $\because V_{GS} = 0$

(g) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(h) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(i) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

20. (a) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )

(b) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )

(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH}$  &  
 $V_{DS} \ll 2(V_{GS} - V_{TH})$


(d) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

- 6.21 Since they're being used as current sources, assume  $M_1$  and  $M_2$  are in saturation for this problem. To find the maximum allowable value of  $\lambda$ , we should evaluate  $\lambda$  when  $0.99I_{D2} = I_{D1}$  and  $1.01I_{D2} = I_{D1}$ , i.e., at the limits of the allowable values for the currents. However, note that for any valid  $\lambda$  (remember,  $\lambda$  should be non-negative), we know that  $I_{D2} > I_{D1}$  (since  $V_{DS2} > V_{DS1}$ ), so the case where  $1.01I_{D2} = I_{D1}$  (which implies  $I_{D2} < I_{D1}$ ) will produce an invalid value for  $\lambda$  (you can check this yourself). Thus, we need only consider the case when  $0.99I_{D2} = I_{D1}$ .

$$\begin{aligned}
 0.99I_{D2} &= 0.99 \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda V_{DS2}) \\
 &= I_{D1} \\
 &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda V_{DS1}) \\
 0.99(1 + \lambda V_{DS2}) &= 1 + \lambda V_{DS1} \\
 \lambda &= \boxed{0.02 \text{ V}^{-1}}
 \end{aligned}$$



22.

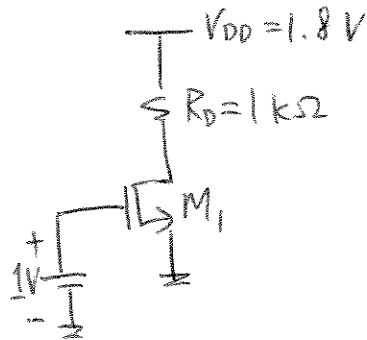

$$\lambda = 0, V_{TH} = 0.4 \text{ V}$$

$$\mu_n C_{ox} = 200 \frac{\mu\text{A}}{\text{V}^2}$$

$M_1$  sits at the edge of saturation when  $V_{DS} = V_{GS} - V_{TH}$ .

$$\Rightarrow V_{DS, \text{edge}} = (1 - 0.4) \text{ V} = 0.6 \text{ V}$$

$$\text{By KCL, } I_{D1} = I_{RD} = \frac{V_{DD} - V_{DS}}{R_D} = \frac{1.2 \text{ V}}{1 \text{ k}\Omega} = 1.2 \text{ mA}$$

$$\therefore I_{D1} = 1.2 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\Rightarrow \frac{W}{L} = \frac{2 I_{D1}}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = \frac{2 (1.2 \text{ mA})}{\left(200 \frac{\mu\text{A}}{\text{V}^2}\right) (1 - 0.4)^2 \text{ V}^2}$$

$$\approx 33.$$

23. If gate oxide thickness,  $t_{ox}$ , doubles, the corresponding capacitance,  $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$ , is halved.

$\Rightarrow \mu_n C_{ox}$  is also halved


$\Rightarrow I_{D1}$  is halved  $\Rightarrow V_{DS}$  increases

$\Rightarrow M_1$  stays in saturation ( $V_{DS} > V_{GS} - V_{TH}$ )

$$I_{D1} = \frac{1.2 \text{ mA}}{2} = 0.6 \text{ mA}$$

$$\Rightarrow V_{DS} = (1.8 \text{ V}) - (0.6 \text{ mA})(1 \text{ k}\Omega) = 1.2 \text{ V}$$

24.

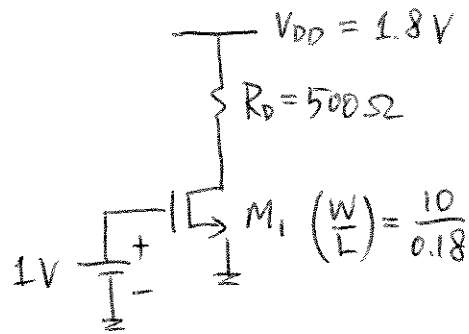

$$\lambda = 0$$

To avoid triode region,  $V_{DS} \geq V_{GS} - V_{TH}$ .

$$\Rightarrow V_{DS} \geq 1 - 0.4 = 0.6V$$


$$\begin{aligned} \Rightarrow I_{D1} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= \frac{1}{2} \left( 200 \frac{\mu A}{V^2} \right) \left( \frac{10}{0.18} \right) (0.6)^2 = 2mA \end{aligned}$$

$$\text{By KCL, } \frac{V_{DD} - V_{DS}}{R_D} = 2mA$$

$$\therefore V_{DD} = (2mA)(500\Omega) + 0.6V = 1.6V$$

$$\text{Minimum } V_{DD} = 1.6V$$

25.

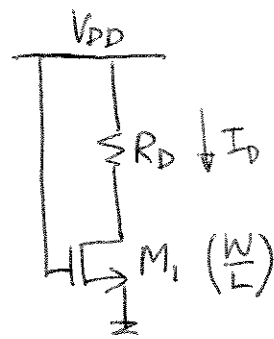


$$\lambda = 0$$

When  $M_1$  operates at the edge of saturation,  $V_{DS} = V_{GS} - V_{TH}$ . Also, by KCL:

$$I_{RD} = I_{D1} \Rightarrow \frac{V_{DD} - (V_{DD} - V_{TH})}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})^2$$

$$\therefore V_{TH} = R_D \cdot \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})^2}_{I_D}$$

2b.

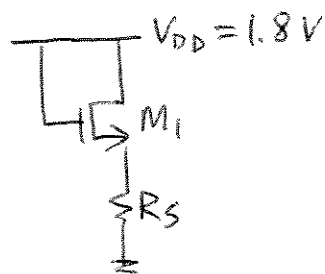

$$\lambda = 0$$

Find  $\left(\frac{W}{L}\right)$  with bias current  $= I_1$ .

Since  $V_{DS} = V_{GS}$  for  $M_1$ , this device always operates in saturation region (given  $V_{GS} > V_{TH}$ ).

By KCL,  $I_1 = I_{R_S}$ ; by Ohm's law,  $V_S = I_1 R_S$

$$\Rightarrow \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - I_1 R_S - V_{TH})^2 = I_1$$

$$\therefore \frac{W}{L} = \frac{2 I_1}{\mu_n C_{ox} (V_{DD} - I_1 R_S - V_{TH})^2}$$

$$\begin{aligned}
V_{DD} - I_D R_D &= V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\
\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}} &= (V_{DD} - V_{TH} - I_D R_D)^2 \\
I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[ (V_{DD} - V_{TH})^2 - 2I_D R_D (V_{DD} - V_{TH}) + I_D^2 R_D^2 \right]
\end{aligned}$$

We can rearrange this to the standard quadratic form as follows:



$$\left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D^2 \right) I_D^2 - \left( \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1 \right) I_D + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})^2 = 0$$

Applying the quadratic formula, we have:



$$\begin{aligned}
I_D &= \frac{(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1) \pm \sqrt{(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1)^2 - 4 \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) \right)^2}}{2 \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D^2 \right)} \\
&= \frac{\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1 \pm \sqrt{(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1)^2 - (\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}))^2}}{\mu_n C_{ox} \frac{W}{L} R_D^2} \\
&= \boxed{\frac{\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1 \pm \sqrt{1 + 2 \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH})}}{\mu_n C_{ox} \frac{W}{L} R_D^2}}
\end{aligned}$$

Note that mathematically, there are two possible solutions for  $I_D$ . However, since  $M_1$  is diode-connected, we know it will either be in saturation or cutoff. Thus, we must reject the value of  $I_D$  that does not match these conditions (for example, a negative value of  $I_D$  would not match cutoff or saturation, so it would be rejected in favor of a positive value).



28. (a)

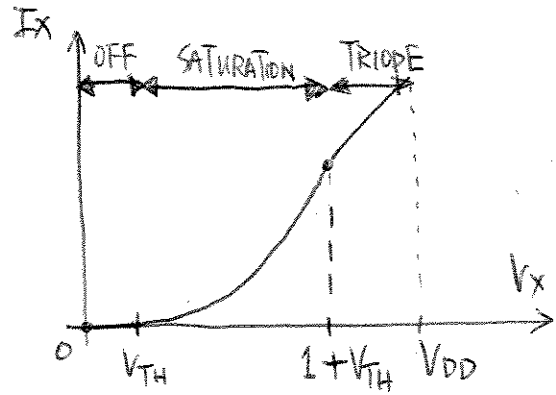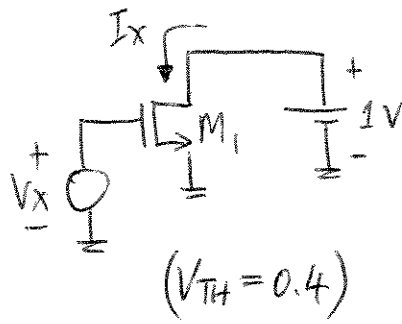



(b)

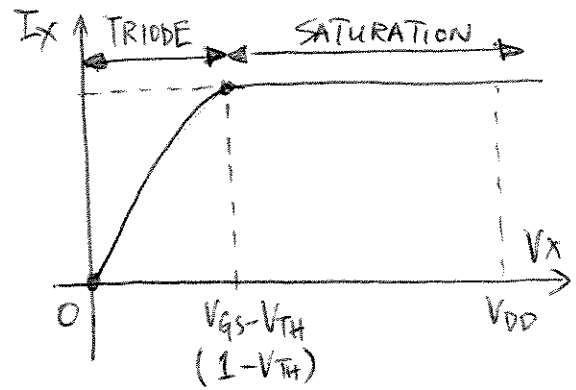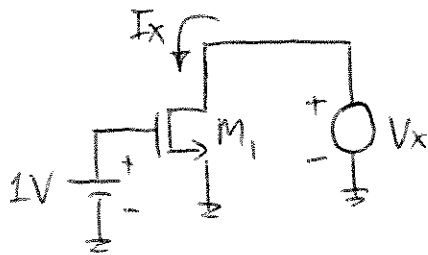


(c)

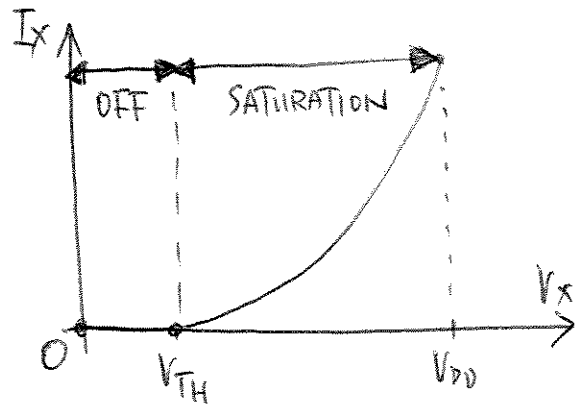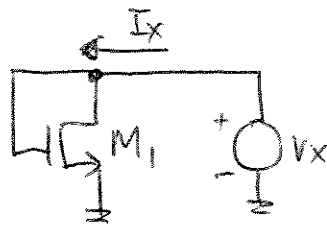

(d)

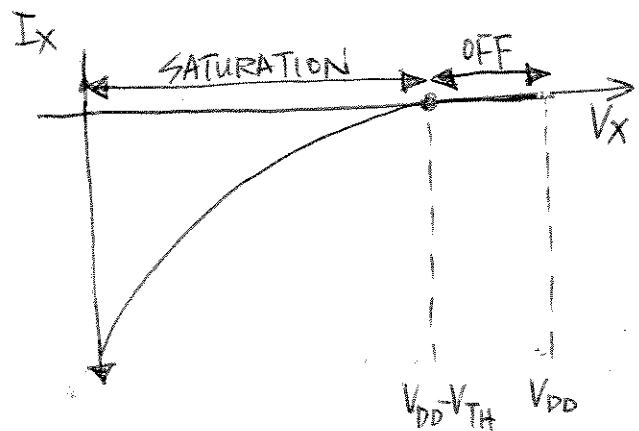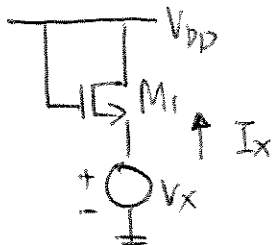

29.

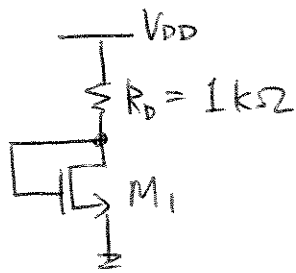

$$\left(\frac{W}{L}\right) = \frac{10}{0.18}, \quad \lambda = 0.1 \text{ V}^{-1}$$

Find  $I_D$ .

Since  $M_1$  is diode-connected, it operates in saturation.

$$\text{By KCL, } \frac{V_{DD} - V_G}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})^2 (1 + \lambda V_G)$$


One can solve this by (1) using a graphing calculator, (2) trial-and-error, (3) or iteratively finding  $V_G$ .

Using any method gives  $V_G \approx 0.807 \text{ V}$

$$\Rightarrow I_D = \frac{V_{DD} - V_G}{R_D} \approx 1 \text{ mA}$$



30.

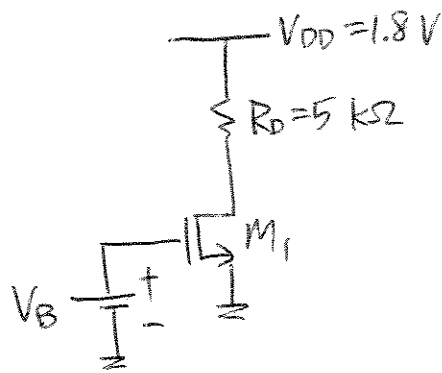

$$\frac{W}{L} = \frac{20}{0.18}, \quad \lambda = 0.1\text{ V}^{-1}$$

At the edge of saturation,

$$I_{D1} = \frac{V_{DD} - (V_B - V_{TH})}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda(V_B - V_{TH}))$$

This equation can be solved by using a graphing calculator, special programs, or iteratively.

Using any method gives  $V_B \approx 0.57\text{ V}$   
 $(I_D \approx 0.33\text{ mA})$

31. An NMOS device with  $\lambda = 0$  must provide a transconductance of  $\frac{1}{50} \frac{1}{\Omega}$ .

(a) Given  $I_D = 0.5 \text{ mA}$ , find  $W/L$ .

$$g_m = \frac{1}{50} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\Rightarrow \frac{W}{L} = \frac{g_m^2}{2 \mu_n C_{ox} I_D} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right)^2}{2 \left(\frac{200 \mu\text{A}}{\text{V}^2}\right) (0.5 \text{ mA})} \approx 2000$$

(b) Given  $V_{GS} - V_{TH} = 0.5 \text{ V}$ , find  $W/L$ .

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$\Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{GS} - V_{TH})} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right)}{\left(\frac{200 \mu\text{A}}{\text{V}^2}\right) (0.5 \text{ V})} \approx 200$$

(c) Given  $V_{GS} - V_{TH} = 0.5 \text{ V}$ , find  $I_D$ .

$$\Rightarrow I_D = \frac{g_m (V_{GS} - V_{TH})}{2} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right) (0.5 \text{ V})}{2} \approx 5 \text{ mA}$$

32. (a)  $g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$  ( $I_D$  constant)

Doubling ( $\frac{W}{L}$ ) implies a  $\sqrt{2}$  times increase in  $g_m$ :  $g_{m_{NEW}} = \sqrt{2\mu_n C_{ox} (2\frac{W}{L}) I_D} = \sqrt{2} g_m$ .

(b)  $g_m = \frac{2I_D}{V_{GS} - V_{TH}}$  ( $I_D$  constant)

Doubling ( $V_{GS} - V_{TH}$ ) decreases  $g_m$  by half:

$$g_{m_{NEW}} = \frac{2I_D}{2(V_{GS} - V_{TH})} = \frac{1}{2} g_m$$

(c)  $g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$  ( $\frac{W}{L}$  constant)

Doubling  $I_D$  increases  $g_m$  by  $\sqrt{2}$  times.

(d)  $g_m = \frac{2I_D}{V_{GS} - V_{TH}}$  ( $V_{GS} - V_{TH}$  constant)

Doubling  $I_D$  increases  $g_m$  by 2 times.

6.33 (a) Assume  $M_1$  is operating in saturation.

$$V_{GS} = 1 \text{ V}$$


$$V_{DS} = V_{DD} - I_D R_D = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) R_D$$

$$V_{DS} = 1.35 \text{ V} > V_{GS} - V_{TH}, \text{ which verifies our assumption}$$

$$I_D = 4.54 \text{ mA}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \boxed{13.333 \text{ mS}}$$
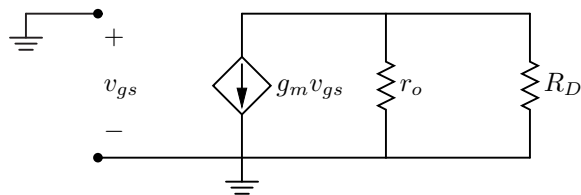
$$r_o = \frac{1}{\lambda I_D} = \boxed{2.203 \text{ k}\Omega}$$



(b) Since  $M_1$  is diode-connected, we know it is operating in saturation.


$$V_{GS} = V_{DS} = V_{DD} - I_D R_D = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS}) R_D$$

$$V_{GS} = V_{DS} = 0.546 \text{ V}$$

$$I_D = 251 \text{ }\mu\text{A}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \boxed{3.251 \text{ mS}}$$
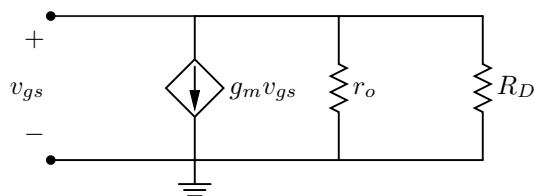
$$r_o = \frac{1}{\lambda I_D} = \boxed{39.881 \text{ k}\Omega}$$




(c) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$I_D = 1 \text{ mA}$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \boxed{6.667 \text{ mS}}$$
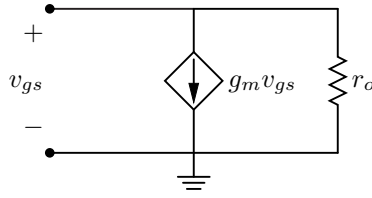
$$r_o = \frac{1}{\lambda I_D} = \boxed{10 \text{ k}\Omega}$$



(d) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$V_{GS} = V_{DS}$$


$$V_{DD} - V_{GS} = I_D(2 \text{ k}\Omega) = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS}) (2 \text{ k}\Omega)$$

$$V_{GS} = V_{DS} = 0.623 \text{ V}$$

$$I_D = 588 \text{ }\mu\text{A}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \boxed{4.961 \text{ mS}}$$
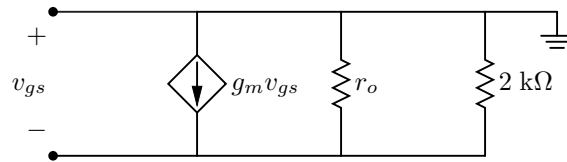
$$r_o = \frac{1}{\lambda I_D} = \boxed{16.996 \text{ k}\Omega}$$




(e) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$I_D = 0.5 \text{ mA}$$


$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \boxed{4.714 \text{ mS}}$$
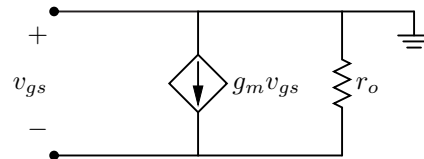
$$r_o = \frac{1}{\lambda I_D} = \boxed{20 \text{ k}\Omega}$$



$$34. \quad g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D} \quad r_o = \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \frac{1}{\lambda I_D}$$


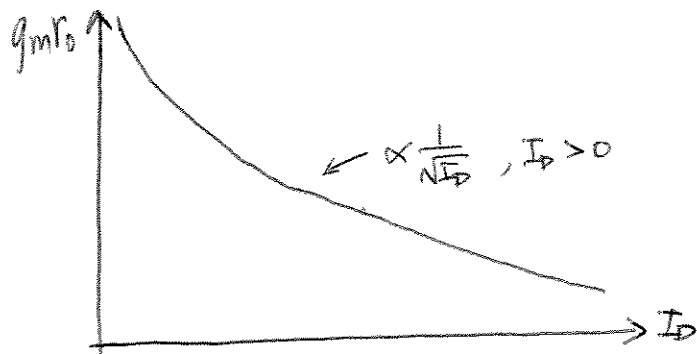
$$g_m r_o = \frac{\sqrt{2\mu C_{ox} \left( \frac{W}{L} \right) I_D}}{\lambda I_D} = \frac{1}{\lambda} \sqrt{\frac{2\mu C_{ox} \left( \frac{W}{L} \right)}{I_D}}$$



35 (a)  $g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$

$$r_o = \frac{1}{\lambda I_D}$$
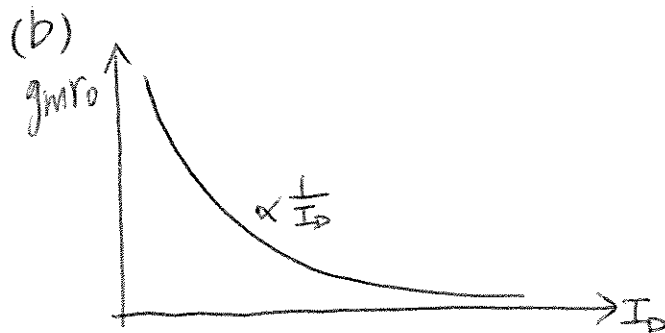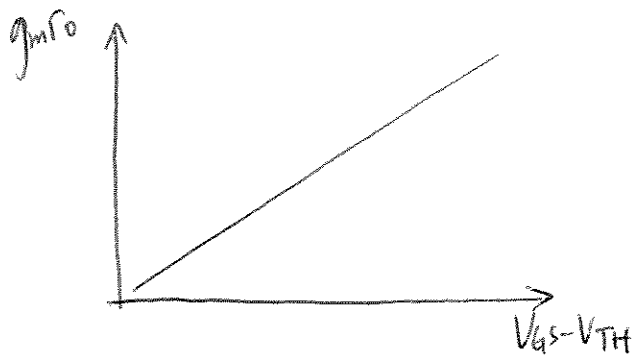
$$g_m r_o = \frac{\mu C_{ox} (W/L) (V_{GS} - V_{TH})}{\lambda I_D}$$



3b. Given NMOS with  $\lambda = 0.1 \text{ V}^{-1}$   $g_m r_o = 20$   
 $V_{DS} = 1.5 \text{ V}$   
 determine  $W/L$  if  $I_D = 0.5 \text{ mA}$ .

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} = 20 \text{ k}\Omega$$


$$\Rightarrow g_m = \frac{20}{20 \text{ k}\Omega} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\therefore \frac{W}{L} = \left( \frac{20}{20 \text{ k}\Omega} \right)^2 \frac{1}{2 \mu_n C_{ox} I_D}$$

$$= \left( \frac{1}{1 \text{ k}\Omega} \right)^2 \frac{1}{2 \left( 200 \frac{\mu\text{A}}{\text{V}^2} \right) (0.5 \text{ mA})} \approx 5.$$



37.

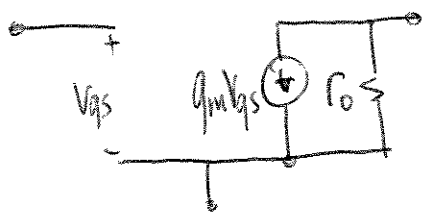

Given  $\lambda = 0.2 \text{ V}^{-1}$

$$g_m r_o = 20$$

$$V_{DS} = 1.5 \text{ V}$$

$$I_D = 0.5 \text{ mA}$$


Calculate  $\frac{W}{L}$ .

$$g_m = \frac{20}{r_o} = 20 \cdot \lambda I_D = 20 (0.2 \text{ V}^{-1}) (0.5 \text{ mA}) = 0.002 \text{ } \Omega^{-1}$$


$$\Rightarrow g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\therefore \frac{W}{L} = \frac{g_m^2}{2 \mu_n C_{ox} I_D} = \frac{(0.002 \text{ } \Omega^{-1})^2}{2 \left( \frac{200 \mu\text{A}}{\text{V}^2} \right) (0.5 \text{ mA})} = 20$$


6.38 (a)

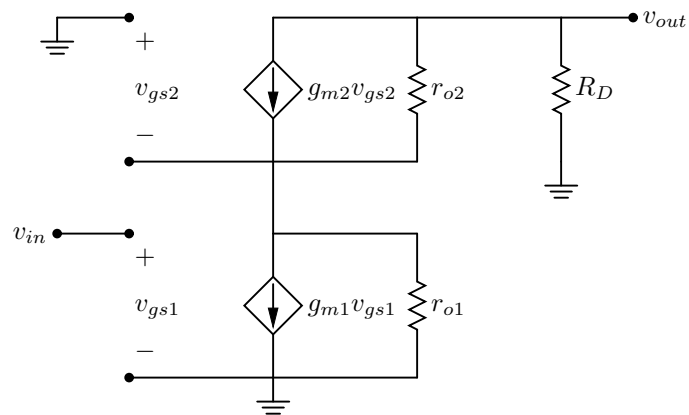


(b)

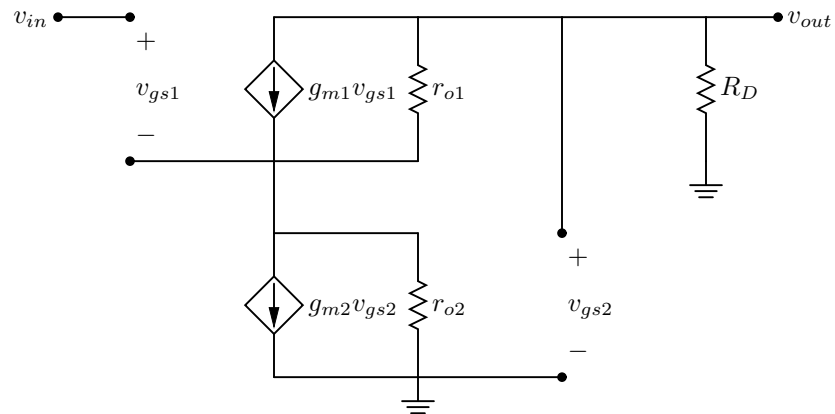


(c)

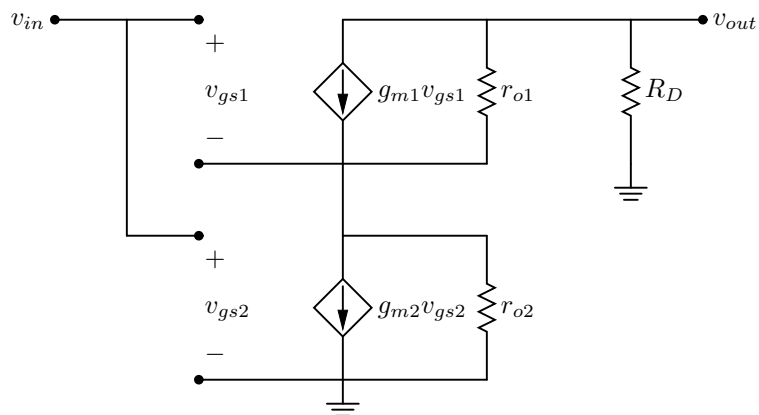

(d)

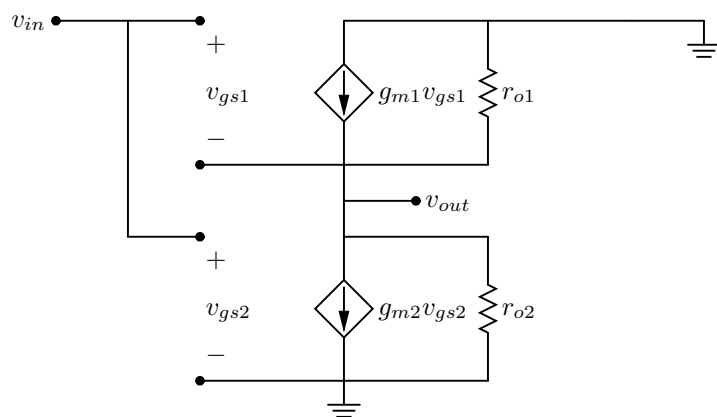

(e)

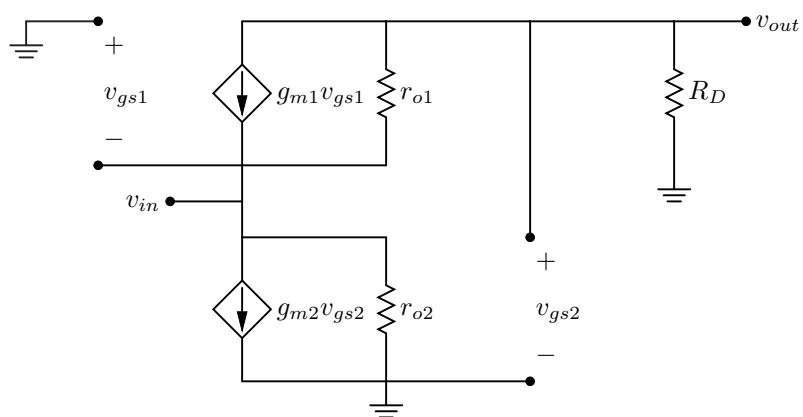

39. (a) OFF  $\because |V_{SG}| = 0$

(b) OFF  $\because |V_{SG}| < |V_{TH}| = 0.4V$

(c) SATURATION  $\because |V_{SD}| > |V_{SG}| - |V_{TH}|$

(d) OFF  $\because V_{SG} < |V_{TH}|$


40. (a) SATURATION  $\because V_{SD} > V_{SG} - |V_{TH}|$

(b) LINEAR (RESISTIVE)  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} \ll 2(V_{SG} - |V_{TH}|)$

(c) (EDGE OF) SATURATION  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} = V_{SG} - |V_{TH}|$

(d) TRIODE  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} < V_{SG} - |V_{TH}|$

41.

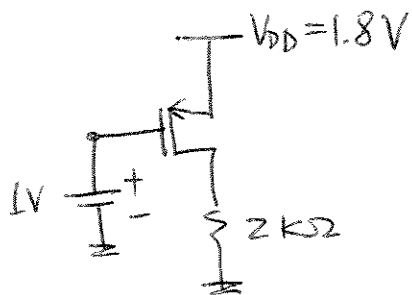

$$\lambda = 0$$

At the edge of saturation,  $V_{SD} = V_{SG} - |V_{TH}|$   
 $\Rightarrow V_D = 1.4 \text{ V.}$


By KCL,  $I_{D1} = I_R$

$$\Rightarrow \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2 = \frac{V_D}{2 \text{ k}\Omega}$$

$$\therefore \frac{W}{L} = \frac{V_D}{2 \text{ k}\Omega} \cdot \frac{2}{\mu_p C_{ox} (V_{SG} - |V_{TH}|)^2}$$

$$= \frac{1.4 \text{ V}}{2 \text{ k}\Omega} \cdot \frac{2}{100 \frac{\mu\text{A}}{\text{V}^2} (0.8 \text{ V} - 0.4 \text{ V})^2} \approx 87.5$$

42.

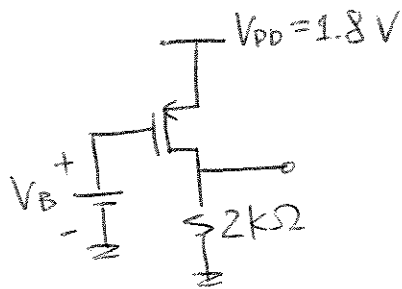

$$\lambda = 0$$

When  $V_B = 1V$ ,  $W/L = 87.5$

When  $V_B = 0.8V$ ,

$$\begin{aligned} I_D &= \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2 \\ &= \frac{1}{2} \left( \frac{100 \mu A}{V^2} \right) (87.5) (1 - 0.4)^2 V^2 \approx 16 mA \end{aligned}$$

$\Rightarrow V_D = I_D (2k\Omega) \approx 3.2V$ , which exceeds the supply voltage!

$\therefore$  PMOS goes into triode:  
( $\because I_D$  is too large)

By KCL,

$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} [(V_{SG} - |V_{TH}|) \cdot 2V_{SD} - V_{SD}^2] = (V_{DD} - V_{SD}) / 2k\Omega$$

Solving this equation numerically (or trial-and-error) gives  $V_{SD} \approx 0.18 \text{ V}$

$$\Rightarrow I_D = \frac{V_{DD} - V_{SD}}{2 \text{ k}\Omega} = \frac{(1.8 - 0.18) \text{ V}}{2 \text{ k}\Omega} \approx 0.81 \text{ mA}$$



6.43 (a) Assume  $M_1$  is operating in triode (since  $|V_{GS}| = 1.8 \text{ V}$  is large).

$$|V_{GS}| = \boxed{1.8 \text{ V}}$$

$$V_{DD} - |V_{DS}| = |I_D| (500 \Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} \left[ 2(|V_{GS}| - |V_{TH}|) |V_{DS}| - |V_{DS}|^2 \right] (500 \Omega)$$

$$|V_{DS}| = \boxed{0.418 \text{ V}} < |V_{GS}| - |V_{TH}|, \text{ which verifies our assumption}$$

$$|I_D| = \boxed{2.764 \text{ mA}}$$

(b) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$|V_{GS}| = |V_{DS}|$$

$$V_{DD} - |V_{GS}| = |I_D| (1 \text{ k}\Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 \text{ k}\Omega)$$

$$|V_{GS}| = |V_{DS}| = \boxed{0.952 \text{ V}}$$

$$|I_D| = \boxed{848 \text{ }\mu\text{A}}$$

(c) Since  $M_1$  is diode-connected, we know it is operating in saturation.


$$|V_{GS}| = |V_{DS}|$$

$$|V_{GS}| = V_{DD} - |I_D| (1 \text{ k}\Omega) = V_{DD} - |I_D| (1 \text{ k}\Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 \text{ k}\Omega)$$

$$|V_{GS}| = |V_{GS}| = \boxed{0.952 \text{ V}}$$


$$|I_D| = \boxed{848 \text{ }\mu\text{A}}$$

6.44 (a)

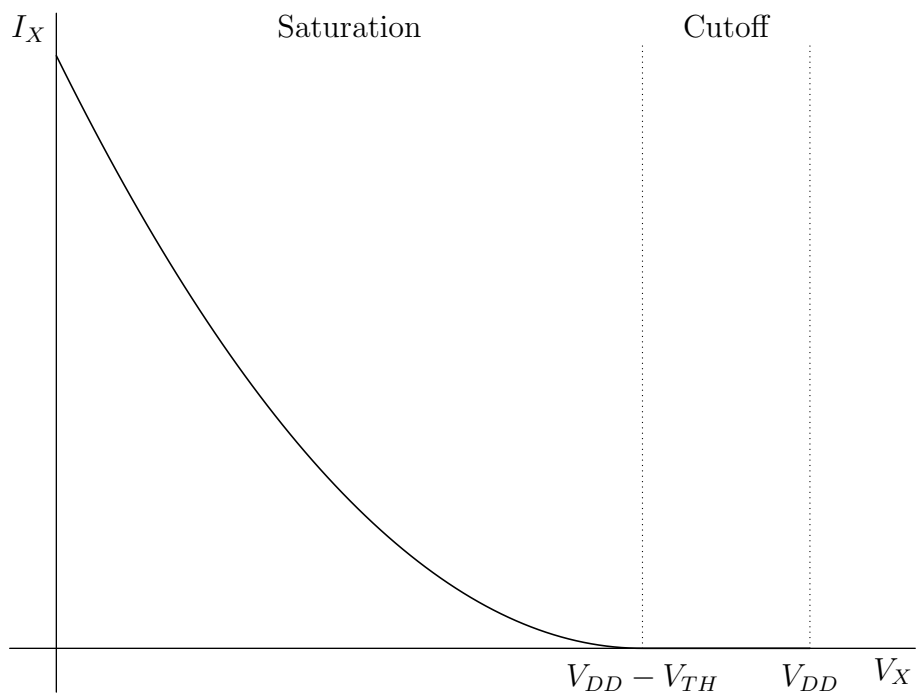


$M_1$  goes from saturation to cutoff when  $V_X = V_{DD} - V_{TH} = 1.4$  V.

(b)

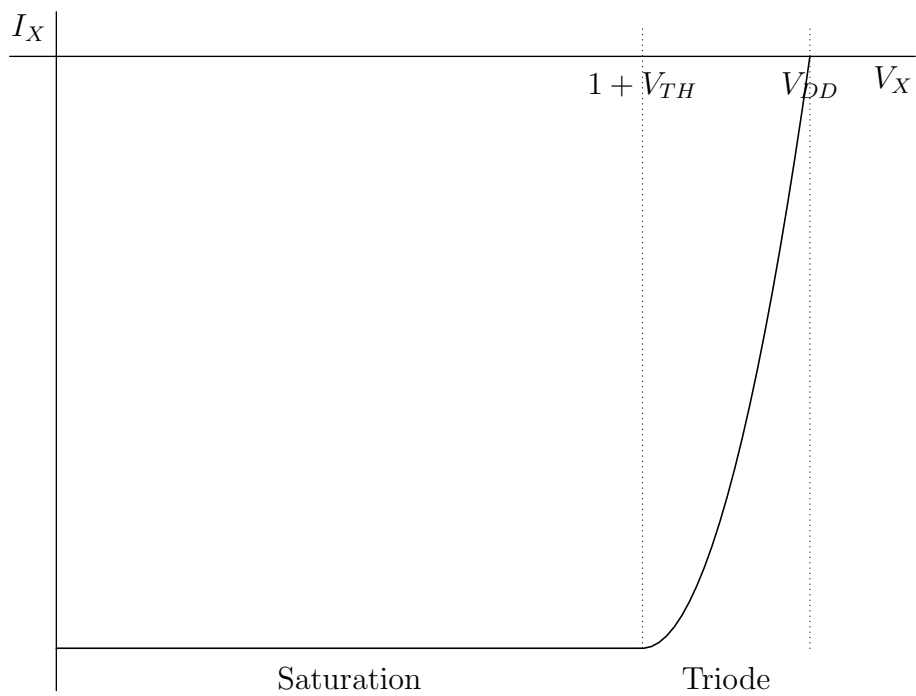


$M_1$  goes from saturation to triode when  $V_X = 1 + V_{TH} = 1.4$  V.

(c)

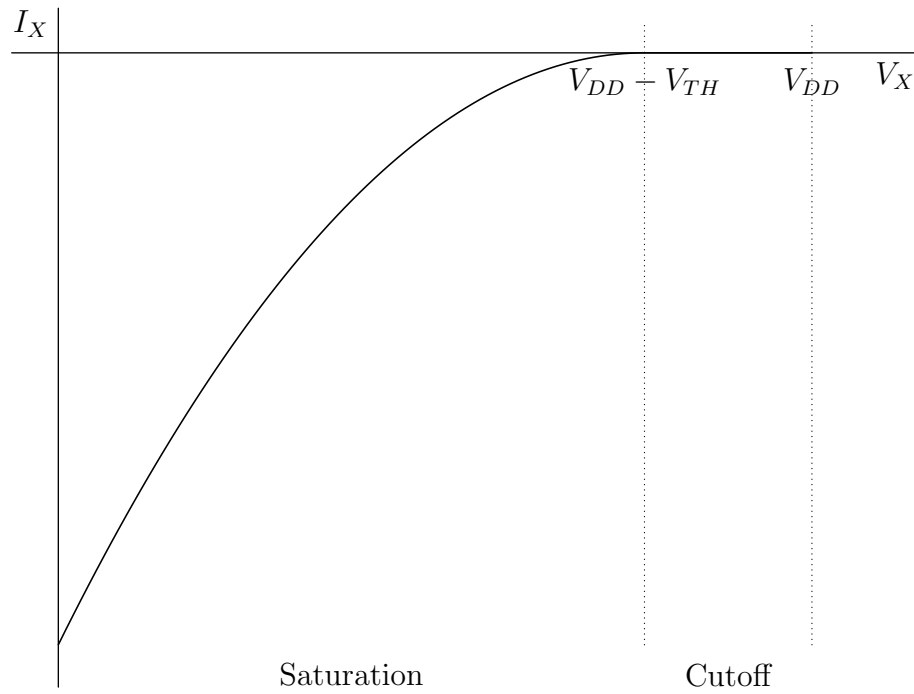



$M_1$  goes from saturation to cutoff when  $V_X = V_{DD} - V_{TH} = 1.4$  V.

(d)


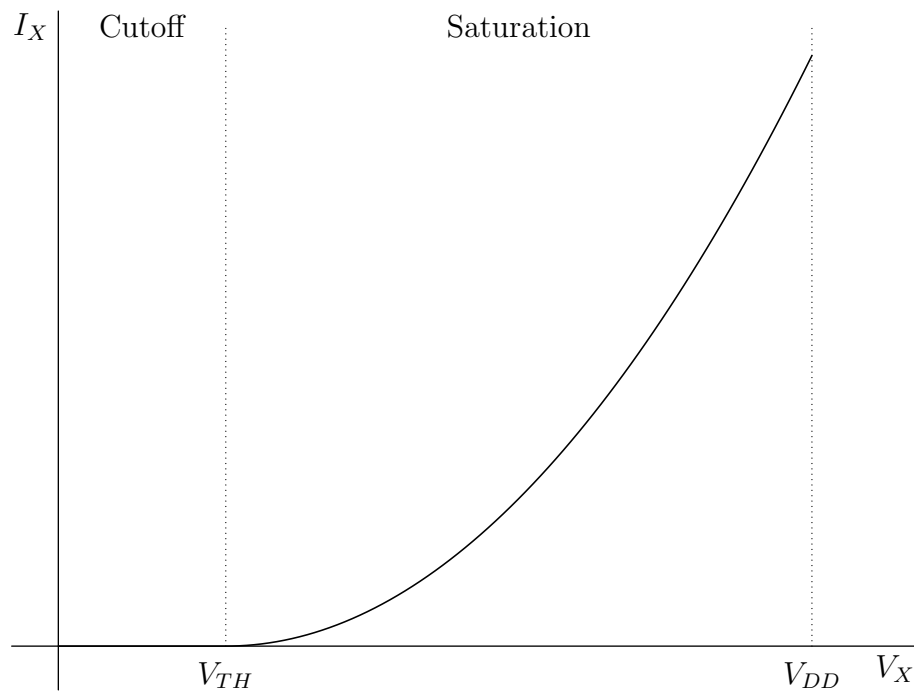


$M_1$  goes from cutoff to saturation when  $V_X = V_{TH} = 0.4$  V.



45. (a)

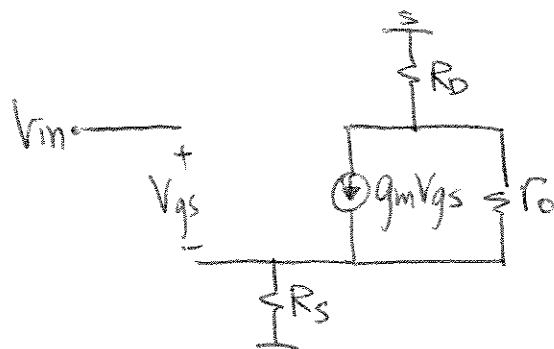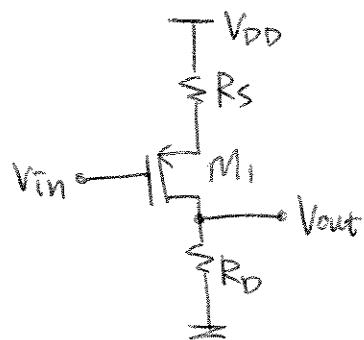



(b)

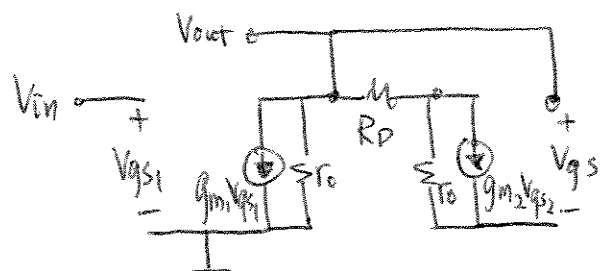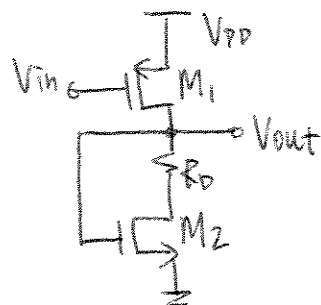



(c)

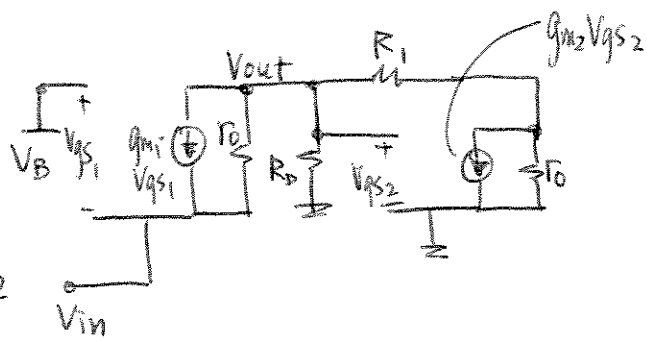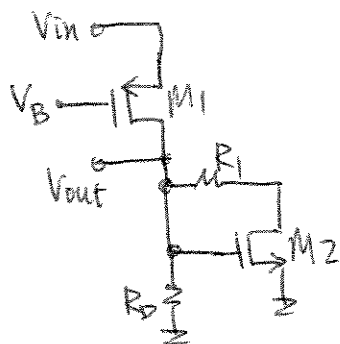


(d)

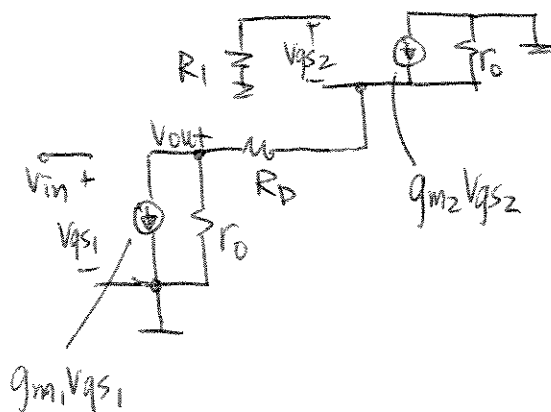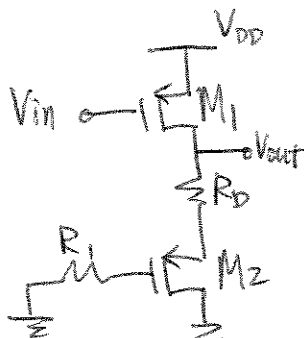

(e)

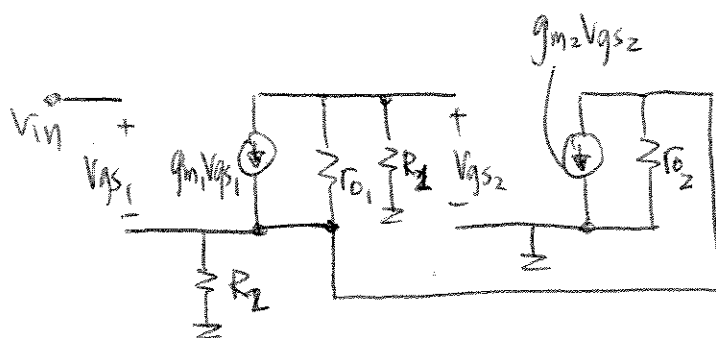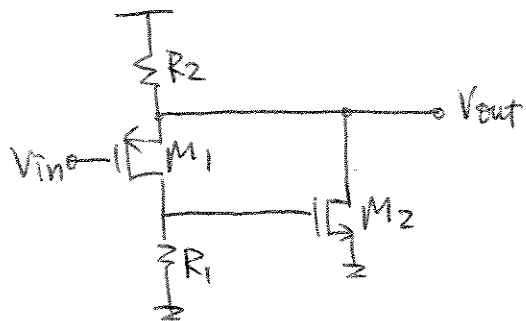


4b.

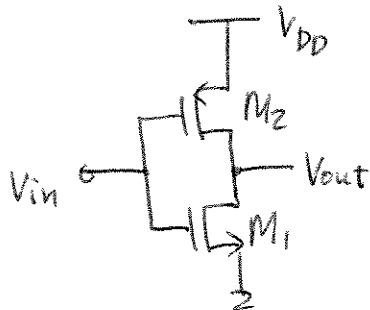


Assume  $\lambda_n$  &  $\lambda_p$ .

(a)

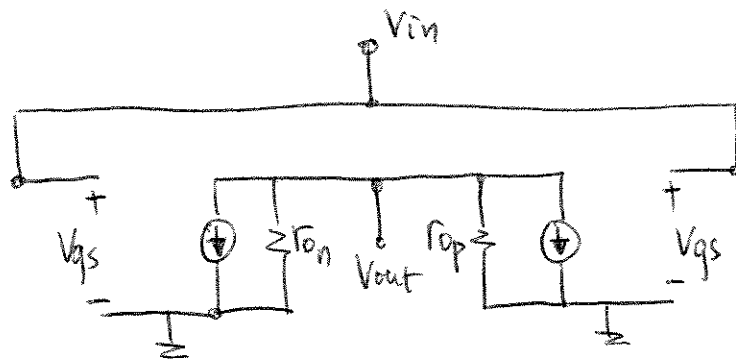

They are in "parallel" because from the small-signal model, both their respective SOURCE and DRAIN nodes are the same.

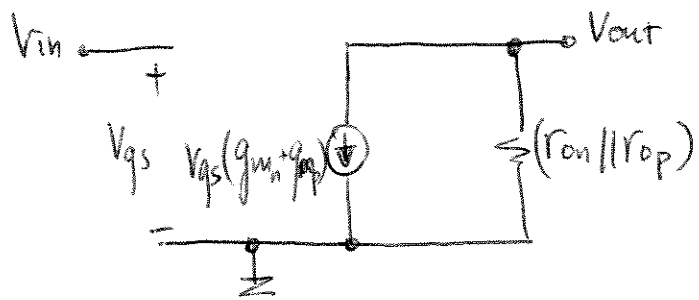(b) Assuming both  $M_1$  &  $M_2$  are in saturation, we can combine  $r_o$ 's &  $g_m$ 's :



$$\therefore \frac{V_{out}}{V_{in}} = -(g_{mn} + g_{mp})(r_{on} || r_{op})$$