
 


Assignment-2 (CMOS Analog Circuit Design)

Q1.	<p>Suppose the total capacitance between adjacent lines in Fig. 4.2 is 10 fF and the capacitance from the drains of M_1 and M_2 to ground is 100 fF.</p> <p>(a) What is the amplitude of the glitches in the analog output in Fig. 4.2(a) for a clock swing of 3 V?</p> <p>(b) If in Fig. 4.2(b), the capacitance between L_1 and L_2 is 10% less than that between L_1 and L_3, what is the amplitude of the glitches in the differential analog output for a clock swing of 3 V?</p>
Q2.	<p>In the circuit of Fig. 4.10, $(W/L)_{1,2} = 50/0.5$ and $I_{SS} = 0.5$ mA.</p> <p>(a) What is the maximum allowable output voltage swing if $V_{in,CM} = 1.2$ V?</p> <p>(b) What is the voltage gain under this condition?</p>
Q3	<p>A differential pair uses input NMOS devices with $W/L = 50/0.5$ and a tail current of 1 mA.</p> <p>(a) What is the equilibrium overdrive voltage of each transistor?</p> <p>(b) How is the tail current shared between the two sides if $V_{in1} - V_{in2} = 50$ mV?</p> <p>(c) What is the equivalent G_m under this condition?</p>
Q4	<p>For the differential pairs of Fig. 4.32(a) calculate the differential voltage gain if $I_{SS} = 1$ mA, $(W/L)_{1,2} = 50/0.5$, and $(W/L)_{3,4} = 50/1$. What is the minimum allowable input CM level if I_{SS} requires at least 0.4 V across it? Using this value for $V_{in,CM}$, calculate the maximum output voltage swing</p>
Q5	<p>In the circuit shown below, sketch V_X and V_Y as a function of I_{REF}. If I_{REF} requires 0.5 V to operate as a current source, what is its maximum value?</p>

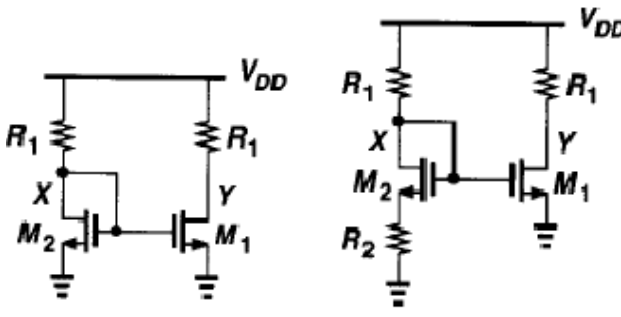

Q6.	<p>In Fig. 5.2, assume $(W/L)_1 = 50/0.5$, $\lambda = 0$, $I_{out} = 0.5$ mA, and M_1 is saturated.</p> <p>(a) Determine R_2/R_1.</p> <p>(b) Calculate the sensitivity of I_{out} to V_{DD}, defined as $\partial I_{out} / \partial V_{DD}$ and normalized to I_{out}.</p> <p>(c) How much does I_{out} change if V_{TH} changes by 50 mV?</p>
Q7.	<p>Consider the circuit of Fig. 5.9(a), assuming $(W/L)_{1-3} = 40/0.5$, $I_{REF} = 0.3$ mA, and $\gamma = 0$.</p> <p>(a) Determine V_b such that $V_X = V_Y$.</p> <p>(b) If V_b deviates from the value calculated in part (a) by 100 mV, what is the mismatch between I_{out} and I_{REF}?</p> <p>(c) If the circuit fed by the cascode current source changes V_P by 1 V, how much does V_Y change?</p>
Q8.	<p>Consider the circuit of Fig. 5.22(a) with $(W/L)_{1-5} = 50/0.5$ and $I_{D5} = 0.5$ mA.</p> <p>(a) Calculate the deviation of V_{out} from V_F if V_{TH3} is 1 mV less than V_{TH4}.</p>
Q9.	<p>Sketch V_X and V_Y as a function of V_{DD} for each circuit. Assume the transistors in each circuit are identical.</p>

	
Q10.	Derive an expression for small signal voltage gain of active current mirror assuming ideal tail current source.

Note : Please refer Text Book (Behzad Razavi, "Design of Analog CMOS Integrated Circuits", McGraw-Hill Edition, 2002) for the Figure Numbers indicated in the Questions.