

DATE


NETWORK THEOREM

30th Sep '19


MILLMAN'S THEOREM : allows to reduce any no. of parallel voltage sources to one.

STEPS :

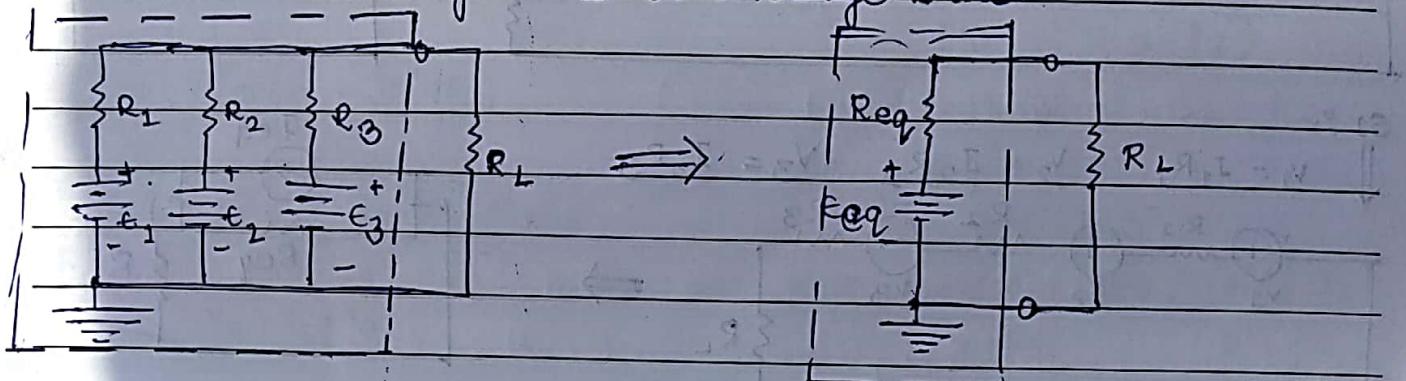- * Convert all voltage source to current source.
- * Combine all three current source.
- * Convert the resulting source to a voltage source.



$$I_T = I_1 + I_2 + I_3$$

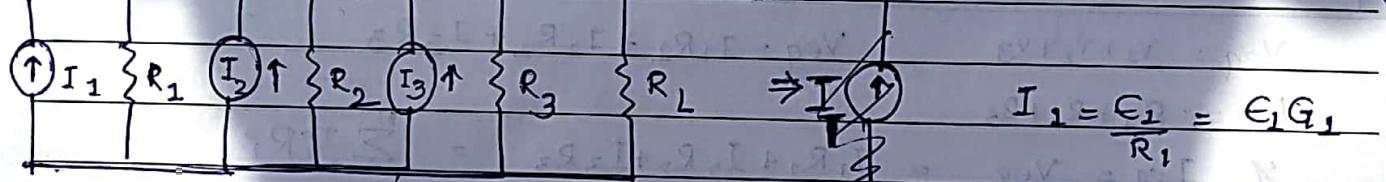

$$I_1 = \frac{E_1}{R_1} = E_1 G_1$$

$$\frac{1}{Req} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_2 = E_2 G_2$$

$$I_3 = E_3 G_3$$

$$R_2 R_3 + R_1 R_3 + R_1 R_2$$

$$E_{eq} = \frac{E_1 G_1 + E_2 G_2 + E_3 G_3}{G_1 + G_2 + G_3}$$

$$G_{eq} = G_1 + G_2 + G_3$$

$$n = 3$$

$$= \sum_{i=1}^{n=3} E_i G_i$$


$$E_{eq} = I_T \cdot Req$$

$$= I_T = I_1 + I_2 + I_3$$

$$Req = \frac{1}{\sum_{i=1}^{n=3} G_i} = \frac{1}{G_{eq}}$$

DC \rightarrow Admittance $\rightarrow Y$

$$G_{eq} = \frac{1}{G_1 + G_2 + G_3}$$

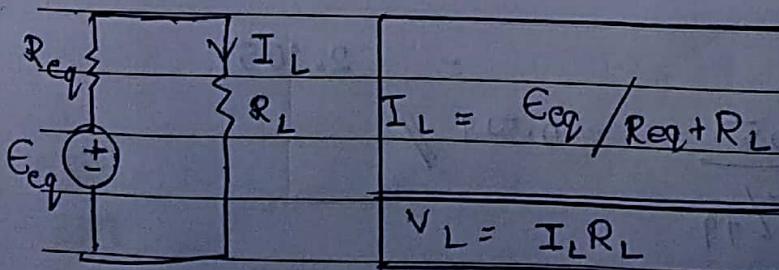


$$\sum_{i=1}^{n=3} G_i$$

DATE


MILLMAN'S THEOREM

→ DUAL

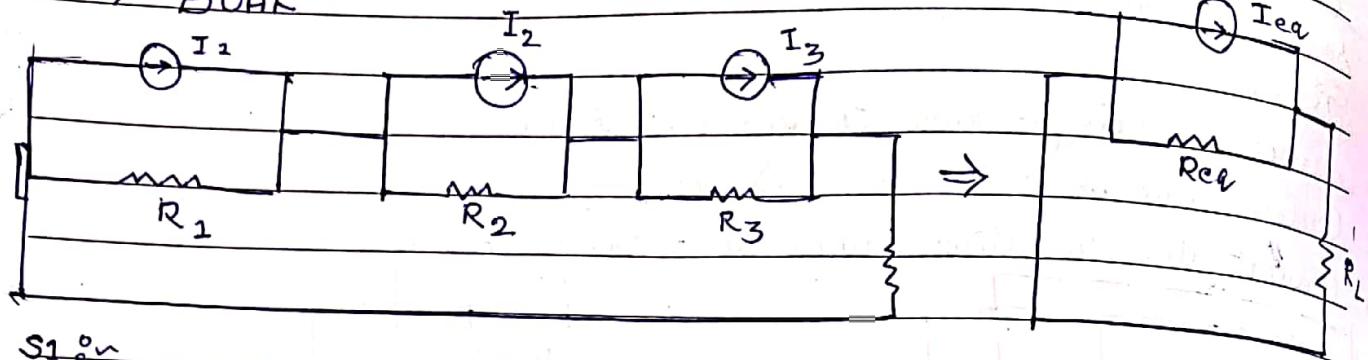

S1 on
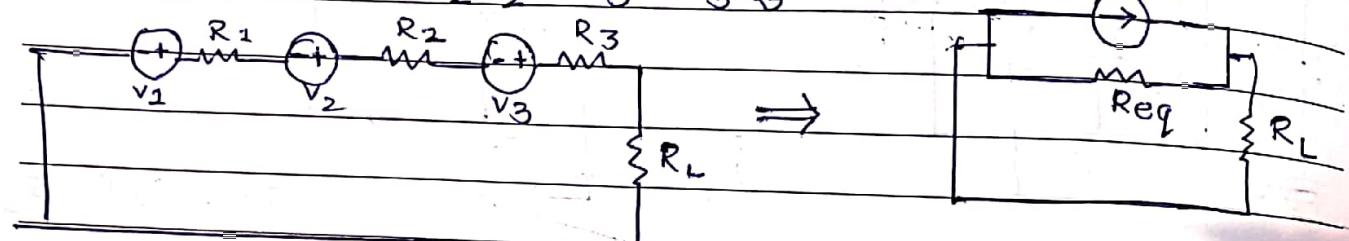
$$V_1 = I_1 R_1 \quad V_2 = I_2 R_2 \quad V_3 = I_3 R_3$$




$$V_{eq} = V_1 + V_2 + V_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$\therefore I_{eq} = \frac{V_{eq}}{R_{eq}} = \frac{I_1 R_1 + I_2 R_2 + I_3 R_3}{R_1 + R_2 + R_3} = \frac{\sum_{i=1}^n I_i R_i}{\sum_{i=1}^n R_i}$$

Ex 1

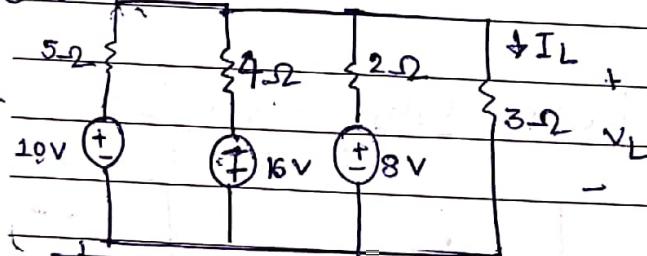

$$E_{eq} = 10(G_1) + 16(G_2) + 8(G_3)$$

$$G_1 + G_2 + G_3$$

$$= 50 + -64 + 16$$

11

$$= 0.18$$

$$= 10\left(\frac{1}{5}\right) - 16\left(\frac{1}{4}\right) + 8\left(\frac{1}{3}\right)$$


- 0.95

$$= \frac{10 - 4 + 4}{0.95} = 2 - 4 + 4$$

$$R_{eq} = \frac{20}{19}$$

$$I_L = \frac{2.105}{\frac{20}{19} + 3} = \frac{2.105}{47/19} = 0.519 \text{ A}$$

$$V_L = 1.559 V //$$

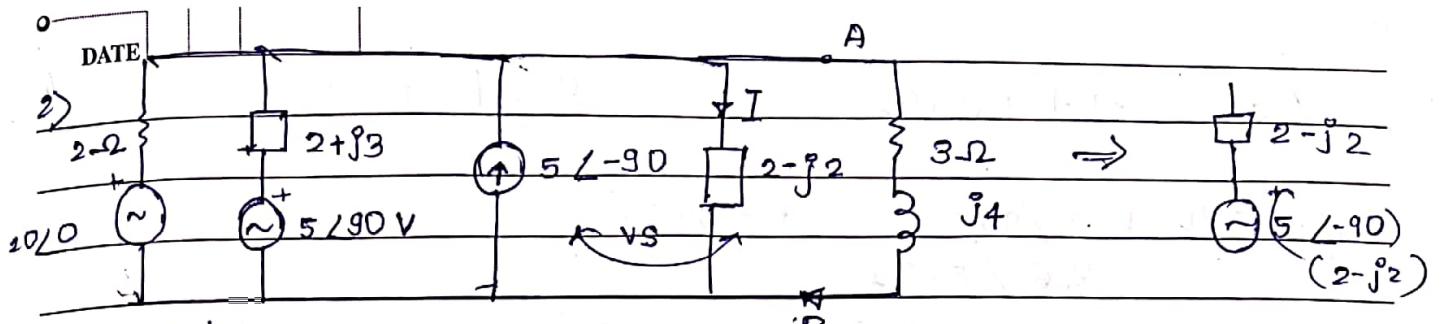

$$\epsilon_1 = V / \theta$$

$$= V [\cos \theta + j \sin \theta]$$

$$\epsilon = V / -\theta$$

$$= V [\cos \theta - j \sin \theta]$$

$$\epsilon_{eq} = \left(\frac{1}{2}\right) (10) + (0+j5)(2+j3) + (0-5j)(2-j2)$$

$$\frac{1}{2} + \frac{2+j3}{2+j3} + \frac{-1}{2-j2}$$

$$\epsilon_{eq} = \epsilon_1 Y_1 + \epsilon_2 Y_2 + \epsilon_3 Y_3$$

$$= 5 + 10j + 15j^2$$

$$R_{eq} = \frac{1}{Y_1 + Y_2 + Y_3}$$

$$= \frac{10 \angle 0}{2} + \frac{5 \angle 90}{2+j3} + \frac{5 \angle -90}{2-j2}$$

$$\frac{1}{2} + \frac{1}{2+j3} + \frac{1}{2-j2}$$

$$\Rightarrow 5 \angle 0 + 5 \angle 90 + 5 \angle -90$$

$$3.60 / 56.3$$

$$\Rightarrow 5 \angle 0 + 1.388 \angle 33.7 + 5 \angle -90$$

$$Y_2 = \frac{1}{2+j3} \times \frac{2-j3}{2-j3} = \frac{2-j3}{(2)^2 - (j3)^2} = \frac{2-j3}{4+9} = \frac{2-j3}{13}$$

$$Y_3 = \frac{1}{2-j2} \times \frac{2+j2}{2+j2} = \frac{2+j2}{(2)^2 - (j2)^2} = \frac{2+j2}{4+4} = \frac{2+j2}{8}$$

$$\Rightarrow 5 + 1.154 + 0.77j + (-j5) = 6.154 - 4.223j$$

$$0.5 + \frac{2-j3}{13} + \frac{2+j2}{8} = 52 + 16 - 48j + 26 + 26j$$

$$= \frac{640.016 - 439.192j}{94 - 22j} = \frac{776.215}{96.54} \angle -34.458$$

$$Y_{eq} = \frac{1}{2+j3} + \frac{1}{2-j2} = 8.04 \angle -21.286 //$$

$$= 7.5 - 2.91j //$$

$$= 0.5 + \frac{2-j3}{13} + \frac{2+j2}{8}$$

$$= 0.5 + 0.153 - 0.23j + 0.25 + 0.125j = 0.903 - 0.18005j$$

DATE

$$Y_{eq} = 0.904 + j0.02$$

$$0.904 / 1.26^\circ$$

$$E_{eq} = 5/0 + .5/90^\circ + 5/-90^\circ$$

$$3.6 / 56.31$$

$$= \frac{5/0 + 1.38 / 33.69 + 5 / -90^\circ}{0.904 + j0.02}$$

$$= 5 + 1.148 + 0.765j + (-5j)$$

$$0.904 + j0.02$$

$$= \frac{6.148 - 4.235j}{0.904 + j0.02} = \frac{7.465 / -34.56}{0.904 / 1.26^\circ}$$

$$= 8.025^\circ / -35.82^\circ$$

$$= 6.69 - j4.8$$

$$I_L \neq E_{eq}$$

$$Z_{eq} = 1.106 - j0.0236$$

$$1.68 / -48.8^\circ$$

$$I_L = E_{eq}$$

$$= 6.7 - j4.8$$

$$Z_{eq} + R_L = 1.106 - j0.0236 + 3 + j4$$

$$= 6.7 - j4.8$$

$$4.106 + 3.976j$$

$$= 8.242 / -35.618^\circ$$

$$5.715 / 44.078$$

$$= 1.44 / -79.696^\circ$$

$$= 0.25 - 1.41j //$$

$$-V_L = I_L R_L = (0.25 - 1.41j)(3 + j4)$$

$$= (1.432 / -79.945^\circ)(5 / 53.13^\circ)$$

$$= 7.16 / -26.815^\circ$$

DATE | COMPLEX FREQUENCY.

The soln to DE had terms of the form

$$y(t) = k_n e^{s_n t}$$

Complex frequency : $s_n = \sigma_n + j\omega_n$

radian / angular frequency : ω_n rad/sec

$$\omega_n = \frac{2\pi f}{T_n} = \frac{2\pi}{T_n}$$

NEPER frequency : σ_n naper per sec


The unit for the natural logarithm is the naper

Case 1 : $s_n = \sigma_n + j0$ (naper frequency only)

$\sigma > 0$: Increases exponentially

$\sigma < 0$: Decreases or decay exponentially

$\sigma = 0$: Direct current / voltage

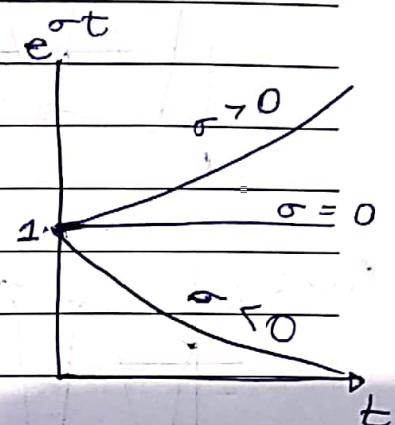

Case 2 : $s_n = 0 + j\omega_n$ (radian frequency only)



$$k_n e^{j\omega_n t} = k_n (\cos \omega_n t + j \sin \omega_n t)$$

* $e^{j\omega_n t}$ is known as unit rotating phasor

* phasor has magnitude & phase wrt a reference

* The unit phasor $e^{j\omega_n t}$ rotates counterclockwise considered (+ve)

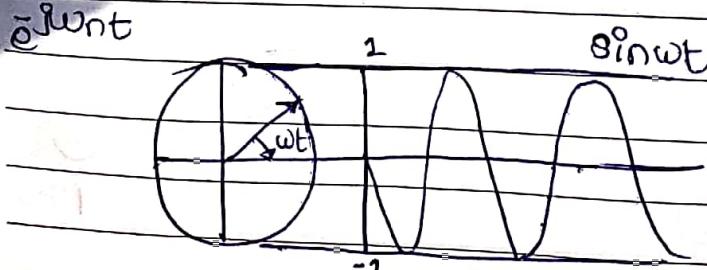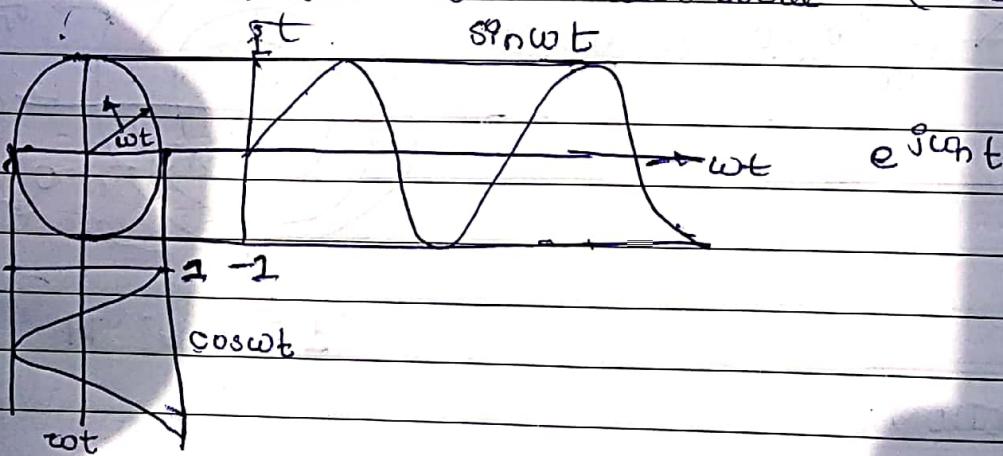* $e^{-j\omega_n t}$ → rotate in the clockwise direction (-ve)



cos \omega_n t will be same as
e^{j\omega_n t}

DATE



$$\text{case 3: } s_n = \sigma_n + j\omega_n$$

$$k_n e^{s_n t} = k_n e^{\sigma_n t} e^{j\omega_n t} = k_n e^{\sigma_n t} (\cos \omega_n t + j \sin \omega_n t)$$



for +ve rotation, for $\sigma_n = 2$

$$\text{Re } e^{s_n t} = e^{\sigma_n t} \cos \omega_n t \quad e^{s_n t} = e^{\sigma_n t} \sin \omega_n t$$

$\sigma_n < 0^\circ$

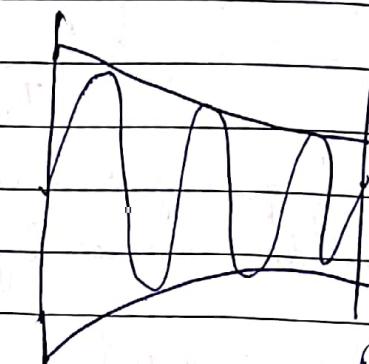
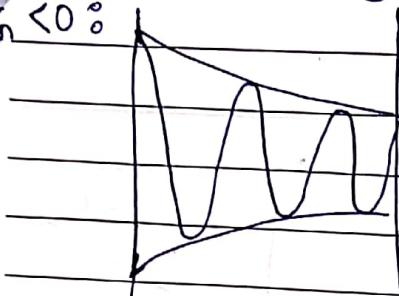


$\sigma_n > 0^\circ$

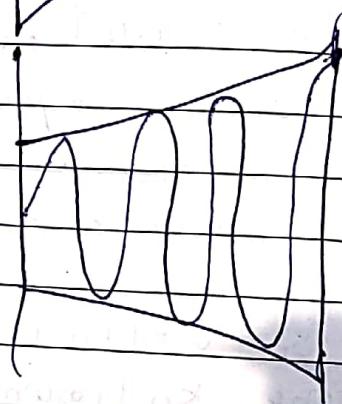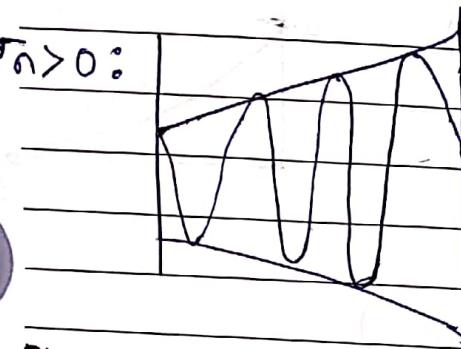

PHASOR REPRESENTATION
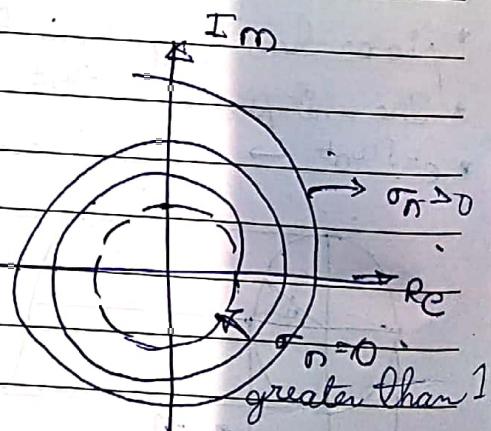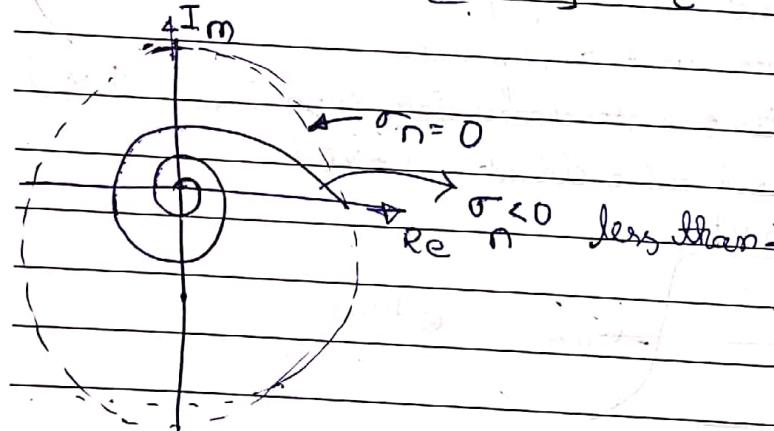
$$y(t) = e^{\sigma_n t} e^{j\omega_n t} \quad [\sigma_n = 0] = e^{j\omega_n t}$$



NETWORK FUNCTIONS

1st Oct' 19

$$\frac{dy}{dt} + \frac{1}{T} y(t) = \epsilon$$

$$s Y(s) - y(0^-) + \frac{1}{T} Y(s) = \epsilon(s)$$

$$Y(s) \left[s + \frac{1}{T} \right] - y(0^-) = \epsilon(s)$$

DATE

$$Y(s) = \frac{E(s) + Y(0^-)}{s + 1/\tau}$$

$$Y(s) = \frac{Y(0^-)}{s + 1/\tau} + \frac{E(s)}{s + 1/\tau} \quad \checkmark$$

$$y(t) = Y(0^-) e^{-t/\tau} + E(s) e^{-t/\tau}$$

Assume

$$Y(0^-) = 0$$

$$Y(s) = \left[\frac{1}{s + 1/\tau} \right] E(s)$$

$$Y(s) = F(s) E(s)$$

$$F(s) = \frac{Y(s)}{E(s)}$$

↓

Network Function

ratio of 2 Laplace Transform

|| by for 2nd order vkt, under zero initial cond^{no}

$$Y(s) = \frac{b_1 s + b_2}{s^2 + \alpha_1 s + \alpha_2} E(s) = F(s) E(s)$$

$$E(s) \xrightarrow{F(s)} Y(s)$$

$E(s) \rightarrow$ Excitation

$Y(s) \rightarrow$ response

$F(s) \rightarrow$ Transform admittance

* If the excitation is a voltage & the response is a current then $F(s)$ is an Admittance

* If the excitation is a current & the response is a voltage then $F(s)$ is Impedance

* Together they are referred to as Immittance.

Resistance \circ

$$V_R(t) = R i_R(t) \rightarrow ① \quad \text{or} \quad V_R(s) = R I_R(s)$$

$$\frac{i_R(t)}{R} = \frac{1}{R} V_R(t) = G V_R(t) \quad \overline{I_R(s)} = \frac{V_R(s)}{R} = G V_R(s) \quad ②$$

$$Z_R(s) \triangleq \frac{V_R(s)}{I_R(s)} = R$$

$$Y_R(s) \triangleq \frac{I_R(s)}{V_R(s)} = G$$

* $Z_R(s)$ is called the Transform Impedance & $Y_R(s)$ is Transform Admittance

DATE

Taking LT of ①


* Resistance won't get change in
Replace domain

$$V_R(s) = R I_R(s)$$

$$\frac{V_R(s)}{I_R(s)} = R = Z_R(s)$$

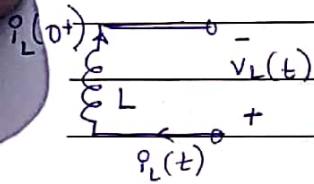2) INDUCTANCE (L)

$$V_L(t) = L \frac{di}{dt} \rightarrow 0$$



Taking LT


$$V_L(s) = L [s I_L(s) - i_L(0^-)]$$

$$V_L(s) = L s I_L(s) - i_L(0^-) L I_L(0^-)$$

$$V_L(s) + L I_L(0^-) = L s I_L(s)$$

$$v_1(s) = s L I_L(s)$$
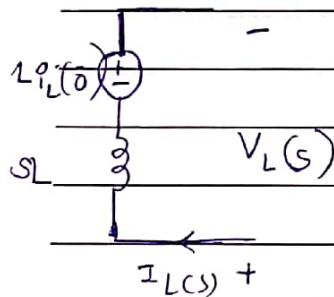
$$\frac{V_L(s)}{I_L(s)} = \frac{sL}{Z_L(s)} \rightarrow \text{Transform Impedance.}$$




$$b) i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(z) dz = \frac{1}{L} \int_{-\infty}^0 v_1(z) dz + \frac{1}{L} \int_0^t v_L(z) dz$$

$i_L(0^-)$

$$i_L(t) = i_L(0^-) + \frac{1}{L} \int_0^t v_L(z) dz$$
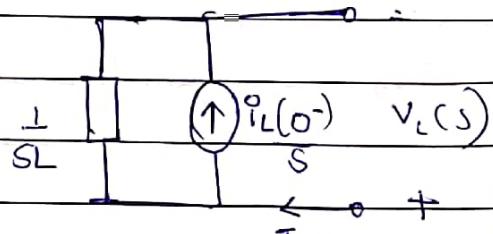
$$I_L(s) = i_L(0^-) + \frac{1}{s} V_L(s)$$



$$\frac{I_L(s) - i_L(0^-)}{s} = \frac{1}{sL} V_L(s)$$


$$I_1(s) = \frac{1}{sL} V_L(s)$$

$$\frac{I_1(s)}{V_L(s)} = \frac{1}{sL} = Y_L(s) \rightarrow \text{Transform admittance}$$

DATE

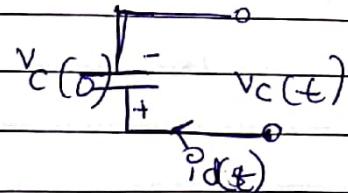
3) CAPACITANCE :-

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(\tau) d\tau \rightarrow ①$$



$$= \frac{1}{C} \int_{-\infty}^0 v_i(\tau) d\tau + \frac{1}{C} \int_0^t i_C(\tau) d\tau$$

$V_C(0^-)$

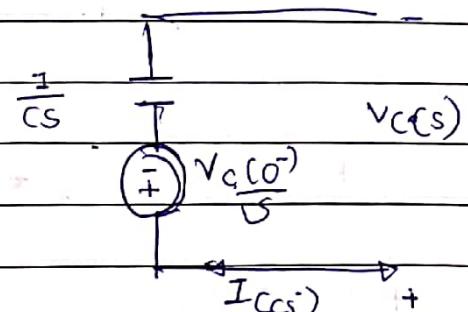


$$V_C(s) = \frac{V_C(0^-)}{s} + \frac{1}{C s} I_C(s) \rightarrow ②$$

$$\underbrace{V_C(s) - V_C(0^-)}_s = \frac{1}{C s} I_C(s)$$

$$V_I(s) = \frac{1}{C s} I_C(s)$$

$$= \frac{V_I(s)}{I_C(s)} = \frac{1}{C s} // \quad \text{Transform Impedance}$$

b) $i_C(t) = C \frac{dV_C}{dt}$

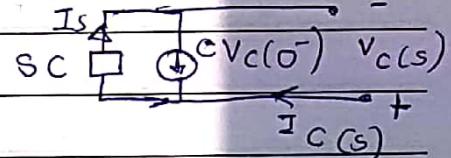


$$I_C(s) = C [sV_C(s) - V_C(0^-)] = CSV_C(s) - CV_C(0^-)$$

$$I_C(s) = CSV_C(s) - CV_C(0^-)$$

$$\underbrace{I_C(s) + CV_C(0^-)}_{I_1} = CSV_C(s)$$

$$\frac{I_1}{V_C(s)} = CS \quad \text{Transform Admittance}$$

Ex 1 :-

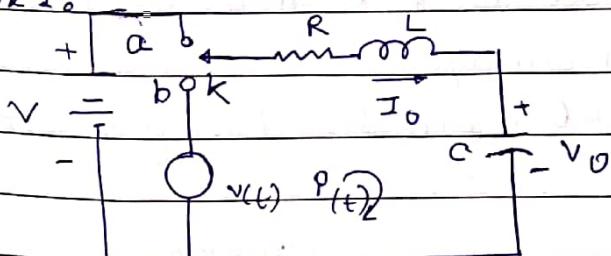


Initial current is I_0 & voltage is V_0

Find the Transform $I(s)$

DATE

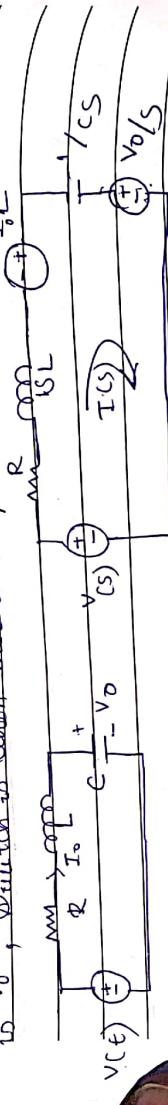Switch 'A' on 'A' position. Current through I_{01} & I_{02} will flow through V_o .
 Switch 'B' on 'B', switch 'A' moved to position 'B'.
 V_o




$$V(s) = RI(s) + SLI(s) \Rightarrow L I_0 + \frac{1}{s} I(s) + \frac{V_o}{s}$$

$$\underbrace{V(s) + LI_0}_{V_1(s)} + \underbrace{\frac{V_o}{s}}_{Z(s)} = I_s \left[R + sL + \frac{1}{sC} \right]$$


$$\frac{V_1(s)}{Z(s)} = \frac{V_1(s)}{Z(s)}$$

$$\begin{aligned} I(s) &= \frac{V(s) + LI_0 - \frac{V_o}{s}}{R + sL + \frac{1}{sC}} \\ &= \frac{sV(s) + sLI_0 - V_o}{s^2 + RS + 1/C} \end{aligned}$$


2)

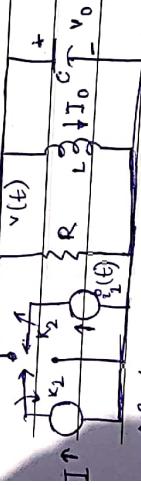

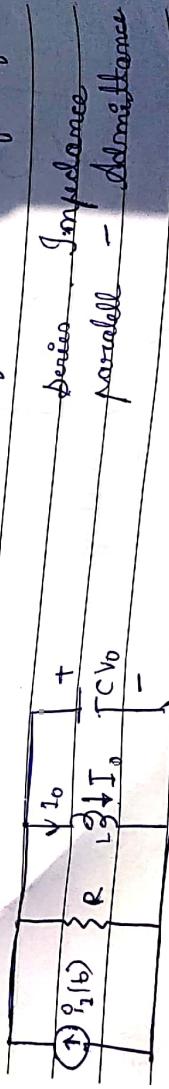Switch k_1 gets connected to the left at $t = 0^-$ with initial current I_0 in the inductor L and initial voltage V_0 across capacitor C .
 Switch k_2 gets connected to left at $t = 0$. find the node voltage $v(t)$.



5th Oct 919

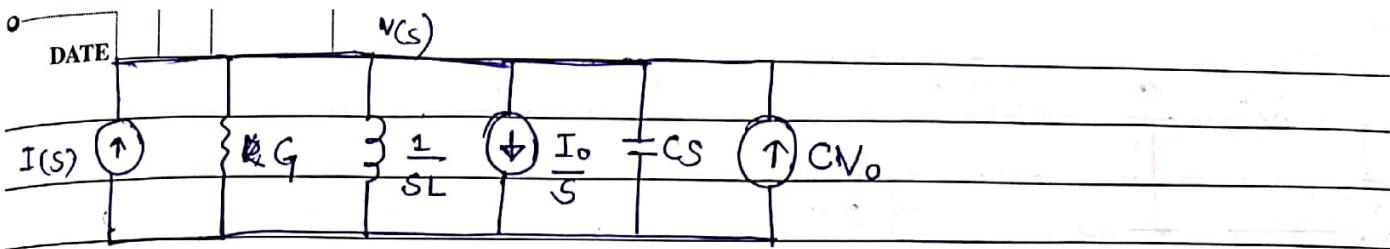

$$V(s) = \frac{I(s)}{Y(s)}$$


$$I(s) = I_1(s) + CV_o - \frac{I_o}{s}$$

$$Y(s) = G + \frac{I_o}{sL} + CY_o - CS$$


$$V(s) = I_1(s) + CV_o - \frac{I_o}{s} + G + \frac{1}{sL} + CS$$

$V(s) = \frac{sI_1(s) + CSV_o - I_o}{s^2 + \frac{1}{sL} + GS}$
L

Transform Impedance & Admittance

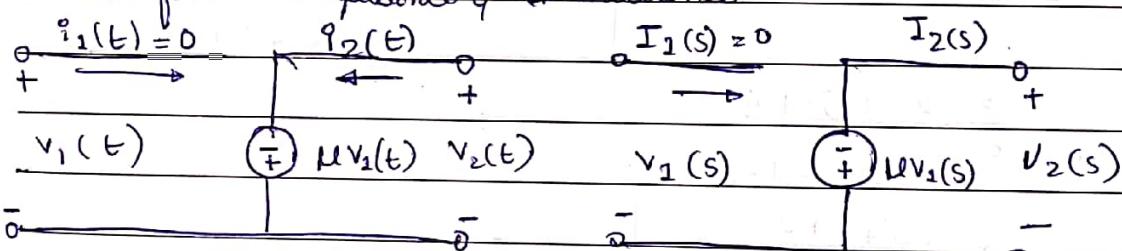


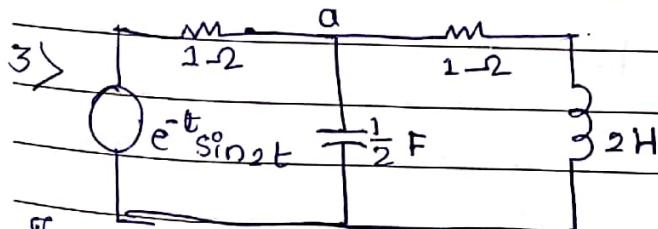Network functions are \therefore impedance or voltage gain / current gain
Initial condition: No voltage across capacitor, no current across inductor at zero time is a network function.




Find the current supplied by source in the laplace domain
 $I(s)$,

DATE

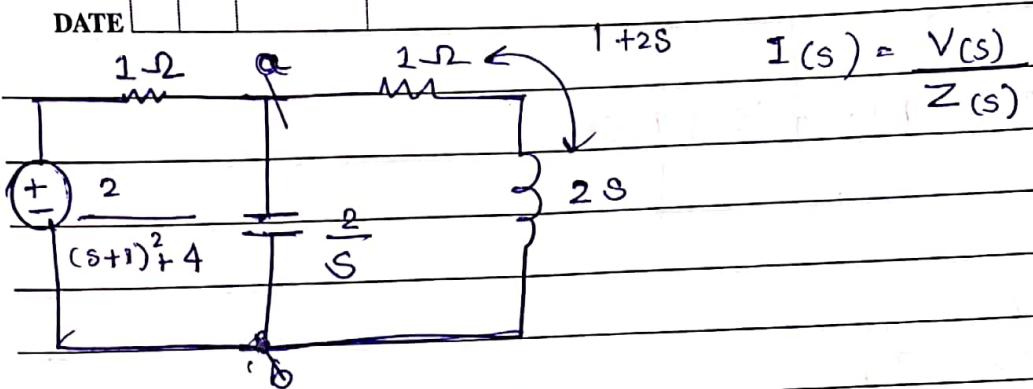

$$Y_{ab}(s) = \frac{2}{(s+1)^2 + 4} + \frac{2}{s} - \frac{1}{1+2s} - \frac{s+2s^2+2}{2+4s}$$

$$Z_{ab}(s) = \frac{2(2s+1)}{2s^2+s+2}$$

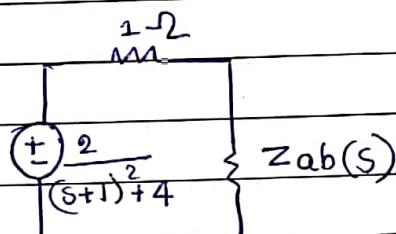

$$Z(s) = 1 + Z_{ab}s$$


$$1 + \frac{2(2s+1)}{2s^2+s+2} = \frac{2s^2+s+2+4s+2}{2s^2+s+2} = \frac{2s^2+5s+4}{2s^2+s+2}$$

$$Z(s) = \frac{2s^2+5s+4}{2s^2+s+2}$$

$$I(s) = \frac{2}{(s+1)^2 + 4} = \frac{2s^2+5s+4}{2s^2+s+2}$$

$$I(s) = \frac{2}{(s+1)^2 + 4} \times \frac{2s^2+s+2+s}{2s^2+5s+4}$$

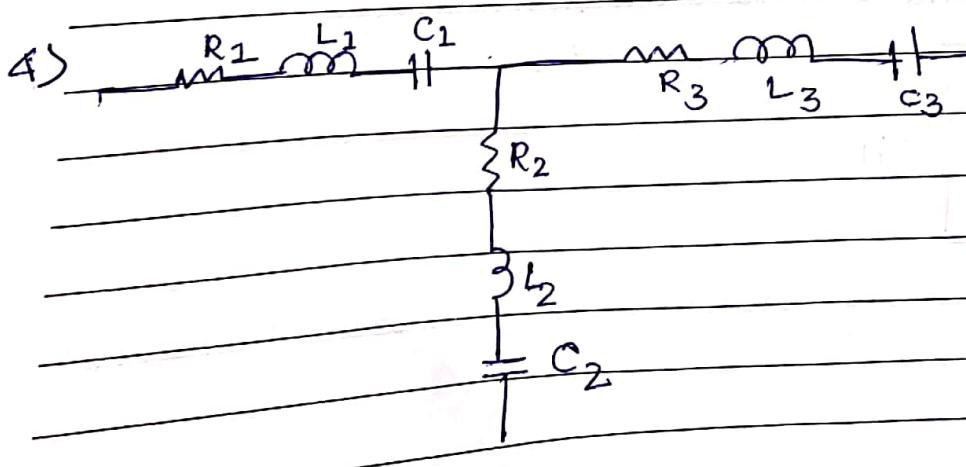Assignment $\stackrel{s^2+2s+5}{\sim}$ Find $I(t)$?



DATE

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} v_a(s) \\ -v_b(s) \end{bmatrix}$$

$$z_{11} I_1(s) + z_{12} I_2(s) = v_a(s)$$

$$z_{21} I_1(s) + z_{22} I_2(s) = -v_b(s)$$

parallel \rightarrow admittance

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} v_1(s) \\ v_2(s) \end{bmatrix} = \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$

$$z_{11} = (R_1 + sL_1 + \frac{1}{C_1 s}) \quad z_{12} = (R_2 + sL_2 + \frac{1}{C_2 s})$$

$$z_{12} = z_{21}$$

$$z_{22} = R_3 + sL_3 + \frac{1}{C_3 s}$$

L

$$\sum_{k=1}^3 z_k(s) I_k(s) = V_k(s)$$

General $(z)(I) = (v) + (v_0) = (v')$ $| \alpha(y)v = (I) + (I_0) = (I')$

$$\begin{bmatrix} z_{11} & z_{12} & z_{13} \\ z_{21} & z_{22} & z_{23} \\ z_{31} & z_{32} & z_{33} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \end{bmatrix} = \begin{bmatrix} v'_1(s) \\ v'_2(s) \\ v'_3(s) \end{bmatrix}$$

To find $I_1(s) \Rightarrow$ find $I_{11}(s)$ by shorting $v'_{2(s)}$ & $v'_{3(s)} = 0$

$$I_{12}(s) \rightarrow v'_{1(s)} \& v'_{3(s)} = 0$$

$$I_{13}(s) \rightarrow v'_{2(s)} \& v'_{1(s)} = 0$$

This theorem is known as
Superposition Theorem

$$I'(s) = I_{11}(s) + I_{12}(s) + I_{13}(s)$$

Principle of Linearity

$$I = [I_1(s) \ I_2(s) \ \dots \ I_L(s)]^T$$

Each current (or voltage) is obtained by determining the individual responses to a voltage (or current) & then summing up the responses

DATE

RECIPROCITY THEOREM

9th Oct 9, 19

1) No initial conditions

$$[Z][I] = [v_0] + [v] = [v']$$

$$[Z][I] = [v]$$

2) $[Z]$ is Symmetric

$$Z_{12} = Z_{21}$$

$$Z_{13} = Z_{31}$$

$$\begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{12} & Z_{22} & Z_{23} \\ Z_{13} & Z_{23} & Z_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

To find I_1 .

$$I_1 = \Delta I_1$$

$\Delta \rightarrow$ Determinant of matrix

$\Delta I_1 \rightarrow$ Replace 1st column row by the v_1, v_2, v_3

$$\Delta I_1 = \begin{vmatrix} v_1 & Z_{12} & Z_{13} \\ v_2 & Z_{22} & Z_{23} \\ v_3 & Z_{23} & Z_{33} \end{vmatrix} \quad \Delta_{11} = \begin{bmatrix} 22 & 23 \\ 23 & 33 \end{bmatrix}$$

$$I_1 = \frac{v_1 \Delta_{11}}{\Delta} + \frac{v_2 \Delta_{12}}{\Delta} + \frac{\Delta_{13} v_3}{\Delta} \rightarrow ①$$

To find $I_3 = \frac{\Delta I_3}{\Delta}$ 3rd column shld be replaced with v_1, v_2, v_3

$$\Delta I_3 = \begin{vmatrix} Z_{11} & Z_{12} & v_1 \\ Z_{12} & Z_{22} & v_2 \\ Z_{13} & Z_{23} & v_3 \end{vmatrix}$$

$$I_3 = \frac{v_1 \Delta_{13}}{\Delta} + \frac{v_2 \Delta_{23}}{\Delta} + \frac{v_3 \Delta_{33}}{\Delta} \rightarrow ②$$

Assuming $v_1 \neq v_2 = 0$ in 1st equation

$$I_1 = \frac{v_3 \Delta_{13}}{\Delta} \rightarrow ③$$

Assuming $v_2 \neq v_3 = 0$ in ② eqn

$$I_3 = \frac{v_1 \Delta_{13}}{\Delta} \rightarrow ④$$

We take this condition in such a way get the symmetric equations in the both equations

DATE

from (3) $\frac{I_1}{V_3} = \frac{\Delta_{13}}{\Delta} \rightarrow S_a$

from (4) $\frac{I_3}{V_1} = \frac{\Delta_{13}}{\Delta} \rightarrow S_b$


S_a & S_b 's RHS are equal so LHS are also equal

$$\frac{I_1}{V_3} = \frac{I_3}{V_1}$$

This holds good only when

$$\begin{cases} I_1 = I_3 \\ V_1 = V_3 \end{cases}$$

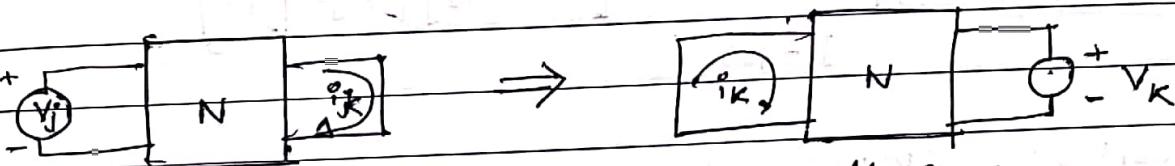
Generally $\frac{I_k}{V_j} = \frac{I_j}{V_k}$



- * V_j is the only source in network. This results in the current I_k in k^{th} loop
- * If we shifted voltage source to k^{th} loop then current flowing in the j^{th} loop is I_j .
- * The ratio of the response transform to the excitation transform is invariant to an interchange of the position in the network of the excitation & the response.

CONDITIONS FOR GKT TO BE RECIPROCAL

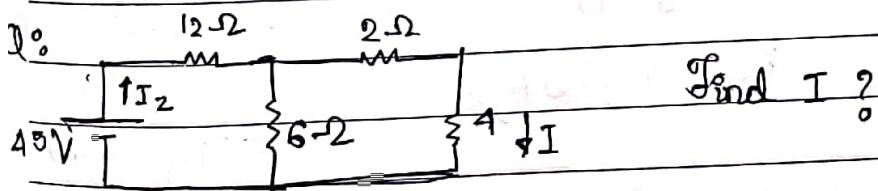- * for a network to be reciprocal, there should not be any dependent sources
- * There should be only R, L, C & Transformers as elements
- * Only one voltage source should be there.
- * The impedances should be symmetric
- * No initial conditions



Find I ?

$$= \begin{bmatrix} 18 & -6 \\ -6 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 45 \\ 0 \end{bmatrix}$$

$$I_1 = 3A$$

$$I_2 = 1.5A$$

DATE

Where we are asked to find current replace that voltage source in the same branch where we are asked to find the current.

To reduce voltage to zero, what that, if current source is there open it that


$$I = 1.5 \text{ A}$$

$$\begin{bmatrix} 12 \\ 2 \end{bmatrix} = \begin{bmatrix} 18 & -6 \\ -6 & 12 \end{bmatrix} \begin{bmatrix} I \\ I_Z \end{bmatrix} = \begin{bmatrix} 0 \\ 45 \end{bmatrix}$$

$$I = 1.5$$

SUPERPOSITION PROBLEMS

(1)

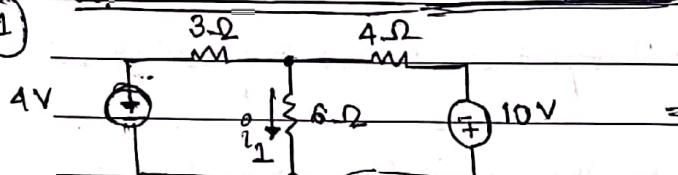

(a) Due to only 4V source

$$\begin{bmatrix} 3 \\ 4 \end{bmatrix} = \begin{bmatrix} 9 & -6 \\ -6 & 10 \end{bmatrix} \begin{bmatrix} i_{1a} \\ i_{2a} \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \end{bmatrix} \times$$

$$i_{1a} = 0.6667 \text{ A} // = +0.259 \text{ A}$$

(b) Due to only 10V

$$\begin{bmatrix} 3 \\ 4 \end{bmatrix} = \begin{bmatrix} 9 & -6 \\ 10 & -6 \end{bmatrix} \begin{bmatrix} i_{1a} \\ i_{1b} \end{bmatrix} = \begin{bmatrix} 0 \\ 10 \end{bmatrix} \times$$

$$i_{1b} = -0.553 \text{ A} //$$

$$i_t = i_a + i_b = -0.294 \text{ A} //$$

$$4 - 3i_1 - 6i_1 = 0$$

$$-4i_2 + 6(i_2 - i_1) = 0$$

$$4 - 9i_1 = 0$$


$$4 - 3i_1 - 6i_1 + 6i_2 = 0 \Rightarrow -9i_1 + 6i_2 = 0$$

$$-9i_1 + 6i_2 = -4$$


$$-4i_2 - 6i_2 + 6i_1 = 0$$

$$-10i_2 + 6i_1 = 0$$

$$6i_1 - 10i_2 = 0$$

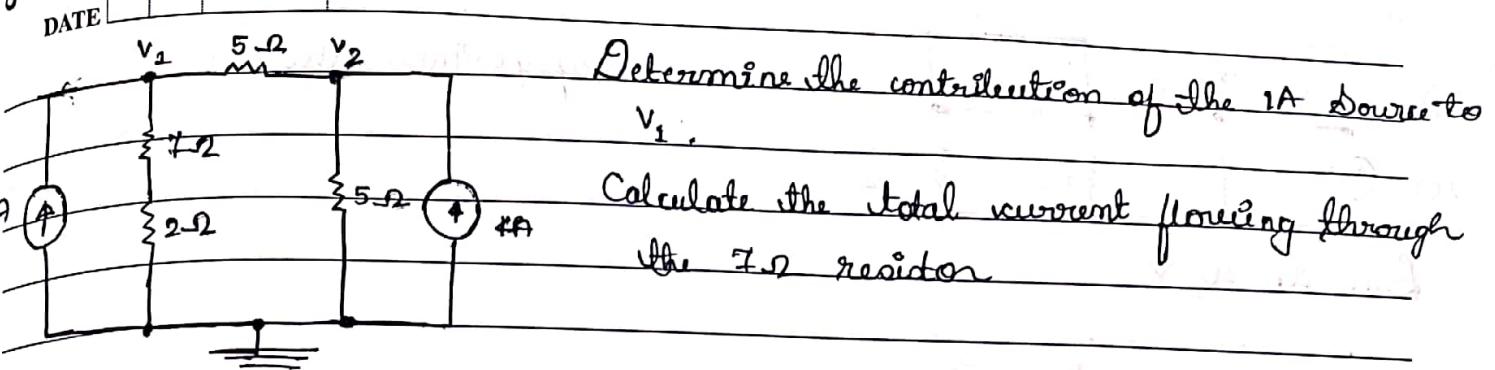


Open the one of the source (4A source).

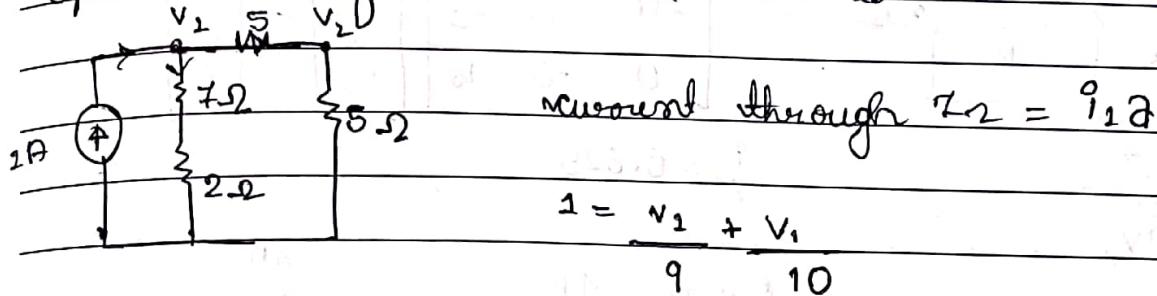

$$i_{1A} = \frac{V_1}{9} = 0.526 A.$$

Open the 1A

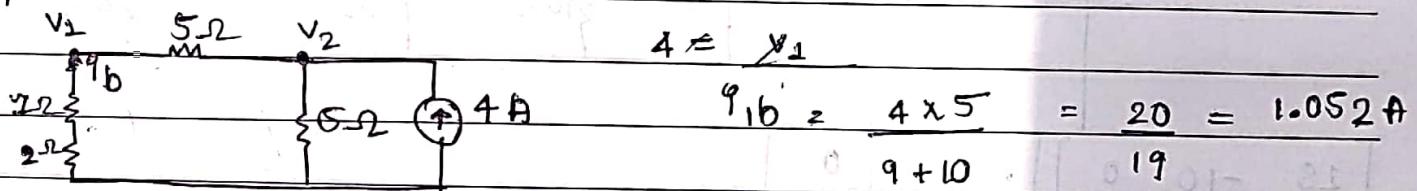

$$i_t = 1.052 + 0.526 = 1.579 A$$

$$4 - 3i_1 - 6(i_1 - i_2) = 0 \Rightarrow 4 - 9i_1 + 6i_2 = 0$$

$$-4i_2 - 6(i_2 - i_1) = 0 \Rightarrow -10i_2 + 6i_1 = 0$$

$$-9i_1 + 6i_2 = -4 \quad \times 10 \Rightarrow -90i_1 + 60i_2 = -40$$

$$6i_1 - 10i_2 = 0 \quad \times 6 \Rightarrow 36i_1 - 60i_2 = 0$$

$$-90i_1 + 60i_2 = -40$$

$$36i_1 - 60i_2 = 0$$

$$-54i_1 = -40$$


$$i_1 = 0.74$$

$$-6i_2 + 6i_2 = -4$$

$$6i_2 = 2.667$$


$$i_2 = 0.44 = 0.33$$

12th Oct' 19

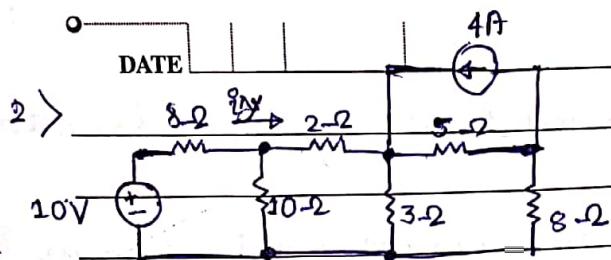

Use superposition theorem.

Due to 10 V

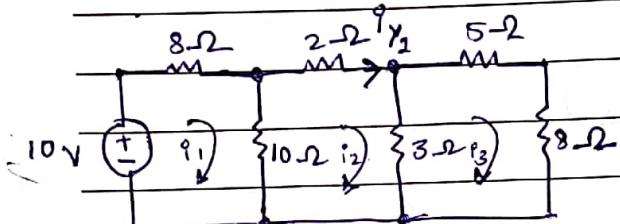


$$i_2 = 0.625$$

$$\frac{\Delta I_2}{\Delta} = I_2 = i_{y_2}$$


$$= \begin{vmatrix} 18 & 10 & 0 \\ -10 & 0 & -3 \\ 0 & 0 & 16 \end{vmatrix}$$

Due to 4A

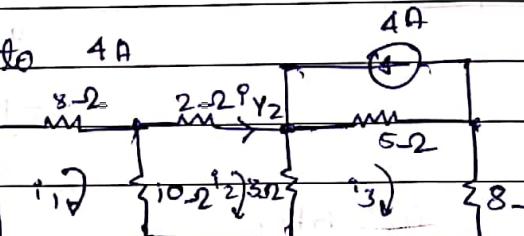

$\Rightarrow -\infty$


$$18 \quad -10 \quad 0$$

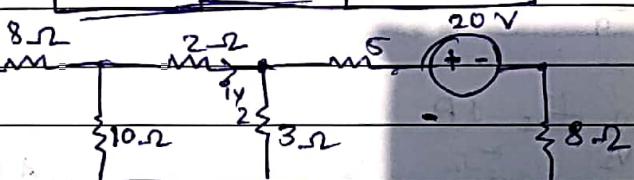

$$= \begin{vmatrix} 18 & -10 & 0 \\ -10 & 15 & -3 \\ 0 & -3 & 16 \end{vmatrix} \begin{Bmatrix} i_1 \\ i_2 \\ i_3 \end{Bmatrix} = \begin{Bmatrix} 0 \\ 0 \\ -20 \end{Bmatrix}$$

$$i_{y_2} = -0.457 \\ = p_{y_1} + p_{y_2}$$

$$i_y = 0.203 //$$

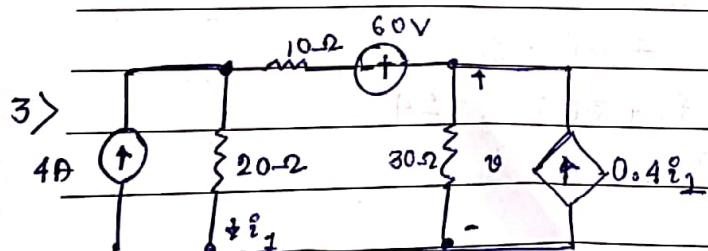


Use superposition theorem for finding

Due to 4A only:

KCL at node V_2 :

$$i_1 = \frac{V_2}{20}$$

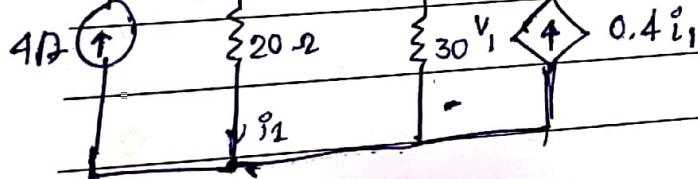

$$I = \frac{V_2}{20} + \frac{V_2 - V_1}{10}$$

$$4 = \frac{V_2}{20} + \frac{V_2 - V_1}{10} \\ 4 = \frac{3V_2}{20} - \frac{V_1}{10} \\ 80 = 3V_2 - 2V_1$$

DATE

$$\text{KCL at node } V_2 = \frac{V_1}{30} - \frac{V_2 - V_1}{10} + 0.4 \left(\frac{V_2}{20} \right)$$

$$\Rightarrow V_1 = \frac{V_2}{30} - \frac{V_1}{10} + \frac{V_2}{50}$$

$$\Rightarrow \frac{2}{15} V_1 = \frac{3 V_2}{25}$$


$$\therefore V_1 = \frac{3}{25} \times \frac{15}{2} V_2 = \boxed{\frac{9}{10} V_2 - V_1}$$

$$80 = 3 V_2 - 2 \left(\frac{9}{10} V_2 \right) \Rightarrow 80 = 3 V_2 - \frac{9}{5} V_2 \Rightarrow 80 = \frac{6}{5} V_2$$

$$V_2 = 66.667 \quad \times$$

$$V_1 = 60.0003$$

Due to 60 V

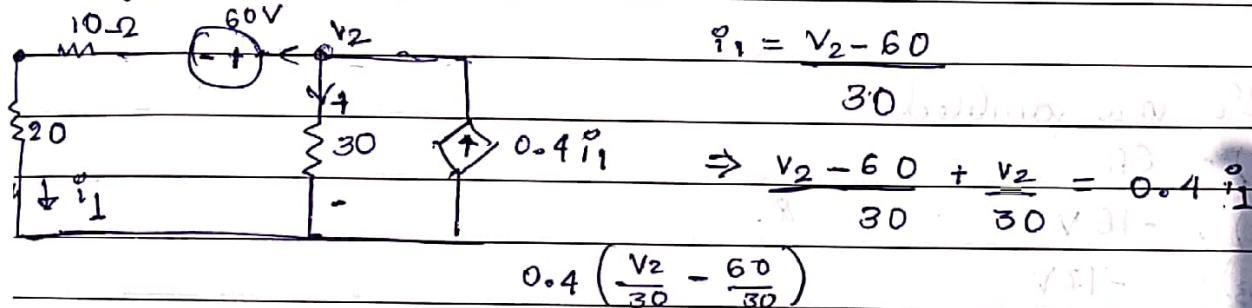

$$\Rightarrow \frac{V_2}{30} - 2 + \frac{V_2}{30} = 0.4 V_2 - \frac{4}{5}$$


$$\Rightarrow \frac{V_2}{15} - 0.4 \frac{V_2}{30} = 2 - \frac{4}{5}$$

$$\Rightarrow \frac{4}{75} V_2 = \frac{6}{5}$$

$$V_2 = \frac{6}{5} \times \frac{75}{4} = \frac{45}{2} = 22.5$$

$$V = V_1 + V_2 = 82.514 V$$

3Q

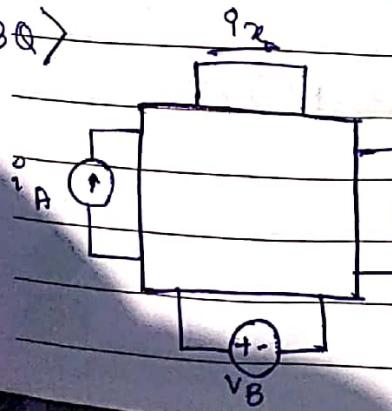i) With sources i_A & v_B on, $v_C = 0$, $i_x = 20A$ ii) With source i_A & v_C on, $v_B = 0$, $i_x = -5A$ iii) With all 3 sources on, $i_x = 12A$ iv) Find i_x if the only source operating is

- (a) i_A
- (b) v_B
- (c) v_C

DATE

doubled

Find i_x if i_A & v_c were obtained in magnitude & v_B is reversed.

Ans

$$i_x(i_A) + i_x(v_B) = 20A \rightarrow ①$$

$$i_x(i_A) + i_x(v_c) = -5A \rightarrow ②$$

$$i_x(i_A) + i_x(v_B) + i_x(v_c) = 12 \rightarrow ③$$

$$\Rightarrow 20 + i_x(v_c) = 12$$

$$\Rightarrow i_x(v_c) = -8A$$

$$i_x(i_A) - 8 = -5$$

$$i_x(i_A) = 3A$$

$$\Rightarrow 3 + i_x(v_B) - 8 = 12$$

$$\Rightarrow i_x(v_B) = 12 + 8 - 3 = 17$$

i_A & v_c were doubled

$$i_x(2i_A) = 6A$$

$$i_x(2v_c) = -16V$$


$$i_x(-v_B) = -17V$$

$$i_x(i_A) + i_x(v_B) + i_x(v_c) = 12$$

$$6 - 17 - 16$$

$$= -27$$

Q: 4)

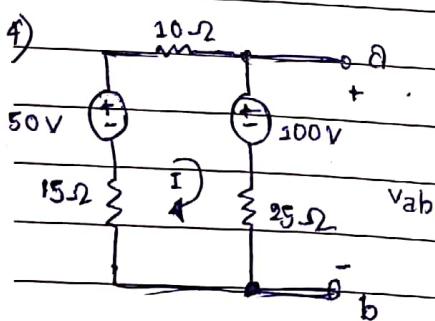

Find the Thevenin equivalent at terminals a & b.
How much power would be delivered to a resistor connected to a & b if R_{ab} equals
(a) 50Ω (b) 12.5Ω

$$(a) v_{th} = +v_{ab} - 100 - 25I - v_b = 0$$

$$v_{ab} = 100 + 25I$$

$$-15I + 50 - 10I - 100 - 25I$$

$$-50I - 50$$

$$-50I = 50 \quad I = -1$$

$$\begin{array}{l}
 \text{Circuit diagram: } \\
 \text{Top branch: } 10\Omega \text{ in series with } 15V \text{ DC voltage source} \\
 \text{Bottom branch: } 25\Omega \text{ resistor} \\
 \text{Right branch: } 12.5\Omega \text{ resistor} \\
 \text{Nodal analysis: } V_a = 15V, V_b = ? \\
 \text{Equations: } \\
 15 - 10\Omega I + 25\Omega (V_b - 15) = 0 \\
 15 - 12.5\Omega (V_b - 15) = 0 \\
 \Rightarrow 15 = 12.5(V_b - 15) \\
 \Rightarrow V_b = 12.5 + 15 = 27.5V
 \end{array}$$


$$\begin{array}{l}
 \text{Circuit diagram: } \\
 \text{Top branch: } 12.5\Omega \text{ resistor} \\
 \text{Bottom branch: } -75V \text{ DC voltage source} \\
 \text{Right branch: } 50\Omega \text{ resistor} \\
 \text{Nodal analysis: } V_a = -75V, V_b = ? \\
 \text{Equations: } \\
 -75 - 12.5\Omega I + 50\Omega (V_b + 75) = 0 \\
 -75 - 50\Omega (V_b + 75) = 0 \\
 \Rightarrow -75 = 12.5(V_b + 75) \\
 \Rightarrow V_b = -75 - 12.5 = -87.5V
 \end{array}$$

$$R_{ab} = 12.5\Omega$$

$$q_5 = 25i$$

$$i = 3$$

Find the corresponding

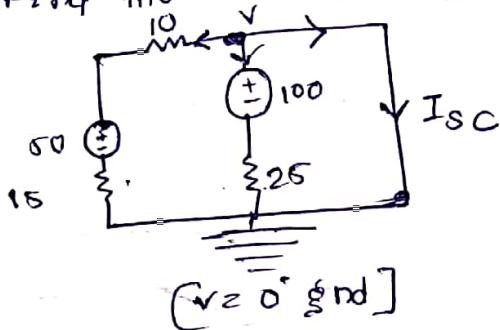


$$\begin{aligned}
 P &= (3)^2 \times 50 \cdot 12.5 \\
 &= 112.5
 \end{aligned}$$

Norton.

By nodal analysis
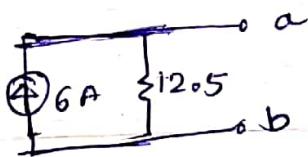
$$\begin{aligned}
 \frac{V-50}{25} + \frac{V-100}{25} &\neq I_{SC} = 0 \\
 \frac{V}{10} + \frac{V}{25} - 2 - 4 &= I_{SC} \Rightarrow \frac{7V}{50} - 9 = I_{SC} \\
 I_{SC} &= +6
 \end{aligned}$$



12th Oct '19

THEVENIN'S & NORTON'S THEOREM

DATE



a) → Remove load

- 1) Find the voltage across the AB = $V_{AB} = V_{Th}$
- 2) Zero the all independent sources & find the eq resistance across ab





NORTON's

short the the ab terminal




$$I_{SC} = I_N$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$

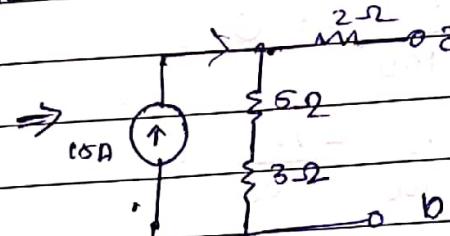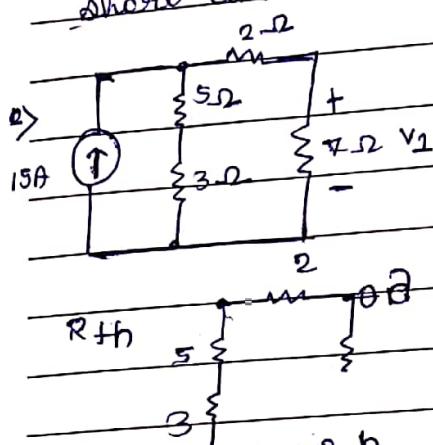


$$V_{Th} = (15)(8) = 120$$

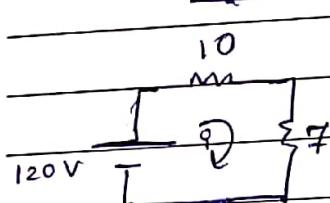

$$I = \frac{120}{17} = 7.058$$

$$V_{(7\Omega)} = 49.41$$

Norton

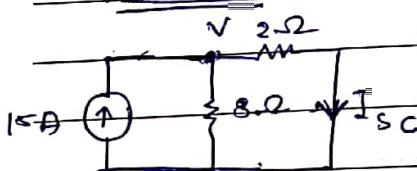


$$15 = \frac{V}{8} + \frac{V}{2} = \frac{120}{24} = 5V$$

$$V = 48.24$$



$$I_{SC} = \frac{24}{2} = 12$$

$$R_{Th} = 10$$

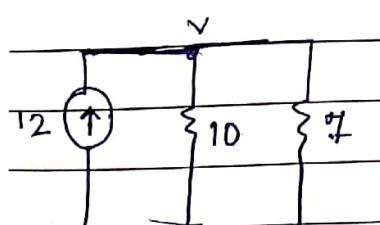

$$12 = \frac{V}{10} + \frac{V}{7}$$

$$V = 49.41$$

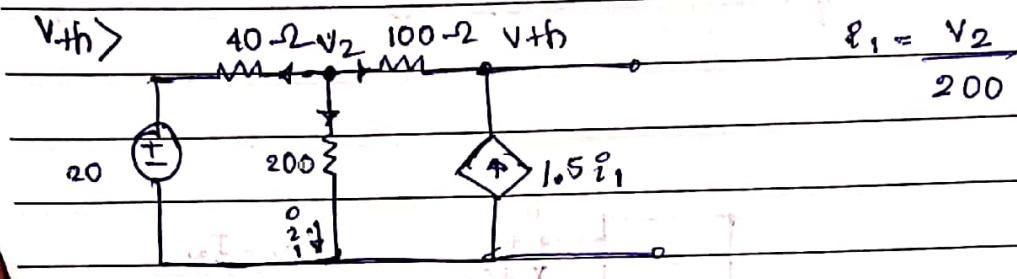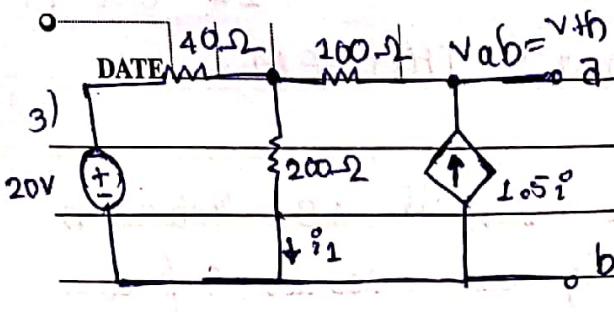

KCL at node V_2

$$\frac{V - 20}{40} + \frac{V_2}{200} + \frac{V_2 - V_{th}}{100} = 0$$

$$\frac{V_2 - 1}{40} + \frac{V_2}{200} + \frac{V_2}{100} - \frac{V_{th}}{100} = 0$$

$$\Rightarrow \frac{3}{100} V_2 - \frac{V_{th}}{25} = 0.5$$

KCL at node V_{ab}

$$\frac{V_2 - V_{ab}}{100} + 1.5 \left(\frac{V_2}{200} \right) = 0$$

$$\Rightarrow \frac{V_2}{100} + \frac{1.5}{200} V_2 - \frac{V_{ab}}{100} = 0$$

$$\Rightarrow \frac{7}{400} V_2 = V_{ab}$$

$$V_2 = \frac{400}{7 \times 100} V_{ab} = \frac{4}{7} V_{ab} = 22.22$$


$$\frac{4}{175} V_{ab} - \frac{1}{100} V_{ab} = 0.5$$

$$\frac{9}{700} V_{ab} = 0.5$$

$$V_{ab} = 38.889 //$$

$R+L$ in Cannot deactivate the Dependent

Special Case //

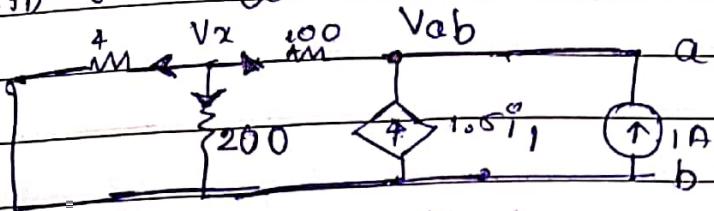

Supply variable voltage on current value find the current & voltage across it respectively assuming it to 1V & 1Ω.

KCL at V_x

$$\frac{V_x}{40} + \frac{V_x}{200} + \frac{V_x - V_{ab}}{100} = 0$$

$$I_1 = \frac{V_x}{200}$$

$$\frac{V_x - V_{ab}}{25} = 0$$

$$\frac{V_x}{25} = \frac{V_{ab}}{100}$$

$$V_{ab} = 4V_x$$

KCL at V_{ab}

$$\frac{V_x - V_{ab}}{100} + 1.5I_1 + 1 = 0$$

$$= \frac{V_x}{100} - \frac{V_{ab}}{100} + \frac{3}{4}V_x + 1 = 0$$

$$= \frac{7}{400}V_x - \frac{V_{ab}}{100} + 1 = 0$$

$$\frac{7}{1600}V_{ab} - \frac{V_{ab}}{100} + 1 = 0$$

$$\frac{7}{1600}V_{ab} = +1$$

$$9V_{ab} = 1600$$

$$V_{ab} = 177.77 \text{ V} = R+L$$

177.77


M

$$38.88 = 277.77 I$$

$$I = 0.1399$$

$$P = 1.96 \text{ W}_{\parallel}$$

14/10/19

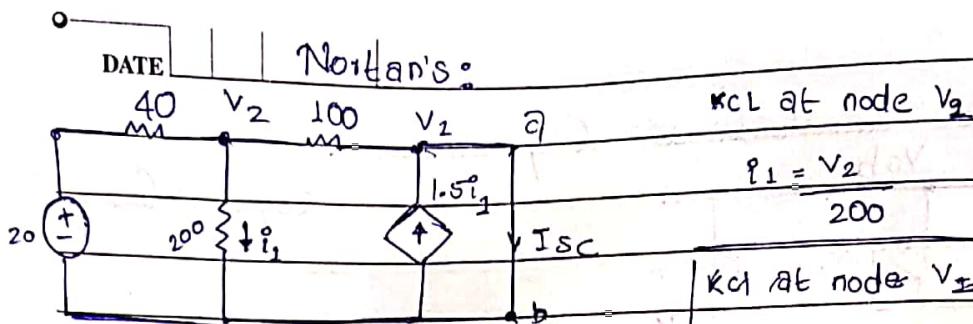

$$\frac{V_2 - 20}{40} + \frac{V_2 - 0}{200} + \frac{V_2 - V_1}{100} = 0$$

$$5V_2 - 100 + V_2 + 2V_2 - 2V_1 = 0$$

$$8V_2 - 2V_1 = 100$$

$$-4V_2 - V_1 = 50$$

$$V_1 = 0 \Rightarrow V_2 = 12.5$$

$$\frac{V_2 - V_1}{100} + \frac{1.5V_1}{200} = I_{SC}$$

$$\frac{V_2 - V_1}{100} + \frac{1.5V_2}{200} = I_{SC}$$

$$2V_2 - 2V_1 + 1.5V_2 = 200 I_{SC}$$


$$3.5V_2 = 200 I_{SC}$$

$$I_N = I_{SC} = 0.2187 A$$



$$R_{th} = R_N = 147.77 \Omega$$

when no independent sources in the ckt

$$V_{th} = 0 = V_N \text{ always}$$

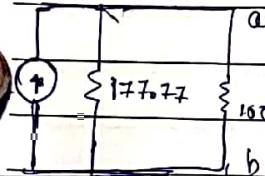

(a) R_N :

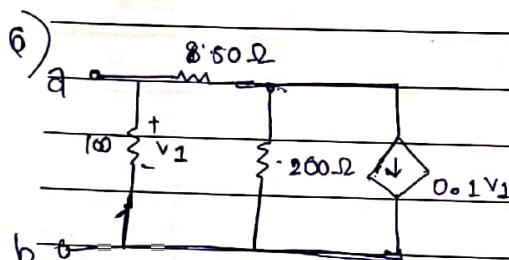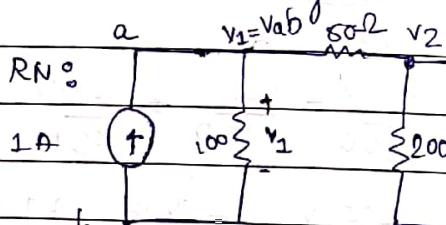

$$V_{ab} = 1 = \frac{V_1}{100} + \frac{V_1 - V_2}{50}$$

$$100 = V_1 + 2V_1 - 2V_2$$

$$100 = 3V_1 - 2V_2$$

node at V_2 :


$$\frac{V_1 - V_2}{50} = \frac{V_2 + 0.1V_1}{200}$$

$$50 = V_2 + 2V_1$$

$$16V_1 + 5V_2 = 0$$

$$V_1 = 10.638, V_2 = -34.64$$

$$R_{th} = R_N = 10.638 \Omega$$

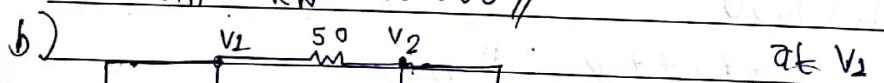

$$I_{SC} = \frac{V_1}{100} + \frac{V_1 - V_2}{50}$$

$$I_{SC} = \frac{3V_1 - 2V_2}{100} \approx 3V_1 - 2 \left(\frac{-16V_1}{5} \right)$$

at V_2 : $\frac{V_1 - V_2}{50} = \frac{V_2}{200} + 0.1V_1$

$$= 3V_1 + \frac{32V_1}{5} \approx 47V_1 = 180$$


$$16V_1 + 5V_2 = 0$$

$$V_1 = 0 \Rightarrow I_{SC} = 0$$

DATE

Equivalent vkt°

10.638

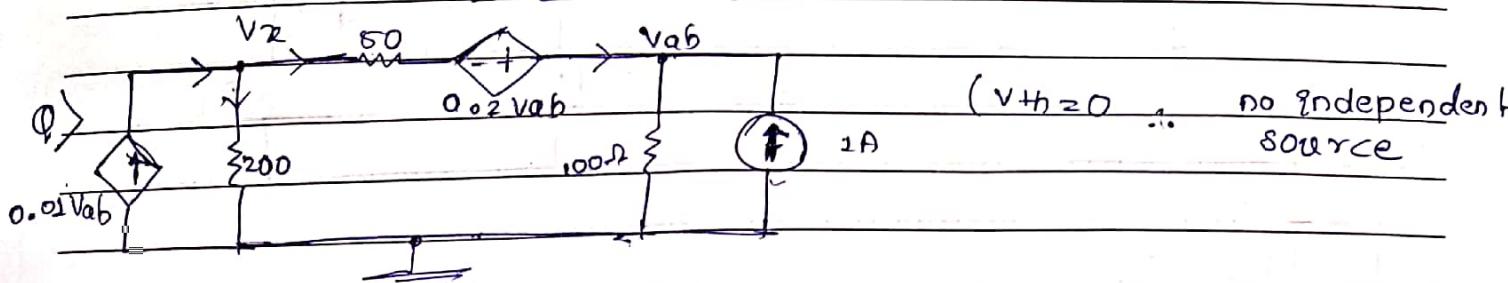KCL at node V_{ab}

$$\frac{0.02V_{ab}}{50} + \frac{V_x - V_{ab}}{100} + 1 = \frac{V_{ab}}{100}$$

$(V_{ab} = 0) \therefore$ no independent source

KCL at node V_{2p}

$$\frac{V_x}{200} + \frac{V_x - 0.02V_{ab} - V_{ab}}{50} = \frac{0.01V_{ab}}{50}$$

$$\frac{V_{ab}}{100} = 2 + \frac{V_x}{50} - 0.8V_{ab}$$

$$V_x + 4V_x - 3.2V_{ab} = 2V_{ab}$$

$$V_{ab} = 100 + 2V_x - 1.6V_{ab}$$

$$2.6V_{ab} = 100 + 2V_x$$

$$V_{ab} = 192.307V$$

$$V_x + 50 = 1.3V_{ab}$$

$$R_{th} = 192.307\Omega$$

$$5.2V_{ab} + 50 = 1.3V_{ab}$$

$$50 = (1.3 - 5.2)V_{ab}$$

$$50 = 0.26V_{ab}$$

MAX POWER TRANSFORM THEOREM

PURELY RESISTIVE LOAD

 R_s

$$I_L = V_s$$

$$P_L = I_L^2 R_L$$

$$R_s + R_L$$

$$P_L = \left(\frac{V_s}{R_s + R_L}\right)^2 R_L$$

Max power delivered

$$\frac{\partial P_L}{\partial R_L} = 0 \Rightarrow \frac{V_s^2 (R_s + R_L)^2 - V_s^2 R_L \cdot 2(R_s + R_L)}{(R_s + R_L)^4}$$

$$= V_s^2 (R_s + R_L)^2 = V_s^2 R_L^2 (2)(R_s + R_L)$$

$$R_s + R_L = 2 R_L$$


$$R_s = R_L //$$

DATE

2) PURELY RESISTIVE LOAD WITH SOURCE IMPEDANCE

$$I_L = \frac{V_s}{(R_s + R_L) + jX_s}$$

$$(R_s + R_L) + jX_s$$

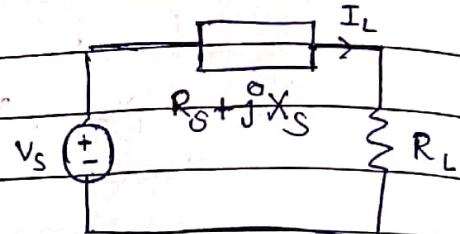

$$|I_L| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + X_s^2}}$$

$$\sqrt{(R_s + R_L)^2 + X_s^2}$$

$$P_L = |I_L|^2 R_L$$

$$= \frac{V_s^2 R_L}{(R_s + R_L)^2 + X_s^2}$$

$$= \frac{V_s^2 R_L}{(R_s + R_L)^2 + X_s^2}$$

$$(R_s + R_L)^2 + X_s^2$$

$$\frac{dP_L}{dR_L} = 0 \Rightarrow \frac{V_s^2 [(R_s + R_L)^2 + X_s^2] - V_s^2 R_L [2(R_s + R_L)]}{[(R_s + R_L)^2 + (X_s)^2] j^2}$$

$$V_s^2 [(R_s + R_L)^2 + X_s^2] = V_s^2 R_L [2(R_s + R_L)]$$

$$R_s^2 + R_L^2 + 2R_s R_L + X_s^2 = 2R_s R_L + 2R_L^2$$

$$R_s^2 = R_L^2 - X_s^2$$

$$R_s^2 + X_s^2 = R_L^2$$

$$R_L = \sqrt{R_s^2 + X_s^2}$$

(c) VARIABLE LOAD IMP WITH SOURCE IMPEDANCE

$$I_L = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$|I_L| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}$$

$$P_L = |I_L|^2 R_L$$

$$= \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

$$(R_s + R_L)^2 + (X_s + X_L)^2$$

Assume $R_L = K$: ($\because R_L \propto X_L$ both variables)




$$\frac{dP_L}{dX_L} = 0 \Rightarrow \frac{V_s^2 [(R_s + R_L)^2 + (X_s + X_L)^2] - V_s^2 R_L [2(R_s + R_L)]}{[(R_s + R_L)^2 + (X_s + X_L)^2]^2}$$

$$\Rightarrow R_L^2 (R_s + R_L) = (R_s + R_L)^2 + (X_s + X_L)^2$$

$$2R_L R_s + R_L^2 = R_s^2 + R_L^2 + 2R_s R_L + (X_s + X_L)^2$$


$$R_L^2 = R_s^2 + (X_s + X_L)^2$$

DATE

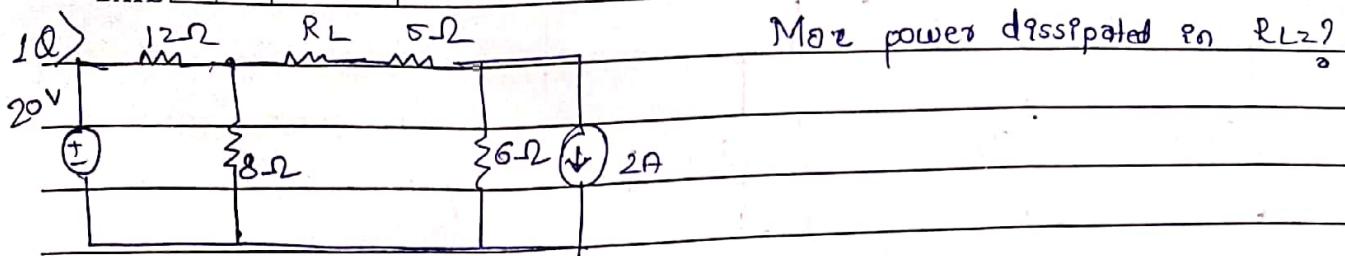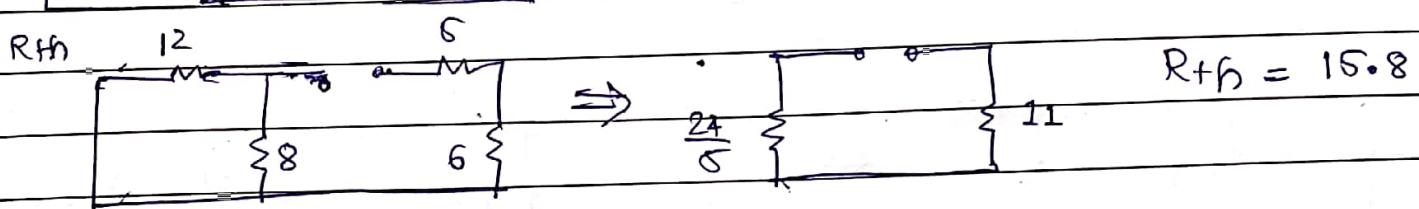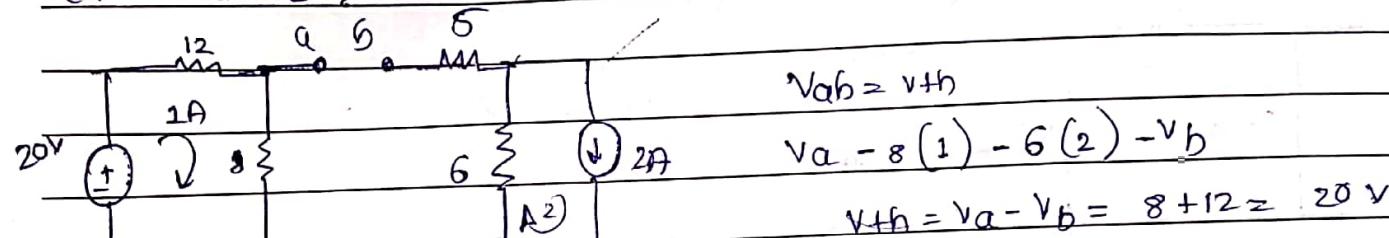Q1) Find R_{th} ?

Q2) Thevenin equivalent = ? Max power = ?

$$i_{10} = 5A \quad (\text{open circuit})$$

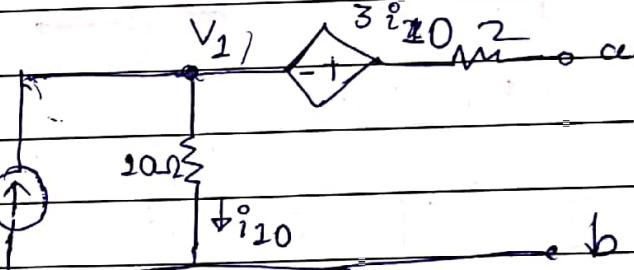
Node V_1 

$$5 = 5 + \frac{V_1 + 3i_{10} - V_a}{2}$$

$$V_1 + 15 - V_a = 0$$

$$(10)(5) + 15 = V_a$$

$$V_a = 65$$

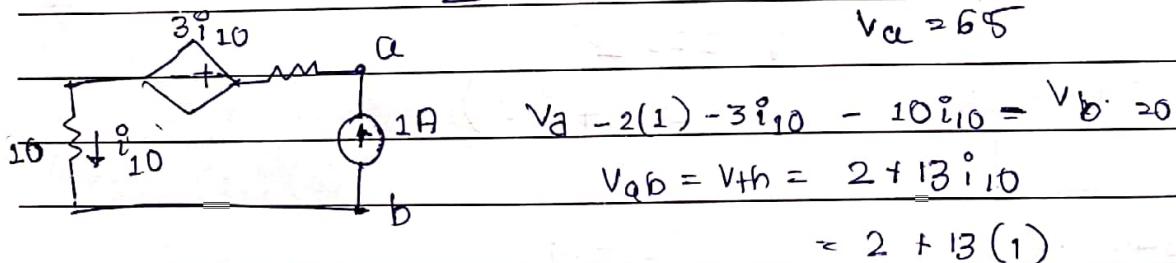

$$V_{ab} = 15$$




$$R_{ab} = 15$$

Thevenins :

$$R_{th} = R_{ab} = 15$$


$$P = I^2 R_L$$
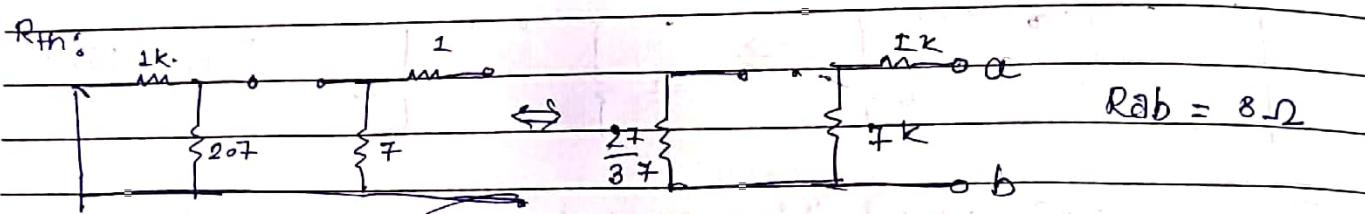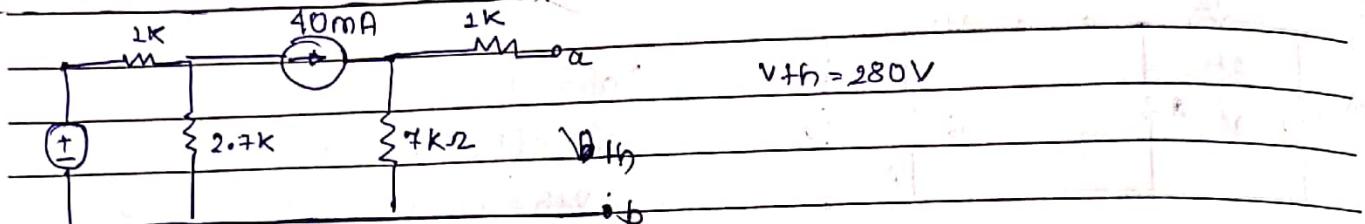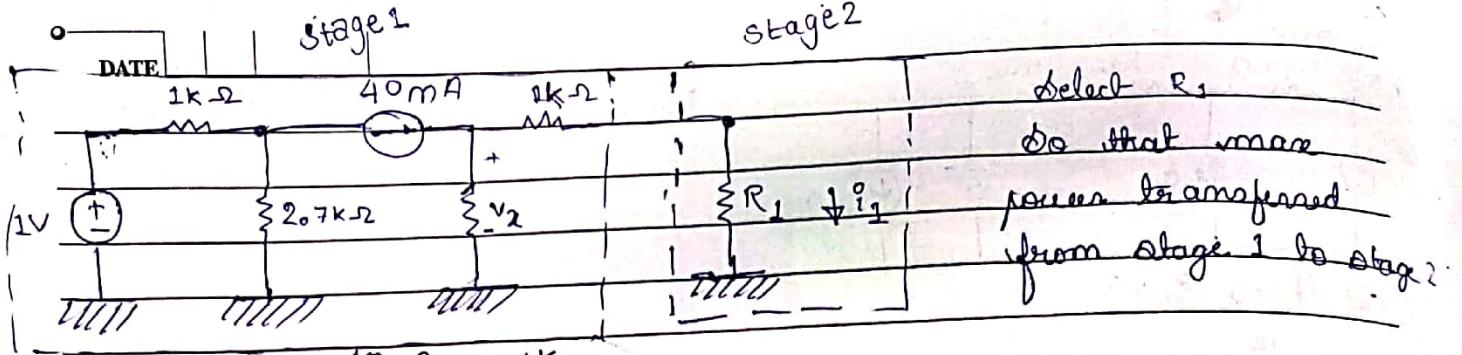
$$= 15 \times \left[\frac{13}{6} \right]^2 = 70.42W$$



$$R_L = R_{ab} = 8\text{k}\Omega$$
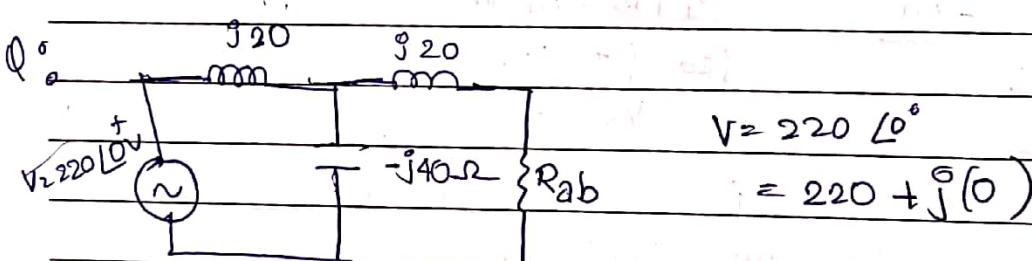
$$\frac{280}{8} = 17.5 \quad i = \frac{280}{16} = 17.5 \quad P_8 = i^2 (8) \text{W} \\ \approx 2450\text{mW}$$



$$V_{th} = ? \Rightarrow (-j40)(\frac{i}{220}) \quad i = \frac{j20 - j40}{220}$$

$$V_{th} = -j(40) (11) = \frac{-j(20)}{220}$$

$$= 40 \times 11 = 440V$$

$$\frac{i}{i} = -\frac{j}{11} \quad i = \frac{-11 \times j}{j \times j} \Rightarrow i = 11j$$

Z_{th} :


$R_{th} = \frac{j20 \times (-j40)}{j20 + (-j40)} = \frac{800 \times j}{j(-20) + j}$

DATE


$$Z_{in} = 40j + j20 = 60j$$

$$R_L = \sqrt{60^2} = 60\Omega$$
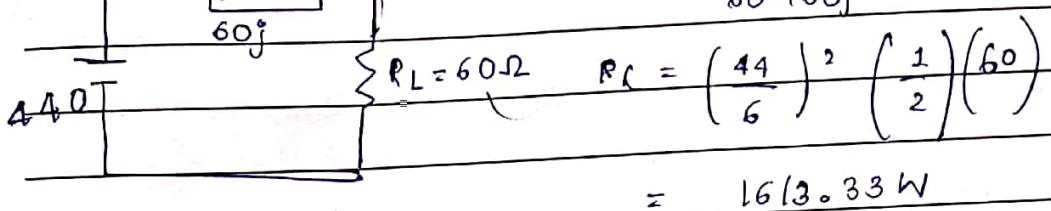
$$P_L = \frac{440}{60 + 60j} = \frac{440}{60(1+j)} = \frac{440}{60\sqrt{2}}$$



$$R_6 = 5$$

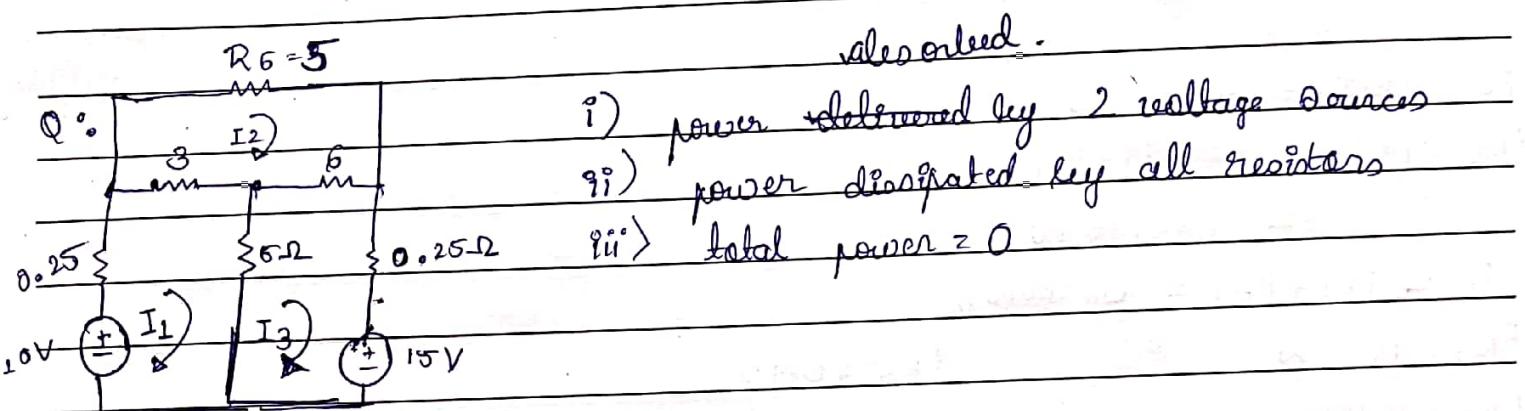

8.25	-3	-5	I_1	10	$\dot{q}_1 = -0.283A$, $= IR_1$
-3	14	-6	I_2	0	$\dot{q}_2 = -0.889A$
-5	-6	11.25	I_3	-15	$\dot{q}_3 = -1.933A$, $= 0.609A$

$$\text{i) (a)} P_{E1} = (+10)(+I_1) = (-10)(-0.283) = 2.83$$

$$\text{ii) } P_{E2} = (-15)(-1.933) = 28.995 \text{ (supplied)} \quad (\text{dissipated} \rightarrow -28.995)$$

$$\text{iii) } PR_1 = -(I_1)^2 R_1 = +0.02$$

$$PR_2 = -(I_1 - I_2)^2 R_2 = -8.167W$$

$$PR_3 = (I_3)^2 R_3 = +8.68W$$

$$PR_4 = (I_3 - I_2)^2 R_4 = +6.54W$$

$$PR_5 = (I_3)^2 R_5 = +0.934W$$

$$PR_6 = (I_2)^2 R_6 = -3.9516$$

$$P_{E1} + P_{E2} = 26.16$$

$$\text{Total power} = 2.83 + 28.995 - 0.02 - 8.167 - 8.68 - 6.54 - 0.934 - 3.9516.$$

DATE

$$I_1 = -0.2829 \text{ A} = IR_1$$

$$I_{R4} = -1.044 \text{ A}$$

$$I_{R2} = 0.609 \text{ A}$$

$$I_{R5} = I_2 = -1.933 \text{ A}$$

$$I_{R3} = 1.653 \text{ A}$$

$$I_3 = I_{R6} = -0.889 \text{ A}$$

In any ckt the algebraic sum of power supplied (instantaneous or complex power) & power absorbed by passive elements is Zero.

This is Tellegen's Theorem.

$$\Phi E_1 = 10 I_1 = -2.829 \text{ W}$$

$$\Phi E_2 = 15 I_2 = -28.995 \text{ W} \quad (\text{also}) \\ = 28.995 \text{ W}$$

$$P_E = P_E_1 + P_E_2 = 26.166 \text{ W} //$$

$$P_{R1} = 0.02 \text{ W}$$

$$P_{R5} = 0.934 \text{ W}$$

$$P_{R2} = 1.101 \text{ W}$$

$$P_{R6} = 3.95 \text{ W}$$

$$P_{R3} = 13.6125 \text{ W}$$


$$P_E - P_R = 0$$

$$P_{R4} = 6.539 \text{ W}$$


$$P_R = 26.166 \text{ W} //$$

$$P_E = P_R$$

Find Thevenin's equivalent for ckt shown

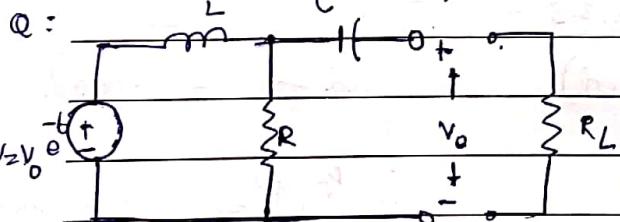


If L, C were there convert into S domain

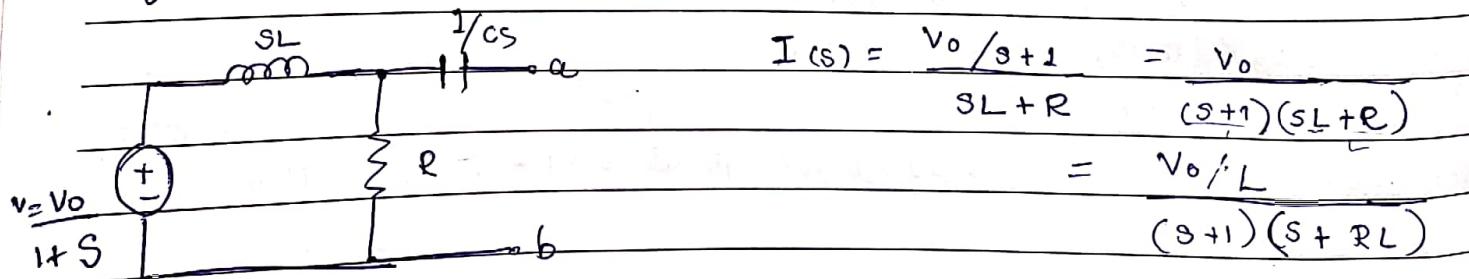

$$V_\theta = R I(s) = \frac{v_o R}{L(s+1)(s+RL)} = V_{th}$$

DATE

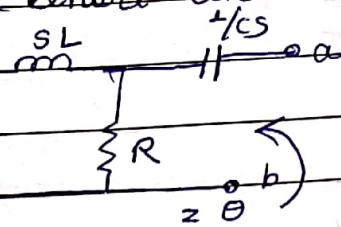 R_{th} , (short the source)

$$Z_\theta = (S L || R) + \frac{1}{C_S}$$

$$= \text{Reqt} \cdot \frac{S L R}{S L + R} + \frac{1}{C_S}$$

$$= C_S^2 L R + S L + R$$



$$= C_S^2 L + C_S R$$

$$= \frac{S C L R + L + R / S}{C S L + C R}$$

$$= \frac{S C R + 1 + R / S L}{C S + C R / L}$$

$$= \frac{R (S C + 1 / R + 1 / S L)}{C (S + R / L)}$$

Eqvt %

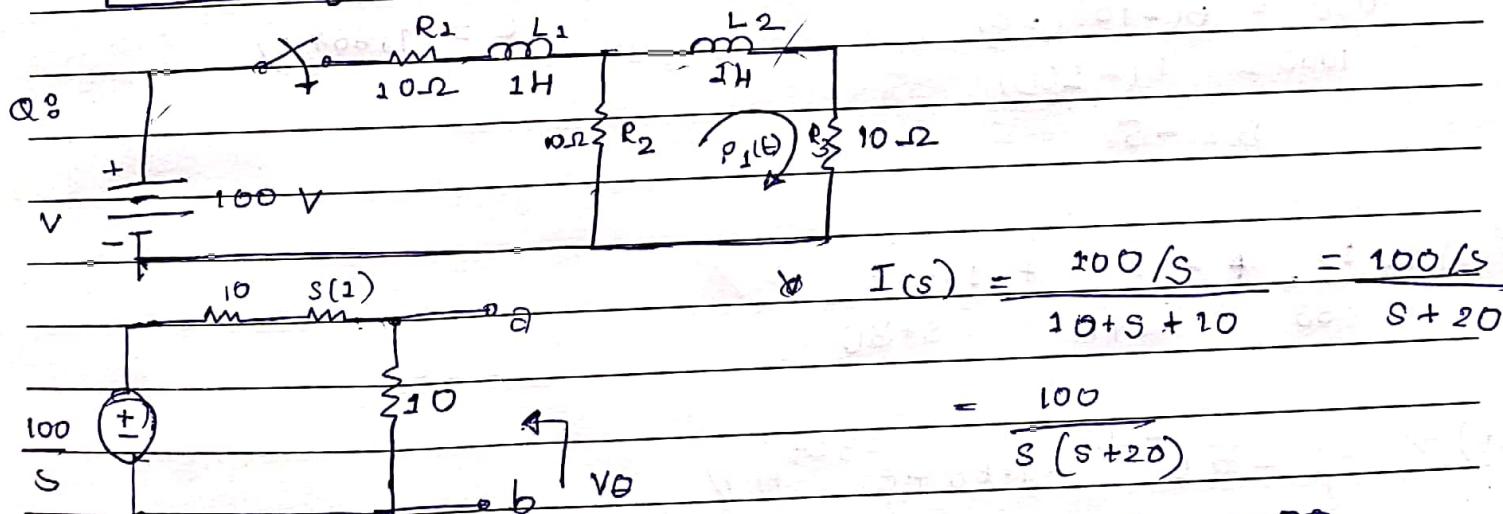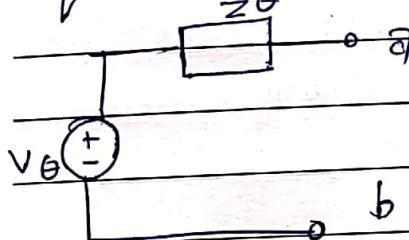

$$I(s) = \frac{100 / s}{10 + s + 10} = \frac{100 / s}{s + 20}$$

$$= \frac{100}{s(s+20)}$$


$$V_\theta = 10 I(s) = \frac{1000}{s(s+20)}$$

$$Z_\theta = 10 + s || 10$$

$$\frac{1}{Z_\theta} = \frac{1}{10+s} + \frac{1}{10} \Rightarrow \frac{10 + 10 + s}{100 + 10s} = \frac{20 + s}{100 + 10s}$$

$$Z_\theta = \frac{100 + 10s}{20 + s}$$

$$I_2(s) = \frac{1000}{s(s+20)}$$

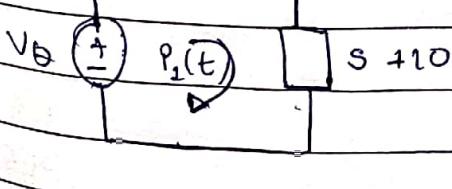

$$= \frac{100 + 10s + s + 10}{20 + s}$$

$$= 100 + 10s + 20s + 200 + s^2 + 10s$$

DATE

$$= \frac{1000}{s(s+10)} \times \frac{300 + 40s + s^2}{300 + 40s + s^2} = \frac{20 + s}{300 + 40s + s^2}$$

$$= \frac{1000}{s(s+10)(s+30)} = \frac{A}{s} + \frac{B}{s+10} + \frac{C}{s+30}$$

Put $s=0$

$$1000 = A(s+10)(s+30) + B(s)(s+30) + C(s)(s+10)$$

Put $s=0$

$$1000 = A(10)(30)$$

$$1000 = A(300)$$

$$A = \frac{10}{3}$$

Put $s+10=0$

$$1000 = B(-10)(20)$$

$$1000 = B(-200)$$

$$B = -5$$

Put $s+30=0$

$$1000 = C(10)(20)$$

$$1000 = C(600)$$

$$\frac{10}{3} = C$$


$$C = 1.667$$

$$i(s) = \frac{10}{3s} - \frac{5}{s+10} + \frac{1.667}{s+30}$$


$$i_1(t) \Rightarrow \frac{10}{3} - 5e^{-10t} + 1.667e^{-30t} A/$$

Ans.

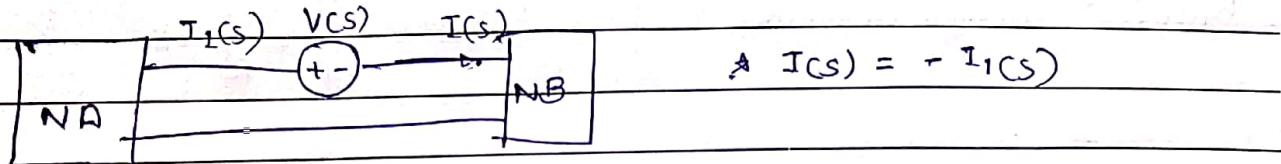- General elements
- Independent & dependent
- Initial conditions passive elements
- b
- A: Linear, nonlinear, time varying
- Ide / Dependent
- Initial conditions on passive elements
- No magnetic / controlled-source coupling to network A




Current is Zero

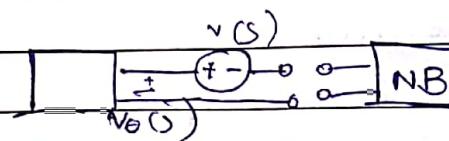

* The voltage at broken terminal is Zero
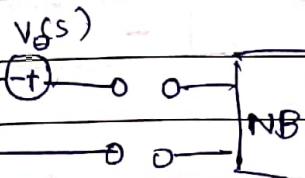
$$\text{By KV } L \quad v_{\theta}(s) = v(s)$$




* all independent sources are reduced to C

* Dependent sources are not changed

* NA is transformed into Network C

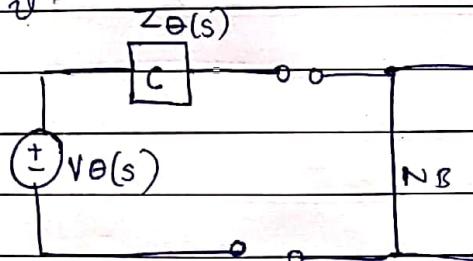* $v_{\theta}(s)$ polarity is reversed so that when connected to B, flow through it.




Thevenin eq network

* If $z_B(s)$ is the impedance of B, then the current is


$$I(s) = \frac{v_{\theta}(s)}{z_{\theta}(s) + z_B(s)}$$

Voltage of network B
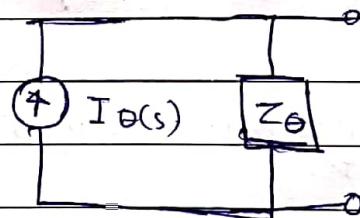
$$V_B(s) = \frac{I_{\theta}(s)}{Y_{\theta}(s) + Y_B(s)}$$



ENERGY & POWER

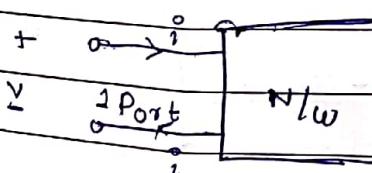

$$P(t) = v(t) \cdot i(t) \quad \text{Instantaneous power (absorbed)}$$

$$W(t) = \int_{t_1}^{t_2} P(t) dt \rightarrow \text{Energy absorbed}$$

② Resistor: $v = IR \rightarrow (1)$

(a) Instantaneous power = $v(t) \cdot i(t)$

$$= i^2(t) R / \frac{v^2(t)}{R} \quad \text{absorbed}$$

DATE

b) $W_R(t) \rightarrow$ energy absorbed = $\int_{t_1}^{t_2} i^2(t) R dt = \int_{t_1}^{t_2} \frac{v^2(t)}{R} dt$

c) For sinusoid: $i(t) = I_m \sin \omega t$

Instantaneous power = $P(t) = v(t) \cdot i(t)$

$$= i^2(t) R$$

$$= I_m^2 R s^2 \omega t = \boxed{\frac{I_m^2 R}{2} [1 - \cos 2\omega t]}$$

opt

$$\text{Energy} = \int_0^T P(\tau) d\tau$$

$$= \int_0^T \frac{R I_m^2}{2} [1 - \cos 2\omega \tau] d\tau = \frac{R I_m^2}{2} \int_0^T (1 - \cos 2\omega \tau) d\tau$$

$$= \frac{R I_m^2}{2} \left(t - \frac{\sin 2\omega t}{2\omega} \right) \rightarrow \boxed{\frac{R I_m^2}{2} \left(T - \frac{\sin 2\omega T}{2\omega} \right)}$$

d) Average power = $P_{av} = \frac{1}{nT} \int_0^{nT} P(\tau) d\tau$

$$= \frac{1}{nT} \int_0^{nT} \frac{R I_m^2}{2} [1 - \cos 2\omega \tau] d\tau = \frac{R I_m^2}{2nT} \left[\tau - \frac{\sin 2\omega \tau}{2\omega} \Big|_0^{nT} \right]$$

$$= \frac{R I_m^2}{2nT} \left[nT - \frac{\sin 2\omega nT}{2\omega} \right] = \frac{R I_m^2}{2} \left[T - \frac{\sin 2\omega T}{2\omega} \right] = 0 \quad \text{for any value of } n$$

$$\boxed{\frac{R I_m^2}{2}}$$

e) Average Energy / cycle = $\int_0^{nT} \frac{R I_m^2}{2} [1 - \cos 2\omega \tau] d\tau$

$$= \frac{R I_m^2}{2} \left[T - \frac{\sin 2\omega T}{2\omega} \right] = \boxed{\frac{R I_m^2}{2} T}$$

always power absorbed

DATE

② INDUCTANCE $\therefore v = L \frac{di}{dt} \rightarrow ①$

a) Instantaneous power $P_L(t) = V(t) \cdot i(t)$
 $= i(t) \cdot L \frac{di}{dt}$

b) Energy $\therefore w_L(t) = \int_{t_1}^{t_2} P_L(t) dt = \int_{t_1}^{t_2} i(t) L \frac{di}{dt} dt = i(t) \frac{L^2 i^2}{2} \Big|_{t_1}^{t_2}$

$$= \frac{L}{2} \left[i^2(t_2) - i^2(t_1) \right]$$

c) For a sinusoid $\therefore i(t) = I_m \sin \omega t$

Instant power $= i(t) \frac{di(t)}{dt} = L I_m \sin \omega t (I_m \omega \cos \omega t)$
 $= L I_m^2 \omega \sin \omega t \cos \omega t$

$$\therefore P_L(t) = \frac{L I_m^2 \omega \sin(2\omega t)}{2}$$

(d) Gross Energy $w_L(t) = \frac{1}{2} L i^2(t)$

$$= \frac{1}{2} L I_m^2 \sin^2 \omega t$$

$$= \frac{1}{4} L I_m^2 [1 - \cos 2\omega t]$$

(e) Average Power (A) $\therefore P_{avg} = \frac{1}{nT} \int_0^{nT} P_L(t) dt$

$$= \frac{1}{nT} \int_0^{nT} \frac{L I_m^2 \omega \sin(2\omega t)}{2} dt$$

$\cos 2x \frac{2\pi}{T} \times nT$

periodic signal, integrating goes to zero

$$\boxed{P_{avg} = 0}$$

(*) Average Energy/cycle = Zero



DATE

3) CAPACITANCE: $i(t) = C \frac{dv(t)}{dt} \rightarrow ①$

a) Instant Power $P_c(t) = i(t)v(t)$
 $= v(t)C \frac{dv(t)}{dt}$

b) Energy $w_c(t) = \int_{t_1}^{t_2} P_c(z) dz$
 $= \int_{t_1}^{t_2} v(z)C \frac{dv(z)}{dz} dz$
 $= C \left[\frac{v^2(z)}{2} \right]_{t_1}^{t_2} = \boxed{\frac{1}{2} C [v^2(t_2) - v^2(t_1)]}$

c) For a Sinusoid:

$v(t) = V_m \sin \omega t$

d) Instant power: $\sim P_c(t) = v(t)i(t)$
 ~~$= C V_m \sin \omega t \cdot V_m \omega \cos \omega t$~~
 $= C V_m^2 \omega \sin(\omega t)$
 $= \frac{1}{2} C V_m^2 \omega \sin(2\omega t)$

e) Energy: $\frac{1}{2} C V^2(t) = \frac{1}{2} C V_m^2 \sin^2 \omega t = \boxed{\frac{1}{4} C V_m^2 [1 - \cos 2\omega t]}$

f) Average Power:

$P_{avg} = \frac{1}{nT} \int_0^{nT} P_c(z) dz = \frac{1}{nT} \int_0^{nT} \frac{1}{2} C V_m^2 \omega \sin 2\omega t dt$
 $= 0$

g) Average Energy = 0

DATE

EFFECTIVE / RMS VALUES

The effective / RMS value of a periodic current is that steady DC current that will produce same power in a resistor as produced on an average by the periodic current for the same time.

Let the steady current = I

$$P = I^2 R$$

$$\text{Now, } P_{av} = \frac{1}{T} \int_0^T I_m^2 R dt = I^2 R$$

$$I = \frac{I_m}{\sqrt{2}} = I_{rms} = I_{eff}$$

By	$V_{rms} = V_{eff} = \frac{V_m}{\sqrt{2}}$
----	--

$$\begin{aligned} \text{Average Power} &= I_{rms}^2 R \\ &= \frac{V_{rms}^2}{R} \end{aligned}$$

$$P_{av} = I_{eff} \times V_{eff}$$

The RMS value of a non sinusoidal but periodic current of period T is given by

$$P_{av} = \frac{1}{T} \int_0^T R i^2(t) dt$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$V_{eff} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

POWER FACTOR

$$P_{av} = I_{rms}^2 R = I_{eff} V_{eff}$$


$$Z(j\omega) = R + jX(j\omega)$$

$$Z(s) = R + jX(s)$$

$$P_{av} = I_{rms}^2 R \operatorname{Re}\{z(j\omega)\}$$

$$I^2 R \operatorname{Re}\{z(j\omega)\}$$
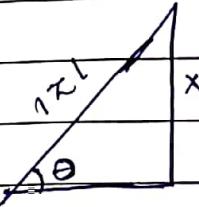
$$I^2 R \operatorname{Re}\{z(j\omega)\}$$



$$\frac{R}{|Z|} = \cos \theta$$

$$R = |Z| \cos \theta$$

$$\theta = \tan^{-1} \left(\frac{X(j\omega)}{R} \right)$$

DATE

- * Power factor is the cosine of angle of impedance
- * Power factor is also the cosine of the angle between V_E, I .

$$Ex: If V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \theta) \text{ leads } \theta \parallel$$

If i leads v , power factor is leading