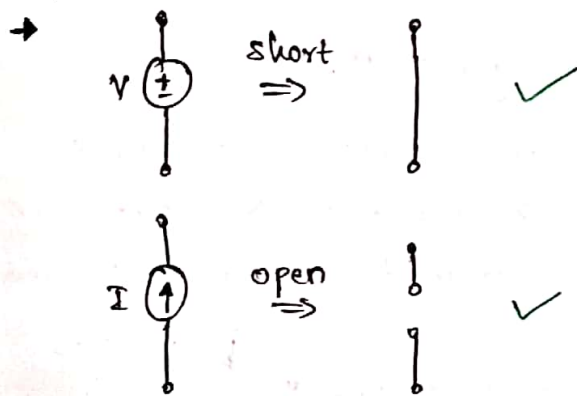


# NAS: NETWORK THEOREMS

## \* Superposition Theorem

In any linear resistive network, the voltage across or the current through any resistor or source may be calculated by adding algebraically all the individual voltages or currents caused by the separate independent sources acting alone, with all other independent voltage sources replaced by short circuits and all other independent current sources replaced by open circuits.



## \* Thevenin's theorem


### Steps

- (i) Find thevenin's resistance  $R_{th}$  by removing all voltage sources and open circuiting current sources. (don't consider the load resistor  $R_L$ )
- (ii) Find thevenin's voltage by plugging in the voltages, i.e. measure the open circuit voltage  $V_{th}$ .
- (iii) Use the  $R_{th}$  and  $V_{th}$  to find current through load resistor  $R_L$

## \* Norton's theorem


### Steps

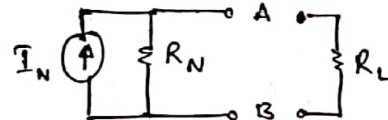- (i) Short the load resistor
- (ii) Measure the short circuit currents, it's the Norton current ( $I_N$ )
- (iii) Measure the open circuit resistance, i.e. Norton Resistance ( $R_N$ )
- (iv) Now, redraw the circuit, with  $R_N$  parallel with  $I_N$



- (v) Now, calculate load current  $I_L$  using current divider rule.
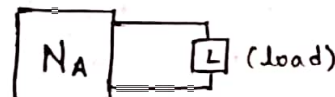
## \* Maximum power transfer theorem - Consider the general network,



Let resistor in  $N_A$  be  $Z_s$  and load resistor is  $R_L$

case 1:  $Z_s$  is non-complex (pure)  
 $R_L$  is non-complex (pure)

i.e.  $Z_s = R_s$

For maximum power transfer

$$R_L = R_s$$

$$P_{max} = \frac{V^2}{4R_L}$$

case 2:  $Z_s$  is complex and  $R_L$  is pure load

i.e.  $Z_s = R_s + jX_s$

For maximum power transfer

$$R_L = \sqrt{R_s^2 + X_s^2} \quad \text{i.e. } R_L = |Z_s|$$

$$P_{max} = \frac{V^2}{4\sqrt{R_s^2 + X_s^2}}$$

case ③:  $Z_s$  is complex and  $R_L$  is complex.

i.e.  $Z_s = R_s + jX_s$

$R_L = R_s + jX_s$

⑦ For maximum power transfer

$$R_L = Z_s^*$$

i.e.  $R_L + jX_L = R_s - jX_s$

$R_L = R_s$   
 $X_L = -X_s$

$$P_{\max} = \frac{V^2}{4 \sqrt{R_s^2 + X_s^2}}$$

### \* Reciprocity theorem

"In a linear network, if the position of the excitation and response are interchanged, their ratio remain unchanged"

⇒ conditions in order to apply this theorem

(i) The circuit must have a single source

(ii) Initial conditions are assumed to be zero or absent in the circuit

(iii) Dependent sources are excluded even if they are linear

(iv) When the position of source and response are interchanged, their directions should be marked same as in the original circuit.

### ⑧ Millman's theorem

- Applicable for multiple voltage source connected in parallel.
- It is used to convert multiple voltage source in parallel into a single voltage source.


#### Steps

- Convert all voltage source into current source  $I = V/R$
- Combine these current sources ( $I_{eq}$ )
- Find the resultant resistance ( $R_{eq}$ )
- Convert resulting current source into voltage source, series with  $R_{eq}$  ( $I_{eq} R_{eq} = V_{eq}$ )


### \* Tellegen's theorem

"In any electrical network which satisfies Kirchhoff's laws, the summation of instantaneous power in all the branches is equal to zero"

Note ① Power is +ve if current is coming out of +ve terminal

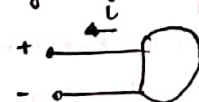$P = +ve$  if 

② Power is -ve if current is entering into the +ve terminal

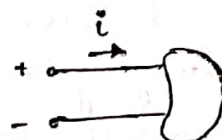$P = -ve$  if 



## ④ Energy (Work) and Power

In general, 
$$W = \int_{t_1}^{t_2} v(t) i(t) dt$$

$$P = \frac{dW}{dt} = v(t) i(t)$$

⇒ For a resistor, with  $i = I_m \sin \omega t$

$$W_R = \frac{R I_m^2}{2} \left( t - \frac{\sin 2\omega t}{2\omega} \right)$$

$$P_R = \frac{R I_m^2}{2} (1 - \cos 2\omega t)$$

⇒ For a inductor, with  $i = I_m \sin \omega t$

$$W_L = \frac{L I_m^2}{4} (1 - \cos 2\omega t)$$

$$P_L = \frac{L I_m^2}{2} \omega \sin 2\omega t$$

⇒ For a capacitor, with  $i = I_m \sin \omega t$   
 $v = V_m \sin \omega t$

$$W_C = \frac{C V_m^2}{4} (1 - \cos 2\omega t)$$

$$P_C = \frac{C V_m^2}{2} \omega \sin 2\omega t$$

□ For non-sinusoidal but periodic current  $i(t)$

$$\Rightarrow P_{avg} = \frac{1}{T} \int_{t_0}^{t_0+T} R i^2(t) dt$$

$$\Rightarrow I_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} i^2(t) dt} = I_{rms}$$

$$\Rightarrow V_{eff} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v^2(t) dt} = V_{rms}$$

## ④ Additional points.

⇒ Complex power

$$\text{If } V = V_m e^{i\theta_v} = V_m \angle \theta_v$$

$$I = I_m e^{i\theta_i} = I_m \angle \theta_i$$

$$\therefore Z = \frac{V}{I} = \frac{V_m}{I_m} \angle \theta_v - \theta_i$$

$$\Rightarrow \boxed{Z = |Z| \angle \theta}$$

Here power factor is

$$\boxed{P.F. = \cos \theta}$$

⇒ pharor power or apparant power (S)

$$\boxed{S = \frac{1}{2} V I^*}$$

→ Reactive power (Q)

$$\boxed{Q = V_{rms} I_{rms} \sin \theta}$$

Note: When  $V = V_m \sin \omega t$ ,

→ P.F is leading if

$$\boxed{I = I_m \sin (\omega t + \theta)}$$

→ P.F is lagging if

$$\boxed{I = I_m \sin (\omega t - \theta)}$$

# NAS : Two Port Networks

## \* TABLE - 1

⇒ Two port parameters

Name	Functions		Equations
	Express (Dep)	In terms of (Indep)	
1) Z-parameters (open-circuit impedance)	$V_1, V_2$	$I_1, I_2$	$V_1 = Z_{11} I_1 + Z_{12} I_2$ $V_2 = Z_{21} I_1 + Z_{22} I_2$
2) Y-parameters (short-circuit impedance)	$I_1, I_2$	$V_1, V_2$	$I_1 = Y_{11} V_1 + Y_{12} V_2$ $I_2 = Y_{21} V_1 + Y_{22} V_2$
3) T-parameters	$V_1, I_1$	$V_2, I_2$	$V_1 = A V_2 - B I_2$ $I_1 = C V_2 - D I_2$
4) Inverse T-parameters	$V_2, I_2$	$V_1, I_1$	$V_2 = A' V_1 - B' I_1$ $I_2 = C' V_1 - D' I_1$
5) H-parameters	$V_1, I_2$	$I_1, V_2$	$V_1 = h_{11} I_1 + h_{12} V_2$ $I_2 = h_{21} I_1 + h_{22} V_2$
6) Inverse H-parameters	$I_1, V_2$	$V_1, I_2$	$I_1 = g_{11} V_1 + g_{12} V_2$ $V_2 = g_{21} V_1 + g_{22} I_2$

## \* TABLE - 2

⇒ Conditions for Passive Networks and Electrical Symmetry.

Parameter	Condition for Passive Ntk.	Condition for Electrical Symmetry
Z	$Z_{12} = Z_{21}$	$Z_{11} = Z_{22}$
Y	$Y_{12} = Y_{21}$	$Y_{11} = Y_{22}$
T	$\Delta T = AD - BC = 1$	$A = D$
$T^{-1}$	$\Delta T^{-1} = A'D' - B'C' = 1$	$A' = D'$
H	$h_{12} = -h_{21}$	$\Delta h = h_{11} h_{22} - h_{21} h_{12} = 1$
$H^{-1}$	$g_{12} = -g_{21}$	$\Delta g = g_{11} g_{22} - g_{21} g_{12} = 1$




\*TABLE - 3 : PARAMETER CONVERSION TABLE

	[Z]		[Y]		[T]		[T']		[H]		[G]	
[Z]	$z_{11}$	$z_{12}$	$\frac{y_{22}}{\Delta Y}$	$-\frac{y_{12}}{\Delta Y}$	$\frac{A}{C}$	$\frac{\Delta T}{C}$	$\frac{D'}{C'}$	$\frac{1}{C'}$	$\frac{\Delta H}{H_2}$	$\frac{H_{12}}{H_{22}}$	$\frac{1}{G_{11}}$	$-\frac{G_{12}}{G_{11}}$
	$z_{21}$	$z_{22}$	$-\frac{y_{21}}{\Delta Y}$	$\frac{y_{11}}{\Delta Y}$	$\frac{1}{C}$	$\frac{D}{C}$	$\frac{\Delta T'}{C'}$	$\frac{A'}{C'}$	$-\frac{H_{22}}{H_{22}}$	$\frac{1}{H_{22}}$	$\frac{G_{21}}{G_{11}}$	$\frac{\Delta G}{G_{11}}$
[Y]	$\frac{z_{22}}{\Delta Z}$	$-\frac{z_{12}}{\Delta Z}$	$y_{11}$	$y_{12}$	$\frac{D}{B}$	$\frac{\Delta T}{B}$	$\frac{A'}{B'}$	$-\frac{1}{B'}$	$\frac{1}{H_{11}}$	$-\frac{H_{12}}{H_{11}}$	$\frac{\Delta G}{G_{22}}$	$\frac{G_{12}}{G_{22}}$
	$-\frac{z_{21}}{\Delta Z}$	$\frac{z_{11}}{\Delta Z}$	$y_{21}$	$y_{22}$	$-\frac{1}{B}$	$\frac{A}{B}$	$-\frac{\Delta T'}{B'}$	$\frac{D'}{B'}$	$\frac{H_{21}}{H_{11}}$	$\frac{\Delta H}{H_{11}}$	$-\frac{G_{21}}{G_{22}}$	$\frac{1}{G_{22}}$
[T]	$\frac{z_{11}}{z_{21}}$	$\frac{\Delta Z}{z_{21}}$	$-\frac{y_{22}}{y_{21}}$	$-\frac{1}{y_{21}}$	A	B	$\frac{D'}{\Delta T'}$	$\frac{B'}{\Delta T'}$	$-\frac{\Delta H}{H_{21}}$	$-\frac{H_{11}}{H_{21}}$	$\frac{1}{G_{21}}$	$\frac{G_{22}}{G_{21}}$
	$\frac{1}{z_{21}}$	$\frac{z_{22}}{z_{21}}$	$-\frac{\Delta Y}{y_{21}}$	$-\frac{y_{11}}{y_{21}}$	C	D	$\frac{C'}{\Delta T'}$	$\frac{A'}{\Delta T'}$	$-\frac{H_{22}}{H_{21}}$	$-\frac{1}{H_{21}}$	$\frac{G_{11}}{G_{21}}$	$\frac{\Delta G}{G_{21}}$
[T']	$\frac{z_{22}}{z_{12}}$	$\frac{\Delta Z}{z_{12}}$	$-\frac{y_{11}}{y_{12}}$	$-\frac{1}{y_{12}}$	$\frac{D}{\Delta T}$	$\frac{B}{\Delta T}$	A'	B'	$\frac{1}{H_{12}}$	$\frac{H_{11}}{H_{12}}$	$-\frac{\Delta G}{G_{12}}$	$-\frac{G_{22}}{G_{12}}$
	$\frac{1}{z_{12}}$	$\frac{z_{11}}{z_{12}}$	$-\frac{\Delta Y}{y_{12}}$	$-\frac{y_{22}}{y_{12}}$	$\frac{C}{\Delta T}$	$\frac{A}{\Delta T}$	C'	D'	$\frac{H_{22}}{H_{12}}$	$\frac{\Delta H}{H_{12}}$	$-\frac{G_{11}}{G_{12}}$	$\frac{1}{G_{12}}$
[H]	$\frac{\Delta Z}{z_{22}}$	$\frac{z_{12}}{z_{22}}$	$\frac{1}{y_{11}}$	$-\frac{y_{12}}{y_{11}}$	$\frac{B}{D}$	$\frac{\Delta T}{D}$	$\frac{B'}{A'}$	$\frac{1}{A'}$	$H_{11}$	$H_{12}$	$\frac{G_{22}}{\Delta G}$	$\frac{G_{12}}{\Delta G}$
	$-\frac{z_{21}}{z_{22}}$	$\frac{1}{z_{22}}$	$\frac{y_{21}}{y_{11}}$	$\frac{\Delta Y}{y_{11}}$	$-\frac{1}{D}$	$\frac{C}{D}$	$-\frac{\Delta T'}{A'}$	$\frac{C'}{A'}$	$H_{21}$	$H_{22}$	$-\frac{G_{21}}{\Delta G}$	$\frac{G_{11}}{\Delta G}$
[G]	$\frac{1}{z_{11}}$	$-\frac{z_{12}}{z_{11}}$	$\frac{\Delta Y}{y_{22}}$	$\frac{y_{12}}{y_{22}}$	$\frac{C}{A}$	$-\frac{\Delta T}{A}$	$\frac{C'}{D'}$	$-\frac{1}{D'}$	$\frac{H_{22}}{\Delta H}$	$-\frac{H_{12}}{\Delta H}$	$G_{11}$	$G_{12}$
	$\frac{z_{21}}{z_{11}}$	$\frac{\Delta Z}{z_{11}}$	$-\frac{y_{21}}{y_{22}}$	$\frac{1}{y_{22}}$	$\frac{1}{A}$	$\frac{B}{A}$	$\frac{\Delta T'}{D'}$	$\frac{B'}{D'}$	$-\frac{H_{21}}{\Delta H}$	$\frac{H_{11}}{\Delta H}$	$G_{21}$	$G_{22}$


## \* Important points.

### ① 'T' Equivalent of Z-parameters.

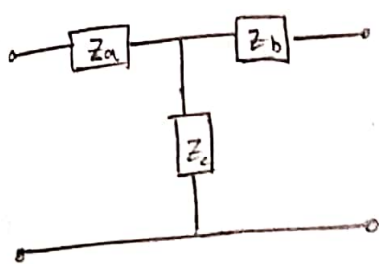


$$\begin{aligned} Z_{11} &= Z_a + Z_c \\ Z_{22} &= Z_b + Z_c \\ Z_{12} &= Z_c \\ Z_{21} &= Z_c \end{aligned}$$

### ② 'Π' Equivalent of Y-parameters

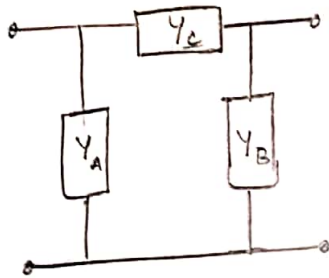

$$\begin{aligned} Y_{11} &= Y_A + Y_C \\ Y_{22} &= Y_B + Y_C \\ Y_{12} &= -Y_C \\ Y_{21} &= -Y_C \end{aligned}$$


### ③ Cascade connected two networks

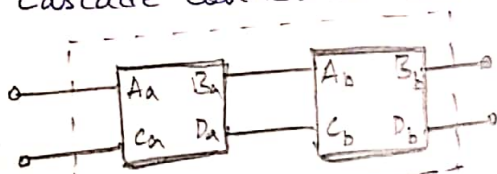

Equivalent parameter matrix

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$


### ④ Parallel connected two networks

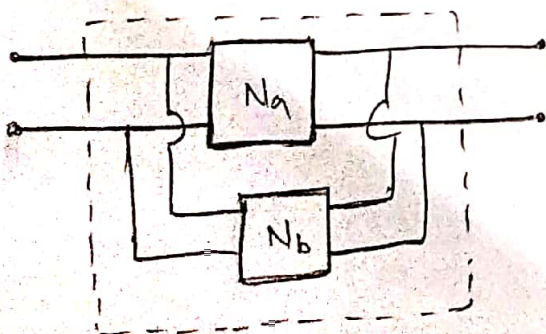

Equivalent parameter matrix

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_{11a} + Y_{11b} & Y_{12a} + Y_{12b} \\ Y_{21a} + Y_{21b} & Y_{22a} + Y_{22b} \end{bmatrix}$$


### ⑤ Series connected two networks

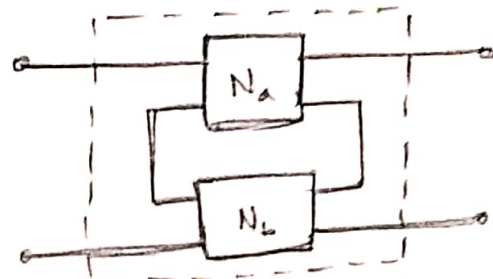

Equivalent parameter matrix

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{21a} + Z_{21b} \\ Z_{12a} + Z_{12b} & Z_{22a} + Z_{22b} \end{bmatrix}$$
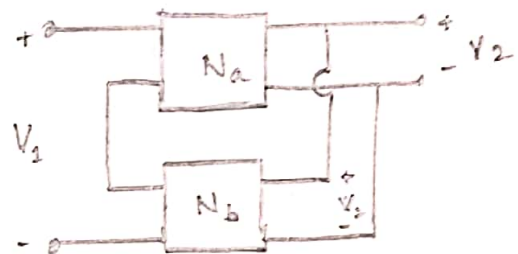
### ⑥ Input series and output parallel two networks.



Equivalent parameter matrix

$$[H] = [H_a] + [H_b]$$

i.e

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} + \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix}$$