Shift Registers

```
To design (a) SISO (b) SIPO (c) PIPO (d) PISO using Verilog
```

```
(i) SISO
         module siso(din ,clk ,reset ,dout);
         output dout;
         input din;
         input clk;
         input reset;
         reg [3:0]s;
         always @ (posedge clk)
         begin
         if(reset)
          s \le 4'b0;
         else
         begin
          s[3] \ll din;
          s[2] \le s[3];
          s[1] \le s[2];
          s[0] \le s[1];
          end
         end
         assign dout = s[0];
```

endmodule

Testbench

```
module tb_siso();
wire dout;
reg din, reset, clk;
siso dut(din ,clk ,reset ,dout);
initial begin
reset = 0; clk = 0; din = 0;
#5 \text{ reset} = 1;
#10 reset =0;
#10 din = 1;
#20 din = 0;
#20 din = 1;
#20 din = 0;
#40 $stop;
end
always #10 clk = ! clk;
endmodule
```



(ii)SIPO


```
module sipo ( din ,clk ,reset ,dout );
             output [3:0] dout;
             input din;
             input clk;
             input reset;
             reg [3:0]s;
             always @ (posedge clk)
             begin if (reset)
             s <= 0;
             else begin
             s[3] \le din;
             s[2] \le s[3];
             s[1] \le s[2];
             s[0] \le s[1];
             end
             end
             assign dout = s;
             endmodule
Testbench
           module tb_sipo;
            reg din,clk,reset;
           wire [3:0] dout;
           sipo uut(din, clk, reset,dout);
           initial
           begin
           reset=0;
           clk=0;
           din=0;
           #20 \text{ reset} = 1;
           #20 reset=0;
           #20 din=1;
           #20 din=0;
           #20 din=1;
           #20 din=0;
           #20 din=1;
           #20 $finish;
           always #10 \text{ clk} = \sim \text{clk};
           endmodule
```



```
(iii)PIPO
```

Testbench

```
module PIPO (din,clk,reset,dout);
output [3:0] dout;
reg [3:0] dout;
input [3:0] din;
input clk, reset;
always @ (posedge clk)
begin if (reset)
dout <= 0;
else
dout <= din;
end
endmodule
 module tb_pipo;
 reg [3:0] din;
 reg clk,reset;
 wire [3:0] dout;
 pipo uut(din, clk, reset,dout);
 initial
 begin
 reset=0;
 clk=0;
 din=4'b0000;
 #20 \text{ reset} = 1;
 #20 reset=0;
 #60 din=4'b1001;
 #60 din=4'b1010;
 #60 din=4'b1111;
 #60 $finish;
 always #10 \text{ clk} = \sim \text{clk};
 endmodule
```

 

```
(iv) PISO
       module piso (din,clk,reset,load,dout);
       output dout;
       reg dout;
       input [3:0] din;
       input load, reset, clk;
       reg [3:0]temp;
       always @ (posedge clk)
       begin if (reset)
       temp <= 1;
       else if (load)
       temp <= din;
       else
       begin
       dout <= temp[3];
       temp <= \{temp[2:0], 1'b0\};
       end
       end
       endmodule
Testbench
          module tb_piso;
          reg [3:0] din;
          reg clk,reset,load;
          wire dout;
          piso uut(din, clk, reset,loaddout);
          initial
          begin
          reset=0;
          load=0;
          clk=0;
```

din=4'b0000; #20 reset =1;

```
#20 reset=0;

#20 load =1;

#20 load =0;

#60 din=4'b1001;

#60 din=4'b1010;

#60 sfinish;

end

always #10 clk = ~ clk;

endmodule
```

Simulation Waveform

Report Utilization Summary